

# EE 220 CIRCUITS I

## Lecture 23

11/23/2022

$$1k(180f + 20f)$$


$$20ps$$

$$1k \cdot \frac{20f \cdot 180f}{20f + 180f} C$$


$$\frac{3600}{200}$$

$$1k \cdot 18ff$$


18ps

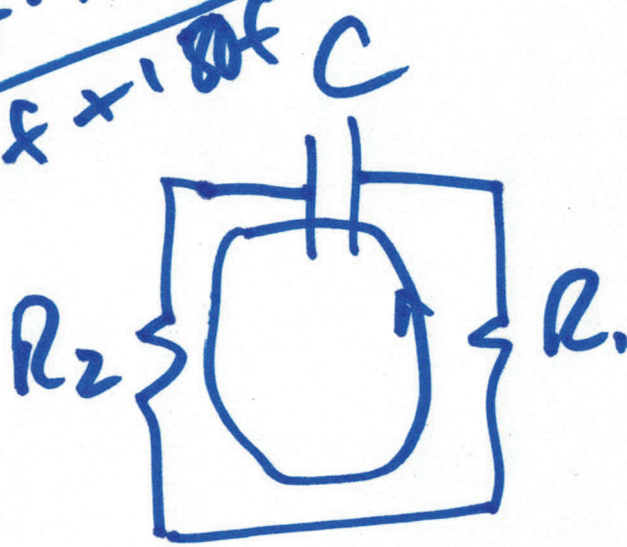

$$\tau = (R_1 + R_2)C$$

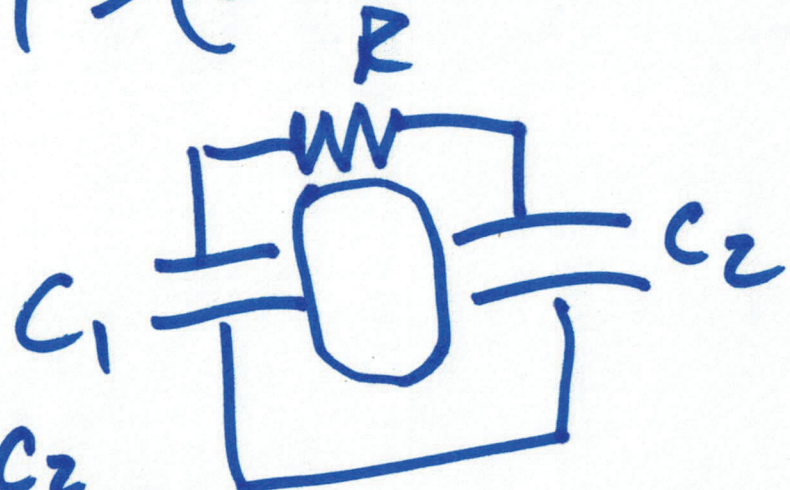

$$\frac{C_1 C_2}{C_1 + C_2}$$

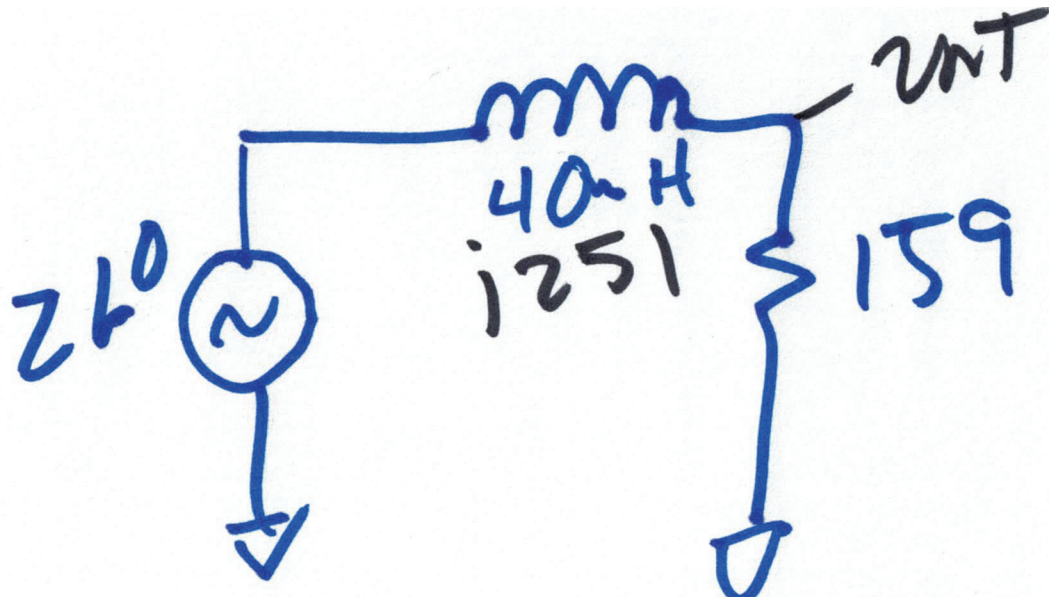

$$Z_C = \frac{1}{j\omega C}$$

$$Z_L = j \cdot \omega \cdot L$$

$$= j 2\pi f L$$

$$j \cdot 2\pi \cdot \underbrace{10^3}_{1 \text{ kHz}} \cdot \underbrace{40 \times 10^{-3}}_{40 \text{ mH}} = \frac{j \cdot 251}{159 + j0}$$

$$v_{out} = 260 \cdot \frac{159 \angle 0}{159 + j251}$$

$$v_{out} = \frac{318 \angle 0}{297.1 \angle 57.65^\circ}$$

2)

$$V_{out} = \frac{318}{297.1} \angle -57.65 = 1.07 \angle -57.65$$



$$V_{out} = 1.07 \sin(2\pi \cdot 10^3 \cdot t - 57.65)$$

$$V_{in} = 2 \sin(2\pi \cdot 10^3 \cdot t)$$

$$\theta = \frac{t_d}{f} \cdot 360 = 57.65$$


$$\frac{1}{f} = 10^{-3} t_d = \frac{57.65 \cdot 10^{-3}}{360}$$

$$t_d = 1604 \mu s$$

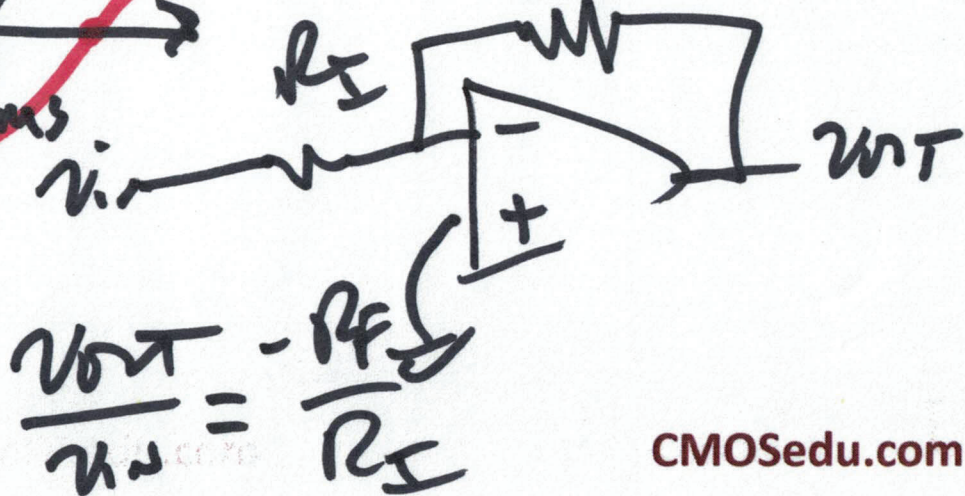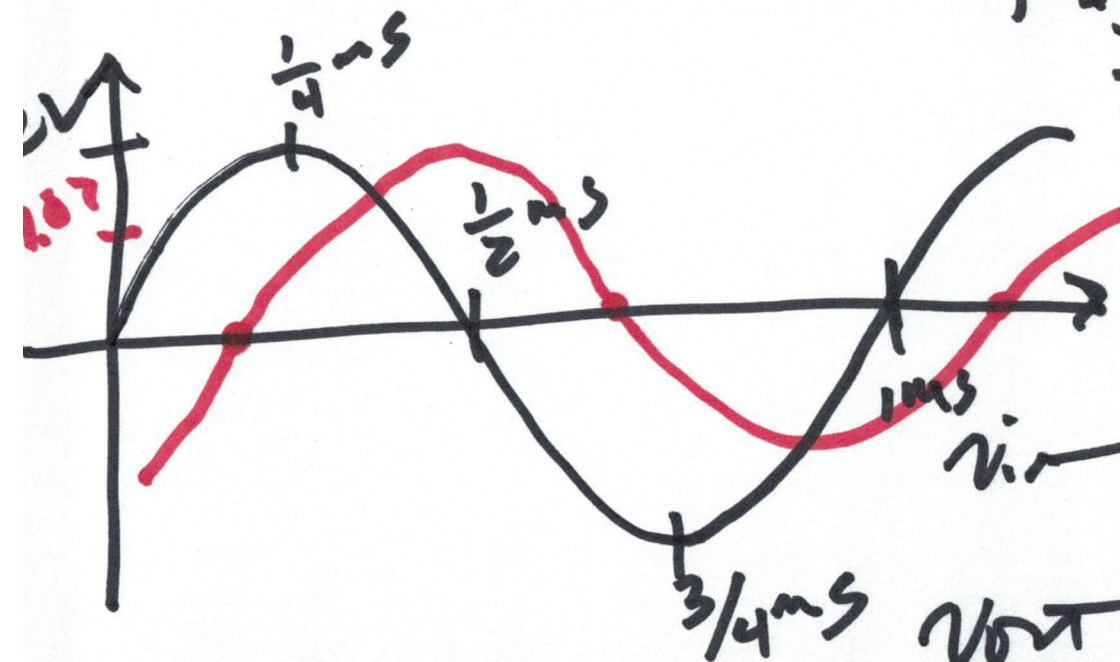

$$\frac{V_{out}}{V_{in}} = -\frac{R_F}{R_I}$$

3)

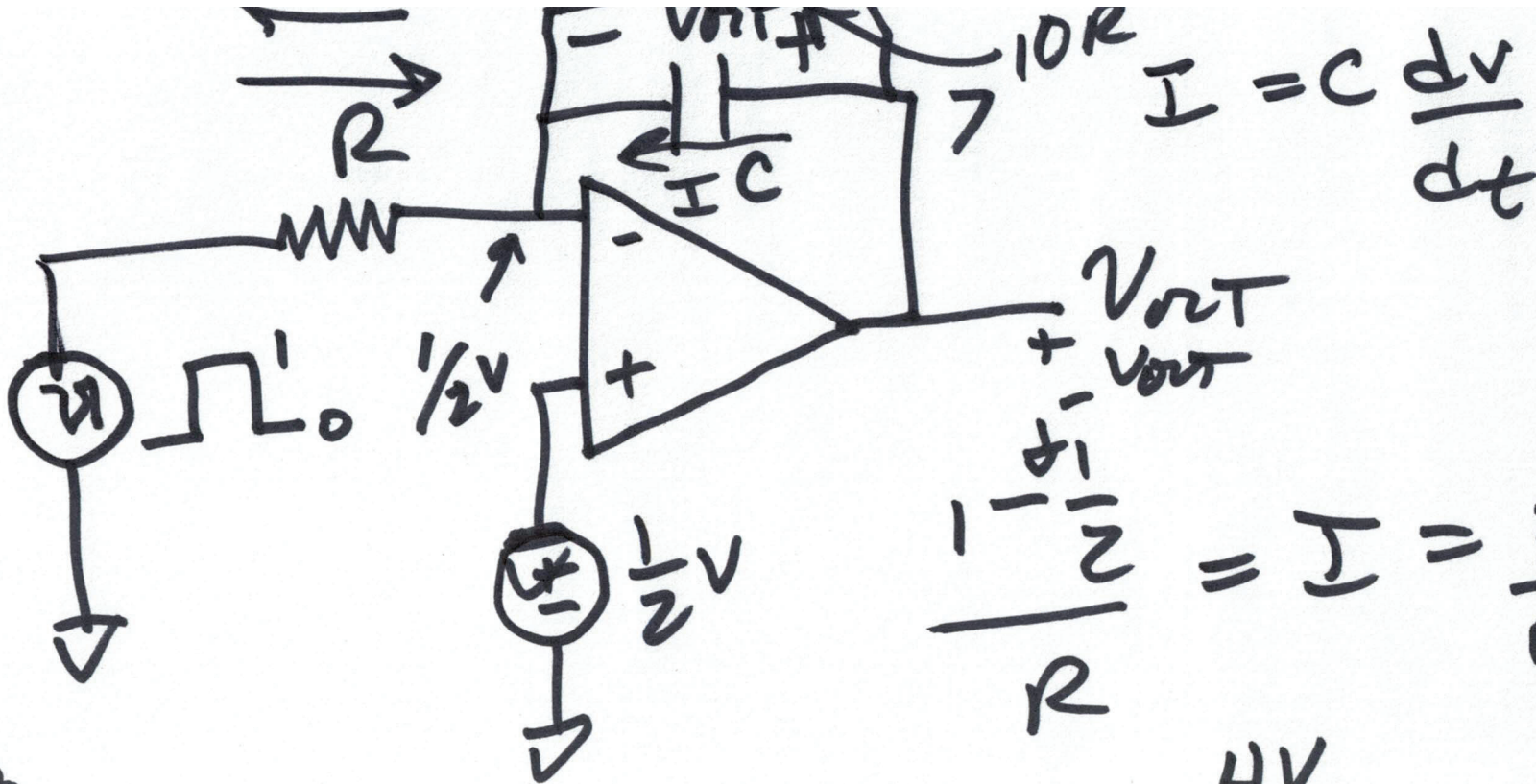


10 kHz  
100ns

$$\frac{1}{2} = C \cdot \frac{dv}{dt} = C \cdot \frac{4V}{50\mu s}$$

$$RC = \frac{50\mu s}{2.4} = 6.25\mu s$$

$$R = 1k$$

$$C = 6.25\mu F = 6,250nF$$

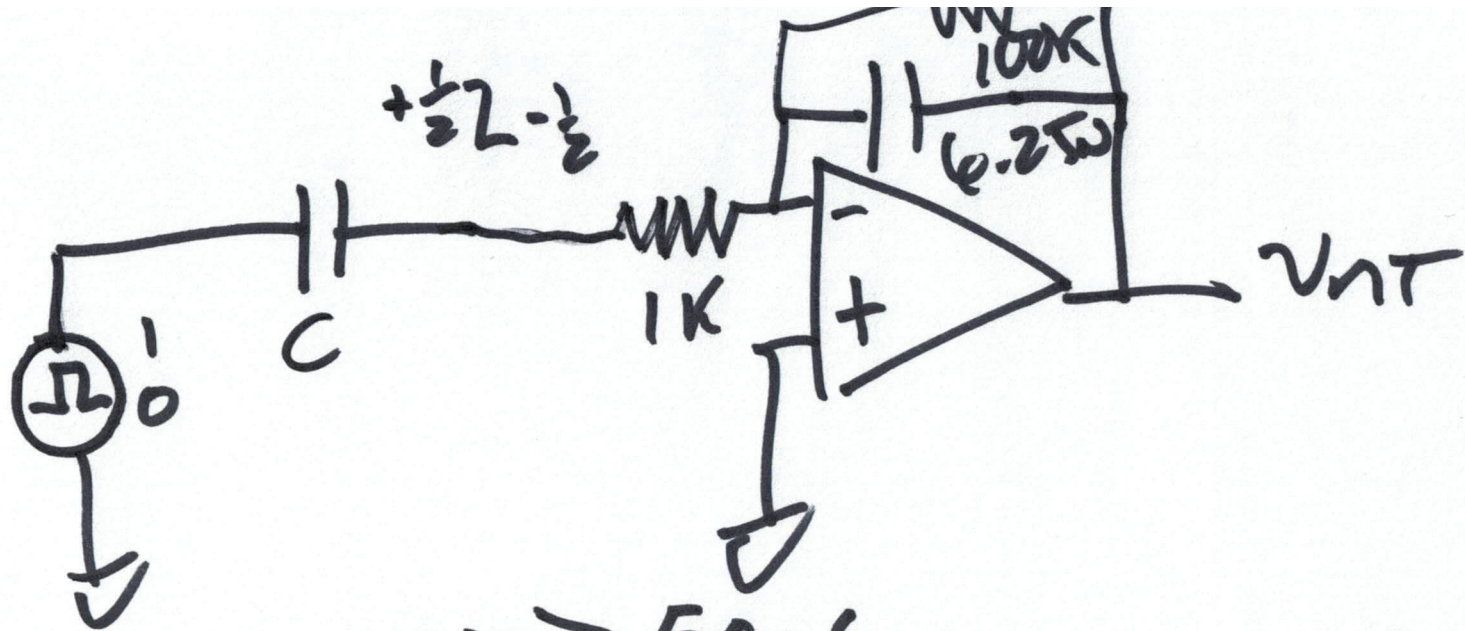


$$C \cdot 1K \gg 50\mu s$$


$$4.74F \cdot 1K$$

$$= 4.7ms$$

# Root Mean Square (RMS)

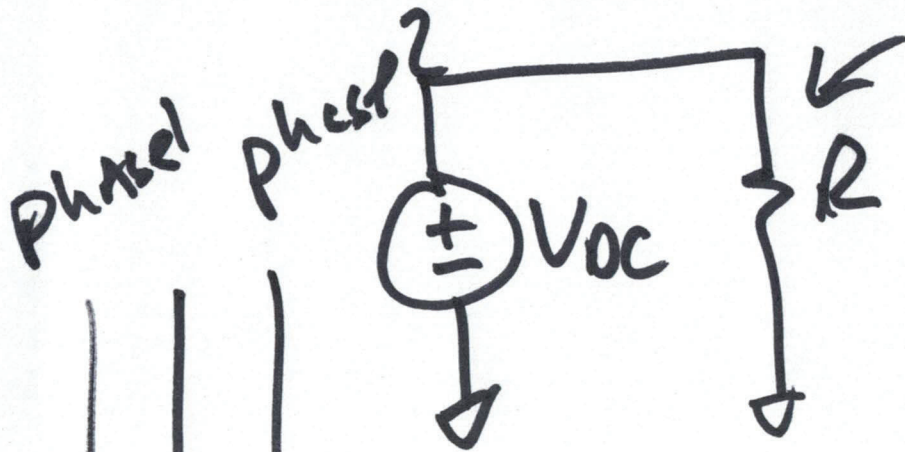

$$P = \frac{V_{OC}^2}{R}$$

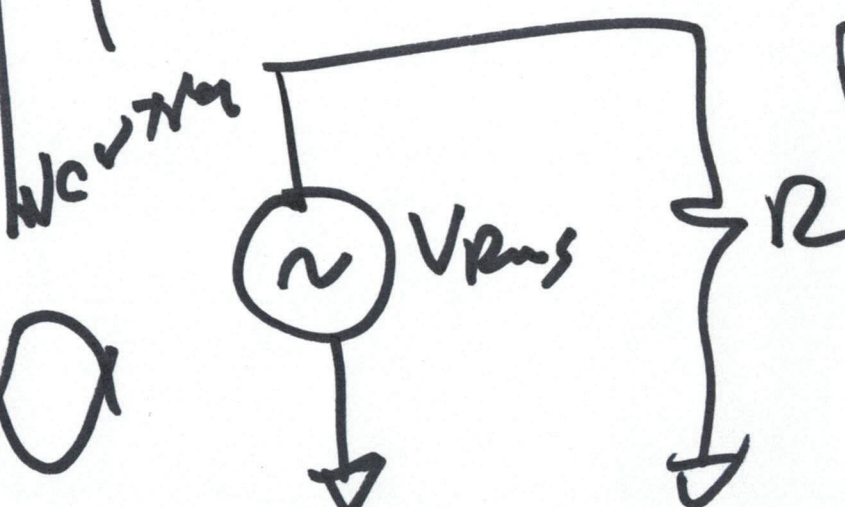


$$P = \frac{V_{RMS}^2}{R}$$


120V RMS

$$V_{RMS} = \frac{V_P}{\sqrt{2}}$$

$$120 \cdot \sqrt{2} = V_P$$

$$V_P = 169.7$$

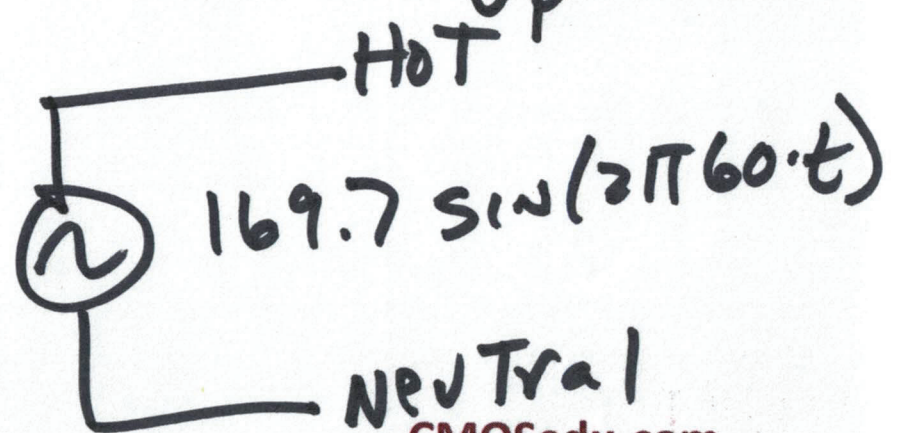

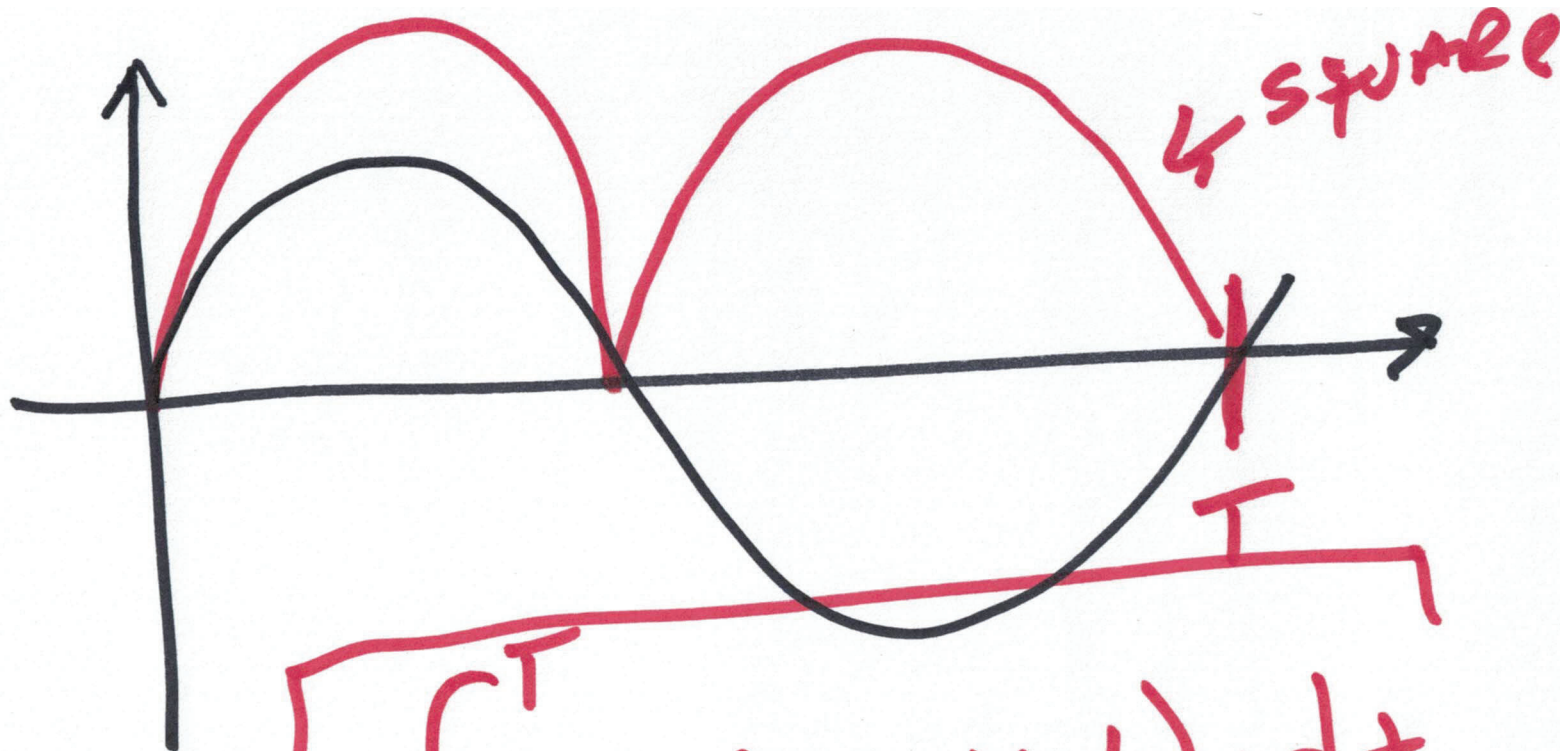

Root

$$\frac{1}{T} \int_0^T V_p^2 \sin^2(2\pi 60 \cdot t) \cdot dt$$

square

mean

$$\sin^2 x = \frac{1 - \cos 2x}{2}$$

RMS

$$\frac{V_p^2}{T} \int_0^T \frac{1 - \cos 2x}{2} \cdot dx$$



$\int dx = x$

$\int_0^T \cos 2x dx$  (with a crossed-out arrow pointing from 0 to T)

$$V_{RMS} = \frac{V_p^2}{T} \left( \int_0^T \frac{1}{2} \cdot dx - \frac{1}{2} \int_0^T \cos 2x dx \right)$$


$$= \frac{V_p^2}{2T} \cdot x \Big|_0^T \Rightarrow \frac{V_p^2}{2}$$

$$\frac{V_p}{\sqrt{2}} = V_{RMS}$$

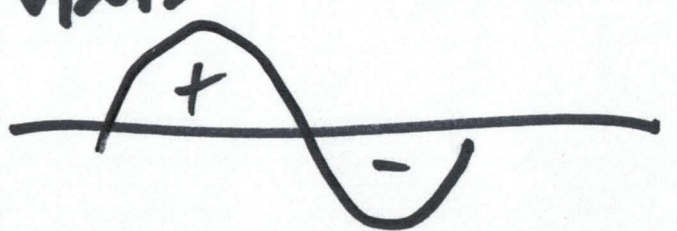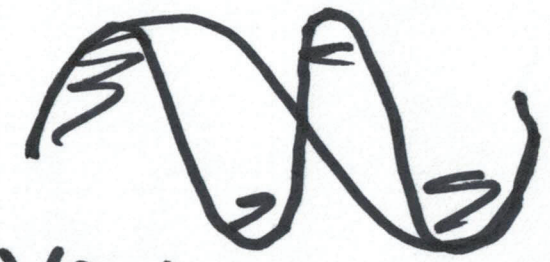

8)



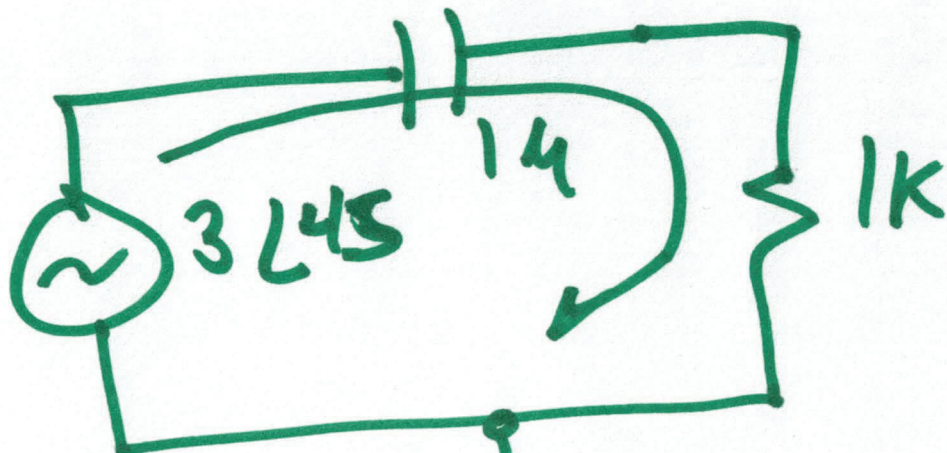

$$f = 1\text{kHz}$$

$$Z_c = \frac{1}{j \cdot 2\pi \cdot 10^3 \cdot 10^{-6}} = -j159$$

$$i = \frac{3245}{10^3 + (-j159)} = \frac{3245}{1012 \angle -9^\circ}$$

$$= 2.96 \text{ mA} \angle 54^\circ$$