
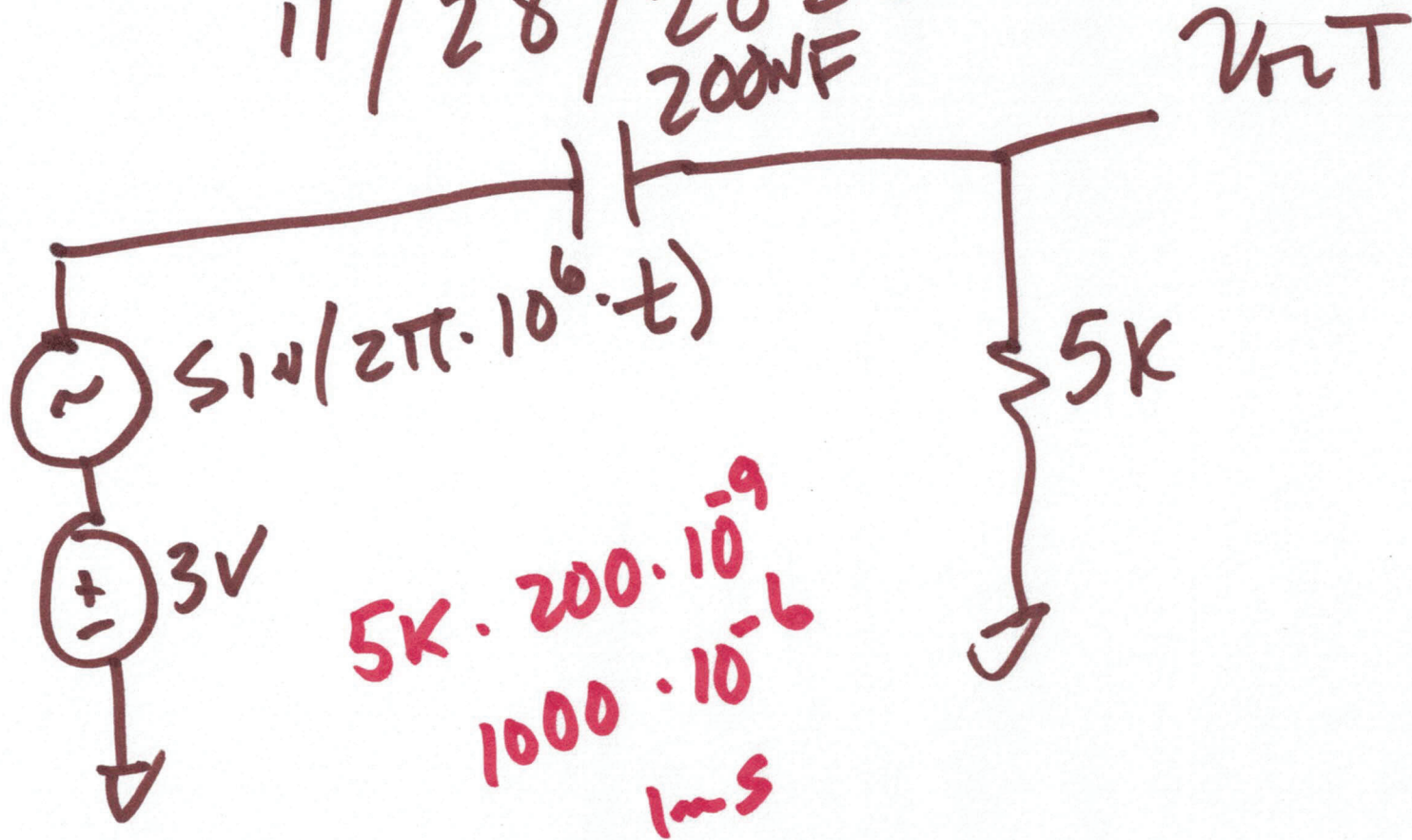


EE 220 CIRCUITS I

Lecture 24

11/28/2022

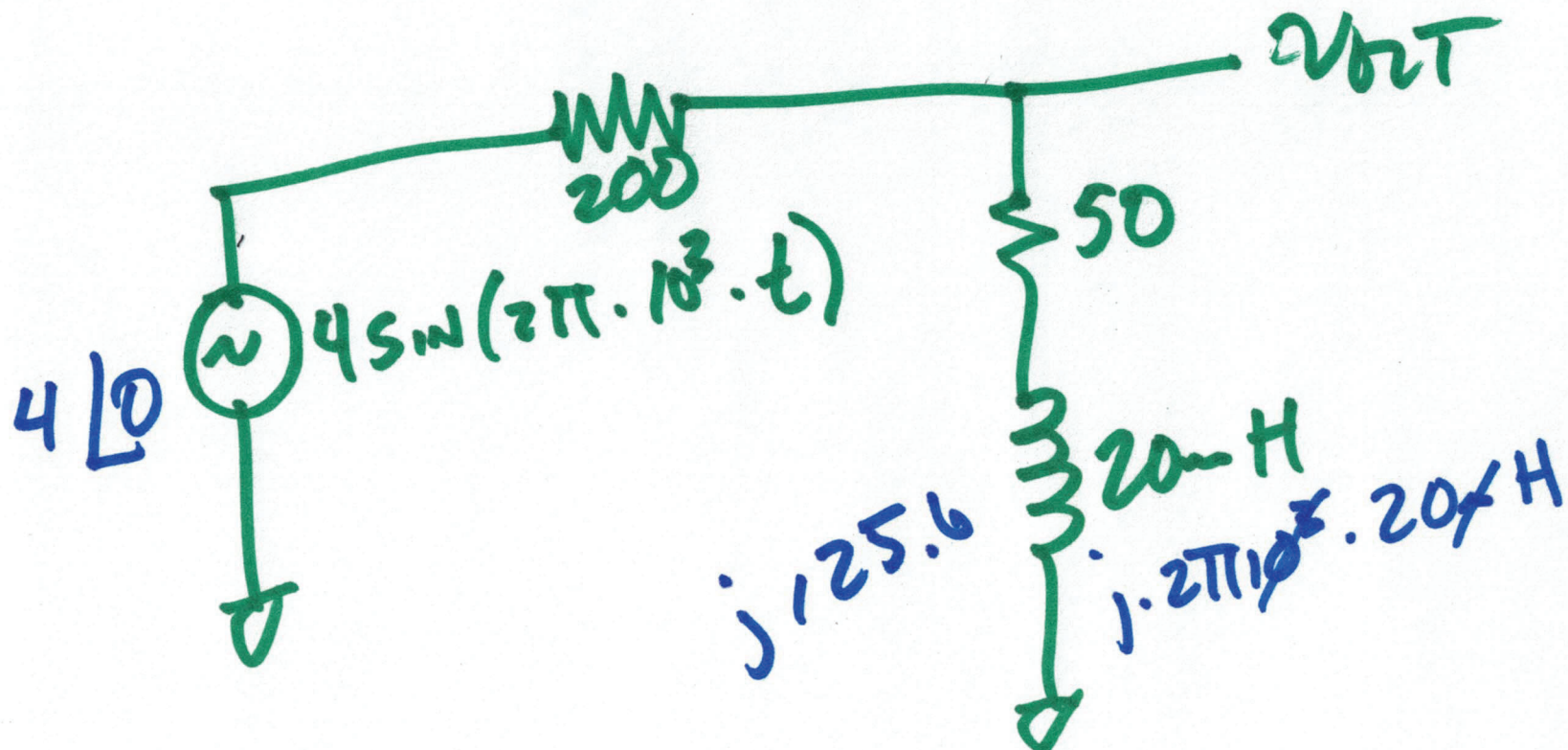




$$\begin{aligned}
 V_{out} &= \frac{50 + j125.6}{200 + 50 + j125.6} \cdot 4 \angle 0 \\
 &= \frac{135 \angle 68.3^\circ}{279.8 \angle 24.7} \cdot 4 \angle 0
 \end{aligned}$$

$$v_{mT} = 1.93 \angle 41.6^\circ \quad f = 10^3 = \frac{1}{10^{-3}} = \frac{1}{T}$$

$$41.6 = \frac{t_d}{1\text{ms}} \cdot 360$$

$$t_d = 115.645 = .116\text{ms}$$

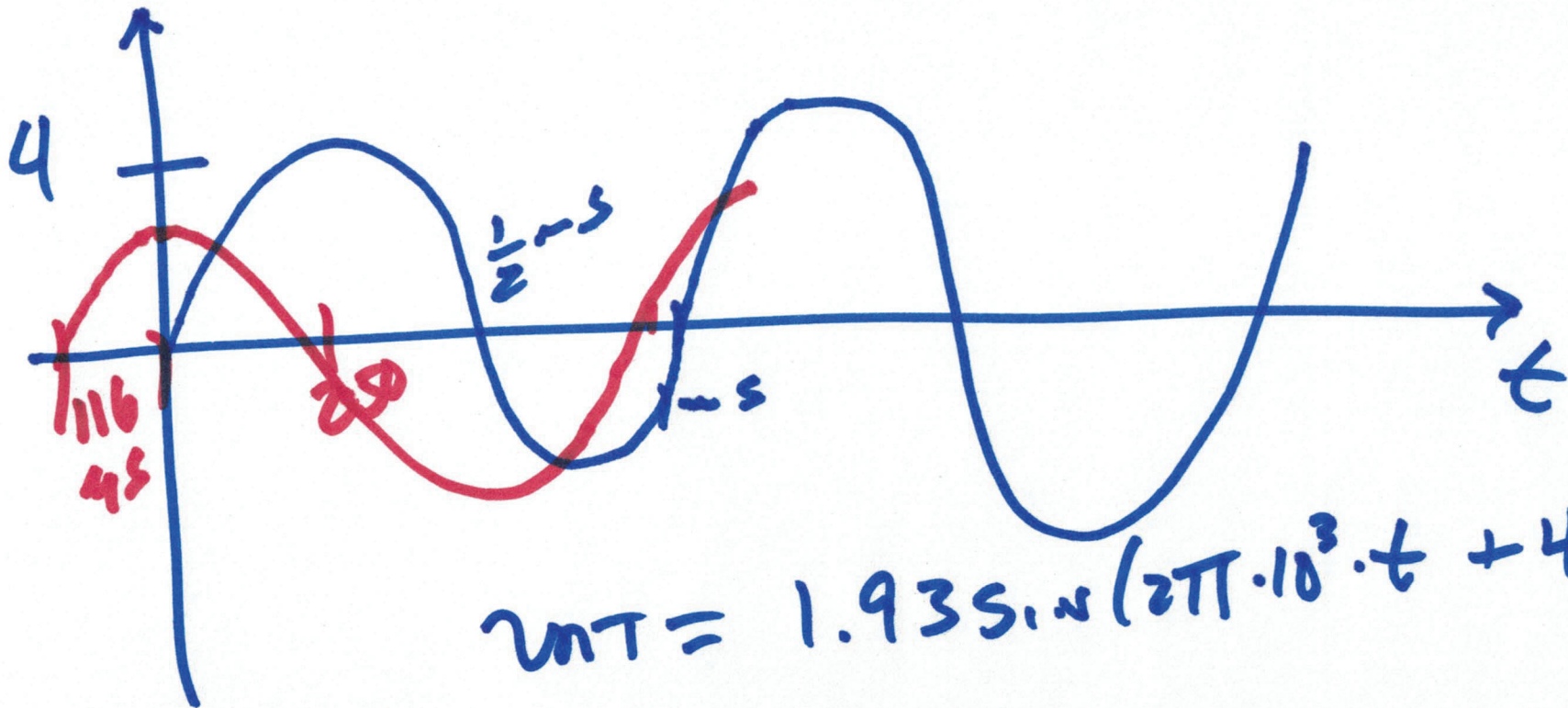


$$v_{mT} = 1.93 \sin(2\pi \cdot 10^3 \cdot t + 41.6)$$

3)

FIRST-ORDER
HAS a single
INDUCTOR OR
CAPACITOR

Second-order
HAVE 1C 1L
2C OR 2L

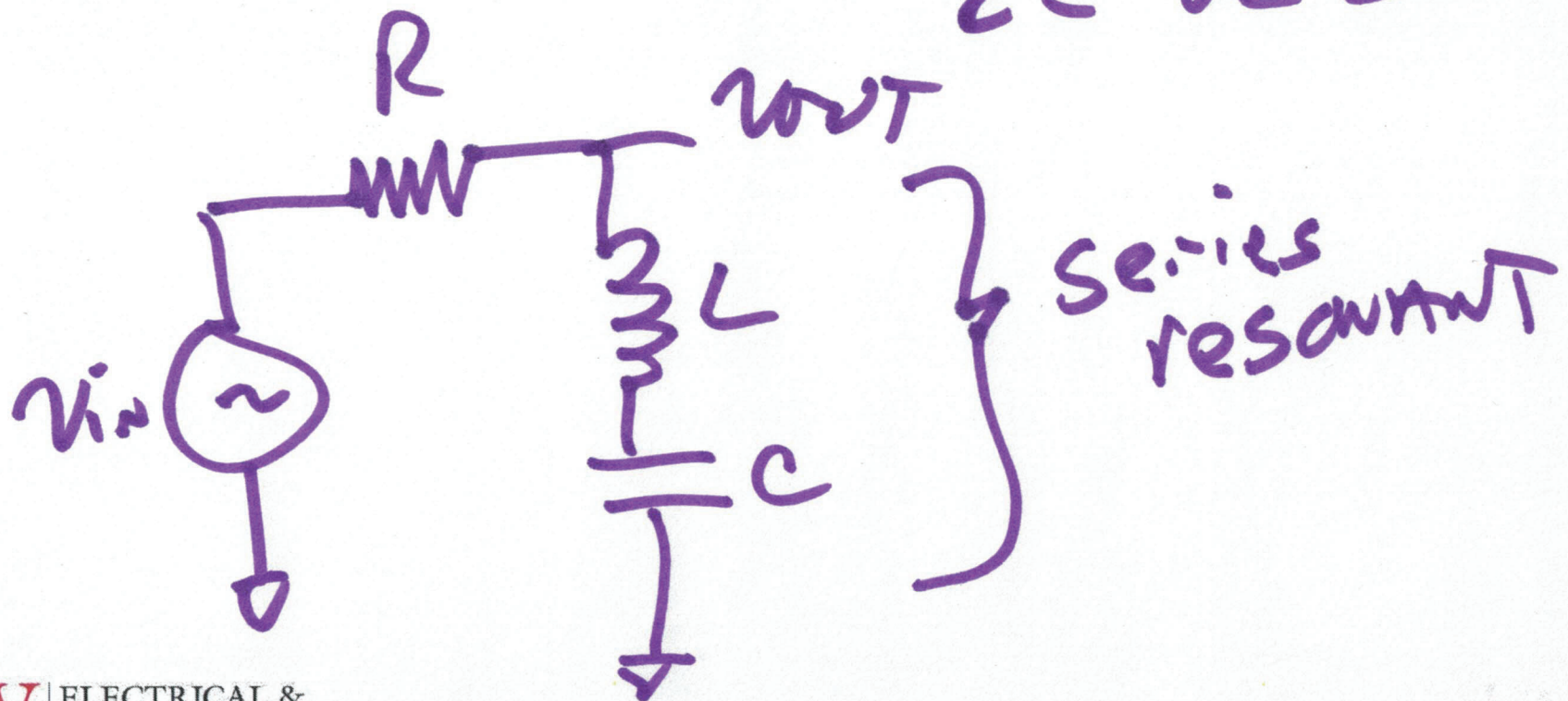

$$V_{out} = V_{in} \cdot \frac{j\omega L + j\omega C}{j\omega L + \frac{1}{j\omega C} + R}$$

transfer
function
↓

$$\frac{V_{out}}{V_{in}} =$$

$$\frac{1 + j\omega L \cdot j\omega C}{j\omega L \cdot j\omega C + 1 + R \cdot j\omega C}$$

$$= \frac{1 + s^2 LC}{s^2 LC + 1 + R \cdot j\omega C}$$

$$s = j\omega = j2\pi f$$

$$\frac{V_{out}}{V_{in}} =$$


$$\frac{1 - \omega^2 LC}{- \omega^2 LC + 1 + Rj\omega C}$$

$$1 + j\omega RC = - \omega^2 LC \text{ parallel}$$

$$1 - \omega^2 LC = 0?$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$f = \frac{1}{2\pi\sqrt{LC}}$$

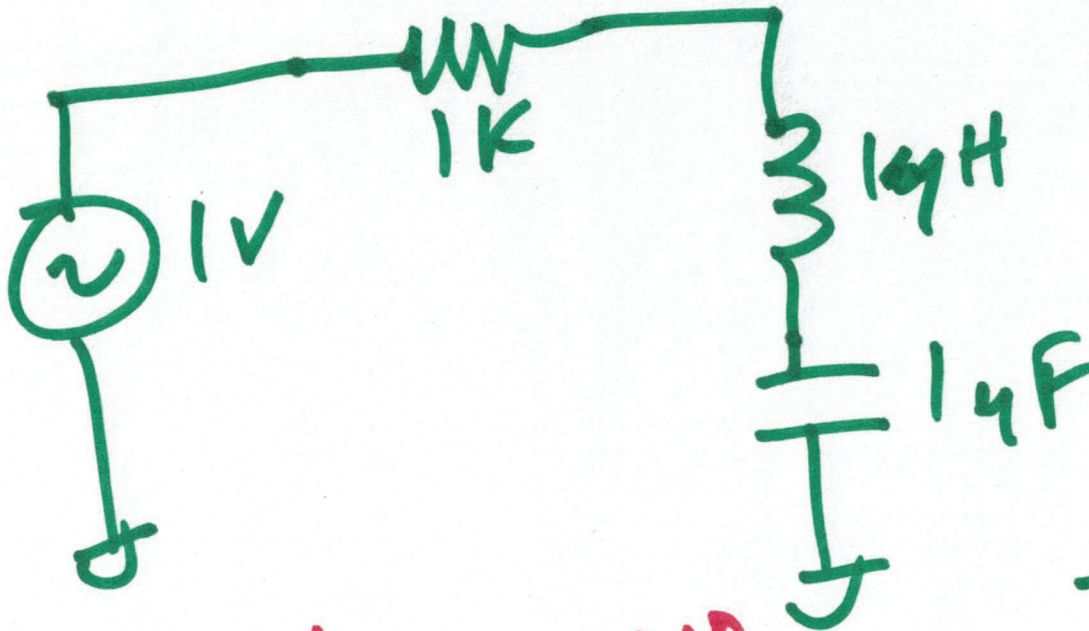

$$f_{Res} = \frac{1}{2\pi \sqrt{10^{-6} \cdot 10^{-6}}}$$

decade →
 octave
 x 2
 ÷ 2

x 10
 ÷ 10

1.23 MHz above
 12.3 MHz
~~123 MHz below~~

$$= \frac{1}{2\pi \cdot 10^{-6}} = 159 \text{ kHz}$$


$$dB = 20 \log \sqrt{v_{out}}$$


$$20 \log 1V = 0 \text{ dB}$$

$$20 \log 10^{-6} = -120 \text{ dB}$$

$$20 \log \frac{1}{10} = -20 \text{ dB}$$

$$20 \log 10 = +20 \text{ dB}$$

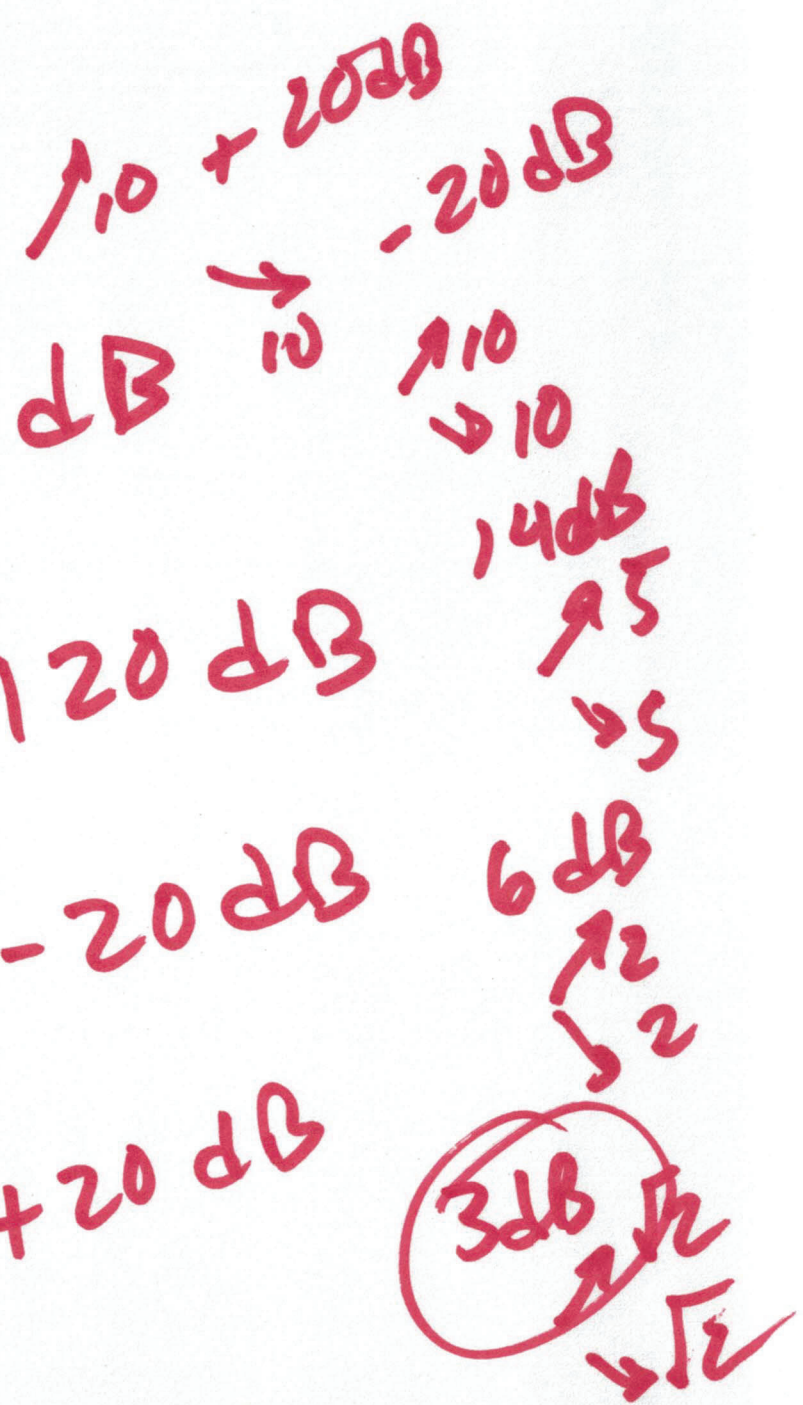

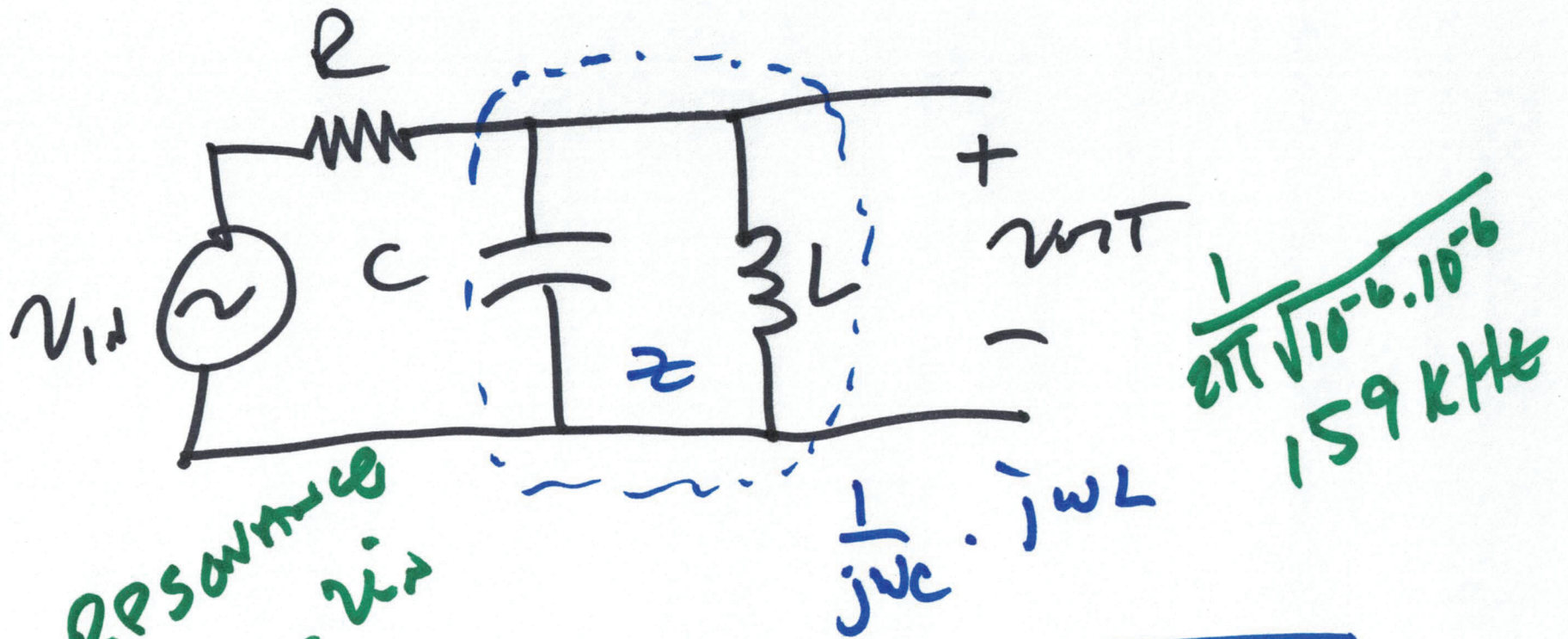

$$Z = \frac{1}{\frac{1}{j\omega C} + j\omega L} \rightarrow 0$$

$$v_{out} = v_{in} \cdot \frac{Z}{R + Z}$$

$$1 + j\omega L \cdot j\omega C = 0$$

$$1 = \omega^2 LC$$

$$\frac{1}{j\omega C} + j\omega L = 0$$

$$f = \frac{1}{2\pi\sqrt{LC}}$$