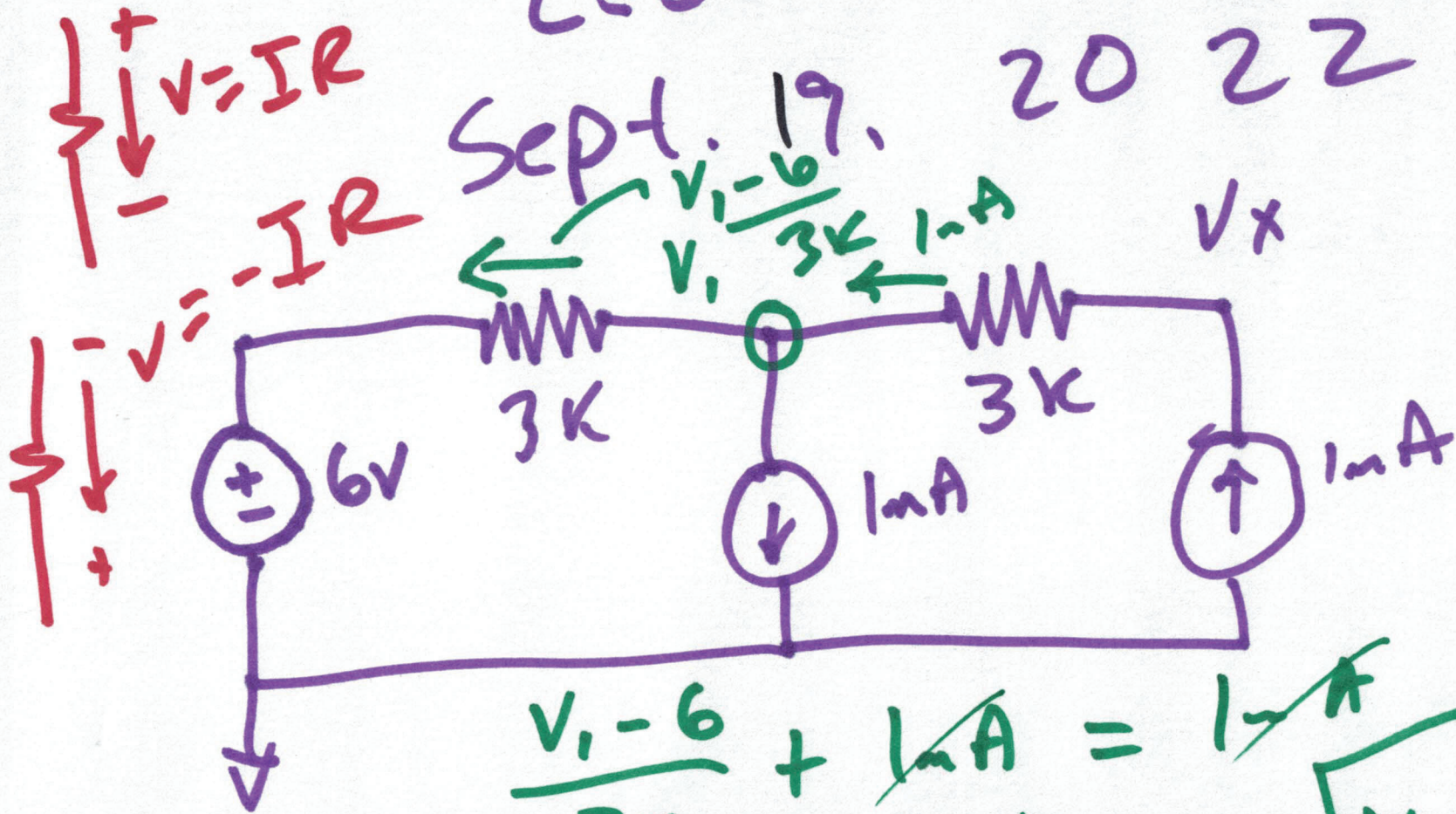


EE 220 circuits I


Lecture 6

Sept. 19, 2022





$$\frac{v_1 - 6}{3k} + 1mA = 1mA$$
$$\frac{v_1 - 6}{3k} = 0$$

$v_1 = 6$

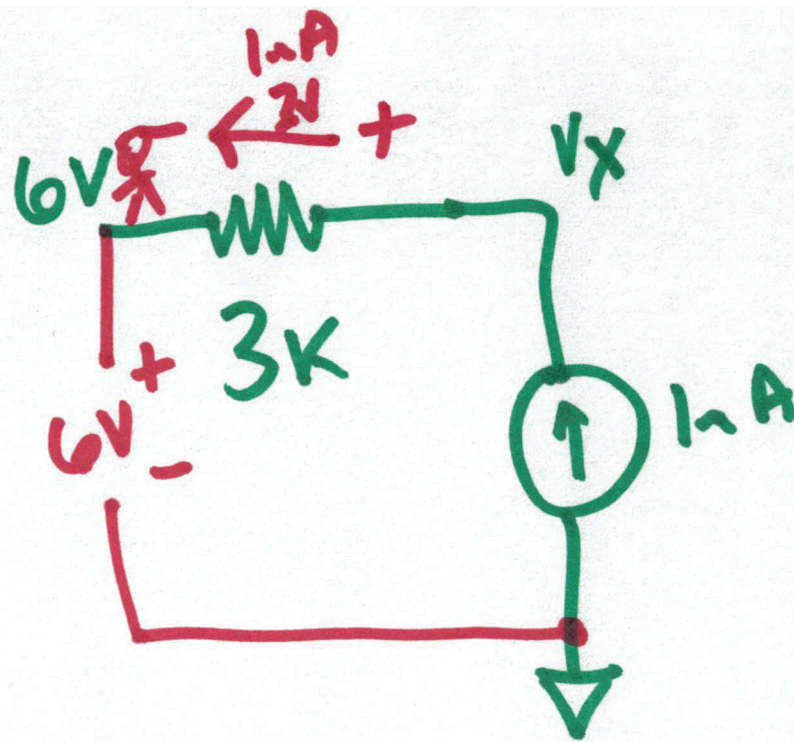


$$6V + 3V = V_x = 9V$$

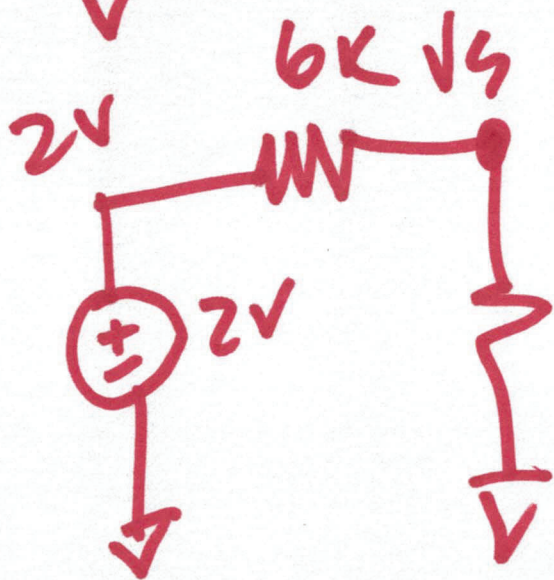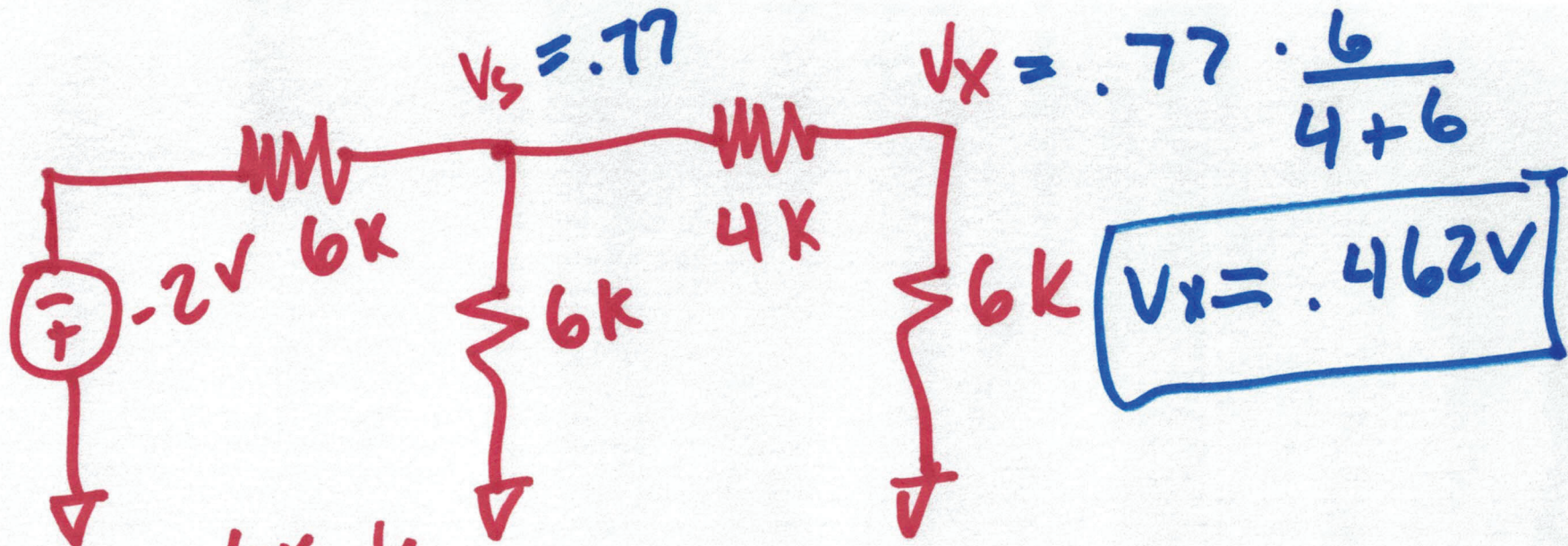

$$6k \parallel 10k = \frac{60}{16} = \frac{15}{4} = 3.75k$$

$$V_s = 2 \cdot \frac{3.75}{6 + 3.75}$$
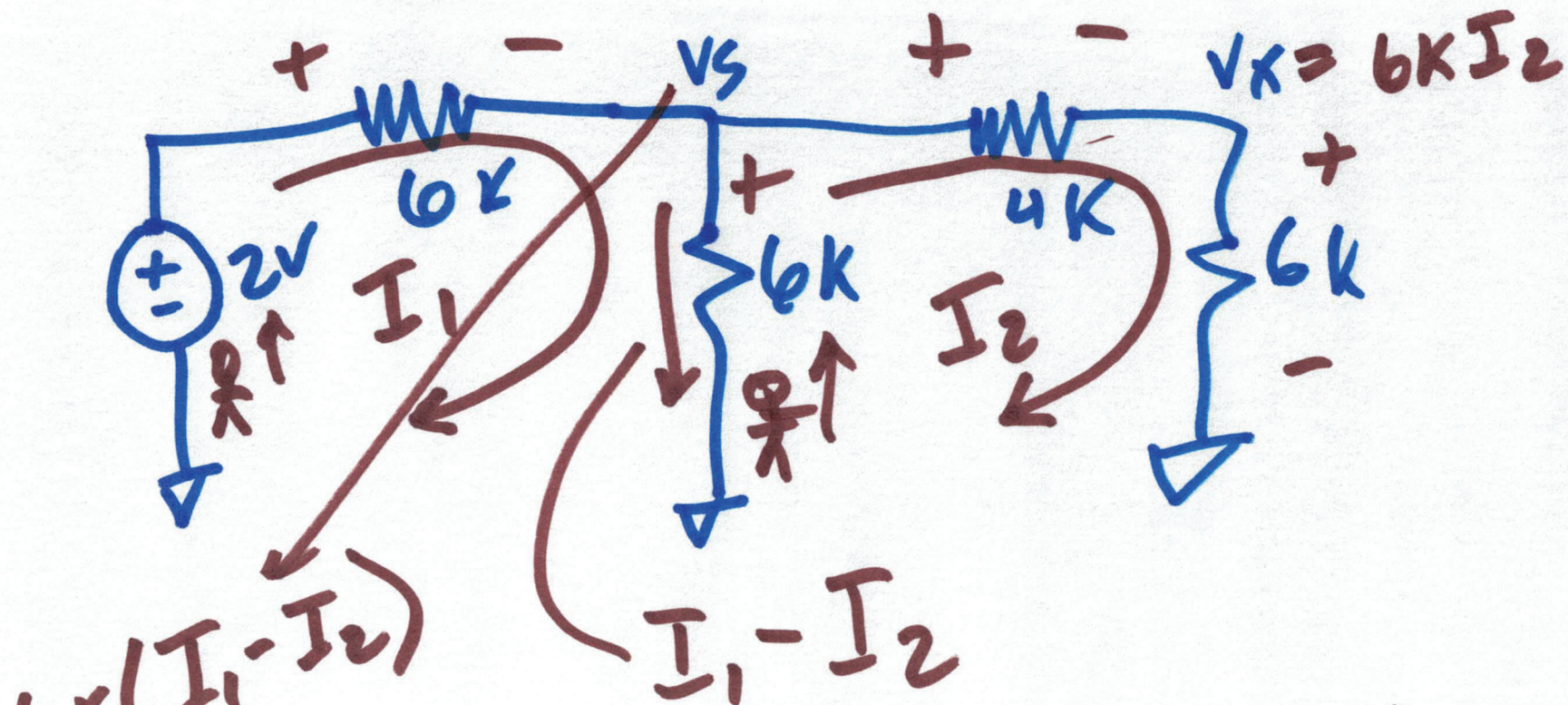
$$= 2 \cdot \frac{3.75}{9.75} = \underline{\underline{.777V}}$$



$$6k(I_1 - I_2) \Rightarrow v_s$$

$$+2 - 6kI_1 - 6k(I_1 - I_2) = 0$$

$$-6kI_2 - 4kI_2 + 6k(I_1 - I_2) = 0$$

$$\frac{1}{3} \text{ mA} - I_1 - I_1 + I_2 = 0$$

$$76.74 \text{ A} = I_2 = 2I_1 - \frac{1}{3} \text{ mA}$$

$$I_2 + \frac{2}{3}I_2 - I_1 + I_2 = 0$$


$$I_2 \left(\frac{8}{3} \right) - I_1 = 0$$

$$\frac{8}{3} \left(2I_1 - \frac{1}{3} \text{ mA} \right) - I_1 = 0$$

$$\frac{16}{3}I_1 - \frac{8}{9} \text{ mA} - I_1 = 0$$


$$\frac{13}{3}I_1 = \frac{8}{9} \text{ mA}$$
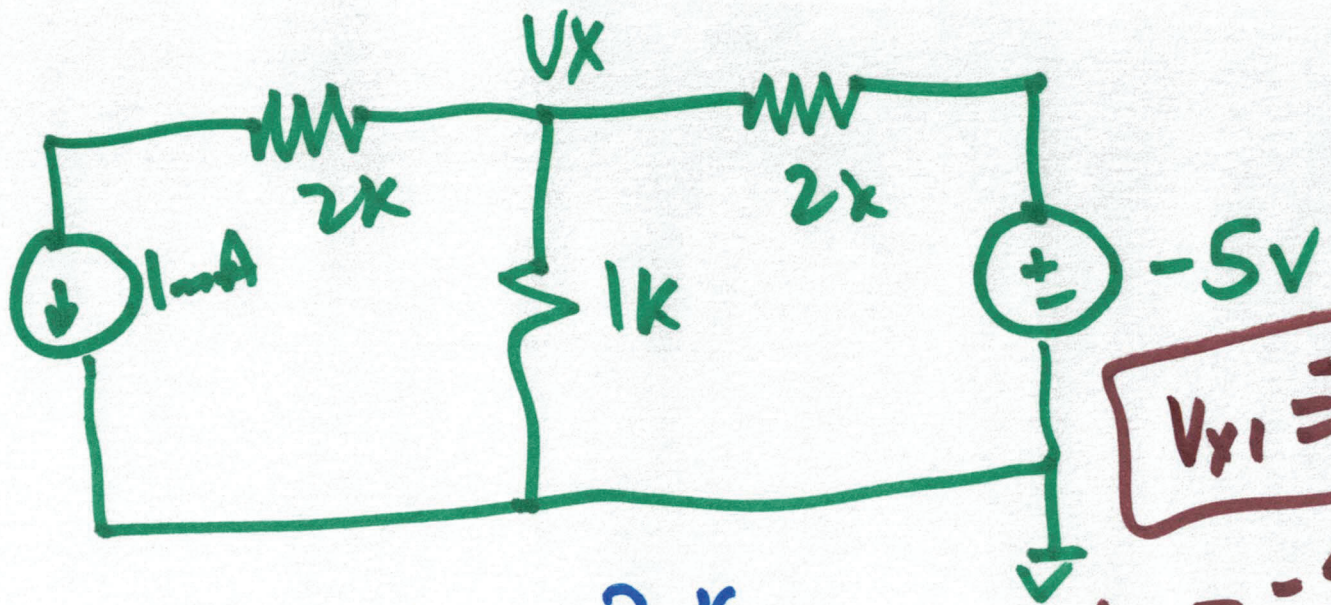
$$I_1 = \frac{24}{117} \text{ mA}$$
$$I_1 = .205 \text{ mA}$$



$$V_{x1} = 1.667V$$



$$V_{x1} = -5 \cdot \frac{1k}{2k + 1k}$$

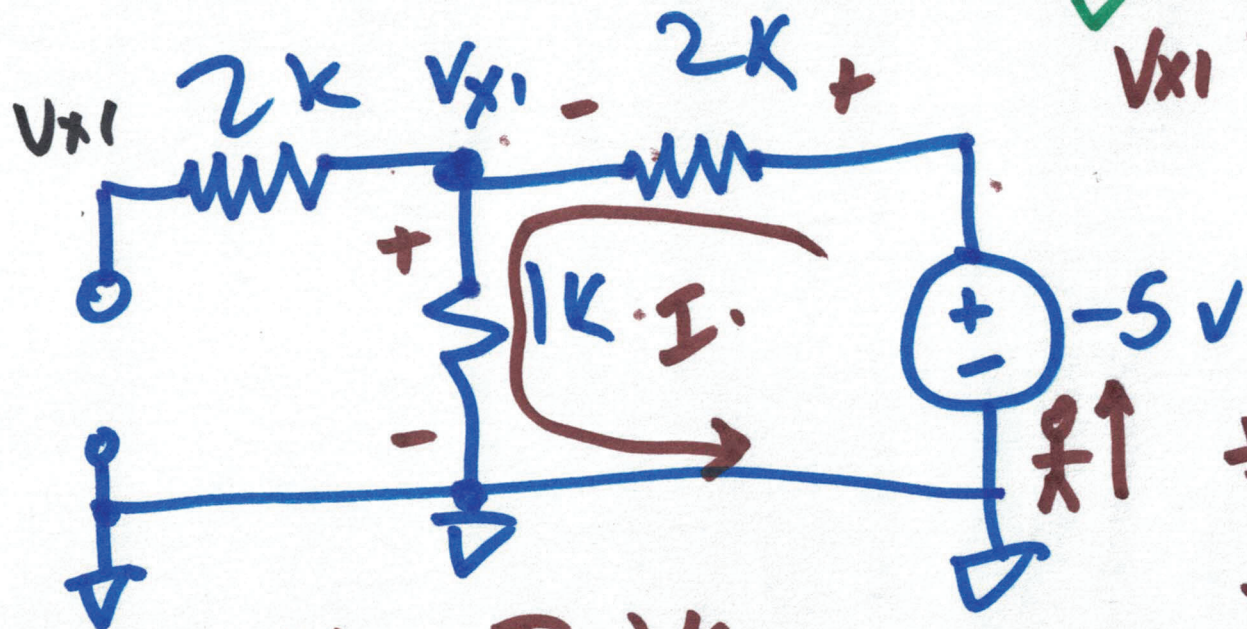

$$V_{x1} = I \cdot 1k$$

$$+(-5V) - 2kI - 1kI = 0$$

$$I = \frac{-5}{2k + 1k}$$

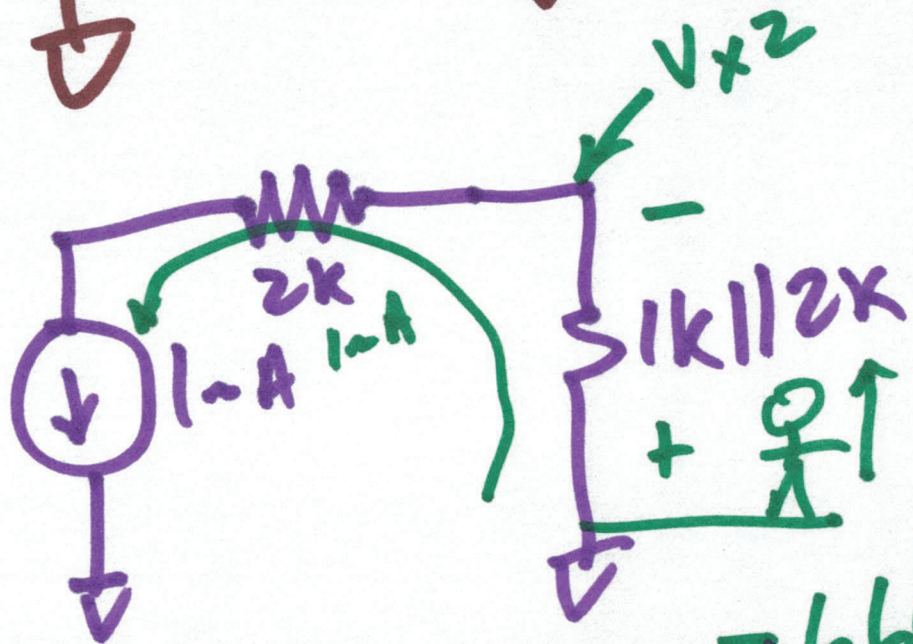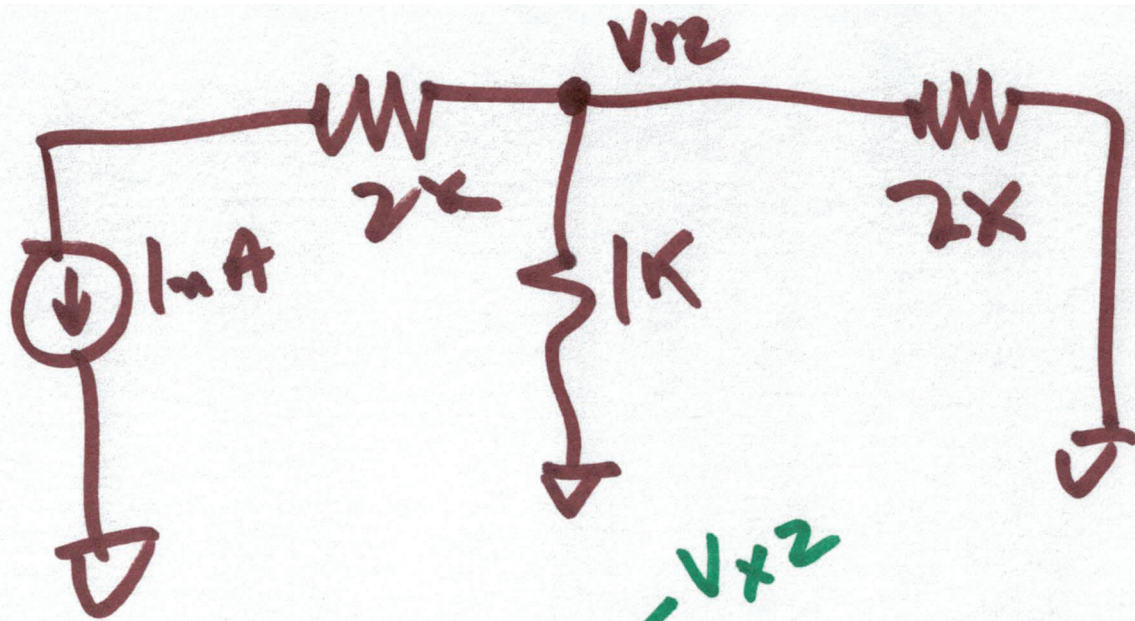


$$1k \parallel 2k = \frac{1k \cdot 2k}{1k + 2k} = 666\Omega$$

$$-666 \cdot 1A = vx2$$

$$vx = -1.667 + (-.667)$$

$$vx = -2.333V$$




$$vx2 = -.666V$$

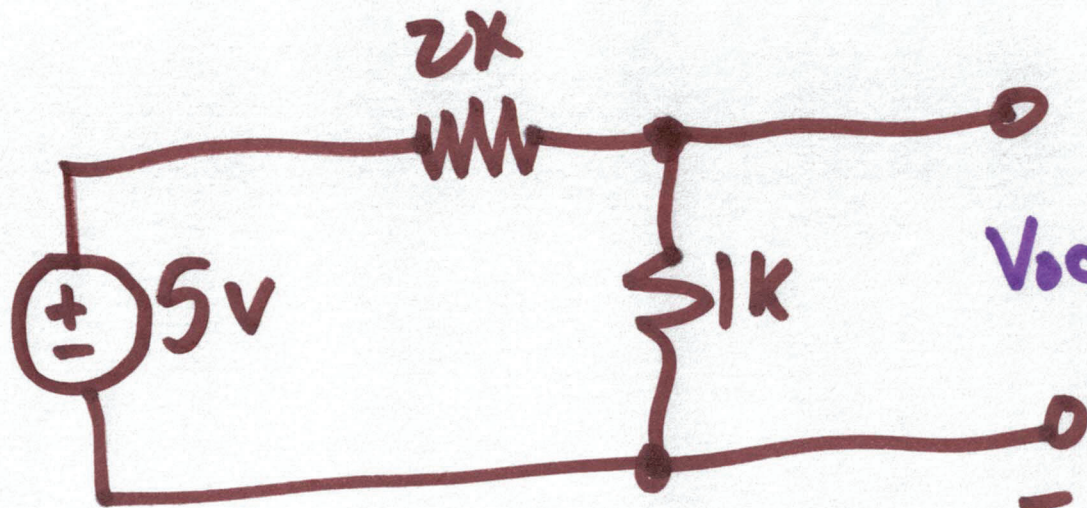


$$V_{oc} = 5 \cdot \frac{1k}{2k + 1k}$$


$$= \frac{5}{3}V$$

THEVENIN EQUIVALENT

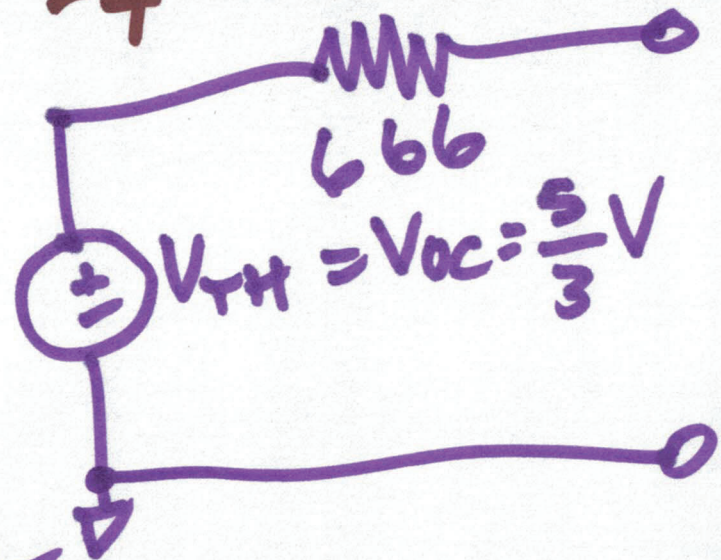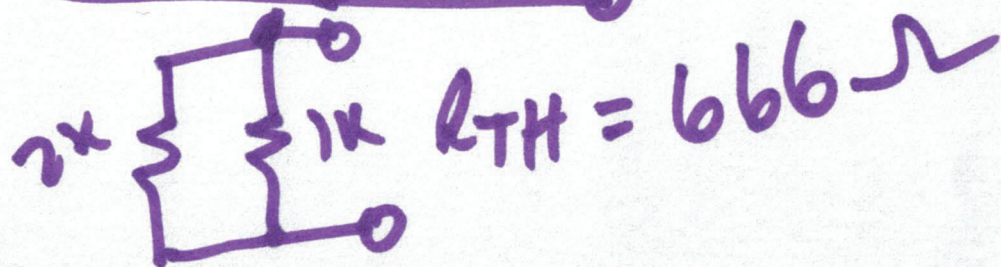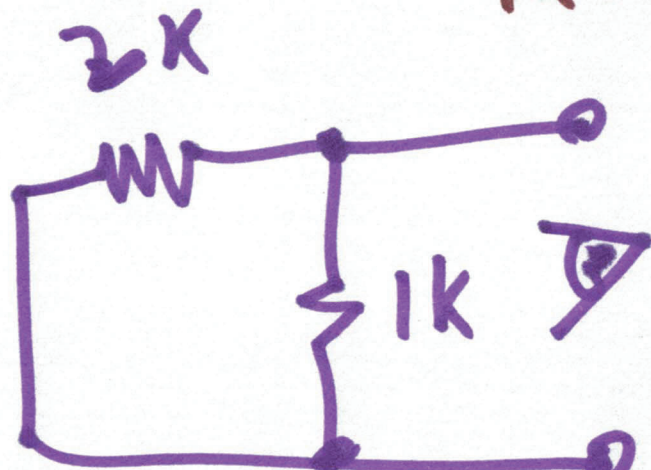

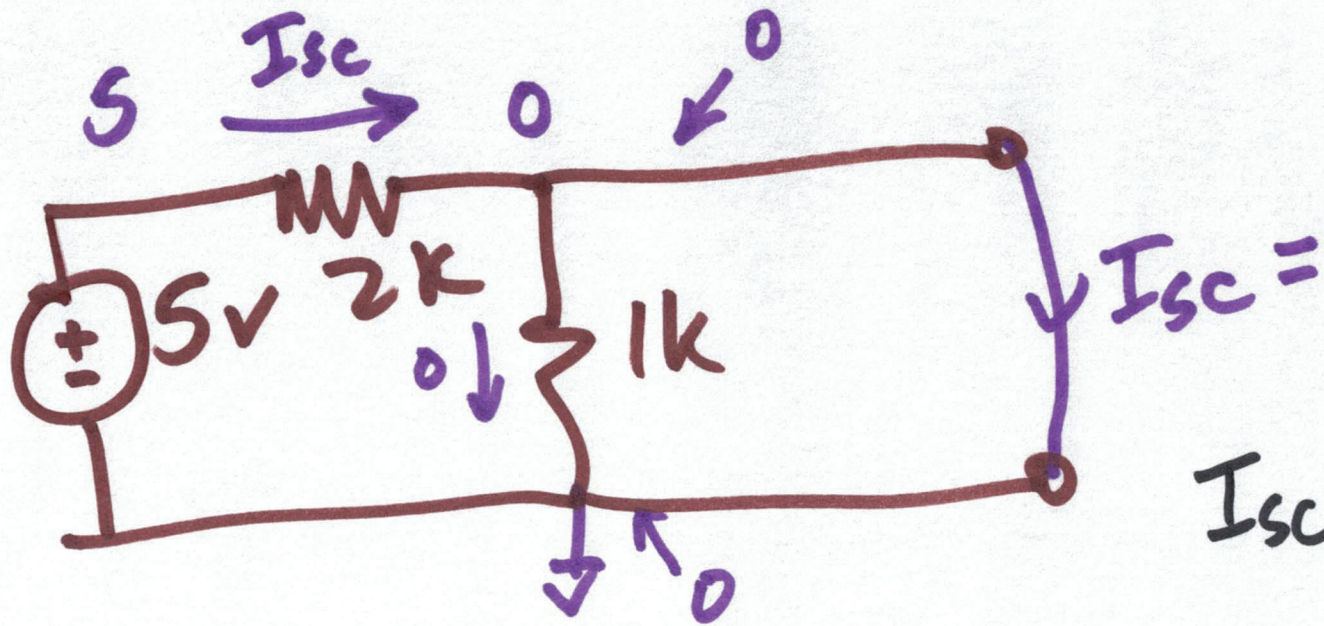
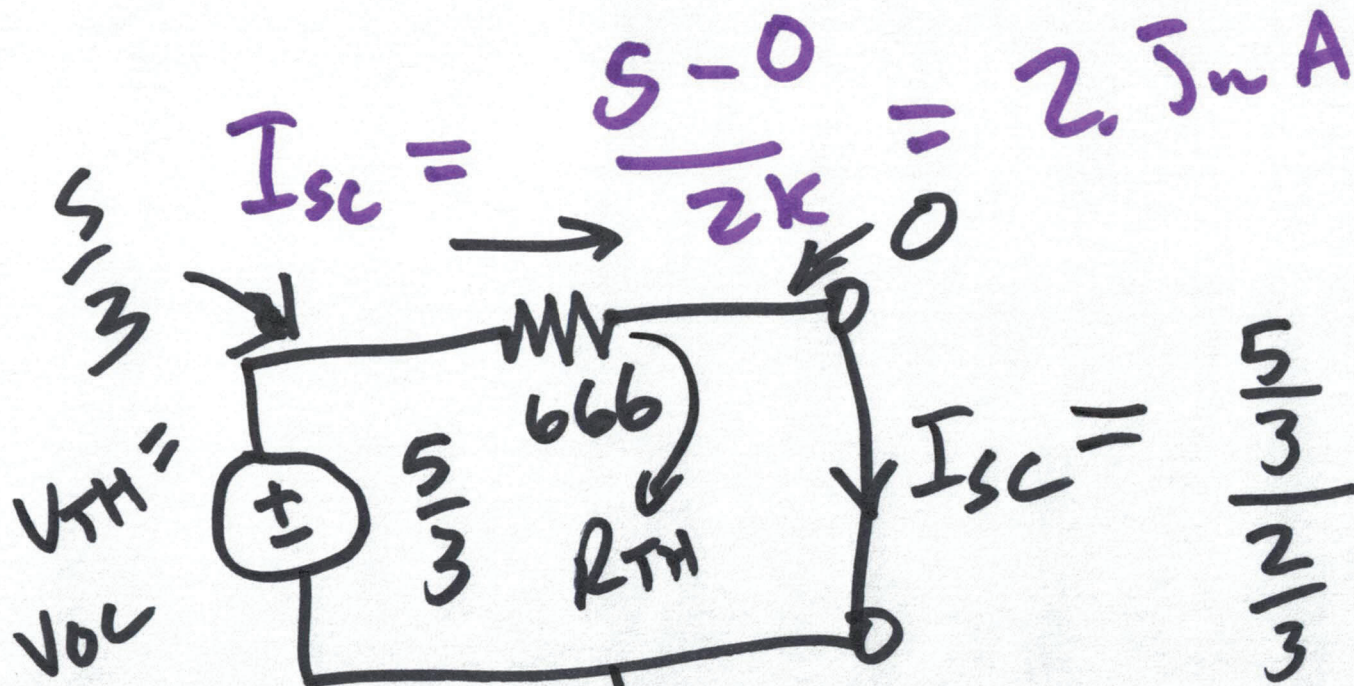
$$I_{sc} = \frac{V_{oc}}{R_{TH}} = \frac{V_{TH}}{R_{TH}}$$



NORTON EQUIVALENT

