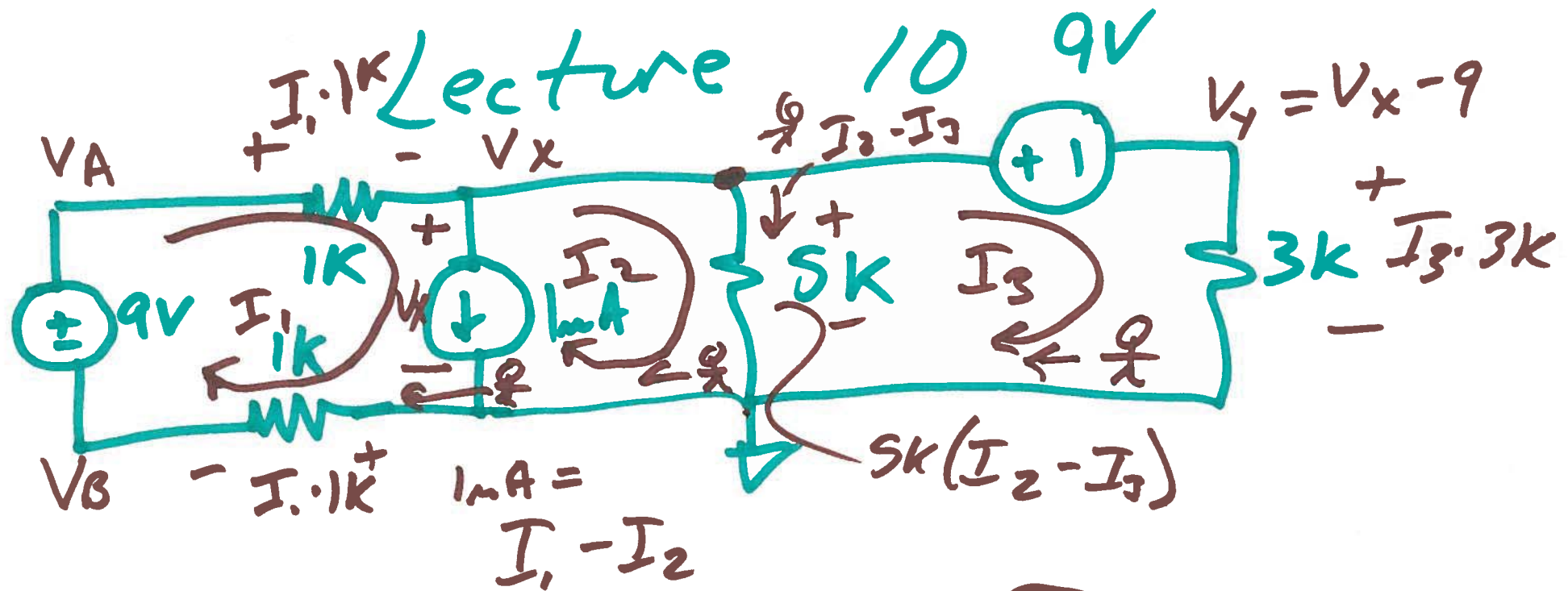


EE 220

Circuits 1



$$\begin{aligned}
 -I_1 \cdot 1k + 9 - I_1 \cdot 1k - V_x &= 0 \\
 +V_x - 5k(I_2 - I_3) &= 0 \rightarrow \frac{V_x}{I_3 \cdot 3k} = 5k(I_2 - I_3) \\
 5k(I_2 - I_3) - 9 &= 0
 \end{aligned}$$

$$I_1 = 1mA + I_2$$

$$-I_1 \cdot 2k + 9 - 5k(I_2 - I_3) = 0$$

$$5kI_2 - 5kI_3 - 9 - 3kI_3 = 0$$

$$I_1 = 1mA + I_2$$

$$\rightarrow I_1(-2k) + I_2(-5k) + I_3(5k) + 9 = 0$$

$$I_2(5k) + I_3(-8k) - 9 = 0$$

$$\rightarrow I_1(-2k) + I_3(-3k) = 0$$

$$-2V + I_2(-2k) + I_3(-3k) = 0$$

$$1mA + I_2 + ~~0.5~~ I_3 = 0$$


$$I_2 = -1mA - 1.5 I_3$$

$$5k(-1mA - 1.5I_3) + I_3(-8k) - 9 = 0$$

$$-5V - 7.5kI_3 + I_3(-8k) - 9 = 0$$

$$I_3(-15.5) = 14$$
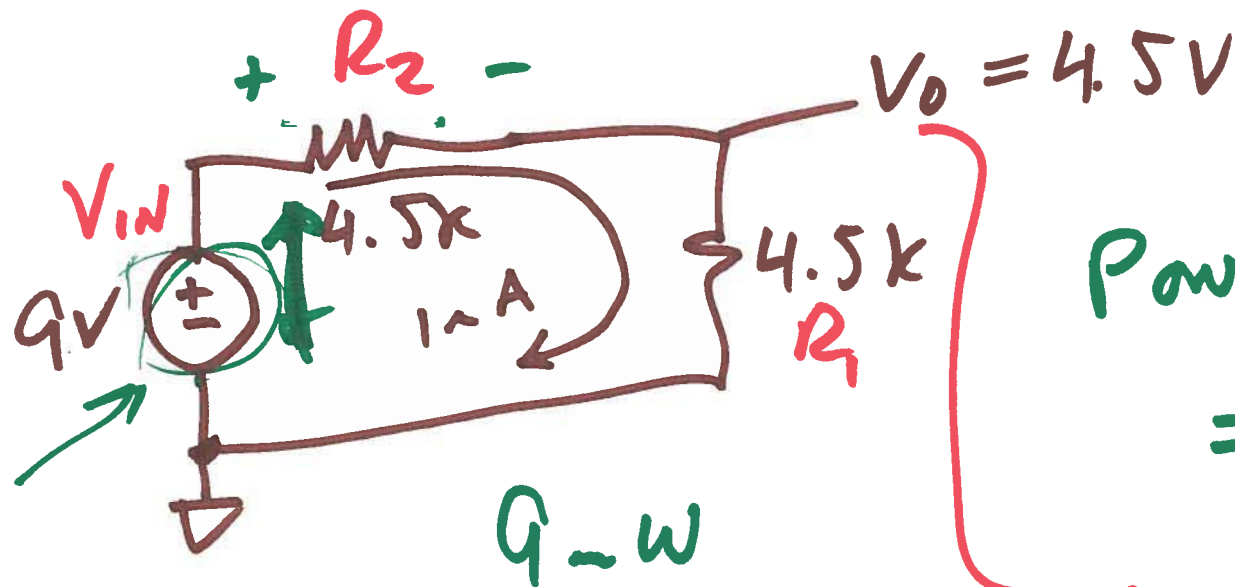
$$I_3 = \frac{-14}{15.5} = \underline{\underline{-0.96}}$$




$$Power = VI$$


$$= 4.5mW$$


$$V_0 = V_{in} \cdot \frac{1}{2} = \frac{R_1}{R_1 + R_2}$$

$$9V \cdot 1mA = -QmW$$

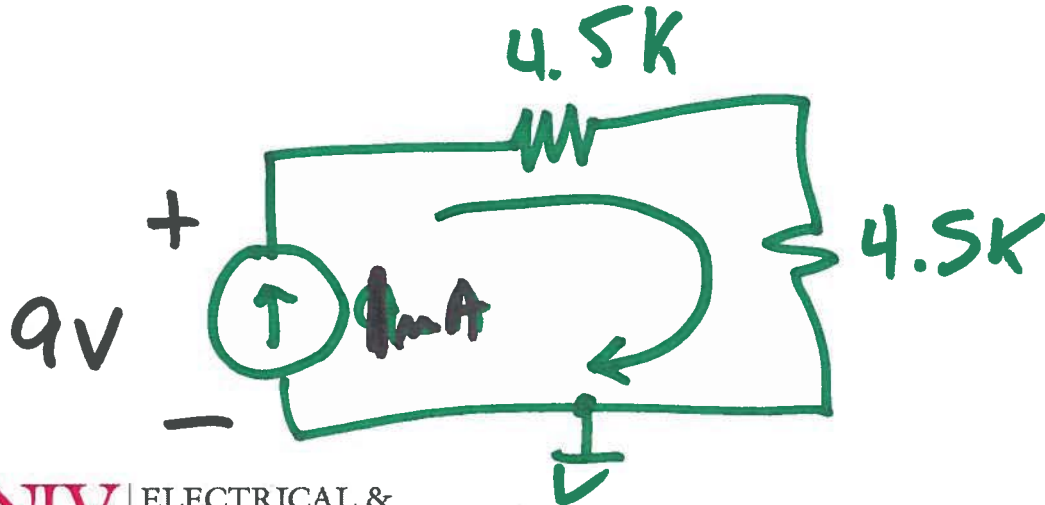

$$y = x = f(x)$$

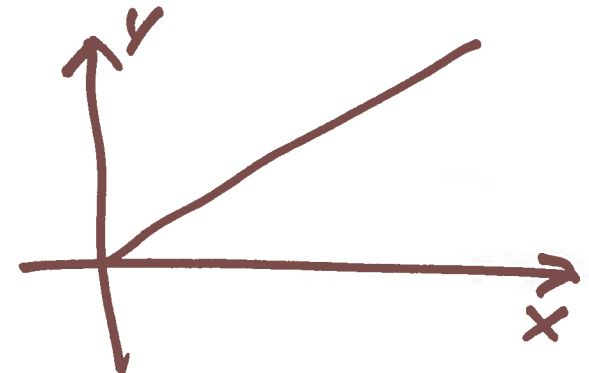

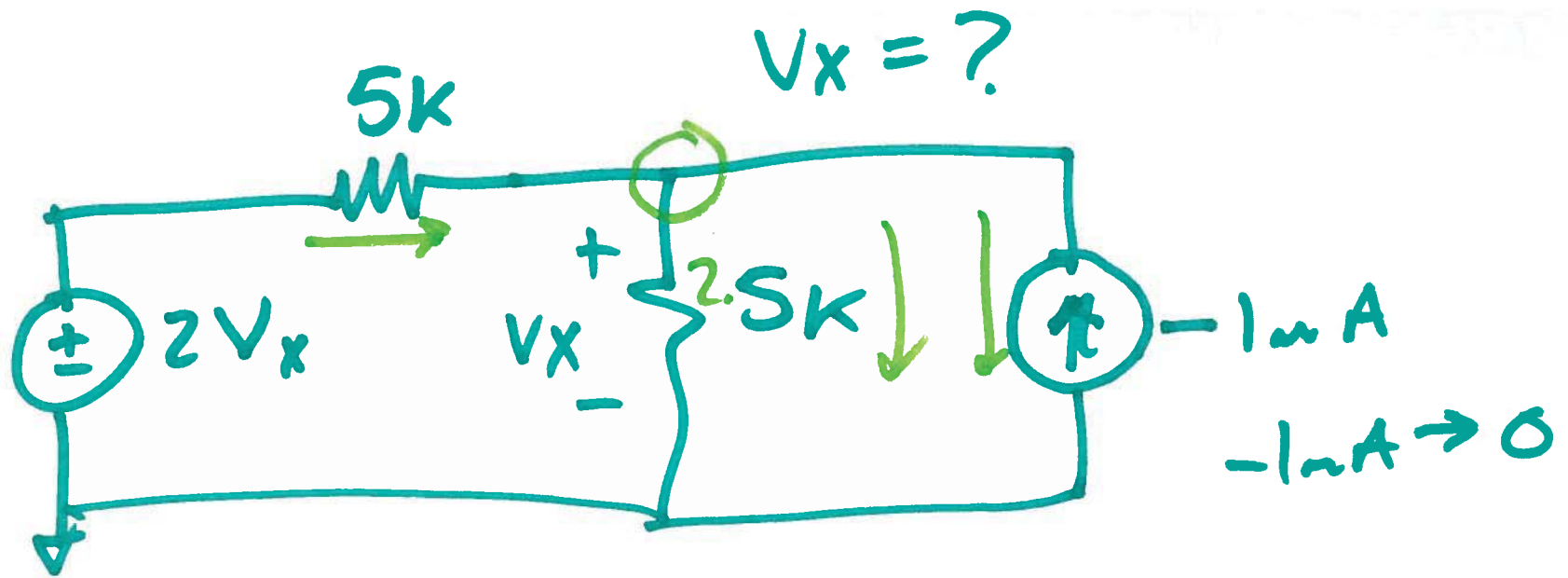

$$\frac{2V_x - V_x}{5k} = \frac{V_x}{2.5k} + 1mA$$

$$\frac{V_x}{5k} = \frac{V_x}{2.5k}$$

$$V_x = 2V_x + \boxed{V_x = -5V}$$


$1mA \rightarrow 0$

$0 < I_x < 1mA$

$5k I_x \rightarrow -V_x = 5 - 0$

$V_x = 0 \rightarrow -5$

$$V_x = -5/I_x$$

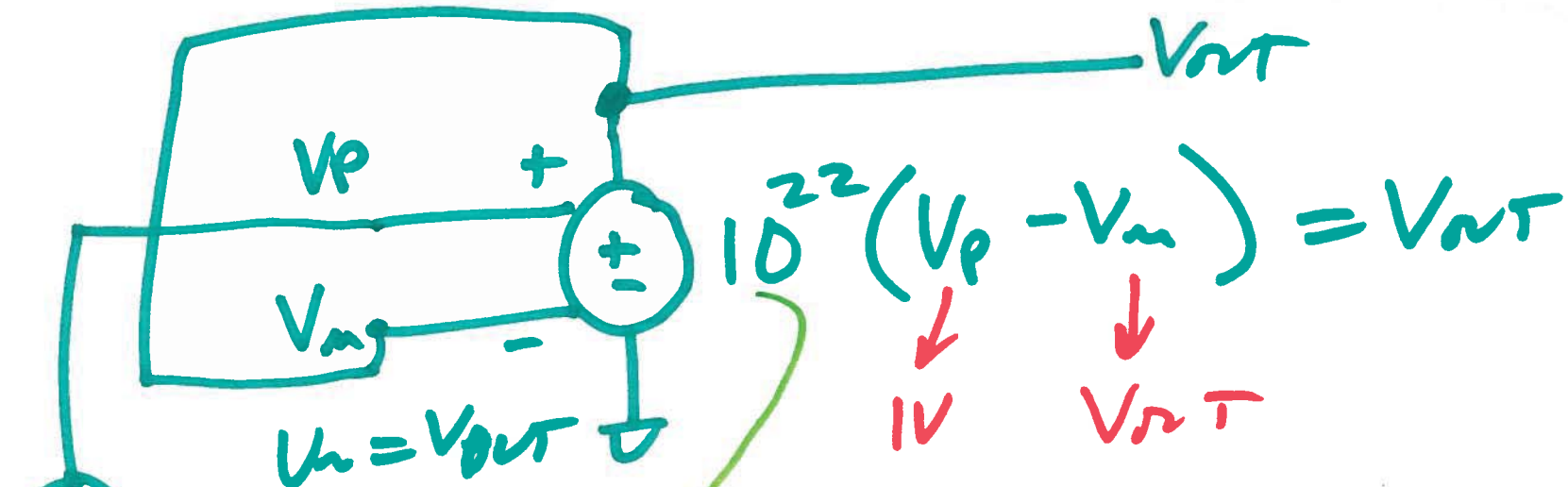


$$10^{22} (1 - V_{out}) = V_{out}$$

open-loop gain = ∞

$$10^{22} - 10^{22} V_{out} = V_{out}$$

$$V_{out} (1 + 10^{22}) = 10^{22}$$
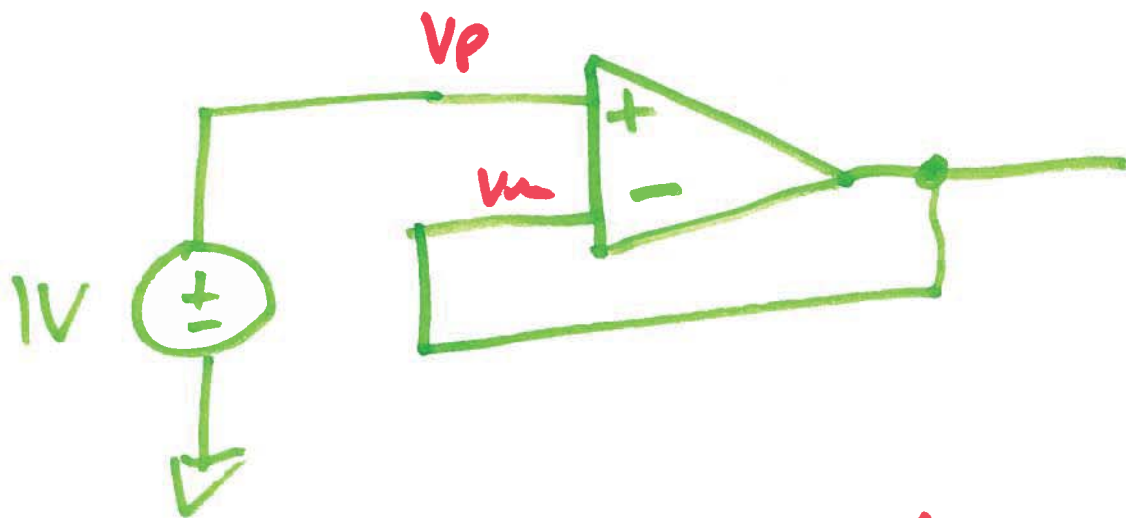
$$V_{out} = \frac{10^{22}}{1 + 10^{22}} = 1$$



$$B_{13}(\infty) \downarrow$$

$$V_{NT} = A_{OL}(V_P - V_n)$$

Annotations: $1V$ points to V_P , and V_{NT} points to V_n .

$$V_{NT} = A_{OL}(1 - V_{NT})$$

$$\lim_{A_{OL} \rightarrow \infty} V_{NT} = \frac{A_{OL}}{1 + A_{OL}} \rightarrow 1V$$