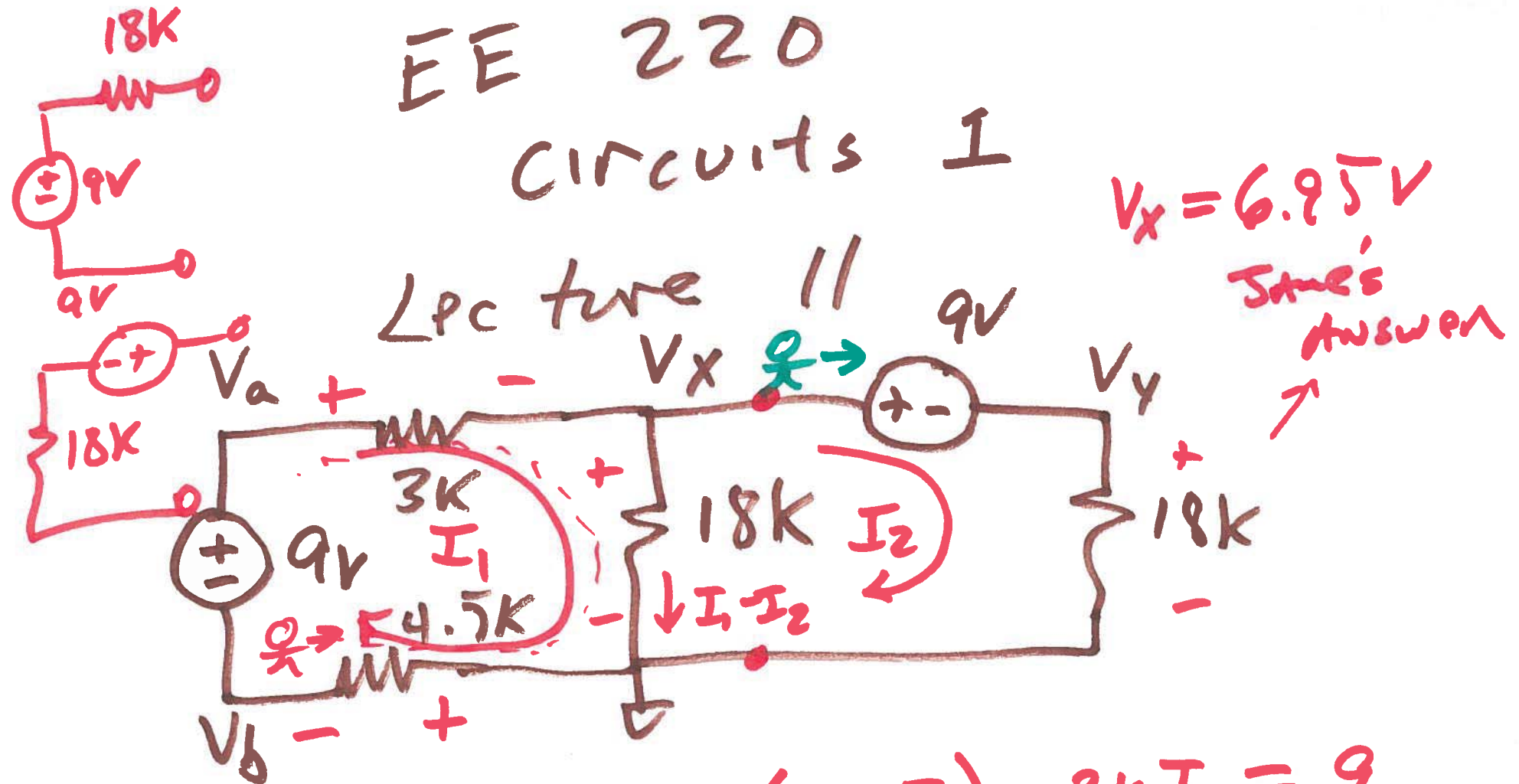


EE 220

Circuits I




$$4.5k \cdot I_1 + 18k(I_1 - I_2) + 3kI_1 = 9$$

$$-9V - 18k I_2 + 18k(I_1 - I_2) = 0$$

$$3I_1 + 12(I_1 - I_2) + 2I_1 = 6mA$$

$$-0.5mA - I_2 + I_1 - I_2 = 0$$

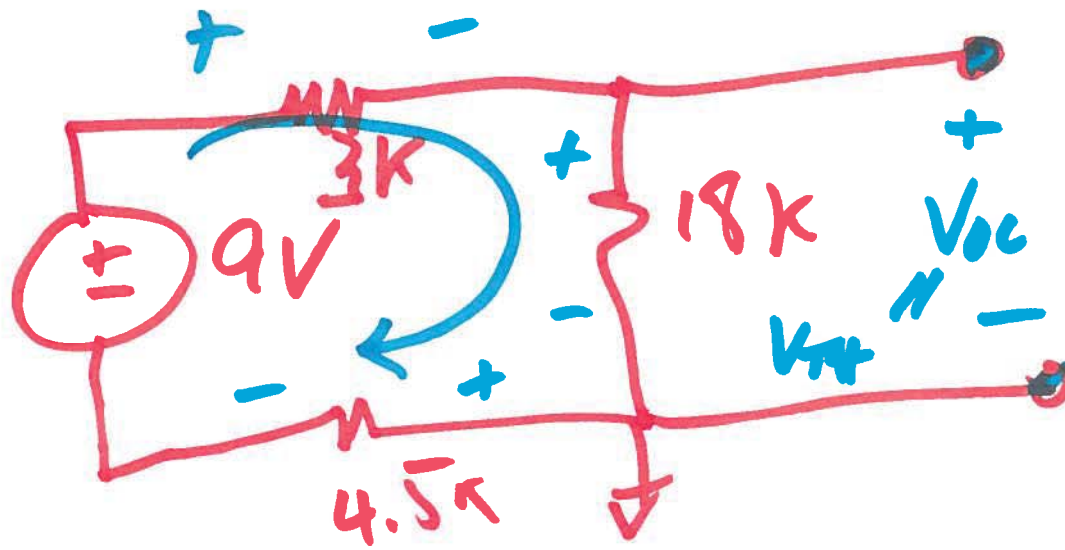


$$R_{TH} = 5.29k$$

$$0 = 9 - I \cdot 3k - I \cdot 18k - 4.5kI$$

$$V_{OC} = 18k \cdot I = \frac{9V \cdot 18k}{3k + 18k + 4.5k} = 3504A \cdot 18k$$

$$V_{TH} = 6.35V$$

2)


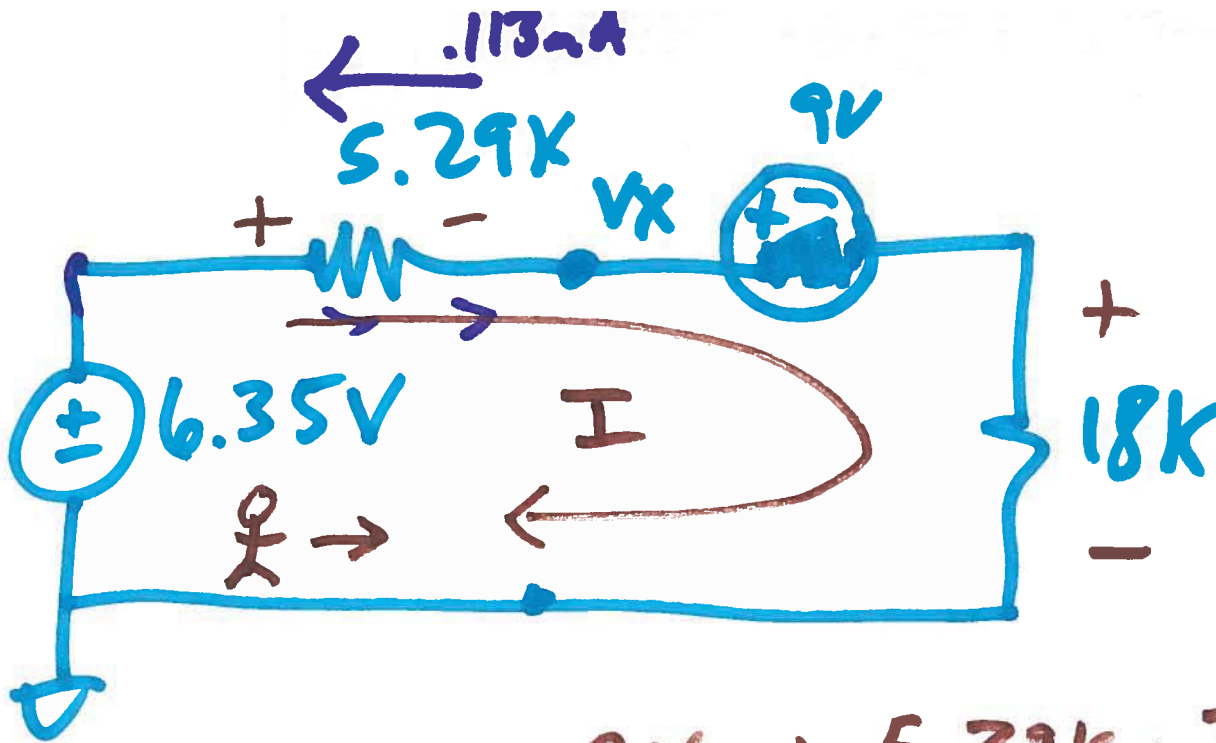


$$18\text{k} \cdot I + 9\text{V} + 5.29\text{k} \cdot I - 6.35\text{V} = 0$$

$$I = \frac{-2.65\text{V}}{23.29\text{k}} = -.113\text{mA}$$


$$V_x = .113\text{mA} \cdot 5.29\text{k} + 6.35\text{V}$$
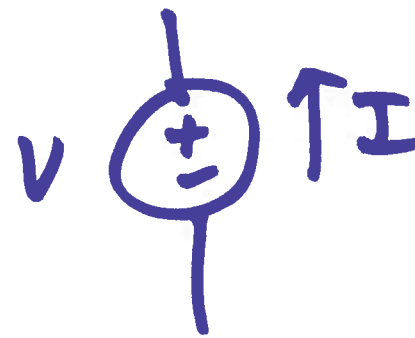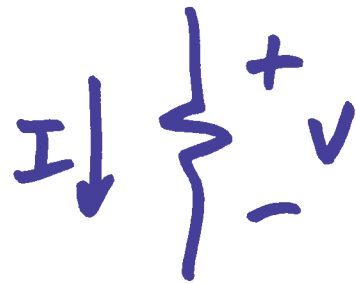
$$= \underline{\underline{6.95\text{V}}}$$



$$\text{power} = v \cdot I$$

$$\text{power} = v \cdot (-I)$$

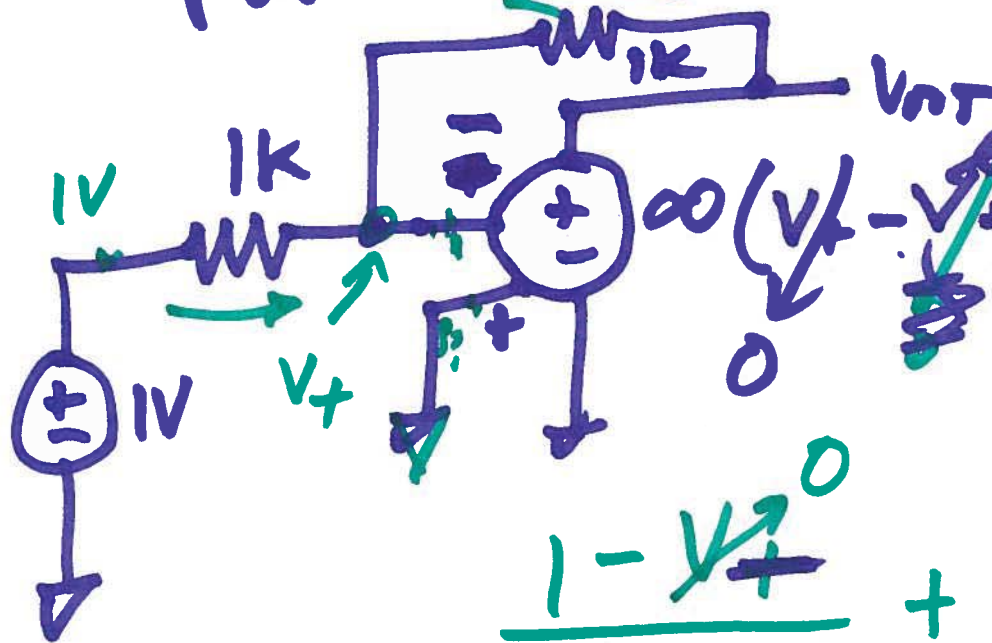


$$(v_+ - v_-) = v_{NT}$$

$$v_- = \frac{v_{NT}}{\infty} = 0$$


$$\frac{1 - v_+}{1k} + \frac{v_{NT} - v_+}{1k} = 0$$

$$v_{NT} = \frac{-1k}{1k} = -1V$$

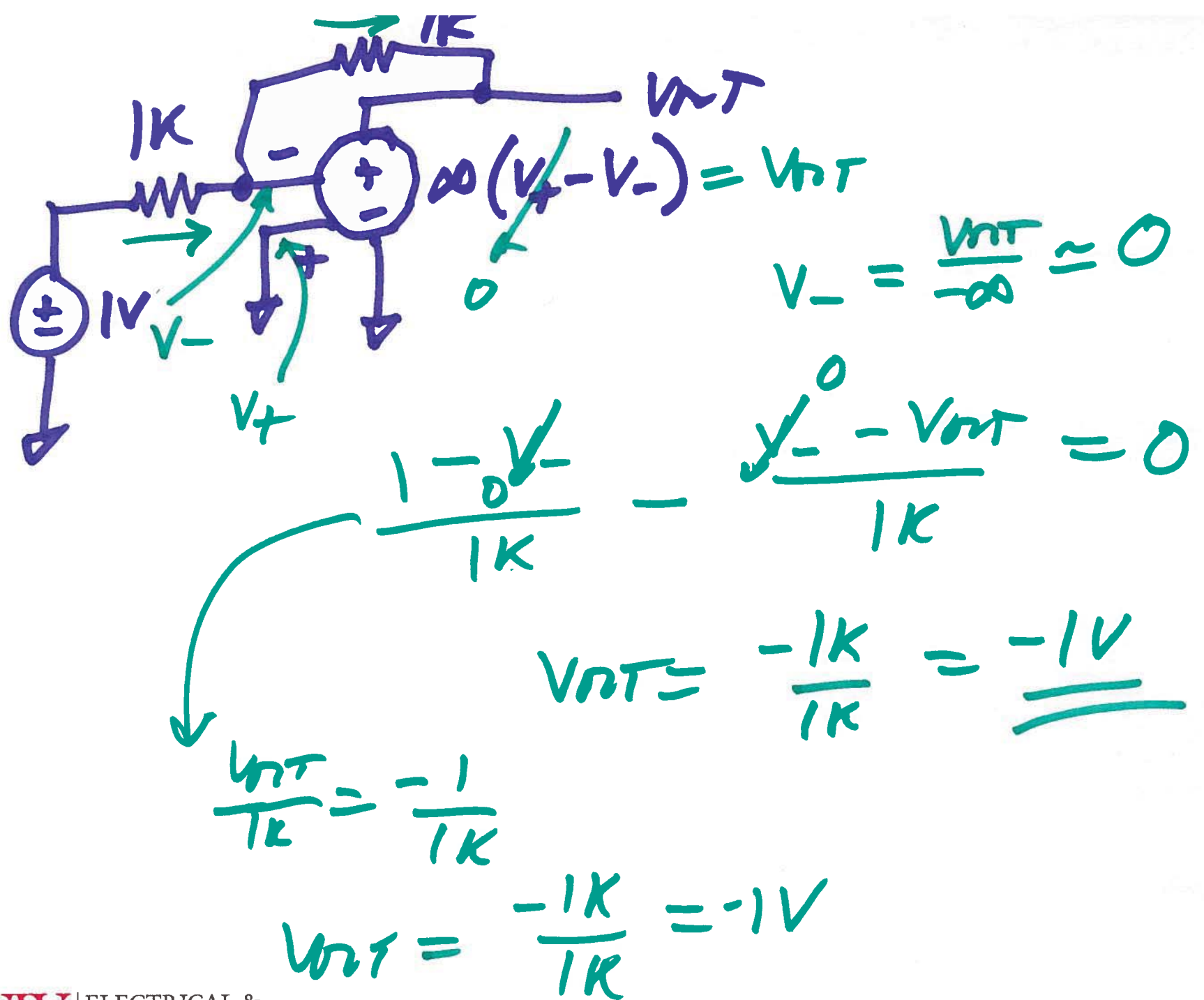

Inverting Op-Amp

! important!

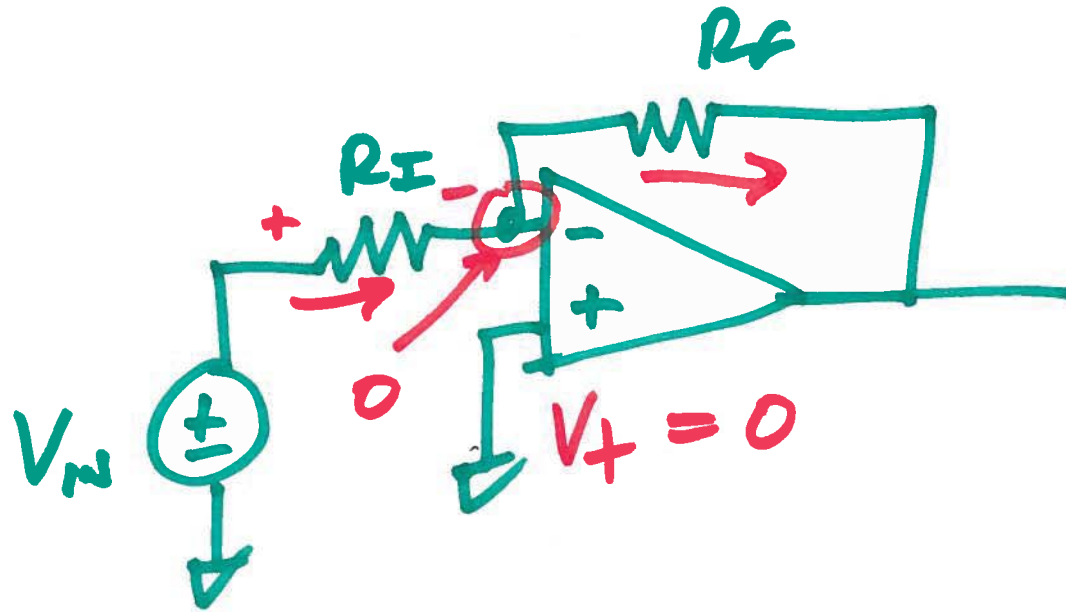

$$V_{OUT} = A_{OL}(V_+ - V_-)$$

1) Determine V_+


2) SET $V_+ = V_-$

3) KCL at ~~Node~~ inverting (V_-) input


$$\frac{V_{IN} - 0}{R_I} = \frac{0 - V_{OUT}}{R_F}$$

$$GAIN = \frac{V_{OUT}}{V_{IN}} = -\frac{R_F}{R_I}$$

4)

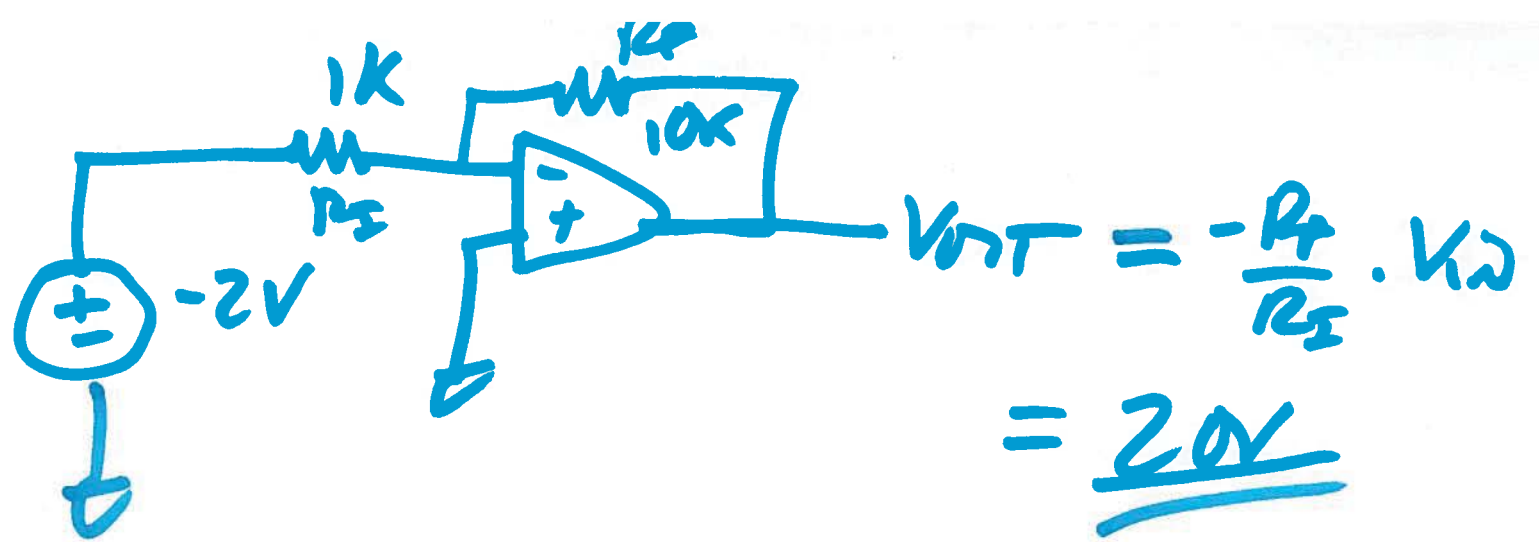

Non-inverting op-amp Amplifier

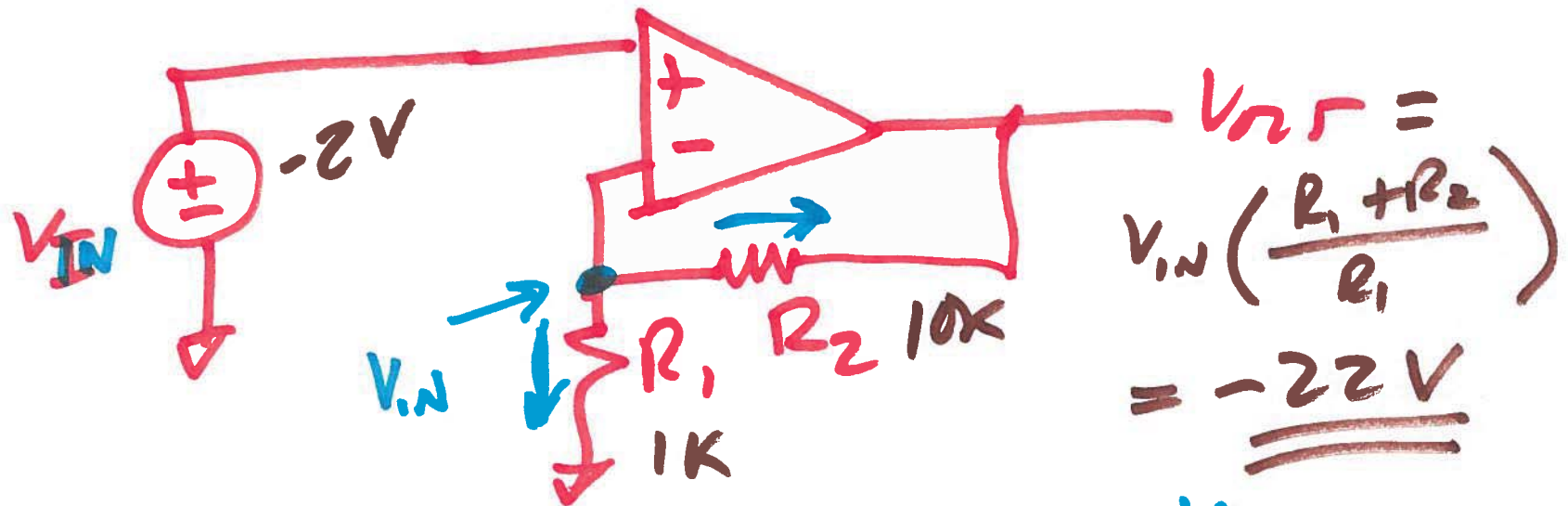

$$V_+ = V_{IN}$$

$$\frac{V_{IN}}{R_1} - \frac{V_{OUT}}{R_2} = 0$$

$$V_{IN} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_{OUT}}{R_2}$$

$$\frac{V_{OUT}}{V_{IN}} = 1 + \frac{R_2}{R_1} = \frac{R_1 + R_2}{R_1}$$