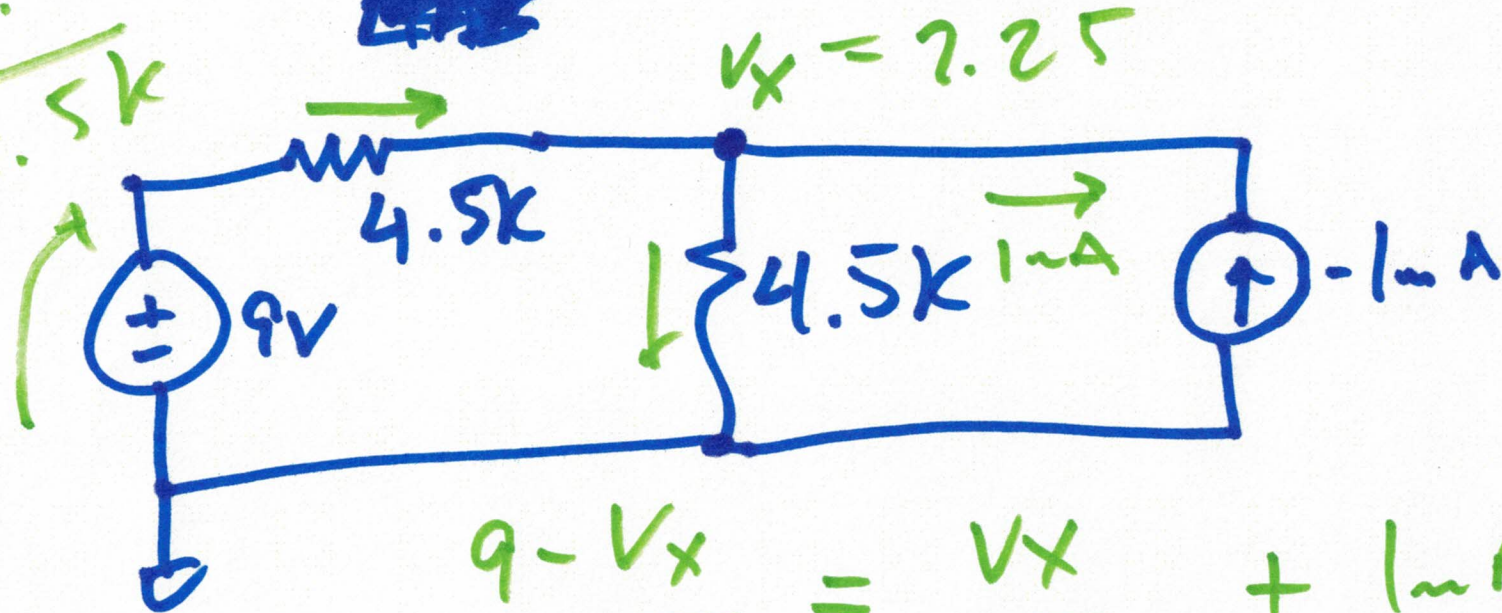


EE 220

6.75
 $9 - 2.25 = 1.5 \mu A$ circuits 1
Lecture 14


$$I_s = 1.5 \mu A$$



$$\frac{9 - V_x}{4.5k} = \frac{V_x}{4.5k} + 1 \mu A$$

$$V_x = 2.25$$

$$9 - V_x = V_x + 4.5V$$
$$4.5 = 2V_x$$

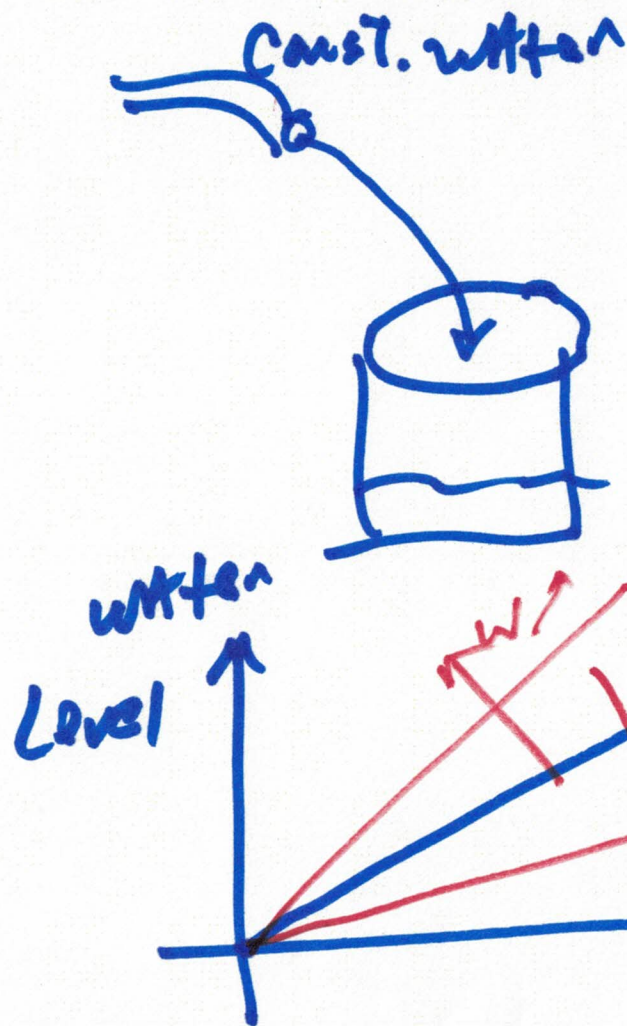


Bucket stores water

$$\text{Water} = \text{Bucket} \cdot \frac{\Delta \text{Level}}{\Delta t}$$


$$w = B \cdot \frac{d \text{Level}}{dt}$$

↑
slope

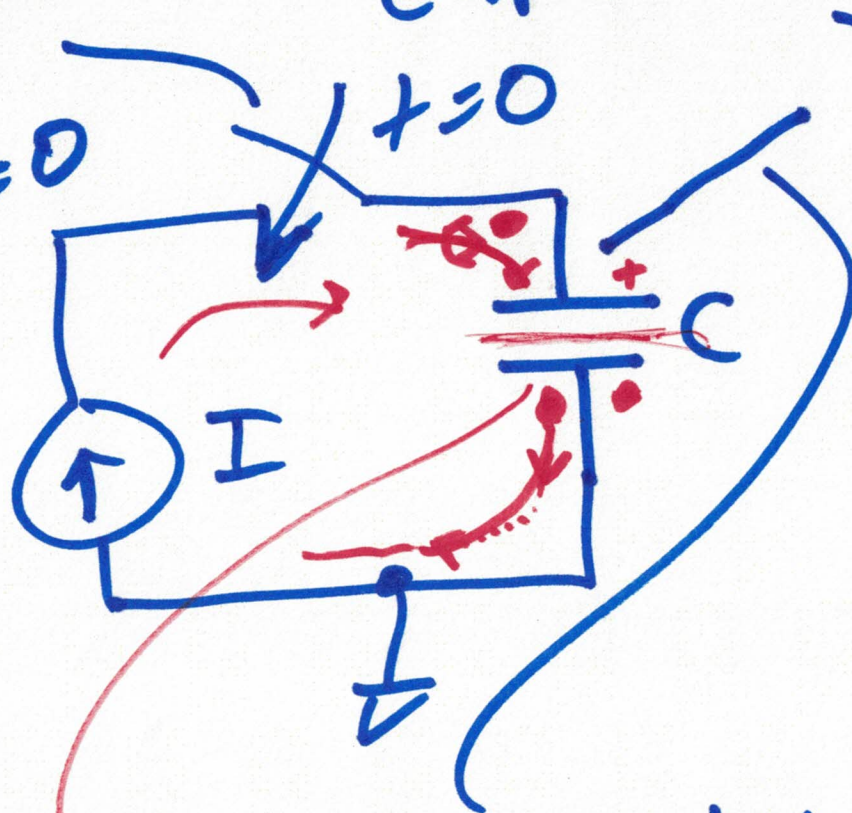switch closes at $t=0$ CAPACITOR (condenser) -



Farads
 $\frac{L}{T} \rightarrow t$

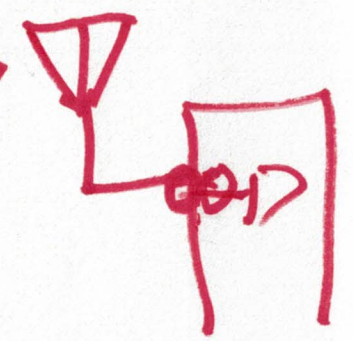

$$C = \frac{Area}{t} \cdot \epsilon$$

dielectric

$$I = C \cdot \frac{dV}{dt}$$

displacement current

conduction current

Memorize

$$C \cdot V = Q$$

capacitance voltage ← charge

$$I = 1 \mu A = 0.001 A = 10^{-3} A$$

$$C = 1,000 \text{ pF} = 1 \text{ nF} = 1,000 \times 10^{-12} \text{ F}$$



$$= 1 \times 10^{-9} \text{ F} = 10^{-9} \text{ F}$$


$$I = C \frac{dV_C(t)}{dt} \Rightarrow \frac{dV_C(t)}{dt} = \text{slope} = \frac{I}{C}$$

$$= \frac{10^{-3}}{10^{-9}} = 10^6$$

$$= \frac{1 \text{ V}}{10^{-6} \text{ s}}$$

$$= \frac{1 \text{ V}}{4 \text{ s}}$$

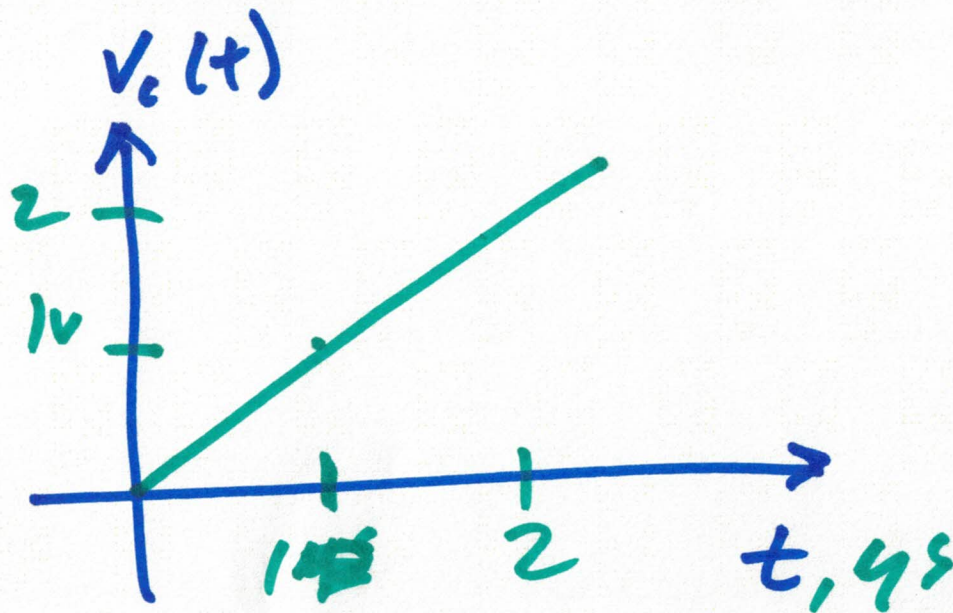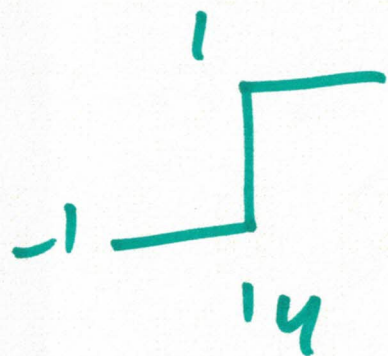

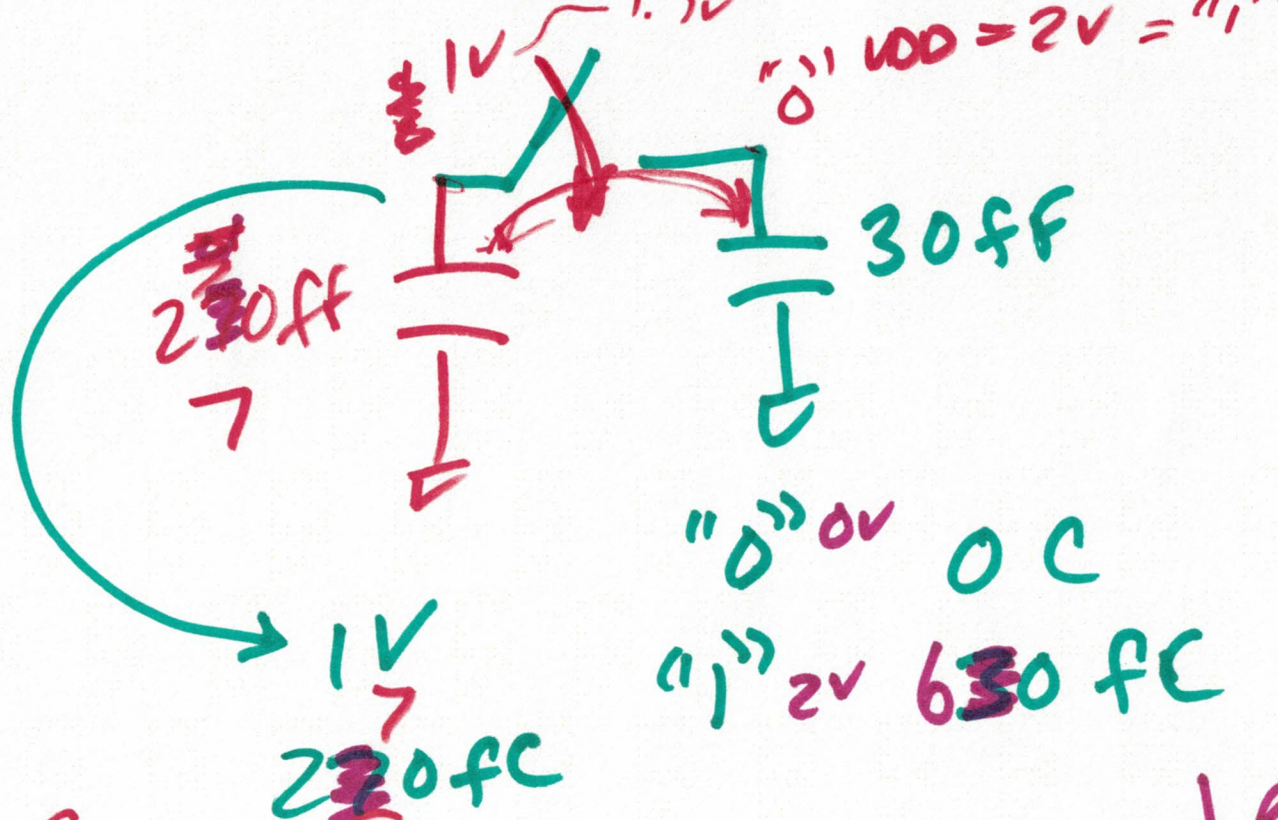

$$Q = 10^{-15}$$

$$f = 10^{-15}$$

$$P = 10^{-12}$$

$$N = 10^{-9}$$

$$CV = Q$$

$$V_f(300fF) = 270fF + 60fF$$

$$V_f = \frac{330}{300} \approx 1.1V$$



$$R_T = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$R_1 \parallel R_2 = R_T$$

$$R_1 \parallel R_2 \Rightarrow R_1 \parallel R_2$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$CV = Q$$

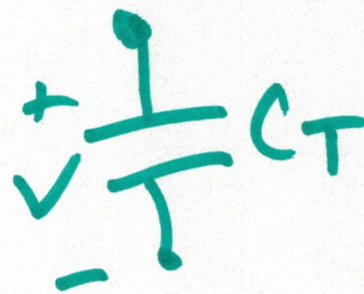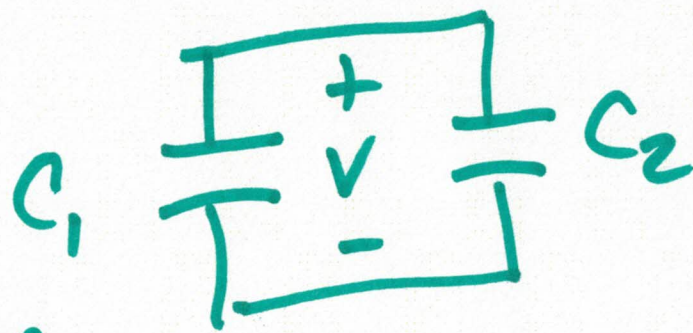

$$V_T = V_1 + V_2$$

$$\frac{Q}{C_T} = \frac{Q}{C_1} + \frac{Q}{C_2}$$

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C_T = C_1 + C_2$$

$$C_T = \frac{C_1 \cdot C_2}{C_1 + C_2}$$

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C_T \cdot V_T = Q$$

$$V_T = V_1 + V_2$$

CMOSedu.com

b)

$$V_2 = \frac{Q}{C_2}$$

$$V_T = \frac{Q}{C_T}$$