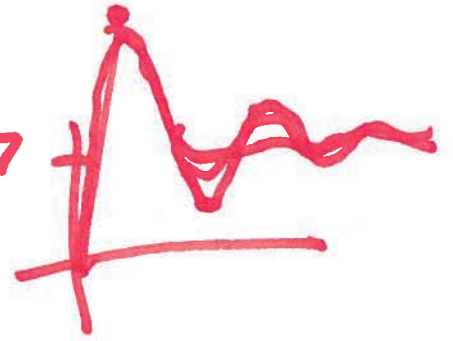


EE 220

Circuits 1







Lecture 17

first-order circuits have "1"
cap or inductor.

EX



second-order
inductor &
cap

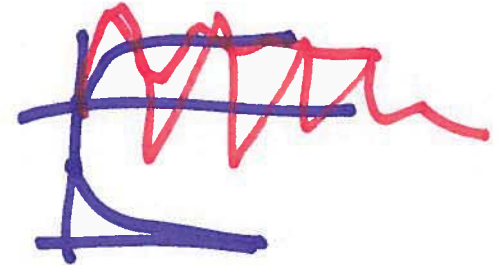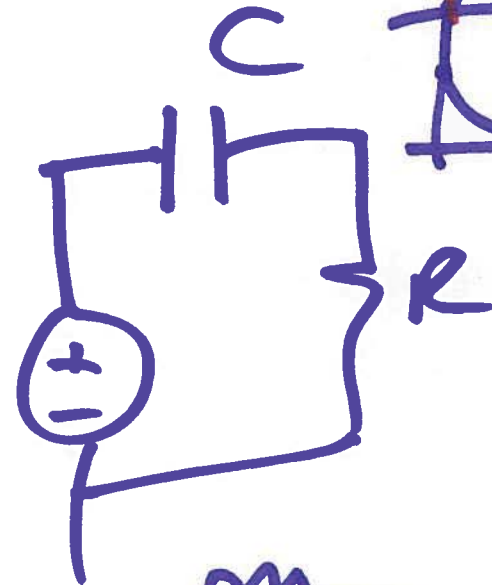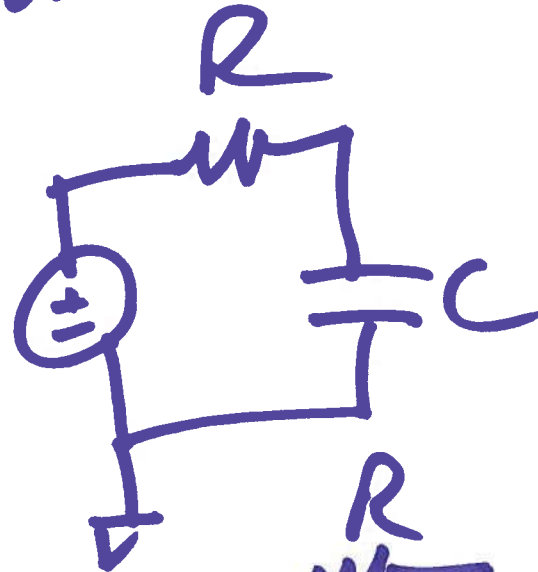

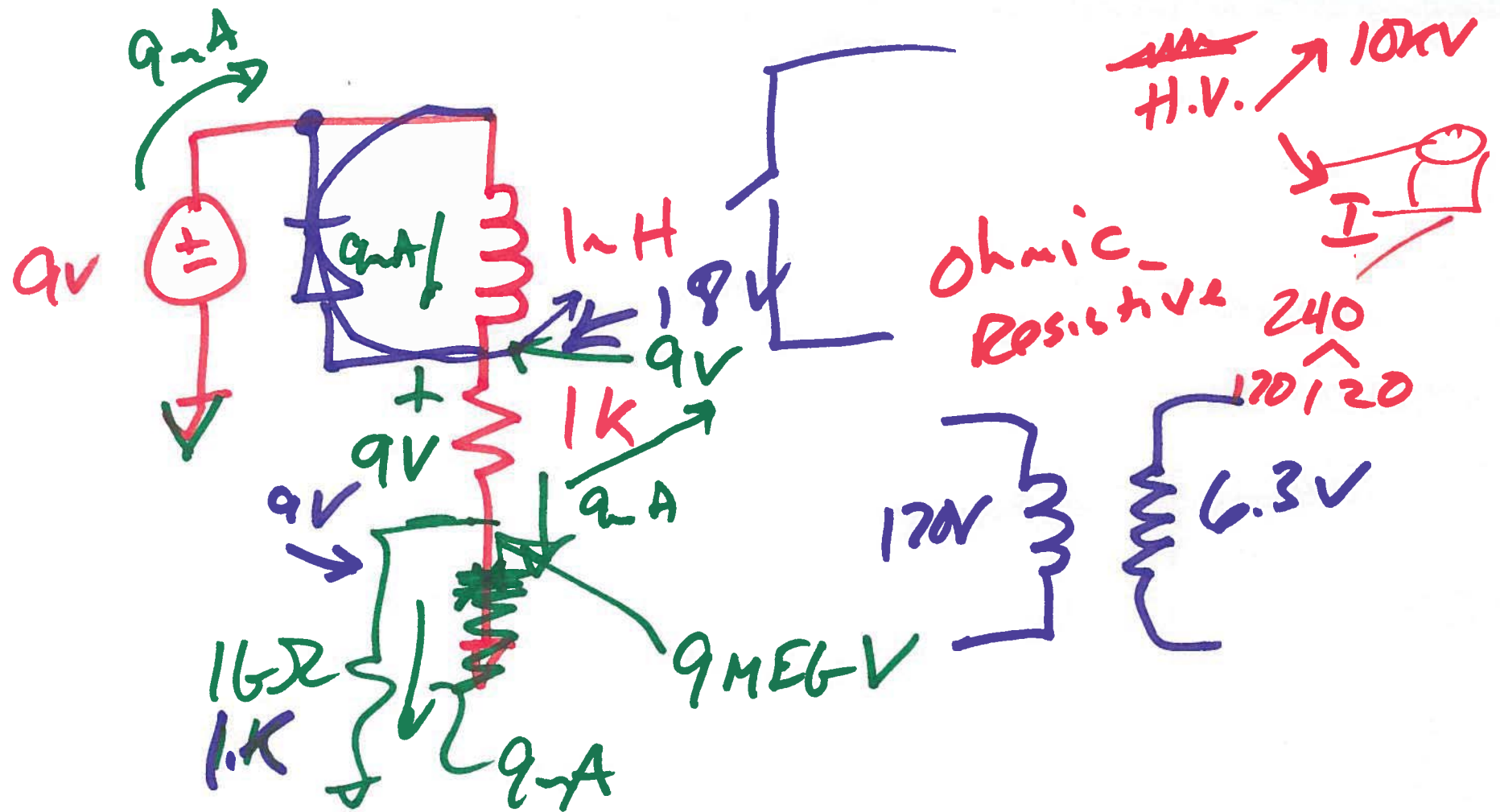

$$i(t) = \frac{9V}{1mH} \cdot t$$
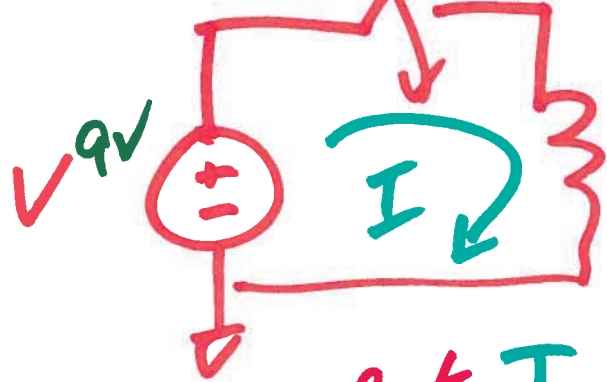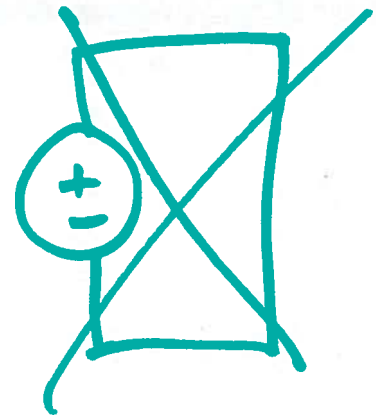
$$\frac{10^{-3}}{10^{-3}} \frac{9A}{ms} = \frac{9A}{ms}$$



3ms

14s

$$i(t) = \frac{1}{1mH} \cdot 9 \cdot t$$


$$V = L \cdot \frac{dI}{dt}$$

$$\frac{V}{L} = \text{slope} = \frac{dI}{dt}$$

$$I = \frac{1}{L} \int_{t_1, 0}^{t_2, 24s} V \cdot dt + I(0^-)$$

$$\frac{V}{1mH} = \frac{9V}{1mH} = \frac{9A}{ms}$$

3)

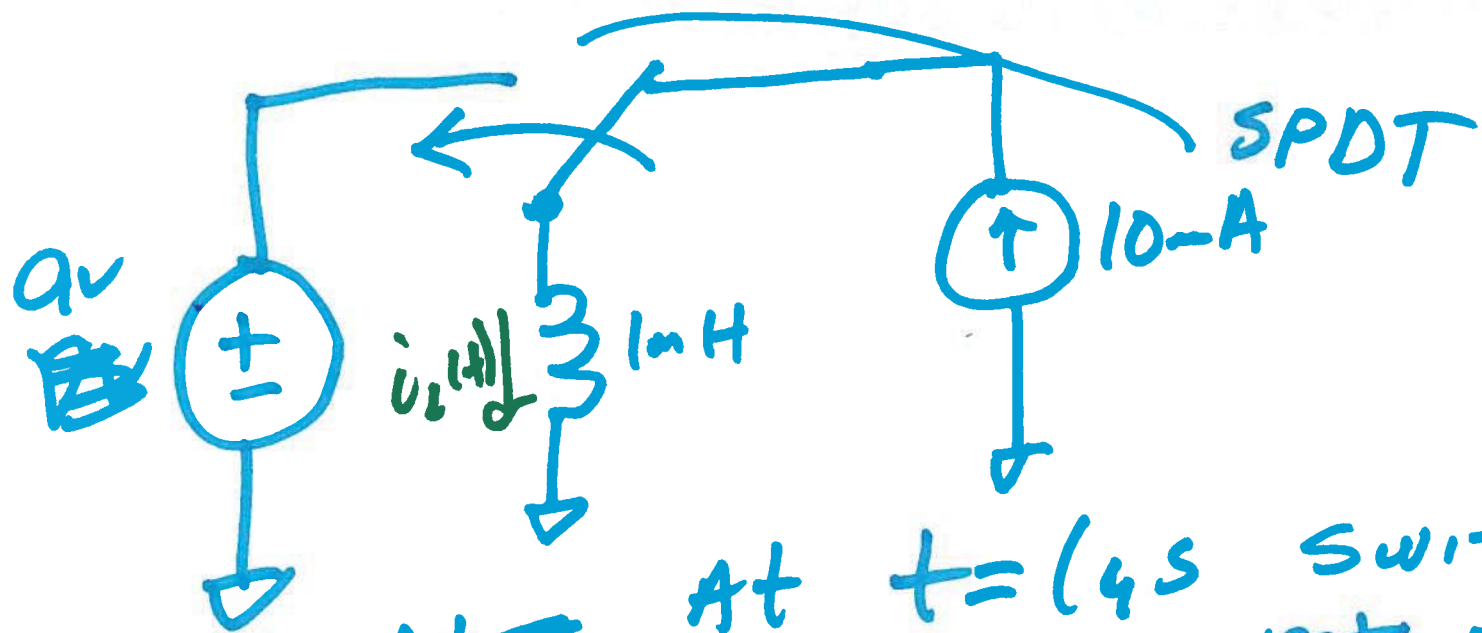


At $t = 14\text{s}$ switch connects to Voltage Source

$$i(t) = \frac{1}{L} \int_{t_1}^{t_2} v_L(t) \cdot dt + i(0^-)$$


$$\frac{9V}{1mH} = \frac{9V}{10^{-3}H} = \frac{9A}{10^{-3}s} = 9 \frac{A}{s}$$

$$= \frac{1}{1mH} 9 \cdot t \Big|_{14}^t + 10mA$$

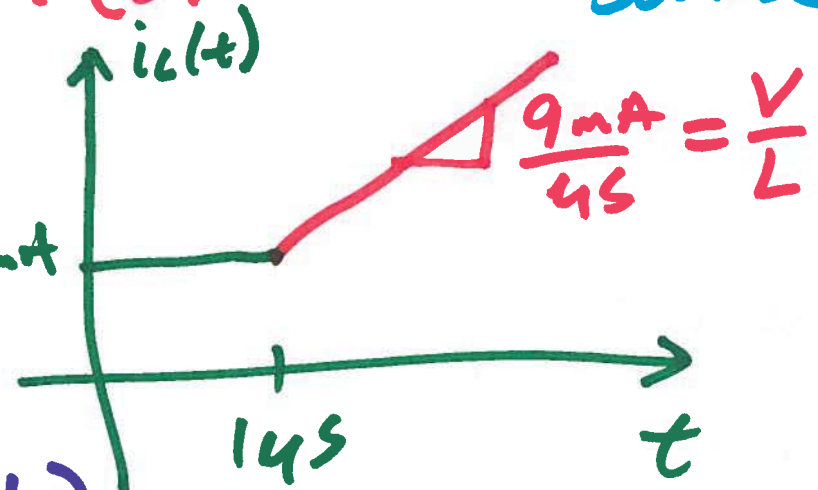

$$i(t) = \frac{9mA}{4s} (t - 14) + 10mA$$

$t > 14s$

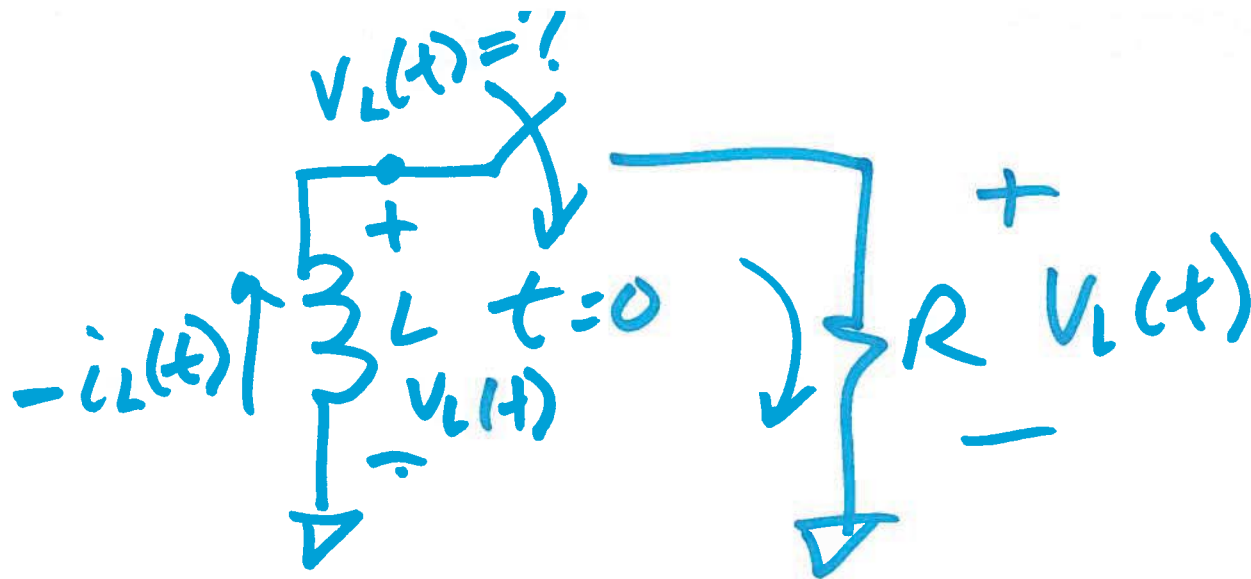

$$v_L(t) = L \cdot$$

$$\frac{v_L(t)}{R} = \frac{L}{R} \cdot \frac{di_L(t)}{dt} = \int \frac{dx}{x} = L \cdot x$$

$$v_L(t) = L \cdot \frac{di_L(t)}{dt}$$

$$\frac{L}{R} \cdot \frac{di_L(t)}{dt} = -i_L(t)$$

$$= \int_{i_{init}}^{i(t)} \frac{di_L(t)}{i_L(t)} = \int_0^t -\frac{R}{L} \cdot dt = -\frac{R}{L} \cdot t$$