
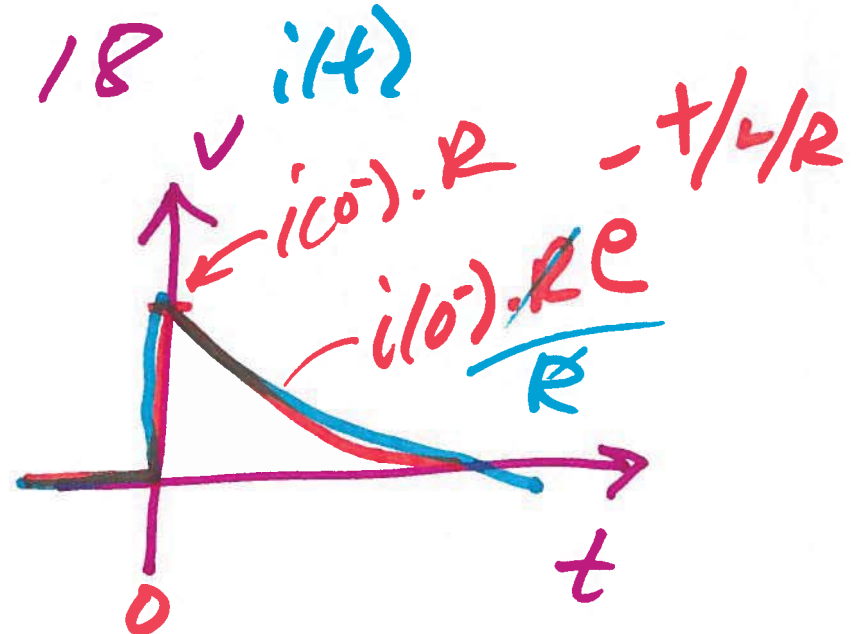


EE 220 Circuits I

Lecture 18

$$i_L \downarrow \uparrow V_L$$

$$V_L = L \cdot \frac{di_L}{dt}$$

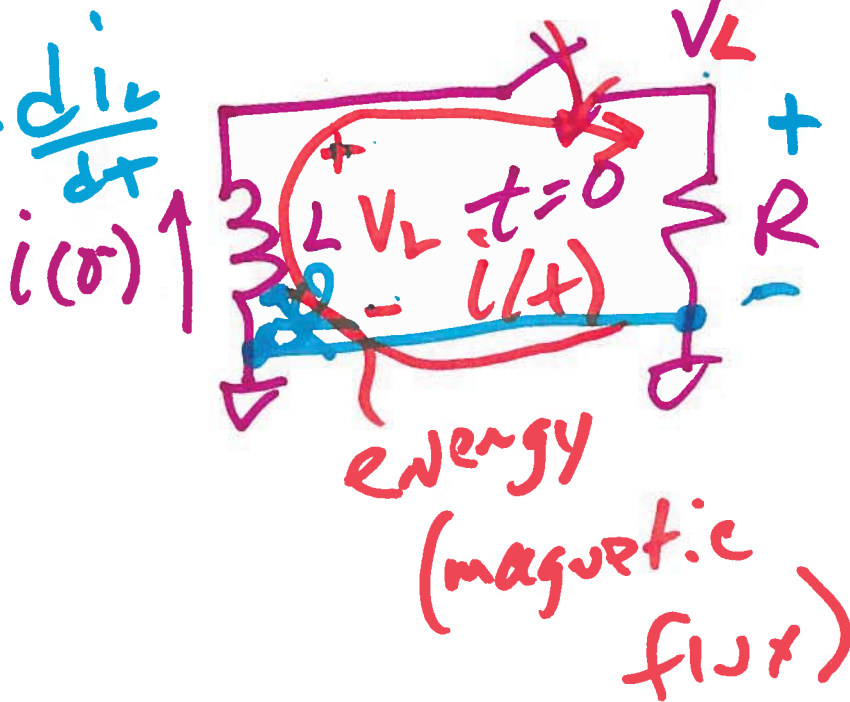

$$V = L \cdot \frac{di}{dt}$$

$$\int_a^b \frac{dx}{x} = \ln x \Big|_a^b \quad V_L - i \cdot R = 0$$

$$= \ln b - \ln a \quad -L \cdot \frac{di}{dt} - i \cdot R = 0$$

$$= \ln \frac{b}{a}$$

$$-L \cdot \frac{di}{dt} = i \cdot R$$

$$(-L) \left(\ln i(t) - \ln i(0^-) \right) = \int_{i(0^-)}^{i(t)} (-L) \cdot \frac{di}{i} = \int_0^t R \cdot dt = R \cdot t$$


$$\Rightarrow -L \cdot \ln \frac{i(t)}{i(0^-)}$$

$$-L \cdot \ln \frac{i(t)}{i(0)} = R \cdot t$$

$$e^{\ln x} = x$$

$$\ln \frac{i(t)}{i(0)} = -\frac{R}{L} \cdot t = -\frac{t}{L/R}$$


$$i(t) = i(0) \cdot e^{-t/L/R}$$

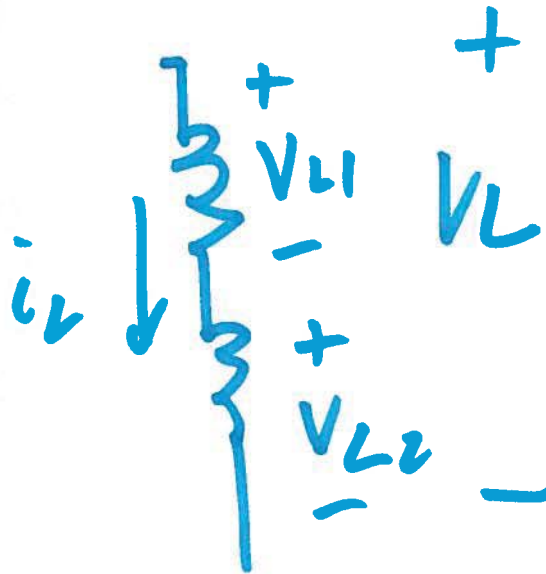

$$i = L \cdot \frac{dv}{dt}$$
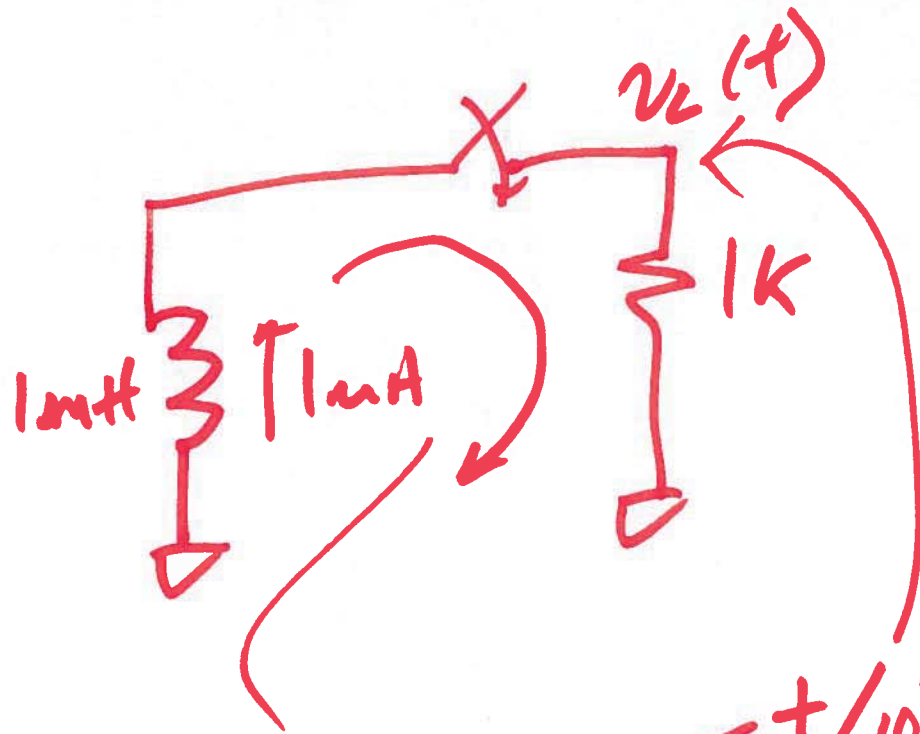
$$\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2}$$






$$V = L \cdot \frac{di}{dt}$$

$$i(t) = 1mA e^{-\frac{t / 10^{-3} H}{10^3 \Omega}} = 1mA e^{-t/1\mu s}$$

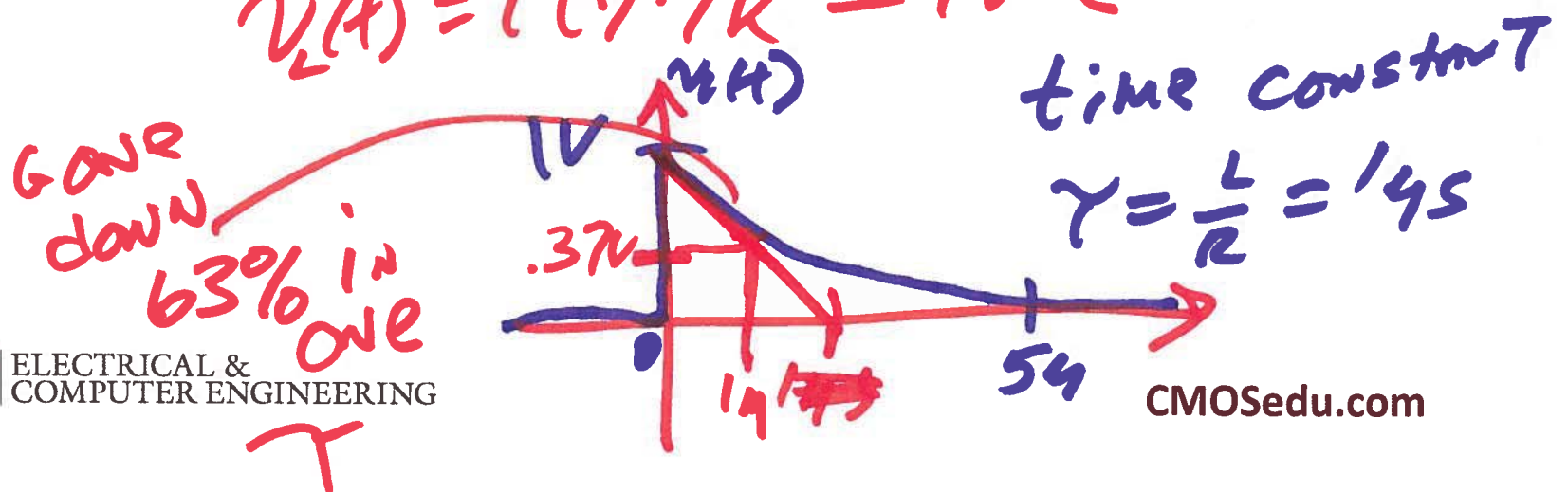
$$v_L(t) = i(t) \cdot 1K = 1V e^{-t/1\mu s}$$




time constant τ

$$\tau = \frac{L}{R} = 1\mu s$$

4)

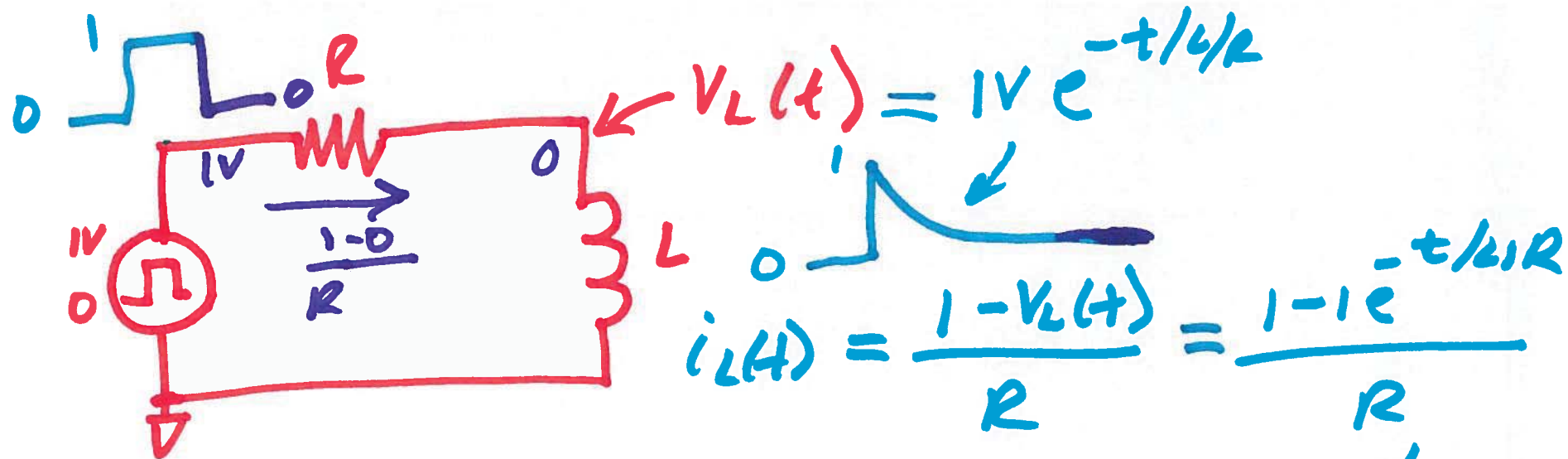

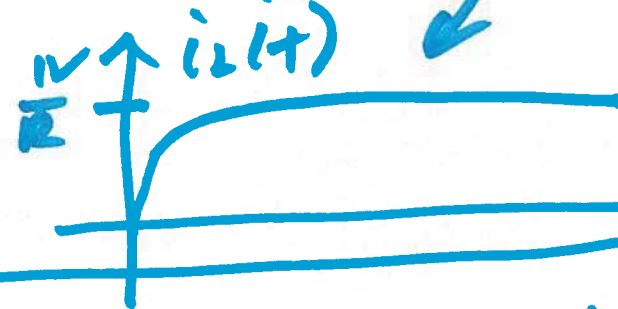
$$\lim_{x \rightarrow \infty} e^{-x} = \lim_{x \rightarrow \infty} \frac{1}{e^x} \rightarrow 0 = \frac{1}{R} \cdot (1 - e^{-t/4/R})$$



$$x(t) = x_f + (x_i - x_f) e^{-t/\tau}$$

$0 \quad (1 - 0) e^{-t/\tau}$

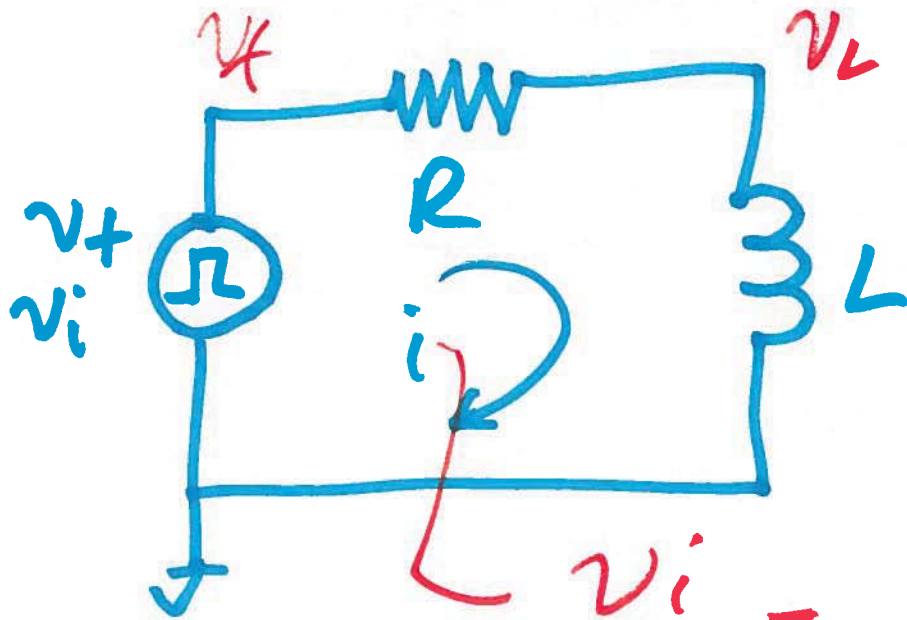

$$\tau = \frac{L}{R}$$


or

$$\tau = RC$$

$$\frac{v_i}{R} = \frac{v_f - v_L}{R}$$

$$v_L = v_f - v_i$$



$$X(t) = X_f + (X_i - X_f)e^{-t/\tau}$$

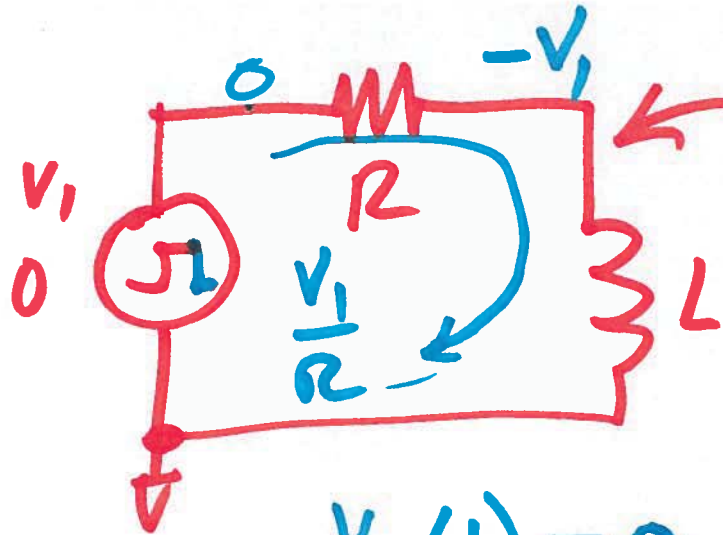

$$V_L(t) = V_f + (v_i - V_f) e^{-t/\tau}$$

$$= 0 + (v_i - 0) e^{-t/\tau}$$

$$V_L(t) = 0 + (-v_i - 0) e^{-t/\tau}$$

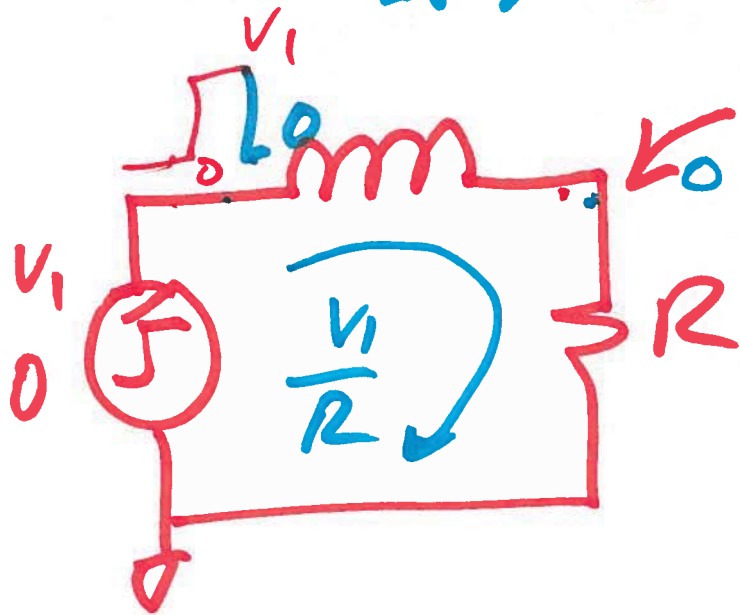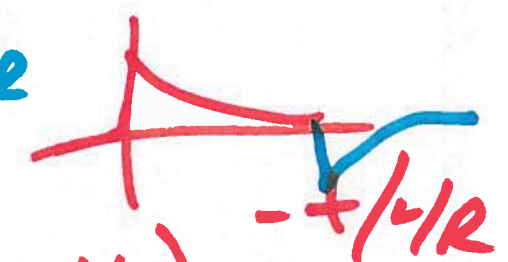

$$V_L(t) = V_f + (v_i - V_f) e^{-t/\tau}$$


$$= v_i + (0 - v_i) e^{-t/\tau}$$

$$= v_i (1 - e^{-t/\tau})$$

$$V_L(t) = 0 + (v_i - 0) e^{-t/\tau}$$

$$= v_i e^{-t/\tau}$$

7)


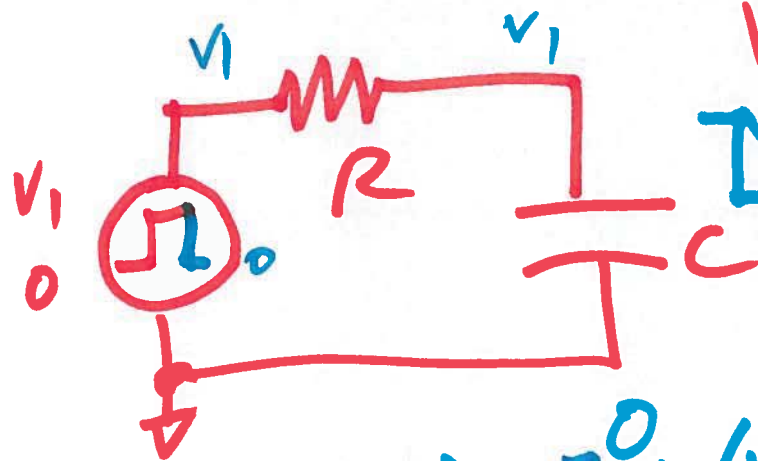


$$V_c(t) = V_f + (V_i - V_f)e^{-t/RC}$$

$$= V_f + (0 - V_i)e^{-t/RC}$$

$$v_c(t) = 0 + (V_i - 0)e^{-t/RC} = V_i(1 - e^{-t/RC})$$

$$= V_i e^{-t/RC}$$

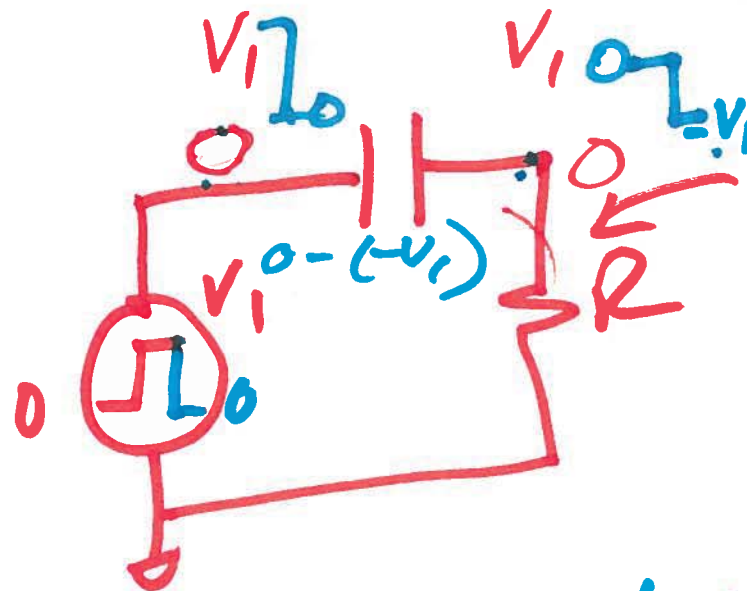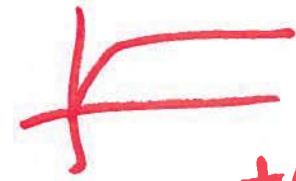


$$V_c(t) = V_f + (V_i - V_f)e^{-t/RC}$$

$$= 0 + (V_i - 0)e^{-t/RC}$$

$$V_c(t) = 0 + (-V_i + 0)e^{-t/RC}$$

$$V_R(t) = V_i e^{-t/RC}$$

$$= V_R(t) = -V_i e^{-t/RC}$$

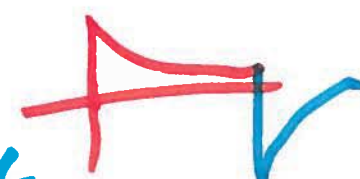

8)