

# EE 220

## Circuits 1

### Lecture 20

octave

$\times 2$   
 $\div 2$



10 N  
VS  
10 $\mu$  1,000 times faster

order of magnitude

$\times 10$   
 $\div 10$


$10 \cdot 10 \cdot 10 = 10^3$   
three orders of magnitude

$10 \cdot 10^{-6} = 10^{-5}$

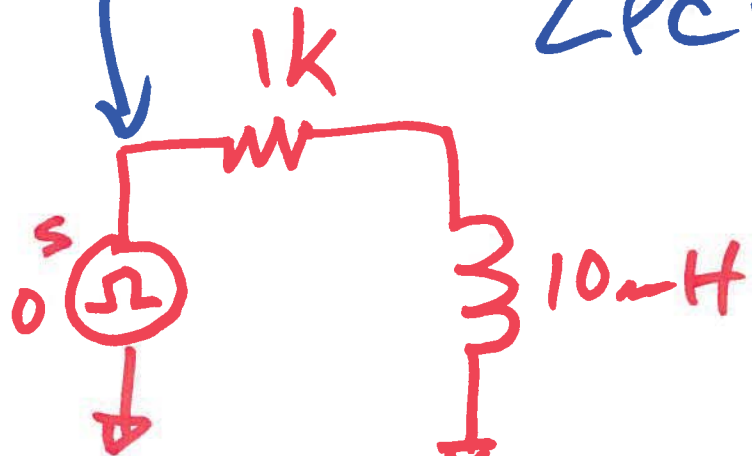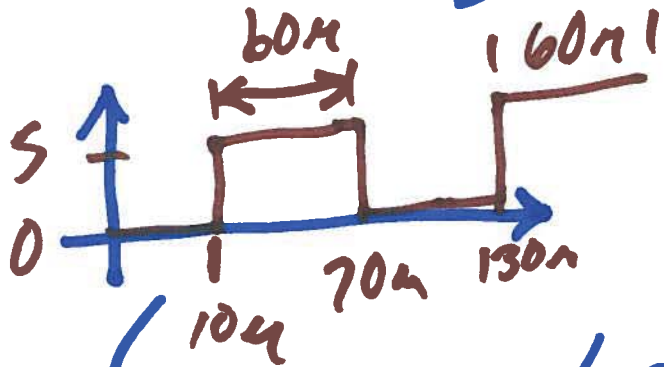

0 s 10μ 10μ 10μ 60μ 130μ

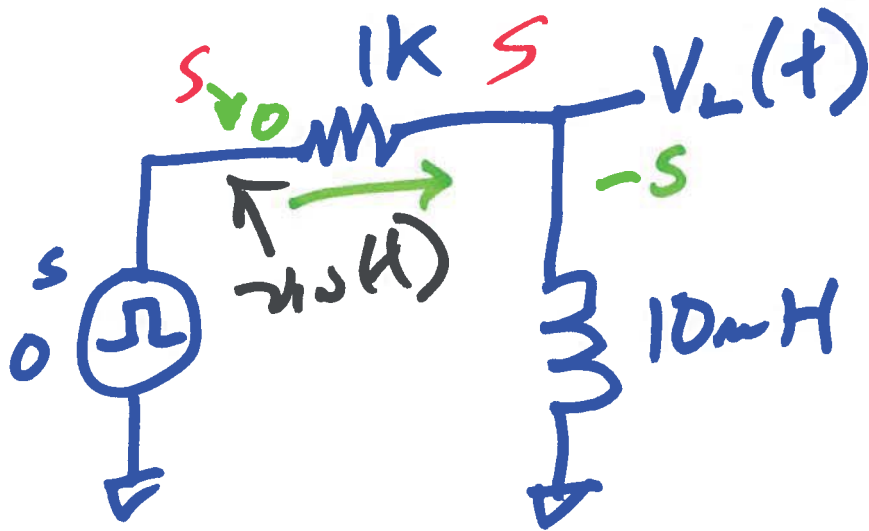
$$\tau = \frac{L}{R} = \frac{10\mu\text{H}}{1\text{k}\Omega} = \frac{10 \cdot 10^{-3}}{1 \cdot 10^3} \cdot \frac{10^{-3}}{10^{-3}} = \frac{10 \cdot 10^{-6}}{1} = 10\mu\text{s}$$





$$v_i = 5V$$

$$v_f = 0$$


$$v_L(t) = 0 + (5-0)e^{-t/\tau}$$


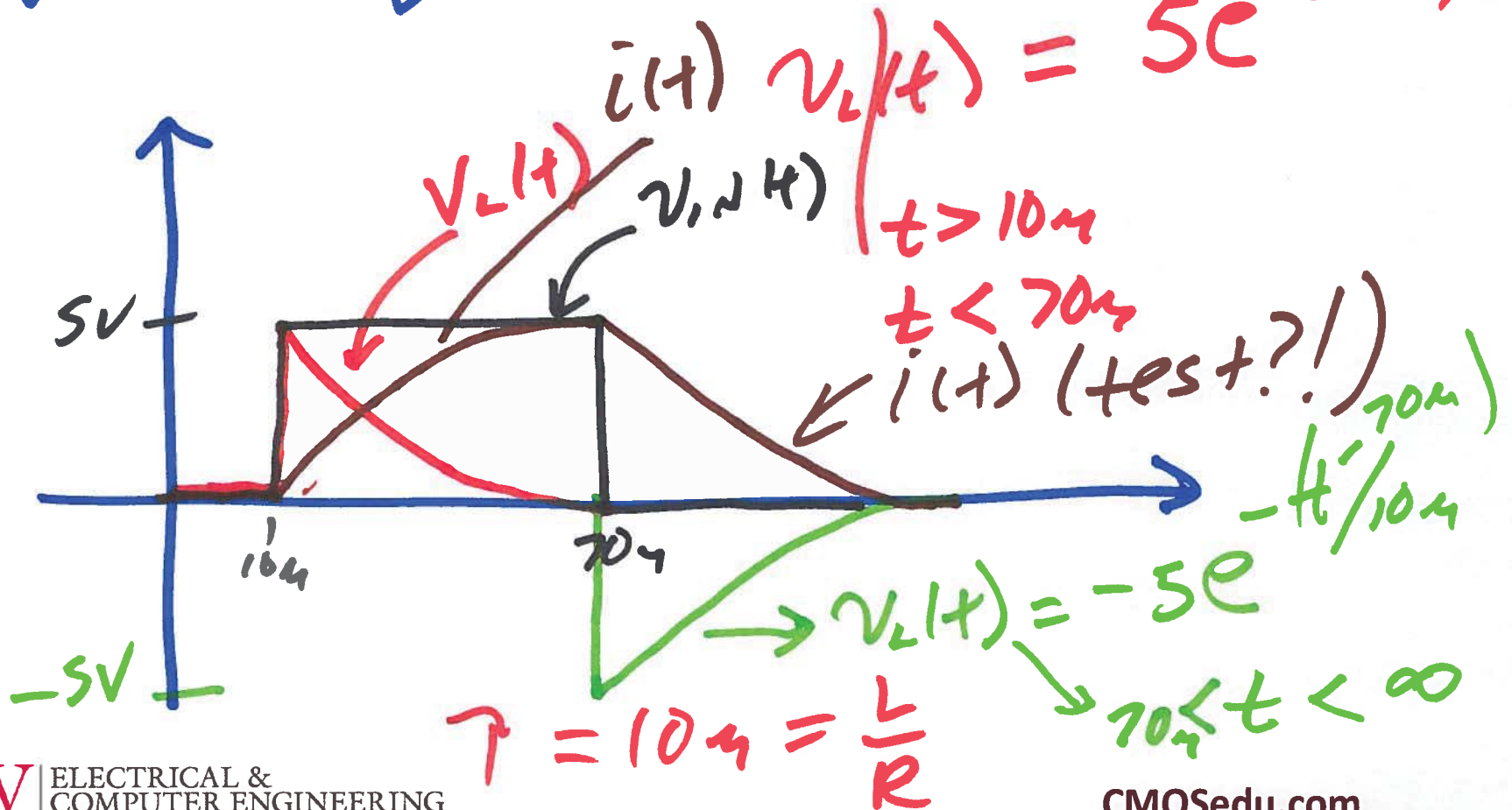


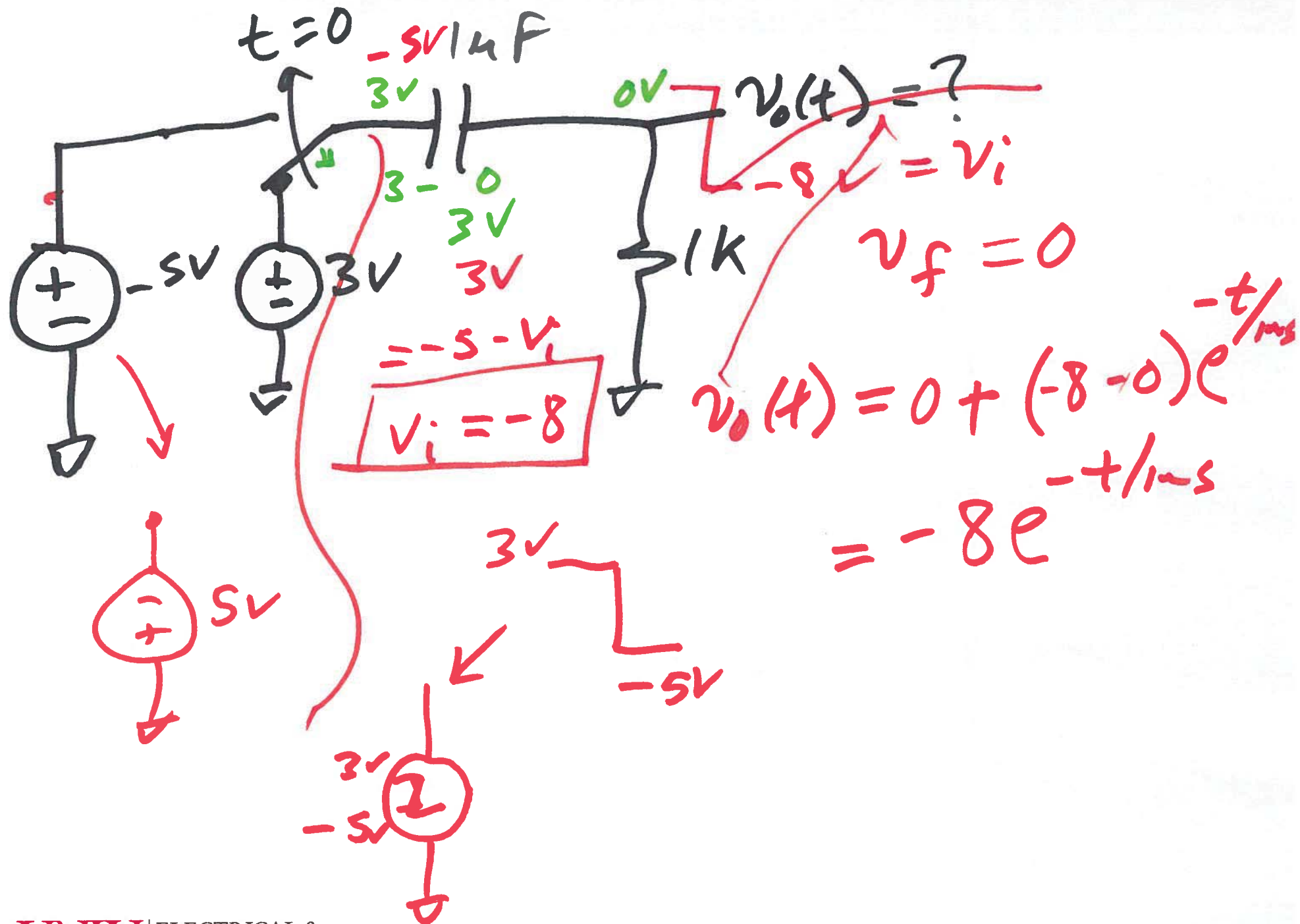

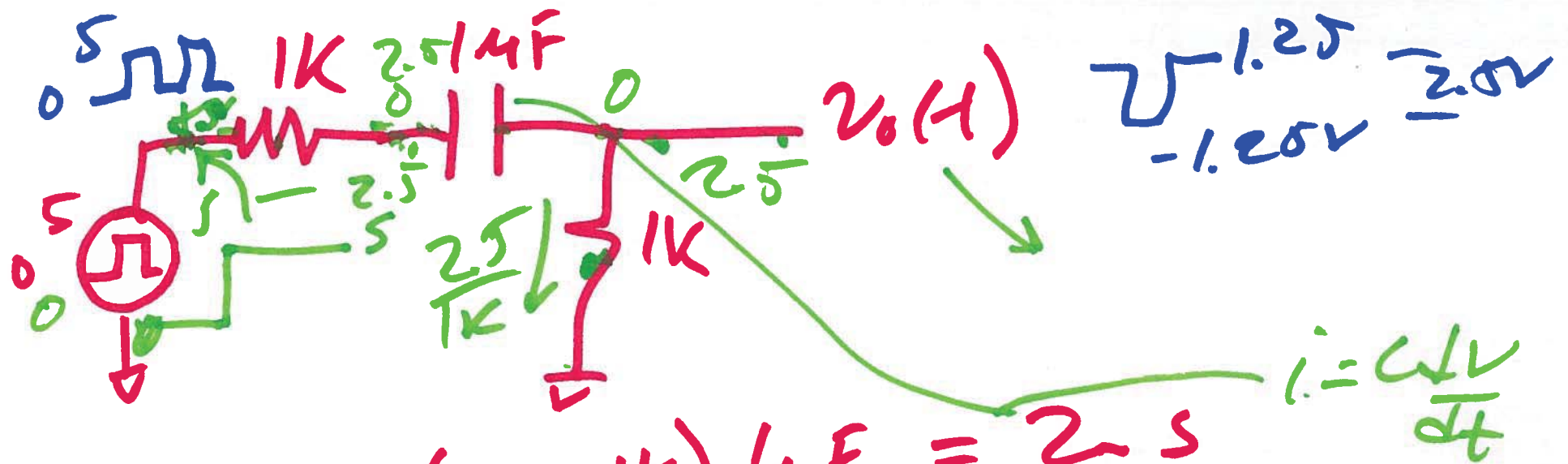

$$\tau = (1k + 1k) \cdot 1.4F = 2s$$

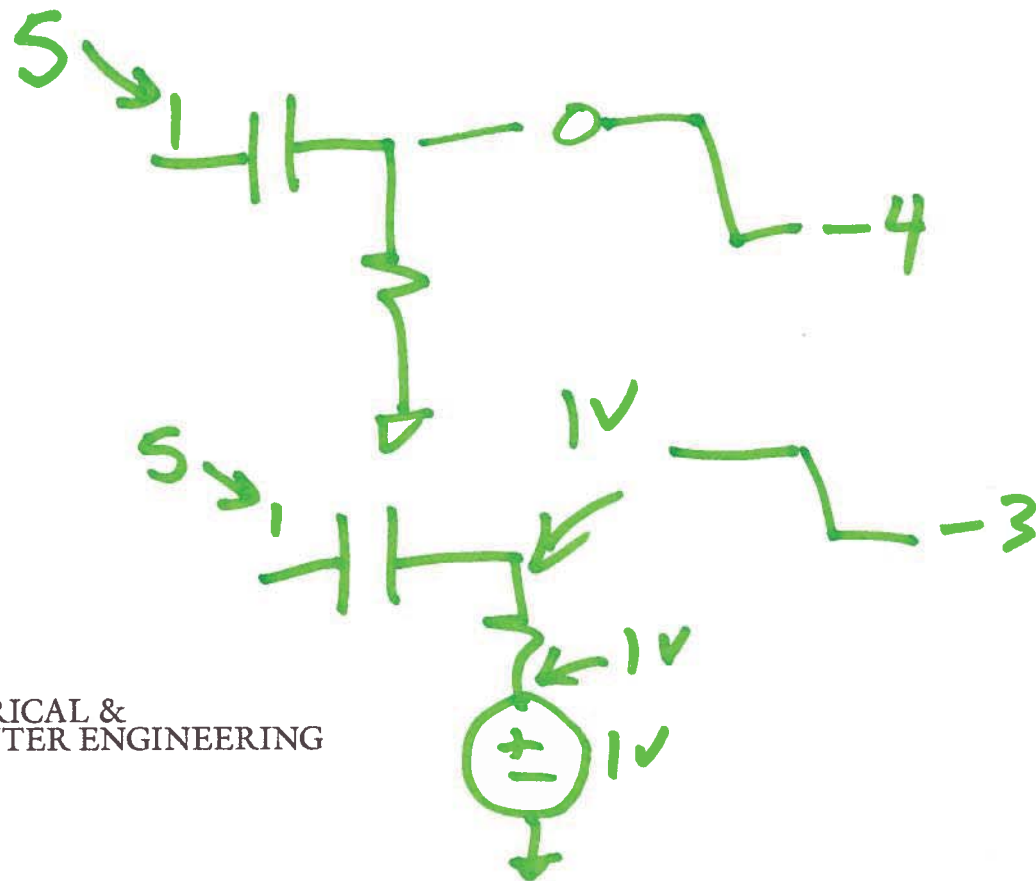

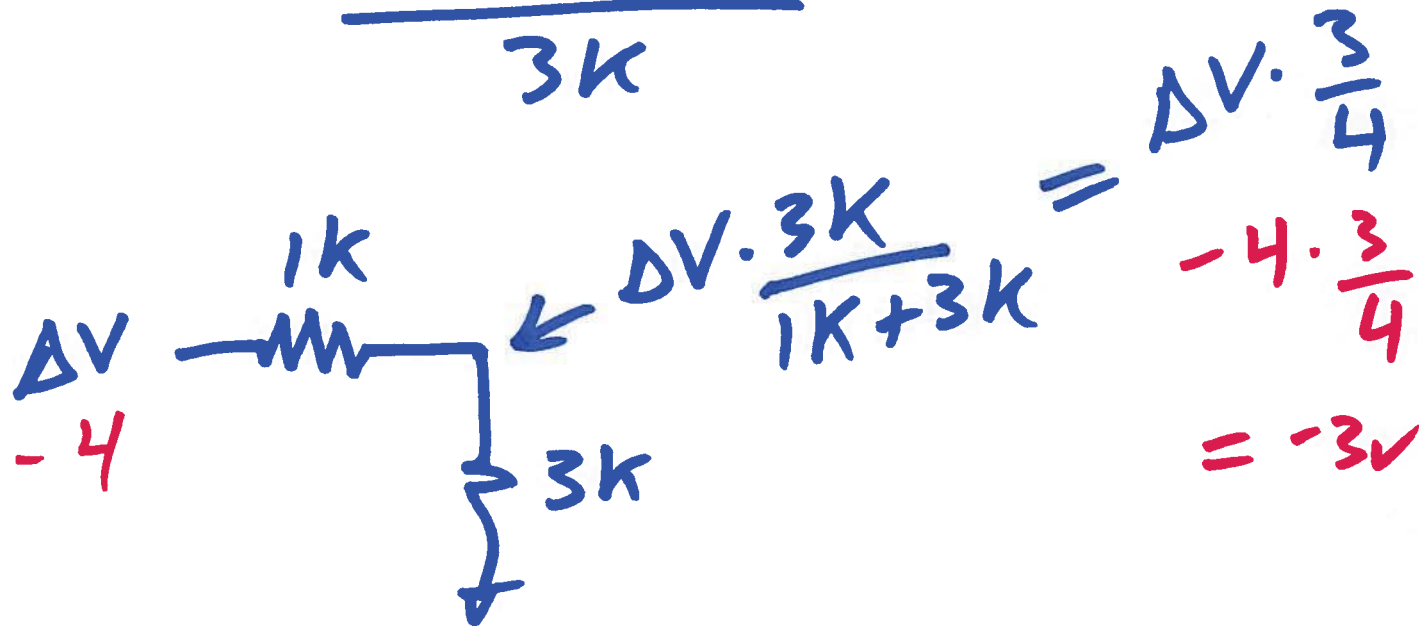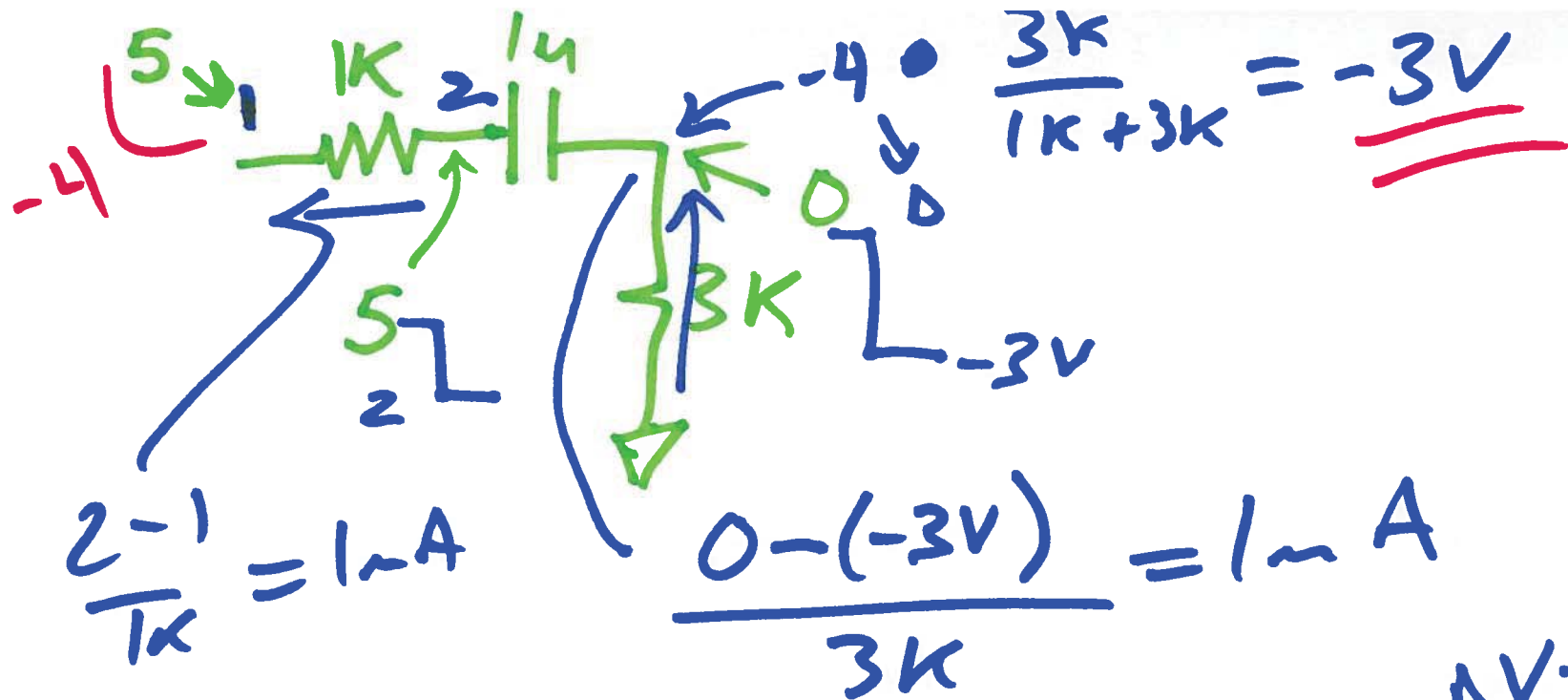

# Integrator


$$I = C \frac{dv}{dt} \Rightarrow \frac{1}{T} \int v$$

$$i_R(t) = \frac{V_{in}}{R}$$

$$\frac{I}{C}$$

$$V_{out}$$

$$= C \cdot \frac{dV_{out}}{dt}$$

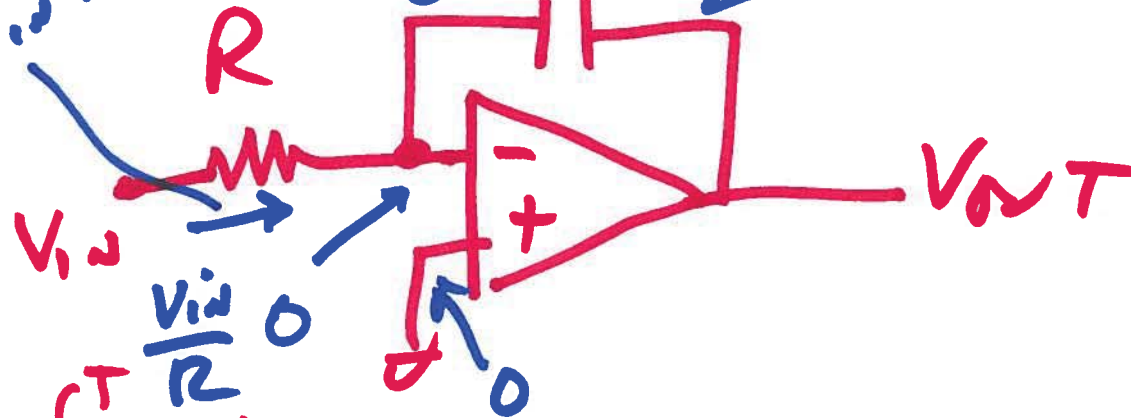


$$= -\frac{1}{C} \cdot \int_0^t i_R(t) \cdot dt = -\frac{1}{C} \cdot \int_0^t \frac{V_{in}}{R} dt + C \frac{dV_{out}}{dt} = 0$$

$$V_{out} = -\frac{1}{RC} \int_0^t V_{in} \cdot dt$$

$$t V_{in} = -RC \cdot \frac{dV_{out}}{dt}$$
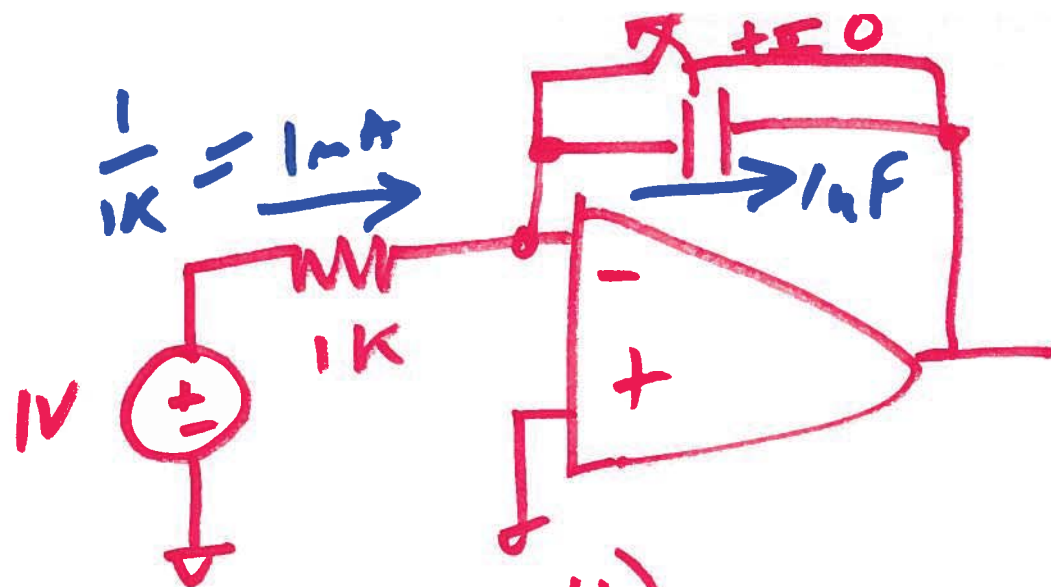
$$\int_0^t V_{in} \cdot dt = -RC \cdot \int_0^{V_{out}} dV_{out}$$



Switch opens at  $t=0$

$$\begin{aligned}
 V_{out} &= \frac{-1}{1K \cdot 1\mu} \int_0^t 1 \cdot dt \\
 &= -\frac{1}{10^{-3}} \cdot 1V \cdot t \\
 &= -\frac{1V}{1ms} \cdot t
 \end{aligned}$$

