


EE 220

Circuits 1

Lecture 21

$$i \downarrow \left\{ \begin{array}{l} + \\ - \end{array} \right. V = L \frac{di}{dt}$$

$$V_L = L \cdot \frac{d(-i(t))}{dt}$$

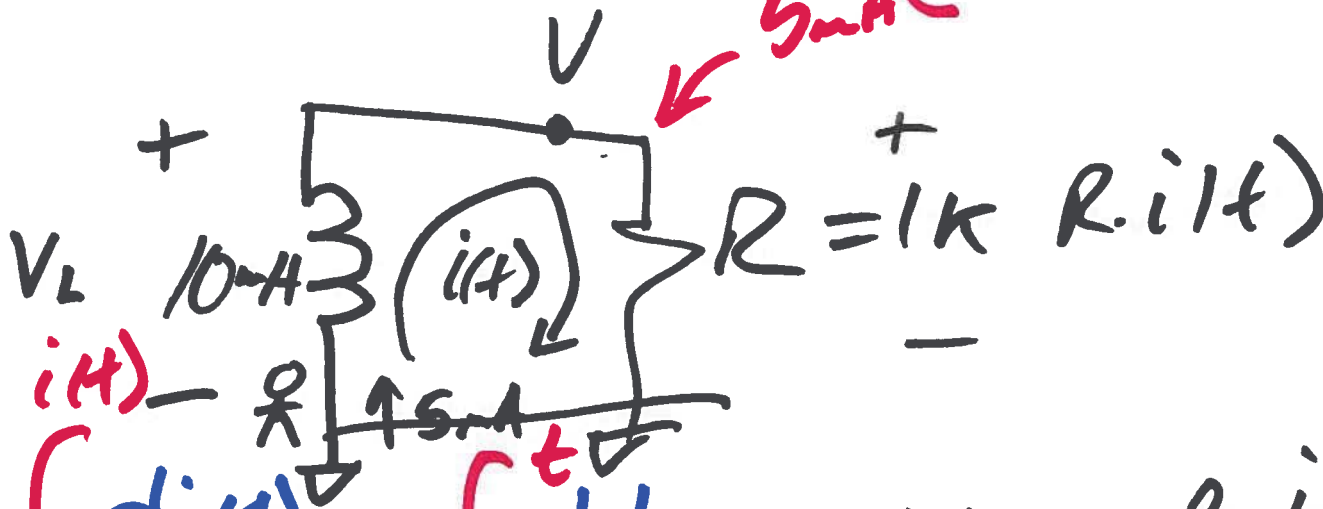

$$-\frac{L}{R} \int_{-i(0)}^{i(t)} \frac{di(t)}{i(t)} = \int_0^t dt$$

$$V_L - R \cdot i(t) = 0$$

$$-L \frac{di(t)}{dt} = R i(t)$$

1)

$$-\frac{L}{R} = -\frac{L}{R} \int_{i(0^-)}^{i(t)} \frac{di}{i} = \int_0^t dt = t$$



$$(\ln i(t) - \ln i(0^-)) = t$$


$$\ln i - \ln i(0^-) = -t/\tau$$

$$\ln \frac{i}{i(0^-)} = -t/\tau$$


$$i(t) = i(0^-) e^{-t/\tau}$$

$$i(t) = 5e^{-t/\tau}$$

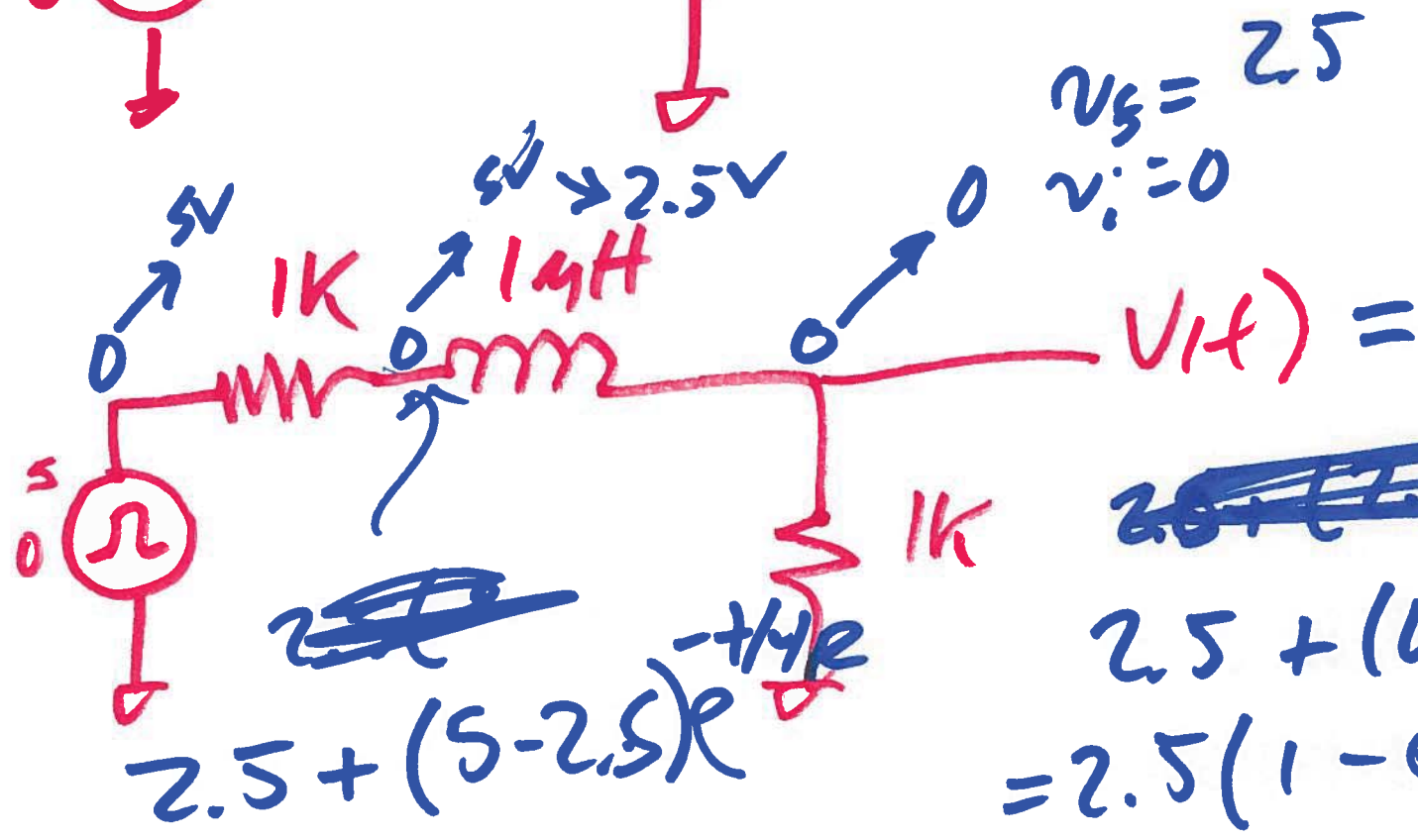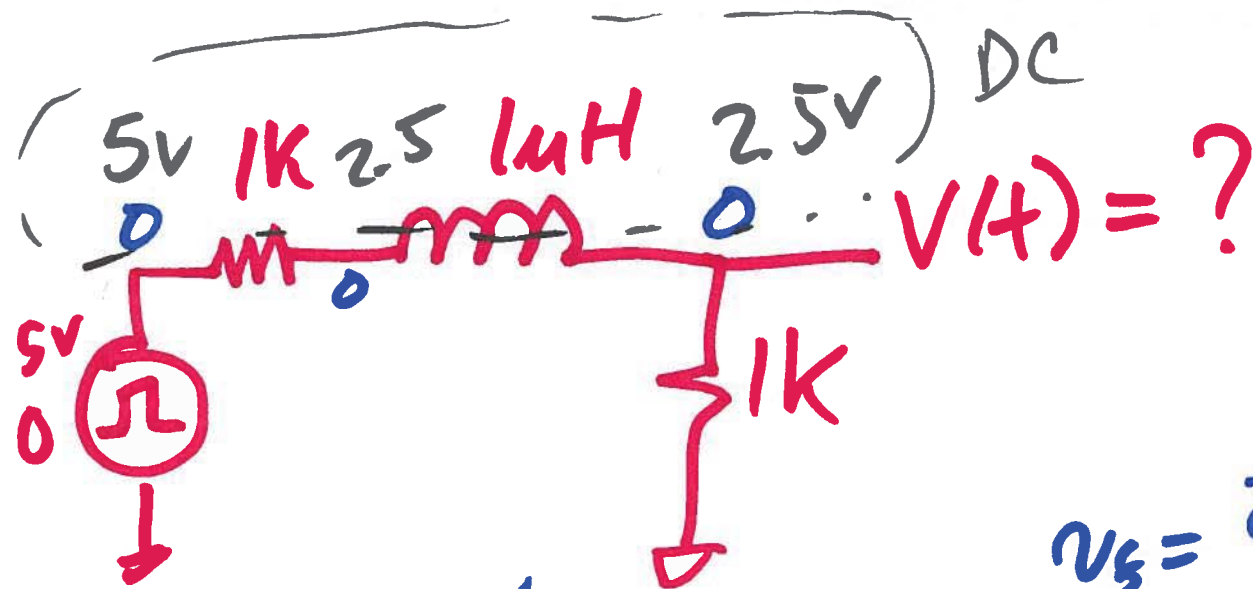

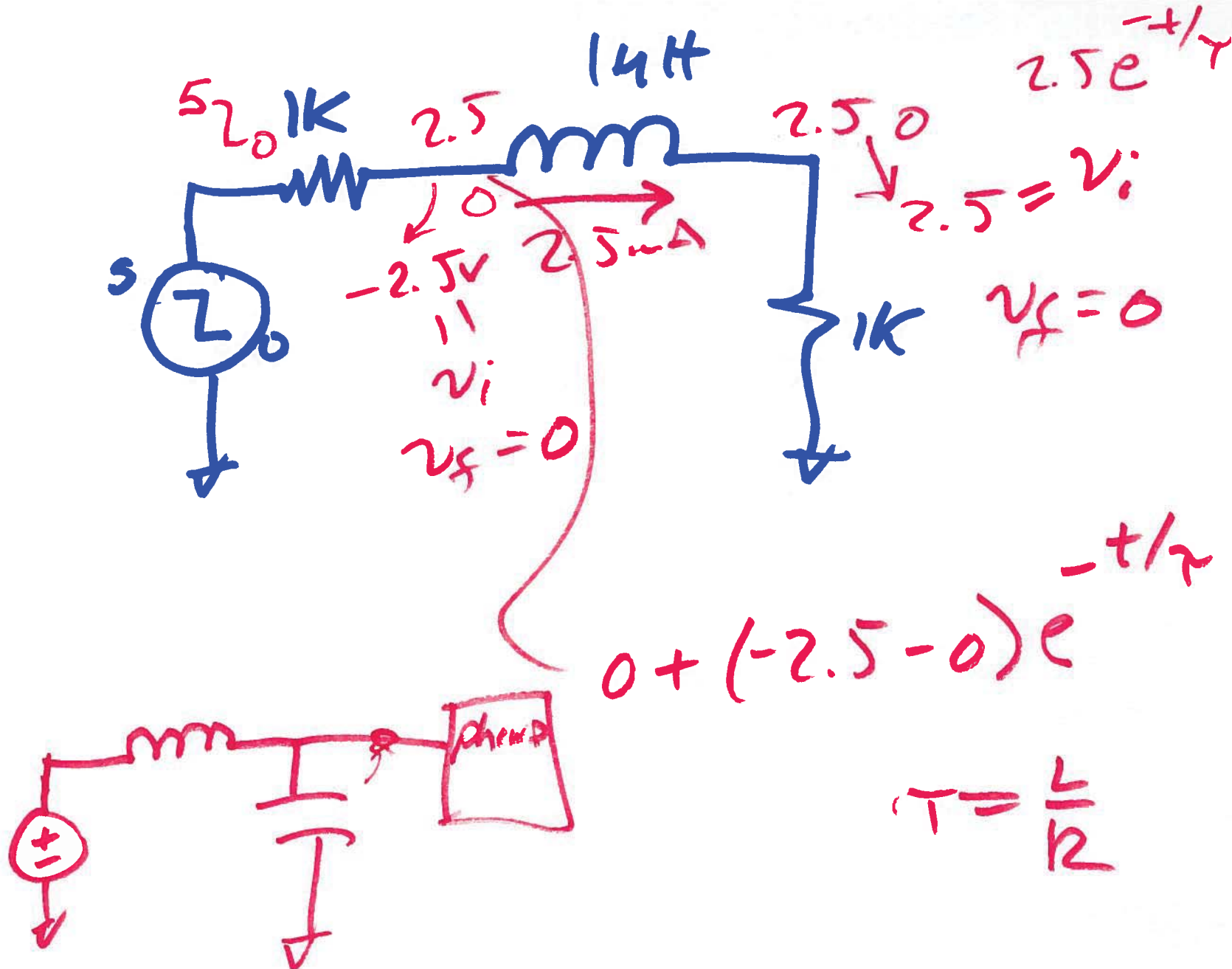

$V_p \angle 0^\circ$ AC voltages QAM

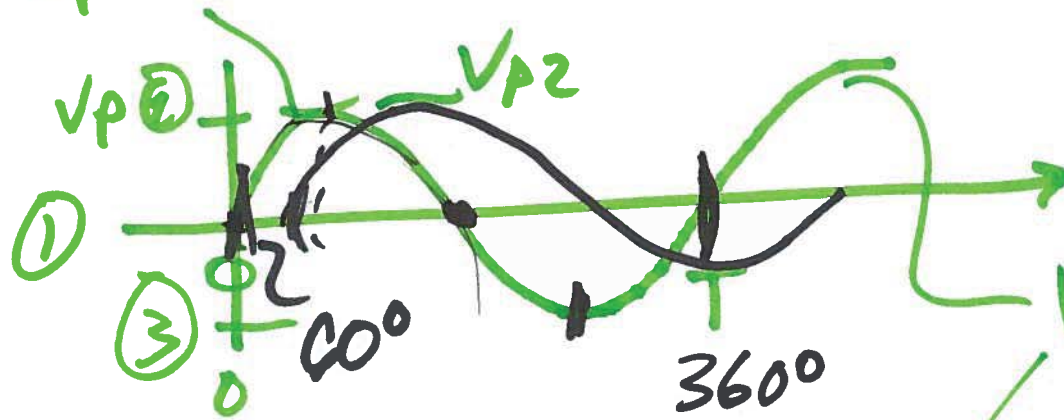



$$f = \frac{1}{T}$$


$$V_p \sin(2\pi \cdot t)$$

$$v_p \sin(360^\circ + 90^\circ)$$

$$\rightarrow V_p \sin(\underline{2\pi \cdot t} + \underline{90^\circ})$$

Def.

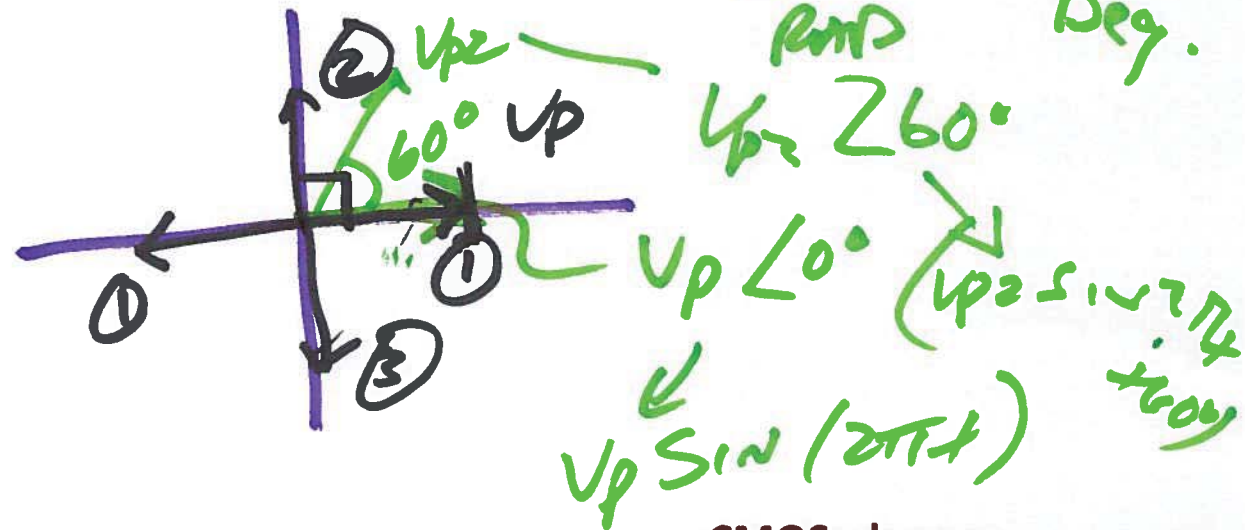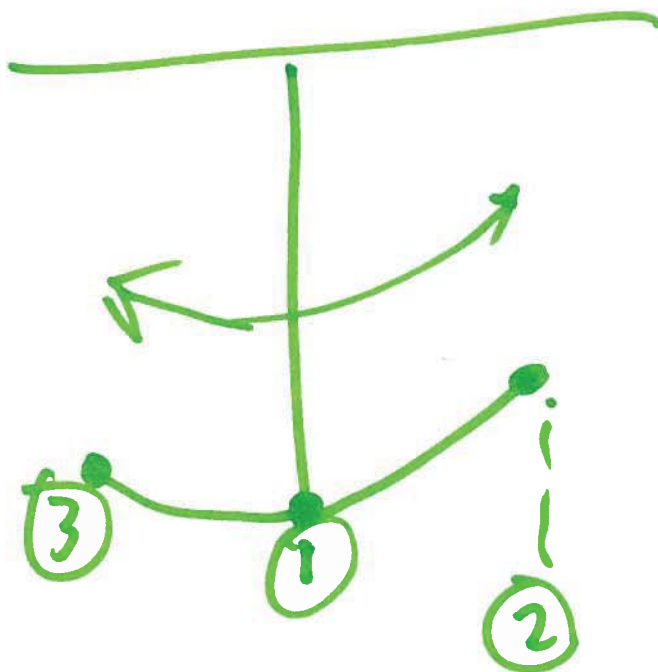

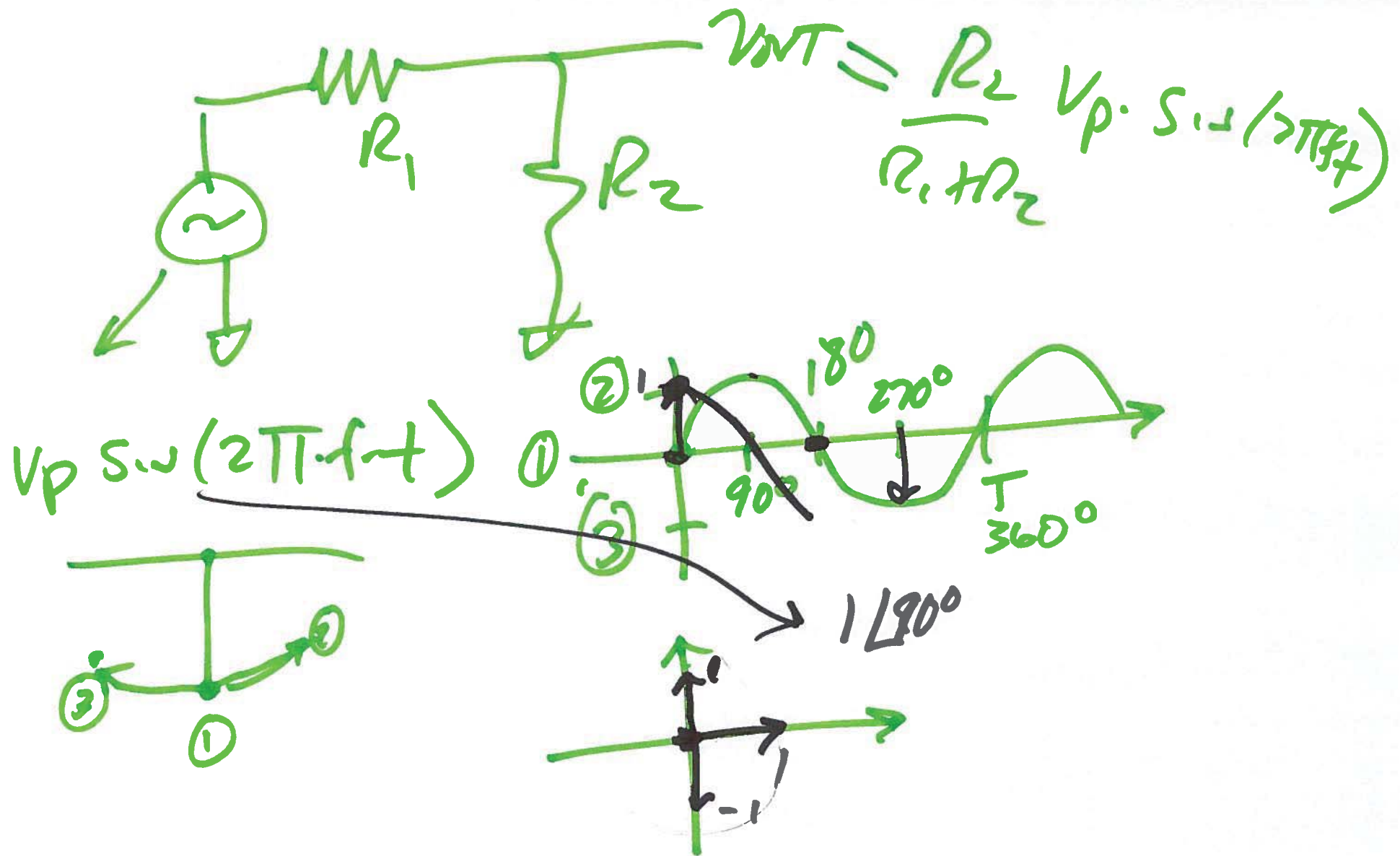

b)

Examples

$$v(t) = \cos(2\pi \cdot 60 \cdot t) \Rightarrow 1 \angle 0^\circ$$


$$= 2 \cos(2\pi \cdot 60 \cdot t) \Rightarrow 2 \angle 0^\circ$$


$$= \sin(2\pi \cdot 60 \cdot t) \Rightarrow 1 \angle 90^\circ$$

$$= 3.2 \cos(2\pi \cdot 60 \cdot t - 30^\circ) \Rightarrow 3.2 \angle -30^\circ$$

$$= 2 \sin(2\pi \cdot 60 \cdot t - 30^\circ)$$

$$\Rightarrow 2 \angle 60^\circ$$

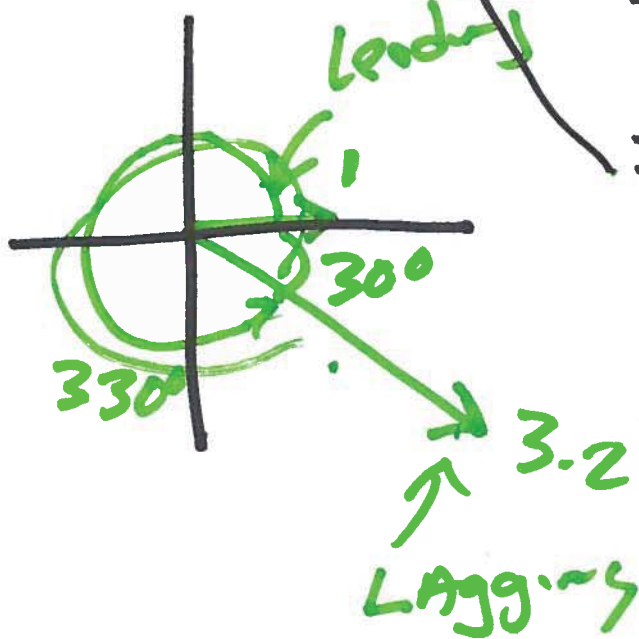

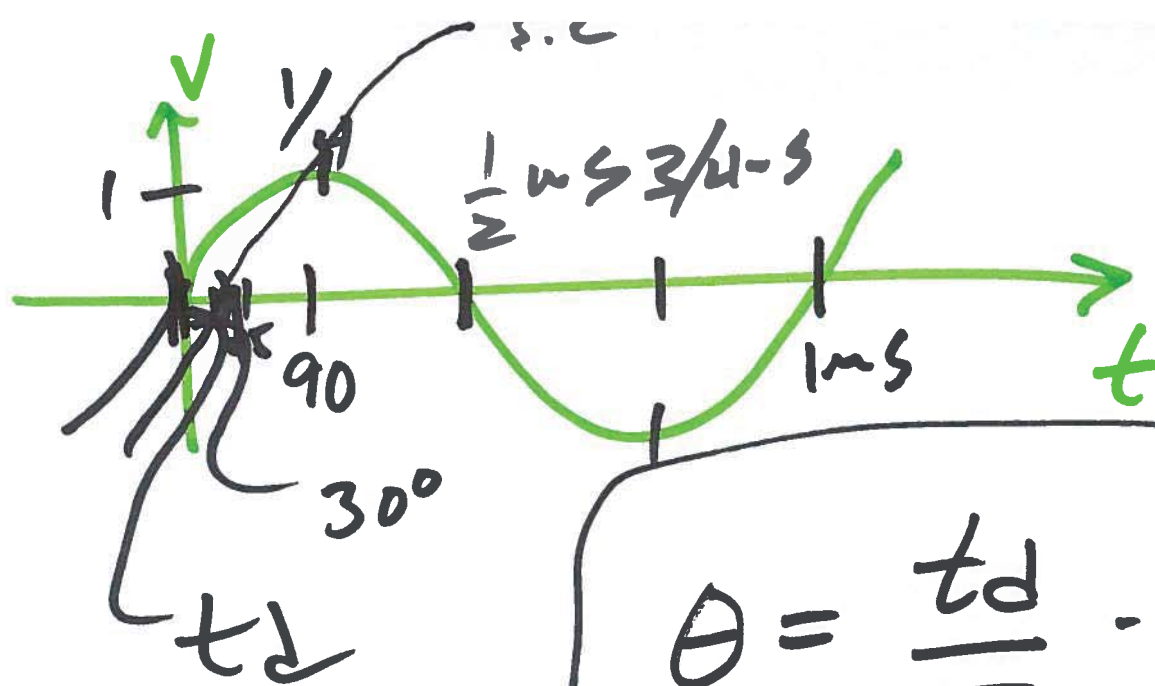

$$\theta = \frac{t_d}{T} \cdot 360$$


$$30^\circ = \frac{t_d}{1\text{ms}} \cdot 360$$


$$t_d = \frac{30}{360} \cdot 1\text{ms}$$

$$= \frac{1}{12}\text{ms}$$

$$\theta = t_d \cdot f \cdot 360$$

$$f = \frac{1}{T}$$

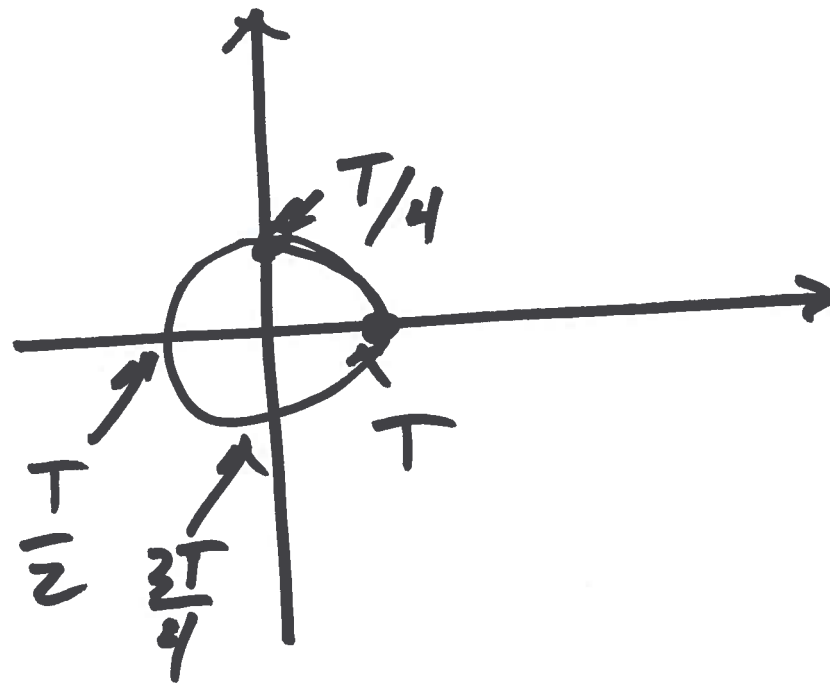

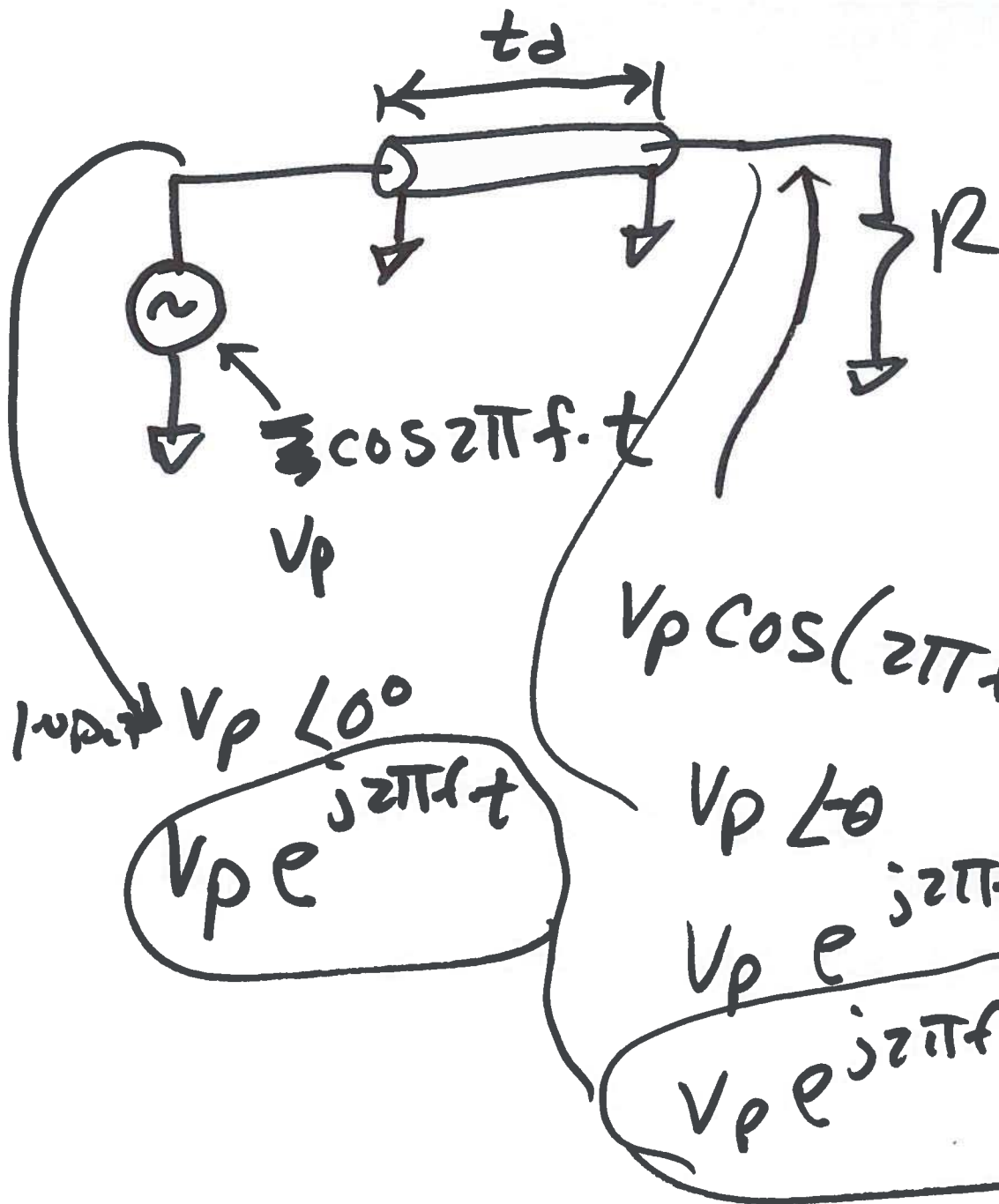

$$\theta = \frac{t_d}{T} \cdot 360$$

$$= t_d \cdot f \cdot 360$$

$$V_p \cos(2\pi f \cdot t - t_d \cdot f \cdot 360)$$

$$V_p \angle -\theta$$

$$V_p e^{j2\pi f \cdot t - \theta}$$

$$V_p e^{j2\pi f \cdot t} \cdot e^{j2\pi f \cdot (-t_d)}$$