


EE 220 circuits 1

Lecture 23

$$i = \frac{V_x + 9}{9k}$$

$$V_B = V_x - 90k \cdot i$$

$$i + \frac{V_x}{9k} + 10i = 0$$

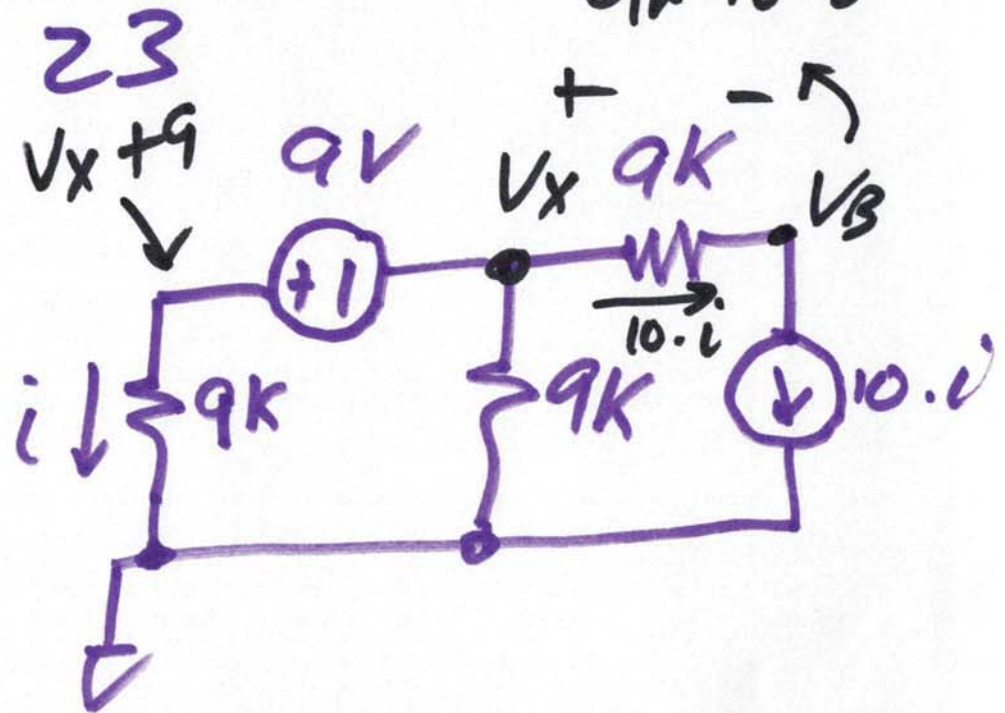


$$V_B = V_x - 10V_x \neq 90 = \frac{-99}{12} + \frac{990}{12}$$

$$\frac{V_x + 9}{9k} + \frac{V_x}{9k} + \frac{10(V_x + 9)}{9k} = 0$$

$$12V_x = -99 \quad V_x = \frac{-99}{12}$$

Phasor $\Rightarrow M \angle \theta$ (polar) $X|_{Re} = M \cos \theta$

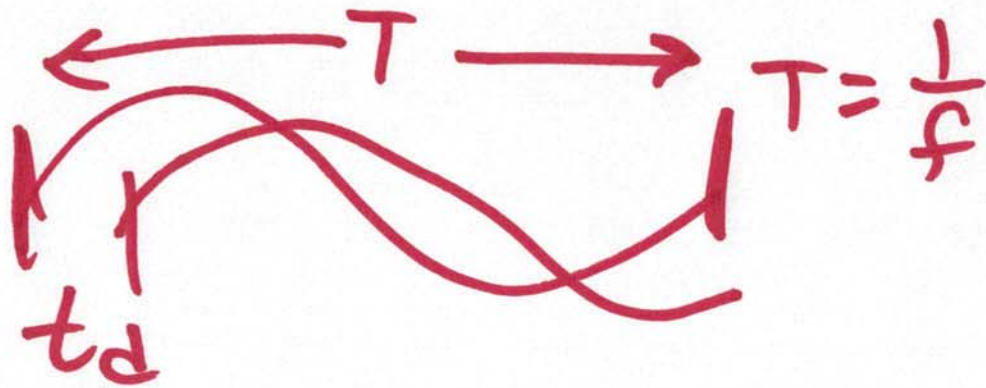


$$Y|_{Im} = M \sin \theta$$

$$x + jy \text{ (Rect)}$$

$$\sqrt{x^2 + y^2}$$

$$\angle = \tan^{-1} \frac{y}{x}$$

$$\theta = \frac{t_d}{T} \cdot 360$$

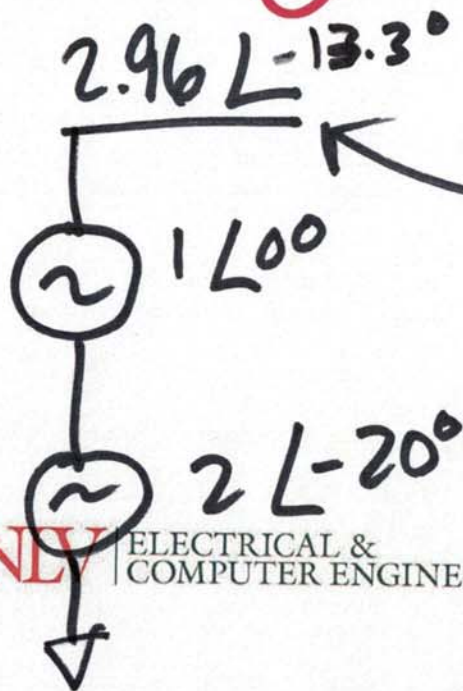


$$1 \angle 0^\circ + 2 \angle -20^\circ$$

$$2 \cdot \cos(-20^\circ) \quad 2 \cdot \sin(-20^\circ)$$

$$1 + j0 + 1.88 + j(-.68)$$


$$2.88 + j(-.68)$$

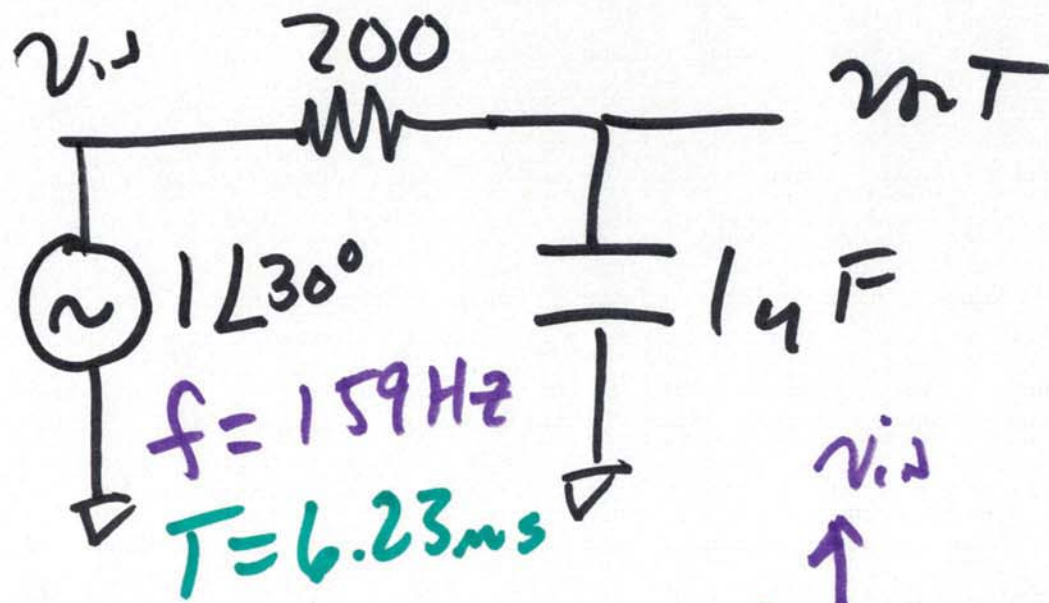

Sketch $2mT$ & v_o on same plot

$$30^\circ = \frac{t_d}{6.23 \text{ ms}} \cdot 360$$

$$t_d = .524 \text{ ms}$$

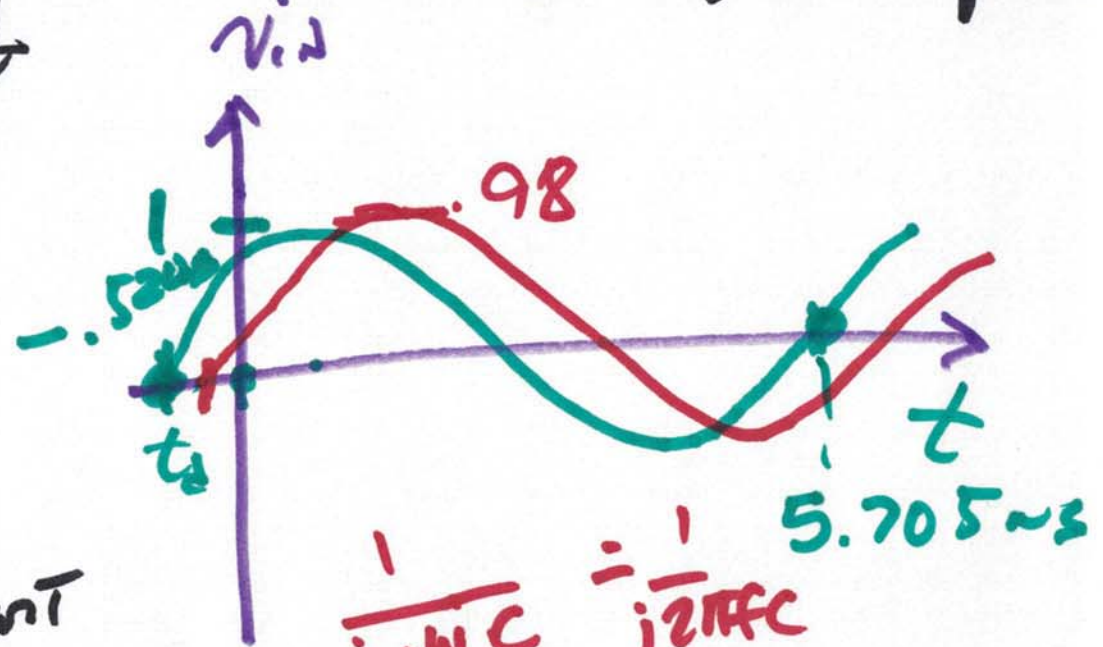

$$200 + j0 \text{ mT}$$

$$\frac{1}{j \cdot 2\pi \cdot 159 \cdot 10^{-6}} = -j10^3 + 0$$

3)

$$\tan^{-1} \frac{-10^3}{0} \quad V_{NT} = 1 \angle 30^\circ \cdot \frac{0 - j \cdot 10^3}{-j \cdot 10^3 + 200}$$

$$= -\tan^{-1} \frac{10^3}{0} \quad -\tan^{-1} \frac{10^3}{0} + j(10^3) = 10^3 \angle -90^\circ$$

$$V_{NT} = \frac{1 \angle 30^\circ \cdot 10^3 \angle -90^\circ}{1019 \angle -78.7^\circ}$$

$$\sqrt{200^2 + 10^3^2} = 1019$$


$$\angle \tan^{-1} \frac{-10^3}{200} = -78.7^\circ$$

$$V_{NT} = \frac{1 \cdot 10^3 \angle 18.7}{1019} \quad \frac{A \angle \theta_1 \cdot B \angle \theta_2}{C \angle \theta_3} = \frac{A \cdot B \angle \theta_1 + \theta_2}{C \angle \theta_3}$$

$$= \frac{AB}{C} \angle \theta_1 + \theta_2 - \theta_3$$

$$= \frac{1 \cdot 10^3}{1019} \angle 18.7 - (-78.7)$$

$$= 98 \angle 18.7^\circ$$

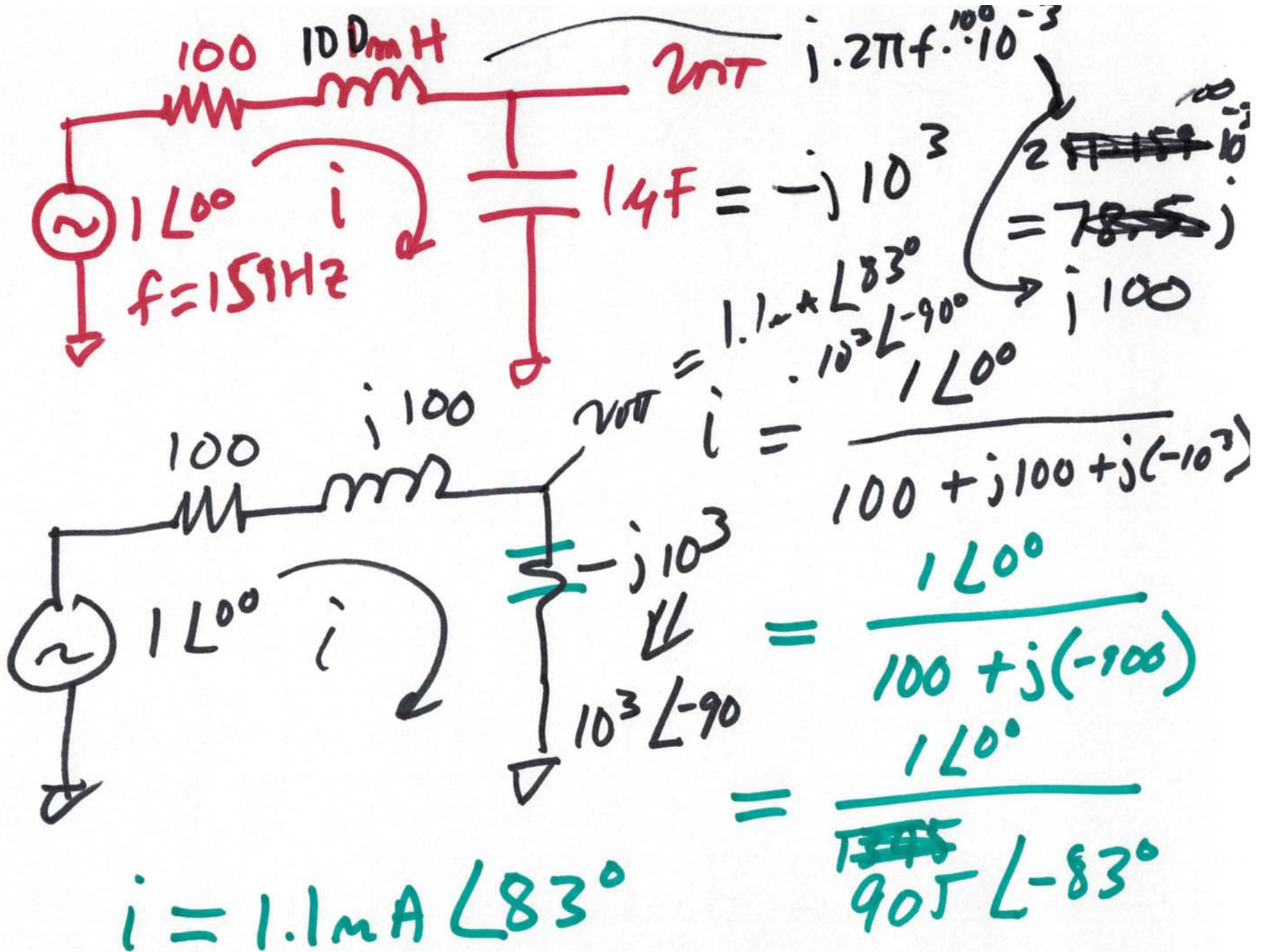

5)