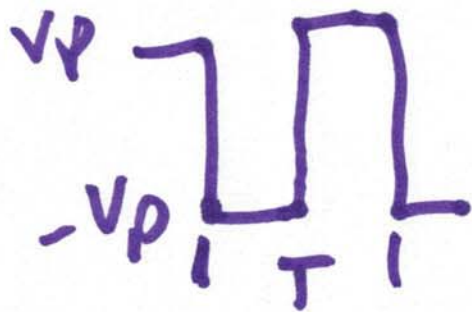


EE 220

Circuits 1

Lecture 25

find the RMS value




$$f = \frac{1}{T}$$

$$\sqrt{\frac{1}{T} \int_0^T V_p^2 \cdot dt} = V_{rms}$$

$$\sqrt{\frac{1}{T} V_p^2 (T - 0)} = V_{rms}$$
$$\underline{\underline{= V_p}}$$

Decibels

$$100 = 10^2$$

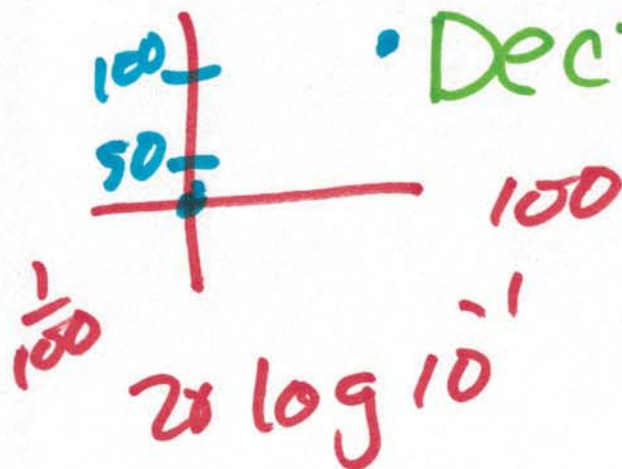

$$dB = 20 \log \frac{V_{out}}{V_{in}}$$

$$20 \log 10^2$$

logarithm used to 40 log 10

$$0.1 \rightarrow -20 dB$$

$$10^{-1}$$

$$0.01 \rightarrow -40 dB$$

Compare / display

Big things with

$$\frac{dB}{dB}$$

$$0 dB$$

Small things

$$5 \rightarrow 14 dB$$

$$2 \rightarrow 6 dB$$

$$\frac{V_{out}}{V_{in}} = 1$$

$$\frac{V_{out}}{V_{in}} = 10$$

$$20 dB$$

$$\frac{V_{out}}{V_{in}} = 100 \rightarrow 40 dB$$

$$1000 \rightarrow 60 dB$$

$$10,000 \rightarrow 80 dB$$

$$\frac{1}{100} \rightarrow -40 \text{ dB}$$

$$\frac{1}{10} \rightarrow -20 \text{ dB}$$

$$\frac{1}{2} \rightarrow -6 \text{ dB}$$

$$\frac{1}{\sqrt{2}} \rightarrow -3 \text{ dB}$$

order of
magnitude

20 dB

x10

two orders of
mag

40 dB

x100

$$50 \rightarrow 34 \text{ dB}$$



$$\log a \cdot b =$$

$$\log a + \log b$$

CMOSedu.com

$$\begin{array}{ll} 2 \rightarrow 6 \text{ dB} & 10 \rightarrow 20 \text{ dB} \\ \sqrt{2} \rightarrow 3 \text{ dB} & 1 \rightarrow 0 \text{ dB} \\ 100 \rightarrow 40 \text{ dB} & 5 \rightarrow 14 \text{ dB} \\ 1000 \rightarrow 60 \text{ dB} & \end{array}$$

logarithmic axis

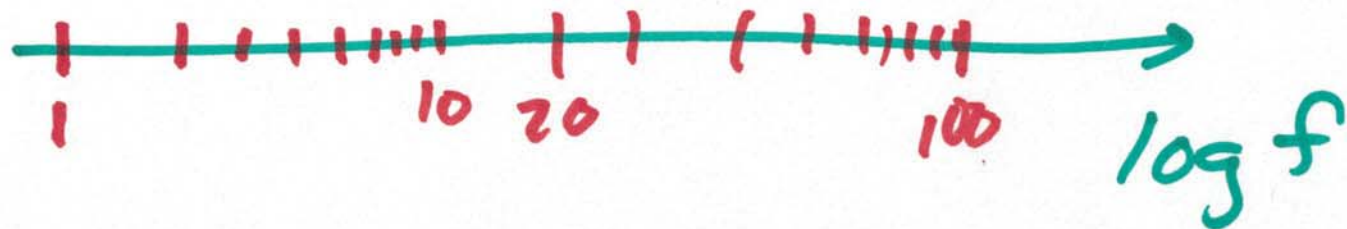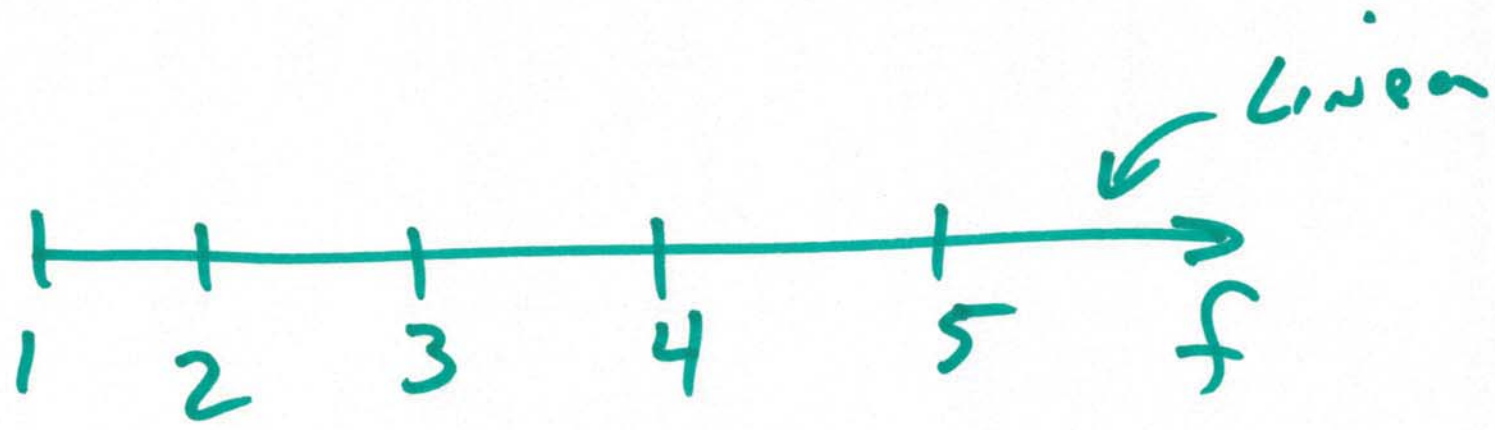



Power

$$20 \log \frac{V_{out}}{V_{in}}$$

$$10 \log \frac{V_{out}^2/R}{V_{in}^2/R}$$

$$10 \text{ dB} = 10 \log \frac{P_{out}}{P_{in}}$$

$$10 \log 10^1 = 10 \text{ dB}$$

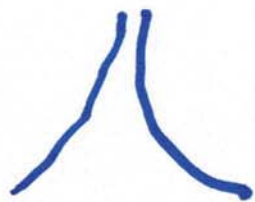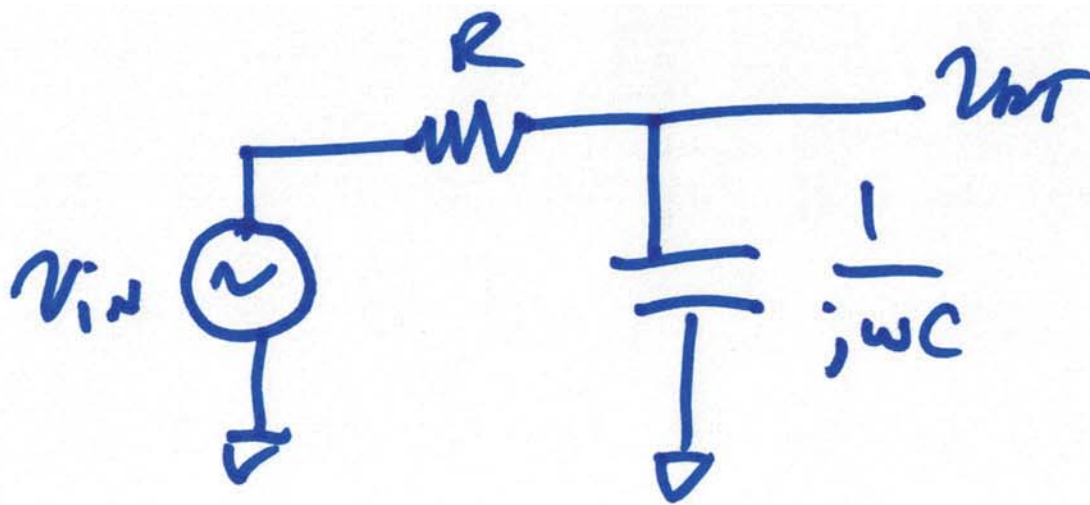

pole

$$f_{3dB} = \frac{1}{2\pi RC}$$

$$v_{out} = v_{in} \cdot \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R}$$

$$\frac{v_{out}}{v_{in}} = \frac{1}{1 + j2\pi f RC}$$

$$= \frac{1}{1 + j \frac{f}{\frac{1}{2\pi RC}}} = \frac{1}{1 + j \frac{f}{f_{3dB}}}$$

$$\frac{V_{in}}{V_{out}} = \frac{1}{1 + j2\pi fRC}$$

$$|a + jb| = \sqrt{a^2 + b^2}$$

$$\angle a + jb = \tan^{-1} \frac{b}{a}$$

$$\angle \frac{1}{a + jb} = -\tan^{-1} \frac{b}{a}$$

$$\frac{1}{a + jb} \cdot \frac{a - jb}{a - jb} = \frac{a}{a^2 + b^2} + j \frac{-b}{a^2 + b^2}$$

$$|\frac{1}{a + jb}| = \sqrt{\frac{a^2}{(a^2 + b^2)^2} + \frac{(-b)^2}{(a^2 + b^2)^2}}$$

$$= \sqrt{\frac{a^2 + b^2}{(a^2 + b^2)^2}}$$

$$\sqrt{\frac{1}{a^2 + b^2}}$$

Complex Conjugate

$$(jb)(-jb) = -1 \cdot -1 \cdot b^2 = b^2$$

$$|\frac{1}{a+ib}| = \frac{1}{\sqrt{a^2+b^2}}$$

$$\angle \frac{1}{a+ib} = -\tan^{-1} \frac{b}{a}$$

$$\rightarrow \left| \frac{a+ib}{c+id} \right| = \frac{\sqrt{a^2+b^2}}{\sqrt{c^2+d^2}}$$

$$\text{Angle} \rightarrow \angle \frac{a+ib}{c+id} = \tan^{-1} \frac{b}{a} - \tan^{-1} \frac{d}{c}$$

$$\frac{v_{out}}{v_{in}} = \frac{1}{1 + j2\pi fRC} = \frac{1}{1 + j \frac{f}{f_{3dB}}}$$

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{1}{\sqrt{1^2 + (2\pi fRC)^2}} = \frac{1}{\sqrt{1 + \left(\frac{f}{f_{3dB}}\right)^2}}$$

$$\angle \frac{v_{out}}{v_{in}} = -\tan^{-1} 2\pi fRC$$


$$= -\tan^{-1} \frac{f}{f_{3dB}}$$

$$\frac{1}{\sqrt{2}} \rightarrow -3dB$$

$$f_{3dB} = \frac{1}{2\pi RC}$$

$$= \frac{1}{2\pi \cdot 200 \cdot 10^{-6}}$$

$$= 796 \text{ Hz}$$

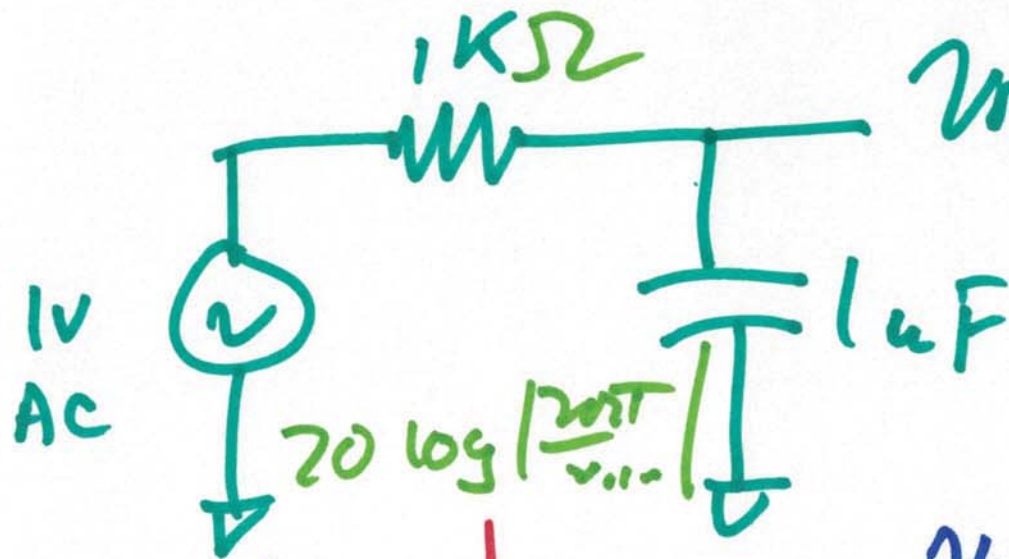

$$V_{out} = V_{in} \cdot \frac{1/j\omega C}{1/j\omega C + R}$$


$$f_{3dB} = \frac{1}{2\pi RC} = 796 \text{ Hz}$$

$\downarrow$ 1k $\downarrow$ 1μF

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + \left(\frac{f}{796} \right)^2}}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + j2\pi RC \cdot f}$$
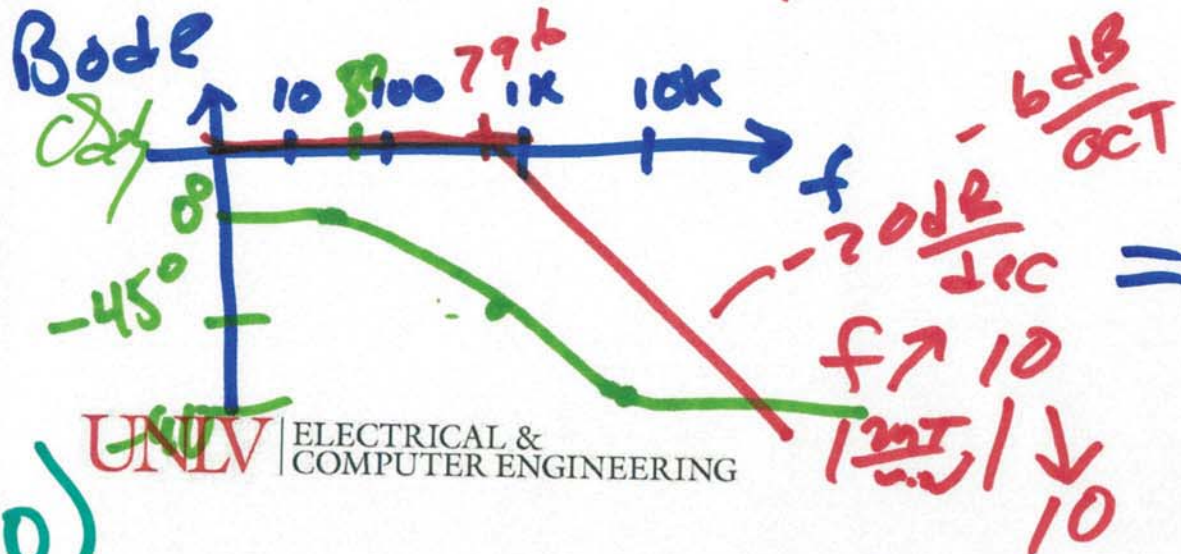
$$\angle \frac{V_{out}}{V_{in}} = -\tan^{-1} \frac{f}{796}$$



$$= \frac{1}{1 + j \frac{f}{796}}$$

$$= \frac{1}{1 + j(1.256 \mu s)f}$$

$$|\frac{V_{out}}{V_{in}}| = -8.8 \text{ dB} \rightarrow -8.8 = 20 \log \frac{V_{out}}{V_{in}}$$

$$\angle = -67.0^\circ$$

$$\frac{V_{out}}{V_{in}} = 10^{-8.8/20} = .363$$


$$T = 500 \mu s$$

$$360 = t_d$$

$$67 = \frac{t_d}{500 \mu s} \cdot 360$$


$V_{in} = 2V$ peak @ 2kHz


Sketch V_{out} & V_{in}

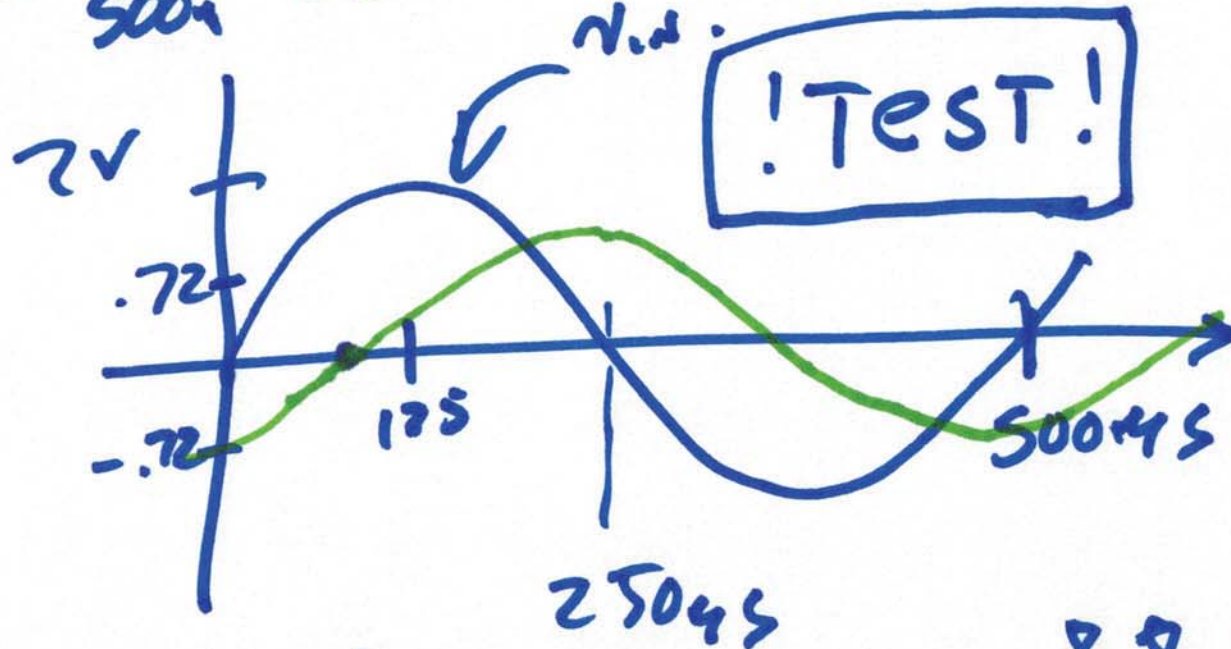

$$V_{out} = 2 \cdot .363 = .72$$
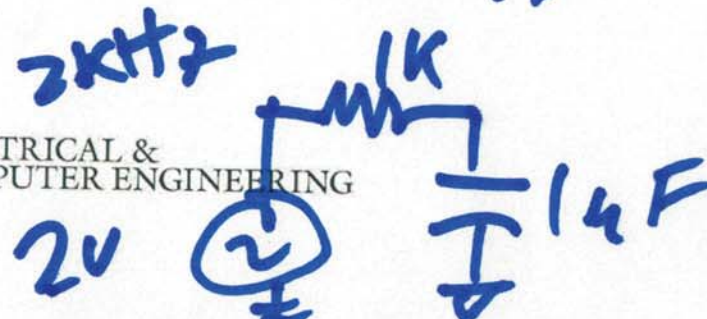
$$-8.8 = 20 \log \frac{V_{out}}{V_{in}}$$



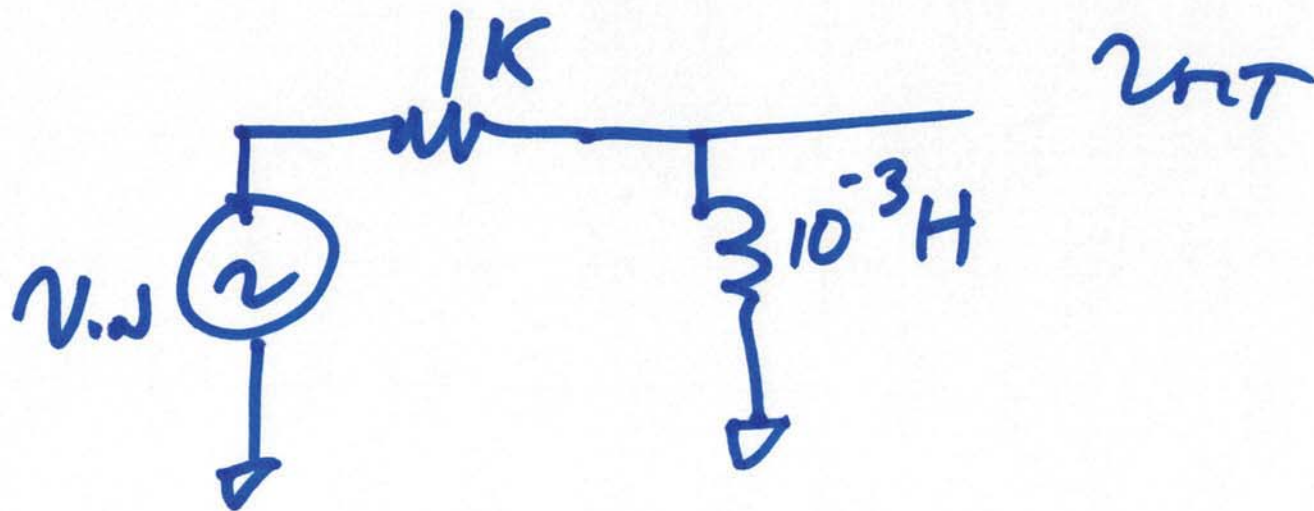

imped of inductor

$$\begin{aligned}
 \tan^{-1} \frac{2\pi f \cdot 10^{-3}}{0} \cdot \frac{v_L}{v_w} &= \frac{0 + j2\pi f \cdot 10^{-3}}{1000 + j2\pi f \cdot 10^{-3}} \\
 - \tan^{-1} \frac{2\pi f \cdot 10^{-3}}{1000} \cdot \frac{v_L}{v_w} &= \frac{\sqrt{0^2 + (2\pi f \cdot 10^{-3})^2}}{\sqrt{1000^2 + (2\pi f \cdot 10^{-3})^2}} \\
 &= \frac{2\pi f \cdot 10^{-3}}{\sqrt{1000^2 + (2\pi f \cdot 10^{-3})^2}}
 \end{aligned}$$

$$f_z = 0$$

$$f_p \Rightarrow 1000 = \frac{1}{2\pi f \cdot 10^{-3}}$$

