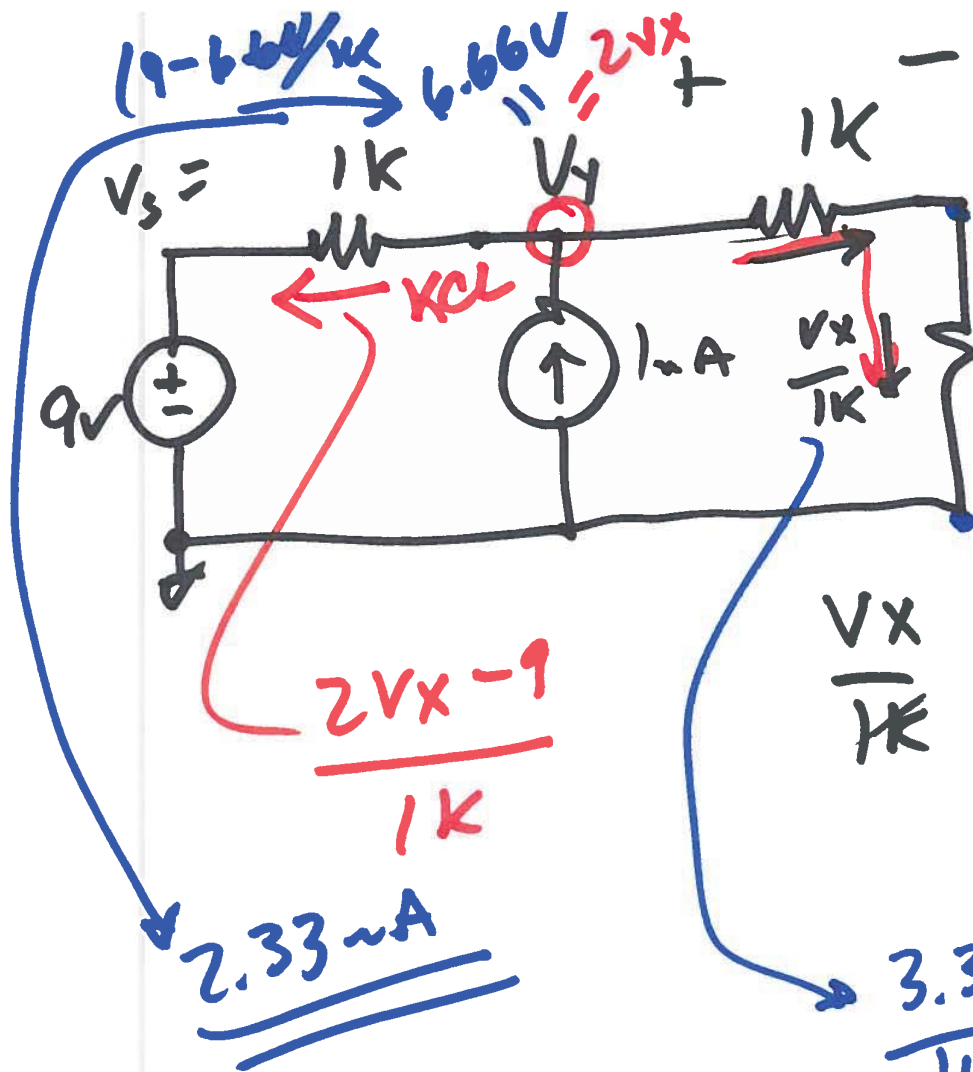




$$\text{KCL } \frac{2V_x - 9}{1K} + \frac{V_x}{1K} = 1mA$$

$$2V_x - 9 + V_x = 1V$$

$$3V_x = 10$$


$$V_x = \frac{10}{3}$$

$$\underline{\underline{V_x = 3.33V}}$$

$$\frac{V_x}{1K} = \frac{V_y - V_x}{1K}$$

$$\underline{\underline{V_y = 2V_x}}$$
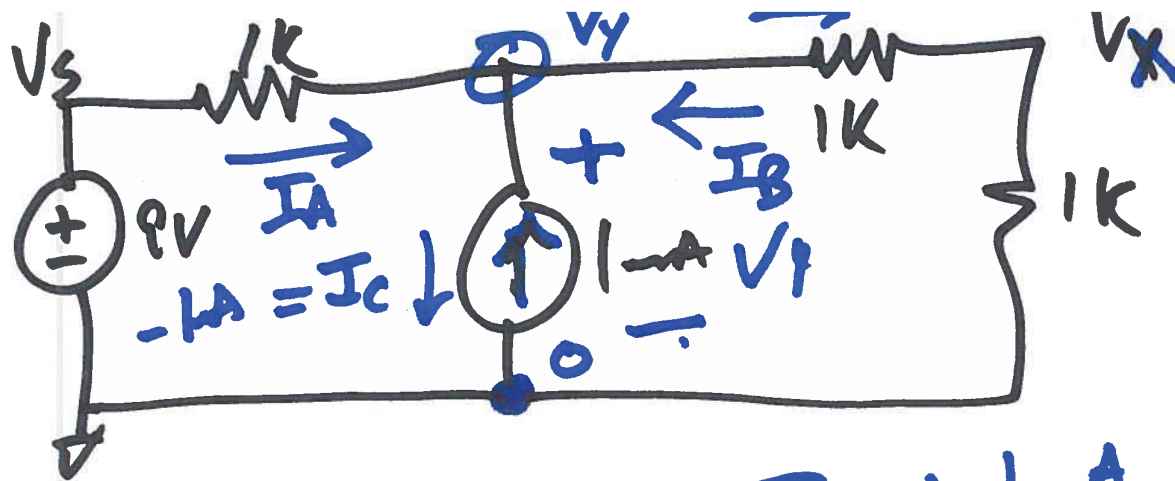
$$\frac{3.33}{1K} = \underline{\underline{3.33mA}}$$



$$\text{KCL: } I_A + I_B + 1\text{mA} = 0$$

$$I_A = \frac{9 - V_Y}{1\text{k}}$$


$$I_B = \frac{V_X - V_Y}{1\text{k}}$$

$$\frac{9 - V_Y}{1\text{k}} + \frac{V_X - V_Y}{1\text{k}} + 1\text{mA} = 0$$


$$9 - V_Y + V_X - V_Y + 1\text{k} = 0$$

$$\frac{V_Y - V_X}{1\text{k}} = \frac{V_X}{1\text{k}} \Rightarrow V_Y = 2V_X$$

Superposition


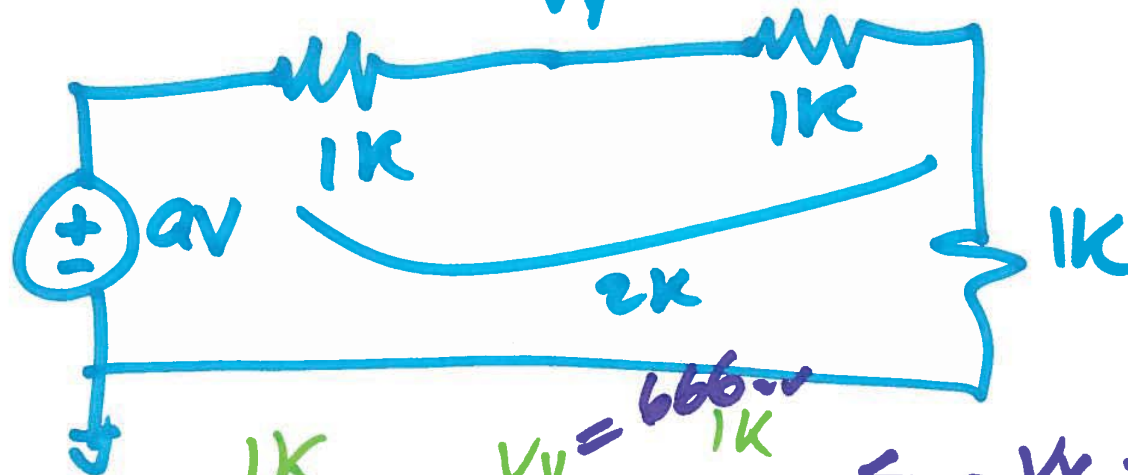

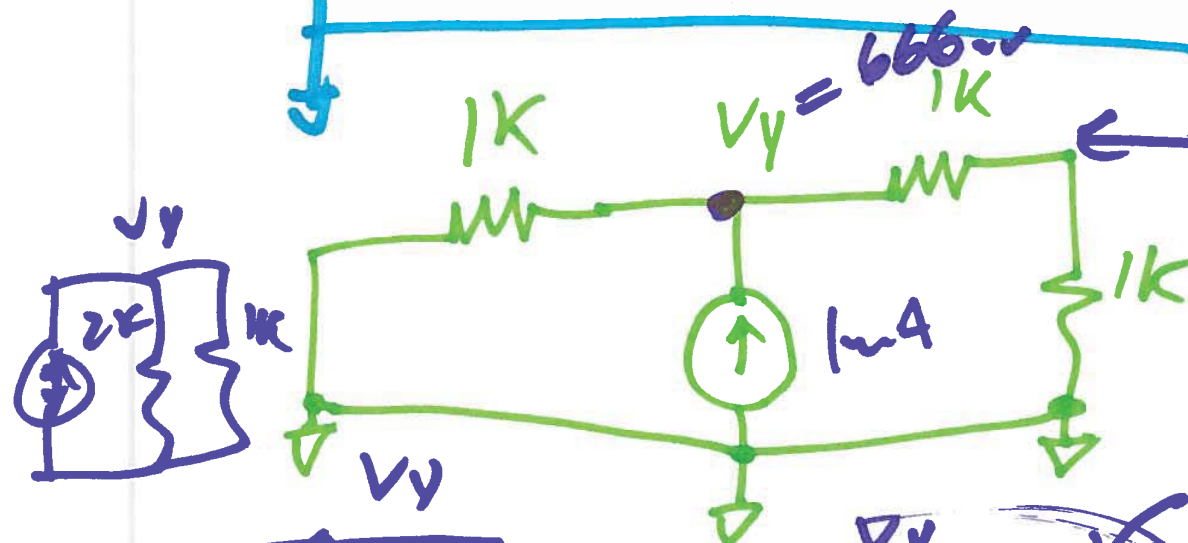
$$V_x = 9V \cdot \frac{1k}{1k + 2k} = \underline{\underline{3V}}$$




$$V_x = 333mV$$
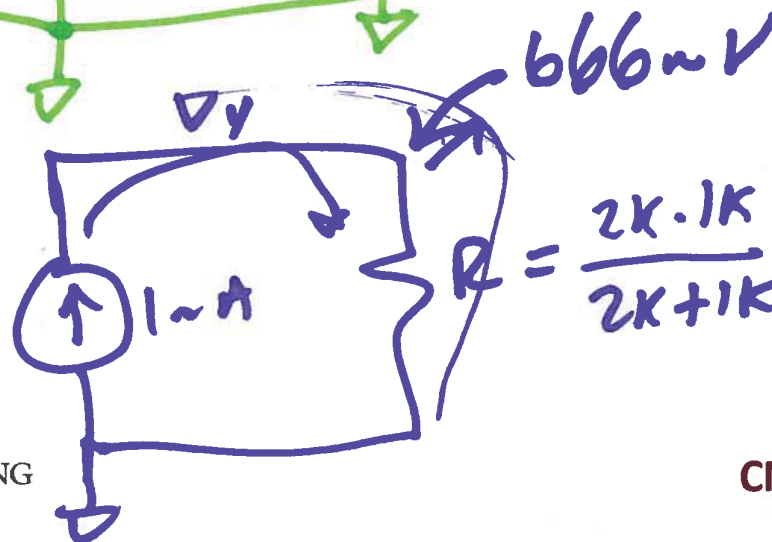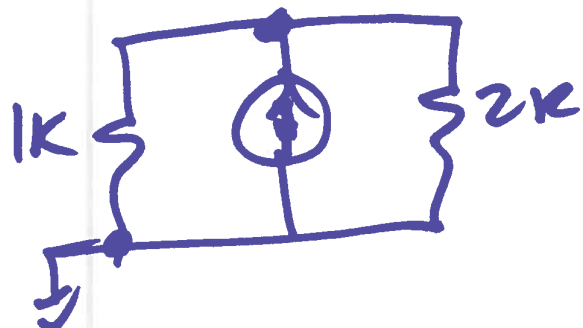
$$V_x / T = \underline{\underline{3.33V}}$$



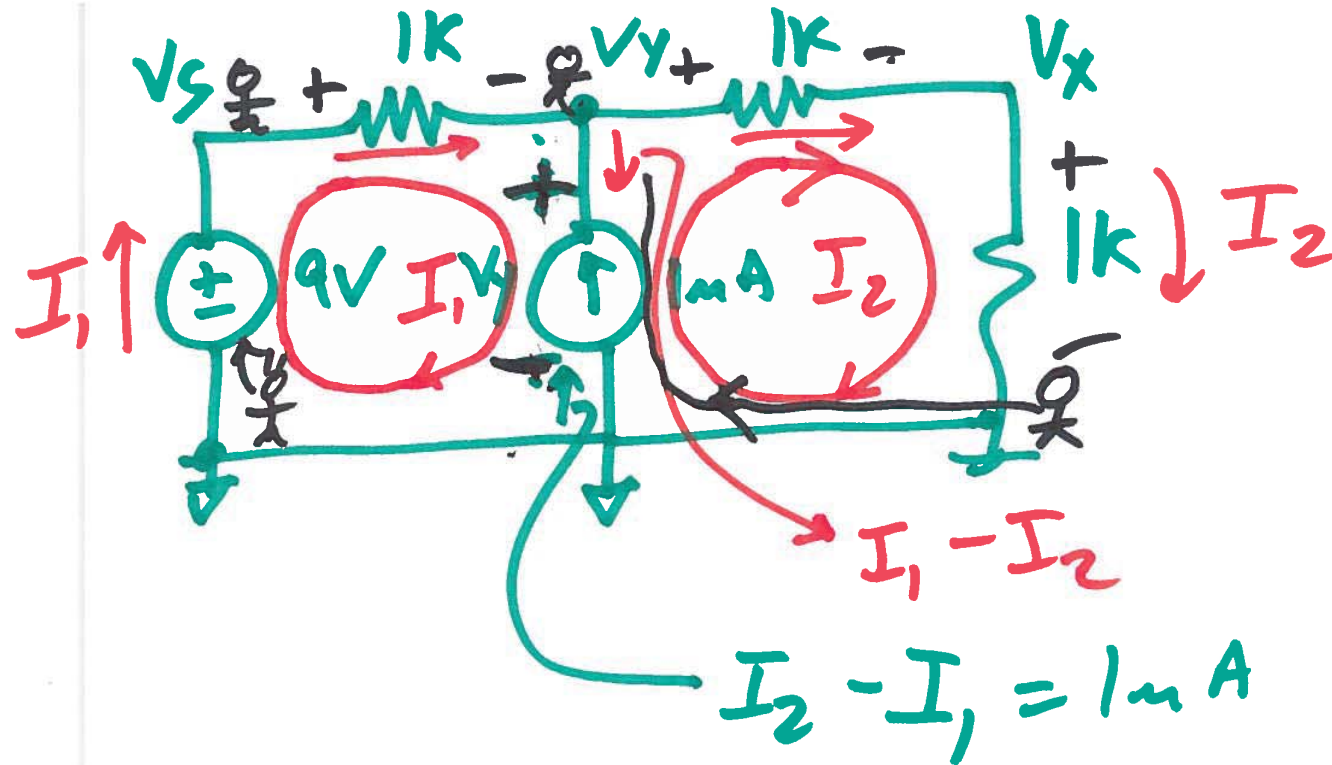
$$R = \frac{2k \cdot 1k}{2k + 1k} = 666\Omega$$



$$9\text{V} - 1\text{k} \cdot I_1 - V_y = 0$$
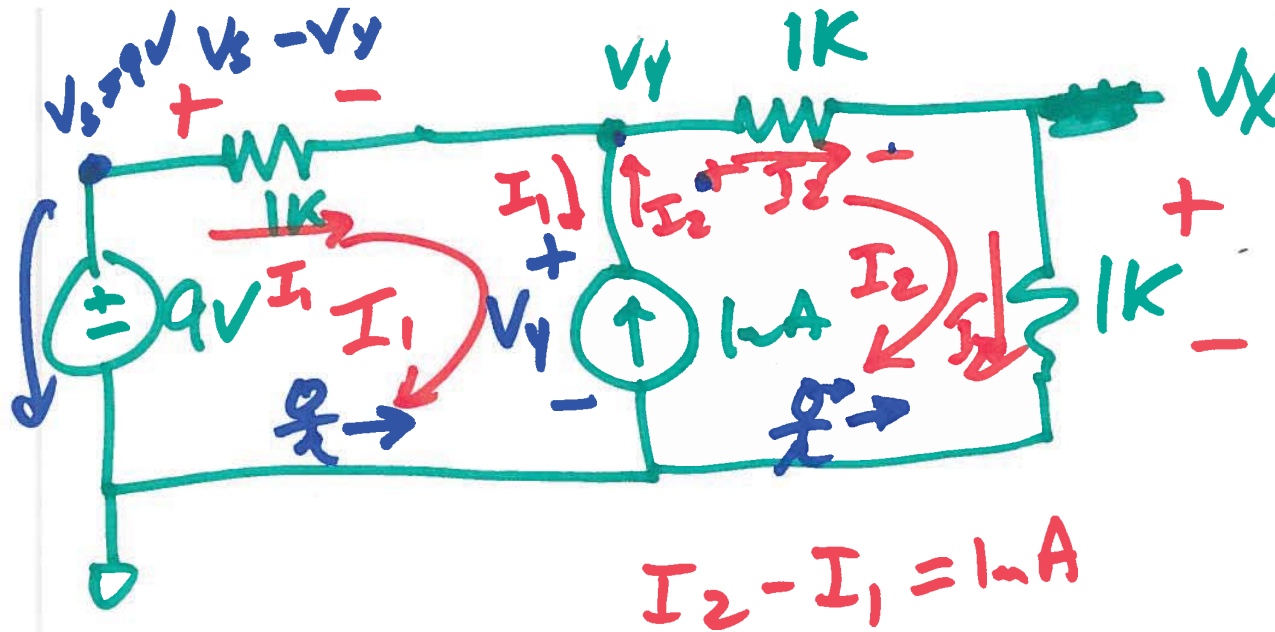
$$V_y - 1\text{k} \cdot I_2 - I_2 \cdot 1\text{k} = 0$$



$$V_y + 1k \cdot I_1 - 9 = 0$$

$$I_2 \cdot 1k + I_2 \cdot 1k - V_y = 0$$