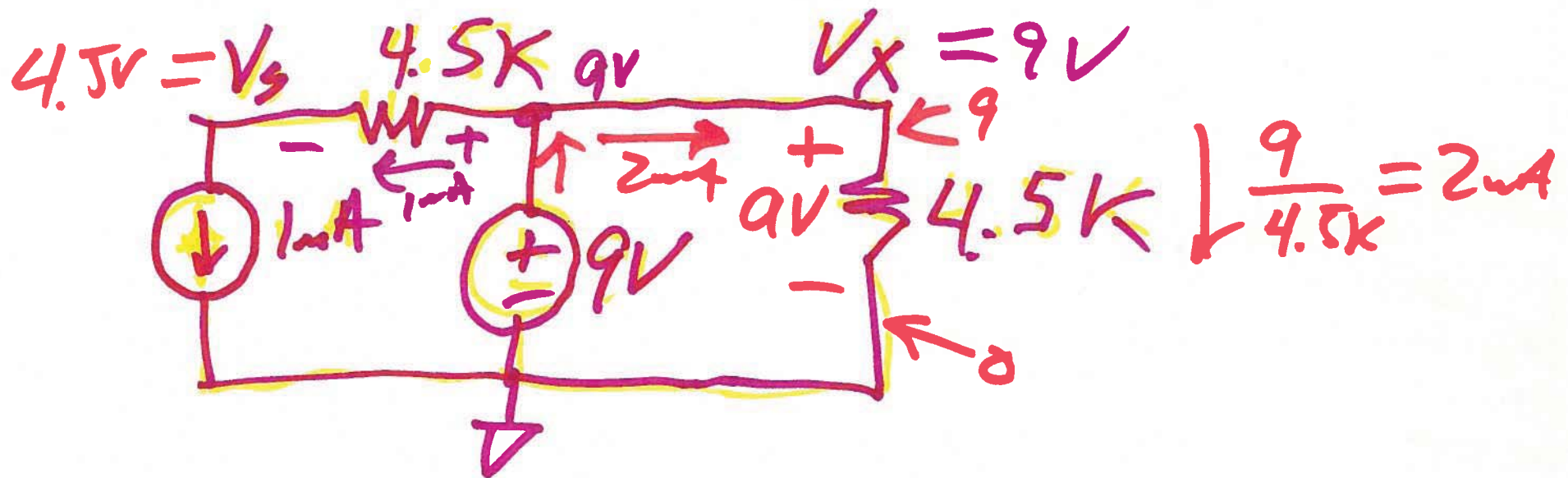



# EE 220

## Circuits I


### Lecture 7




CA. 1980

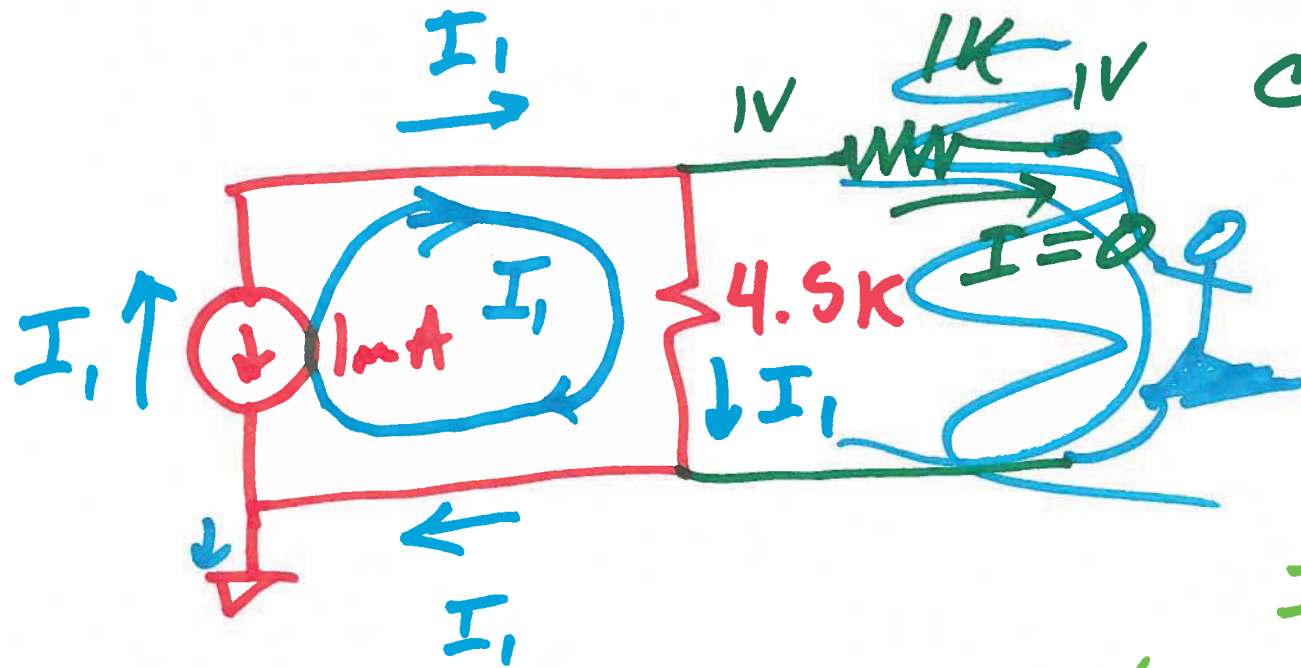

# GFCI

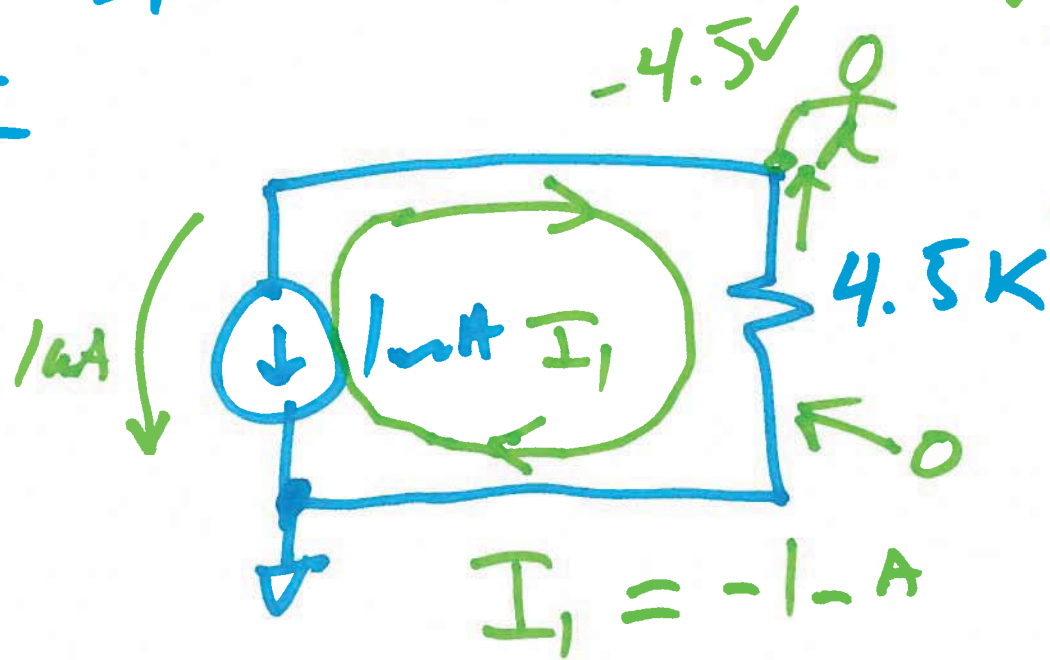


$$+V$$

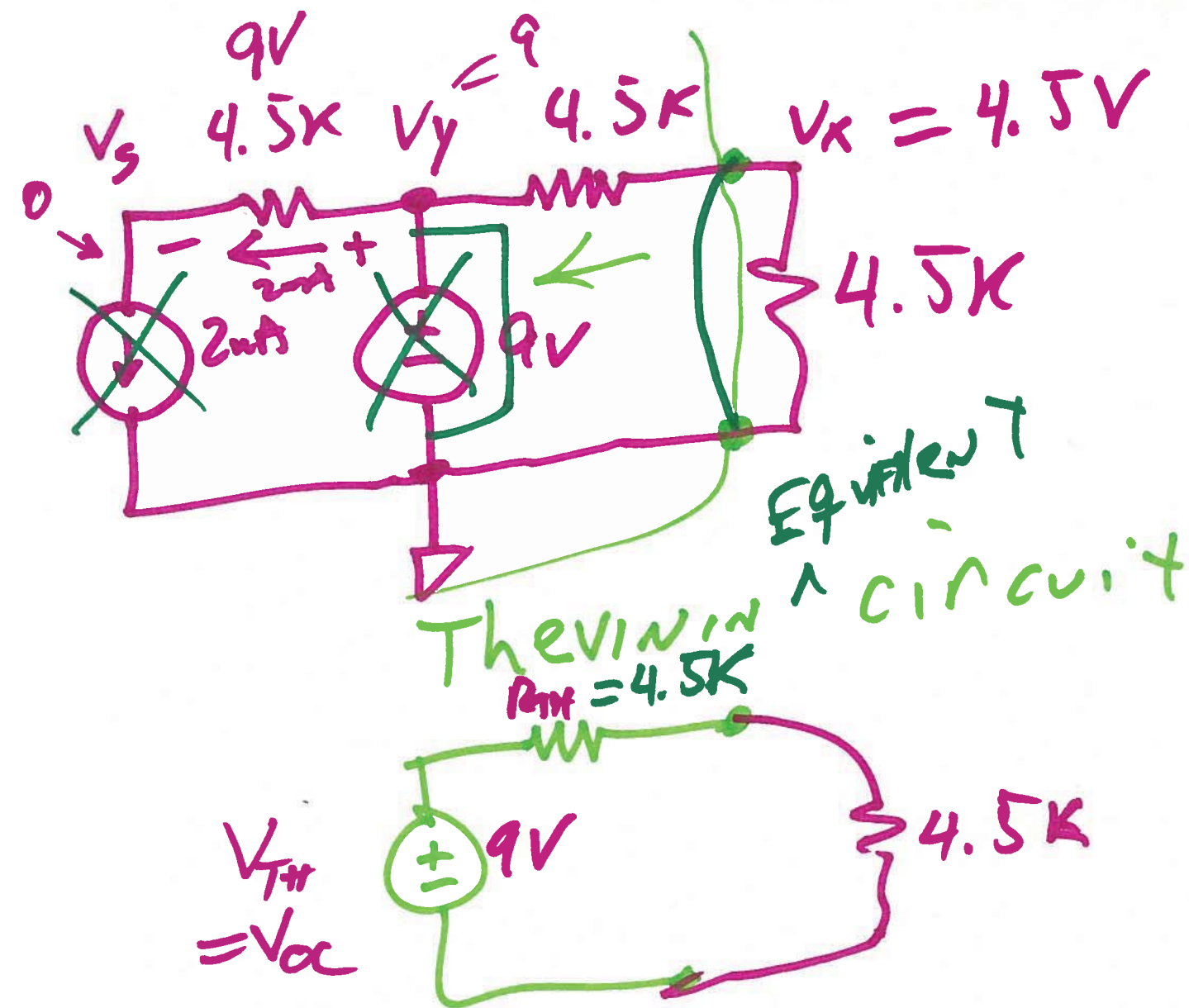
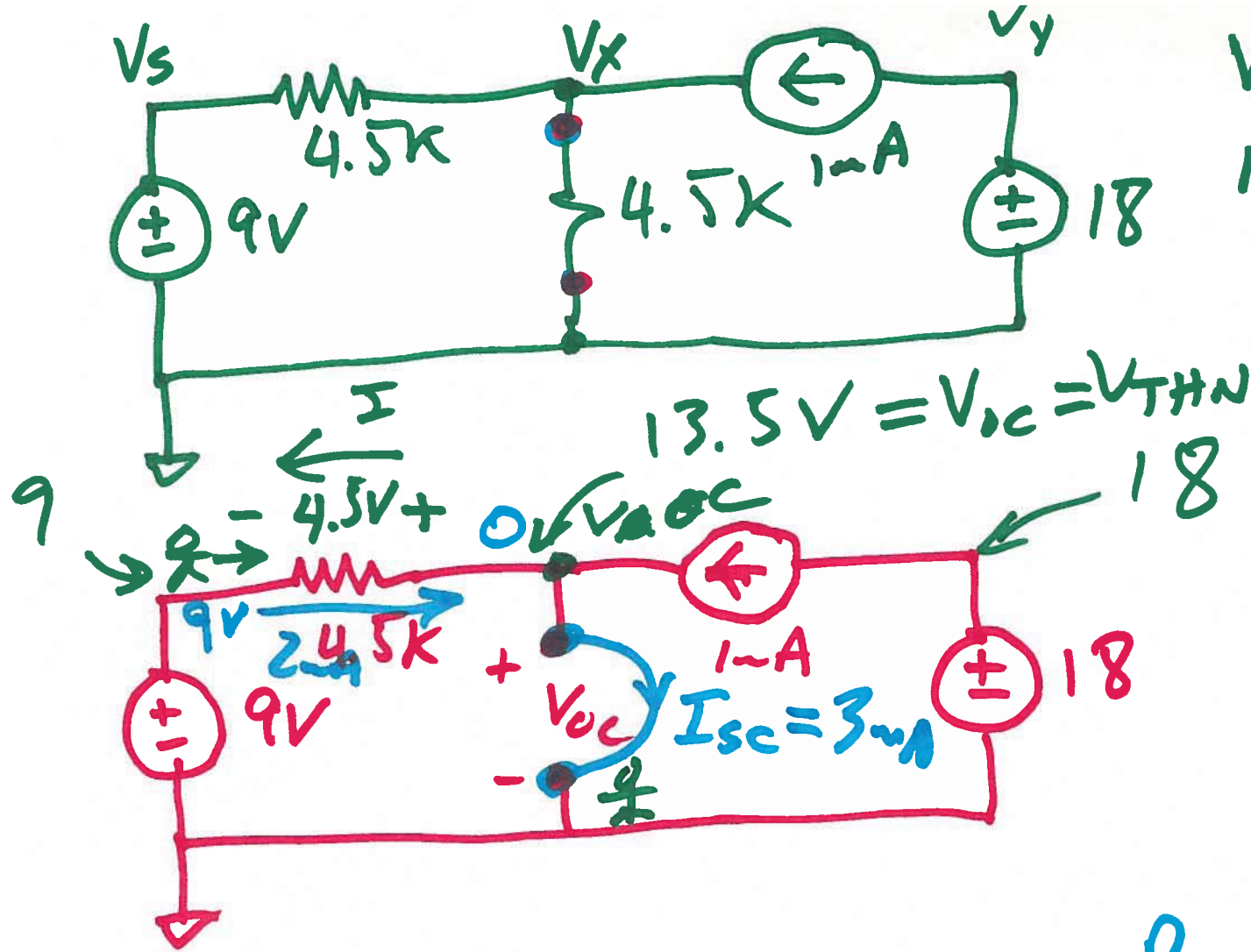
$$V = I \cdot R$$

$$-V$$

$$-V = IR$$







$$V_{TH} = 13.5V$$

$$R_{TH} = 4.5K$$

$$13.5V = V_{oc} = V_{TH}$$


$$V_{oc} = I \cdot 4.5K + 9V$$

$$V_{oc} - I \cdot 4.5K - 9V = 0$$


$$R_{TH} = \frac{V_{oc}}{I_{sc}}$$

$$= \frac{13.5}{3mA}$$

$$= 4.5K$$

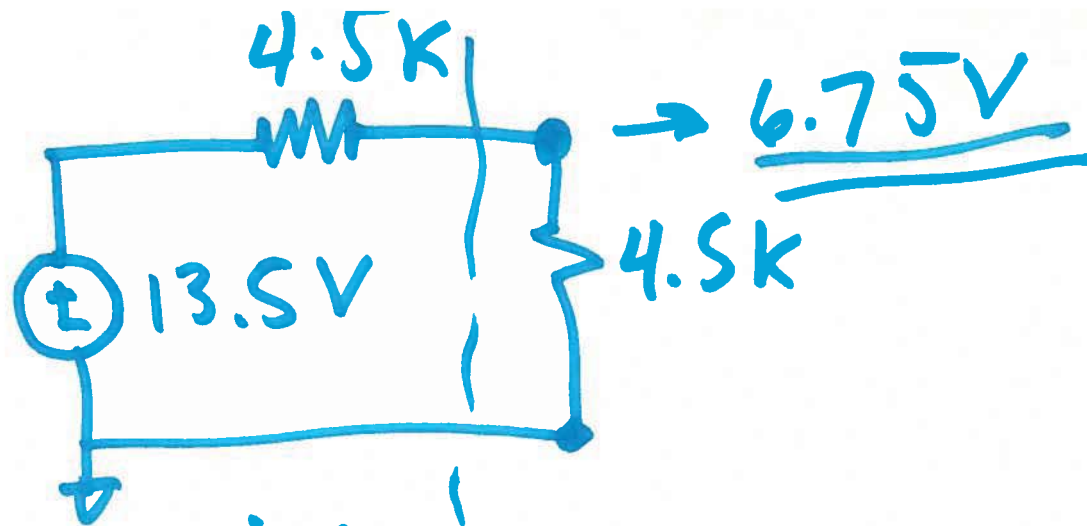

THEVENIN  
equiv.

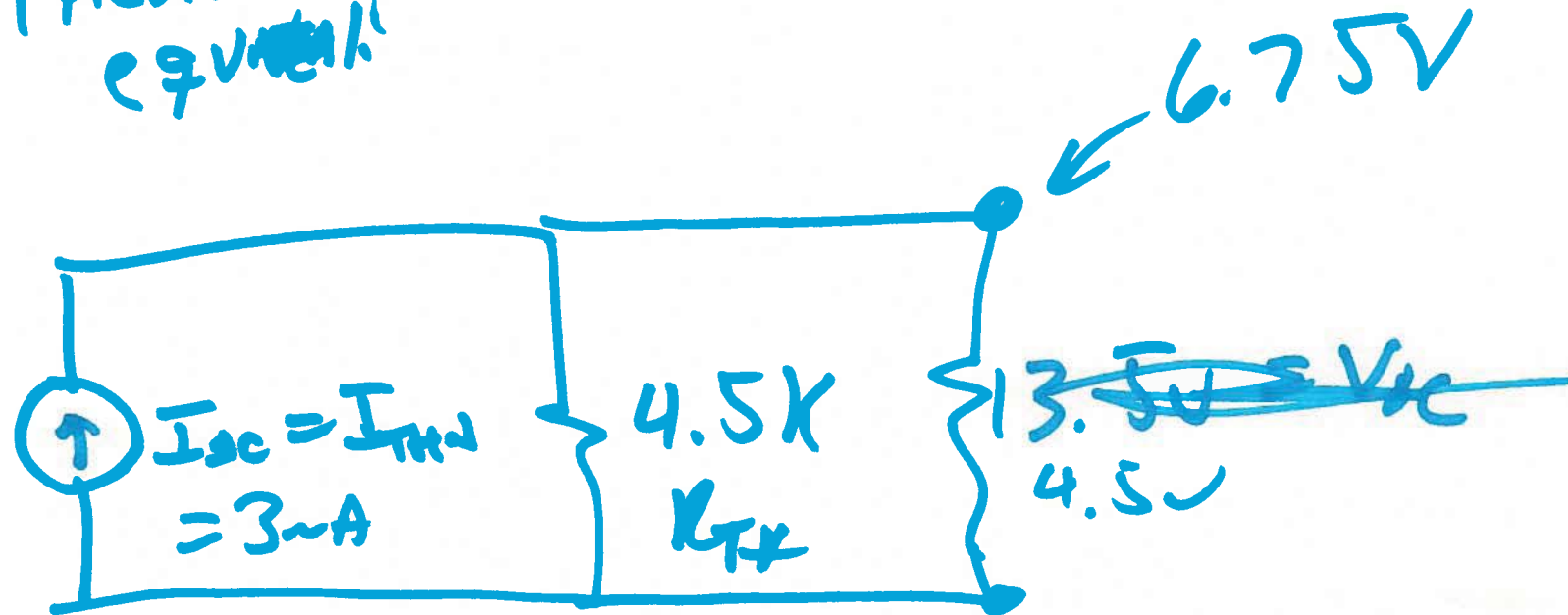

NORTON  
equiv.

5)

