

Closed book and notes.

Show your work for credit!

1. Plot VL for the following simulation on the plot seen below for both transitions of the input pulse. Write equations for both edges as well. Do not derive the equation, simply write it. (5 points)

