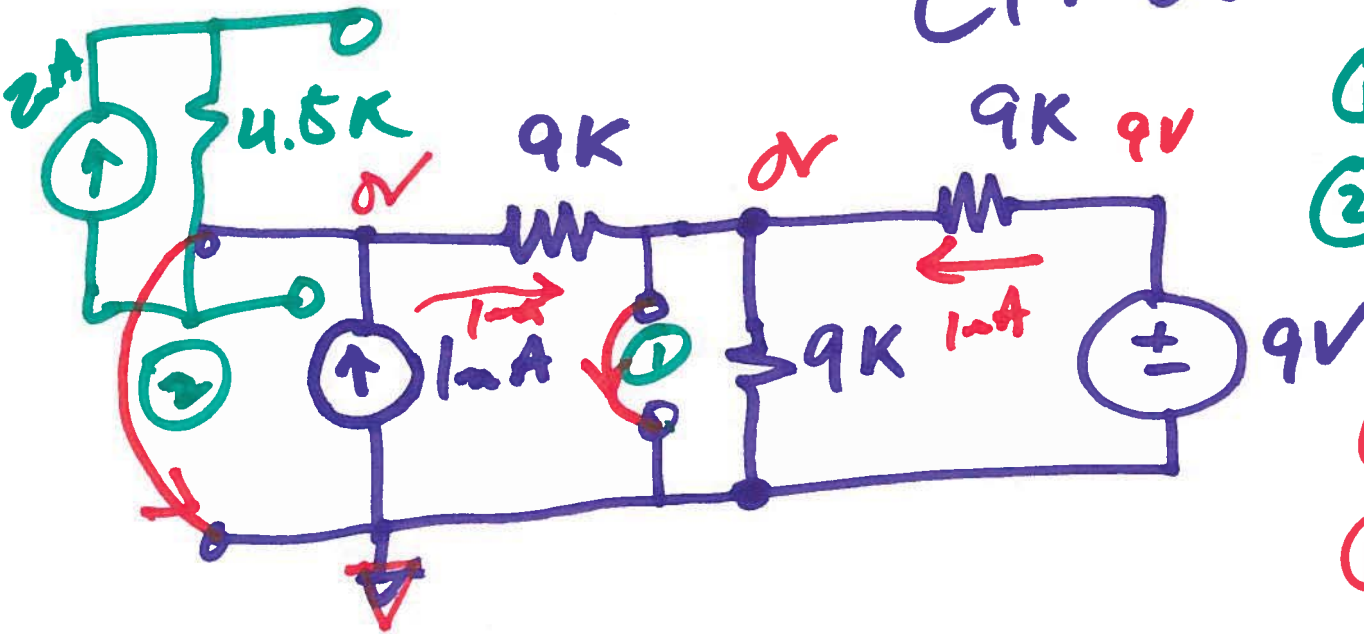


① 4.5K

A circuit diagram showing a series connection of a resistor and a DC voltage source. The resistor is labeled 4.5K and the voltage source is labeled $\frac{4}{9}\text{V}$ with the positive terminal at the top.

- ① $R_{TH} = 4.5\text{ k}\Omega$
- ② $R_{TH} = 13.5\text{ k}\Omega$



① $I_{sc} = 2 \mu A$


② I_{sc}

② I_{sc} .4.5 mA

① $V_{oc} = \frac{I_{sc} \cdot R_{th}}{V_{th}} = \frac{2A \cdot 4.5k}{6.18k}$

~~I_{sc}~~

① $V_{TH} = 9 \frac{4}{5} V$

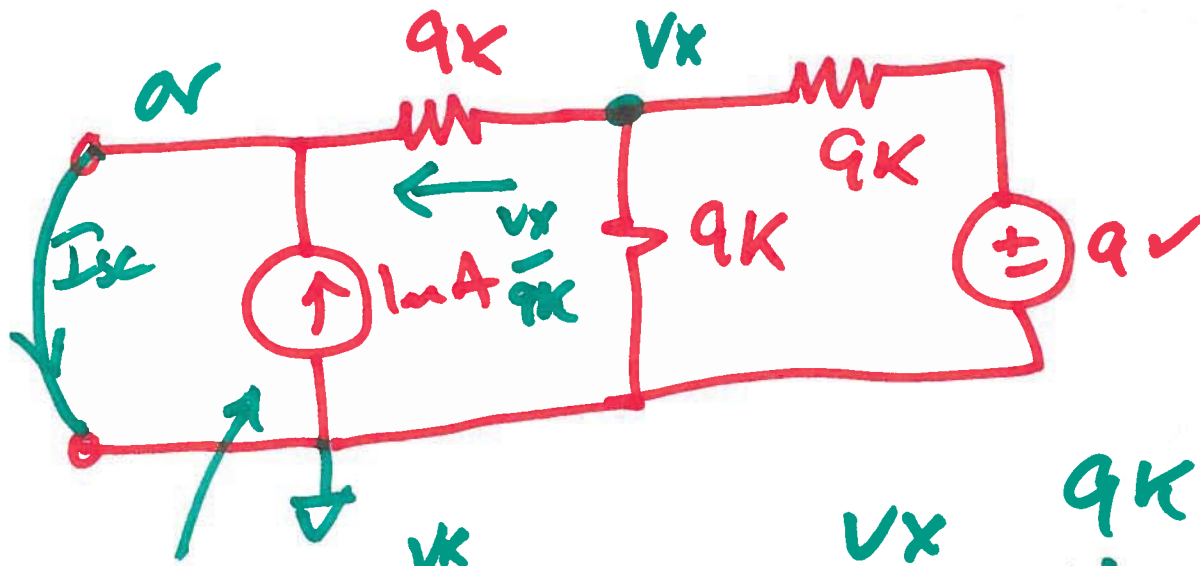


$$I_{sc} = 1mA + \frac{V_x}{9k}$$

$$= 1mA + \frac{3}{9k}$$

$$I_{sc} = \underline{\underline{1.33mA}}$$

$$R_{TH} = 13.5k$$

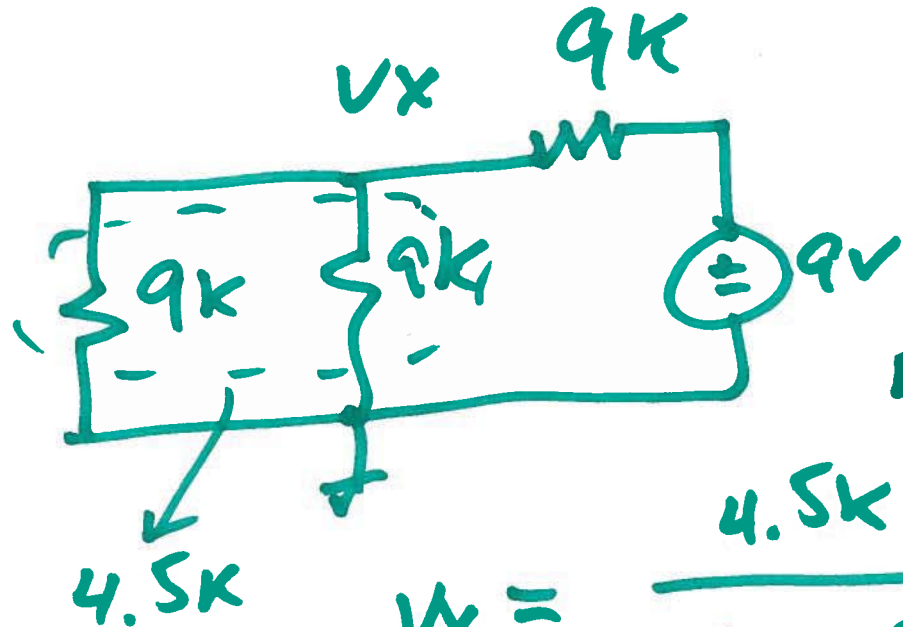

$$V_x = \frac{4.5k}{4.5k + 9k} \cdot 9V$$


$$V_{TH} = 13.5k \cdot 1.33mA + 4.5$$

$$= 13.5V + \frac{13.5}{3}$$

$$= \underline{\underline{18V}}$$

$$\frac{1}{3} \cdot 9V = \frac{9V}{3} = 3V$$

2)


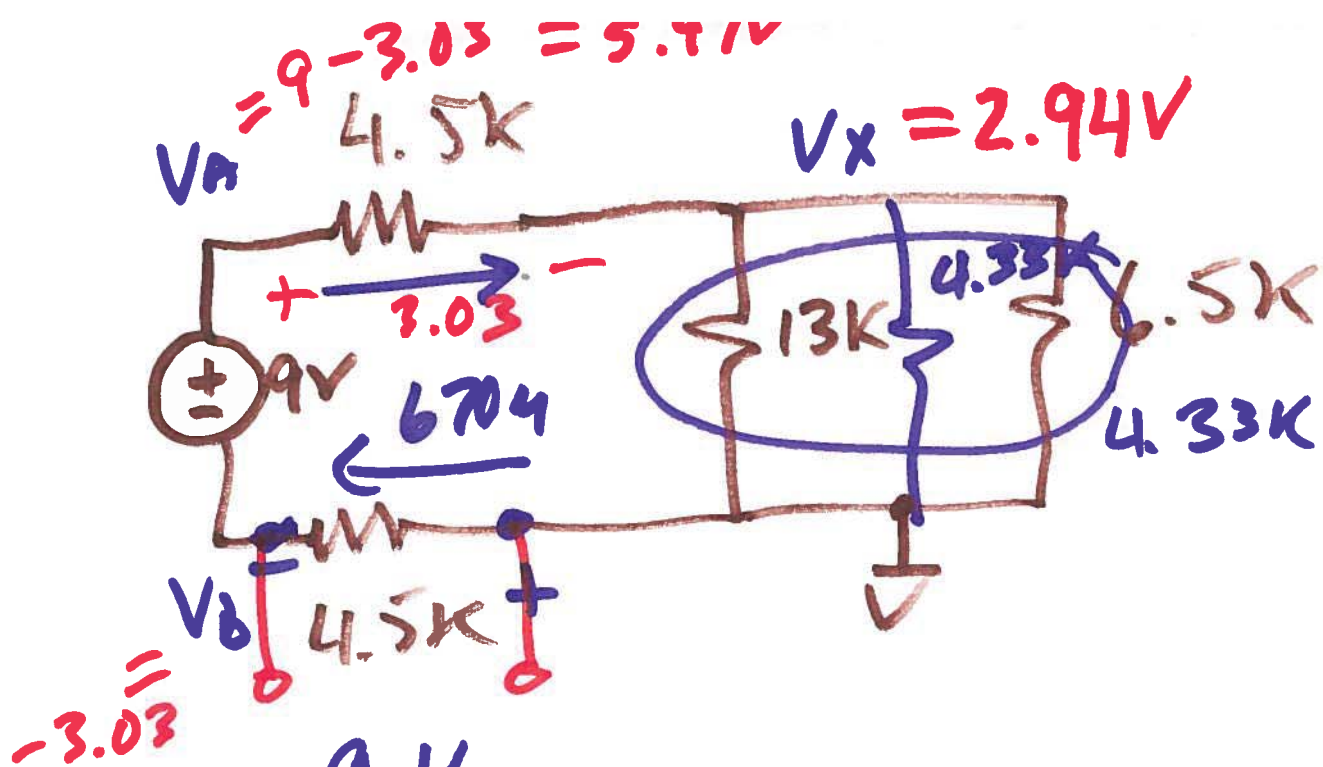


$$\begin{aligned}
 &13k \parallel 6.5k \\
 &\frac{13k \cdot 6.5k}{13k + 6.5k} \\
 &= \frac{13k}{2+1} = \frac{13k}{3}
 \end{aligned}$$

$$13k \parallel 6.5k = 4.33k$$


$$\begin{aligned}
 I &= \frac{9V}{4.5k + 4.5k + 4.33k} \\
 &= \frac{9V}{13.33k} = 0.67 \mu A = 670.4 \mu A
 \end{aligned}$$
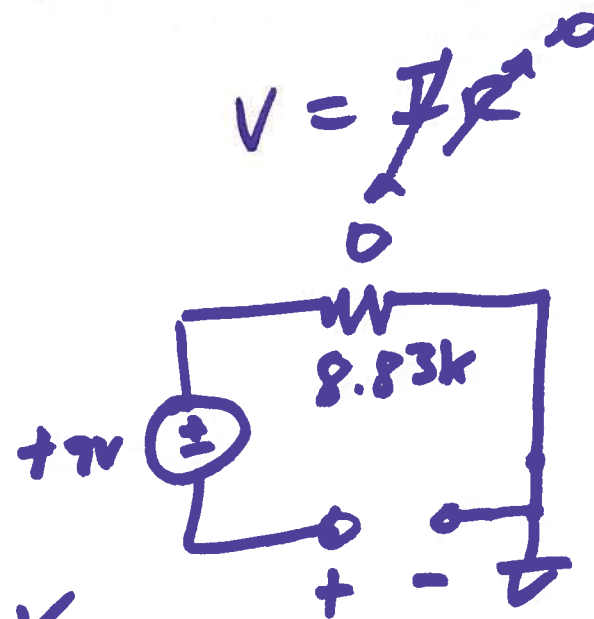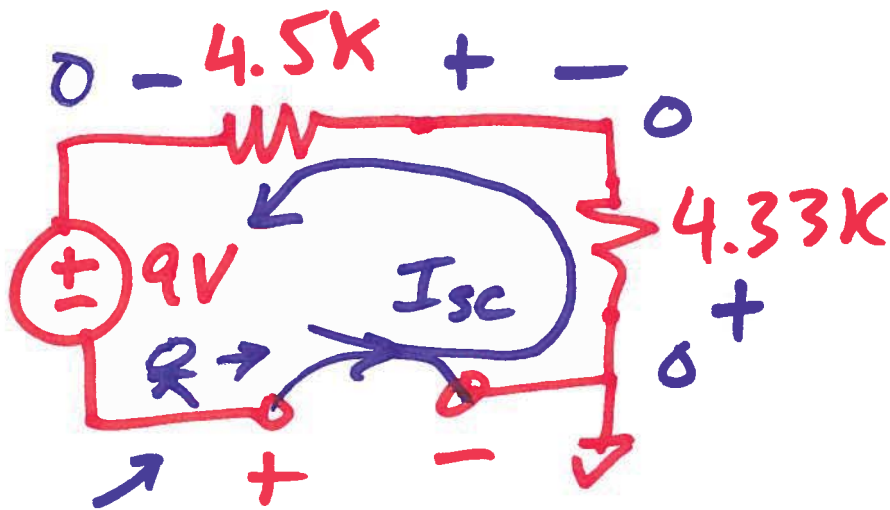
$$V_b = (0 - 670.4 \mu A) \cdot 4.5k = -\underline{\underline{3.03V}}$$



$$V_{th} = V_{oc} = -9V$$
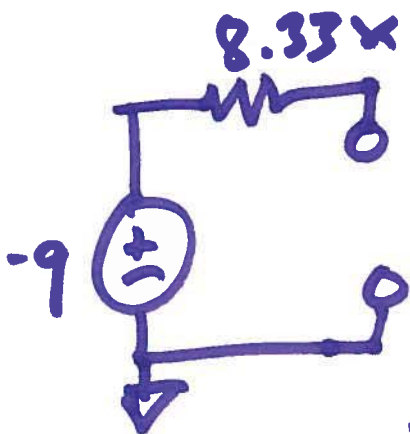
$$R_{th} = 8.83k = \frac{V_{th}}{I_{sc}} = \frac{-9}{\frac{-9}{8.83k}} = 8.83k$$




$$-4.33k \cdot I_{sc} - I_{sc} \cdot 4.5k - 9V$$

$$I_{sc} = \frac{9V}{-8.83k}$$

$$V_{4.5k} = -9 \cdot \frac{4.5k}{8.33k + 4.5k} = -3.03V$$

4)

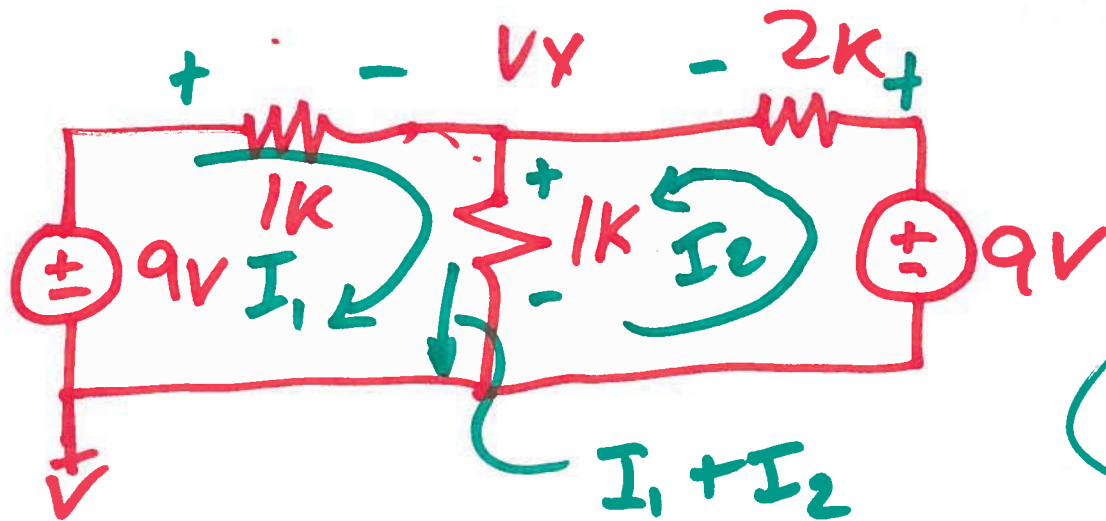

$$I_2 = 1.8 \mu A$$

$$I_2 = 9 \mu A - 7.2 \mu A$$

$$I_2 = 9 \mu A - 2I_1$$

$$I_2 = 2.8 \mu A$$

$$9 - I_1 \cdot 1k - (I_1 + I_2) \cdot 1k = 0 \Rightarrow 9 \mu A - 2I_1 - I_2 = 0$$

$$9 - I_2 \cdot 2k - (I_1 + I_2) \cdot 1k = 0 \Rightarrow 9 \mu A - 3I_2 - I_1 = 0$$


$$I_1 = 3.6 \mu A$$

$$9 \mu A - 27 \mu A + 6I_1 - I_1 = 0$$

$$V_x = (I_1 + I_2) \cdot 1k = \underline{\underline{5.4V}}$$

$$5I_1 = 18 \mu A$$
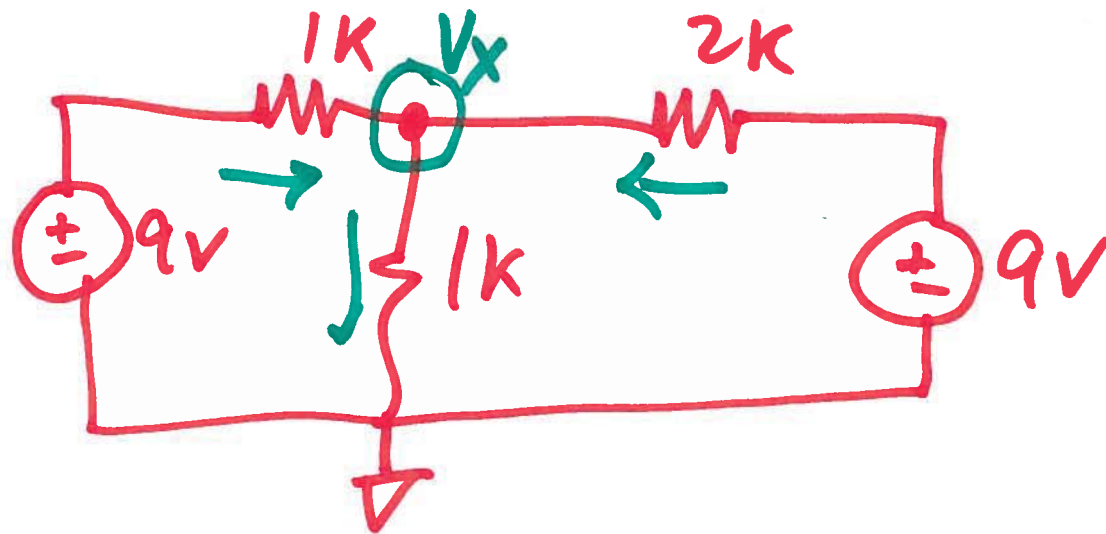
$$I_1 = \frac{18 \mu A}{5} = \underline{\underline{3.6 \mu A}}$$




$$\frac{9 - V_x}{1k} + \frac{9 - V_x}{2k} = \frac{V_x}{1k}$$

$$18 - 2V_x + 9 - V_x = 2V_x$$


$$27 = 5V_x$$
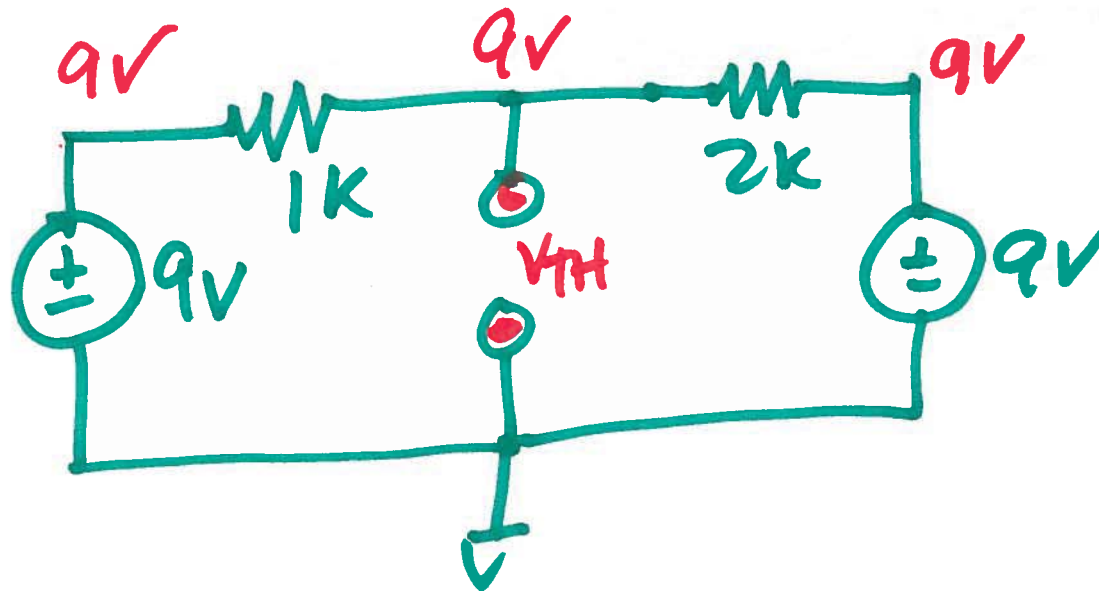
$$V_x = \frac{27}{5} = \underline{\underline{5.4V}}$$




$$V_{TH} = 9V$$

$$R_{TH} = 666\Omega$$



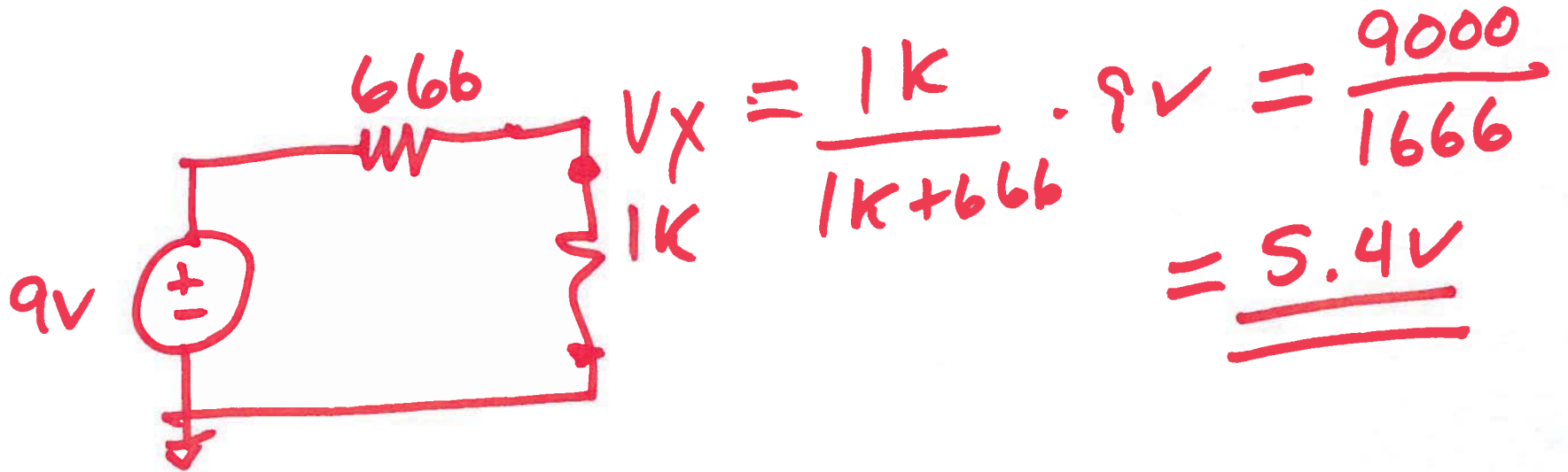


$$V_x = \frac{1k}{1k + 666} \cdot 9V = \frac{9000}{1666}$$


$$= \underline{\underline{5.4V}}$$

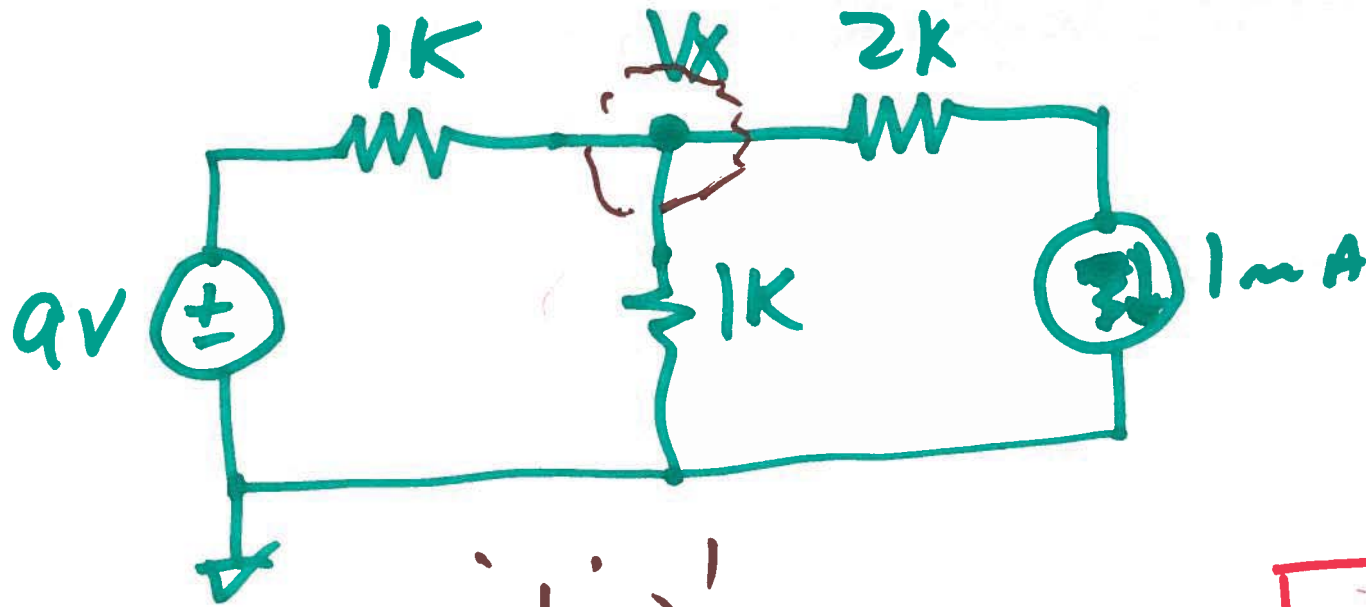

superposition!

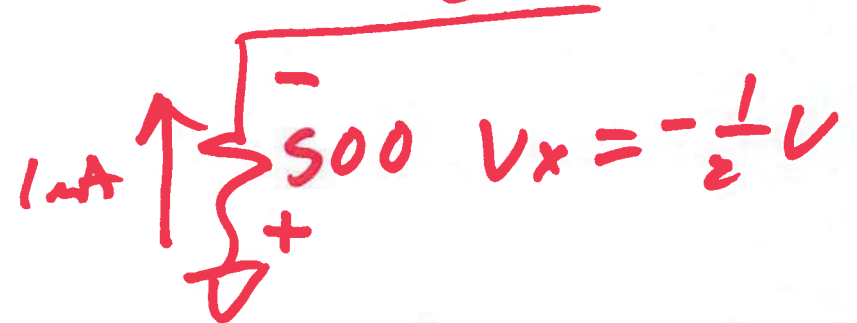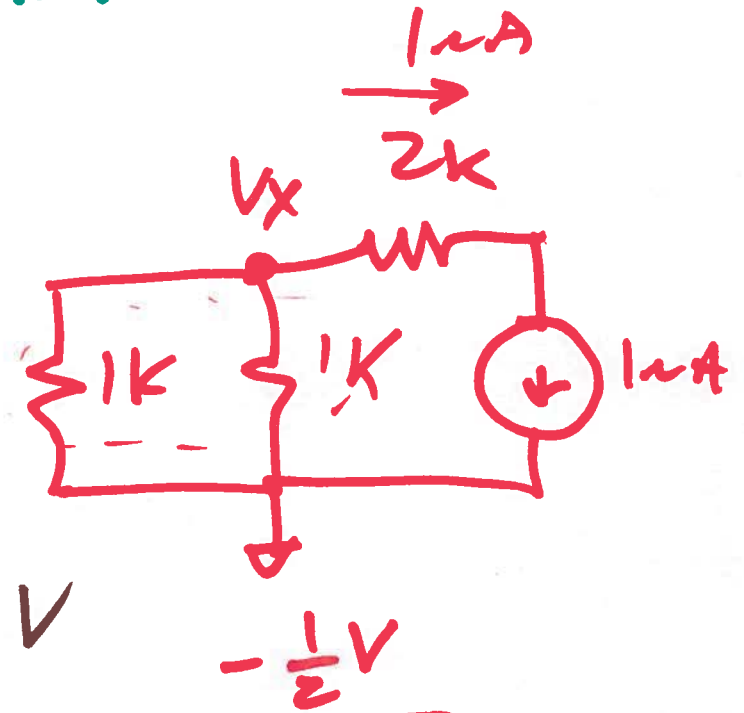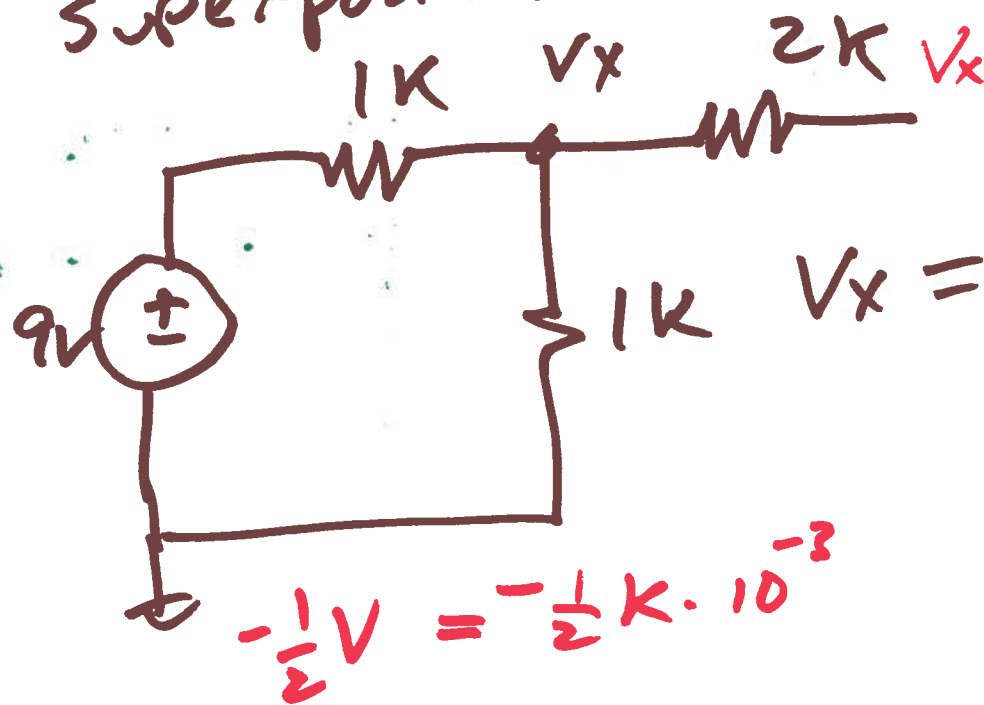

$$V_x = 4.5 - \frac{1}{2} = 4V$$

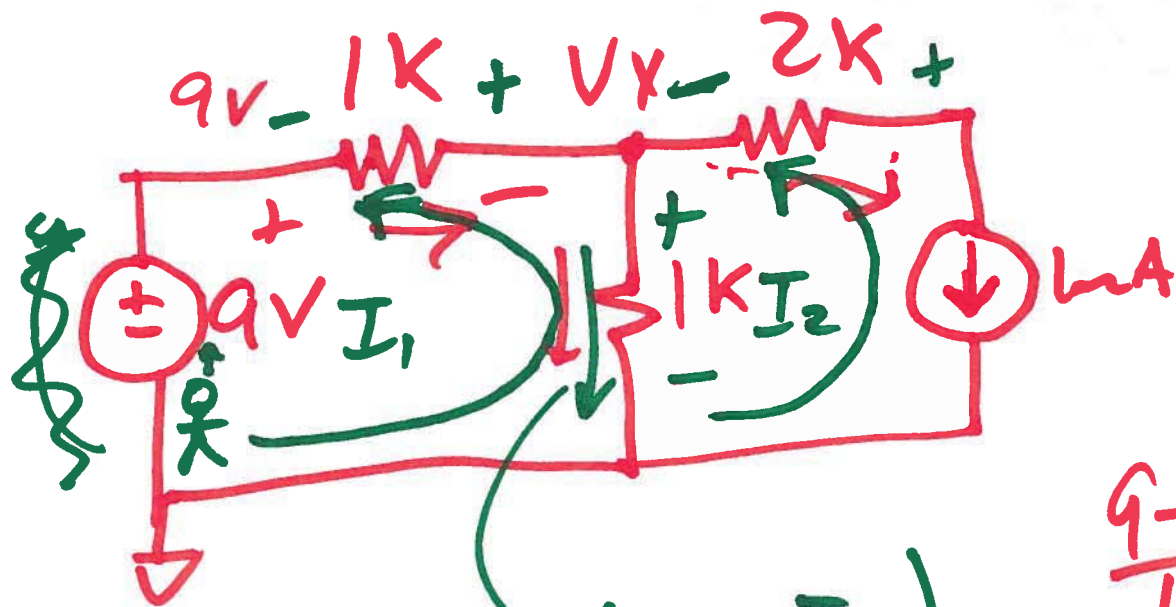

KCL

$$\frac{9 - V_x}{1k} - 1mA + \frac{V_x}{1k}$$

$$\frac{9 - V_x}{1k} - 1mA - \frac{V_x}{1k} = 0$$

$$(-I_1 + I_2)$$


$$(-(-5mA) + 1mA) = 4mA, V_x = 1k \cdot 4mA = \underline{\underline{4V}}$$


$$I_2 = -1mA$$

$$9 + 1k \cdot I_1 - 1k(-I_1 + (-1mA)) = 0$$

$$9mA + 2I_1 + 1mA = 0$$

$$I_1 = -\frac{5}{2}mA$$

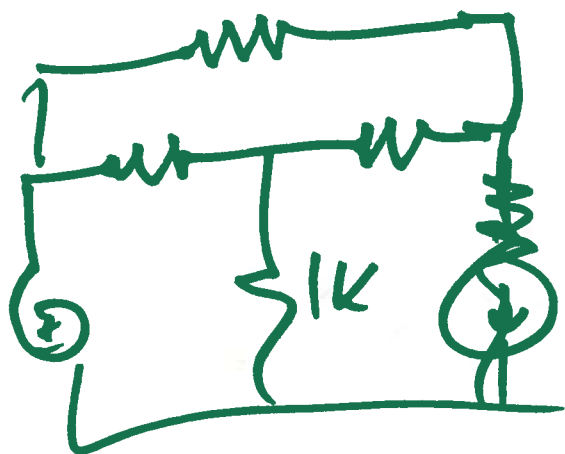

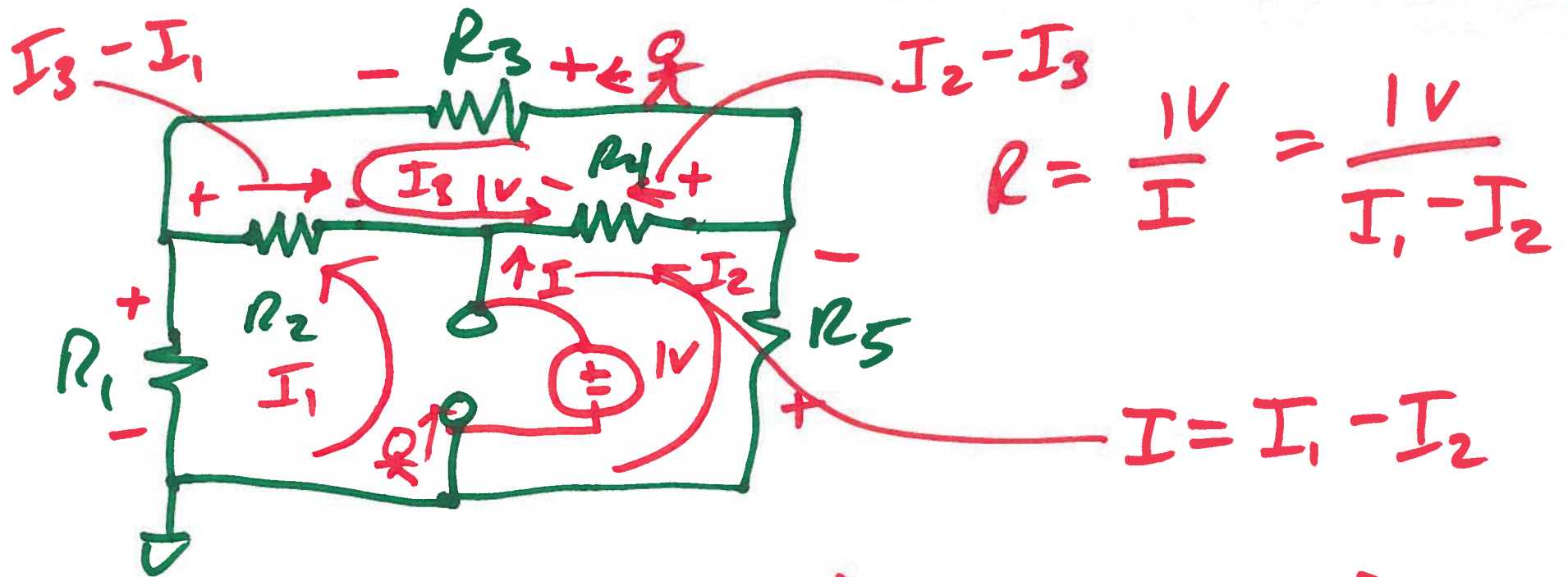



$$1 + R_2(I_3 - I_1) - R \cdot I_1 = 0$$

$$-I_2 R_5 - R_4(I_2 - I_3) - 1 = 0$$



$$-R_3 I_3 - R_2(I_3 - I_1) + R_4(I_2 - I_3) = 0$$

$$1 + R_2 I_3 - I_1 \cdot (R_1 + R_2) = 0$$
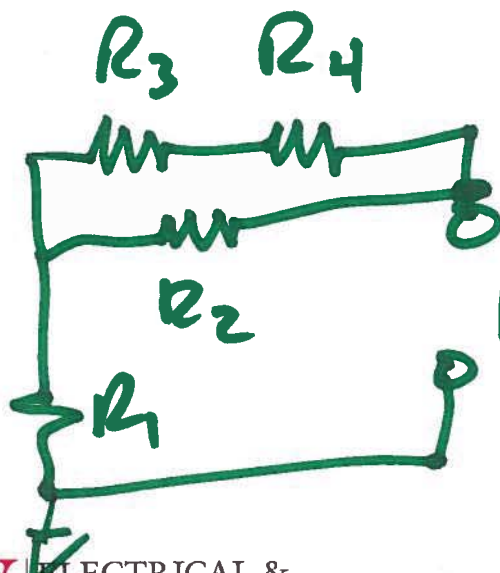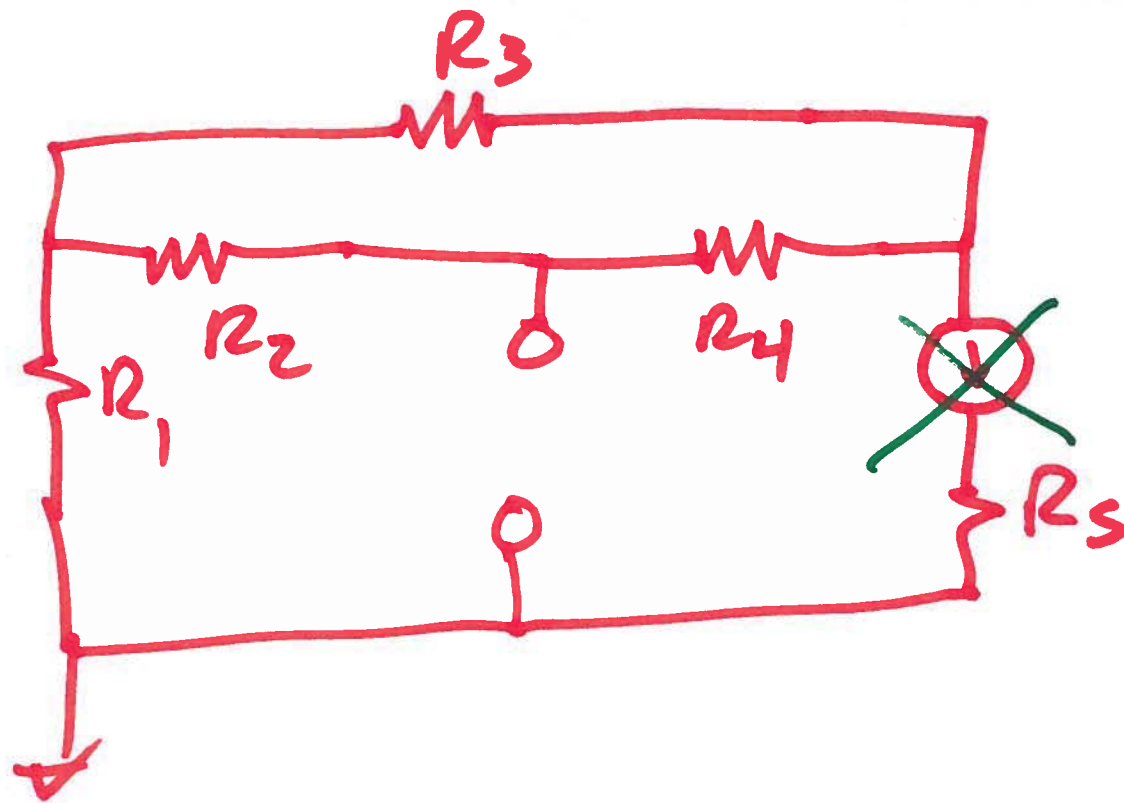
$$I_3 = I_1 \cdot \frac{R_1 + R_2}{R_2} + \frac{1}{R_2}$$


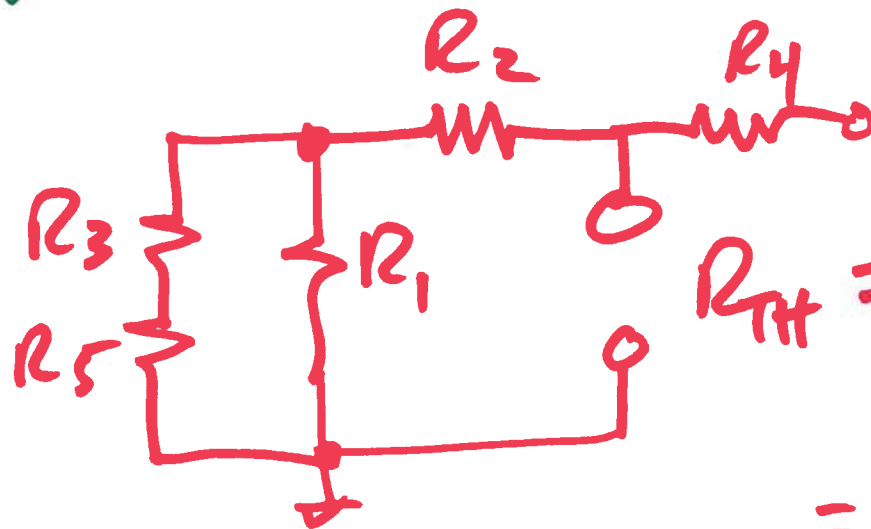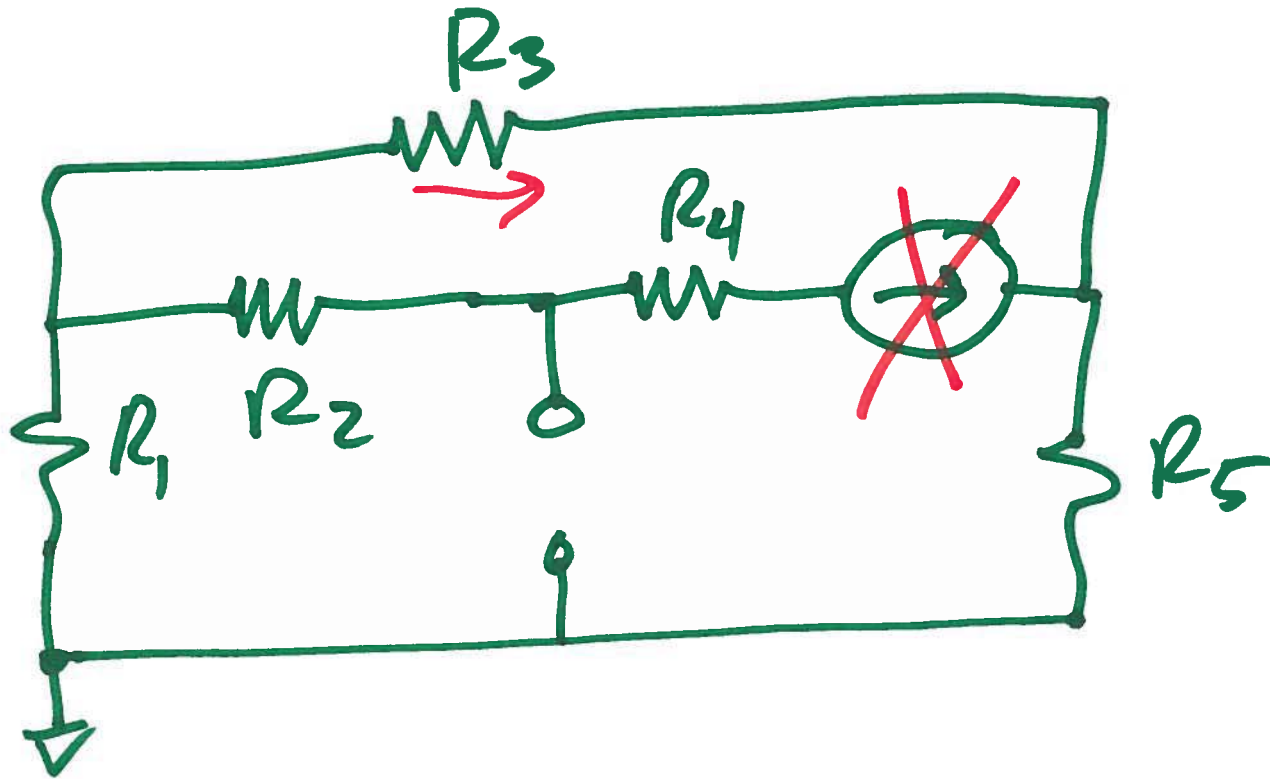
$$R_{TH} = R_1 + (R_3 + R_4) \parallel R_2$$



$$R_{TH} = R_2 + R_1 \parallel (R_3 + R_5)$$

$$= R_2 + \frac{R_1 \cdot (R_3 + R_5)}{R_1 + R_3 + R_5}$$

CMOSedu.com

12)