

Lecture 10D


7/2/14

EE 220D

frequency response

Bode plots

45V first

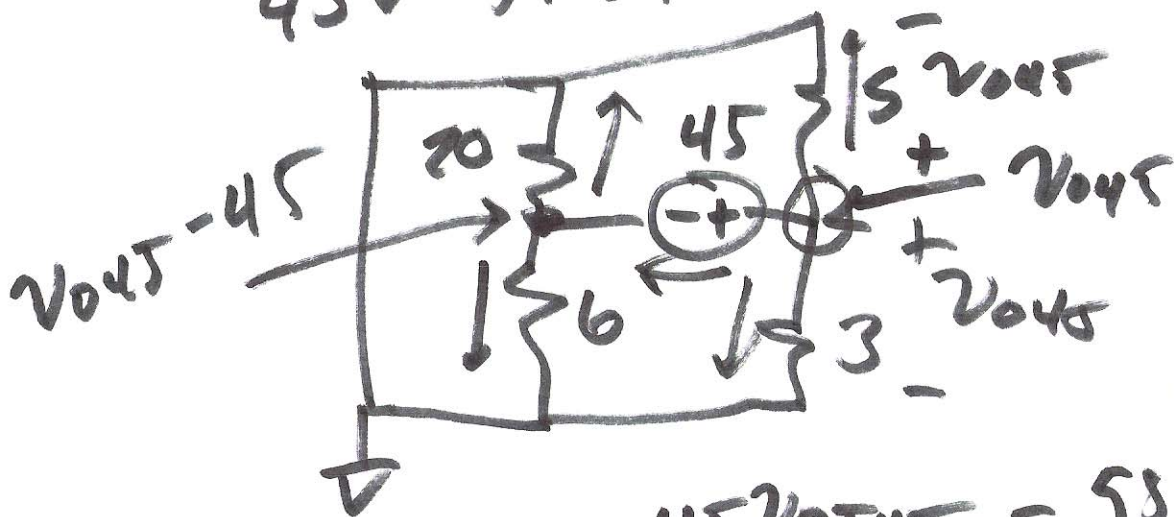



$$v_{out} \left(\frac{1}{3} + \frac{1}{5} \right) + \frac{(v_{out} - 45)}{\left(\frac{1}{6} + \frac{1}{20} \right)} = 0$$

$$20v_{out} + 12v_{out} +$$

$$45v_{out} = 585(v_{out} - 45) \cdot 10 +$$

$$v_{out} = \frac{585}{45} (v_{out} - 45) \cdot 3 = 0$$

$$v_{out} = 13V$$

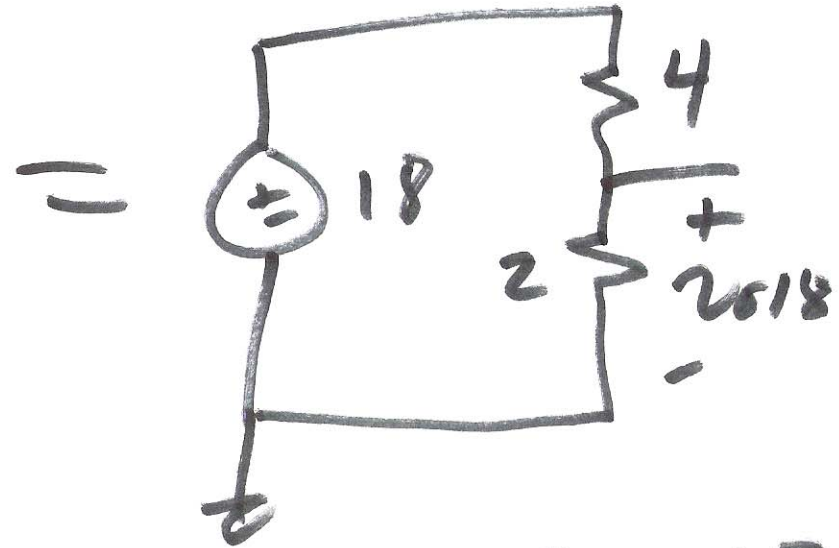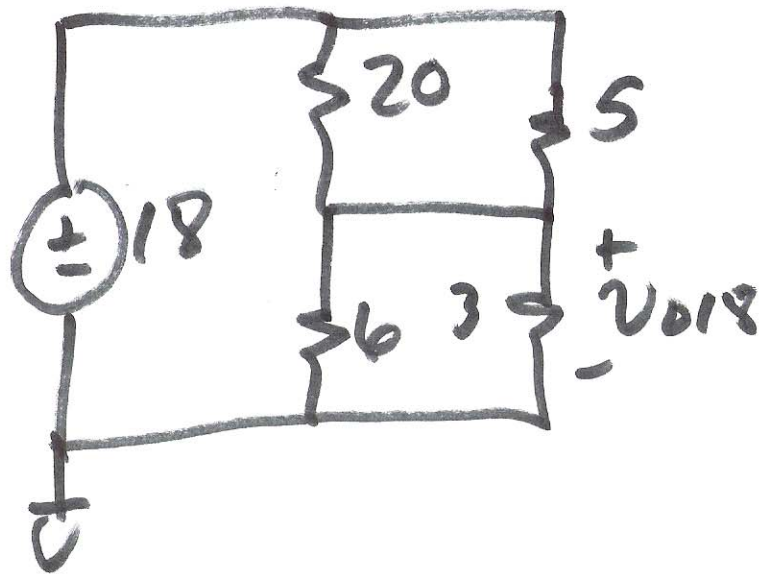

$$\frac{5 \cdot 20}{25} = 4$$


$$\frac{3 \cdot 6}{9} = 2$$

$$v_{018} = \frac{2}{2+4} \cdot 18$$

$$v_{018} = 6V$$

$$v_0 = v_{045} + v_{018} = 19V$$

2)

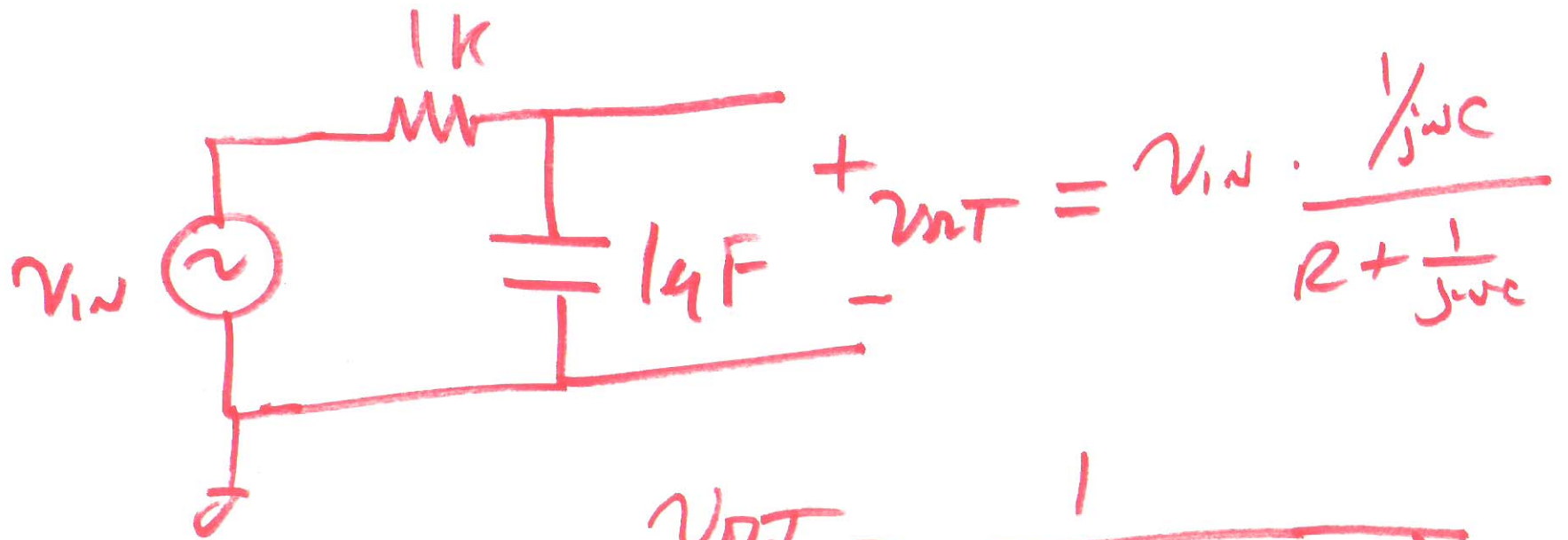

$$2\pi RC = 0.00628 \quad \frac{v_{out}}{v_{in}} = \frac{1}{1 + j(2\pi RC \cdot f)}$$

$$\frac{1}{2\pi RC} = 159 = f_{3dB} = \frac{1}{1 + j \frac{f}{1/2\pi RC}}$$

$$\left| \frac{1}{\sqrt{2}} \right| \Rightarrow -3dB = \frac{1}{1 + j \frac{f}{f_{3dB}}}$$


3)

$$\frac{v_{out}}{v_{in}} = \frac{1 + j0}{1 + j \frac{f}{f_{3dB}}} \quad \left| \frac{v_{out}}{v_{in}} \right| = \frac{\sqrt{1^2 + 0^2}}{\sqrt{1^2 + \left(\frac{f}{f_{3dB}}\right)^2}}$$

$$\angle \frac{v_{out}}{v_{in}} = \frac{\tan^{-1} \frac{0}{1}}{\tan^{-1} \frac{f}{f_{3dB}}} = \frac{0^\circ}{\tan^{-1} \frac{f}{f_{3dB}}} = \frac{1}{\sqrt{1 + \left(\frac{f}{f_{3dB}}\right)^2}}$$

$$= - \tan^{-1} \frac{f}{f_{3dB}}, \quad f_{3dB} = 1591 \text{ Hz}$$

Bode

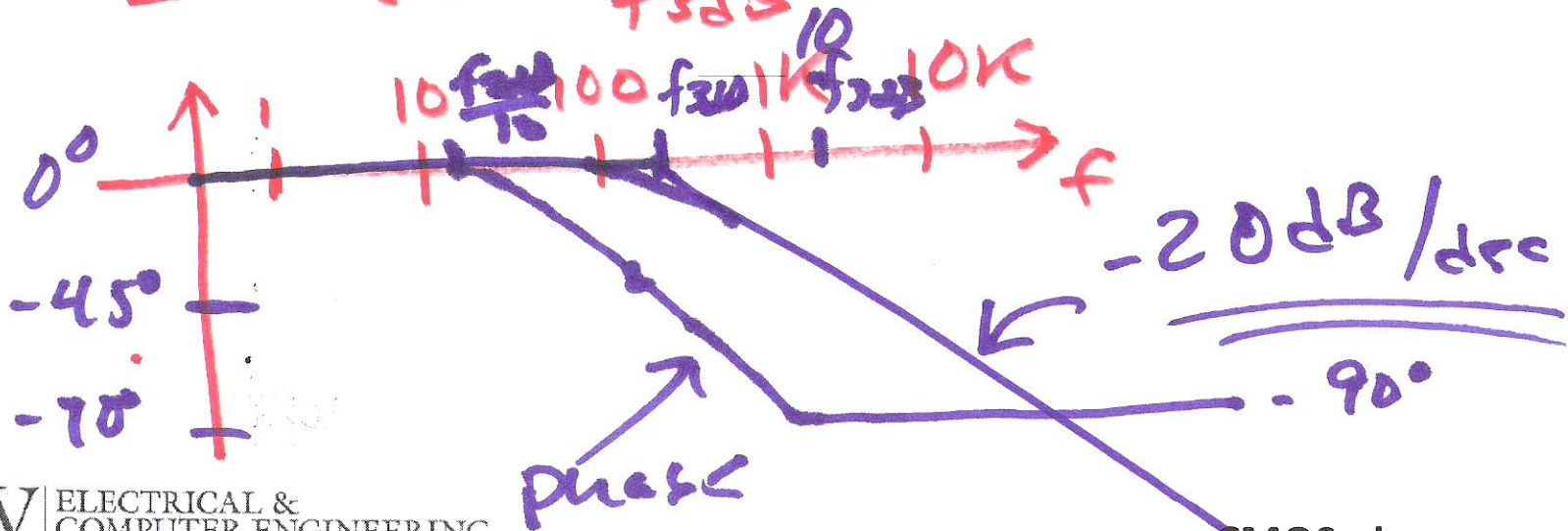

$$\frac{v_{nT}}{v_{in}} = \frac{1}{\sqrt{1 + \left(\frac{f}{f_{3dB}}\right)^2}} = \frac{1}{\sqrt{1 + 16}}$$

$$f = 4 f_{3dB}$$

$$f \gg f_{3dB}$$


$$\left| \frac{v_{nT}}{v_{in}} \right| \approx \frac{1}{\sqrt{\left(\frac{f}{f_{3dB}}\right)^2}} = \frac{1}{\frac{f}{f_{3dB}}}$$

$$20 \log \left| \frac{v_{nT}}{v_{in}} \right| = 20 \log \frac{f_{3dB}}{f} \quad -20dB$$

$$20 \log \frac{f_{3dB}}{10f}$$

$$20 \log \frac{f_{3dB}}{f} + 20 \log \frac{1}{10}$$

5)

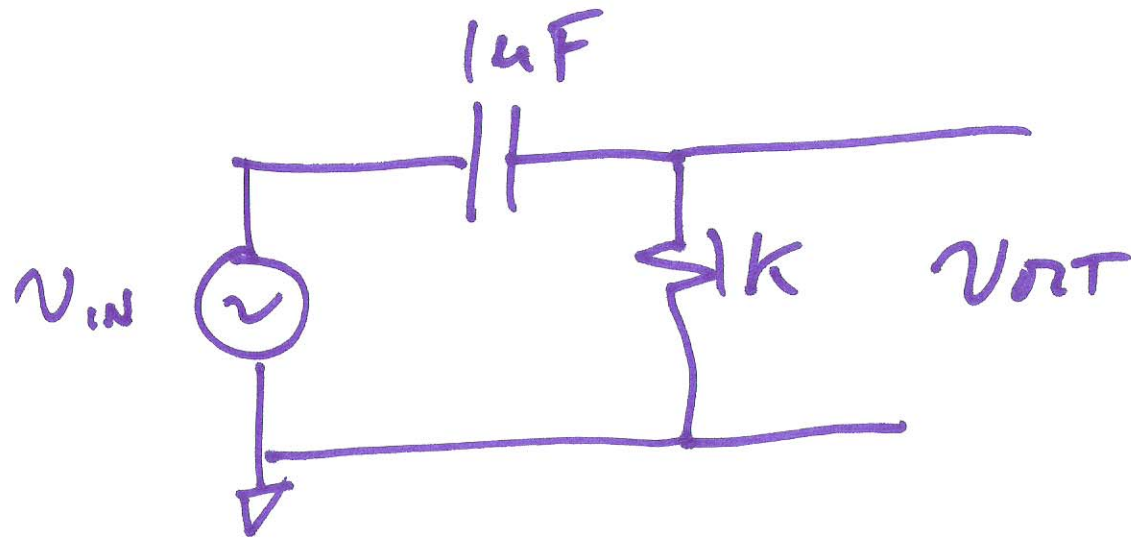

Bode plot

$$\frac{v_{out}}{v_{in}}$$

$$\frac{1}{2\pi RC} = v_{out} = v_{in} \cdot \frac{1k}{1k + \frac{1}{j\omega C}} = \frac{R}{R + \frac{1}{j\omega C}}$$

$$f_c = f_p = \frac{1}{2\pi RC} \left\{ \frac{v_{out}}{v_{in}} \right\} = \frac{0 + j\omega RC}{1 + j\omega RC}$$


$$\frac{v_{out}}{v_{in}} = \frac{0 + j \frac{f}{f_c}}{1 + j \frac{f}{f_p}}$$

b)

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{\sqrt{0^2 + \left(\frac{f}{f_2}\right)^2}}{\sqrt{1^2 + \left(\frac{f}{f_p}\right)^2}} = \frac{f}{f_2} \frac{1}{\sqrt{1 + \left(\frac{f}{f_p}\right)^2}}$$

$f_p = f_2 = 1.59$
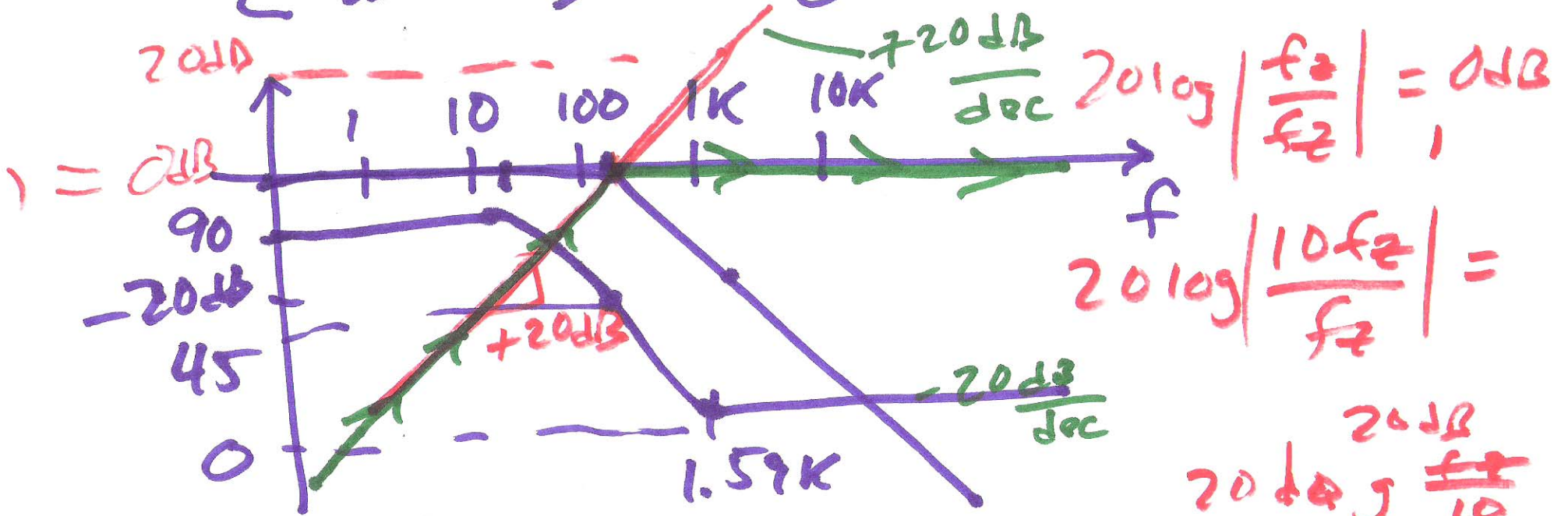
$$\angle \frac{v_{out}}{v_{in}} = \tan^{-1} \frac{f/f_2}{0} - \tan^{-1} \frac{f}{f_p}$$



$$\left| \frac{v_{out}}{v_{in}} \right| = -12 \text{ dB}, \quad \angle \frac{v_{out}}{v_{in}} = 76^\circ$$

$$\theta = \frac{t_d}{T} \cdot 360$$

$$\frac{1}{2} \cdot \frac{1}{2} = \frac{1}{4} = -12 \text{ dB} = -6 \text{ dB} - 6 \text{ dB}$$

$$40 \text{ Hz} \rightarrow T =$$

$$10 \text{ Hz} \rightarrow 0.1 \text{ s} \quad 0.025 \text{ s}$$

$$25 \text{ ns} \cdot \frac{76}{360} = \underline{\underline{5.28 \text{ ns}}}$$

v_{out} leads v_{in} !