

EE 220

Lecture 12D

$$\frac{V_{out}}{V_{in}} =$$

$$\frac{s/c}{(s + \frac{1}{\sqrt{LC}})(s - \frac{1}{\sqrt{LC}})}$$

July 9, 2014

RLC

Circuits

$$s = j\omega$$

$$sL + \frac{1}{sC}$$

DC $s \rightarrow 0$

$f = \infty$ $s \rightarrow \infty$



$$\frac{s/c}{(s + \frac{1}{\sqrt{LC}})(s - \frac{1}{\sqrt{LC}})}$$

$$(s + \frac{1}{\sqrt{LC}})(s - \frac{1}{\sqrt{LC}})$$


$$s_p = \frac{1}{\sqrt{LC}}$$

SECOND-ORDER CKT

$$f_{p1} = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{sL + \frac{1}{sC}}{s^2L + 1/C}$$

1)


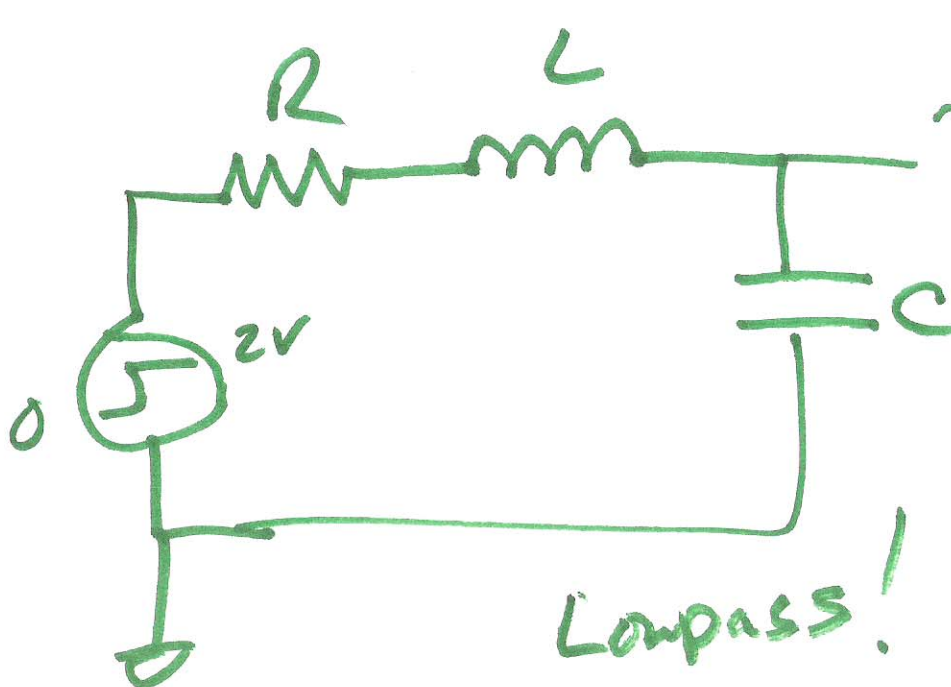


$$V_{out} = V_{in} \cdot \frac{\frac{1}{sC}}{\frac{1}{sC} + Ls + R}$$


$$\frac{V_{out}}{V_{in}} = \frac{1}{s^2LC + sRC + 1}$$

Lowpass!

underdamped

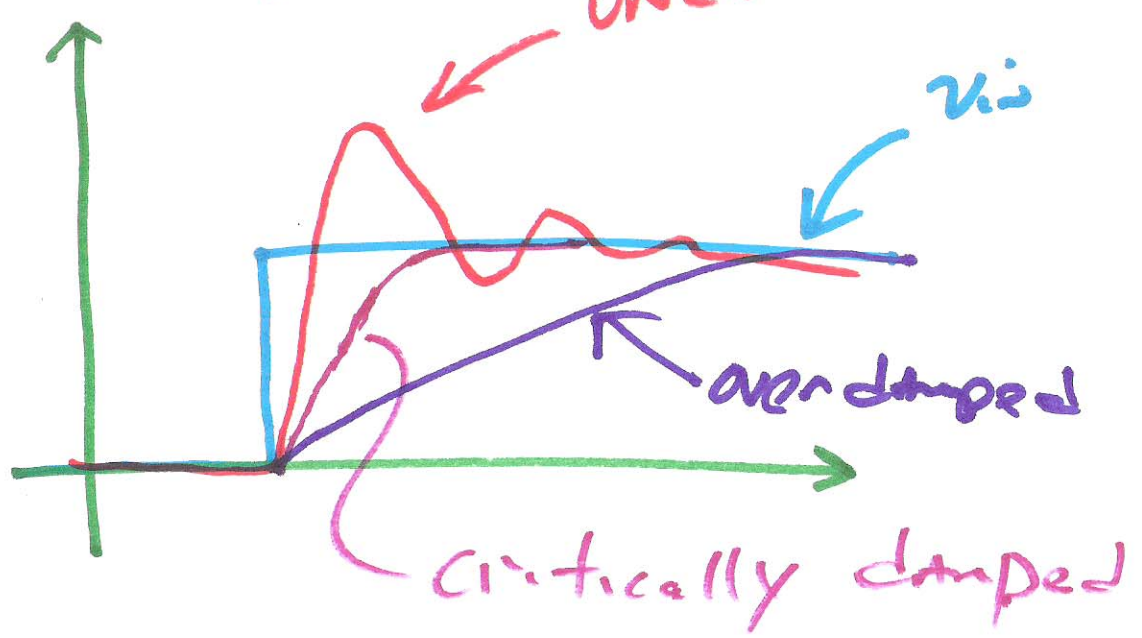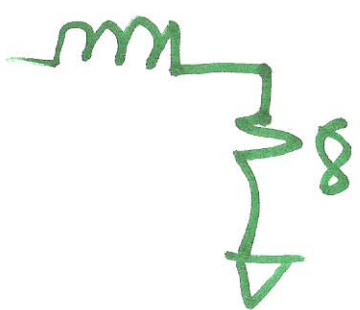


2)

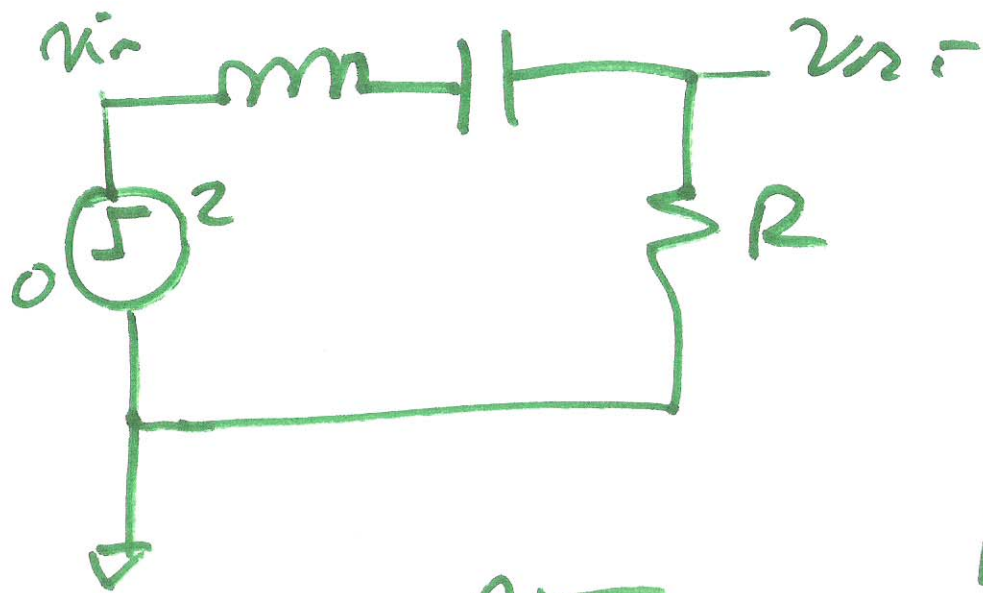

BAND Pass


$$\frac{v_{out}}{v_{in}} = \frac{R}{R + sL + \frac{1}{sC}}$$

$$= \frac{sRC}{s^2LC + sRC + 1}$$

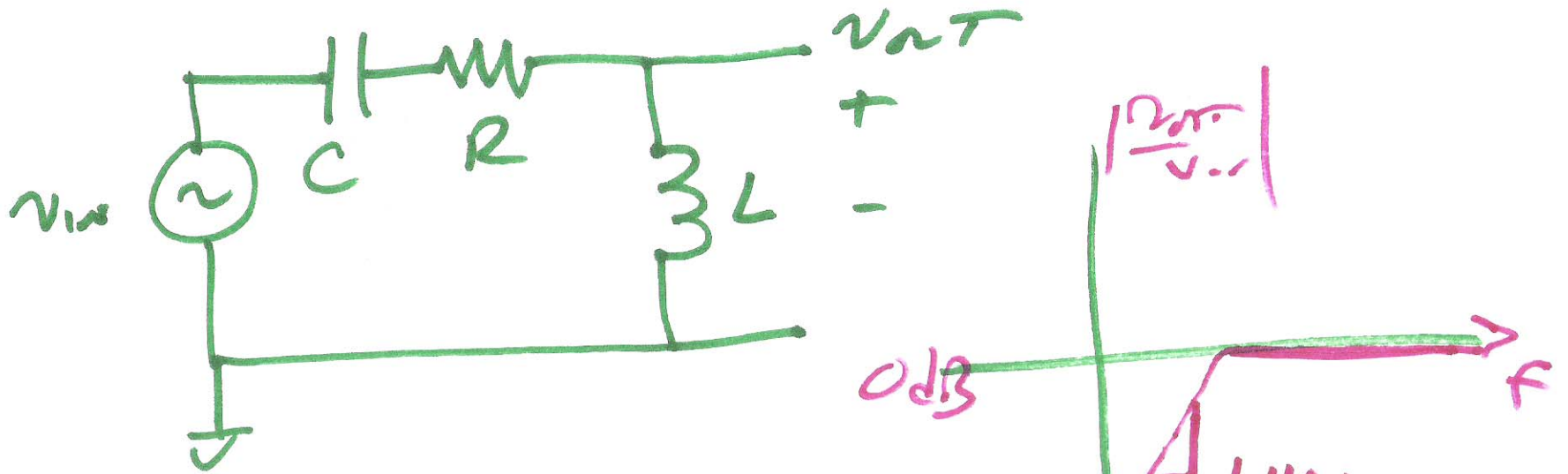

$$\frac{v_{out}}{v_{in}} = \frac{sL}{sL + \frac{1}{sC} + R}$$

$$= \frac{s^2LC}{s^2LC + sRC + 1}$$

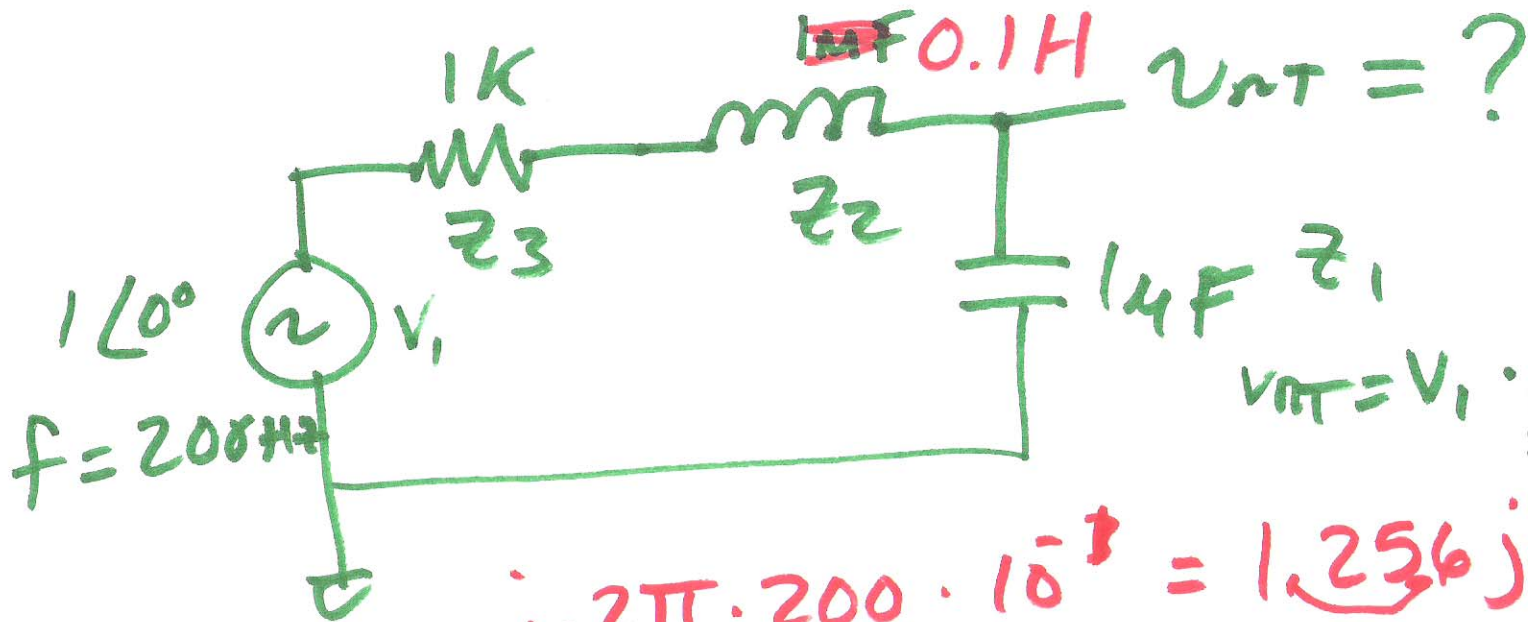

$$v_{out} = v_1 \cdot \frac{z_1}{z_1 + z_2 + z_3}$$

$$j \cdot 2\pi \cdot 200 \cdot 10^{-3} = 1.256j = 125.6j$$

\parallel
 z_2

$$\frac{-j}{2\pi \cdot 200 \cdot 10^{-6}} = -796j = z_1$$



$$\frac{v_{out}}{v_{in}} = \frac{0 + j(-796)}{j(-796 + 125.6) + 1000}$$

$180 + 90 = 270$
 -90

-670

5)

$$| \frac{v_{out}}{v_{in}} | = \frac{796}{\sqrt{10^6 + 670^2}}$$
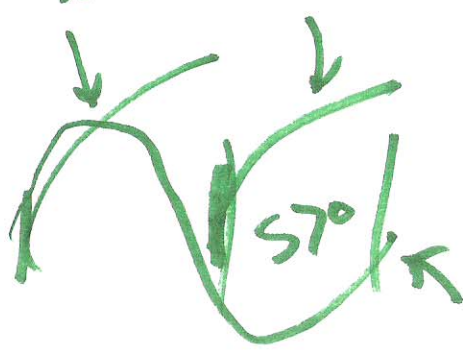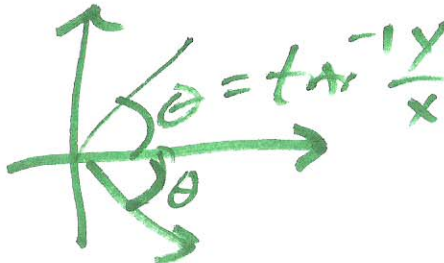
$$= \boxed{0.66}$$



$$-57^\circ \quad \angle \frac{v_{out}}{v_{in}} = 270 + \tan^{-1} \frac{670}{1000}$$

$$= 270 + 33.8 \quad 303.8^\circ$$

$$\frac{t_d \cdot 360}{5ms} = 303.8$$

$$t_d = \frac{303}{360} \cdot 5ms = \underline{\underline{4.2ms}}$$