

# Lecture 13

June 25, 2014



Quiz #11 EE 220 Summer 2014

Name: \_\_\_\_\_

Closed book and notes.



Show your work for credit!

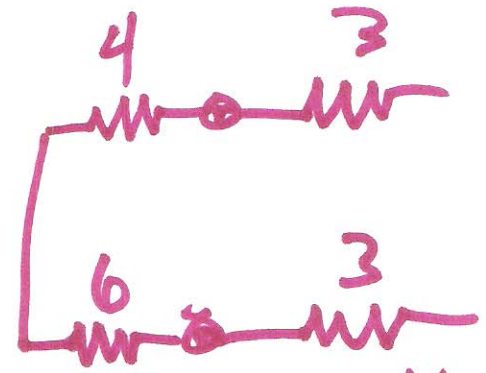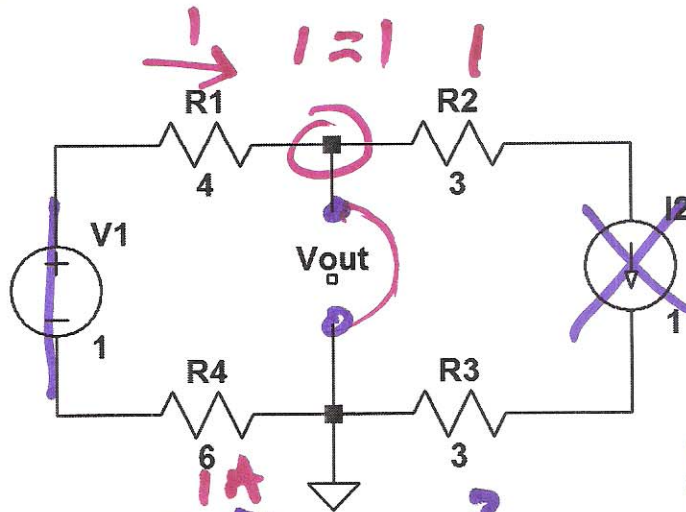- Find the Thevenin and Norton equivalents at the terminals adjacent to  $V_{out}$  in the following circuit. Again, show your work for credit.









$I = \frac{V}{R_{TH}}$

$R_{TH} = 10$

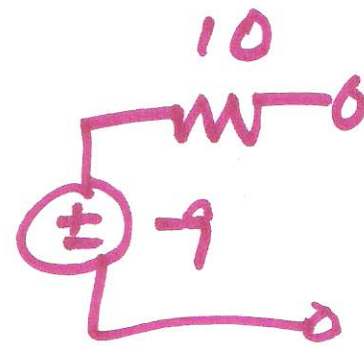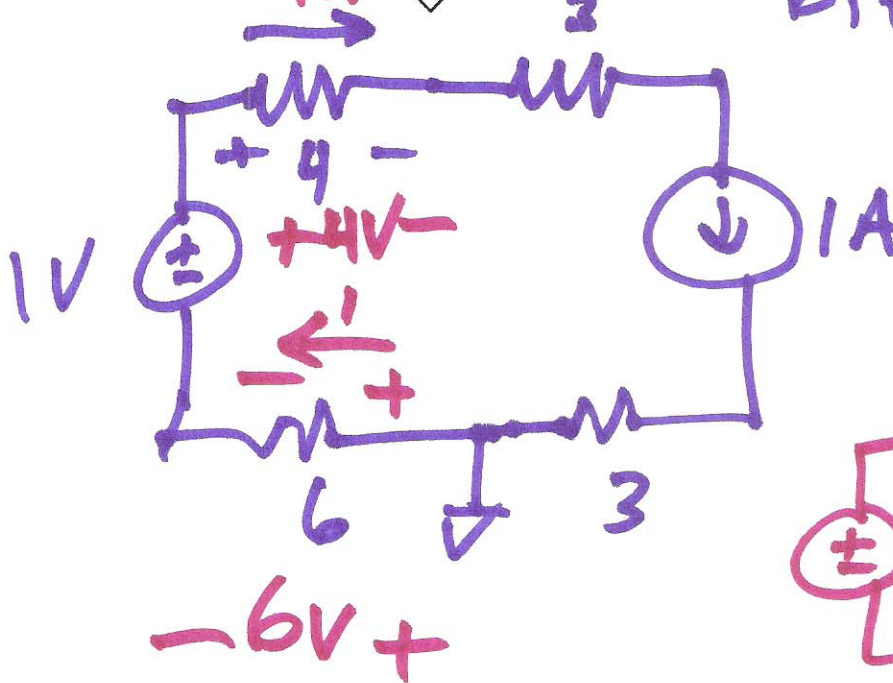


$-6 + 1 - 4 = V_{oc} = -9V$

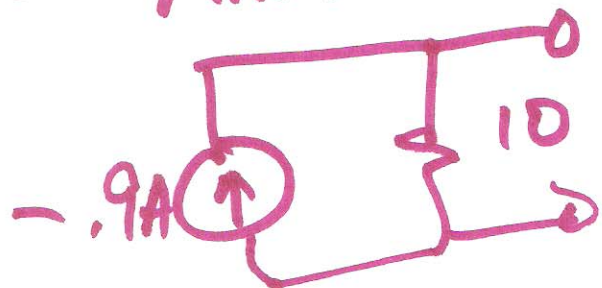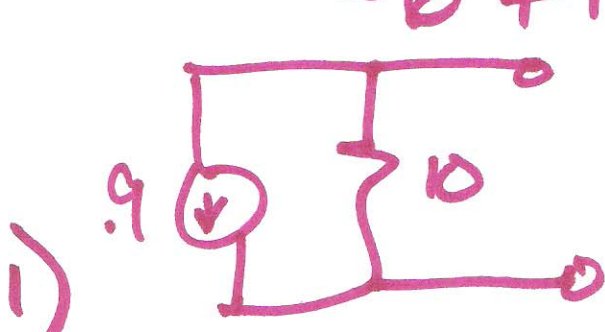

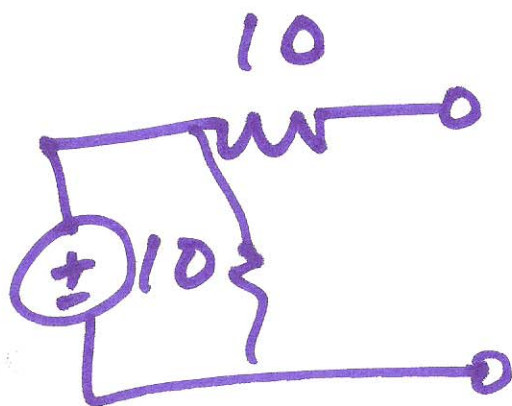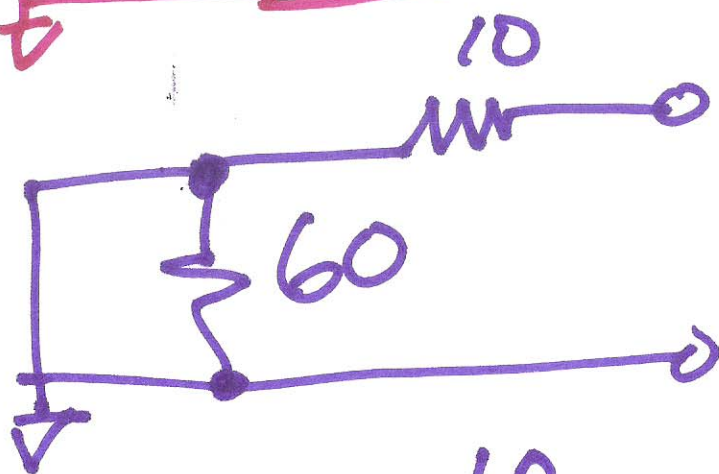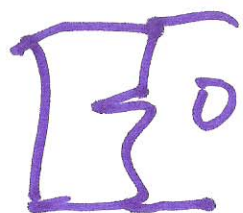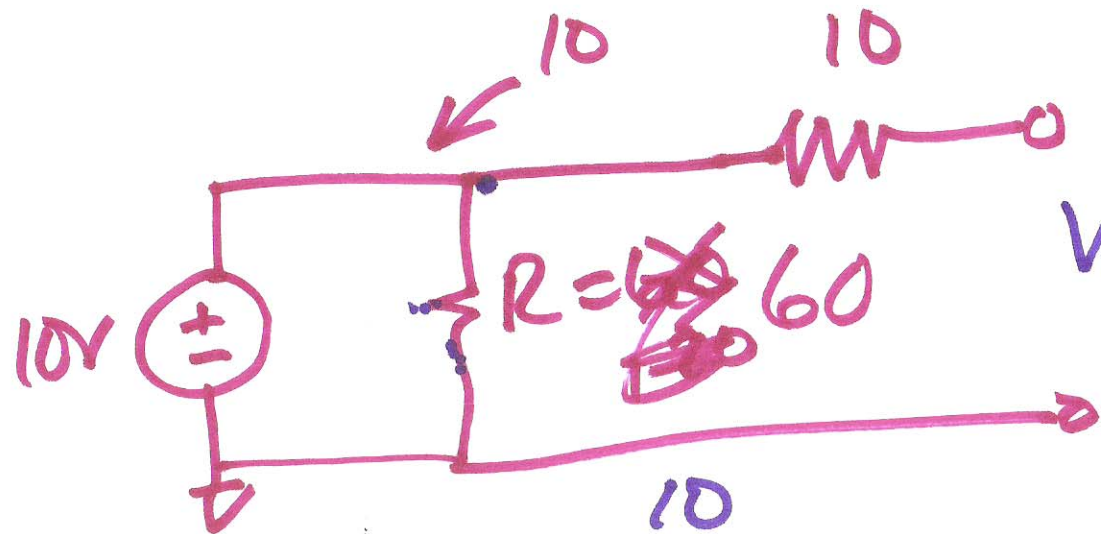

2)

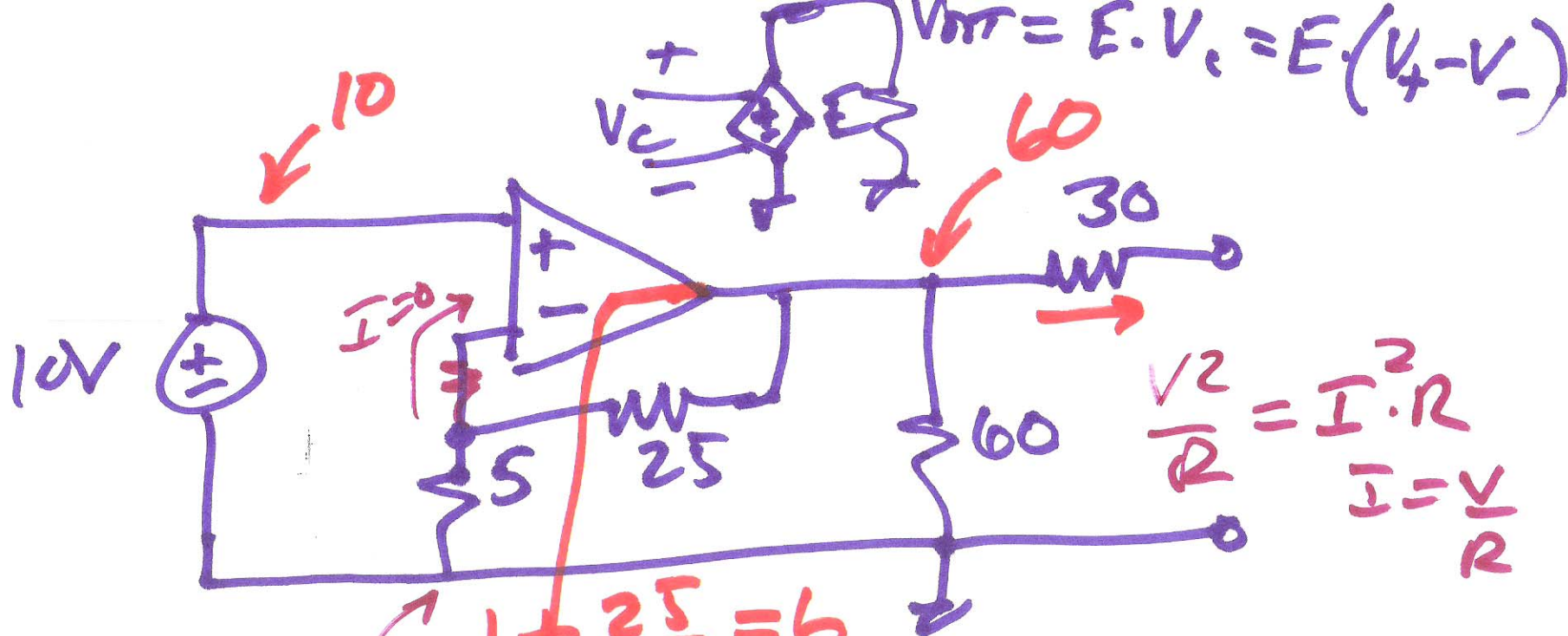


$$\frac{V^2}{R} = I^2 \cdot R$$

$$I = \frac{V}{R}$$

$$1 + \frac{25}{5} = 6$$

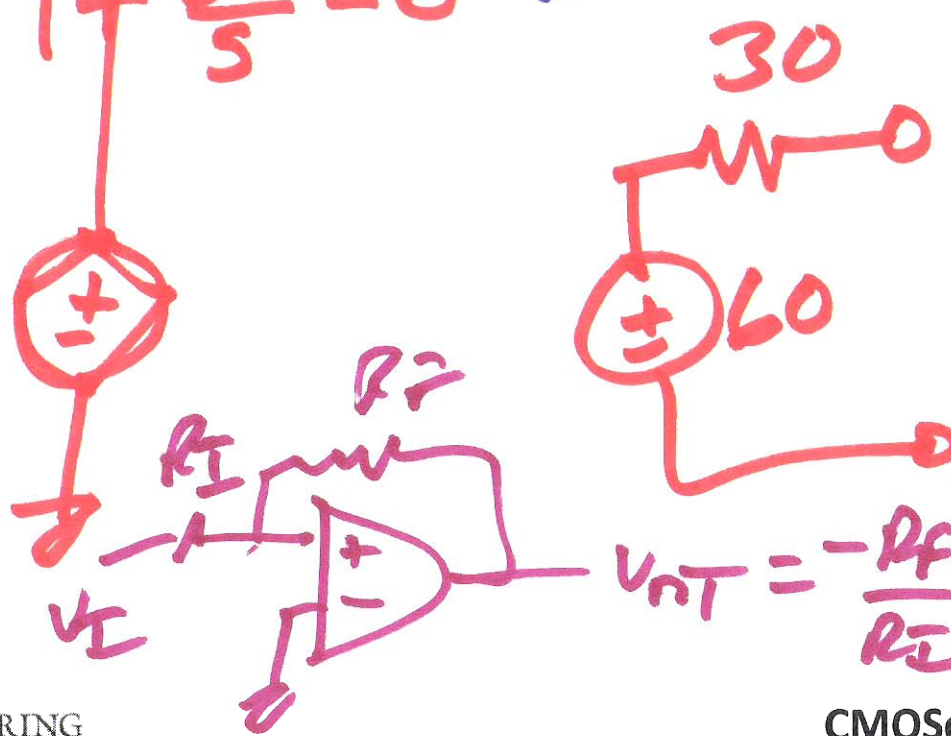
$$\frac{60^2}{60\Omega} + \frac{60^2}{30}$$




$$V_{out} = -\frac{R_F}{R_I} \cdot V_I$$

3)

# Capacitors & Inductors

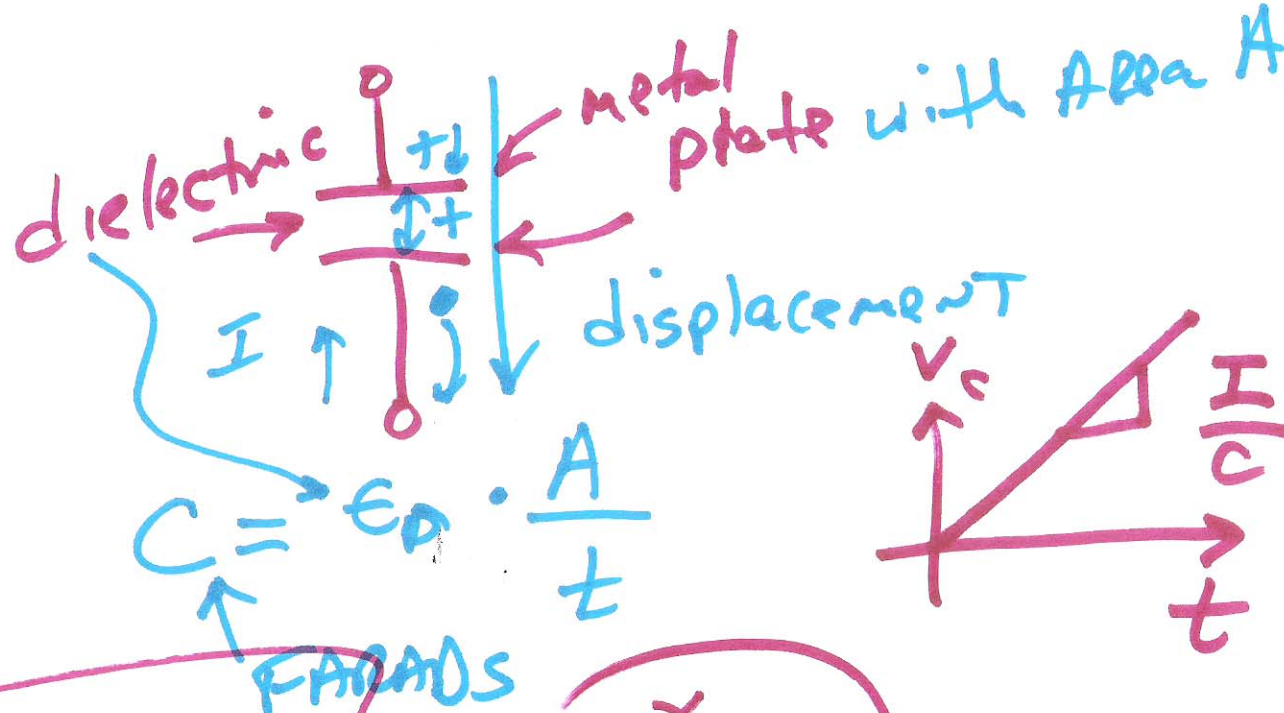


$$I = C \frac{dv_c}{dt}$$

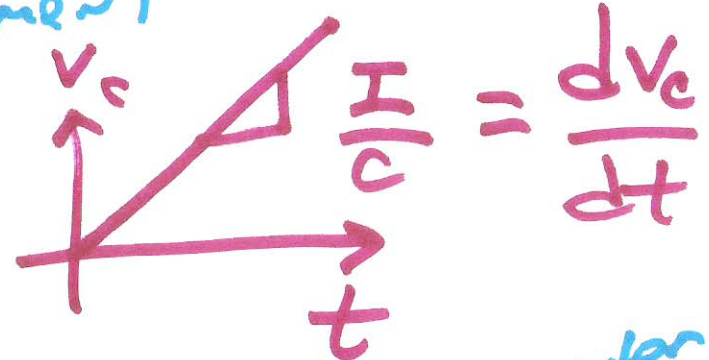


$$Q = C \cdot v_c$$

$$E = \frac{1}{2} C v_c^2$$

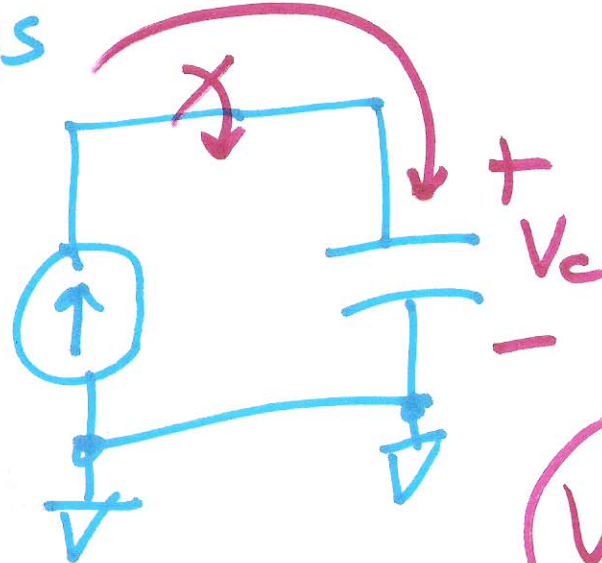
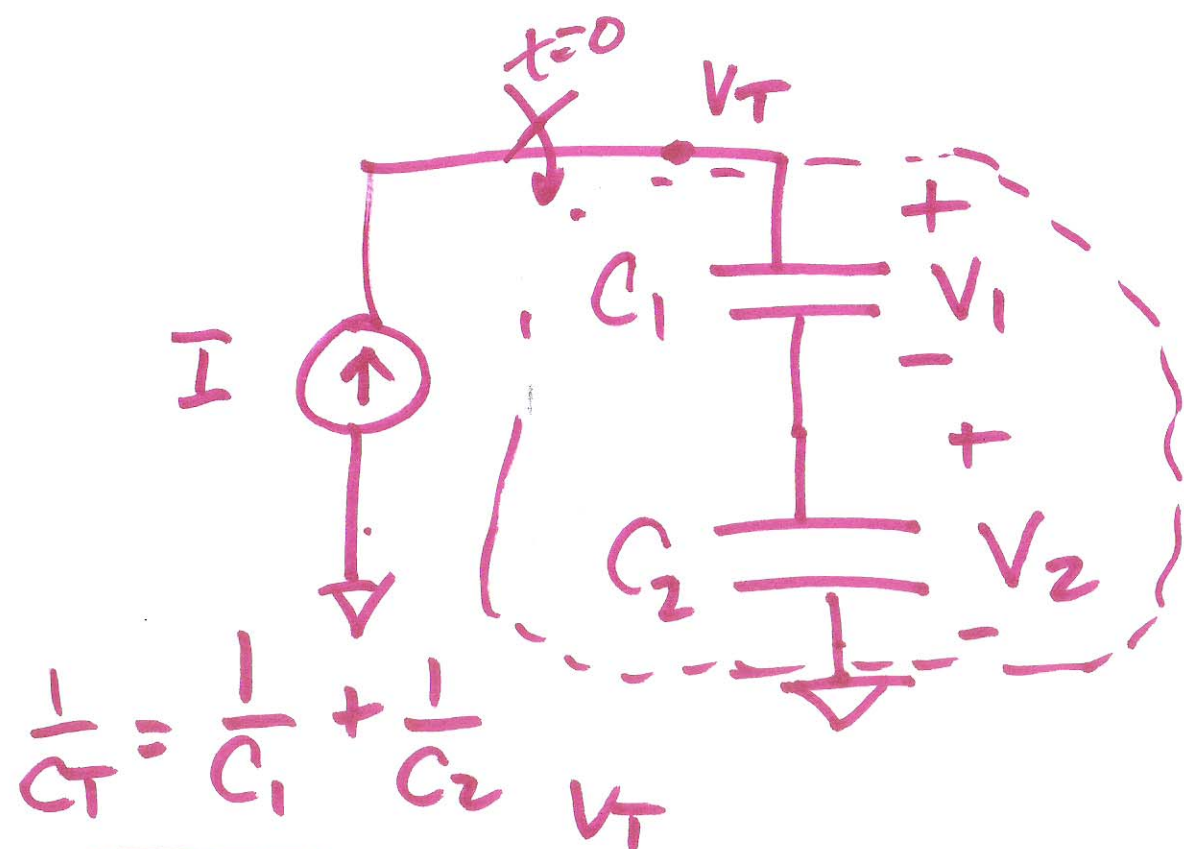
$$v_c = \frac{1}{C} \int_0^t I \cdot dt$$



$$I = C \frac{dV}{dt}$$


$$V = \frac{1}{C} \int I \cdot dt$$

$$CV = Q$$

$$Q_1 = C_1 V_1 = Q_2 = C_2 V_2$$

$$V_T = V_1 + V_2$$
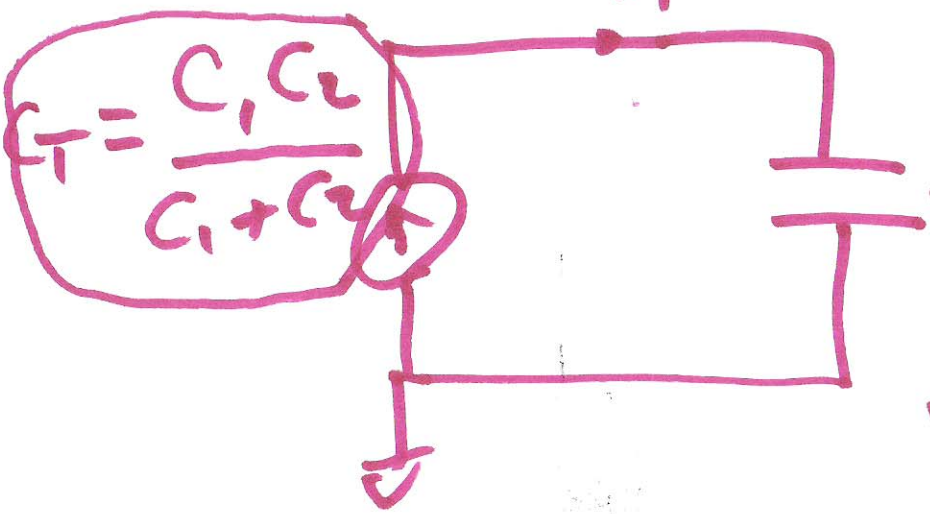
$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2}$$




$$V_T = \frac{1}{C_1} \int I \cdot dt + \frac{1}{C_2} \int I \cdot dt$$

$$V_T = \left( \frac{1}{C_1} + \frac{1}{C_2} \right) \int I \cdot dt$$

$$= \frac{1}{C_T} \int I \cdot dt$$

CMOSedu.com

5)

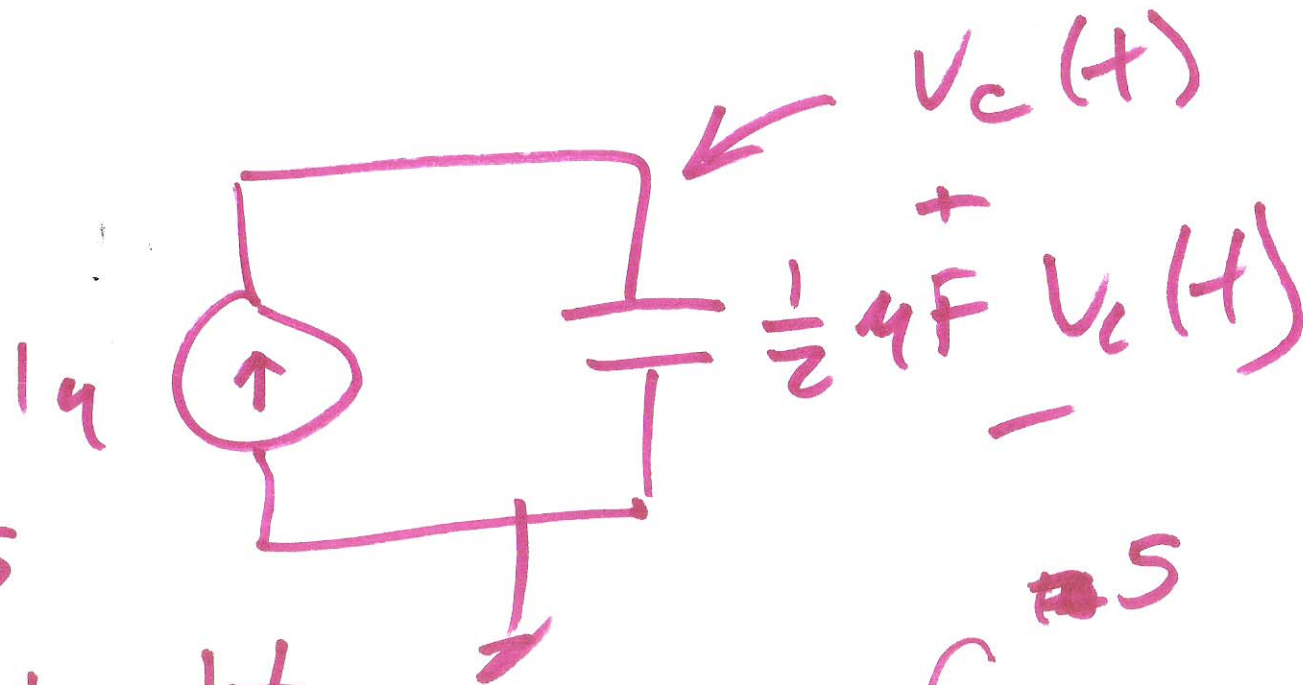

$$= \frac{1}{.84} \int_0^5 14 \cdot dt$$


$$= \frac{5 \cdot 14}{.84} = \underline{\underline{6.25V}}$$

$$V_c(t) =$$

$$= \frac{1}{\frac{1}{2} \cdot 4} \int_0^5 14 \cdot dt$$

$$= \frac{5 \cdot 14}{\frac{1}{2} \cdot 4} = 10 \text{ V}$$

6)

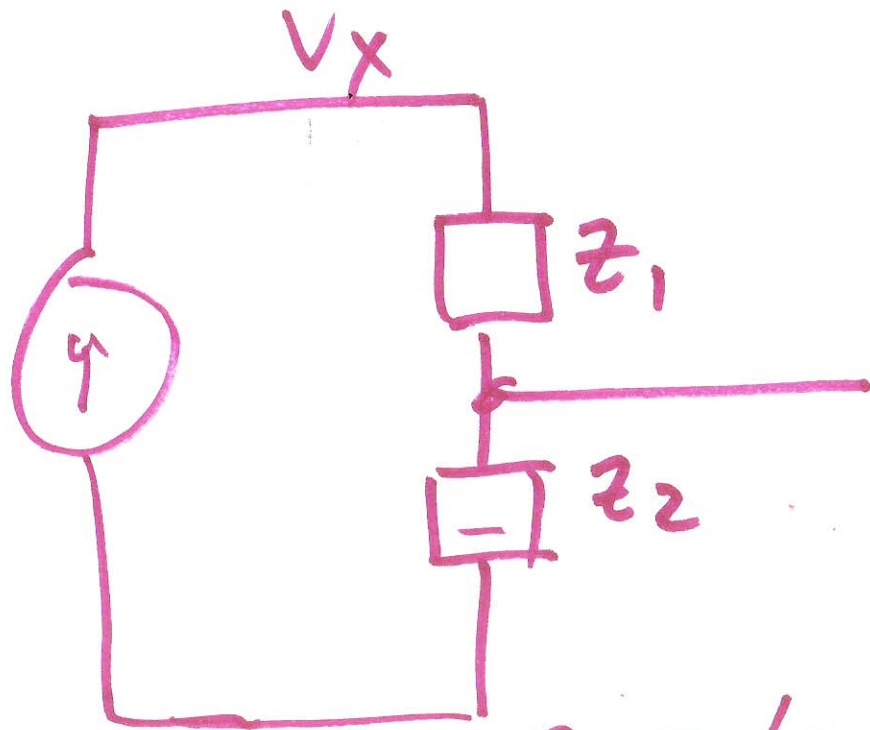

$$\frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} \Rightarrow \frac{1}{\frac{1}{C_T}} = \frac{C_1 C_2}{C_1 + C_2}$$

$$V_y = V_x \cdot \frac{z_2}{z_2 + z_1}$$

$$= V_x \cdot \frac{j\omega C_1 C_2 \left(\frac{1}{j\omega C_2}\right)}{j\omega C_1 C_2 \left(\frac{1}{j\omega C_2} + \frac{1}{j\omega C_1}\right)}$$

$$C_1 = 1\mu$$

$$C_2 = 4\mu$$

$$V_y = \frac{1}{C_2} \int I \cdot dt$$

$$V_x - V_y = \frac{1}{C_1} \int I \cdot dt$$

$$V_x \cdot \frac{C_1}{C_1 + C_2}$$

$$V_x \cdot \frac{1}{5}$$

$$1.25 = \frac{6.25}{5}$$

7)

$\Rightarrow$

$$V_X = \frac{1}{C_1} \int I \cdot dt$$

$$V_Y = \frac{1}{C_2} \int I \cdot dt$$

$$V_X \cdot C_T = \int I \cdot dt$$

$$V_Y \cdot C_2 = \int I \cdot dt$$


$$C_T = \frac{C_1 \cdot C_2}{C_1 + C_2}$$

$$V_X \cdot C_T = V_Y \cdot C_2$$

$$V_X \cdot \frac{C_1}{C_1 + C_2} = V_Y$$

8)



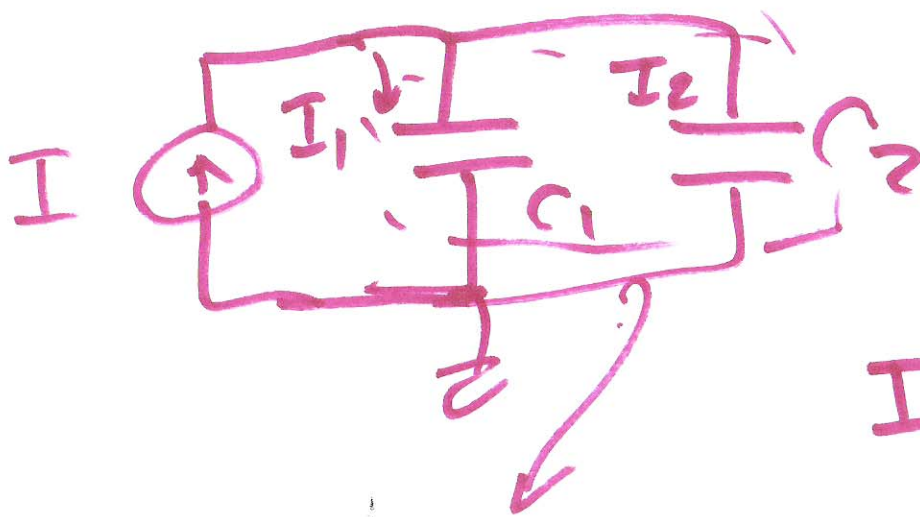

$$I = C \frac{dV}{dt}$$






$$I = I_1 + I_2$$

$$= C_1 \cdot \frac{dV_c}{dt} + R_2 \cdot \frac{dV_c}{dt}$$


$$= (C_1 + R_2) \frac{dV_c}{dt}$$

$C_T$

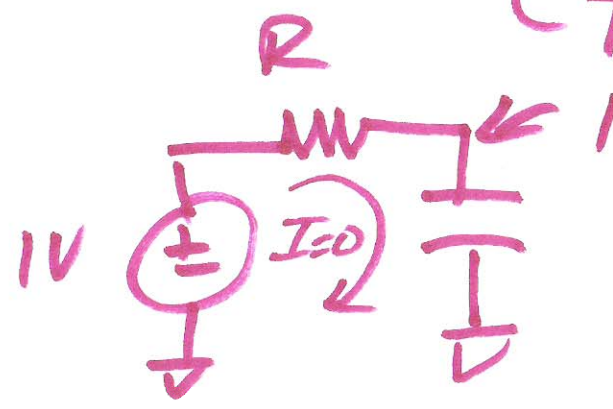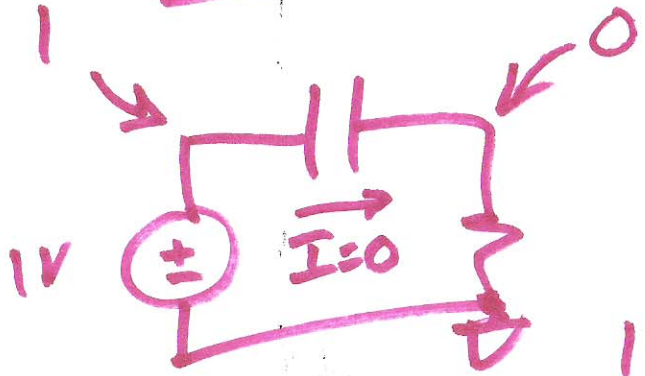
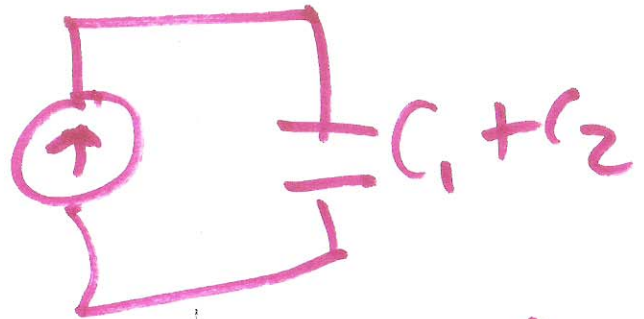


$\frac{1}{s}$  for DC is an open!

9)

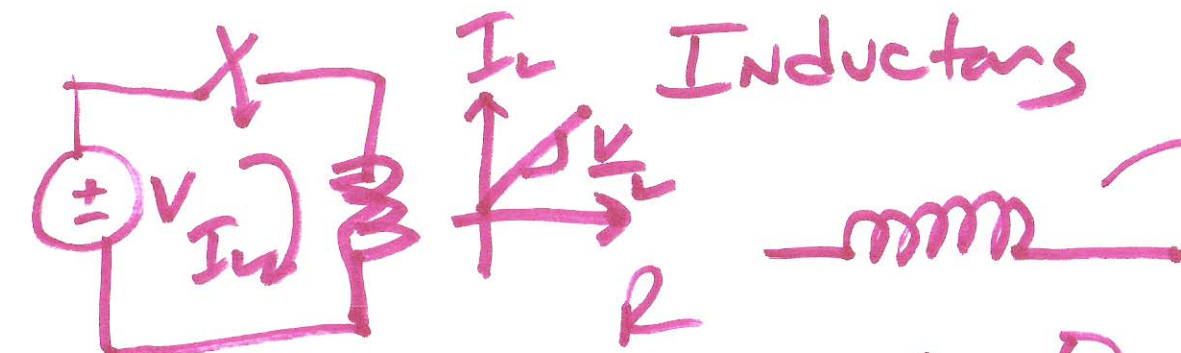



for DC inductors are wires!

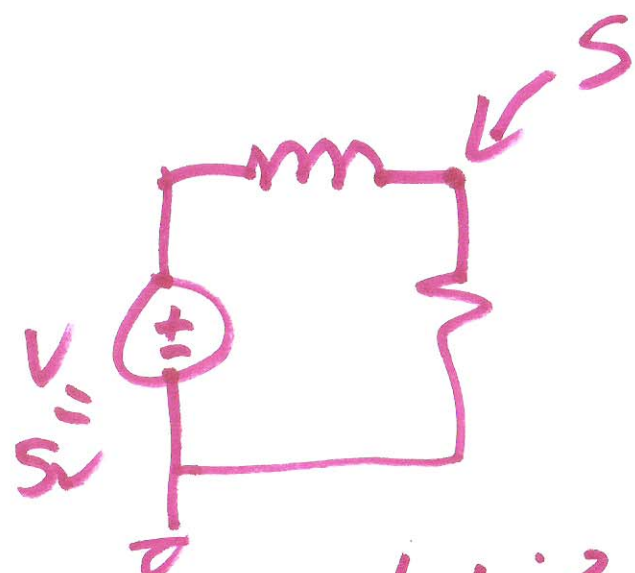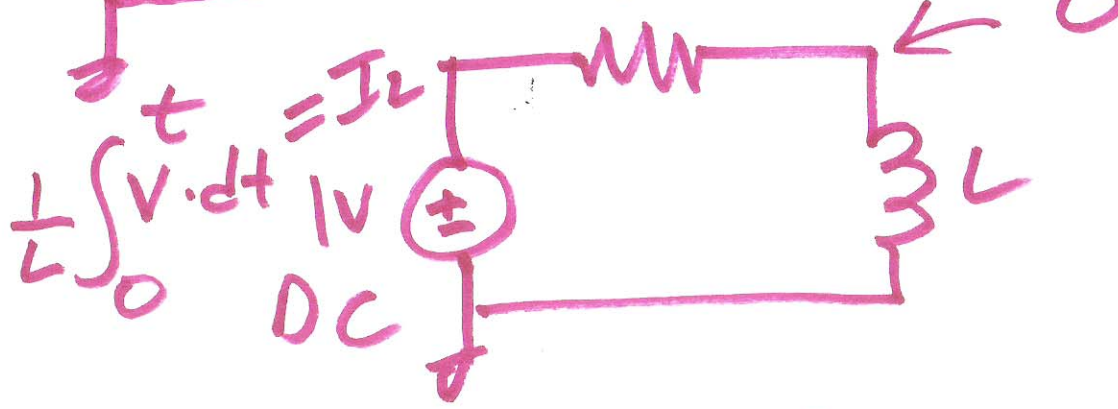


$$E = \frac{1}{2} L i^2$$

$$V_L = L \cdot \frac{dI}{dt}$$

$$I = \frac{1}{L} \int V_L \cdot dt$$

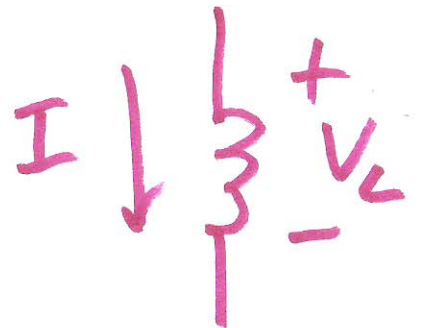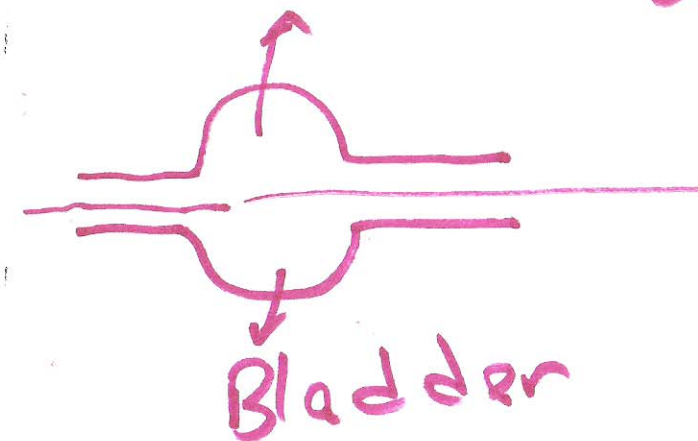

10)

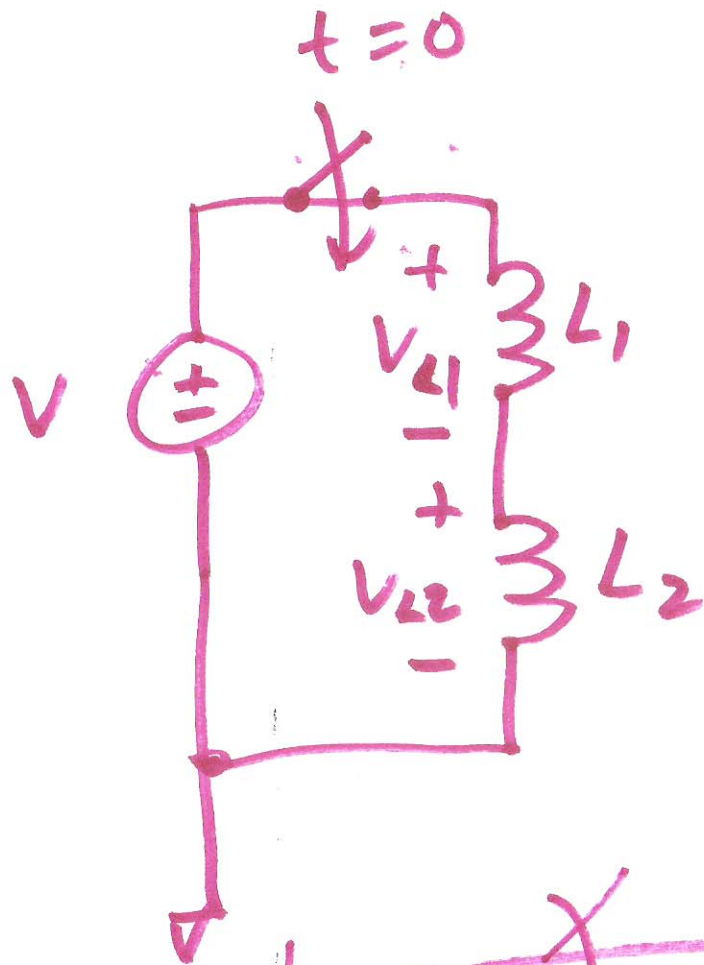


$$I = \frac{1}{L} \int v \cdot dt$$


$$V = V_{L1} + V_{L2}$$

$$= L_1 \frac{dI}{dt} + L_2 \frac{dI}{dt}$$
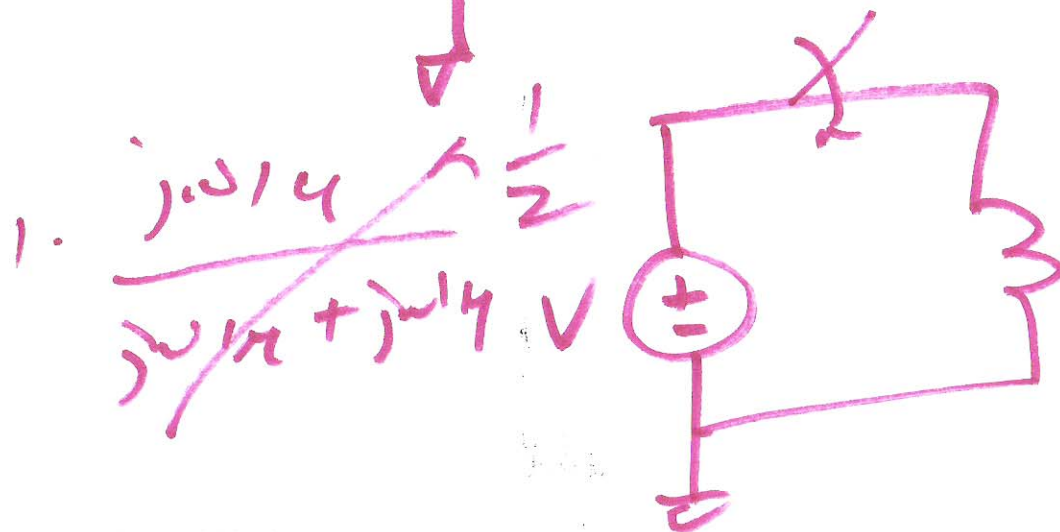
$$= \underbrace{(L_1 + L_2)}_{L_T} \frac{dI}{dt}$$




$$L_T = L_1 + L_2$$

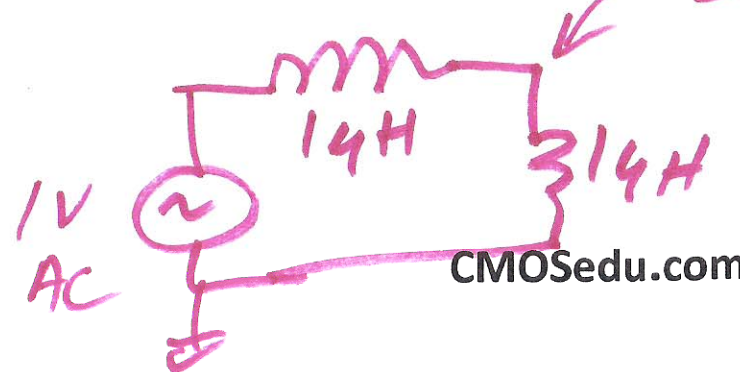

CMOSedu.com

ii)

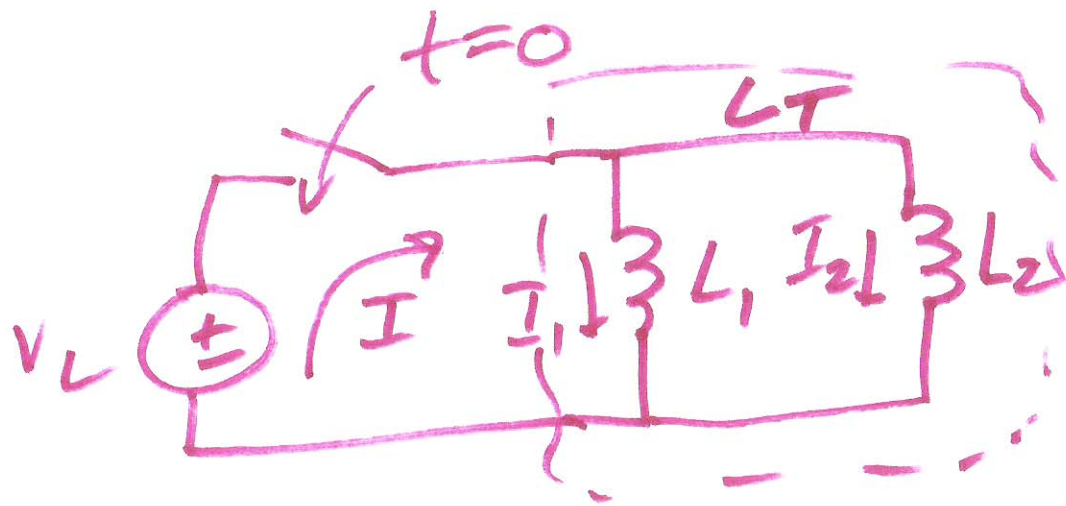

$$I = \frac{1}{L} \int V \cdot dt$$

$$I = I_1 + I_2$$

$$V = L_1 \frac{dI_1}{dt}$$

$$\frac{1}{L_T} \int V \cdot dt = \frac{1}{L_1} \int V \cdot dt + \frac{1}{L_2} \int V \cdot dt$$

~~$$V = L_T \frac{dI}{dt} = L_1 \cdot \frac{dI_1}{dt} = L_2 \frac{dI_2}{dt}$$~~

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2}$$

$$L_T = \frac{L_1 L_2}{L_1 + L_2}$$