

EE 220



6/30/14

$v_x = \frac{I_x}{2} - 3I_x = -\frac{5I_x}{2}$ Lecture 15

Problem

39


Focus!

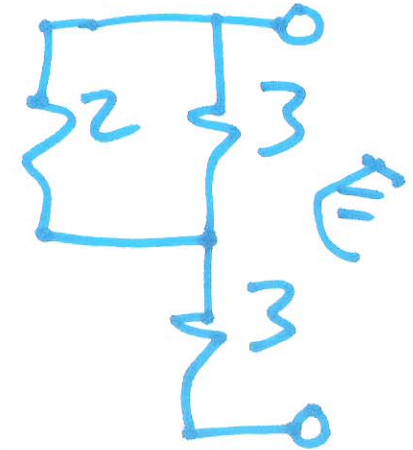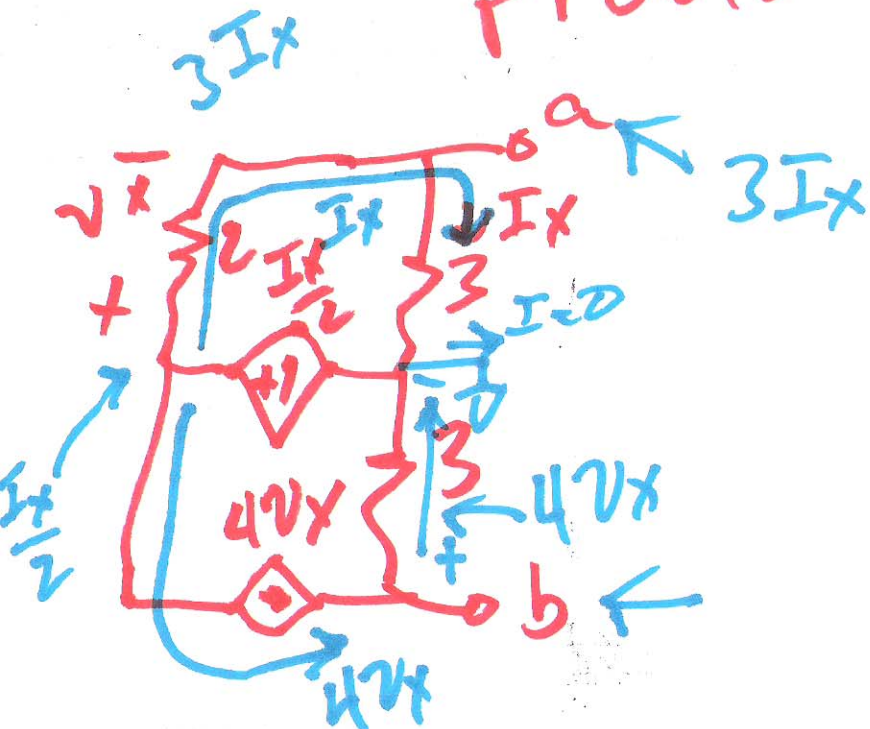


$$3 + \frac{2 \parallel 3}{2} = 4.2$$

$$\frac{-\frac{5I_x}{2}}{2} = I_x$$

$I_x = 0$
$v_x = 0$

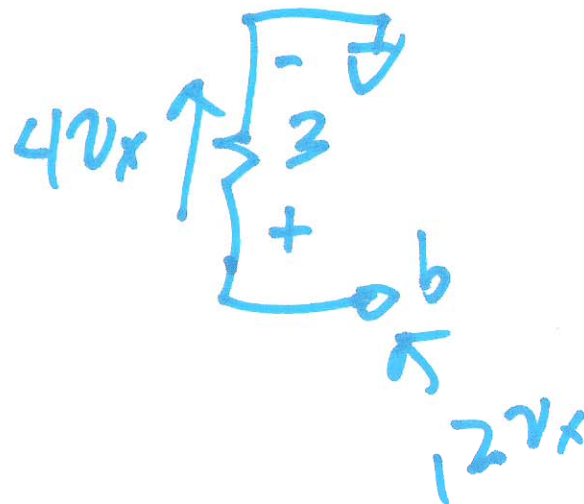

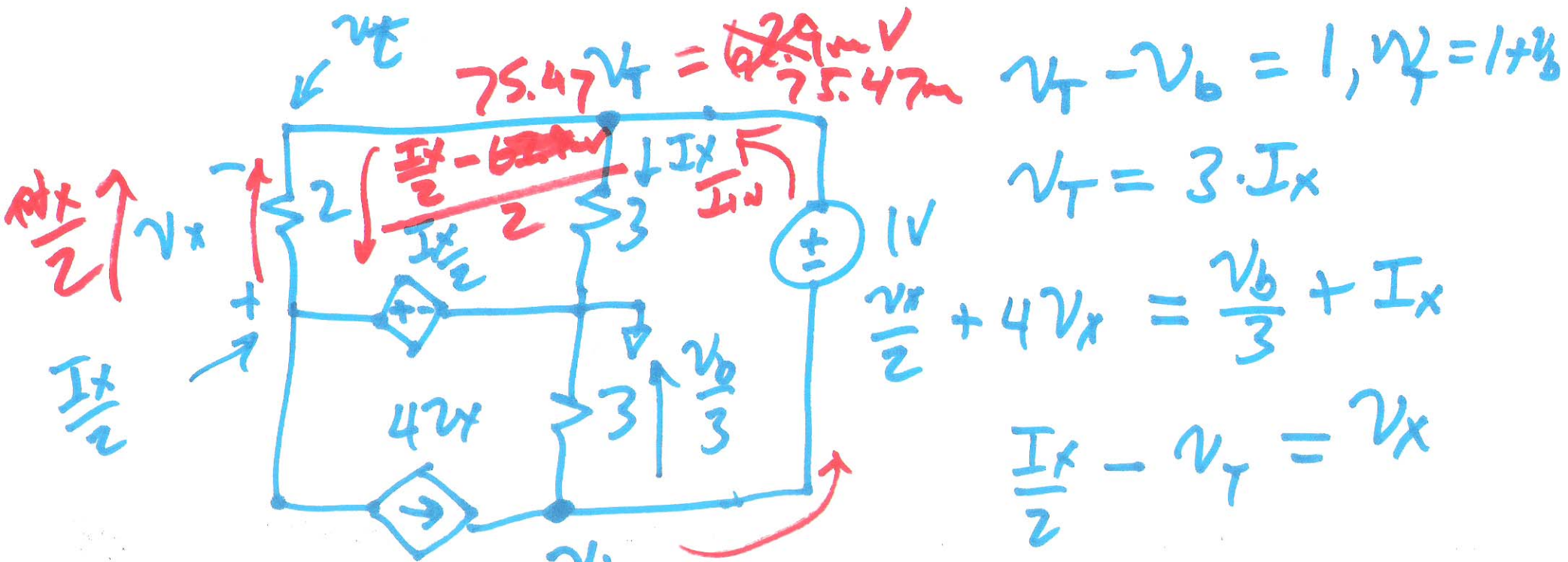

$$4.5v_x = I_x - \frac{1}{3} + I_x$$

$$1 + v_b = 3I_x, \quad v_b = 3I_x - 1$$

$$\frac{I_x}{2} - 1 - 3I_x + 1 = v_x$$

$$v_x 4.5 = \frac{v_b}{3} + I_x$$

$$4.5v_x = 2I_x - \frac{1}{3}$$

$$\frac{I_x}{2} - 1 - v_b = v_x$$

$$13.5v_x = 6I_x - 1$$

2)

$$13.5V_x = 6I_x - 1$$

$$-5I_x = 2V_x, V_x = -2.5 I_x$$

$$13.5 \cdot (-2.5) \cdot I_x = 6I_x - 1$$

$$6I_x + 33.75I_x = 1$$

$$39.75I_x = 1$$

$$\underline{\underline{I_x = 25.16 \text{ mA}}}$$

$$\frac{.02516}{2} - .07547$$

$$2$$

$$= -31.44 \text{ mA}$$

$$I_{in} = 25.16 \text{ mA}$$
$$+ 31.44 \text{ mA}$$

$$56.60 \text{ mA}$$

$$V_T = 75.47 \text{ mV}$$

$$V_x = 62.9 \text{ mV}$$

$$\frac{1V}{.0566} = 17.66 \text{ J}$$

3)

Quiz


$1.2 \angle 0^\circ$

$500k$

0.112

$500k$

$T = 24s$

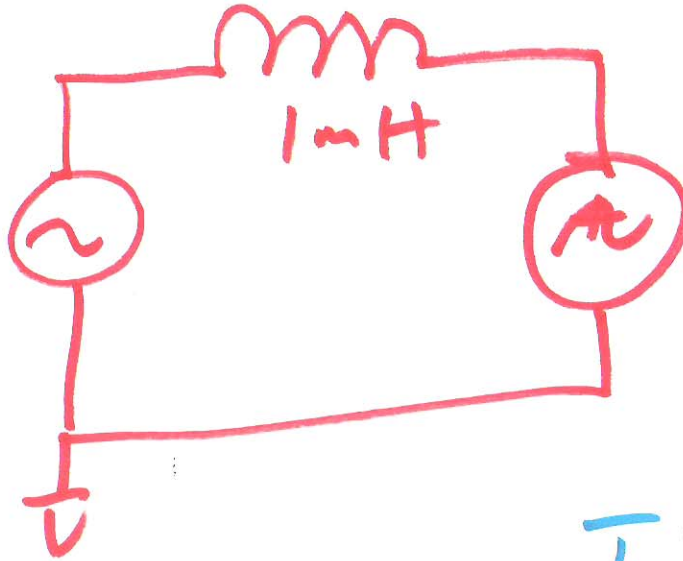

$$\theta = \frac{t_d}{T} \cdot 360, \quad t_d = \frac{131}{360} \cdot 24s = \underline{\underline{739s}}$$

$0.8 \angle 45^\circ$

$\sin(0.8 \text{ Srad} - 2.5 \text{ rad})$





$$I = \frac{1.2 \angle 0 - 0.8 \angle 45}{0 + j \cdot 2\pi \cdot 500k \cdot 10^{-3}}$$

$$= \frac{1.2 + j0 - .566 - j.566}{0 + j3140}$$

$$= \frac{.634 - j.566}{0 + j3140}$$


$$2714A = \frac{.85 \angle -41.75^\circ}{3140 \angle 90^\circ}$$

4)

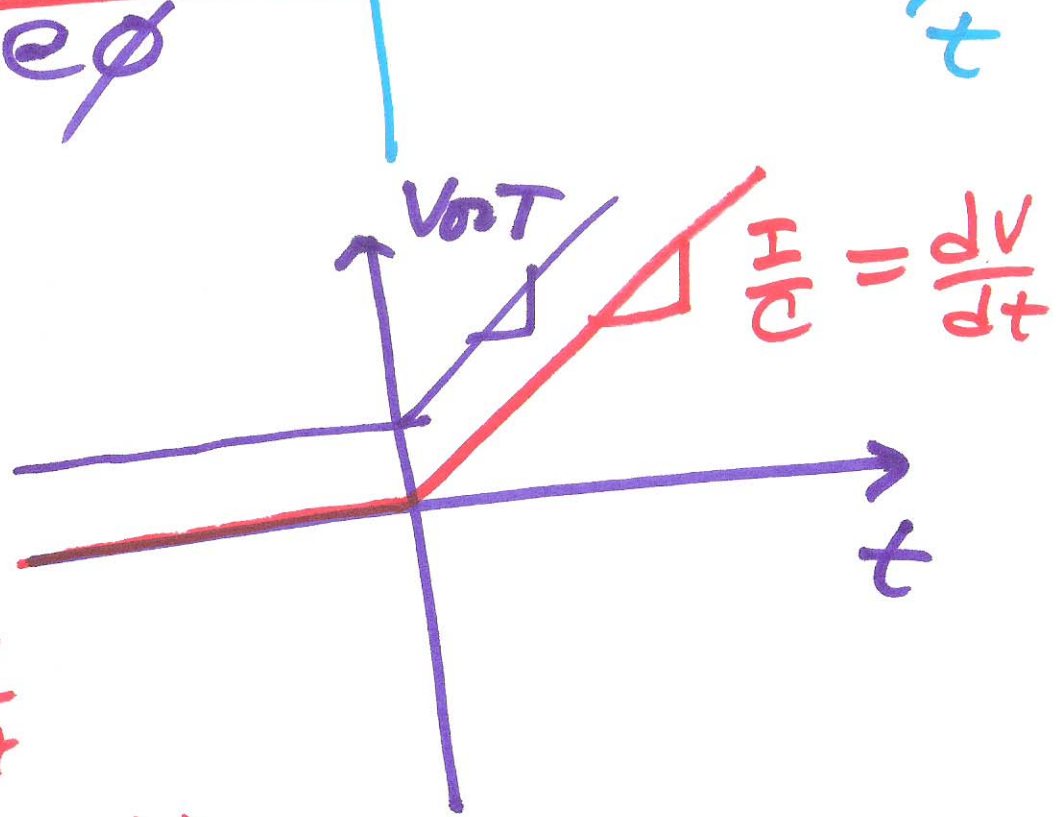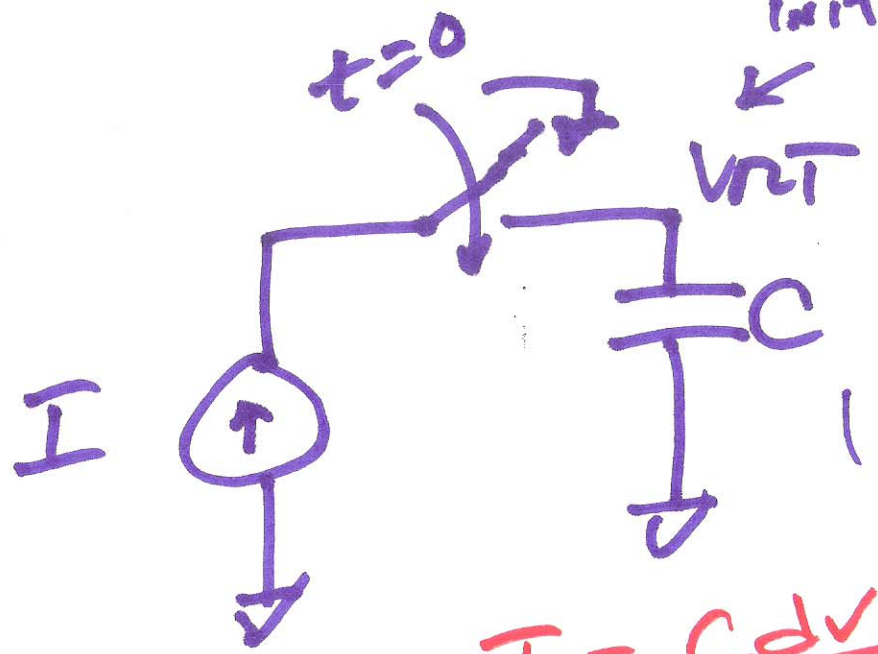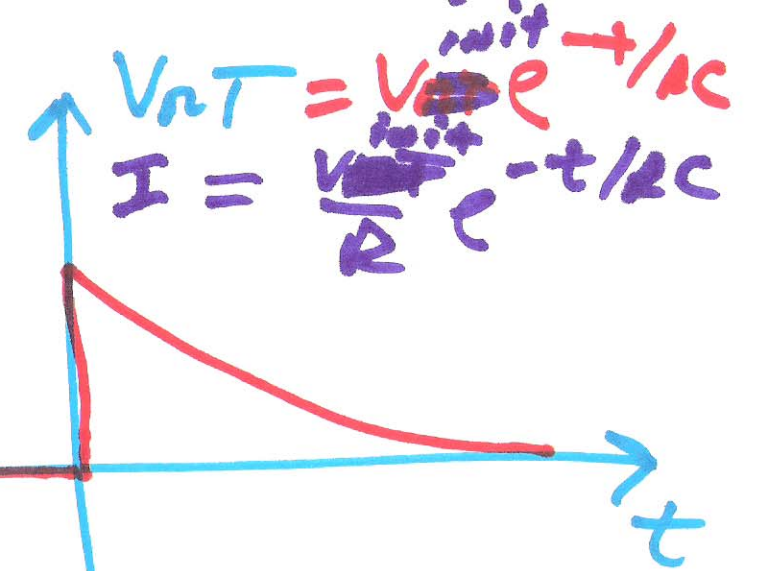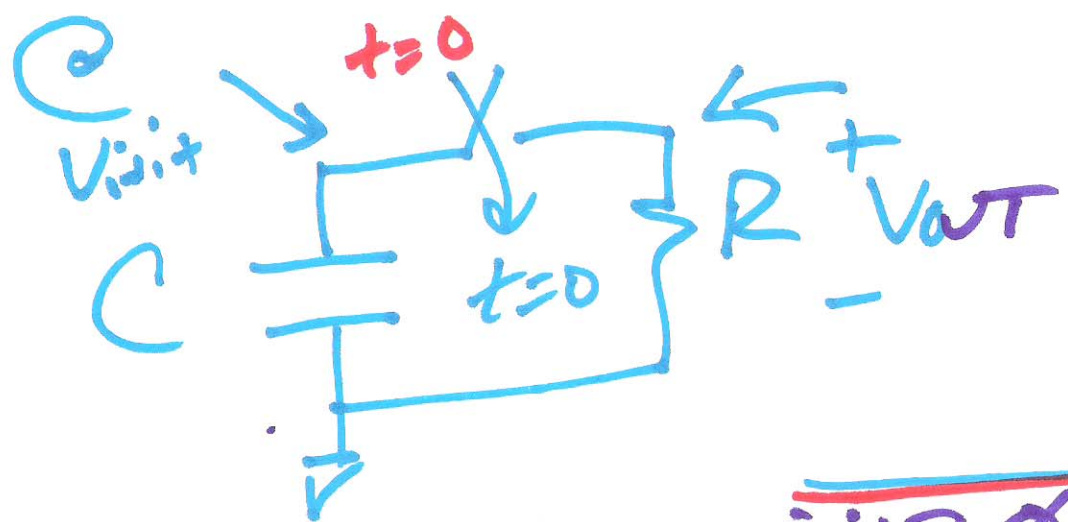


$I = C \frac{dV}{dt}$
 $V = \frac{1}{C} \int I \cdot dt$

5)

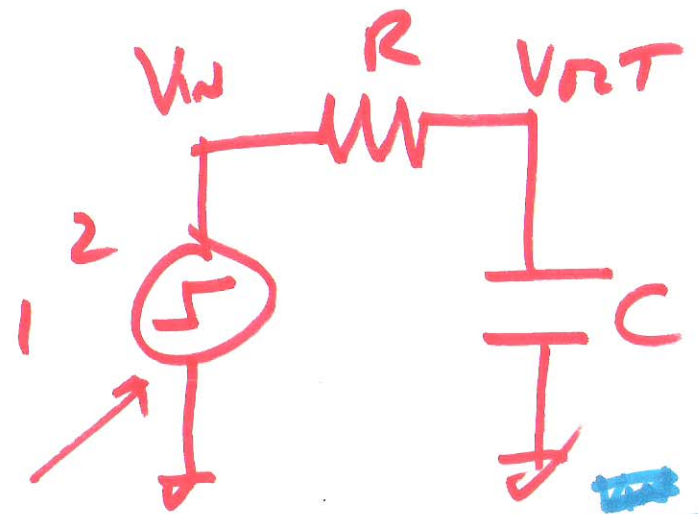

Sketch V_{in} & V_{out}

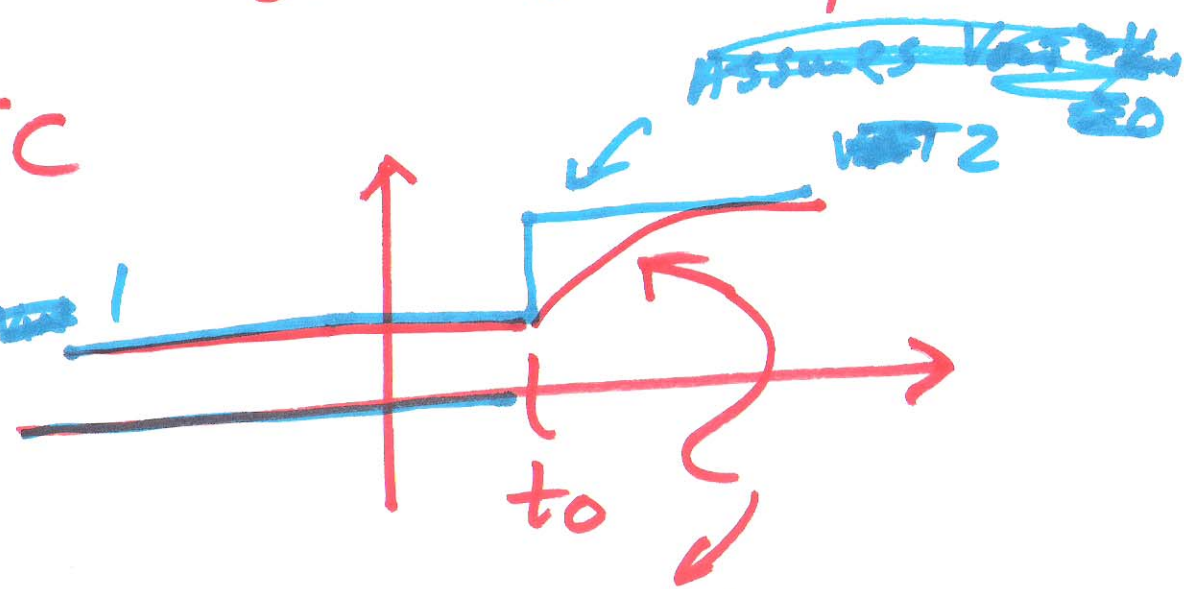


to switches
from 1 \rightarrow 2

$t > t_0$

$$V_{out}(t) = V_{init} + (V_{final} - V_{init}) \left(e^{-\frac{t-t_0}{RC}} + 1 \right)$$


$$V_{out}(t) = V_{init} + (V_{final} - V_{init}) \left(e^{-\frac{t-t_0}{RC}} + 1 \right)$$

6)

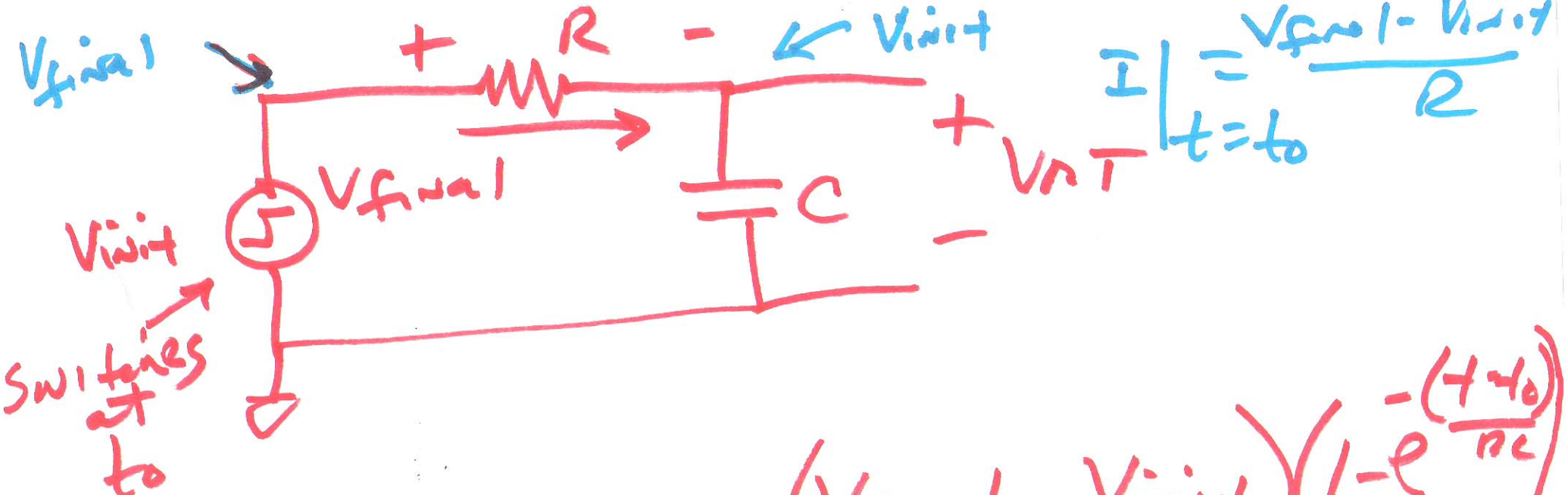

$$V_{out} \Big|_{t > t_0} = V_{init} + (V_{final} - V_{init}) \left(1 - e^{-\frac{(t-t_0)}{RC}} \right)$$

$$I \Big|_{t > t_0} = \frac{V_{final} - V_{out}}{R}$$

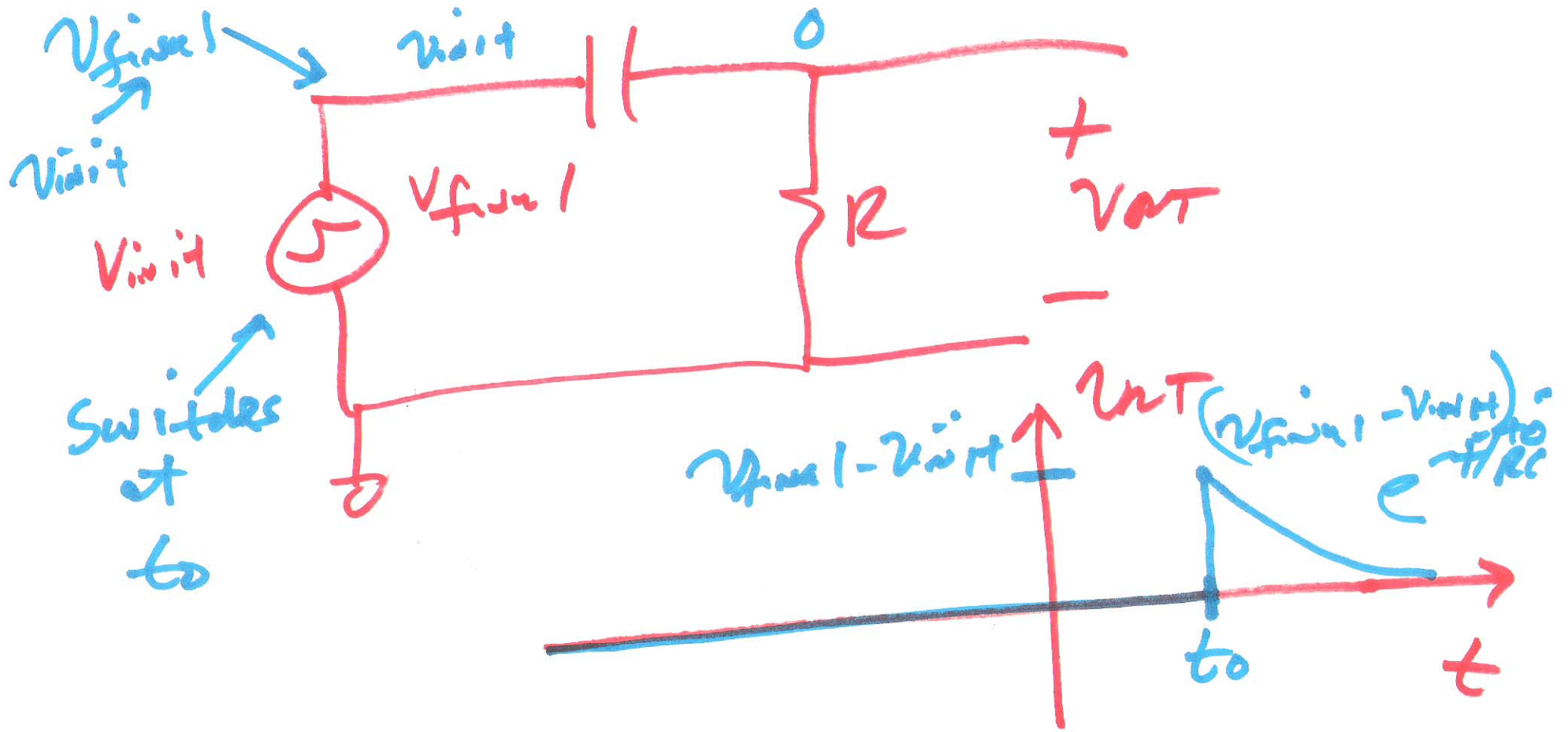

$$V_{final} - (V_R) = V_{init}$$

$$V_R = V_{final} - V_{init}$$

8)