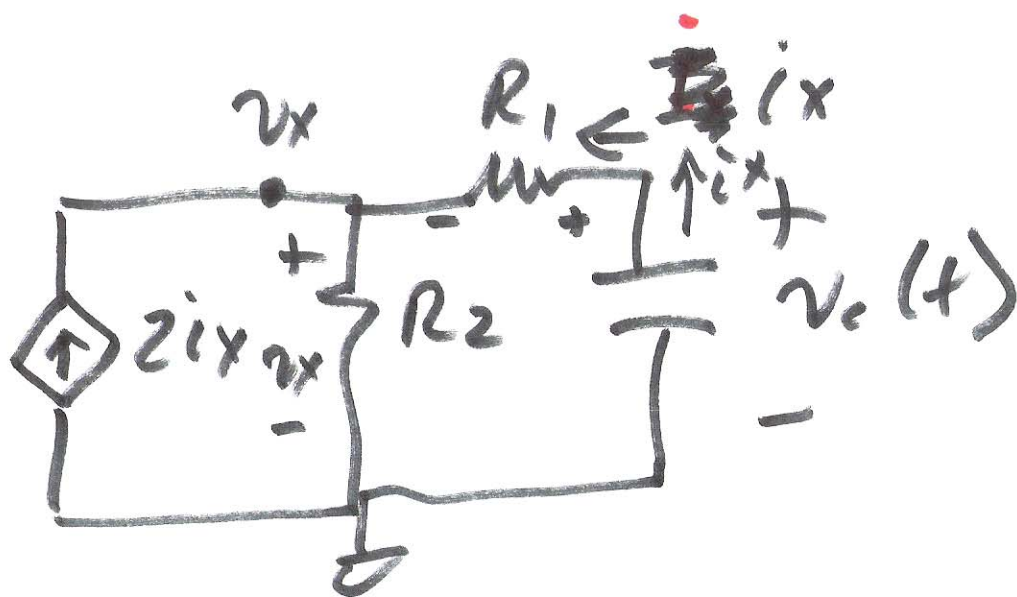


Lecture 18

July 3, 2014

EE 220

8.3




$$v_c - i_x R_1 - v_x = 0$$

$C = ?$ $V_c(0^-) = ?$

$$i_x(0^-) = 0$$

$$2i_x(0^-) = 0$$

$$v_c = v_x = 0$$

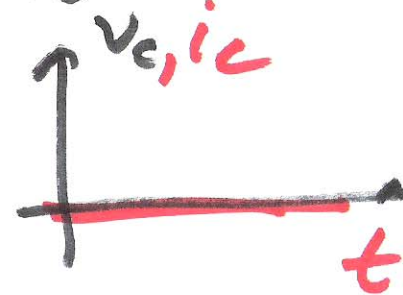

1)

$$i_x + 2i_x = \frac{v_x}{R_2}, \quad v_x = 3i_x R_2$$

$$i_x = -C \frac{dv_c}{dt}$$

$$v_c = i_x \cdot R_1 + v_x = i_x R_1 + 3i_x R_2$$

$$v_c = i_x (R_1 + 3R_2)$$

$$\frac{t-0}{-(R_1+3R_2)C} = \int_0^t \frac{dt}{-(R_1+3R_2)C} = \int_{v_c(0^-)}^{v_c(t)} \frac{dv_c}{v_c} = \ln v_c(t) - \ln v_c(0^-) = \ln \frac{v_c(t)}{v_c(0^-)}$$

2)

$$e^{-t/(R_1 + 3R_2)C} = \frac{v_c(t)}{V_c(0^-)}$$

$$v_c(t) = V_c(0^-) e^{-t/(R_1 + 3R_2)C}$$

$$i_c(t) = C \frac{dv_c}{dt} = \frac{C V_c(0^-)}{-(R_1 + 3R_2)C} e^{-t/(R_1 + 3R_2)C}$$

Assume $C = 1 \mu\text{F}$


$$V(0^-) = 1\text{V}$$

$$\angle \frac{V_{out}}{V_{in}} = 76^\circ = \frac{\angle V_{out}}{\angle V_{in}} = \frac{\angle V_{out}}{\angle 0^\circ}$$


$$0 + 76 \rightarrow \angle V_{out} = 76^\circ$$


$$\frac{\angle V_{out}}{\angle V_{in}} = 76^\circ$$

$$\angle V_{in} = 100^\circ$$

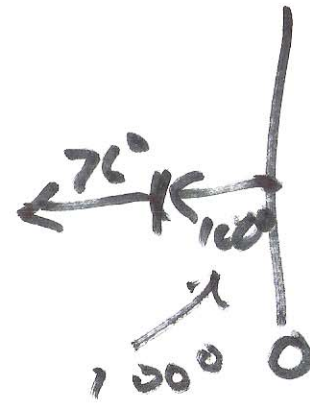


$$\angle 76^\circ = \angle -284^\circ$$

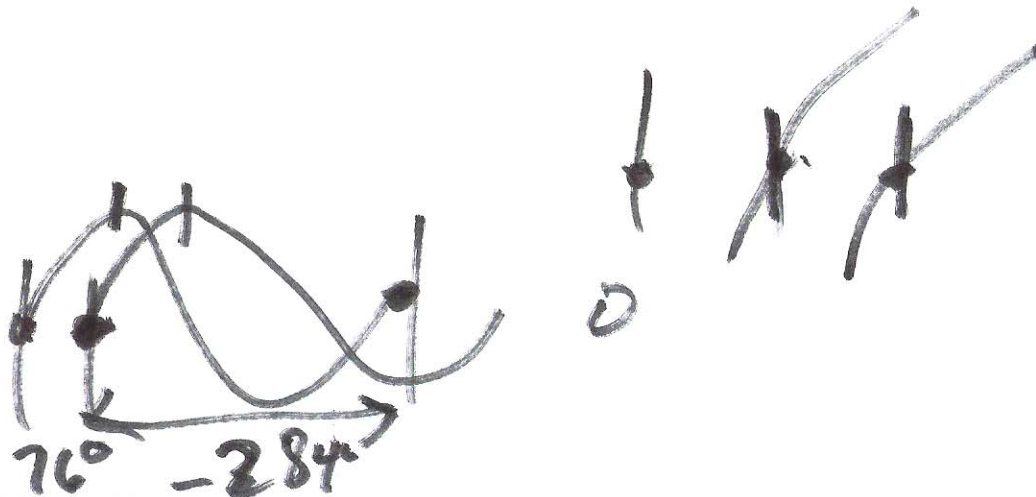


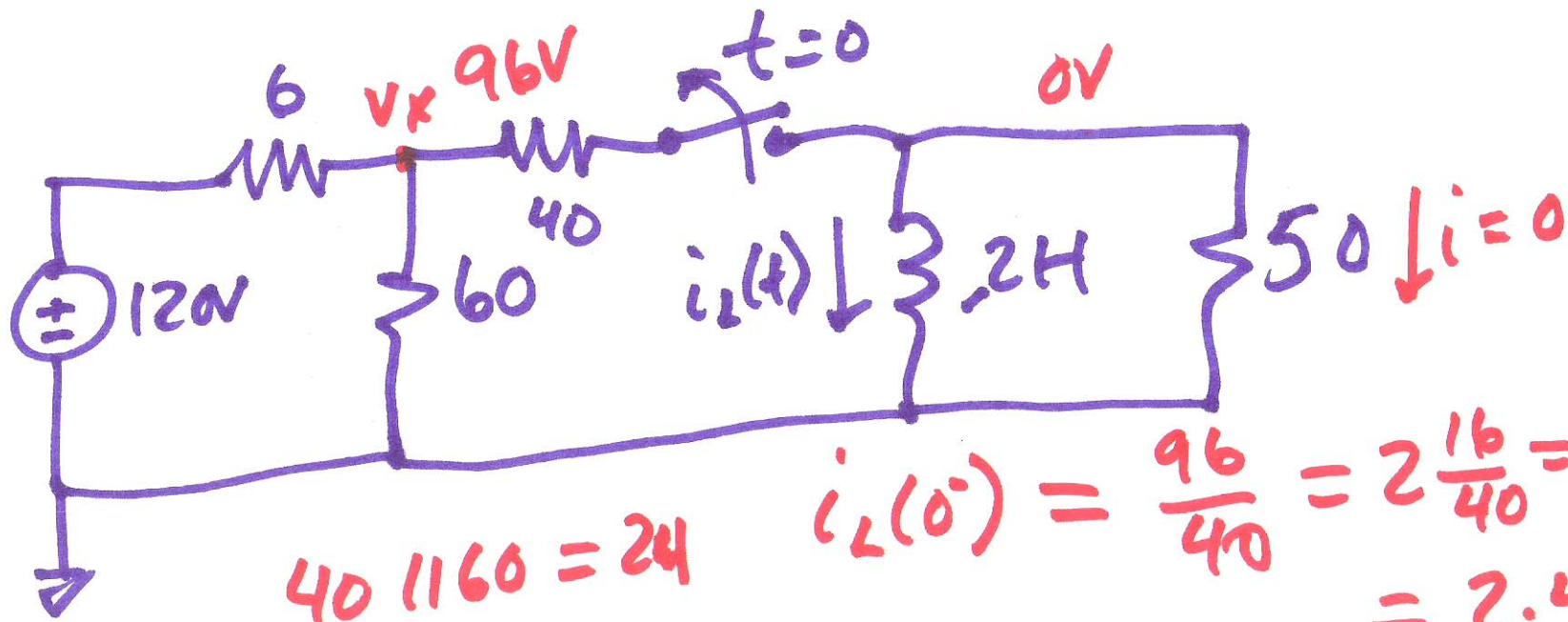

$$40 \parallel 60 = 24 \quad i_L(0^-) = \frac{96}{40} = 2 \frac{16}{40} = 2 \frac{2}{5} = 2.4 A$$
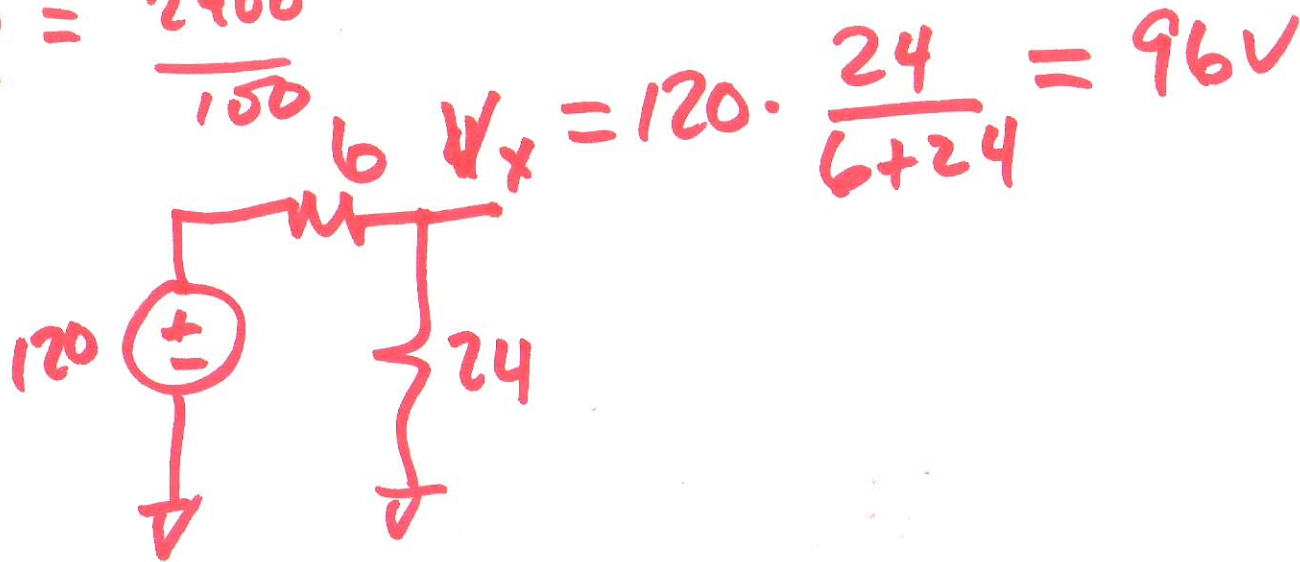
$$\frac{40 \cdot 60}{100} = \frac{2400}{100}$$



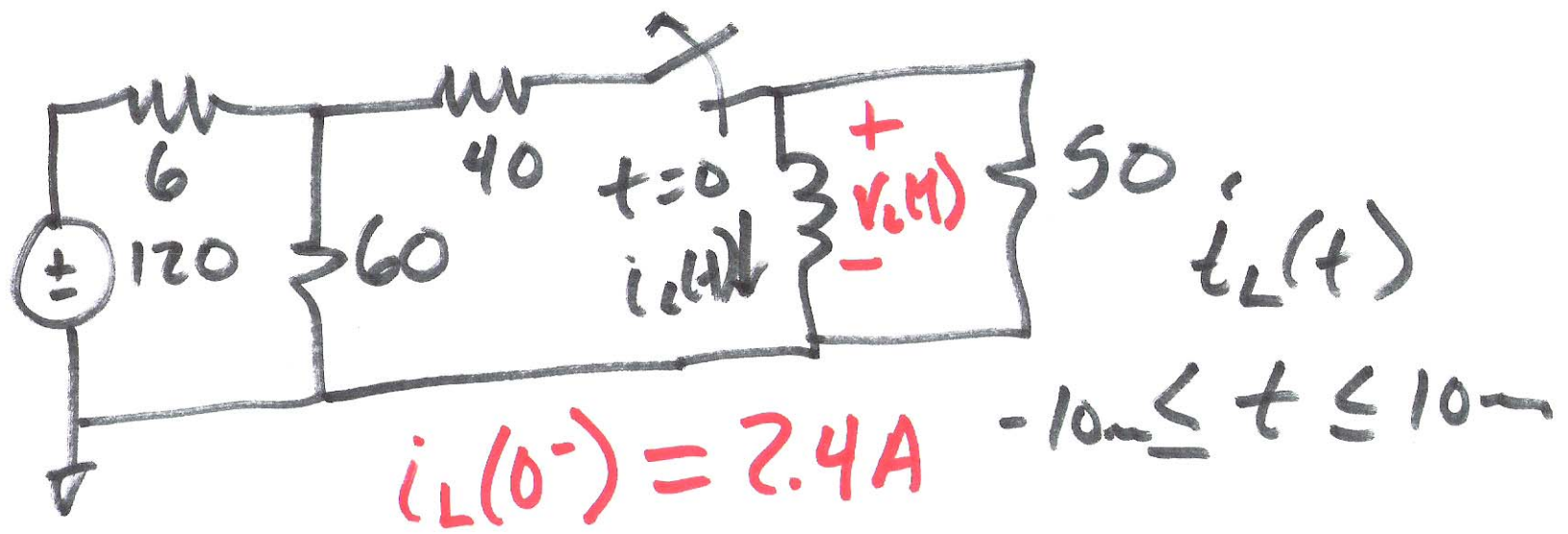

$$-i_L 50 - V_L(t) = 0$$

$$V_L = L \cdot \frac{di_L}{dt}$$

$$-50 \cdot i_L = L \frac{di_L}{dt}$$

$$\int_0^t \frac{dt}{-L/50} = \int_{I_L(0^-)}^{i_L(t)} \frac{di_L}{i_L}$$

67

$$-\frac{t}{L/R} = \ln \frac{i_L(t)}{I_L(0^-)}$$


$$-t/L/R$$


$$i_L(t) = I_L(0^-) e^{-t/L/R}$$

$$L/R = \frac{2}{50} = \frac{4}{1000}$$




$$-t/4\text{ms}$$
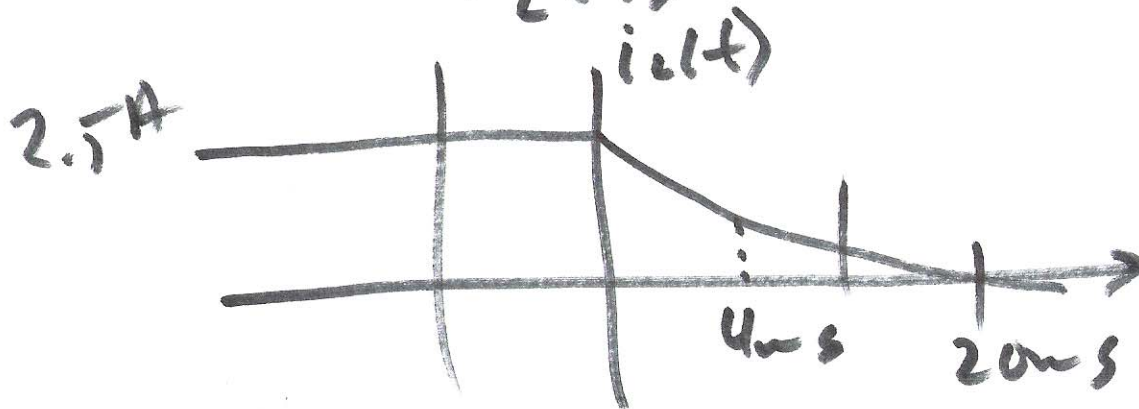
$$i_L(t) = 2.5\text{A} e^{-t/4\text{ms}}$$



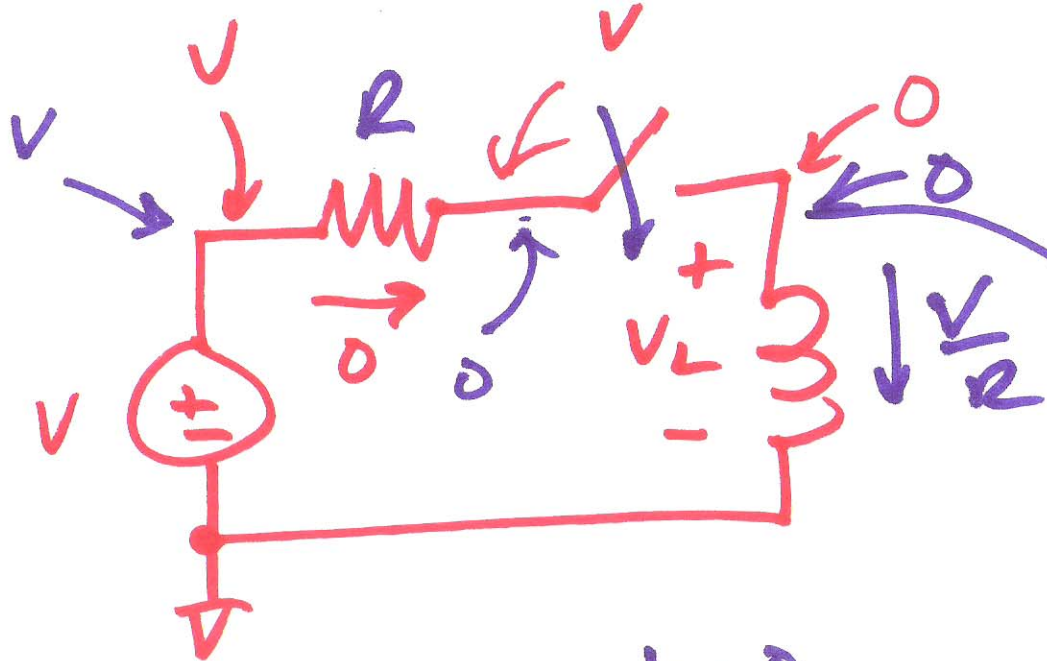


Switch closed
for a long
time

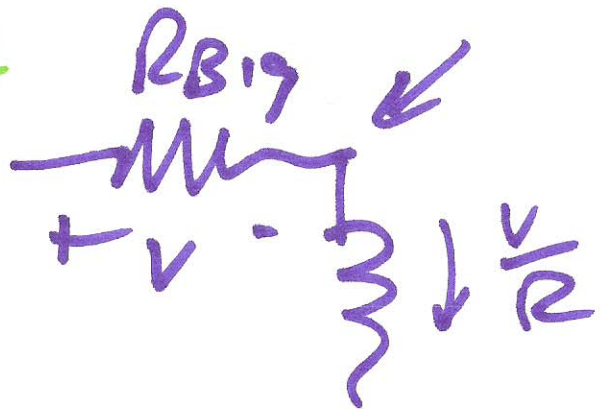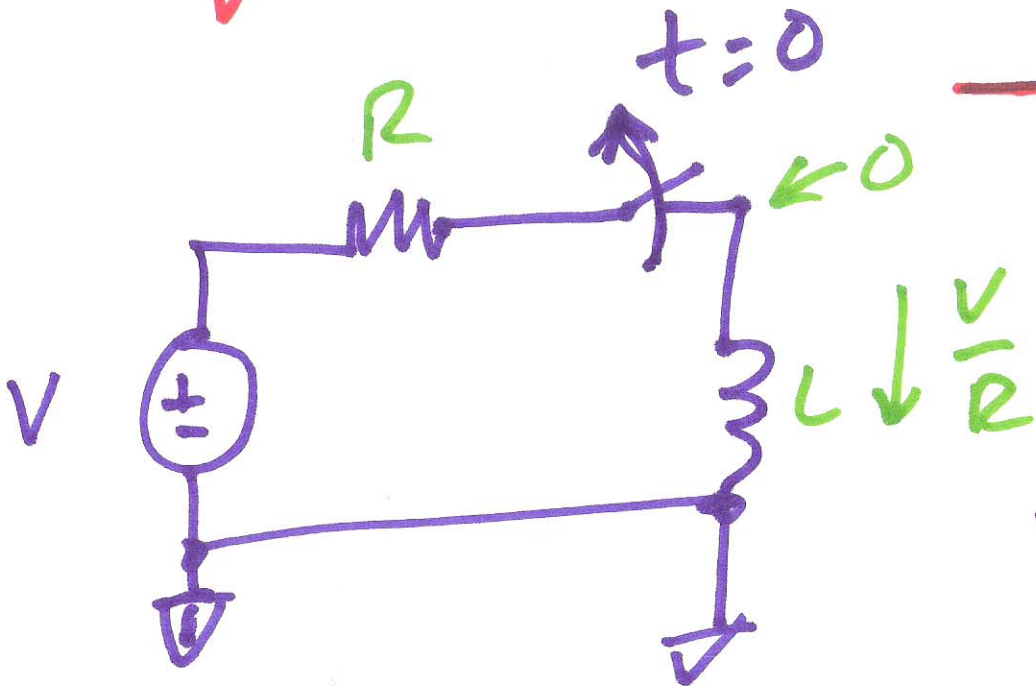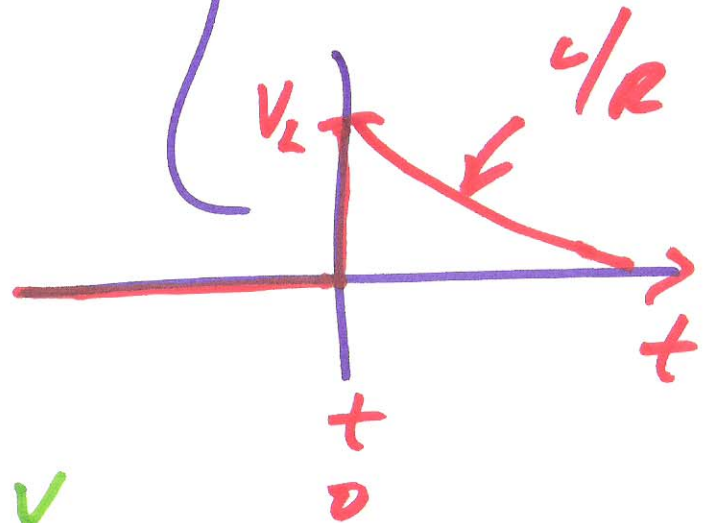


8)


96

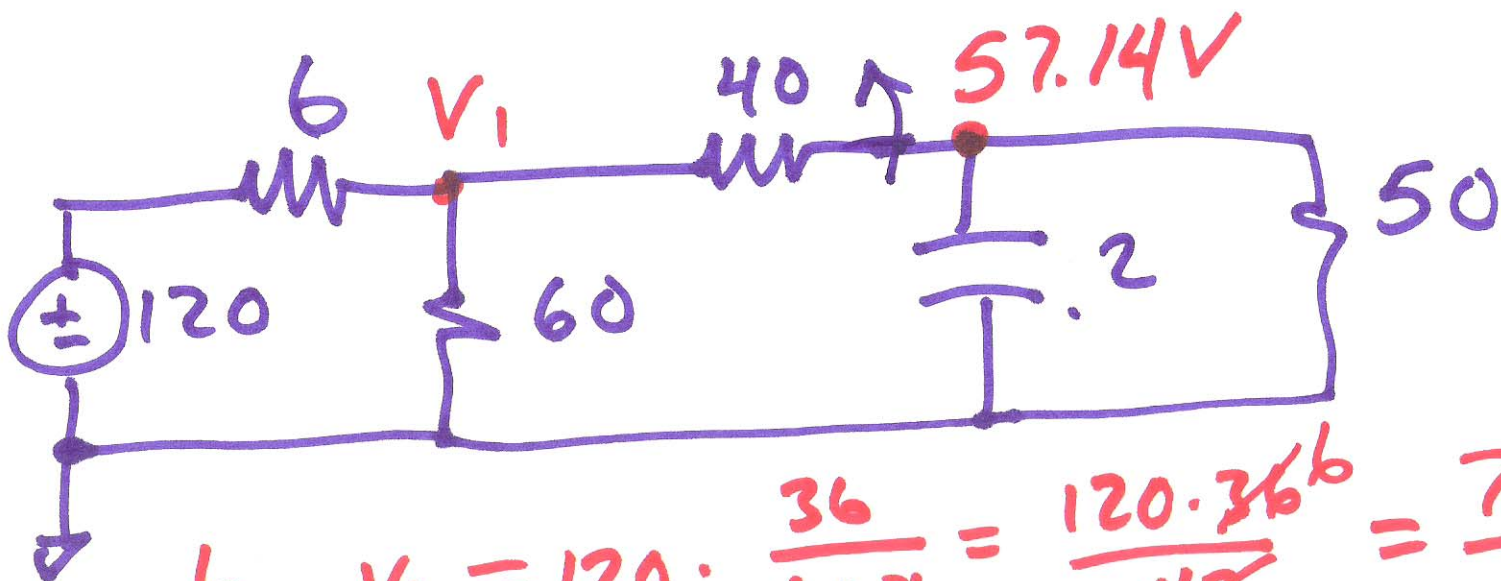
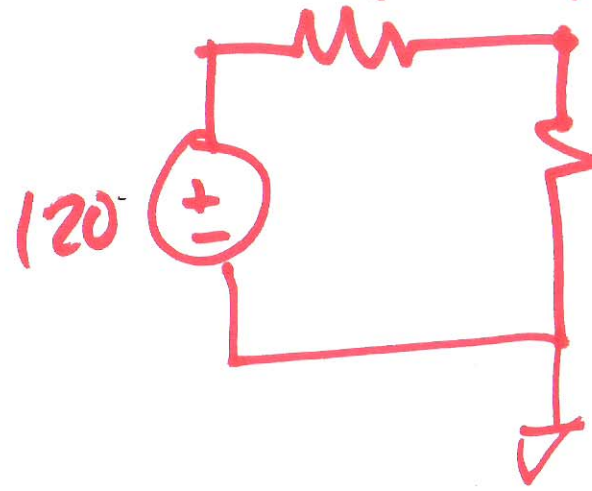
$$V_1 = 120 \cdot \frac{36}{6+36} = \frac{120 \cdot 36}{42} = \frac{720}{7}$$



$$60 \parallel 90 = 36$$

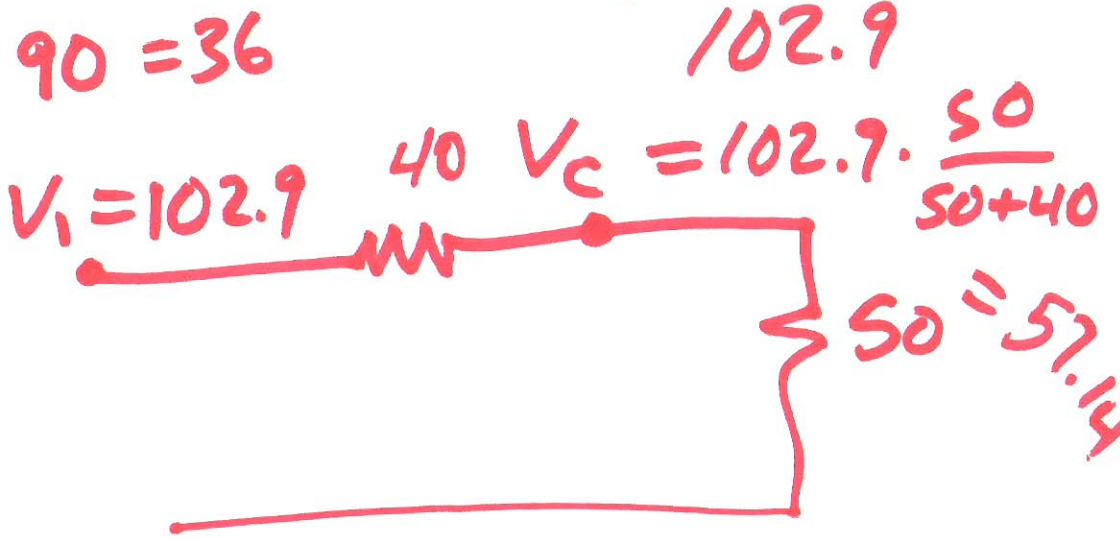


$$V_1 = 102.9$$

$$V_c = 102.9 \cdot \frac{50}{50+40}$$

$$50 = 57.14$$

9)

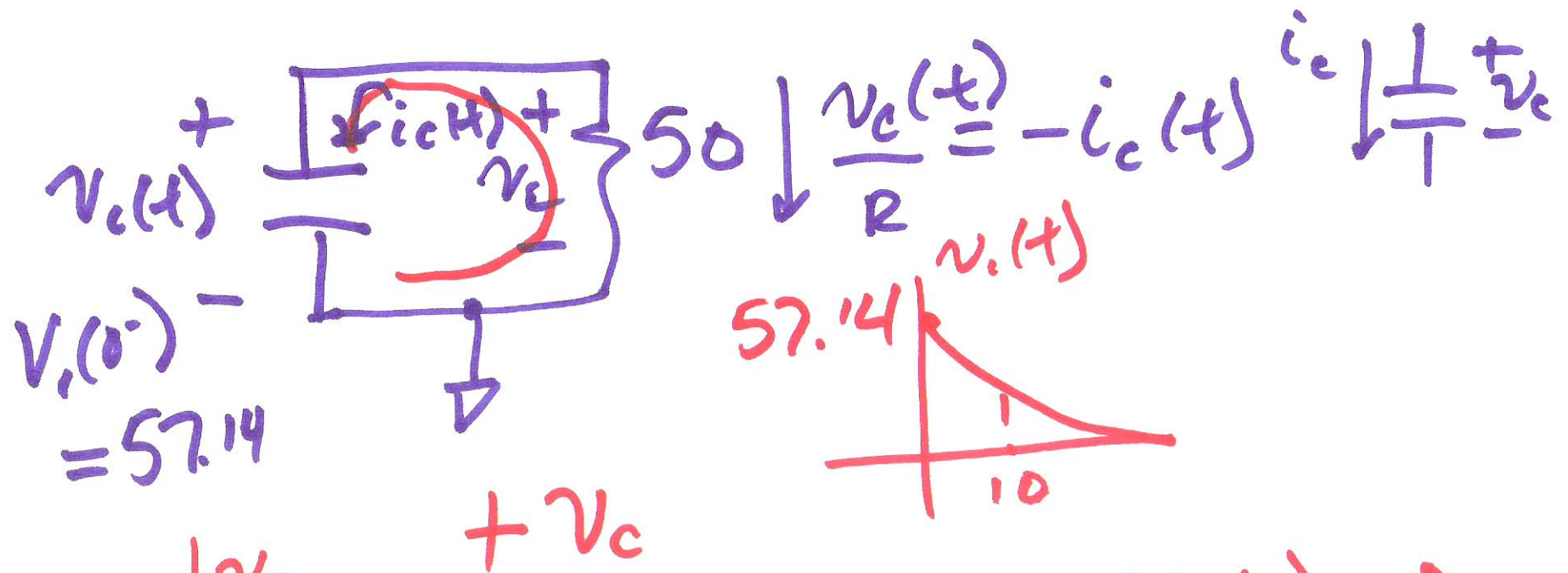

$$v_c = RC \frac{dv_c}{dt} + v_c$$

$$50(-i_c(t)) = -v_c(t) = 0$$

$$v_c(t) = 50 \cdot (-i_c(t))$$

$$i_c = C \frac{dv_c}{dt}$$

$$-\frac{t}{RC} = \ln \frac{v_c}{V_c(0^-)}$$

$$v_c(t) = V_c(0^-) e^{-t/RC}$$

50:2 = 10