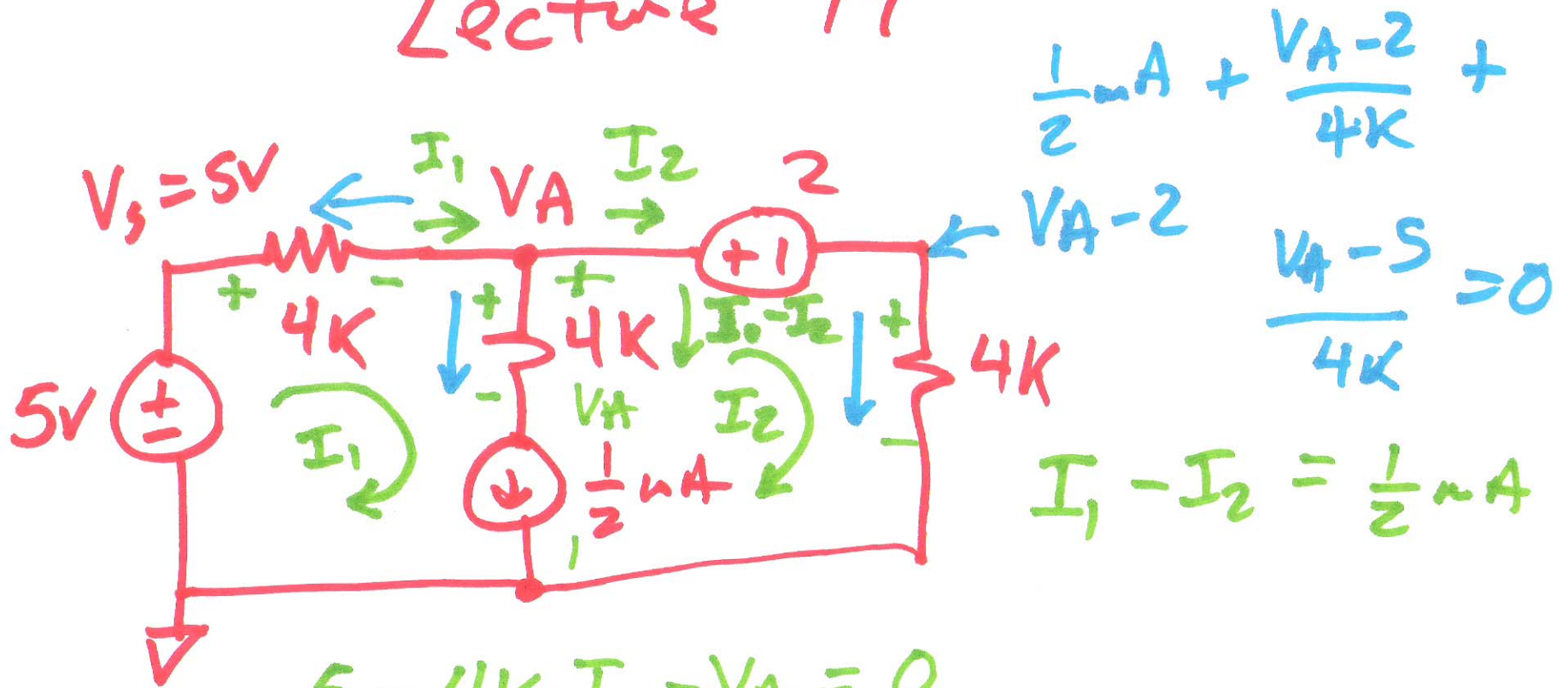


EE 220

July 7, 2014

Lecture 19




$$\frac{1}{2} \mu A + \frac{V_A - 2}{4K} + \frac{V_A - 5}{4K} = 0$$

$$I_1 - I_2 = \frac{1}{2} \mu A$$

$$5 - 4K \cdot I_1 - V_A = 0$$

$$-2 + V_A - 4K \cdot I_2 = 0$$

1)

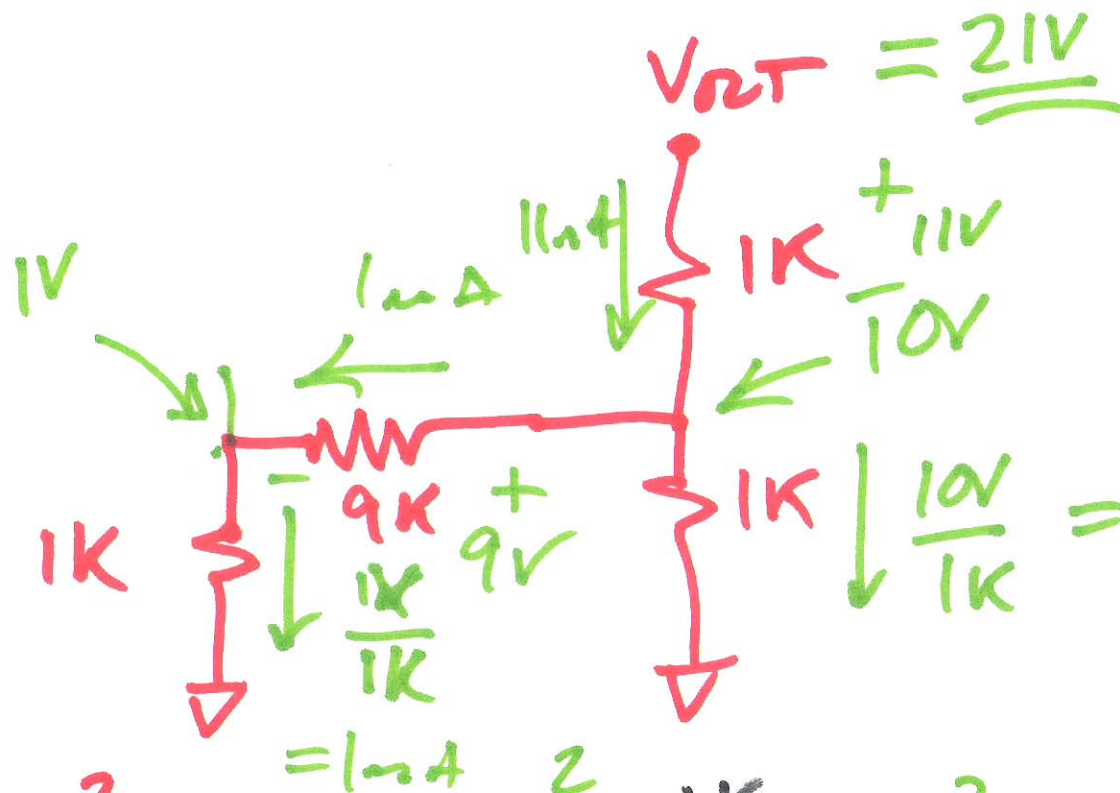


$$R_{TH} = \frac{2V}{6mA} = 333\Omega$$

$$i_x = \frac{V_{oc} - 2}{1K}$$


$$2i_x = -i_x$$

$$i_x = 0$$

$$\boxed{V_{oc} = 2}$$

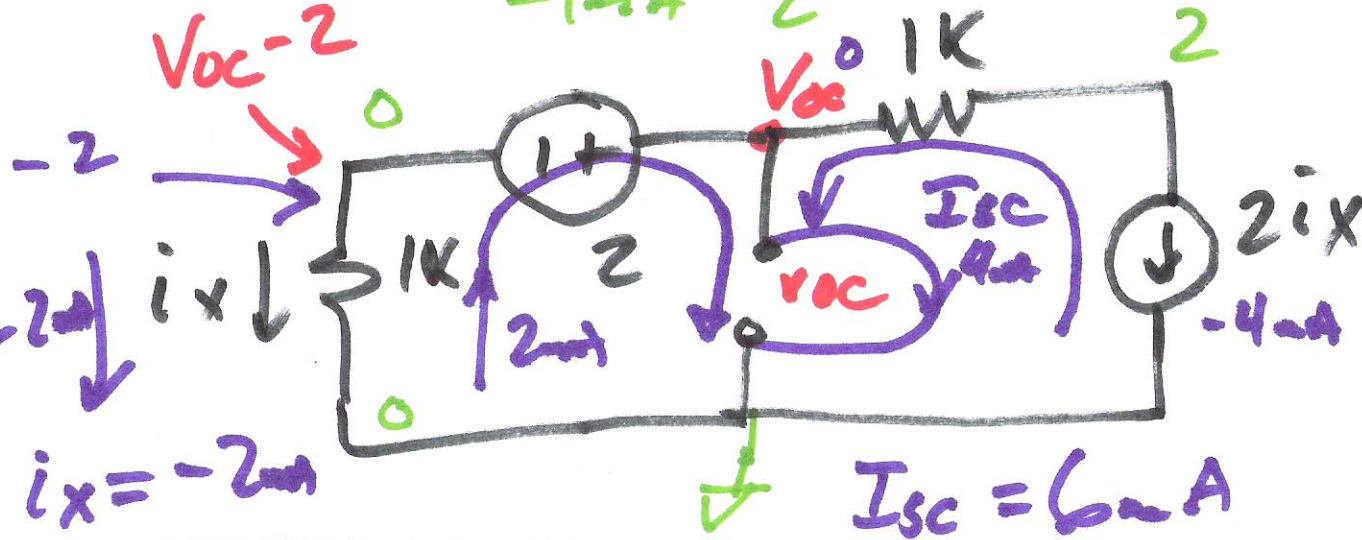

2)


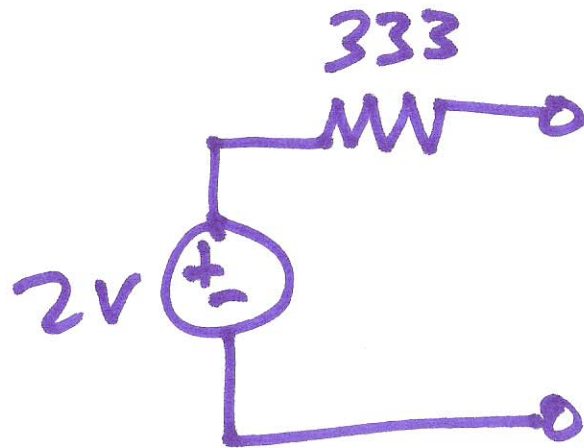


$V_{oc} = -2$

$-6 - 1k \cdot I - 2 - 1k \cdot I = 0$

$-2kI = 8$

$I = -4\mu A$

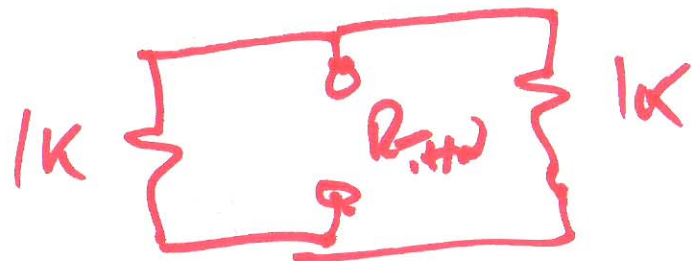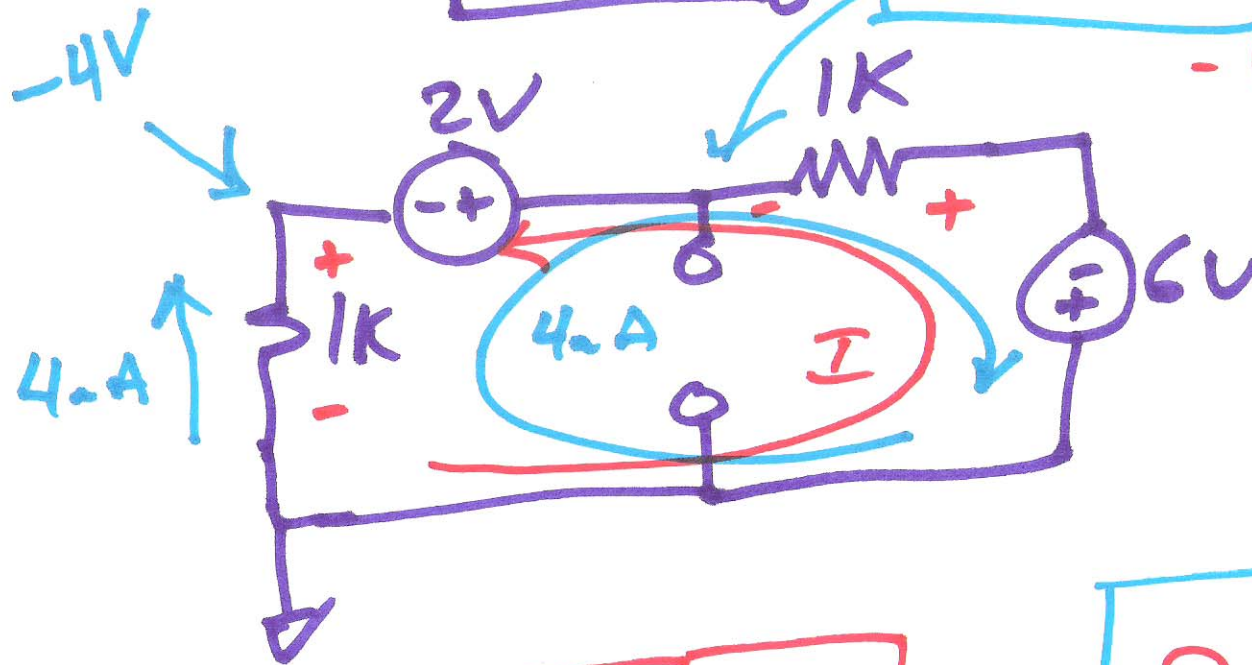

$R_{Th} = 500$

3)

$$\left| \frac{v_{out}}{v_{in}} \right| = -4 \text{ dB}$$

$$f = 600 \text{ kHz}$$

$$\angle \frac{v_{out}}{v_{in}} = +50^\circ$$

$$T = 1.67 \mu\text{s}$$

$$-4 \text{ dB} = 20 \log \left| \frac{v_{out}}{v_{in}} \right|$$

$$\left| \frac{v_{out}}{v_{in}} \right| = 10^{-4/20} = 10^{-1/5} = 10^{-0.2} = .631$$


$$\theta = \frac{t_d}{T} \cdot 360$$

if $v_{in} = 1 \text{ V peak}$


$$\frac{50}{360} \cdot 1.67 \mu\text{s} = t_d$$

$$v_{out} = .631$$

$$t_d = 0.23 \mu\text{s}$$

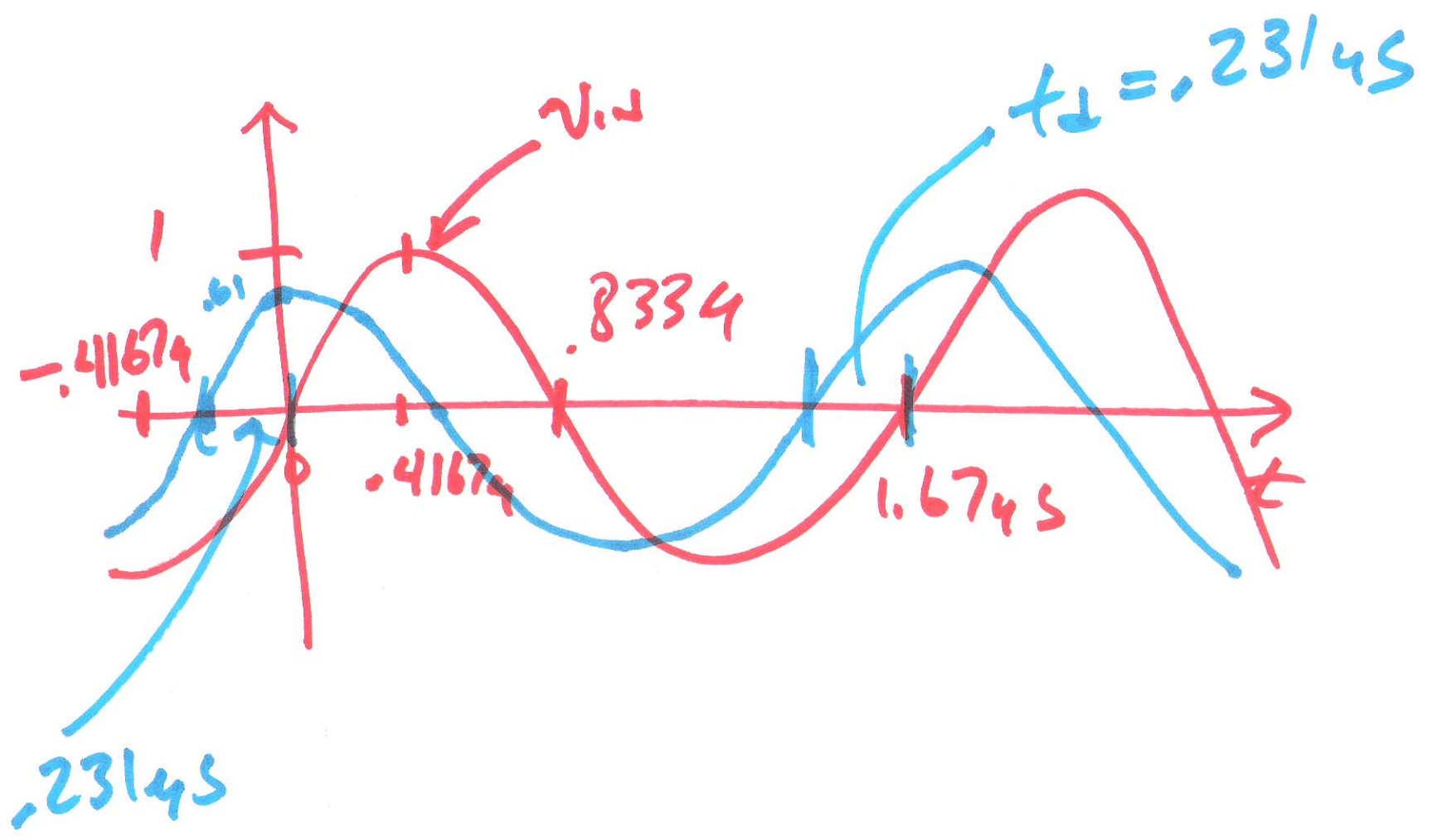

5)

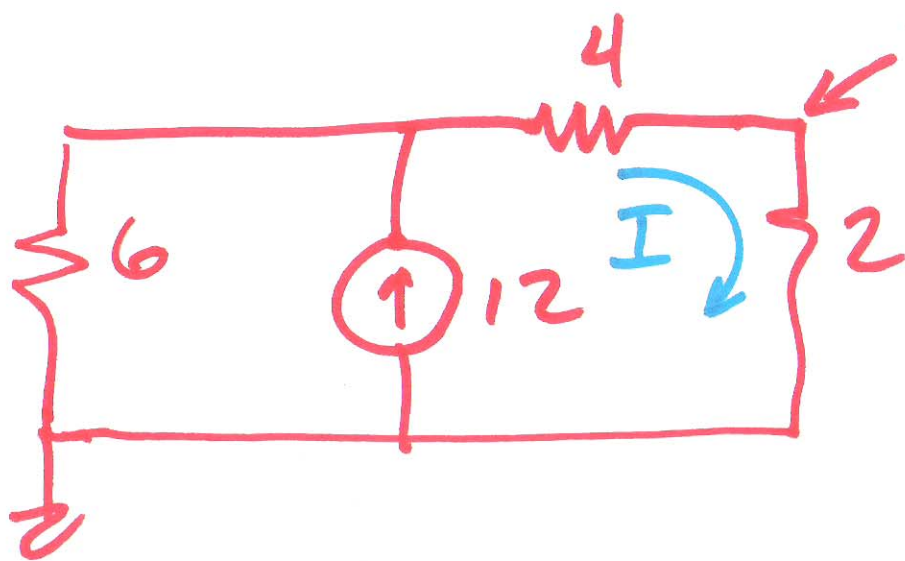


$$V_x = 6 \cdot 2 = \underline{\underline{12V}}$$

$$I = 12 \cdot \frac{6}{6+6}$$


$$= 12 \cdot \frac{6}{6+4+2}$$

$$I = \frac{1}{2} 12 = 6$$

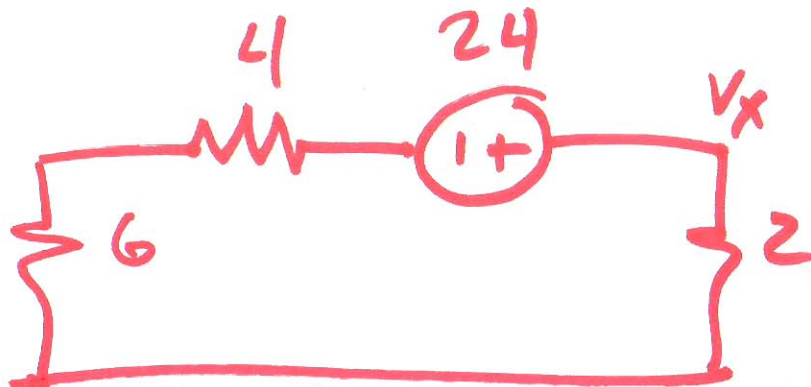

$$V_x = 24 \cdot \frac{2}{2+4+6}$$

$$V_x = \underline{\underline{4.8V}}$$

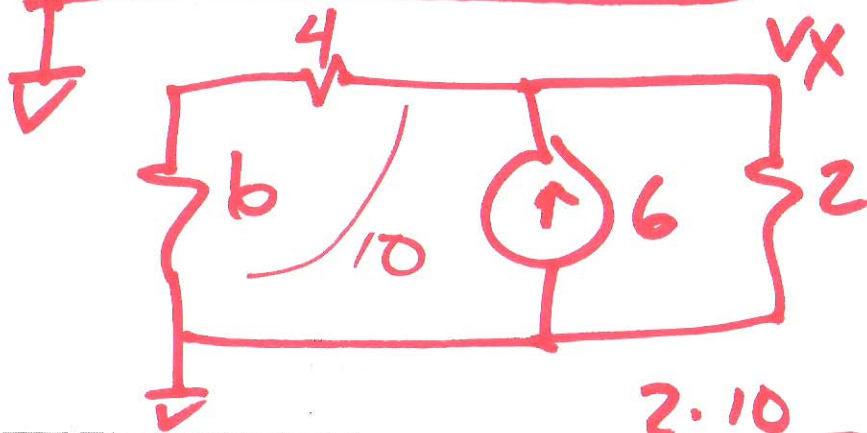

$$V_x = 6 \cdot 2 \parallel 10$$

$$\frac{2 \cdot 10}{12} = \frac{20}{12} = \frac{5}{3} = \underline{\underline{10V}}$$

1.666



$$V_T = \frac{12}{4} = \frac{10}{2} = \underline{\underline{2.6V}}$$

b)

Find the frequency when $V_{out} = 0.707 V_{in}$ (V_{out} is 3dB lower than V_{in}).

$f = 159 \text{ Hz}$

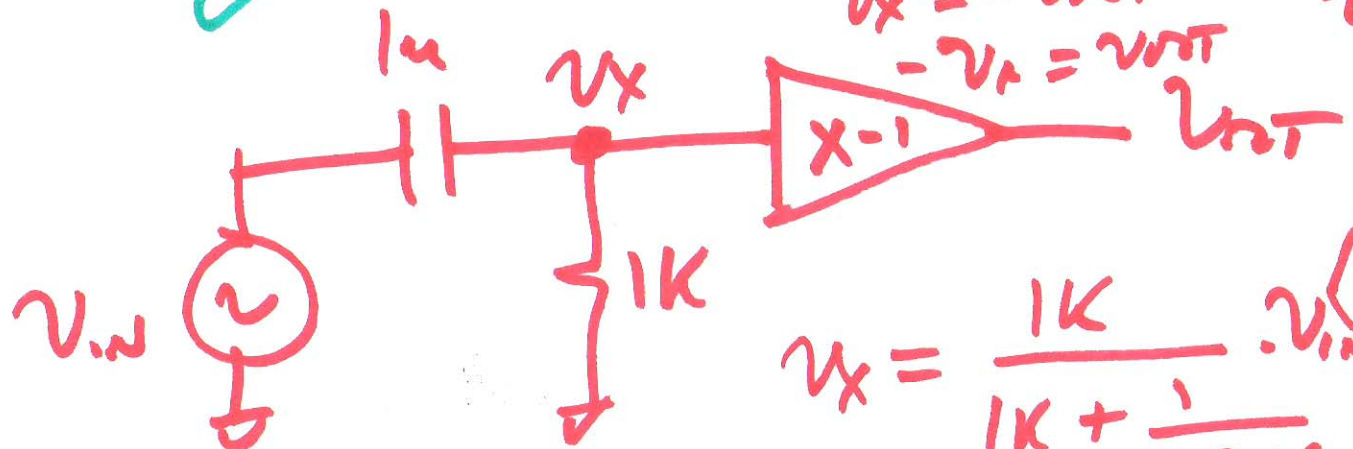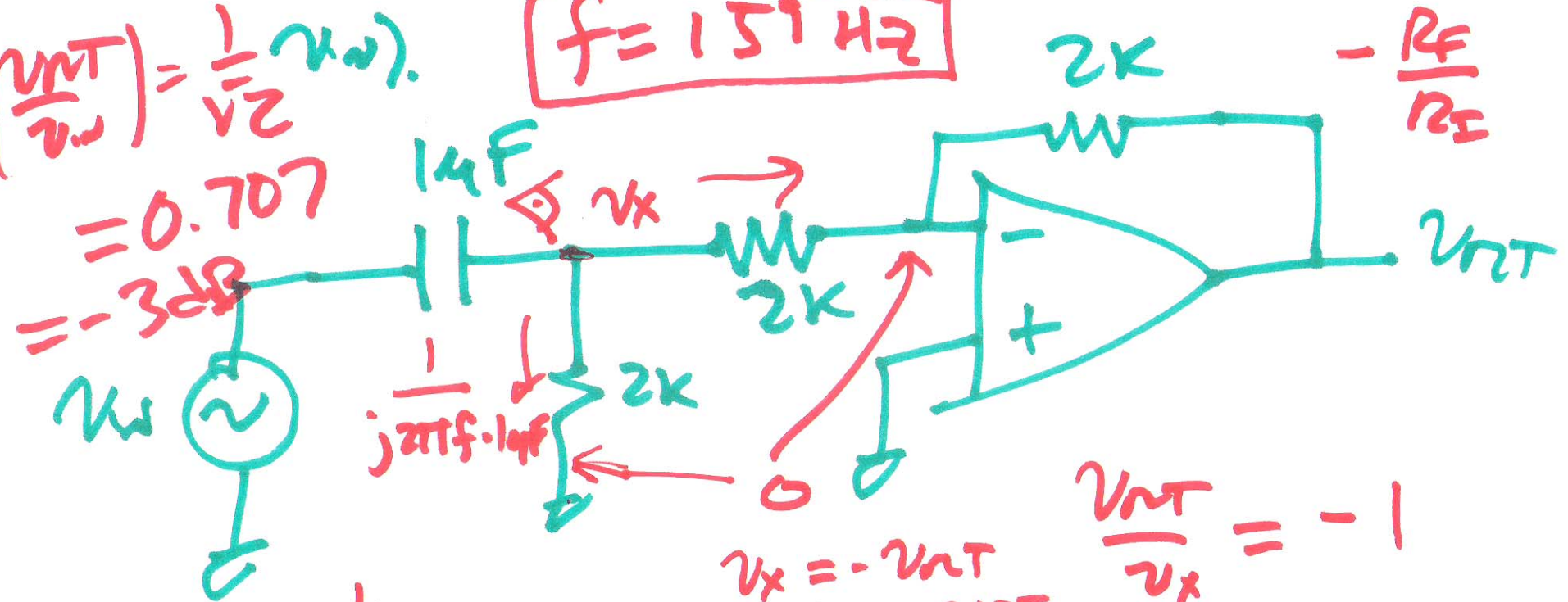$\left(\frac{V_{out}}{V_{in}}\right) = \frac{1}{\sqrt{2}}$
 $= 0.707$
 $= -3\text{dB}$



$v_x = -v_{out}$
 $-v_x = v_{out}$
 $\frac{v_{out}}{v_x} = -1$

$$v_x = \frac{1k}{1k + \frac{1}{j \cdot 2\pi f \cdot 10^{-6}}} \cdot v_{in} = -v_{out}$$

$10^{-6} \cdot 10^3$
 10^{-3}



$$\frac{1}{2\pi \cdot 10^{-3}} = 159$$

$$\frac{1}{159} = 2\pi \cdot 10^{-3}$$

$$\frac{V_{out}}{V_{in}} = - \frac{0 + j \cdot 2\pi f \cdot 10^{-3}}{1 + j \cdot 2\pi f \cdot 10^{-3}}$$

$$= \frac{0 + j \frac{f}{159}}{1 + j \frac{f}{159}}$$


Phase shift: $\angle 180 + 90 - \tan^{-1} \frac{f}{159}$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{2}} = \frac{\sqrt{0^2 + \left(\frac{f}{159}\right)^2}}{\sqrt{1^2 + \left(\frac{f}{159}\right)^2}} = \frac{\frac{f}{159}}{\sqrt{1 + \left(\frac{f}{159}\right)^2}}$$

$$\frac{1}{2} + \frac{1}{2} \left(\frac{f}{159}\right)^2 = \left(\frac{f}{159}\right)^2, \quad \frac{1}{2} = \left(\frac{f}{159}\right)^2 \left(1 - \frac{1}{2}\right)$$

$$\frac{f}{159} = 1 \quad \boxed{f = 159}$$

8)

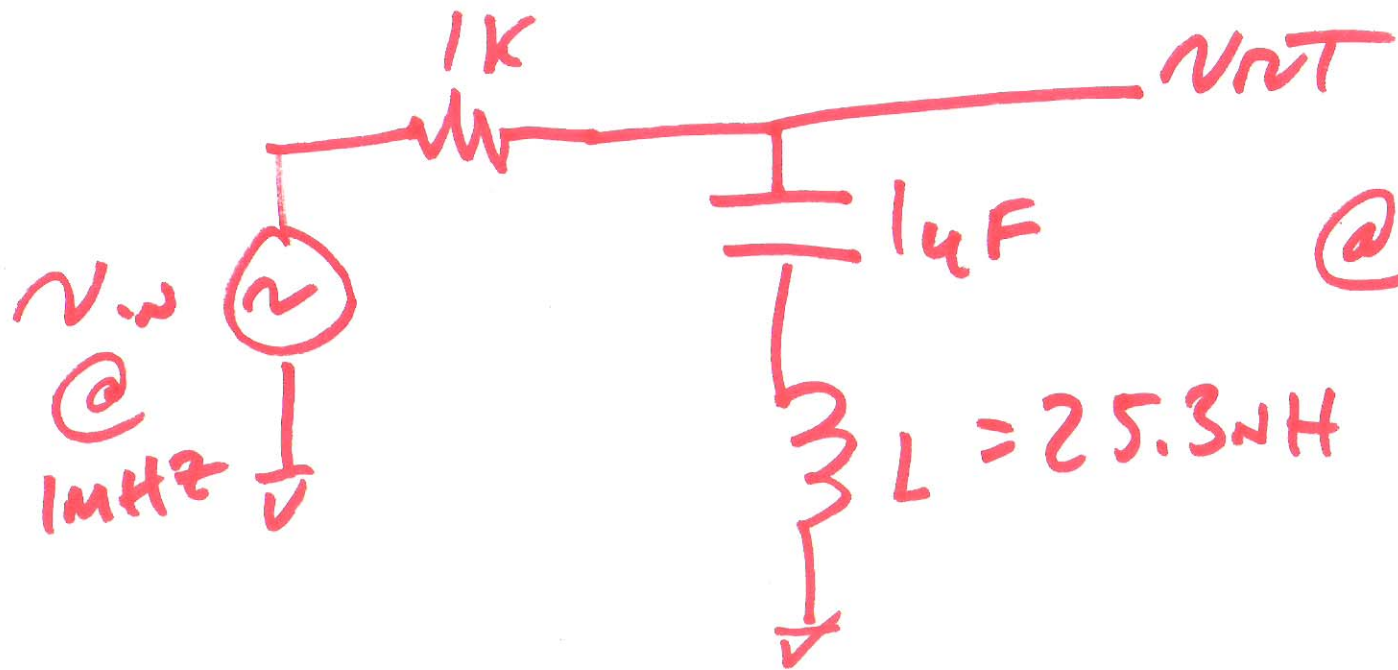

@ what value
 of L
 does v_{out}
 go to zero?

$$L = \frac{10^{-6} \text{ H}}{(6.28)^2} + j \cdot 2\pi \cdot 10^6 \cdot L = 0$$

$$L = \frac{1}{2\pi} \cdot \frac{1}{2\pi \cdot 10^6} \cdot \frac{-j}{2\pi} + j \cdot 2\pi \cdot 10^6 \cdot L = 0$$

$$-\frac{1}{2\pi} + 2\pi \cdot 10^6 \cdot L = 0$$

9)