


EE 220

Circuits I


6/9/14

Ohm's law

Resistor

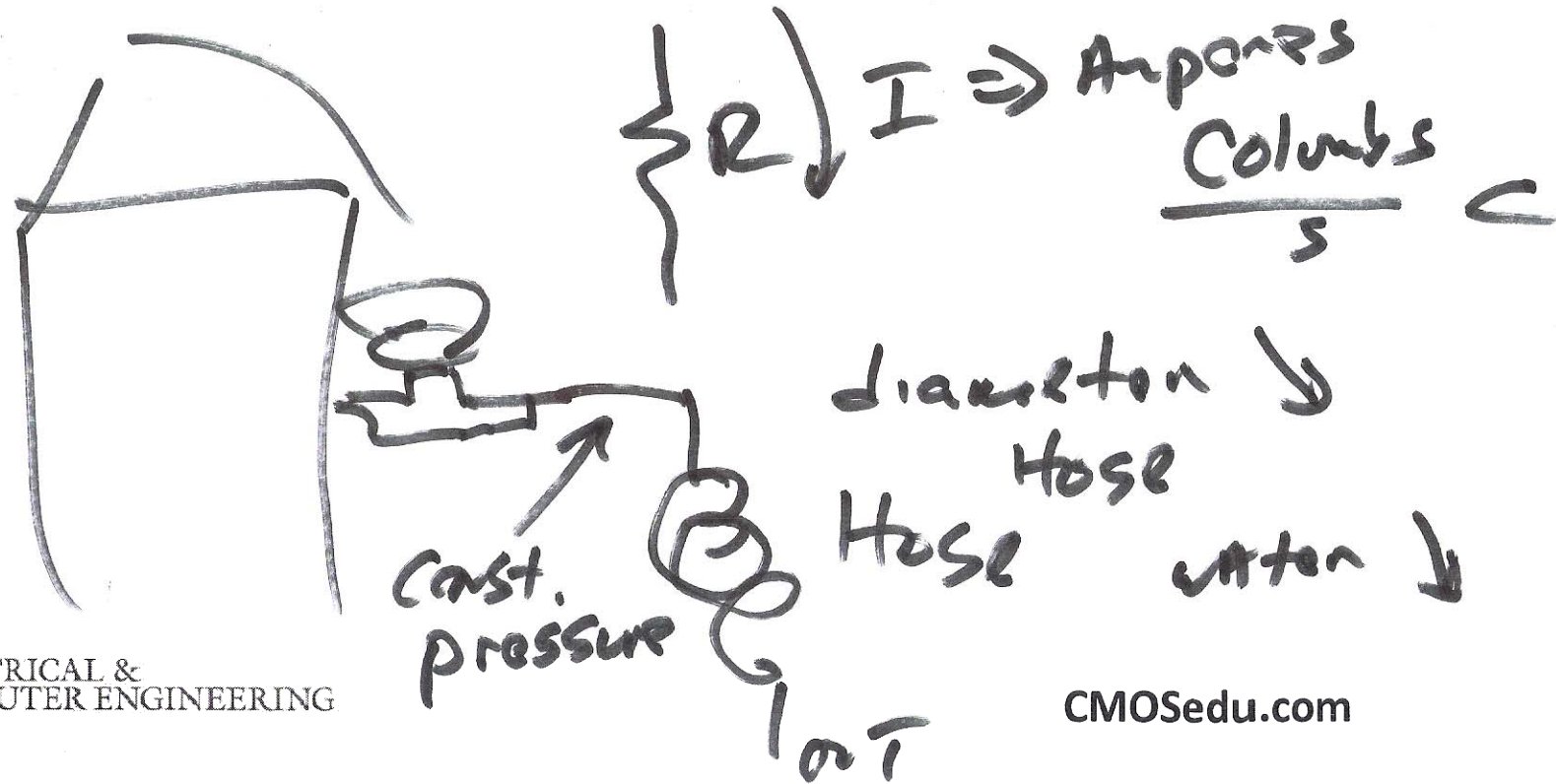


1)

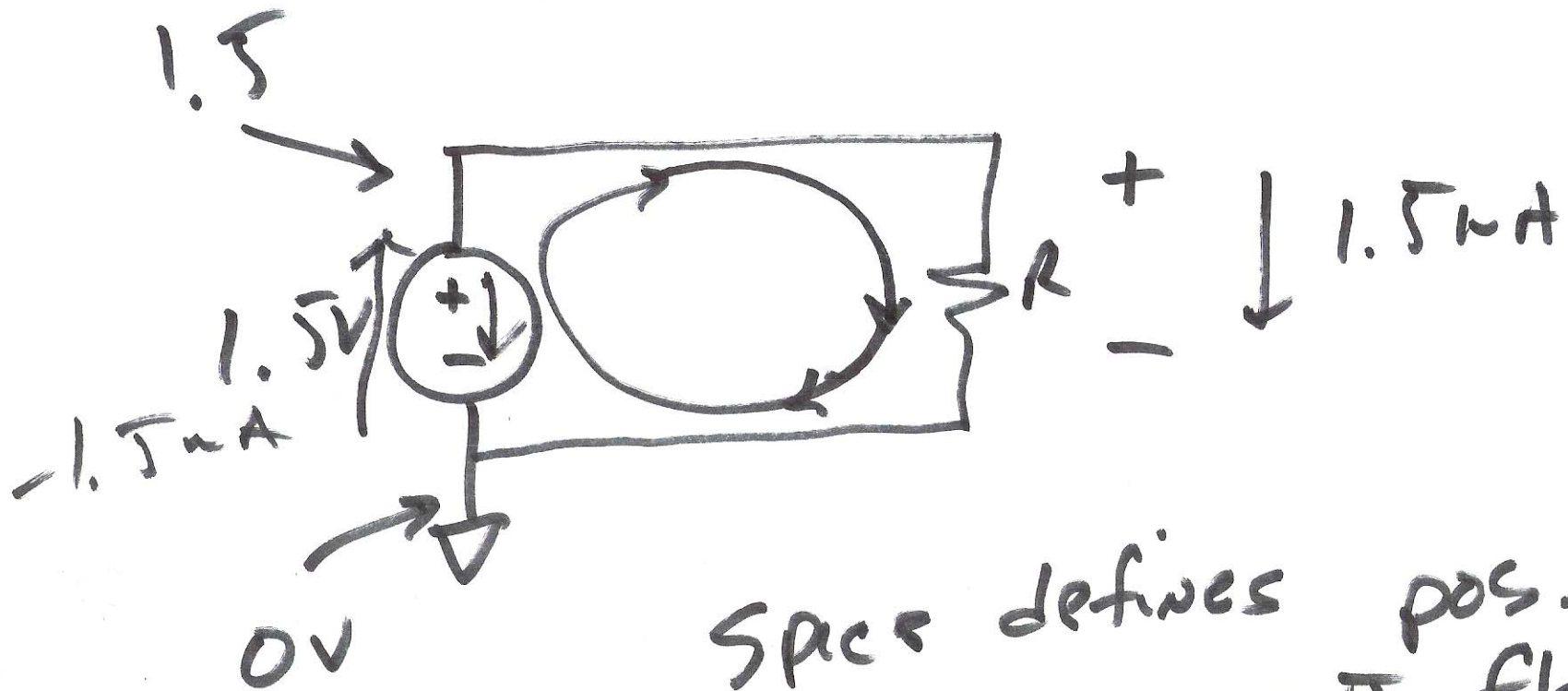


Space defines pos.
 current flow
 as $+ \rightarrow -$

2)

$$V_S - V_R = 0 \Rightarrow V_S = V_R$$

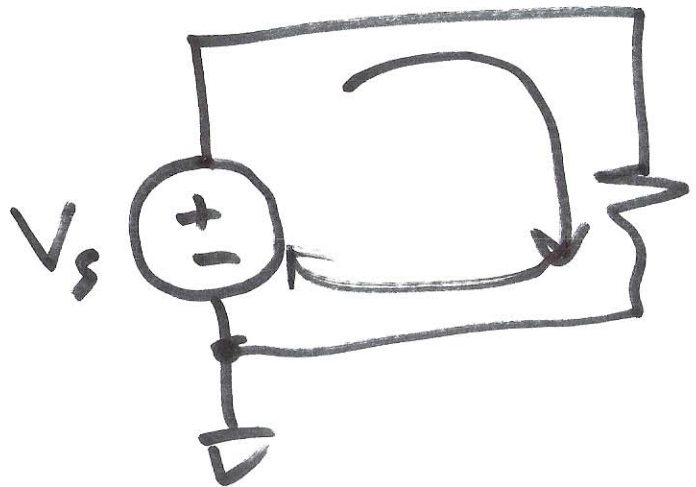

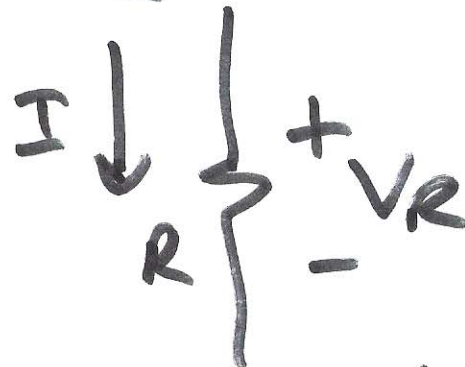
$$R \quad \begin{matrix} + \\ V_R = V_S \\ - \end{matrix} \Rightarrow$$



$$\boxed{V_R = I \cdot R}$$

$$V_S = V_R$$

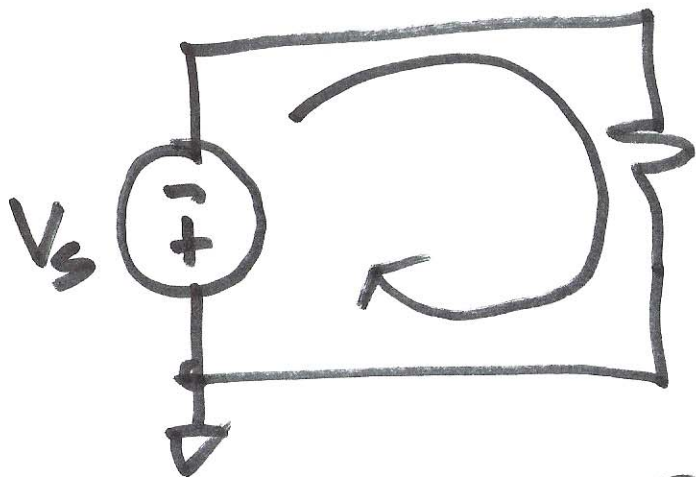

$$\begin{matrix} + & - \\ V_R & \end{matrix} \quad \begin{matrix} + \\ V_S \\ - \end{matrix} \quad \text{KVL}$$

$$V_S + V_R = 0$$

$$-V_S + (-V_R) = 0$$

$$= -V_S$$


$$V_S = -V_R$$

3)

$$I \downarrow \begin{array}{|c} R \\ \hline \end{array} \begin{array}{l} + \\ v_R \\ - \end{array} = I \cdot R$$

$$I \downarrow \begin{array}{|c} R \\ \hline \end{array} \begin{array}{l} - \\ v_R \\ + \end{array} = -I \cdot R$$
$$-v_R = I \cdot R$$

$$\begin{array}{|c} \hline + \\ -v_R \\ - \end{array}$$

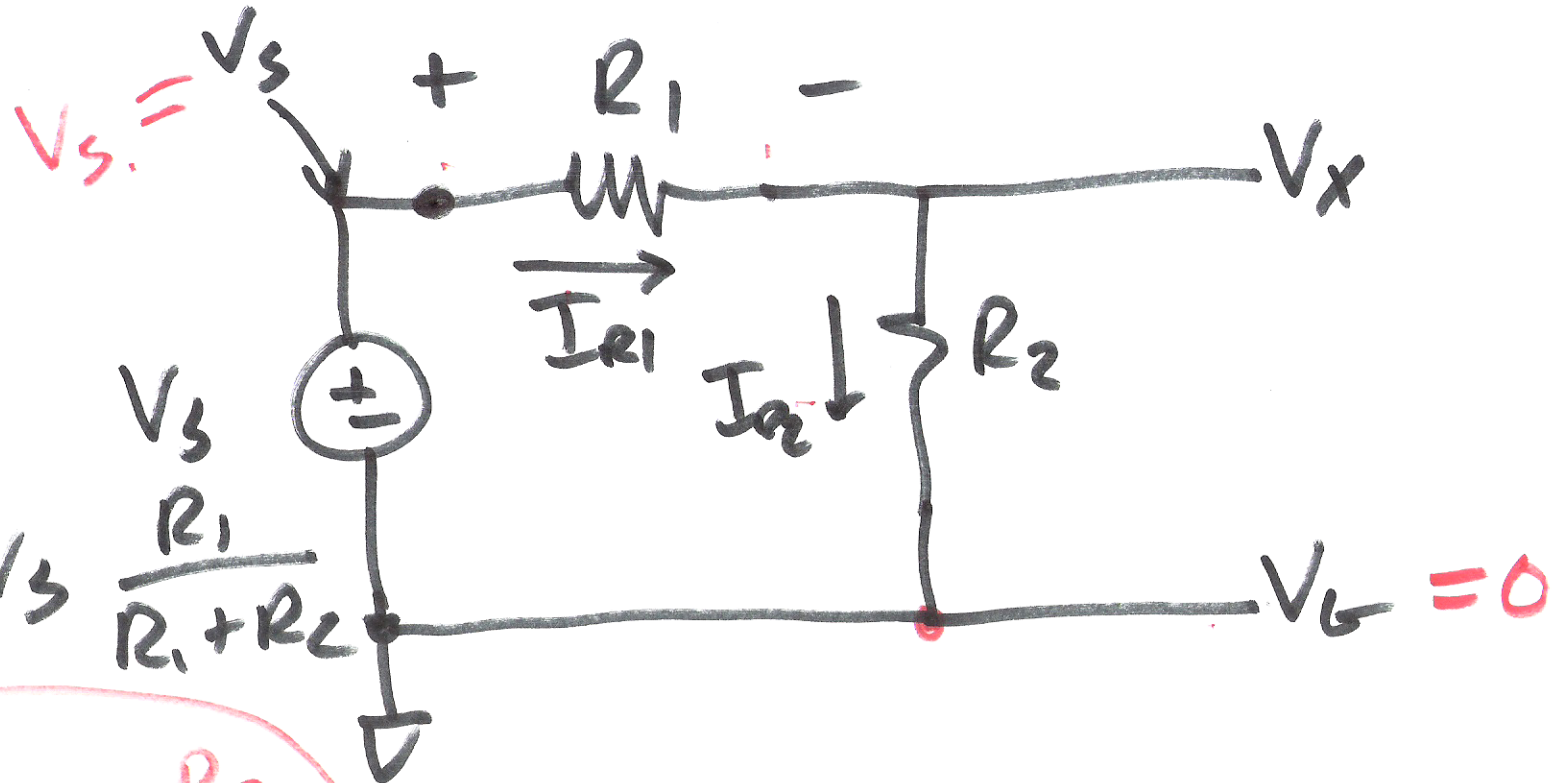

$$V_x = V_s = \frac{R_2}{R_1 + R_2} V_s$$

$$\frac{V_s}{R_1 + R_2} = I = I_{R1} = I_{R2}$$


$$V_{R1} = V_s - V_x$$

$$= V_s - V_s \cdot \frac{R_2}{R_1 + R_2}$$

$$V_x = I \cdot R_2 = V_s \cdot \frac{R_2}{R_1 + R_2}$$

$$V_s \frac{R_1 + R_2}{R_1 + R_2} - V_s \frac{R_2}{R_1 + R_2}$$

5)

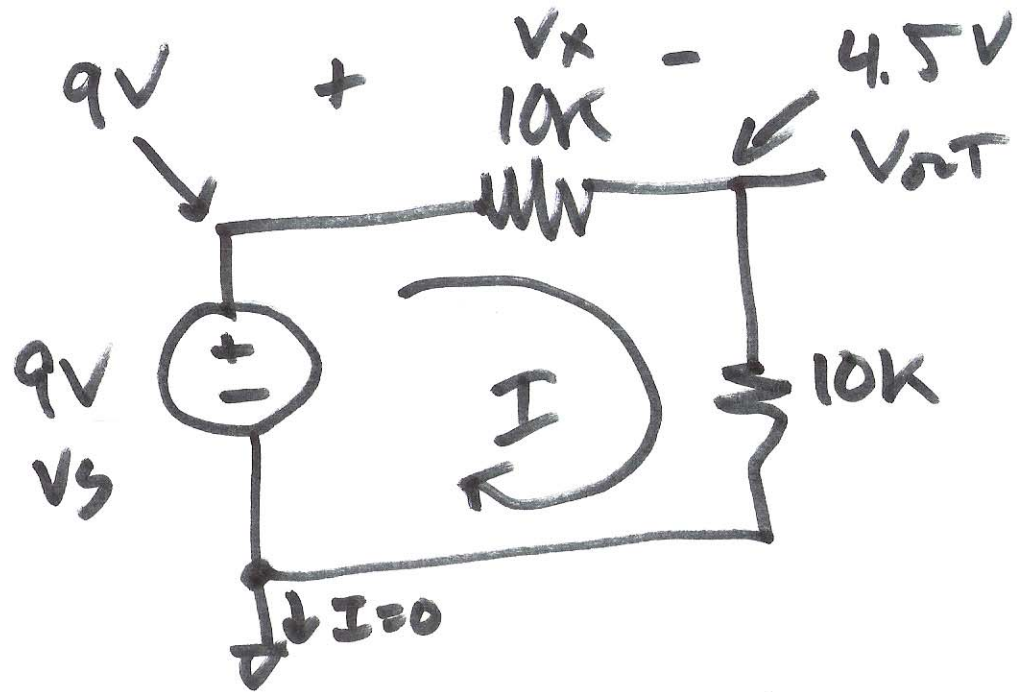


All currents and voltages

$$I = \frac{9}{10k + 10k} = 450 \mu A = 0.45 mA$$

$$V_{out} = 10k \cdot 450 \mu A = 4.5V$$

$$V_x = V_s - V_{out} = 9 - 4.5 = 4.5V$$

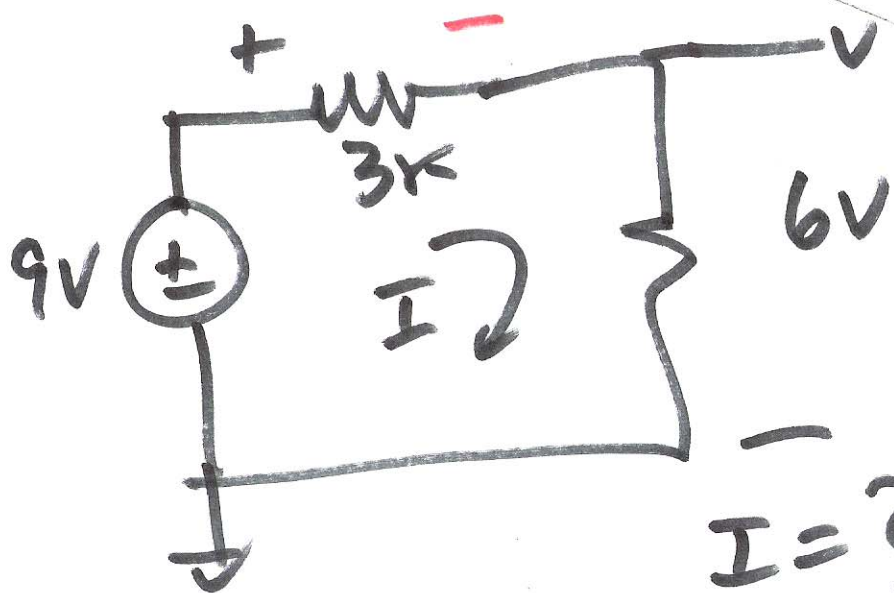


$$I = ?$$

$$V_{3k} = ?$$

$$V_{3k} = 9 - 6 = 3$$

$$\frac{3k}{3k} = I = 1 mA$$

6)

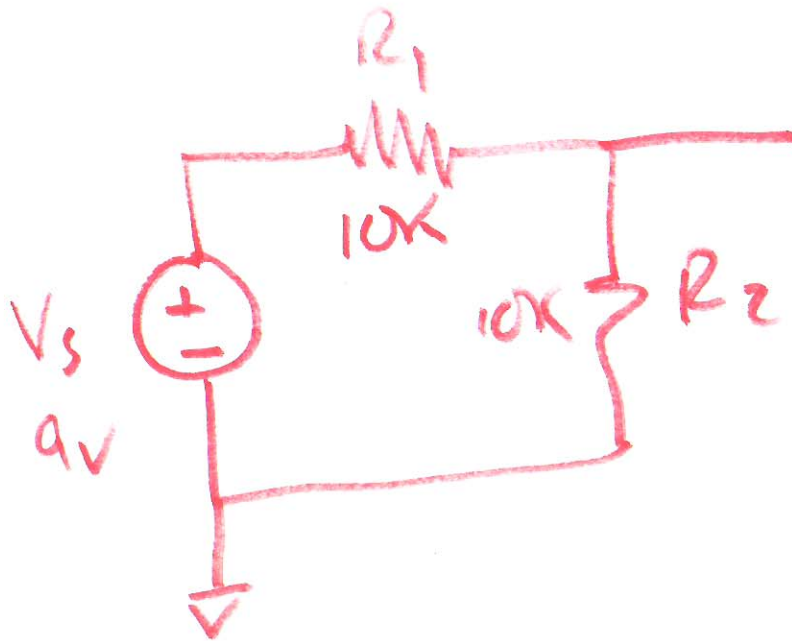


$$V_{out} = V_s \cdot \frac{R_2}{R_1 + R_2} = 9 \cdot \frac{10k}{20k}$$

$$V_{out} = 4.5V$$

$$V_{R1} = V_s \cdot \frac{R_1}{R_1 + R_2} = 4.5V$$

$$I = \frac{V_s}{R_1 + R_2}$$

7)

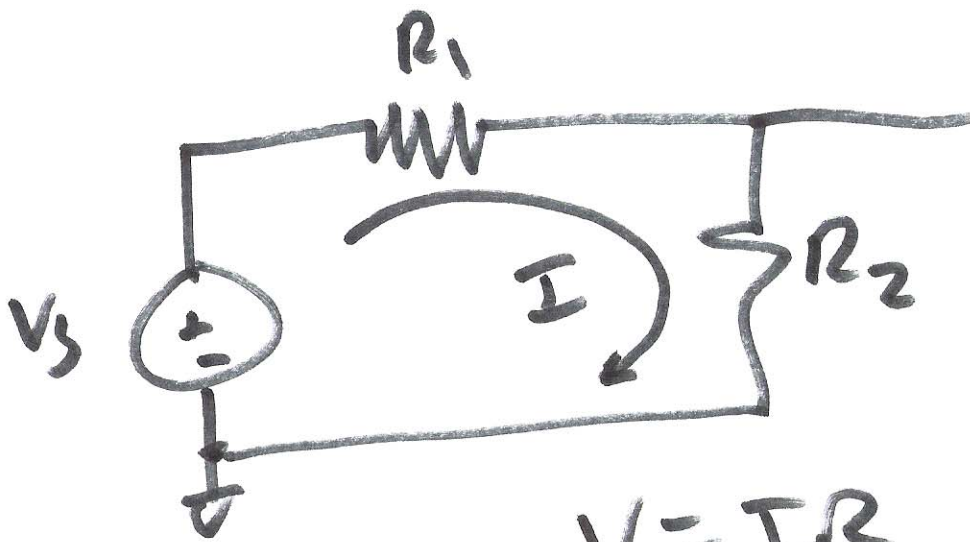

$$V_{OUT} = V_s \cdot \frac{R_2}{R_1 + R_2}$$

Voltage divider equation

$$V = IR$$

$$I = \frac{V}{R}$$

Quiz: Show how to derive the voltage divider equation!

$$I = \frac{V_s}{R_1 + R_2}$$

$$V_{OUT} = I \cdot R_2$$

$$V_{OUT} = V_s \cdot \frac{R_2}{R_1 + R_2}$$




$$V_{R1} = V_s \cdot \frac{R_1}{R_1 + R_2}$$

Do it two ways!



$$I = \frac{V_s}{R_1 + R_2}$$

$$V_{R1} \cong I \cdot R_1$$
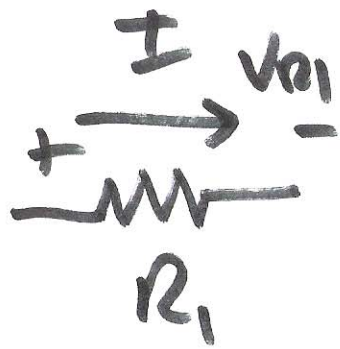
$$V_{R1} = V_s \cdot \frac{R_1}{R_1 + R_2}$$




\Rightarrow

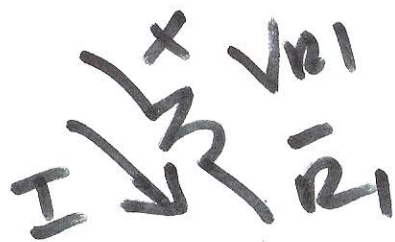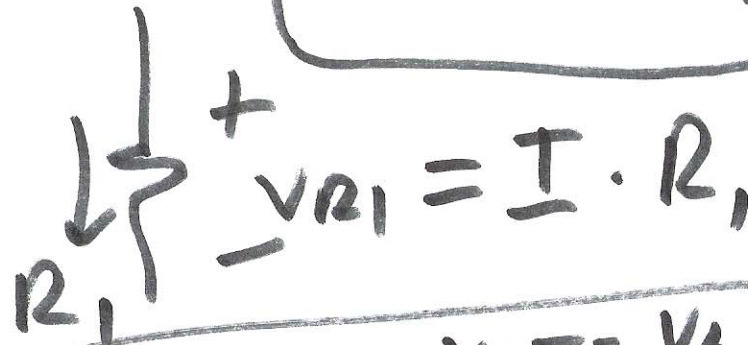


$$V_{R2} = V_s \cdot \frac{R_2}{R_1 + R_2}$$

$$V_{R1} = V_s - V_{R2}$$

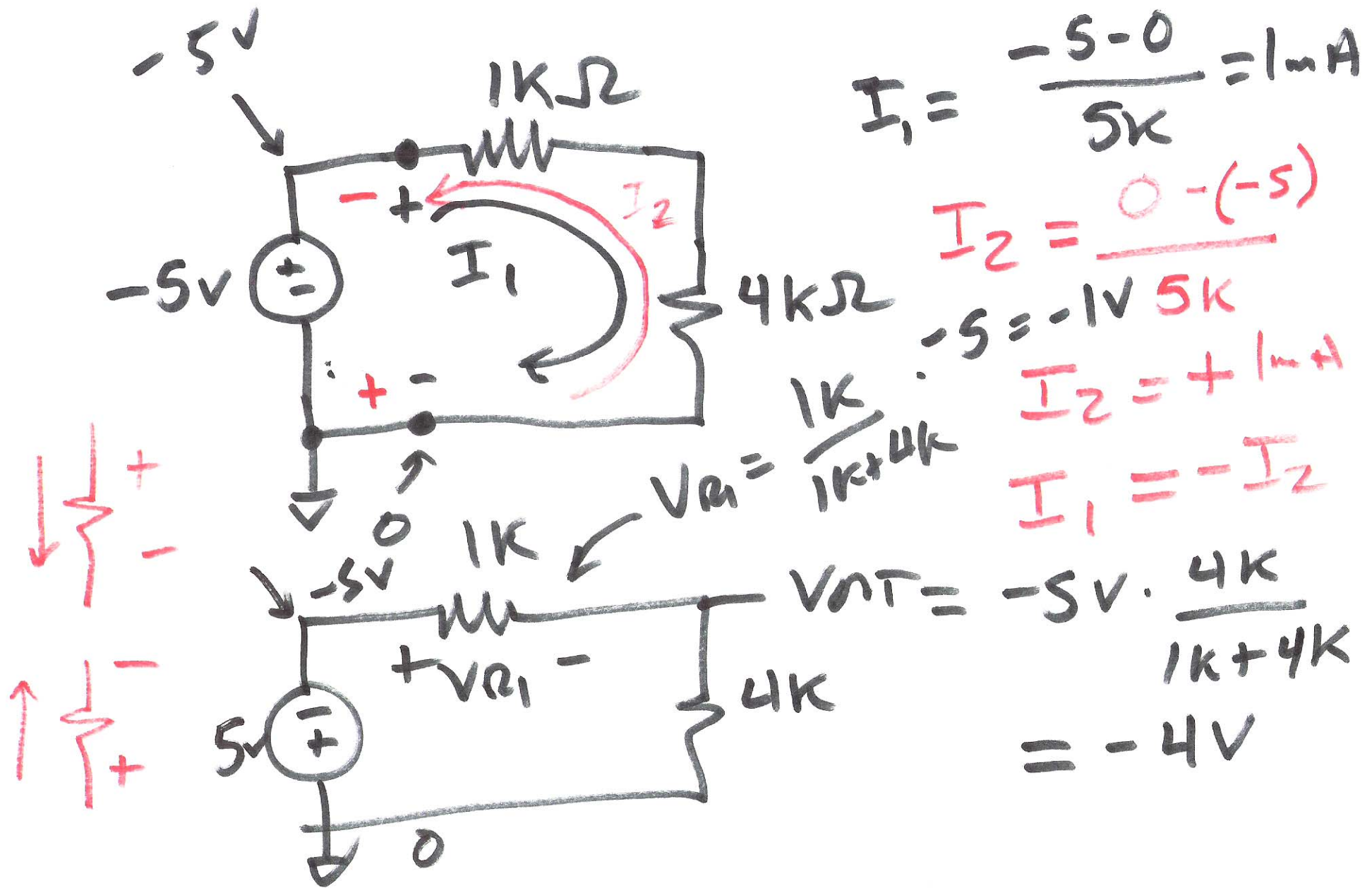
$$V_{R1} = V_s \cdot \frac{R_1}{R_1 + R_2}$$



10)

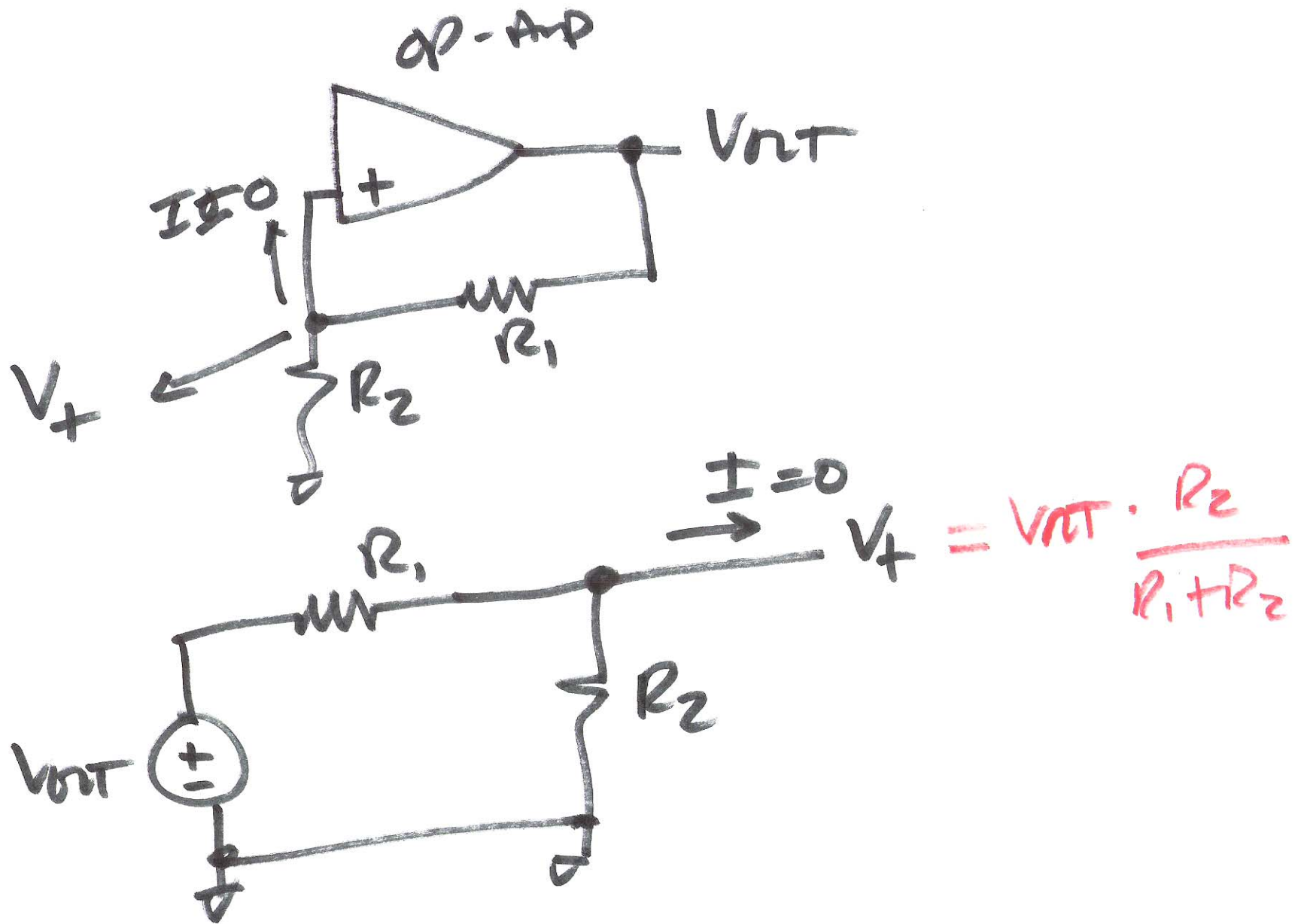

11)

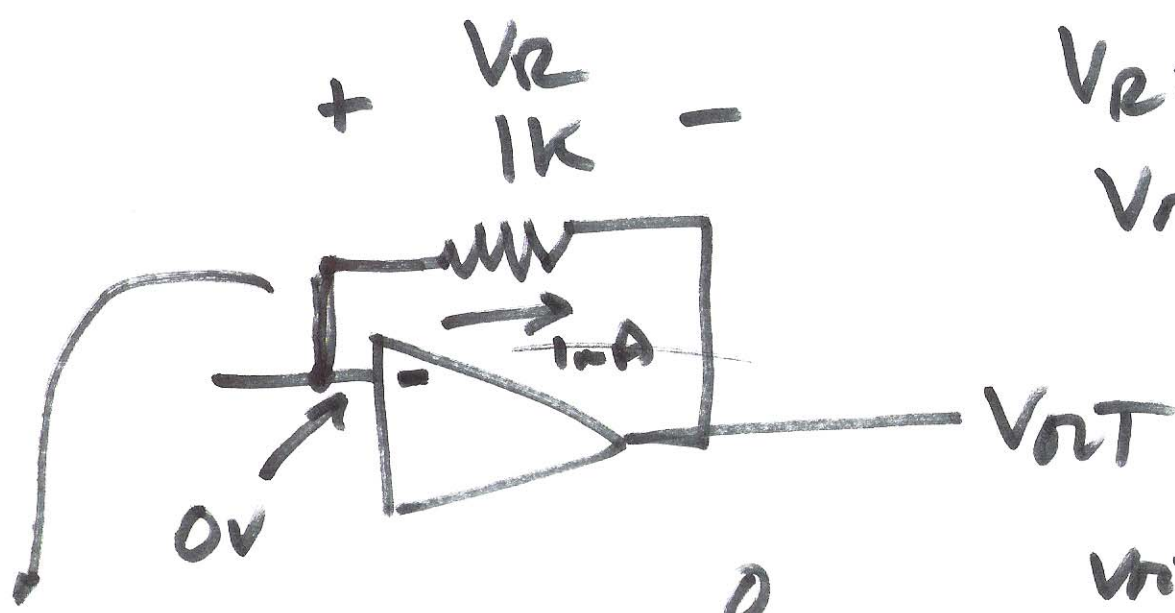

$V_R = ?$
 $V_{out} = ?$



$1mA \downarrow$
 $\left. \begin{array}{l} \text{---} \\ \text{---} \end{array} \right\} 1K$
 $+ 1mA \cdot 1K$
 $= 1V$

$V_R = V_L$
 $V_R = 1V$
 $V_{out} = -1V$

$V_R = -V_{out}$
 $V_R = -V_{out}$

$\left. \begin{array}{l} \text{---} \\ \text{---} \end{array} \right\} R$
 $+ V$
 $-$

12)

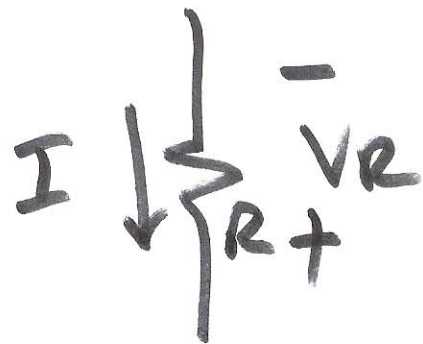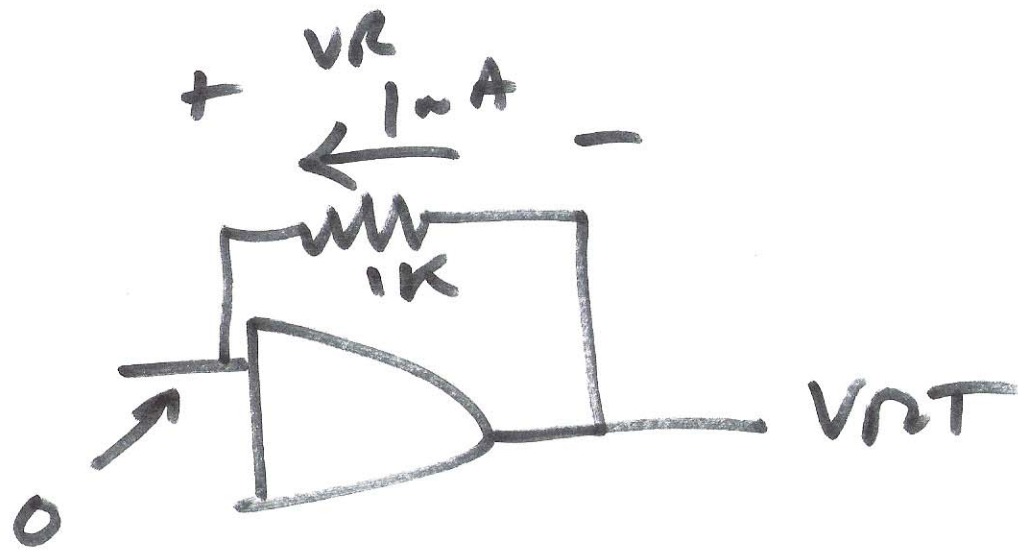


$$V_R = 0 - V_{out} = -V_{out}$$

$$V_R = -1\mu A \cdot 1K = -1V$$

$$V_{out} = 1V$$

$$-V_R = I \cdot R$$


$$V_R = -I \cdot R$$

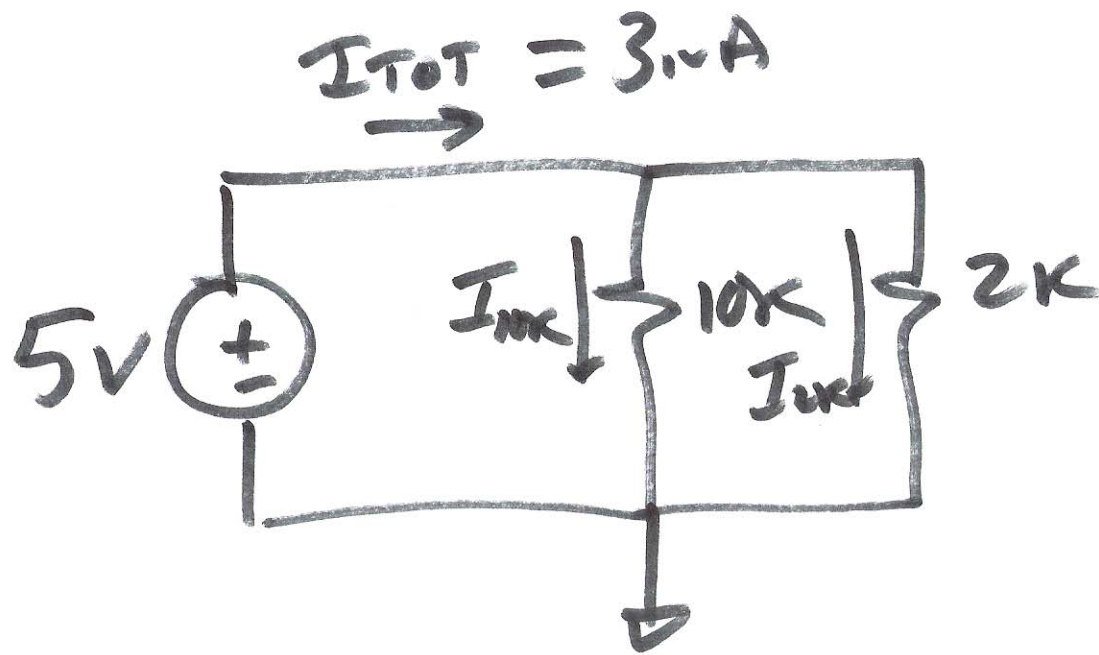

$$I_{10k} = \frac{5}{10k} = \frac{1}{2} \mu A$$

$$I_{2k} = \frac{5}{2k} = 2.5 \mu A$$

$$I_{TOT} = 3 \mu A$$

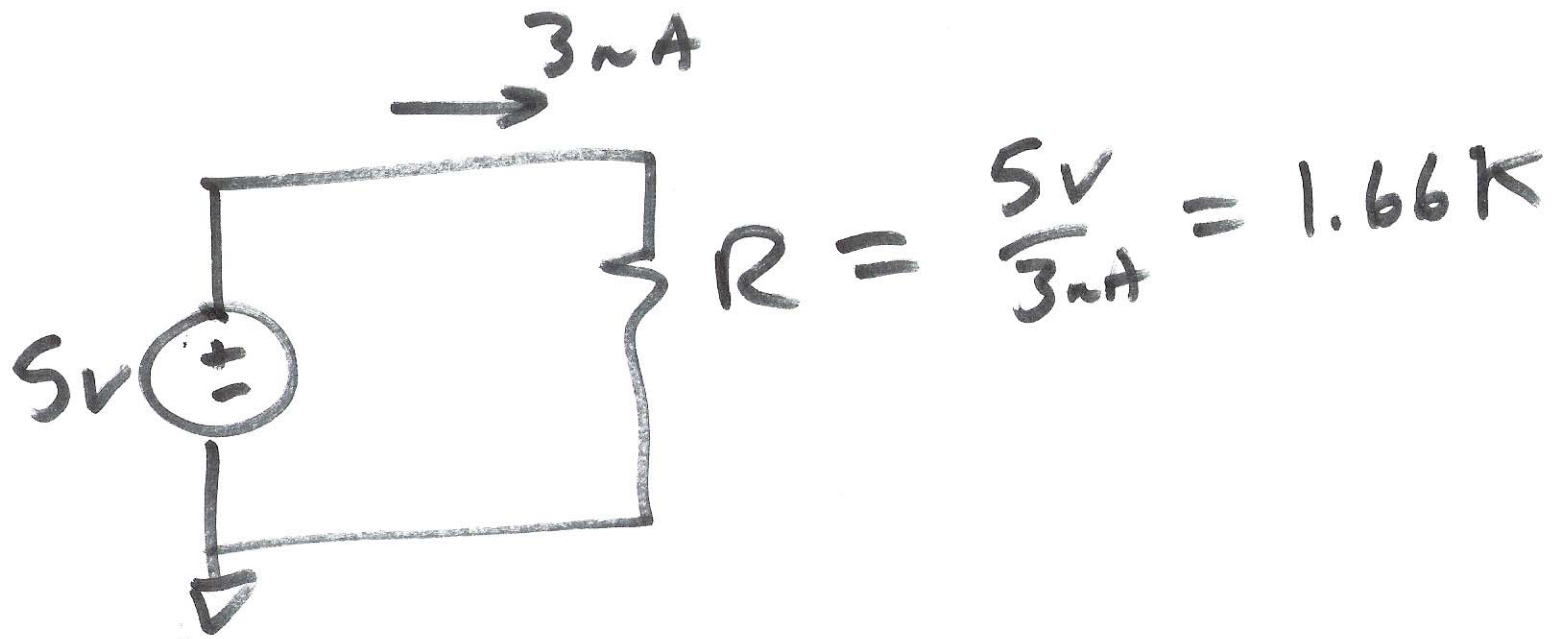

14)



How fast can I fill the pool with both hoses going at once?

$$\frac{1}{T} = \frac{2}{20} + \frac{1}{20}$$

$$= \frac{3}{20} \rightarrow T = \frac{20}{3} = 6.66 \text{ Hours}$$

$$T = \frac{10 \cdot 20}{10 + 20} = 6.66 \text{ Hours}$$