

EE 220


July 7, 2014

Lecture 20


$$V_c(0^-) = 15V$$




8.11

$$V_c(t) \geq 0$$

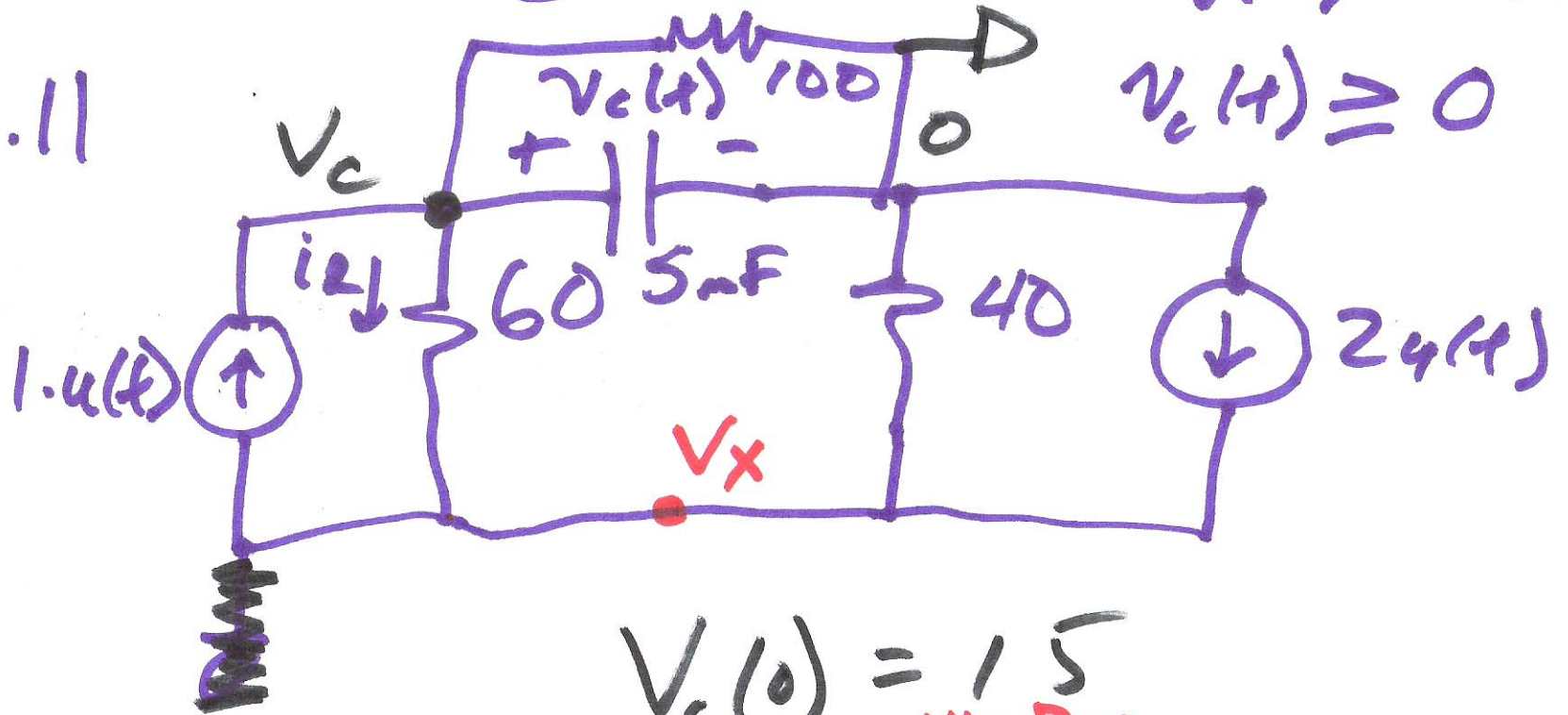

$$V_c(0) = 15$$

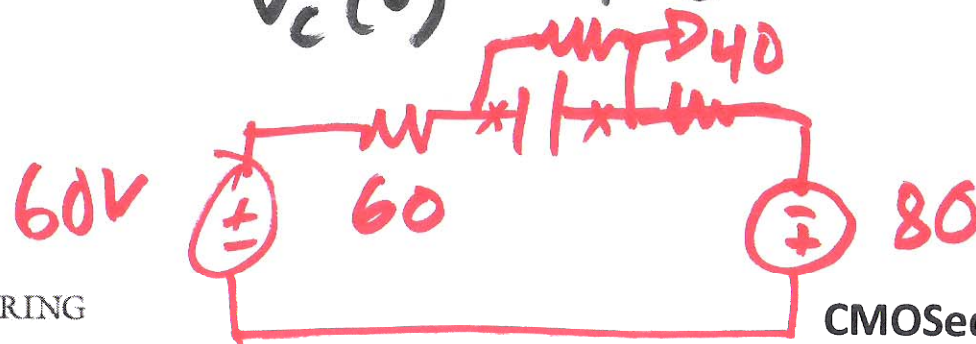

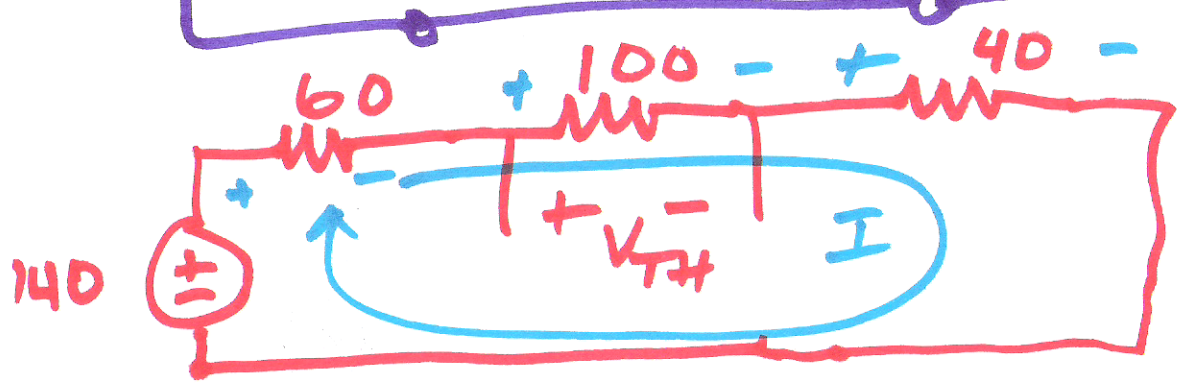
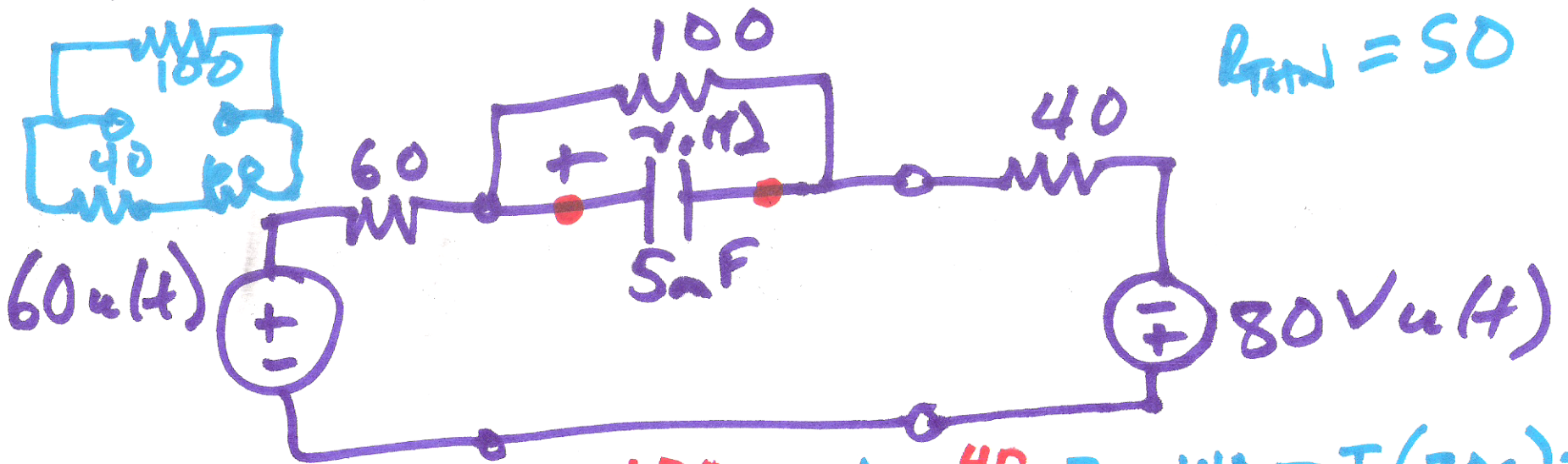
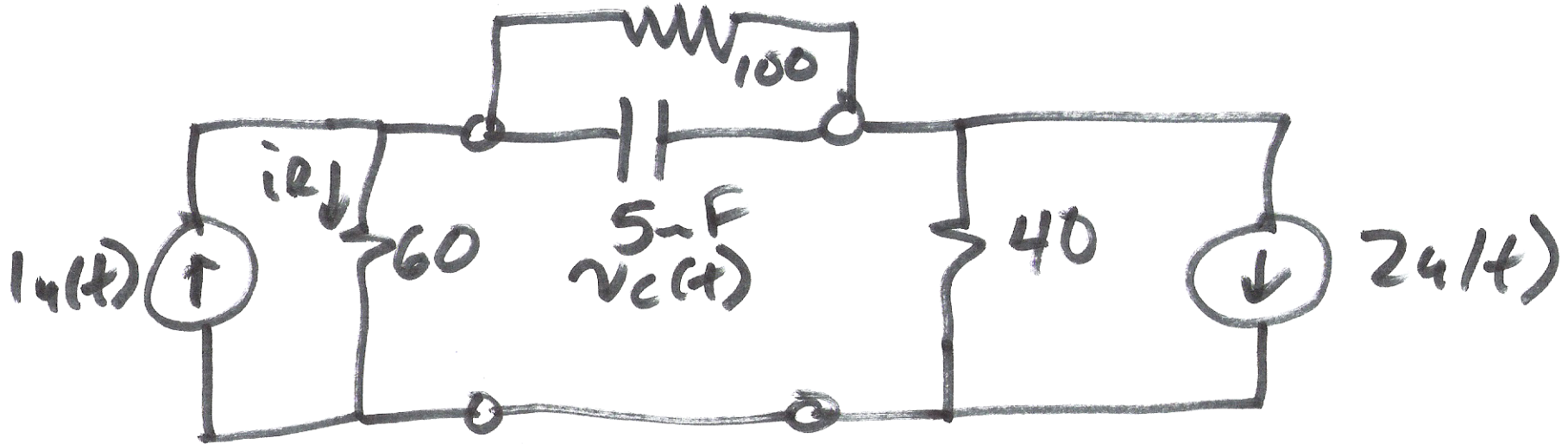


$$140 - I(200) = 0$$


$$I = \frac{140}{200} = 0.7$$

$$V_{TH} = 0.7 \cdot 100 = \underline{\underline{70V}}$$

2)

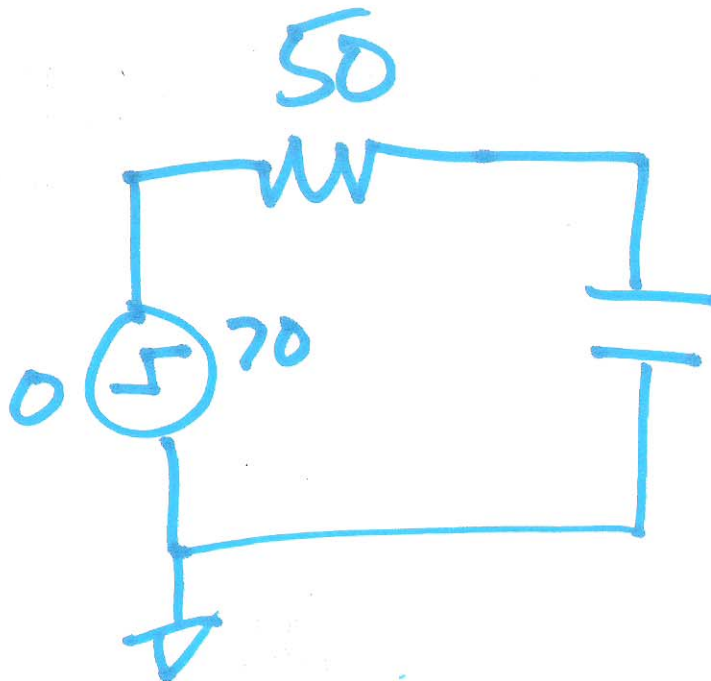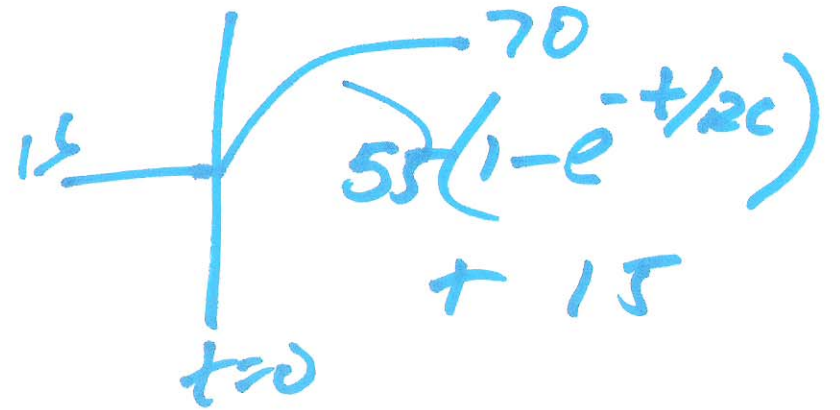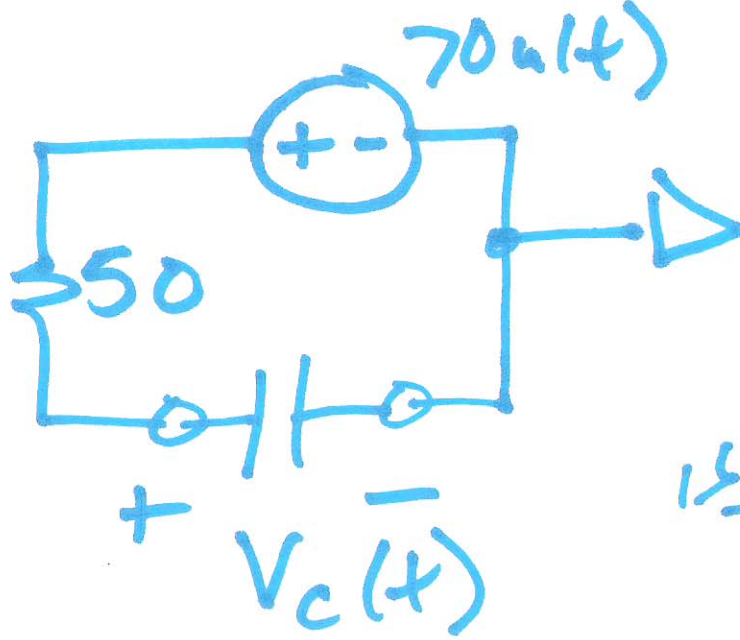


$$V_c(t) = 15 + 55e^{-t/25}$$

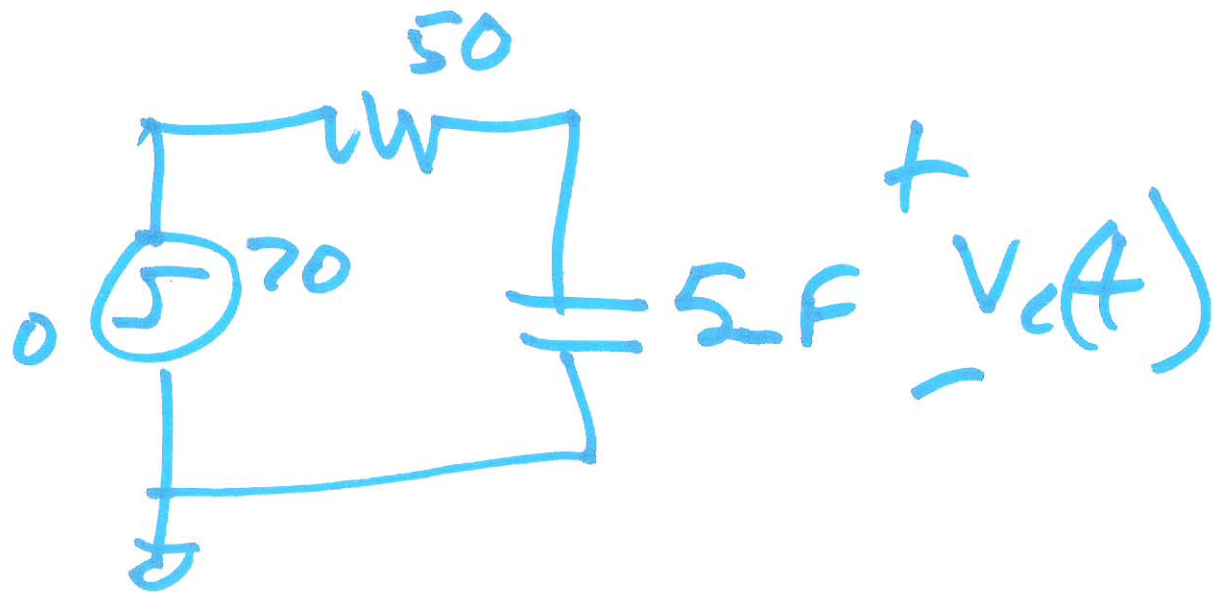

$$V_c(t) = 15 + 55 \left(1 - e^{-t/0.25} \right)$$
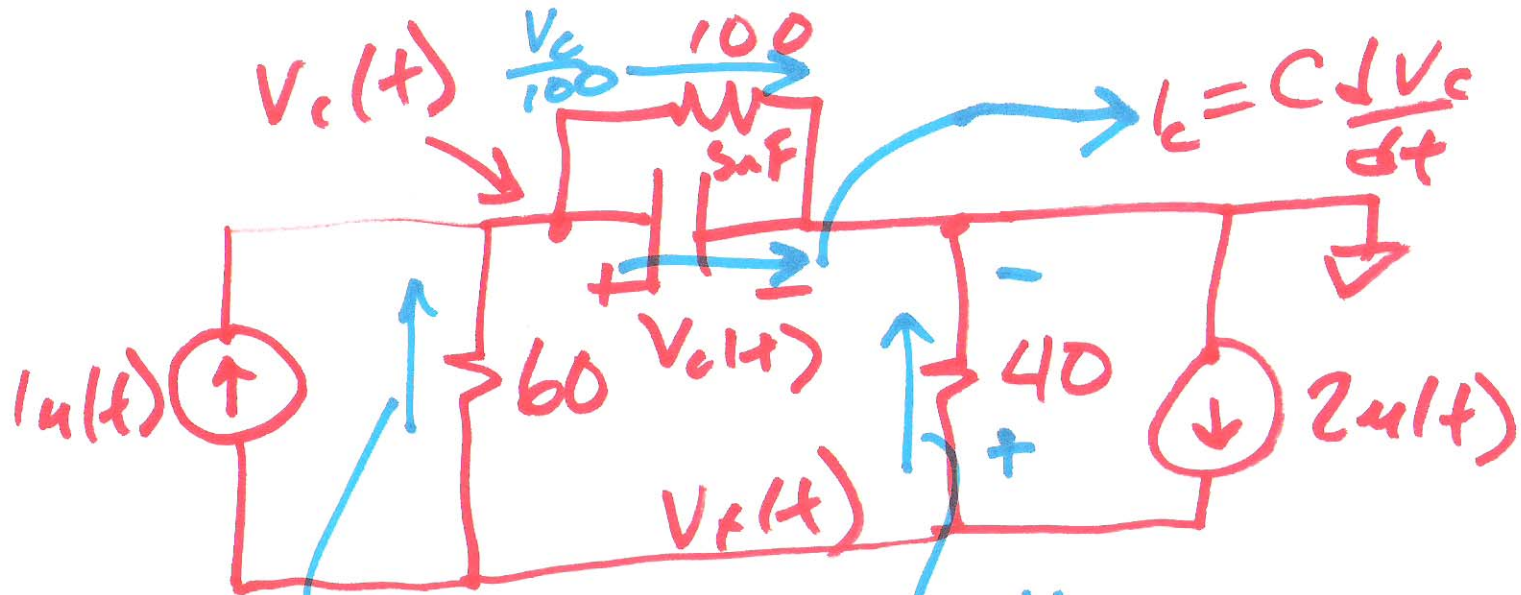
$$i_R = \frac{V_c(t)}{60} = \frac{70 - 55e^{-t/0.25}}{60} = \frac{7}{6} - \frac{11}{12} e^{-t/0.25}$$



$$\frac{V_x - V_c}{60}$$

$$\frac{V_x}{40}$$

$$5V_x - 2V_c = 120$$

$$V_x = \frac{120 + 2V_c}{5}$$

$$1 + \frac{V_x - V_c}{60} + \frac{V_x}{40} = 2, \quad 120 + 2V_x - 2V_c + 3V_x = 240$$

$$1 + \frac{V_x - V_c}{60} = \frac{V_c}{100} + C \frac{dv_c}{dt}$$

5)

$$60 + V_x - V_c = 0.6V_c + 60C \cdot \frac{dV_c}{dt}$$

$$60 + 24 + 0.4V_c - V_c = 0.6V_c + 60C \frac{dV_c}{dt}$$

$$84 = 1.2V_c + 60C \frac{dV_c}{dt}$$

$$V_c(t) = K_0 + K_1 e^{-t/\tau_c}$$

$$V_c(t) = 70 - 55e^{-t/\tau_c} \quad \text{at } t=0 \quad V_c(t) = 15 = K_0 + K_1$$

$$\text{at } t=\infty \quad V_c(t) = 70 = K_0$$

$$K_1 = -55$$

6)

$L = 25.3\mu$
 $C = 1\mu$
 $R = 1K$


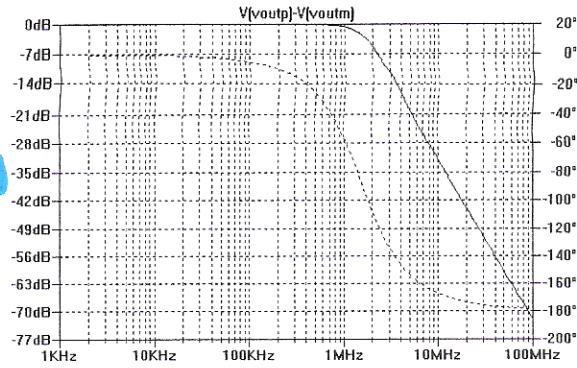


Figure 3.38 Magnitude and phase responses for the active-RC filter of Ex. 3.9.

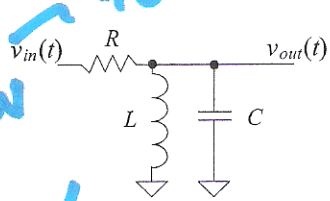$1\mu \approx 40$
 25.3μ
 $\sqrt{\frac{C}{L}} \approx 6$
 $Q = 6000$



$$\frac{v_{out}}{v_{in}} = \frac{s \frac{1}{RC}}{s^2 + s \frac{1}{RC} + \frac{1}{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

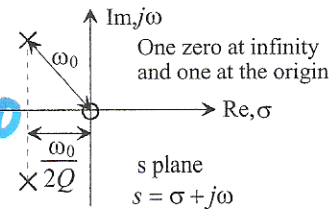
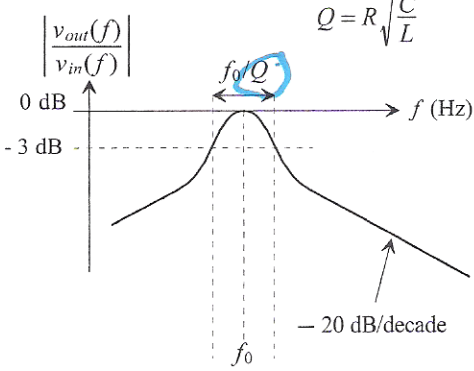


Figure 3.39 Second-order bandpass filter.

Example 3.10

Repeat Ex. 3.8 for the bandpass LRC circuit.

Again, we can set $C = 100$ pF and $L = 100$ μ F. Solving for Q using the equation in Fig. 3.39 results in

$$Q = R \sqrt{\frac{C}{L}} = 0.707 = R \sqrt{\frac{100p}{100\mu}} \rightarrow R = 707$$

The simulation results are seen in Fig. 3.40. ■

7)

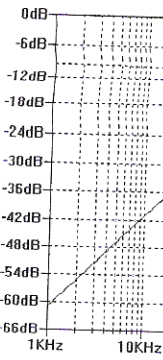


Figure 3.40 Bandpass re

Example 3.11

Repeat Ex. 3.10 if the Q is inc

Figure 3.41 shows the simulat 20k with the inductor and cap

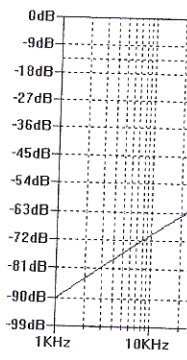


Figure 3.41 Bandpass re


Example 3.12

Use an active-RC filter to imple

Let's begin by writing the filter's

$$\frac{v_{out}}{v_{in}} = \frac{a_1 s}{s^2 + \left(\frac{2\pi f_0}{Q}\right) s + \dots}$$

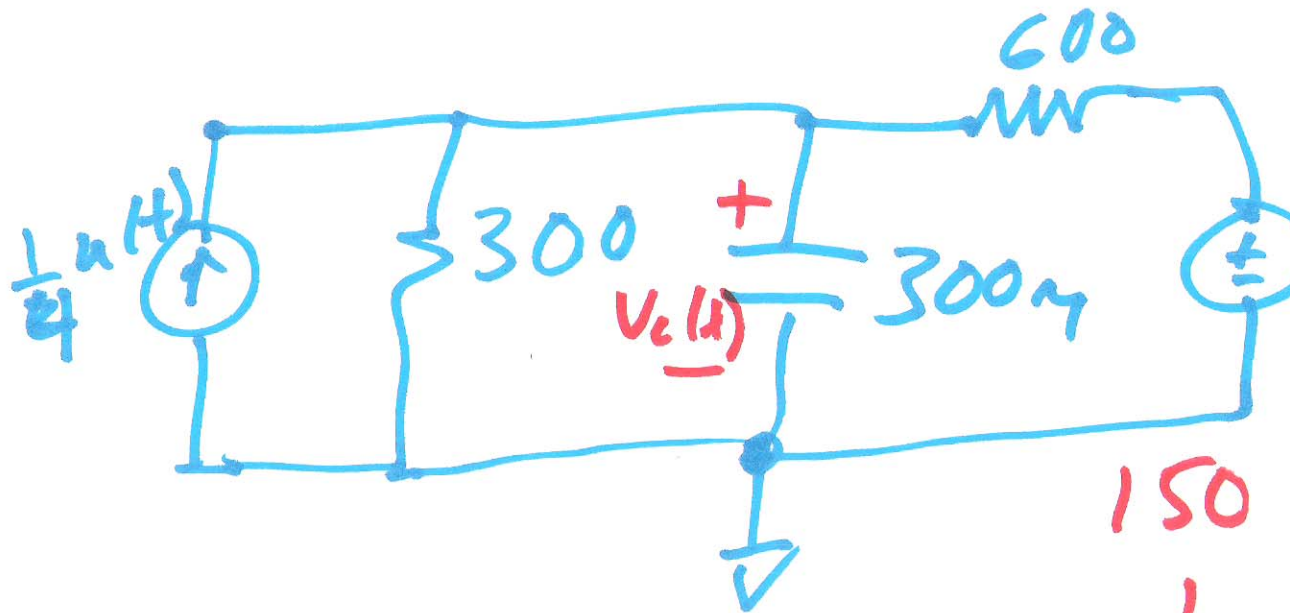Looking at this equation, Eq. (3 $C_{12} = 0$ and $R_{11} = \infty$. Further the



$t=0^-, V_c(0^-)=0$


$100\mu(t-1)$

$3V_c = 250$

$150 = 2V_c + V_c - 100$

$\frac{1}{4} = \frac{V_c(\infty)}{300} + \frac{V_c(\infty) - 100}{600}$

$t = \infty$

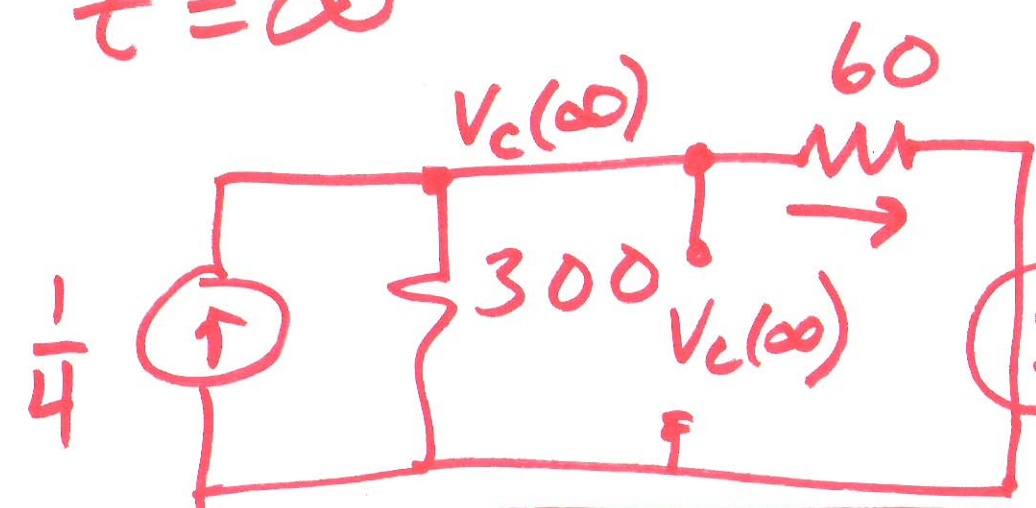

~~$75 = V_c + 5V_c - 500$~~

~~$575 = 6V_c$~~

~~$V_c(\infty) = \frac{575}{6}$~~

~~95.8~~

$V_c(\infty) = \frac{95.8}{1.14} = 83.33$


4)

$$V_c(t) = 0 \quad t < 0$$


$$V_c(t) = 50(1 - e^{-t/\tau}) \quad t > 0$$

$$\tau = 200 \cdot 300 \mu = 60 \mu s$$


$$300 \parallel 600 = 200$$

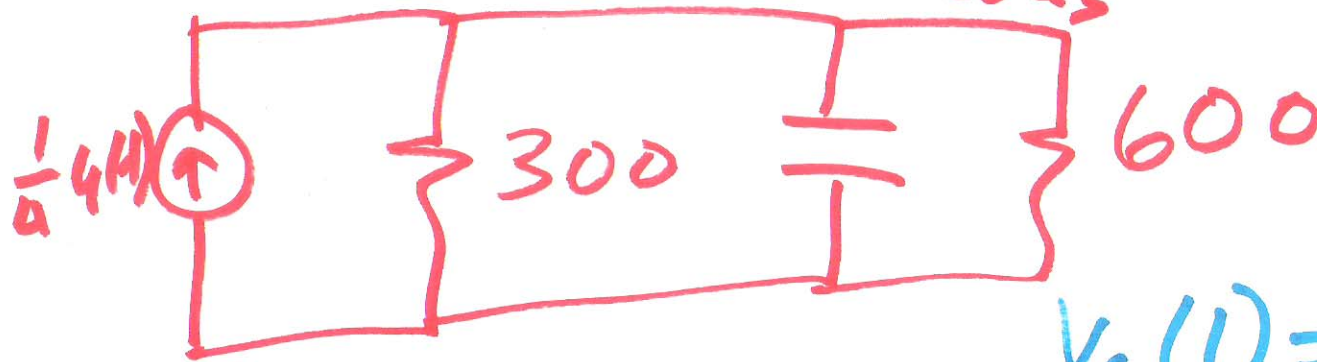

$$V_c(1) = 50 \text{ V}$$

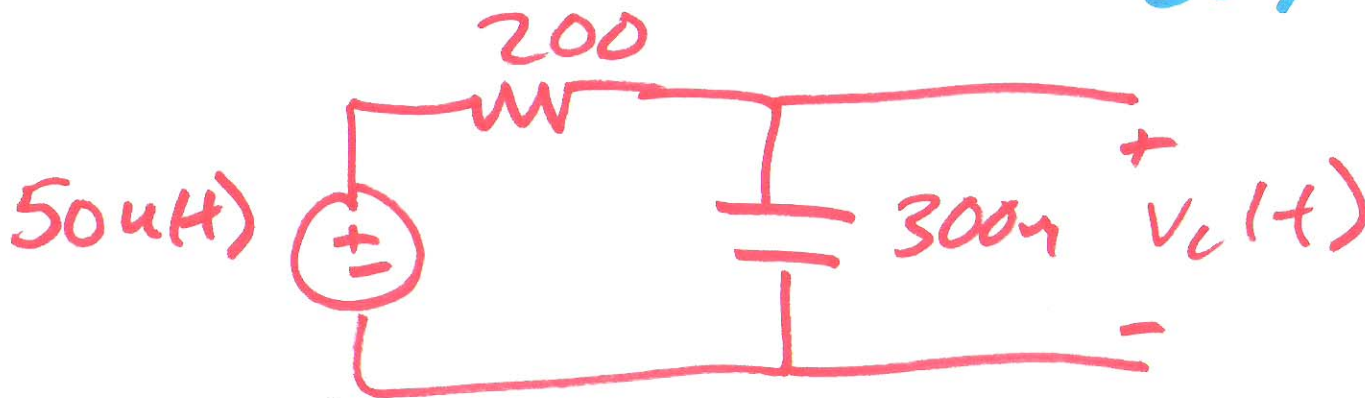


$$V_c(1^-) = 50V$$

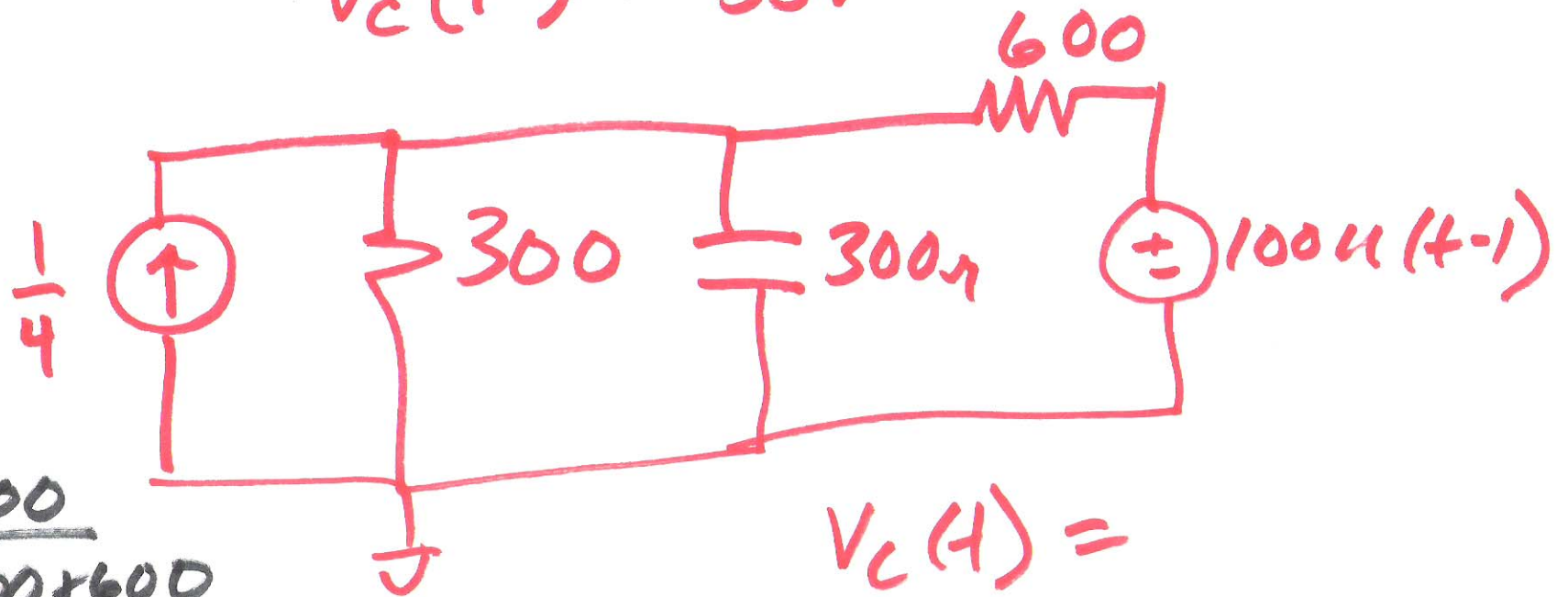


$$100 \cdot \frac{300}{300+600} = 33.33V$$

$$V_c(t) = \quad t > 1$$

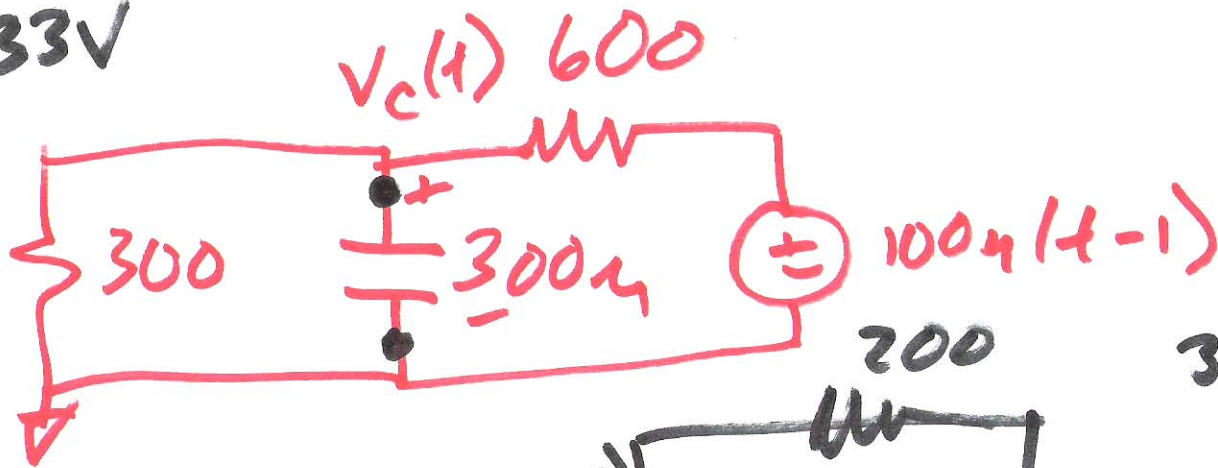
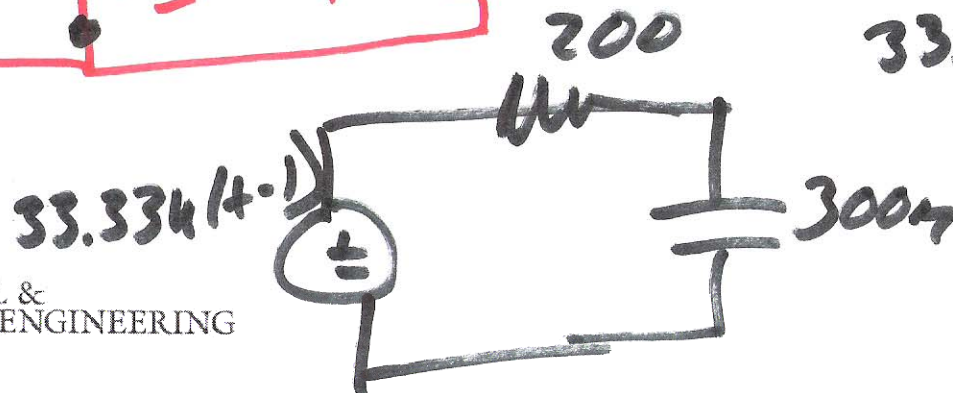
$$33.33 \left(1 - e^{-\frac{(t-1)}{60ms}} \right)$$



10)

$$V_c(t) = 50 + 33.33 \left(1 - e^{-\frac{(t-1)}{60 \mu s}} \right)$$

$t > 1$

$$V_c(t) = 50 \left(1 - e^{-t/60 \mu s} \right) \quad 0 \leq t \leq 1$$

$$V_c(t) = 0 \quad t < 0$$

11)