


EE 220

Lecture 21

$5V - 8k \cdot I_1$

July 9, 2014

$2 + 4kI_2 = V_x$

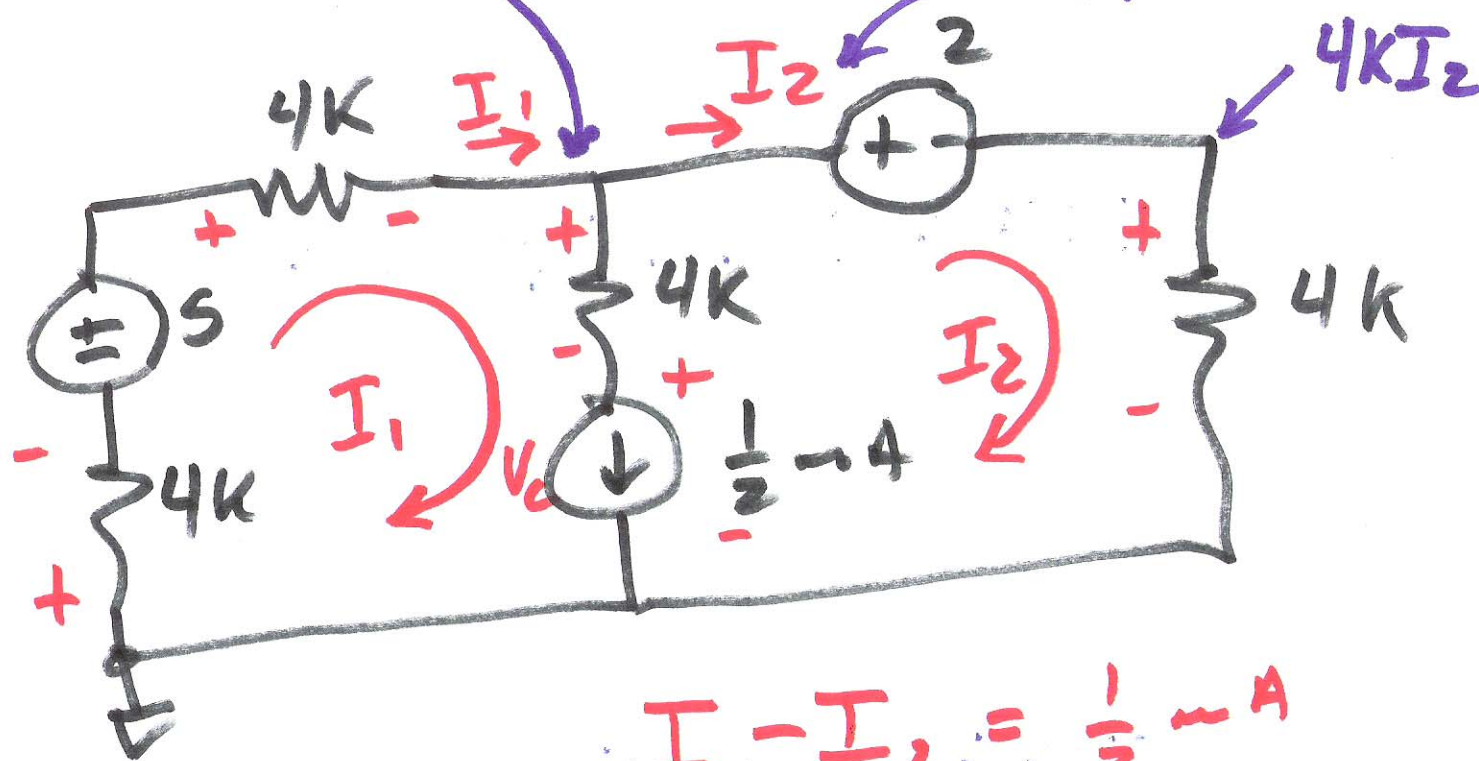

$I_1 - I_2 = \frac{1}{2} \text{ mA}$

$-V_c + 5 - 4kI_1 - 4k(I_1 - I_2) - 4kI_1 = 0$

$V_c + 4k(I_2 - I_1) = 2 + 4kI_2 = 0$

1)

$$5 - 8kI_1 = 2 + 4kI_2$$

$$I_1 = \frac{1}{2}A + I_2$$

$$\frac{5 - 4V}{1} - 8kI_2 = 2 + 4kI_2$$

$$-1 = 12kI_2$$


$$I_2 = \frac{-1}{12k} = -83.34A$$

$$I_1 = .4 \text{ ~~mA~~ } \text{ ~~mA~~ }$$

$$V_x = 2 + 4k \cdot (-83.34A) = \underline{\underline{1.67V}}$$

2)


OP-AMP integrator

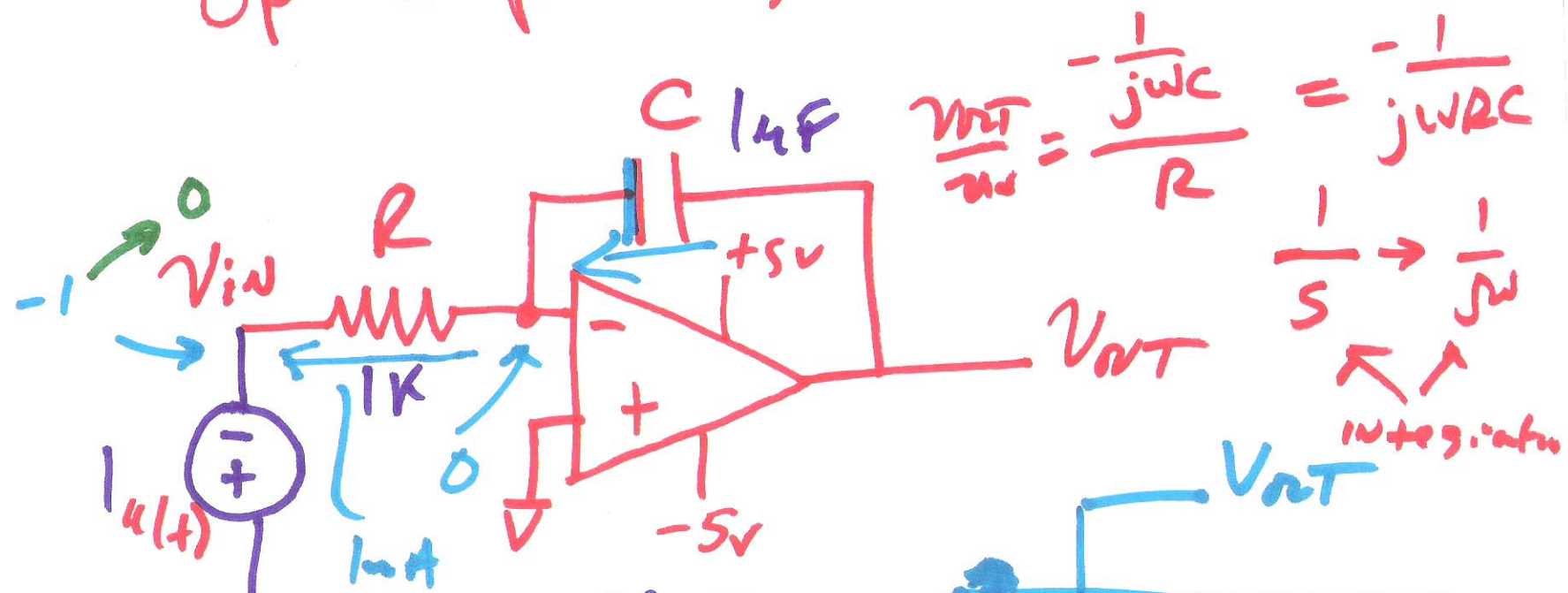

$$\frac{V_{out}}{V_{in}} = \frac{-\frac{1}{j\omega C}}{R} = -\frac{1}{j\omega RC}$$


$\frac{1}{s} \rightarrow \frac{1}{j\omega}$
 ↑ ↑
 integrator

$s \rightarrow j\omega$
 differentiation

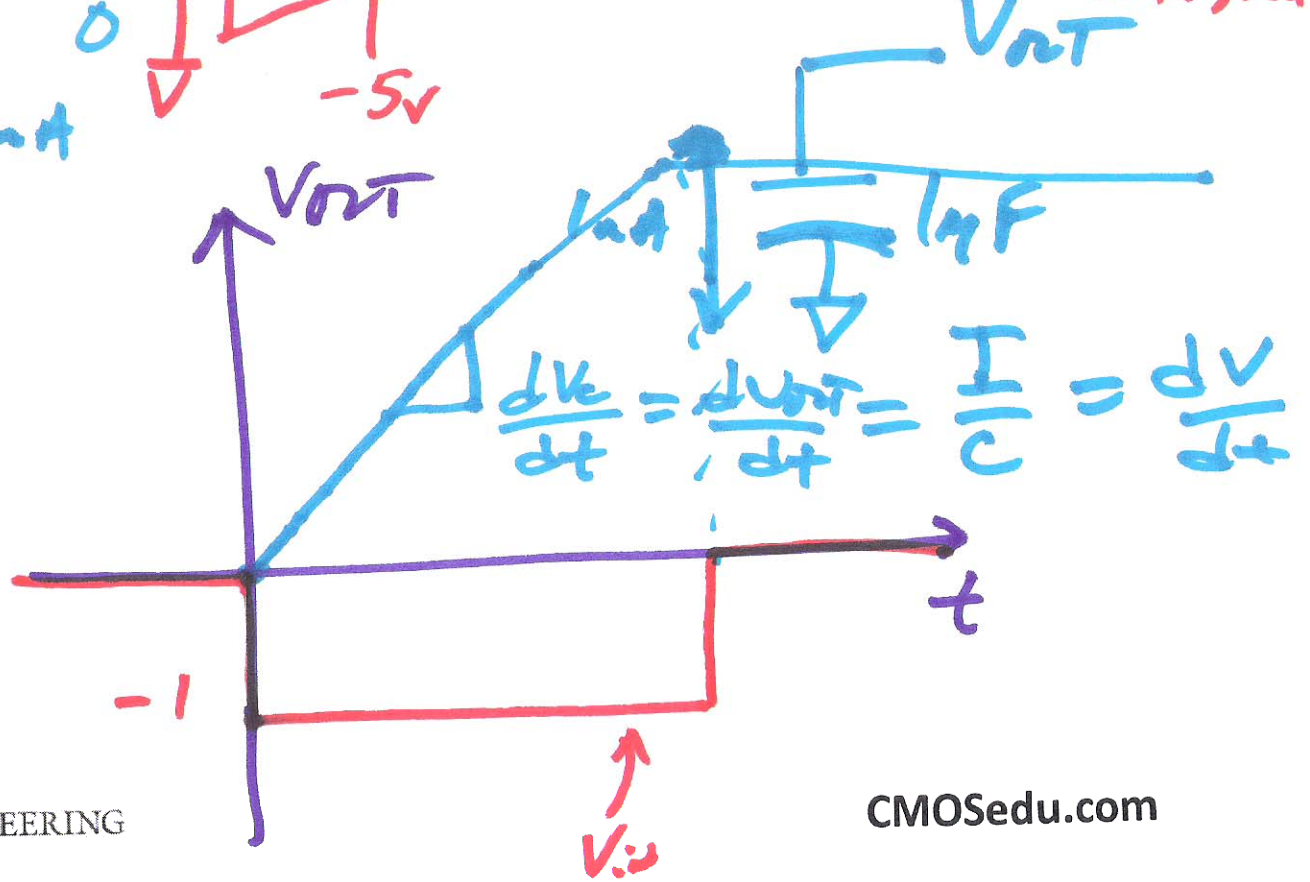


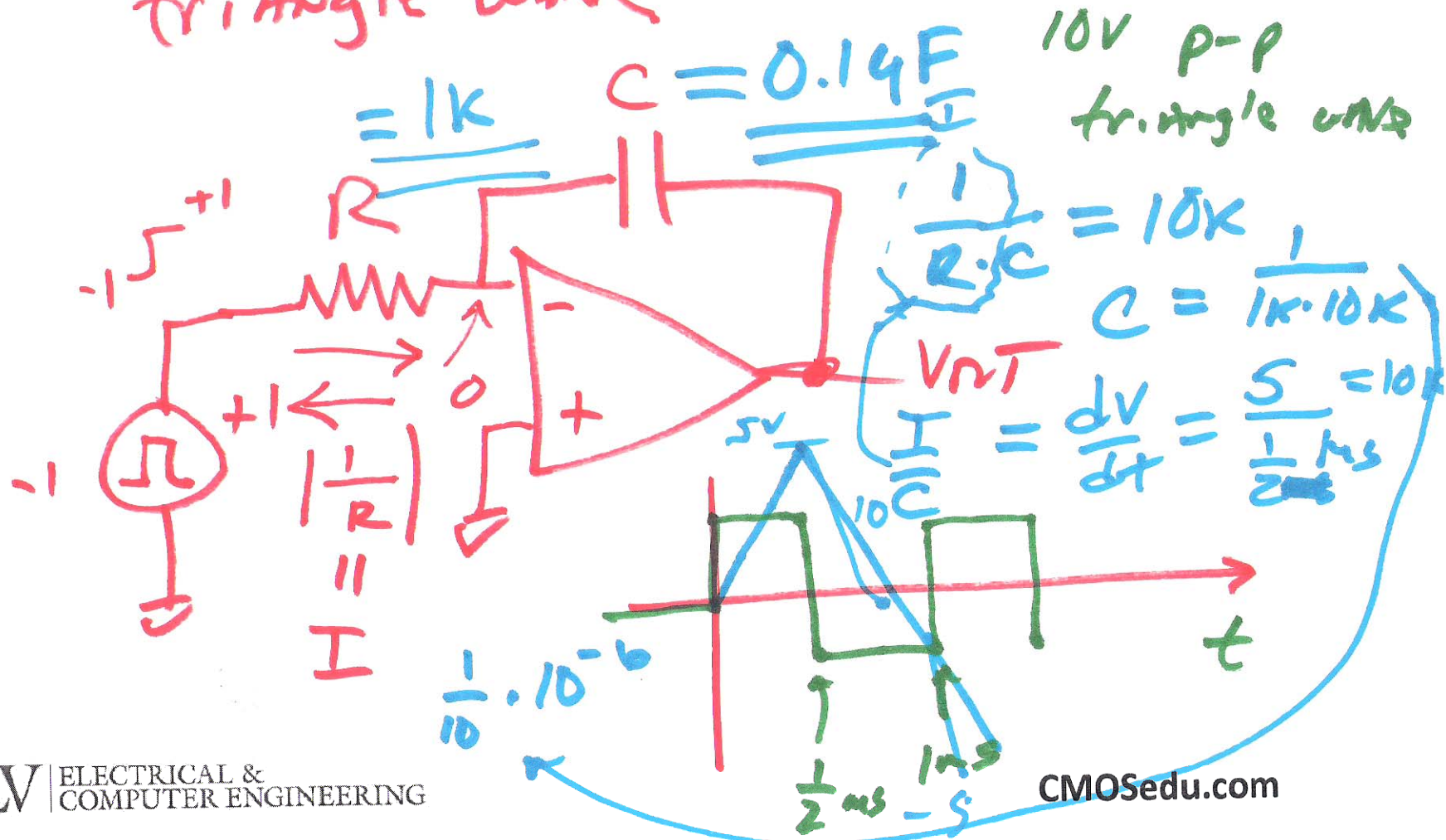3)

DESIGN a circuit that can
 CONVERT a +1 to -1V squarewave
 @ 1kHz into a +5 to -5V
 triangle wave




4)

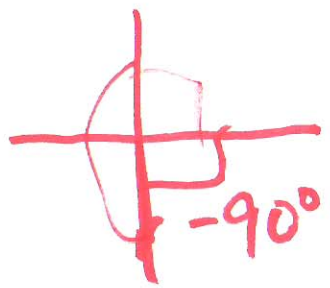

$$\frac{1}{j} = -j$$
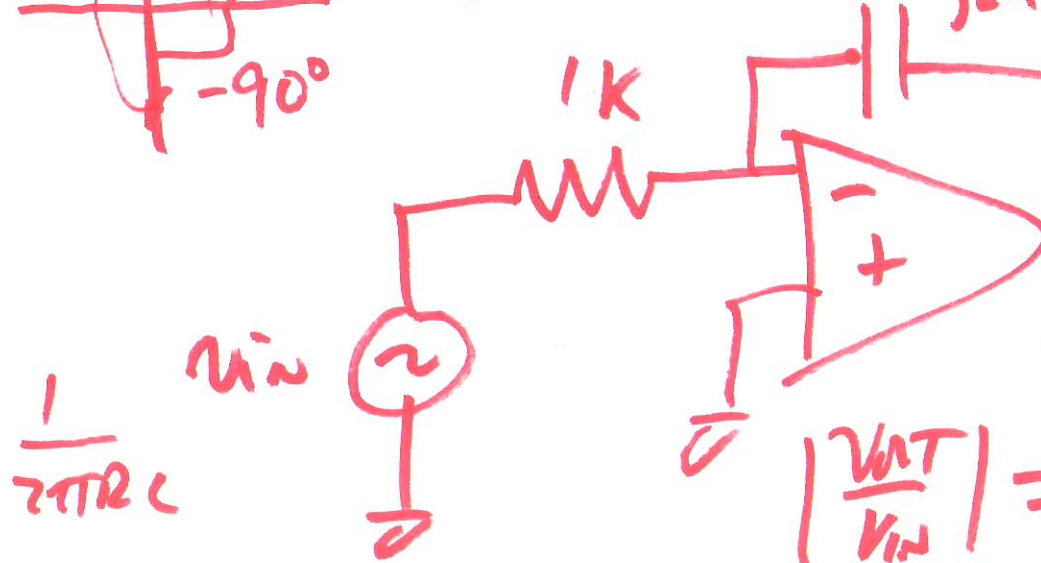
$$\frac{0.14}{j2\pi f \cdot 10^{-6}} \quad 20 \log 10^3$$



$$60 \log 1$$

$$1.59 \quad 60 \text{ dB}$$

$$.159 = \frac{1}{2\pi}$$

$$\frac{1}{2\pi RC}$$

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{1}{2\pi / 10^3 \cdot 10^3 \cdot 10^{-6}}$$

$$2 \rightarrow 6 \text{ dB}$$

$$\sqrt{2} \rightarrow 3 \text{ dB}$$

$$\left| \frac{1}{2\pi f \cdot RC} \right| = 1$$

unity

$$\frac{v_{out}}{v_{in}} = - \frac{1}{j\omega C} = - \frac{1}{j\omega RC} \quad \frac{1}{2} \rightarrow -6 \text{ dB}$$

$$\frac{1}{\sqrt{2}} \rightarrow -3 \text{ dB}$$

$$\angle \frac{v_{out}}{v_{in}} = 180 - 90 = +90^\circ$$

$$2,000 \rightarrow 66 \text{ dB}$$

$$66 \text{ dB} = 20 \log 10^3 + 20 \log 2 = 20 \log 1000 \times 2$$