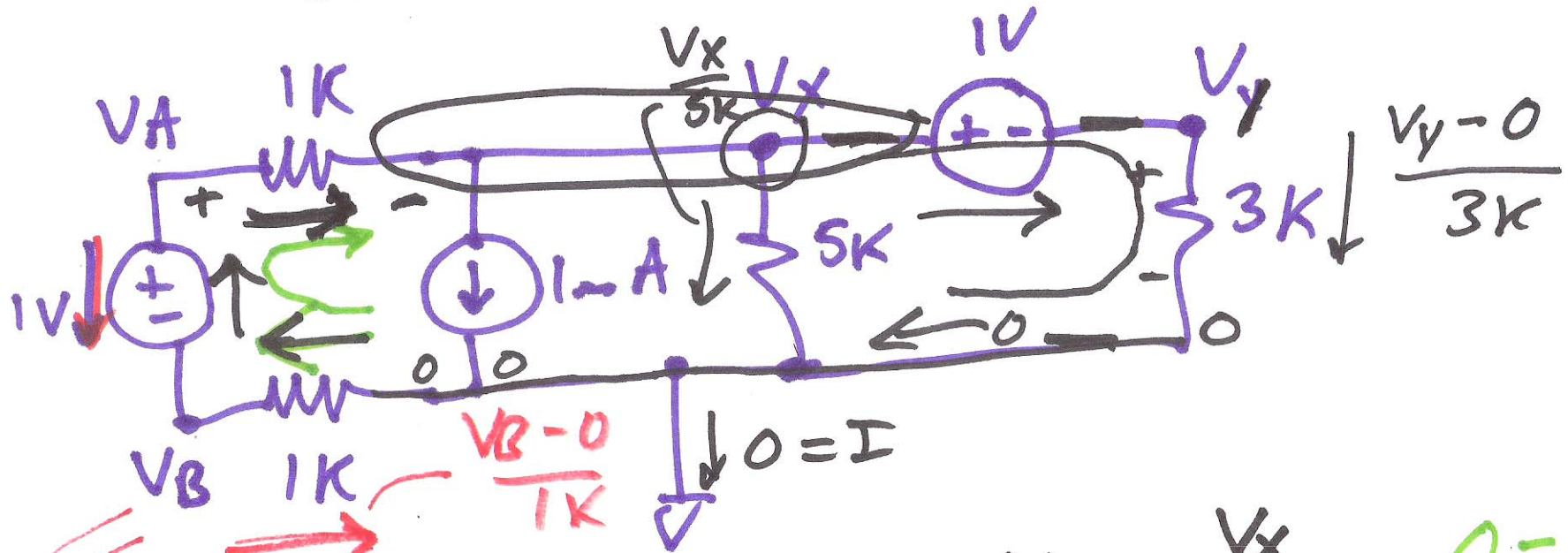


Lec 3

6/11/14


CIRCUITS I EE 220



$$V_A - 1 = V_B \quad \frac{V_y}{3K} + \frac{V_x}{5K} + 1mA = \frac{V_A - V_x}{1K} = \frac{0 - V_B}{1K}$$

Vx
Vy
VA VB

1)

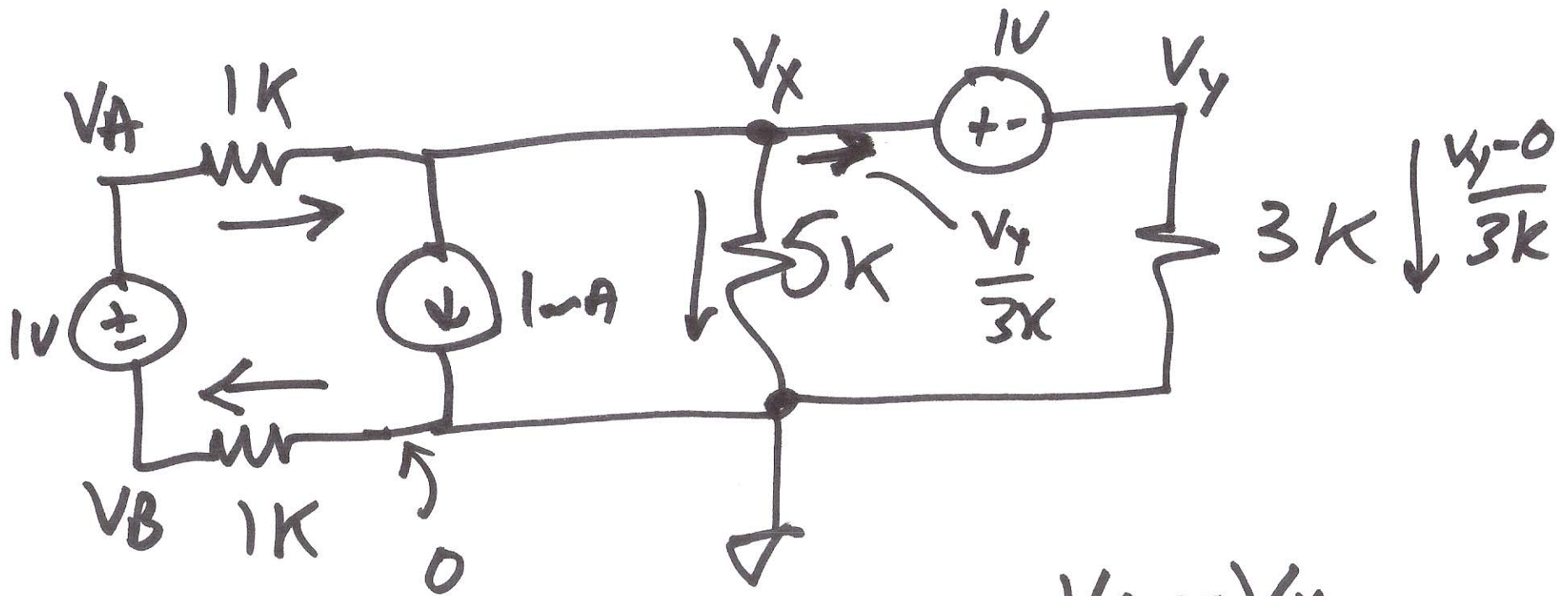

V_y
 V_x
 V_A
 V_B



$$\textcircled{1} \quad \frac{V_y}{3k} + \frac{V_x}{5k} + 1mA = \frac{V_A - V_x}{1k}$$


$$\textcircled{2} \quad \frac{0 - V_B}{1k} = \frac{V_A - V_x}{1k}, \quad V_B = V_A - 1 \quad \textcircled{3}$$

$$V_A - V_B = 1$$

$$V_x - V_y = 1 \quad \textcircled{4}$$


e)

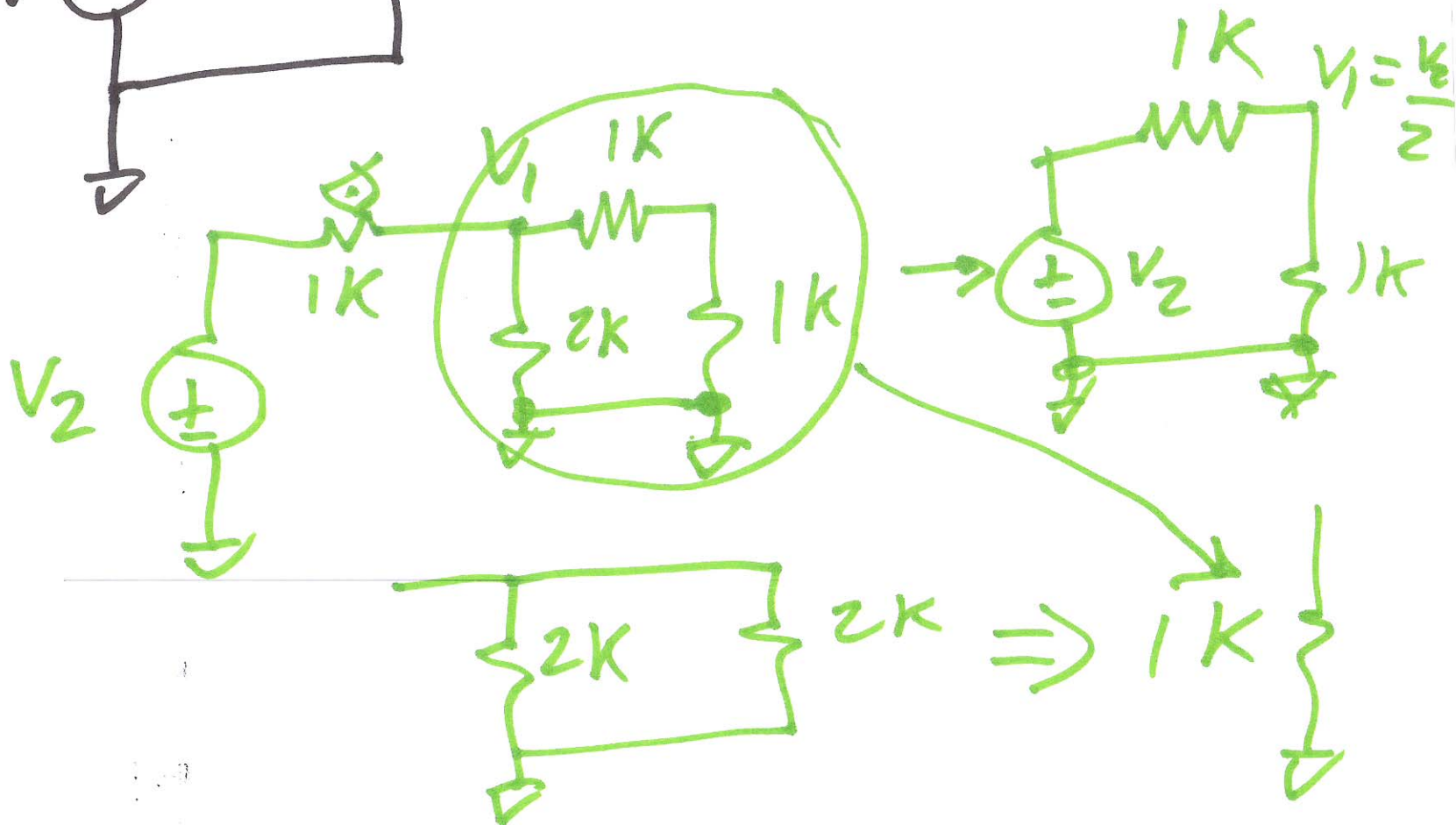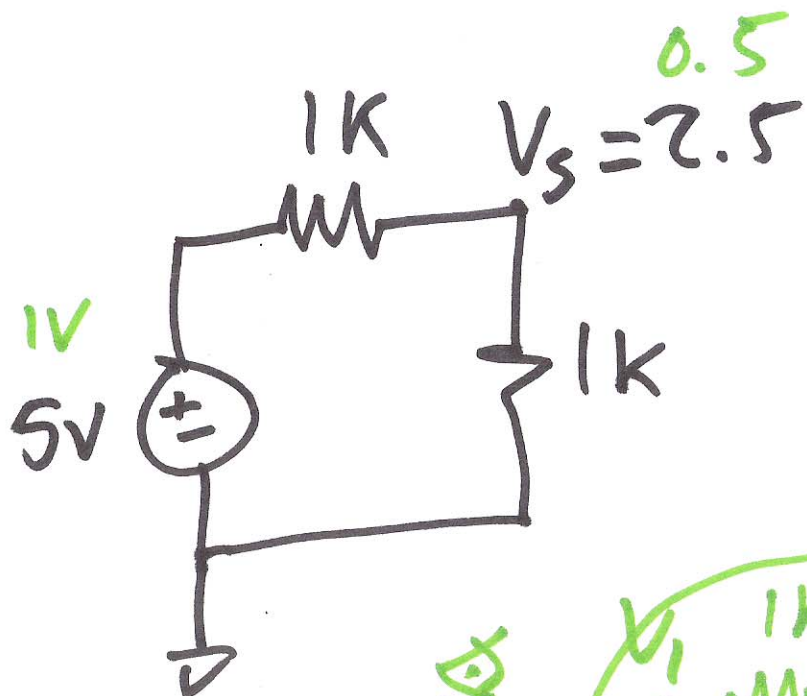

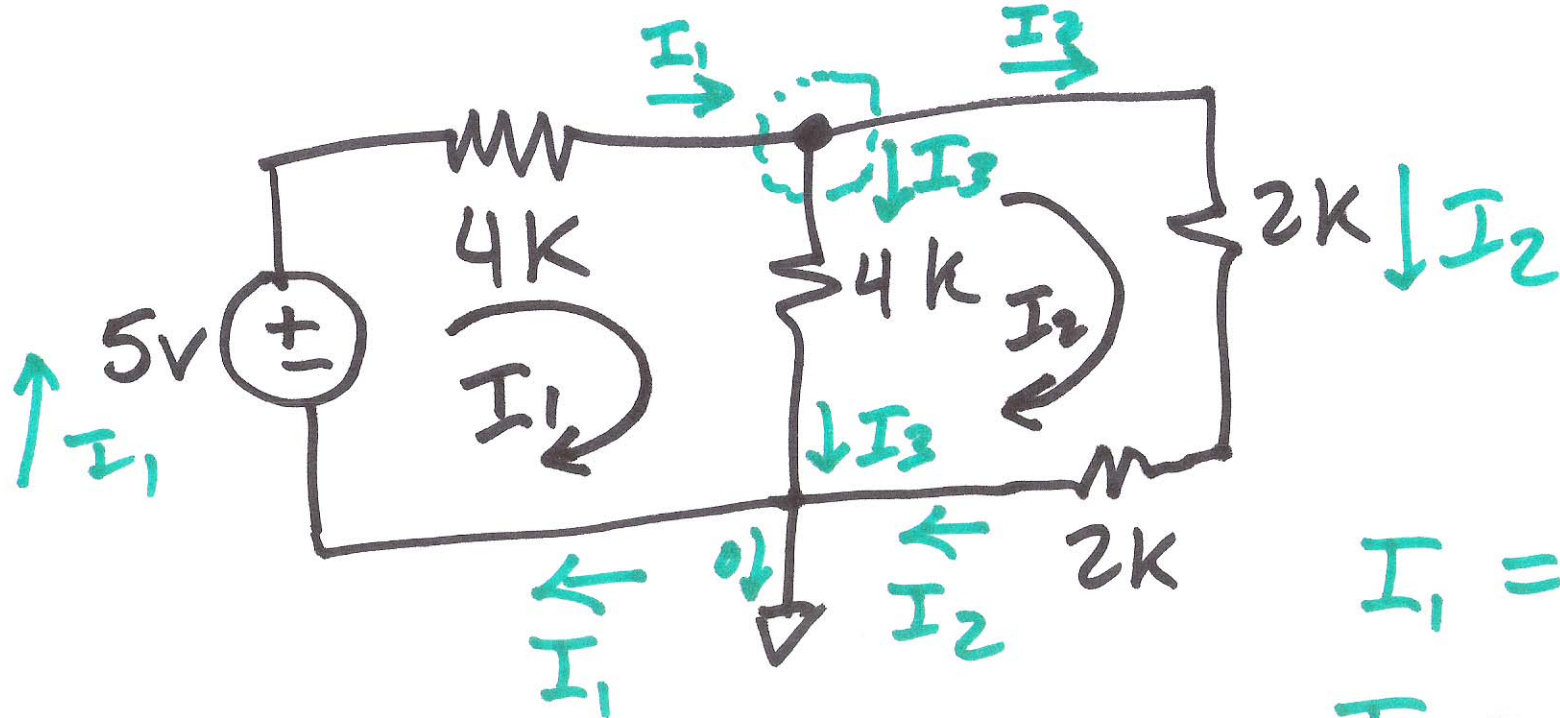

$$I_1 = I_2 + I_3$$

$$I_3 = I_1 - I_2$$

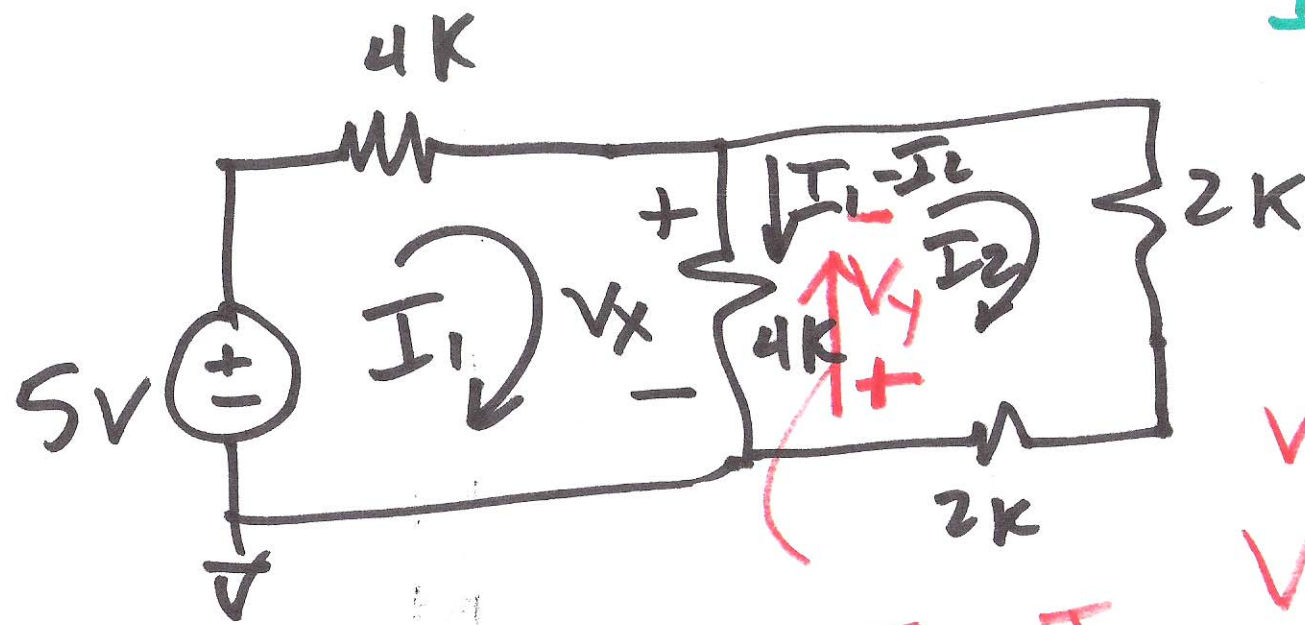


$$V_x = (I_1 - I_2) \cdot 4K$$

$$V_x = -V_y$$

$$V_y = (I_2 - I_1) \cdot 4K$$

$$I_2 - I_1$$

4)

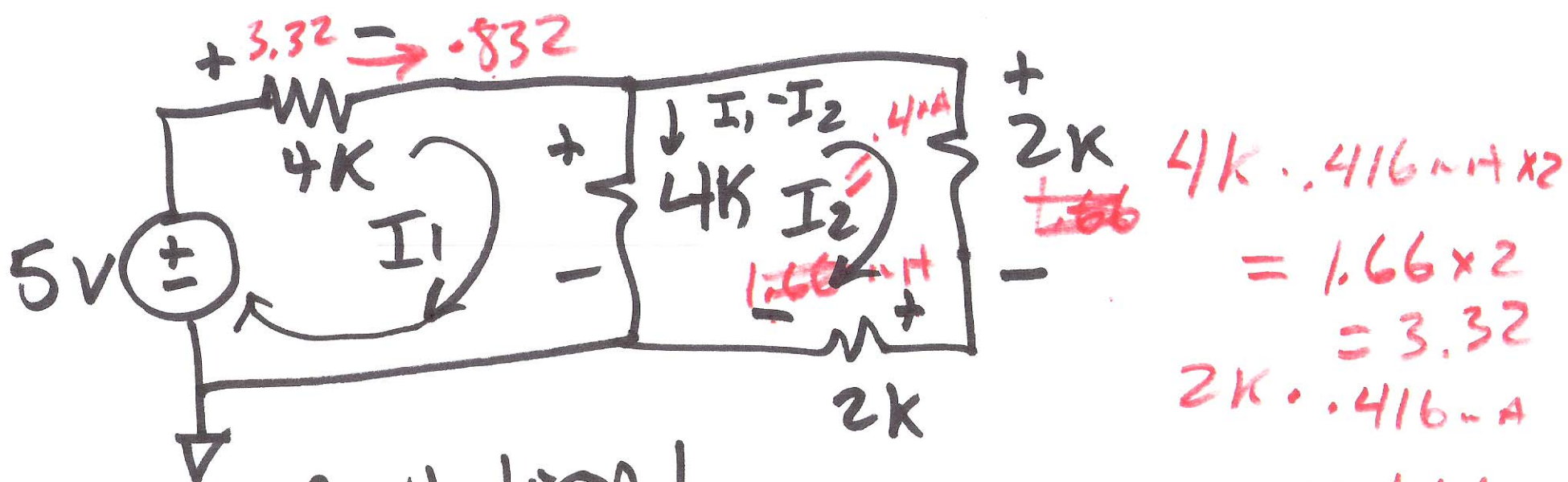

KVL around loop 1

$$5 = 4k \cdot I_1 + 4k(I_1 - I_2)$$

KVL around loop 2



$$4k(I_1 - I_2) = 2kI_2 + 2kI_2 = 4kI_2$$

$$I_1 = 2I_2 \Rightarrow I_1 = 0.832 \text{ A}$$

$$5 = 4k \cdot 2I_2 + 4k(2I_2 - I_2)$$

$$5 = 12k I_2 \Rightarrow I_2 = \frac{5}{12k} = 0.416 \text{ A}$$

5)

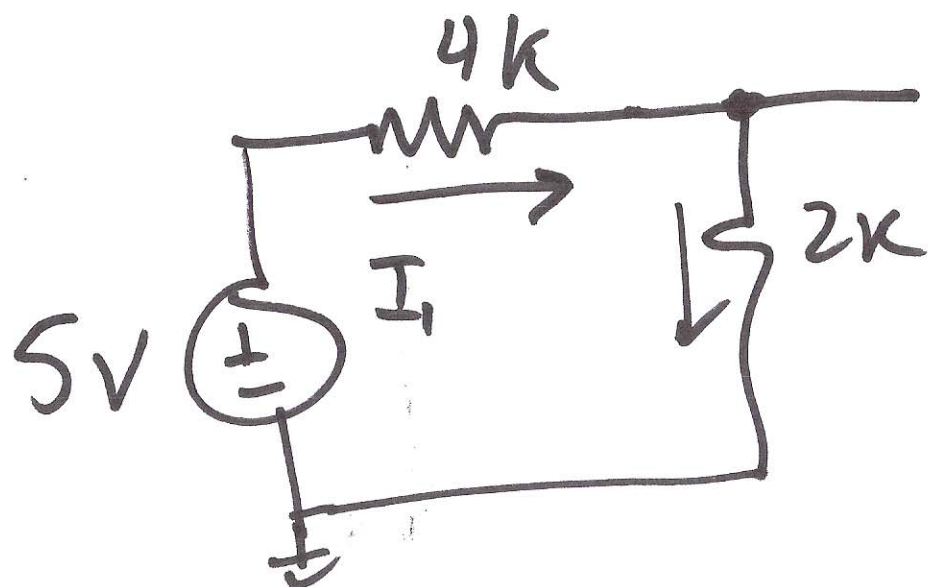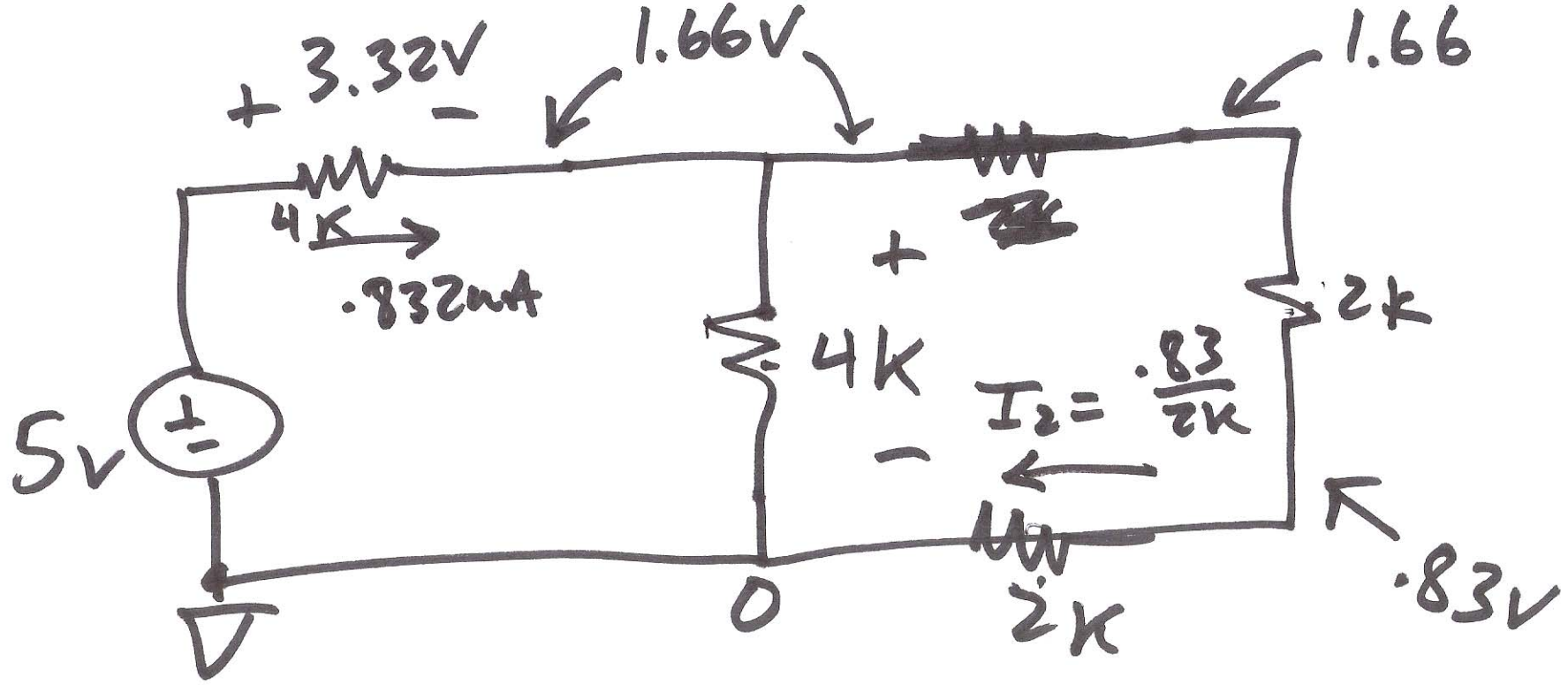


$$5 \cdot \frac{2k}{4k+2k} = \underline{\underline{1.66V}}$$

$$I_1 = \frac{5 - 1.66}{4k} = \underline{\underline{.833 \text{ mA}}}$$

$$I_2 = \underline{\underline{.416 \text{ mA}}}$$

6)

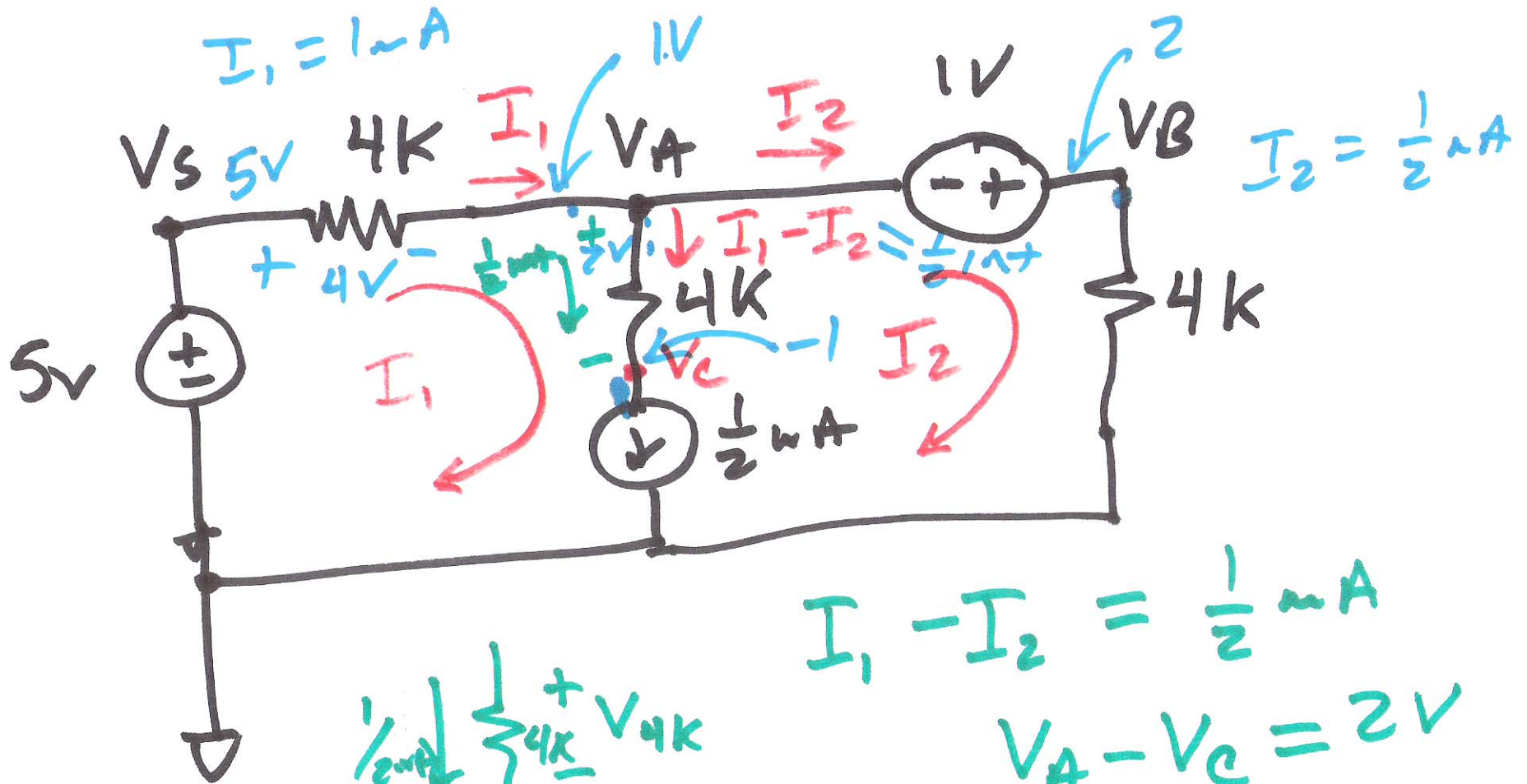


$$I_1 - I_2 = \frac{1}{2} \text{ mA}$$

$$V_A - V_C = 2 \text{ V}$$
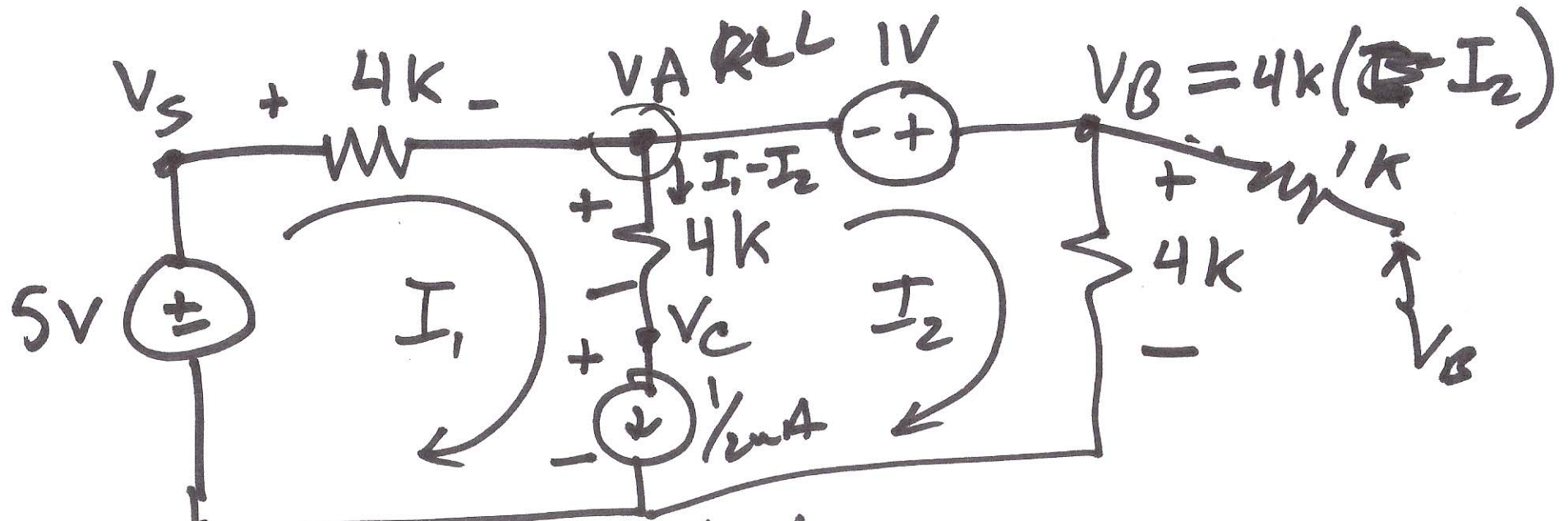
$$\frac{1}{2} \text{ mA} \downarrow \left\{ \begin{array}{l} + \\ - \end{array} \right. \begin{array}{l} V_{4K} \\ 4K \end{array} \\ = 4K \cdot \frac{1}{2} \text{ mA} \\ = \underline{\underline{2 \text{ V}}}$$





Mesh Analysis

$$5 = 4k \cdot I_1 + 4k(I_1 - I_2) + V_C$$

$$V_C + (I_1 - I_2)4k + 1 = 4k \cdot I_2$$

$$V_A - V_C = 4k \cdot (I_1 - I_2)$$

$$V_A = 4k \cdot I_2 - 1$$

$$4kI_2 - 1 - V_c = 4k(I_1 - I_2)$$

$$-V_c = 1 + 4k(I_1 - I_2) - 4kI_2$$

$$\boxed{-V_c = 1 + 4kI_1 - 8kI_2}$$

$$V_c = -1 - 4kI_1 + 8kI_2$$

$$5 = 4kI_1 + \cancel{4kI_1} - \cancel{4kI_2} - 1 - \cancel{4kI_1} + \cancel{8kI_2}$$

$$5 = 4k(I_1 + I_2) - 1$$

$$1.5 \text{ mA} = \frac{6}{4k} = I_1 + I_2$$

$$\boxed{I_1 = 1.5 \text{ mA} - I_2}$$

a)

$$V_c + \frac{1}{2} \mu A \cdot 4K + 1 = 4K I_2$$

$$-1 - 4K I_1 + 8K I_2 + 3 = 4K I_2$$

$$2 = 4K(I_1 - I_2)$$

$$I_1 - I_2 = \frac{1}{2} \mu A$$

$$I_1 + I_2 = 1.5 \mu A$$

$$\frac{1}{2} \mu A + I_2 + I_2 = 1.5 \mu A$$

$$I_2 = \frac{1 \mu A}{2} = \frac{1}{2} \mu A$$

$$I_1 = 1 \mu A$$