

EE 220 D

6/23/14

$\downarrow \rightarrow R$ (resistance)

LPC. 7D


Capacitor $\frac{1}{\downarrow} \frac{1}{j2\pi fC} = \frac{1}{j\omega C} = \frac{1}{sC} \Rightarrow \text{impedance}$

$$v(f) = i(f) \cdot \frac{1}{j\omega C} \quad \left\{ s = j\omega \right.$$

inductor $\downarrow \frac{1}{sL} \Rightarrow j\omega L = j2\pi f \cdot L = sL$

$$v = i \cdot j\omega L$$

$$v = I \cdot \text{imp.}$$

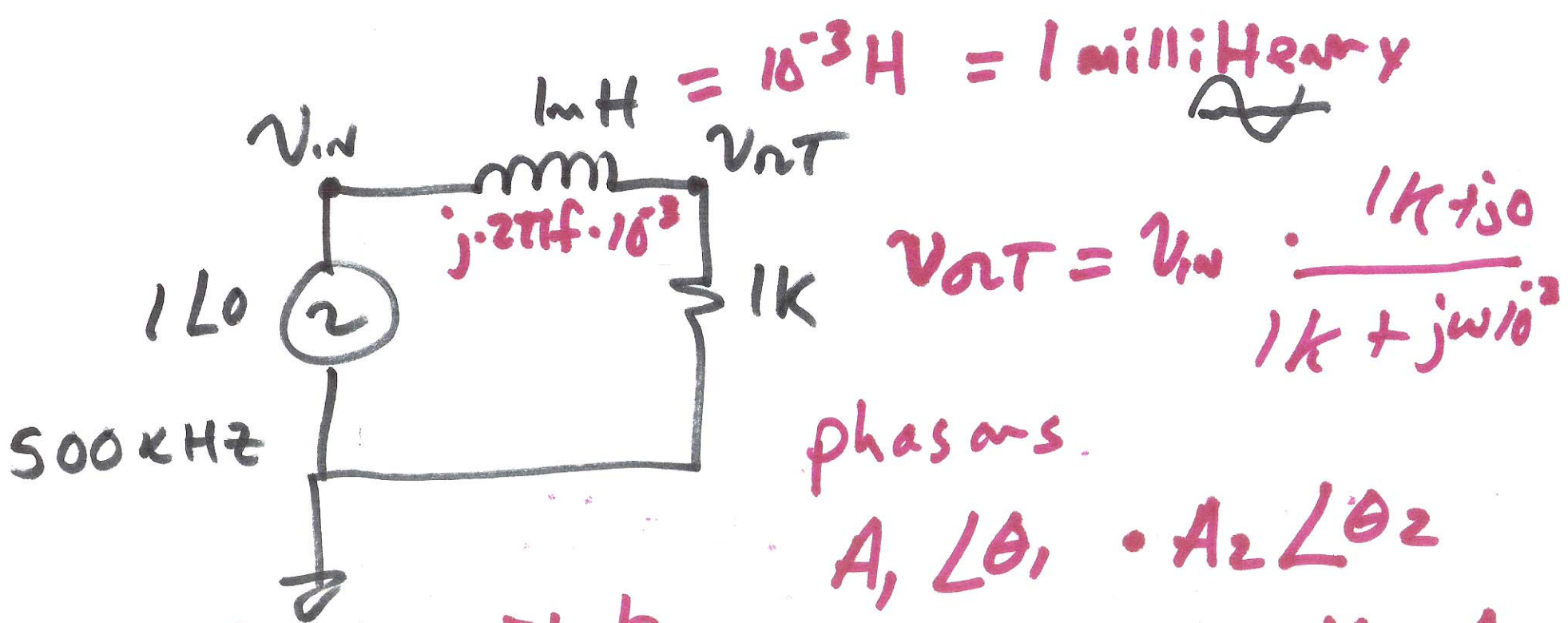

$$v_{out} = v_{in} \cdot \frac{1 \text{ k} + j0}{1 \text{ k} + j\omega 10^{-3}}$$

phasors.

$$A_1 \angle \theta_1 \cdot A_2 \angle \theta_2$$

$$A_1 A_2 \angle \theta_1 + \theta_2$$

$$\frac{A_1 \angle \theta_1}{A_2 \angle \theta_2} = \frac{A_1}{A_2} \angle \theta_1 - \theta_2$$

$$\frac{x + jy}{a + jb} = \frac{\sqrt{x^2 + y^2} \angle \tan^{-1} \frac{y}{x}}{\sqrt{a^2 + b^2} \angle \tan^{-1} \frac{b}{a}}$$

$$\angle \frac{1 + j0}{a + jb} = \tan^{-1} \frac{b}{a}$$

$$\frac{1 \angle 0}{\sqrt{a^2 + b^2} \angle \tan^{-1} \frac{b}{a}} = \frac{1}{\sqrt{a^2 + b^2}} \angle -\tan^{-1} \frac{b}{a}$$

$$\angle -\tan^{-1} \frac{b}{a}$$

$$2) A_1 \cos \theta_1 + A_2 \cos \theta_2 \leftarrow A_1 \angle \theta_1 + A_2 \angle \theta_2 \rightarrow A_1 \sin \theta_1 + A_2 \sin \theta_2$$

$$V_{out} = \frac{1 \angle 0 \cdot 1k \angle 0}{\sqrt{(1k)^2 + 0^2}}$$

$$\sqrt{(1k)^2 + 0^2}$$

$$= \tan^{-1} \frac{0}{1k} = 0$$

$$V_{out} = \frac{1 \angle 0}{1 + j2\pi \cdot 500k \cdot 10^{-6}} \sqrt{(1k)^2 + (2\pi \cdot 500k \cdot 10^{-6})^2}$$

$$.5 \times 10^6 \times 10^{-6} = \frac{1}{2}$$

$$V_{out} = \frac{1 \angle 0 \cdot 1 \angle 0}{\sqrt{1^2 + (3.14)^2}} \angle \tan^{-1} \frac{3.14}{1} = \frac{1 \angle 0}{3.3 \angle 72^\circ}$$

$$T = \frac{1}{500k} = 2\mu$$


$$V_{out} = 300mV \angle -72^\circ \quad 0.445$$

$$t_d = 14.445$$

$$72 = 360 - \frac{t_d}{T} \rightarrow 24$$

CMOSedu.com

3)

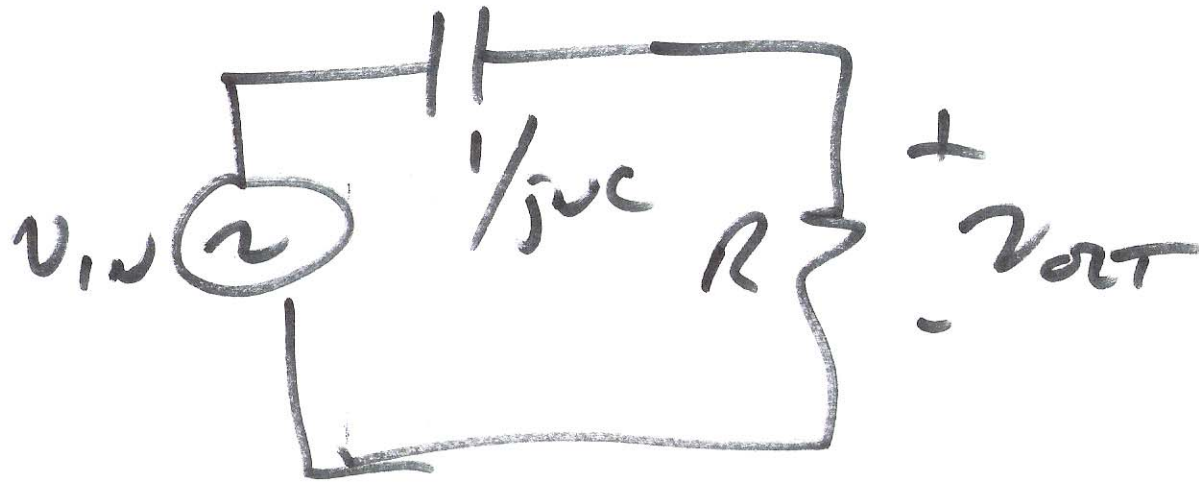

$$v_{out} = v_{in} \frac{R}{R + \frac{1}{j\omega C}}$$

$$v_{out} = v_{in} \frac{0 + j\omega RC}{1 + j\omega RC}$$