


Lecture 7

EE 220

6/17/2014

Quiz 5 work ch. 3 problems

find V_x

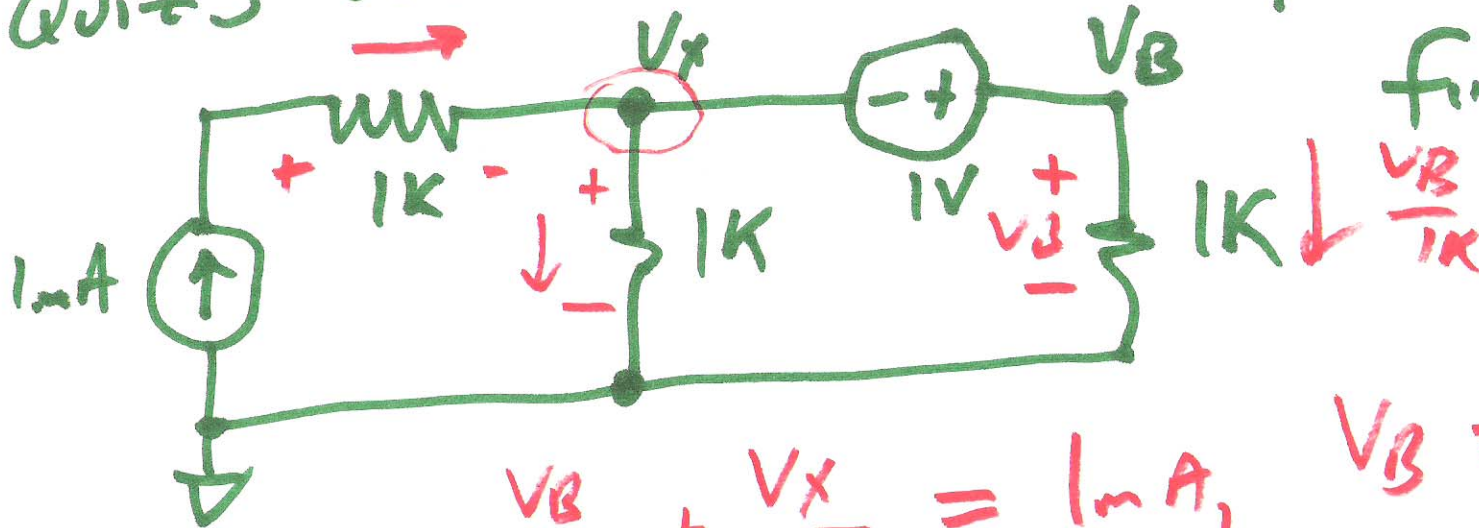


$$\frac{V_B}{1k} + \frac{V_x}{1k} = 1mA, \quad V_B = V_x + 1$$
$$\frac{V_x + 1 + V_x}{1k} = 1mA$$

$$2V_x + 1 = 1, \quad \boxed{V_x = 0}$$

1)

5.)

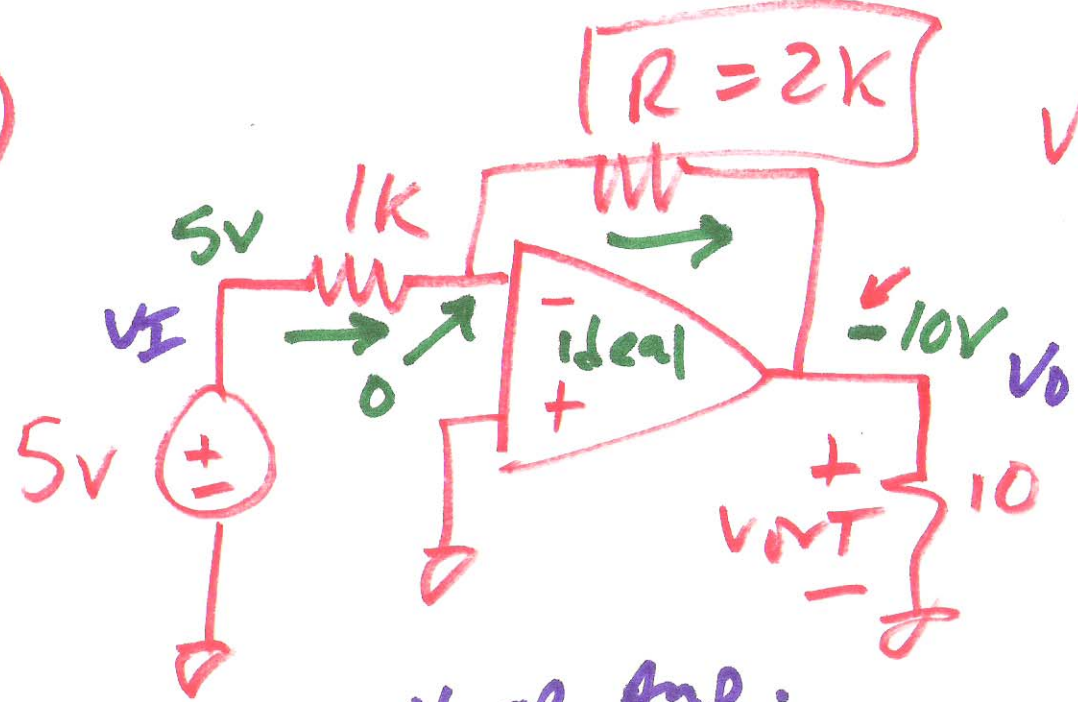

Value of R
 So power diss.
 by 10Ω is
 10 watts

$$P = \frac{V_{R_T}^2}{R} = 10$$



Gain = $\frac{V_o}{V_i} = \text{Voltage Amp.}$

$$\frac{5}{1k} = \frac{0 - (-10)}{R} = \frac{0 - (-10)}{R} \quad V_{R_T} = \sqrt{100} = 10V$$

R = Negative wrong!

$$R = \frac{10k}{5} = \underline{\underline{2k}}$$

2)

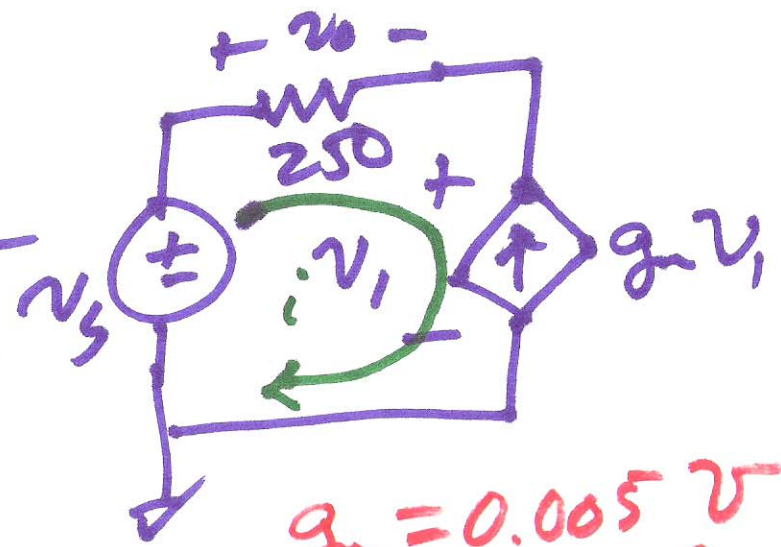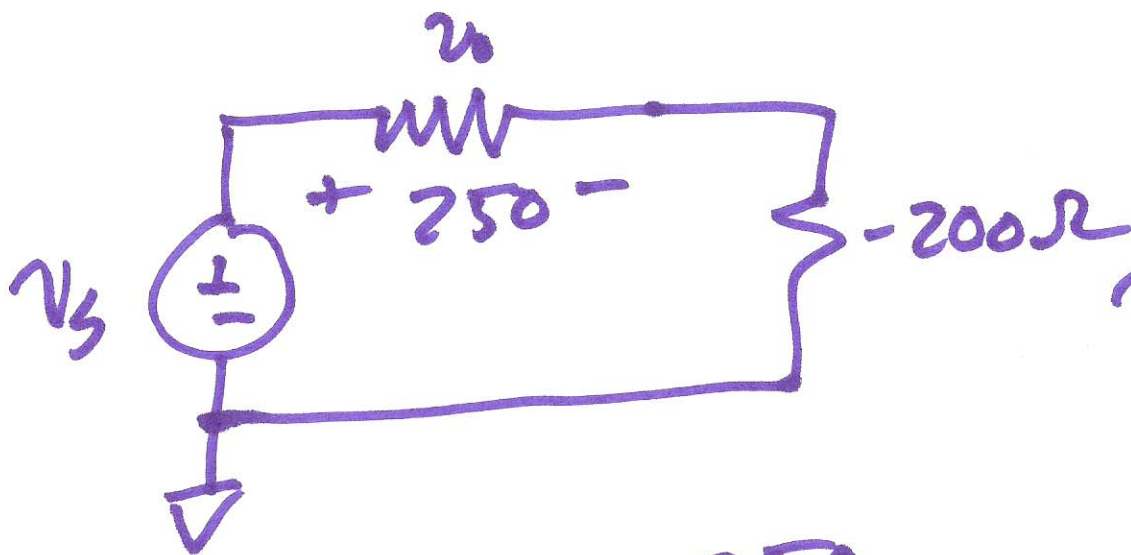

$$v_o = v_s \cdot \frac{250}{250 - 200}$$

$$\boxed{\frac{v_o}{v_s} = 5}$$

$$g_m = 0.005\ \text{V}^{-1}$$

OHM
SIMPSONS

$\frac{1}{R} = \text{conductance}$

$$1.25 = \frac{5}{4}$$

$$v_s = v_o + v_1$$


$$v_o = 250i = -g_m v_1 \cdot 250$$

$$v_1 = \frac{v_o}{-g_m \cdot 250} = \frac{v_o}{-0.005 \cdot 250} = \frac{v_o}{-1.25}$$

$$\frac{v_o}{v_s} = 1 + \frac{-4}{5} = \frac{1}{5}$$

$$\boxed{\frac{v_o}{v_s} = 5}$$



6)

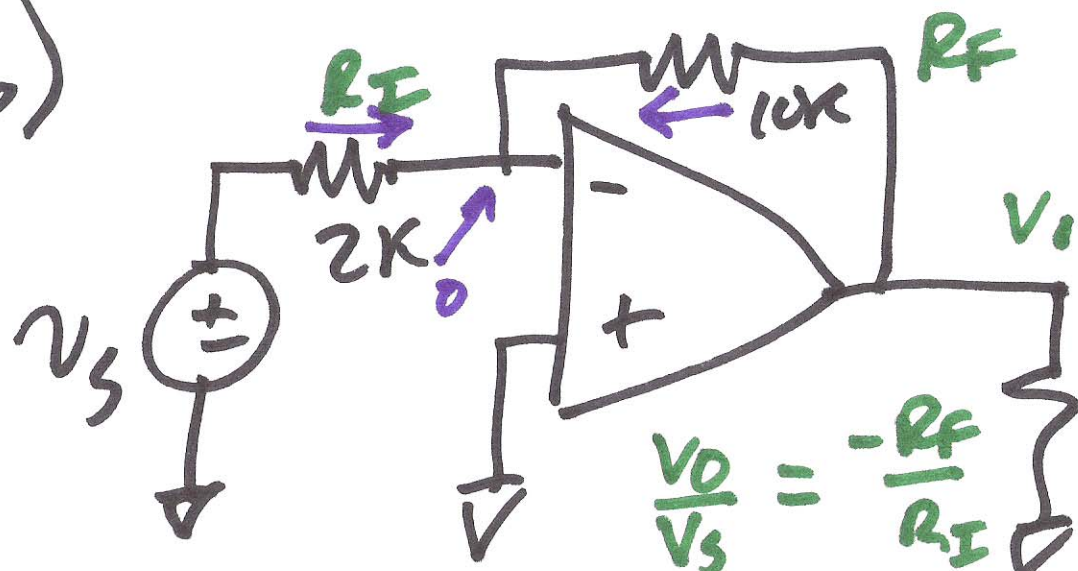

$$\frac{V_o}{V_s} = -\frac{R_F}{R_I}$$

Plot V_o vs. V_s

$$-5 \leq V_s \leq 5$$

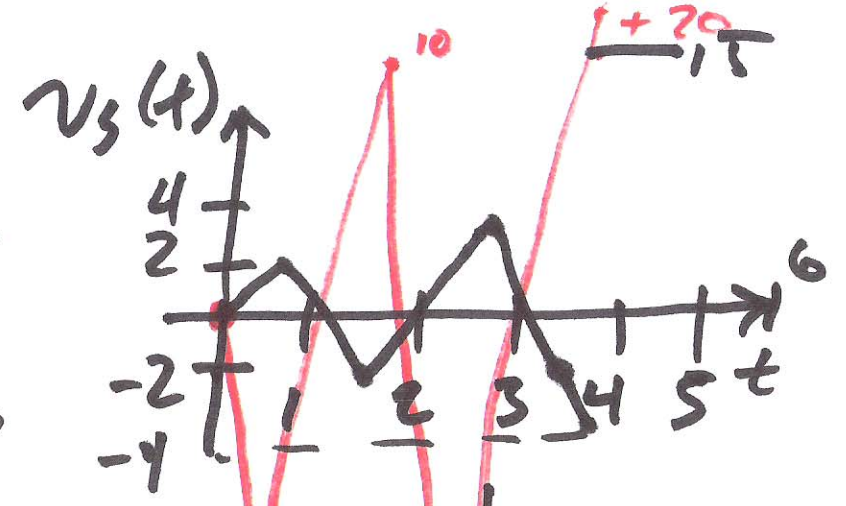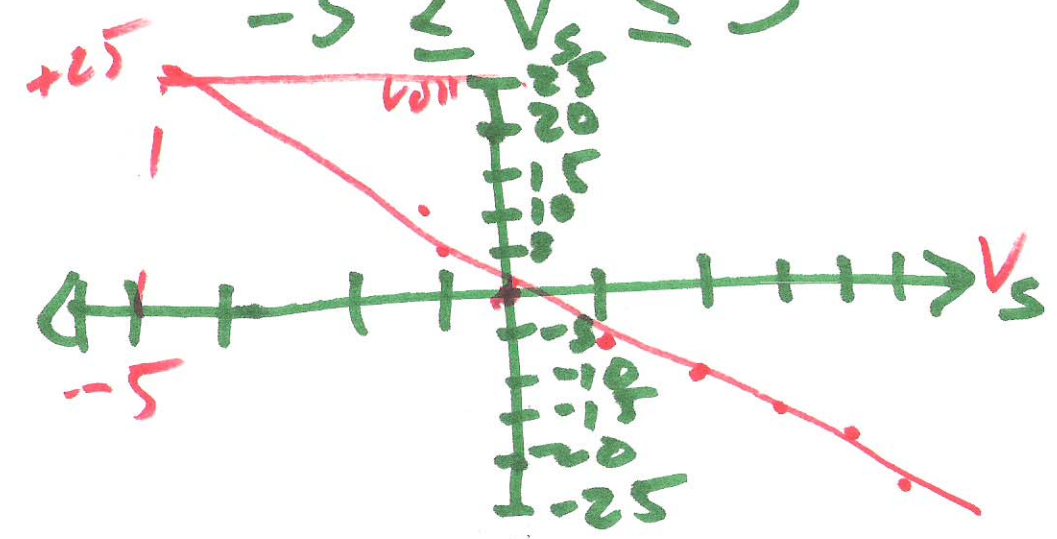


$$V_o = -5 \cdot V_s$$

$$\frac{v_s}{2k} + \frac{v_o}{10k} = 0$$

$$v_o = -5 \cdot v_s$$

4)

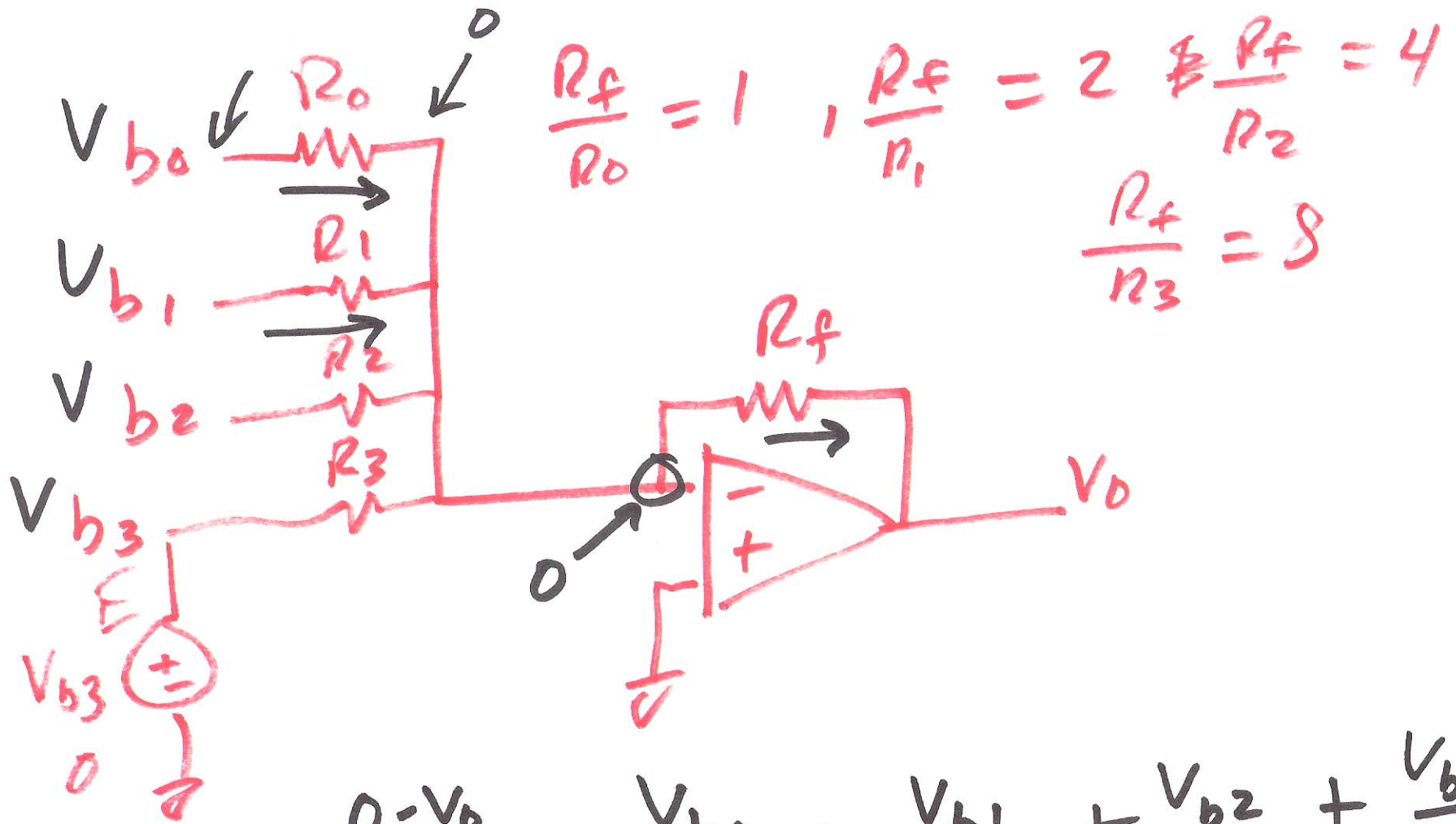


$$\frac{0 - V_o}{R_f} = \frac{V_{b0}}{R_0} + \frac{V_{b1}}{R_1} + \frac{V_{b2}}{R_2} + \frac{V_{b3}}{R_3}$$

$$-V_o = V_{b0} + 2V_{b1} + 4V_{b2} + 8V_{b3}$$

a) E 0 0 E
 $-V_o = 9E$

5
a)

14)

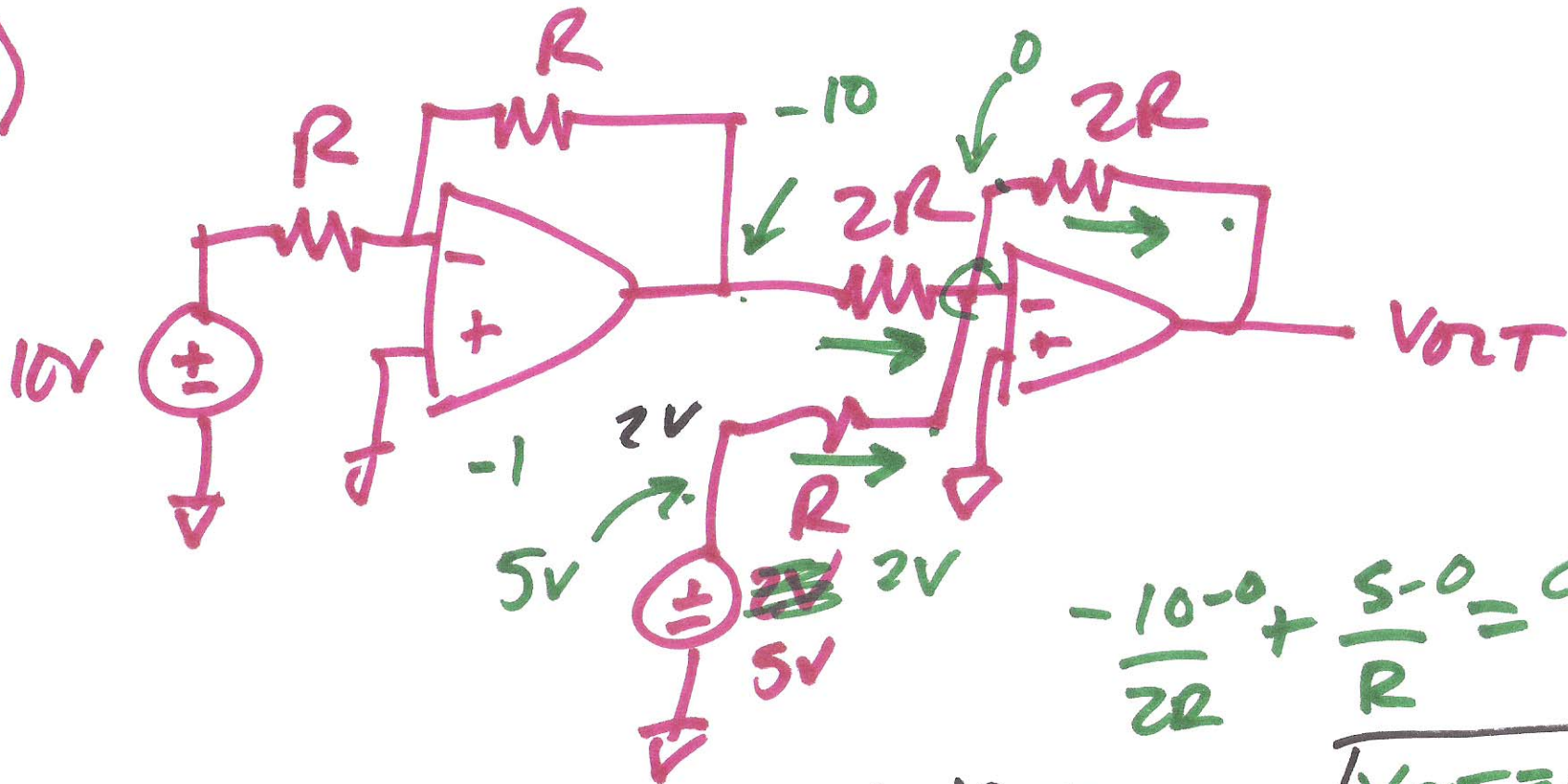

$$\frac{-10-0}{2R} + \frac{2-0}{R} = \frac{0-V_{out}}{2R}$$

$$-5 + 2 = -V_{out}/2$$


$$\boxed{V_{out} = 6V}$$

$$\frac{-10-0}{2R} + \frac{5-0}{R} = \frac{0-V_{out}}{2R}$$

$$\boxed{V_{out} = 0}$$

NON - INVERTING

GAIN! (GAIN is positive)

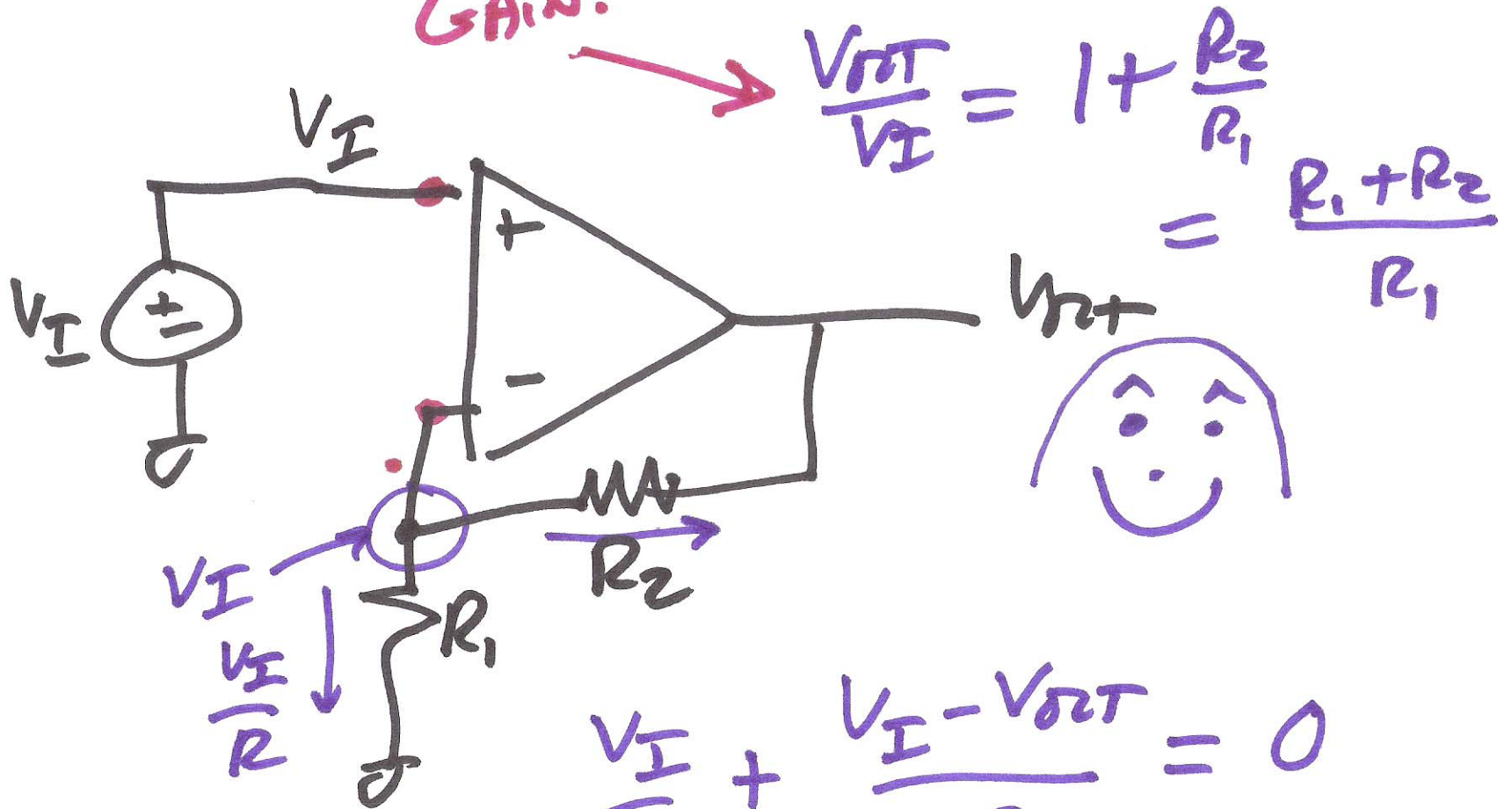


$$\frac{V_I}{R_1} + \frac{V_I - V_{OUT}}{R_2} = 0$$

$$V_I \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = R_2 \cdot V_{OUT}$$

$$V_{OUT} = V_I \left(\frac{R_2}{R_1} + 1 \right)$$

77

Inverting (gain is negative)

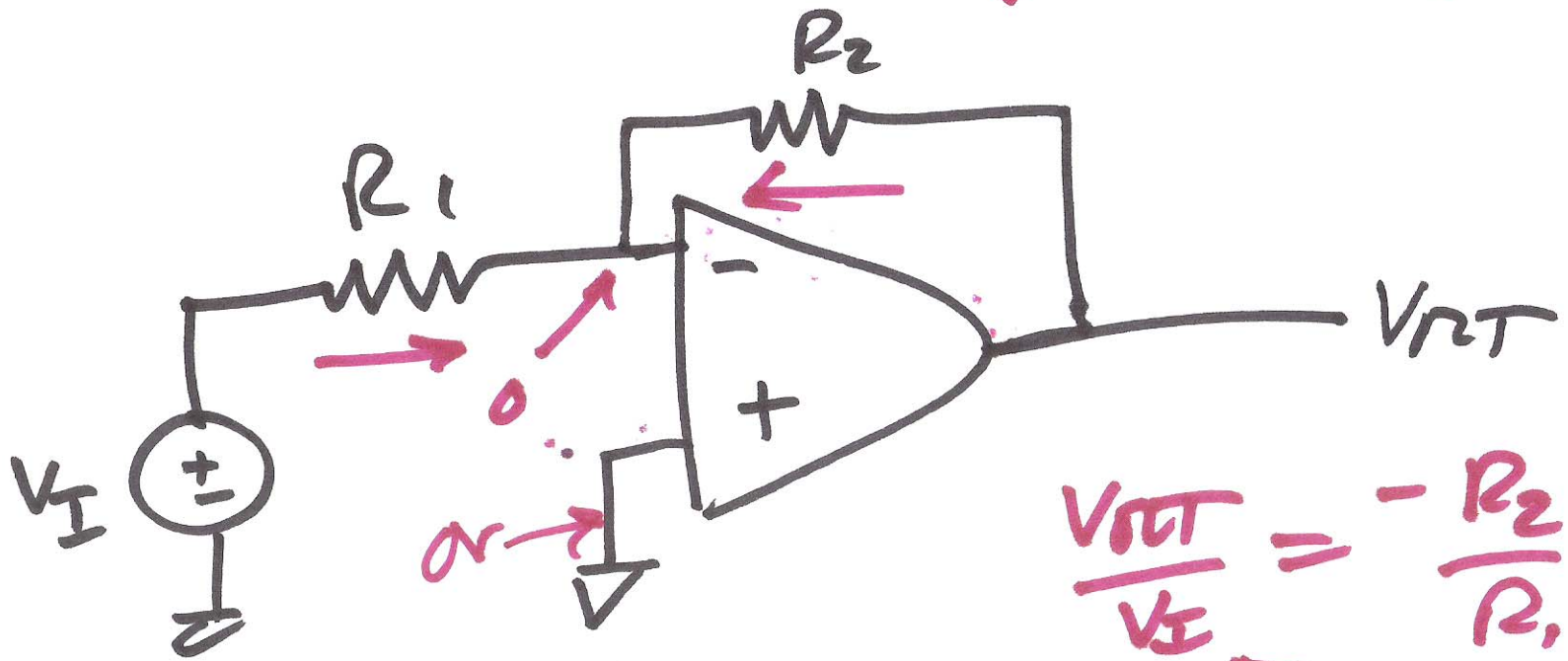


$$\frac{V_{OUT}}{V_I} = -\frac{R_2}{R_1}$$

gain!

$$\frac{V_I}{R_1} + \frac{V_{OUT}}{R_2} = 0$$
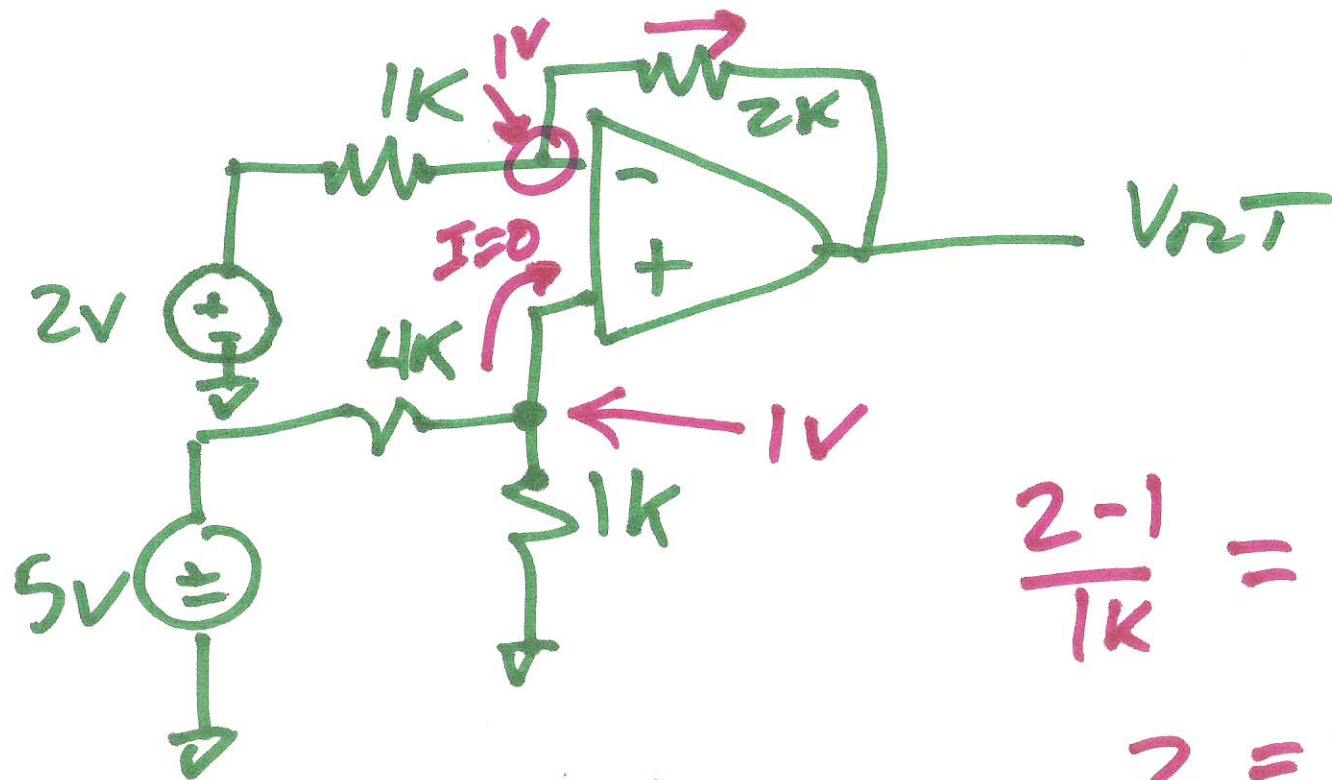
$$\frac{V_I}{R_1} = -\frac{V_{OUT}}{R_2}$$



$$5 \cdot \frac{1k}{1k+4k} = 1V$$

Superposition

$$\frac{2-1}{1k} = \frac{1-V_{out}}{2k}$$

$$2 = 1 - V_{out}$$

$$\underline{V_{out} = -1V}$$

$$V_{out} = -2 \cdot \frac{2k}{1k} +$$



$$1V \cdot \left(1 + \frac{2k}{1k}\right)$$

$$= -4 + 3 = -1V$$

9)


Superposition

look at 2V source
short out 5V

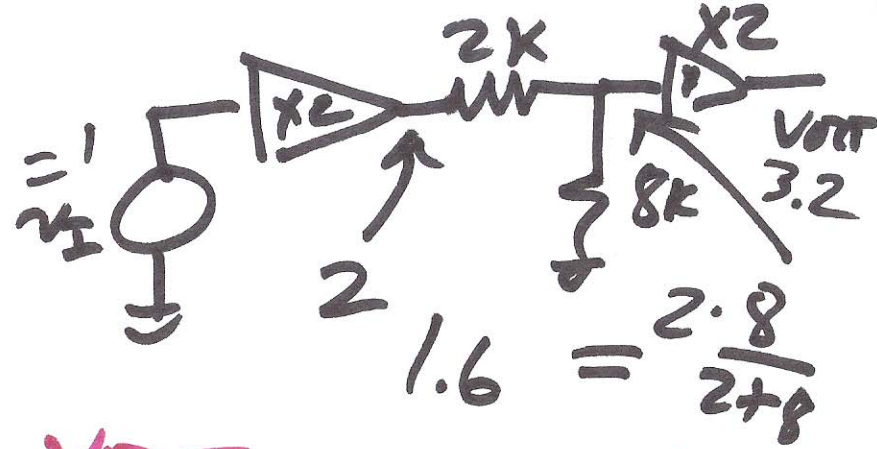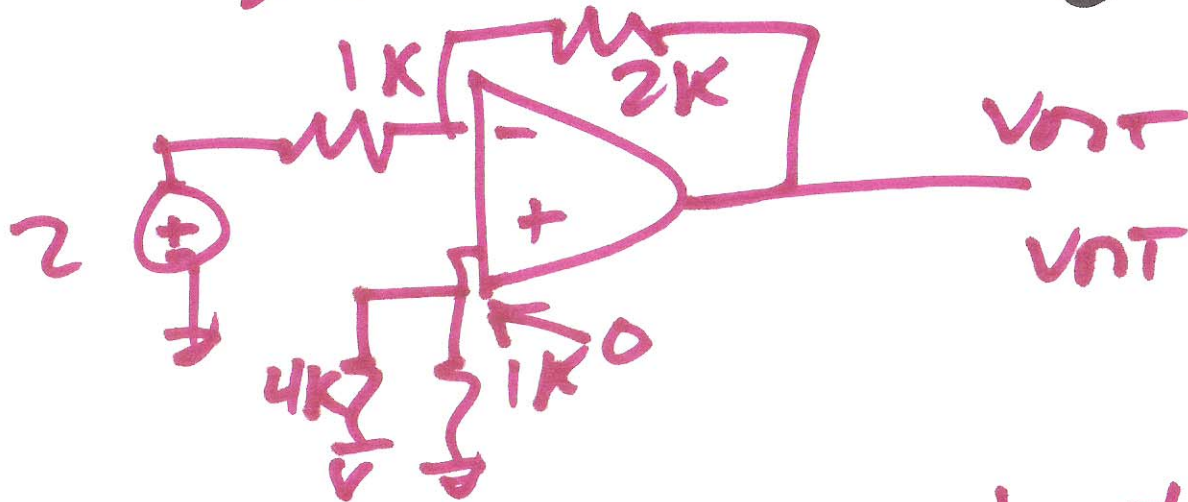


$$V_{out} = 2 \cdot \left(-\frac{2k}{1k} \right) = -4$$

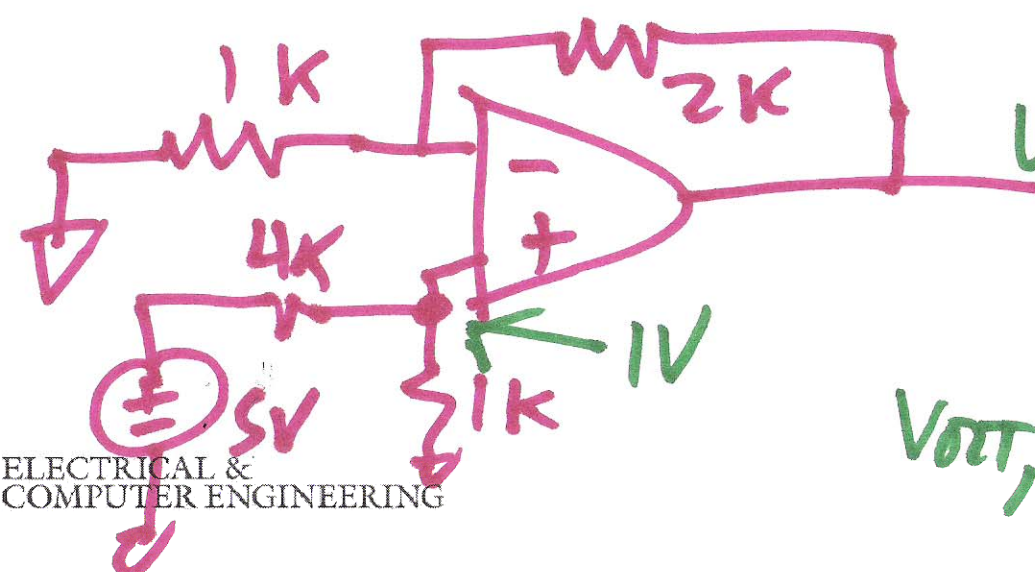look at 5V source, short out the 2V source



$$V_{out} = 1 \left(1 + \frac{2k}{1k} \right) = 3$$
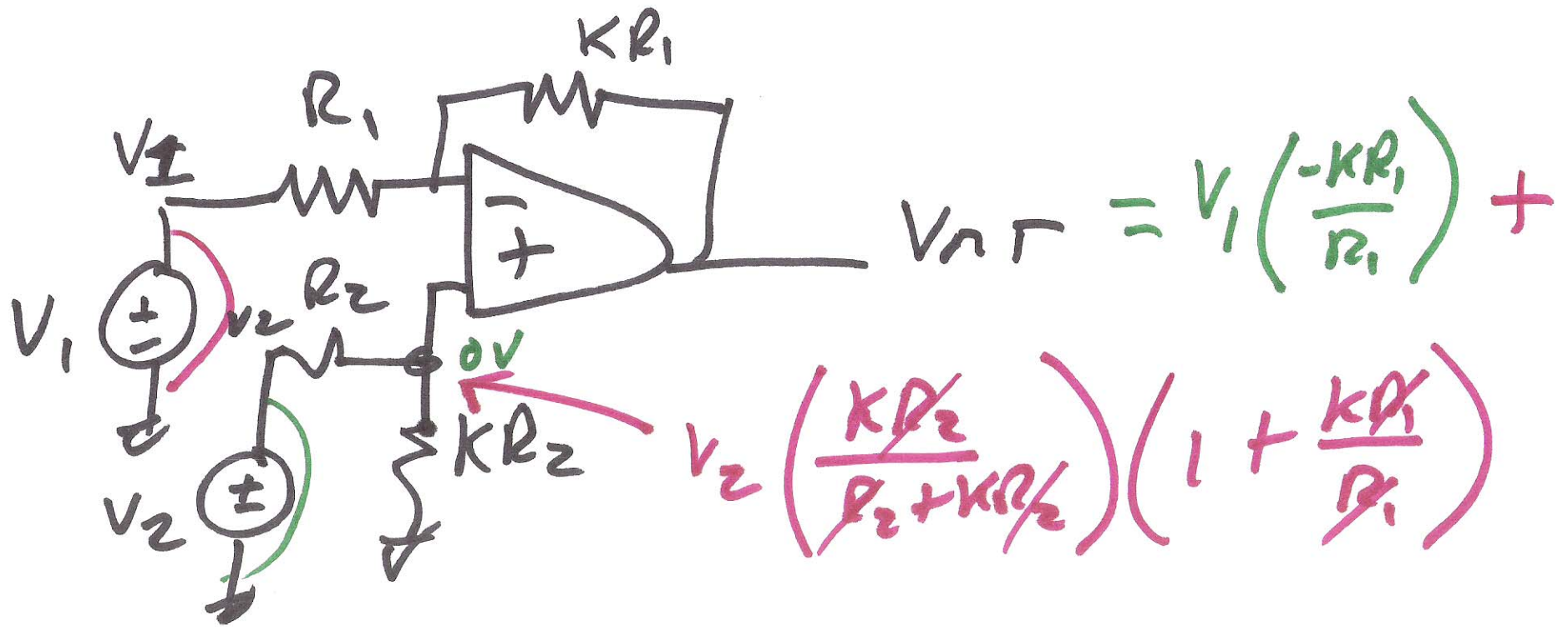
$$V_{out,T} = -4 + 3 = \underline{\underline{-1V}}$$



$$= -KV_1 + V_2 \frac{K}{1+K} \cdot \frac{1+K}{1}$$

$$V_{out} = -KV_1 + KV_2$$

$$= K(V_2 - V_1)$$

117