



EE 221 Circuits II

Lecture 10

Feb. 27, 2019

$$Z_C = \frac{1}{j \cdot 2\pi \cdot C \cdot f}$$


$$= j(-132.7)$$

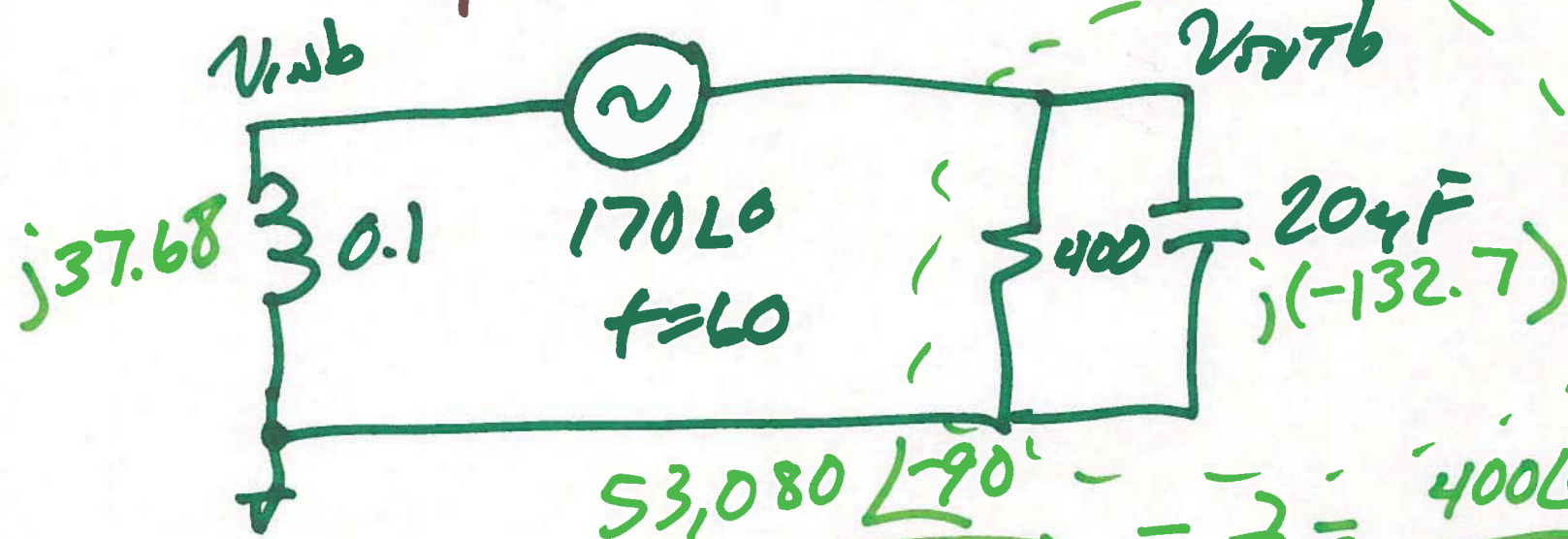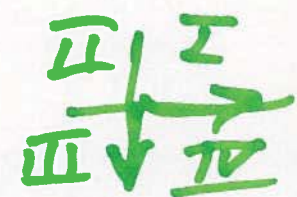

$$\frac{53,080 \angle -90^\circ}{421 \angle -18.35^\circ} = Z = \frac{400 \angle 0^\circ \cdot 132.7 \angle -90^\circ}{400 + j(-132.7)}$$

$$Z = 126 \angle -71.65^\circ$$

1)

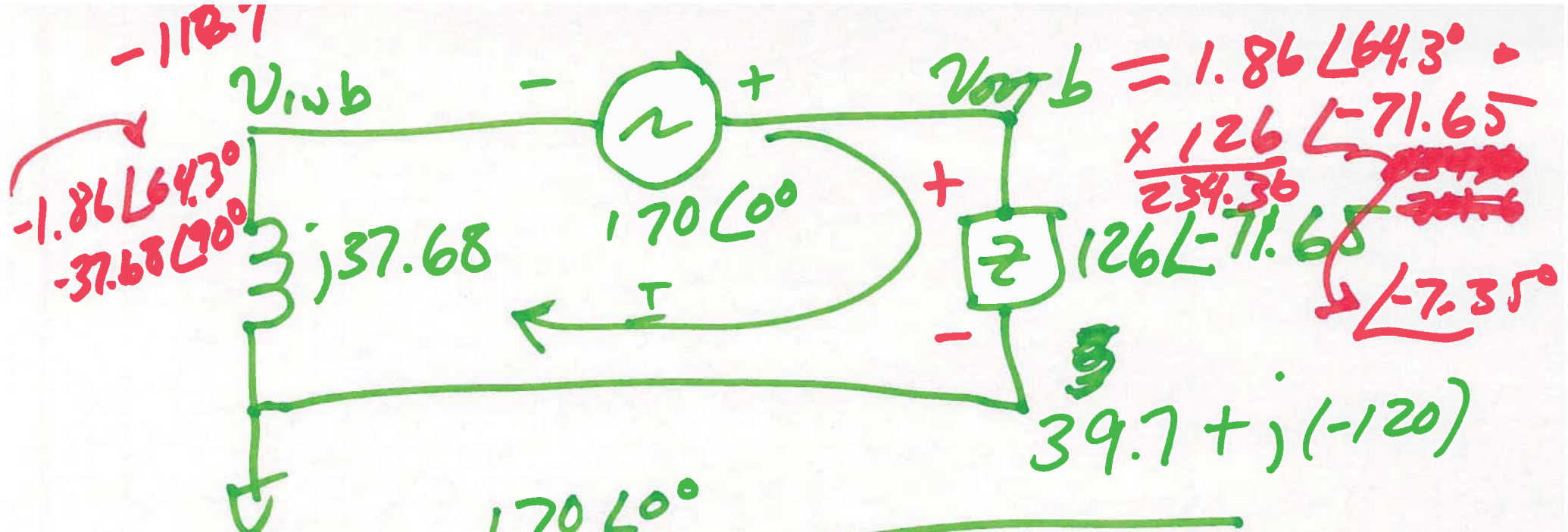


$$\vec{I} = \frac{170 \angle 0^\circ}{j37.68 + 39.7 + j(-120)}$$


$$= \frac{170 \angle 0^\circ}{39.7 + j(-82.32)} = \frac{170 \angle 0^\circ}{91.4 \angle -64.3^\circ}$$

$$|\vec{I}| = 1.86 \angle 64.3^\circ$$

2)

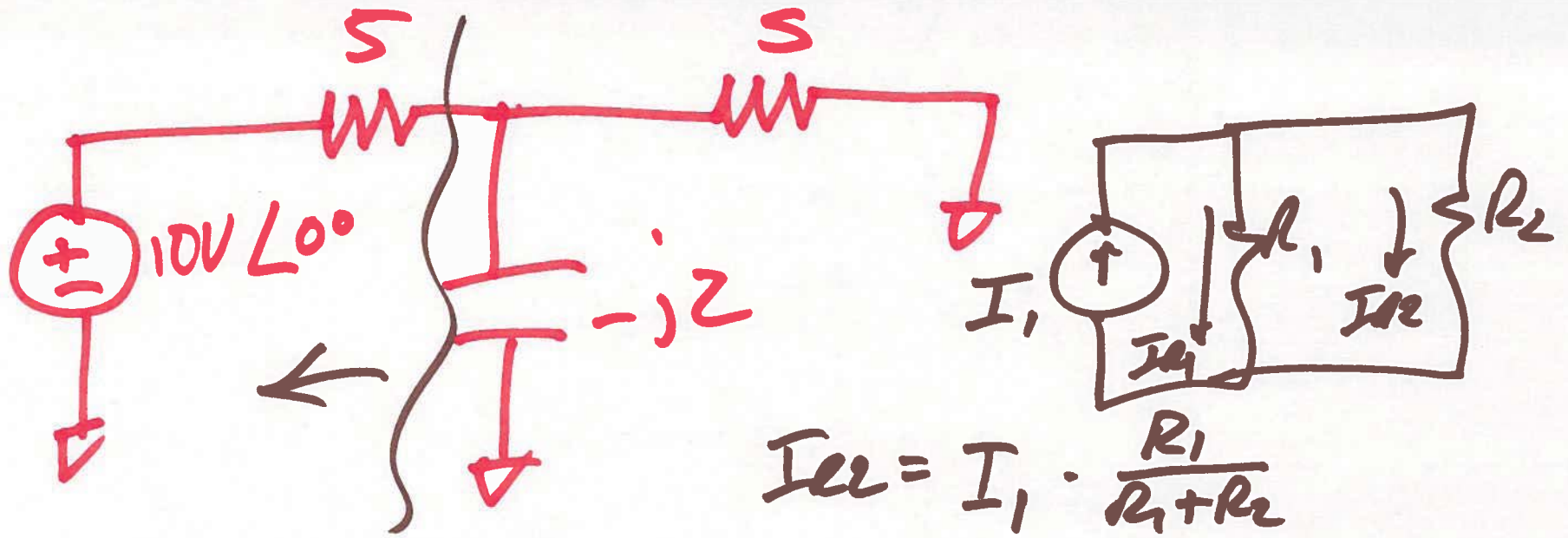

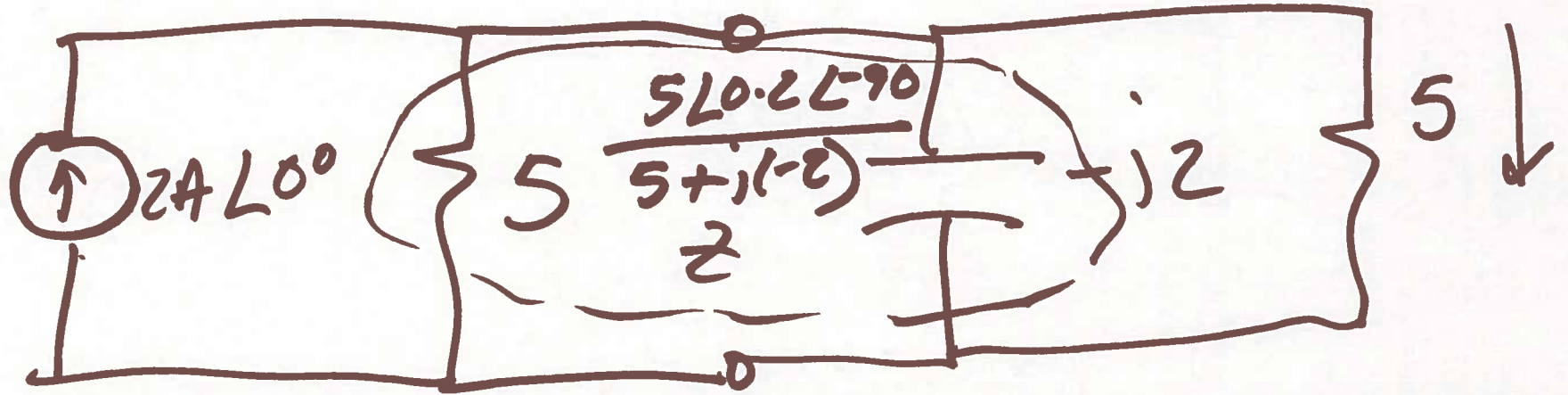
$$I_{R2} = I_1 \cdot \frac{R_1}{R_1 + R_2}$$



$$I = 2A \angle 0^\circ \cdot \frac{2}{2 + 5}$$

3)


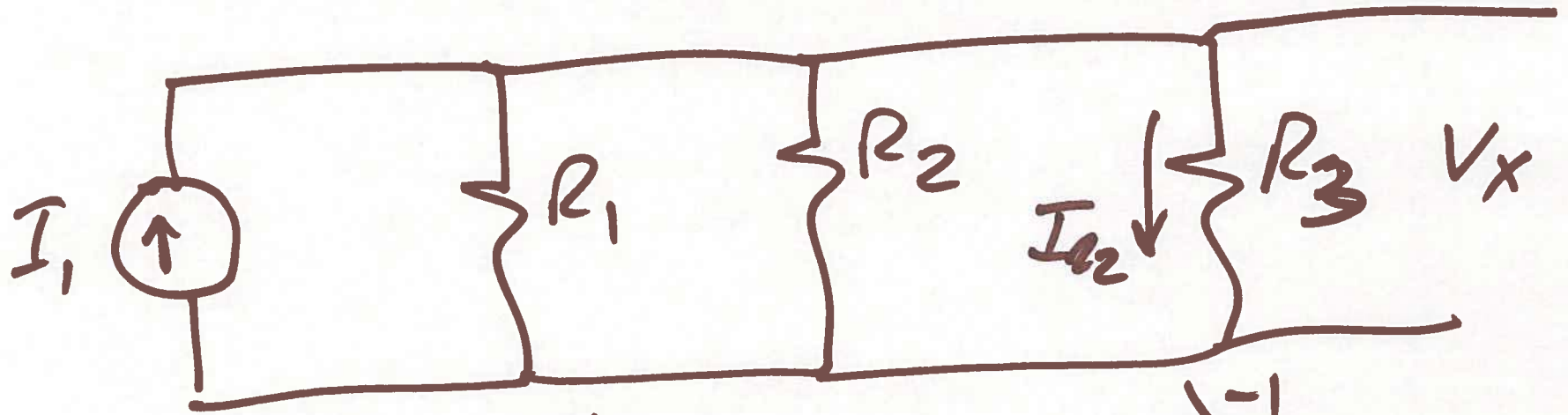


$$V_x = I_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$

$$I_1 = \frac{V_x}{R_1} + \frac{V_x}{R_2} + \frac{V_x}{R_3}$$

$$I_{R2} = \frac{R_1 + R_2}{R_1 + R_2 + R_3} \cdot I_1 \quad ?$$




NO!

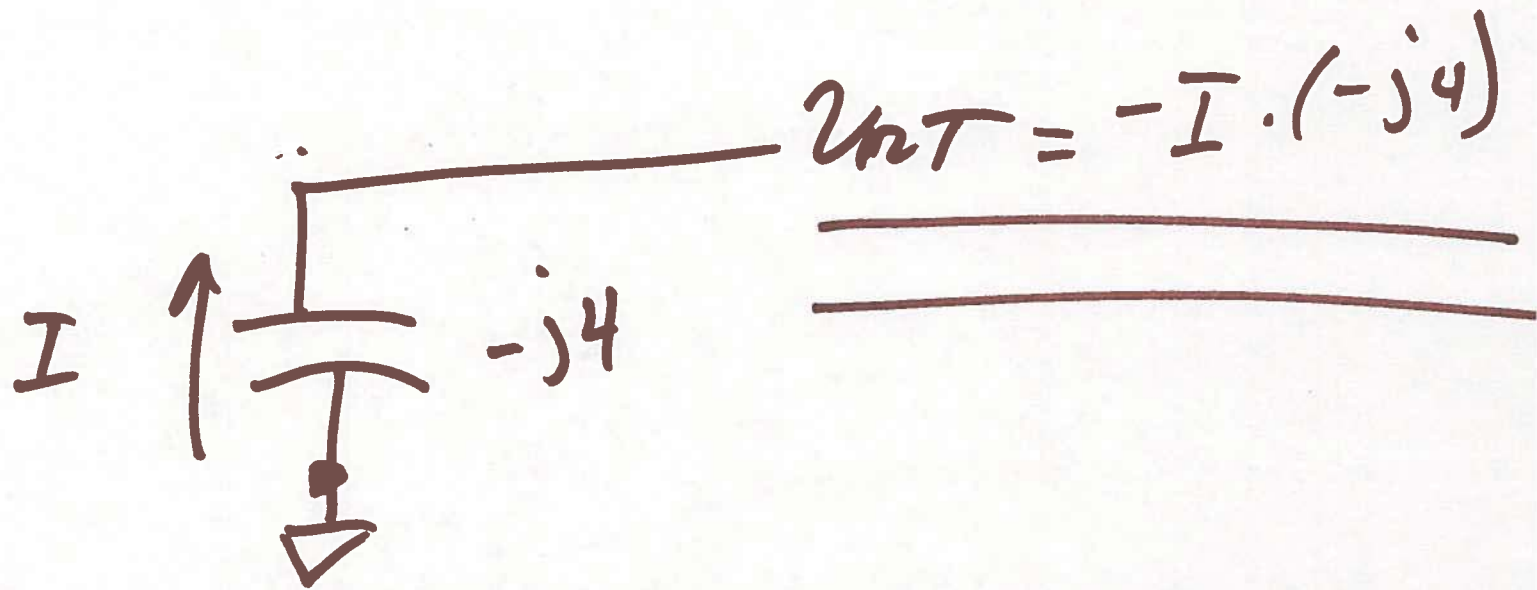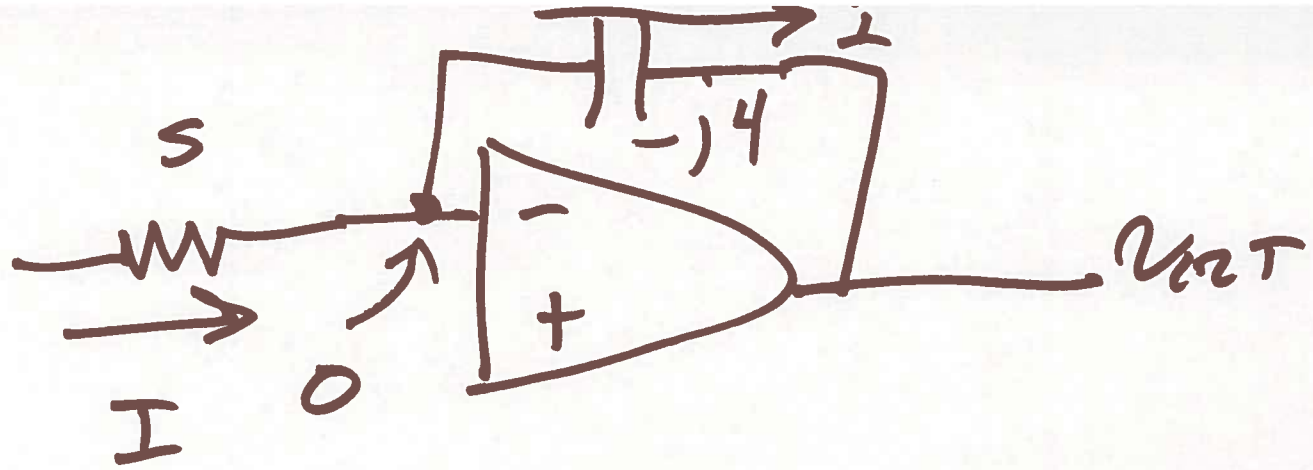

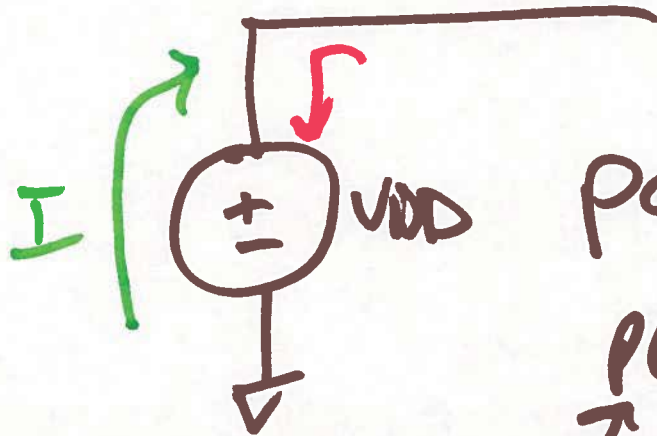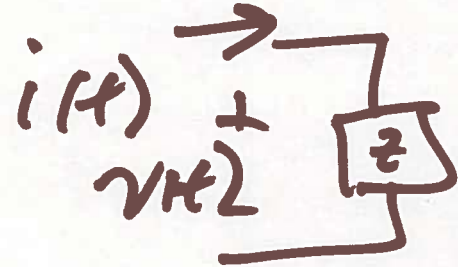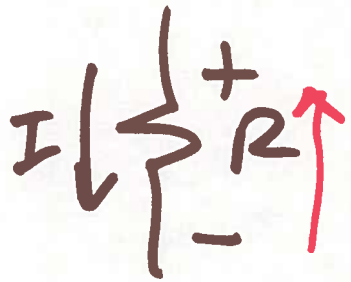5.4)

Ch. 8 of Book
Average (periodic)

$$X_{AVG} = \frac{1}{T} \int_0^T x(t) \cdot dt$$




power supplied

$$P(t) = v(t) \cdot i(t) = VDD \cdot i(t)$$

instantaneous power

b)

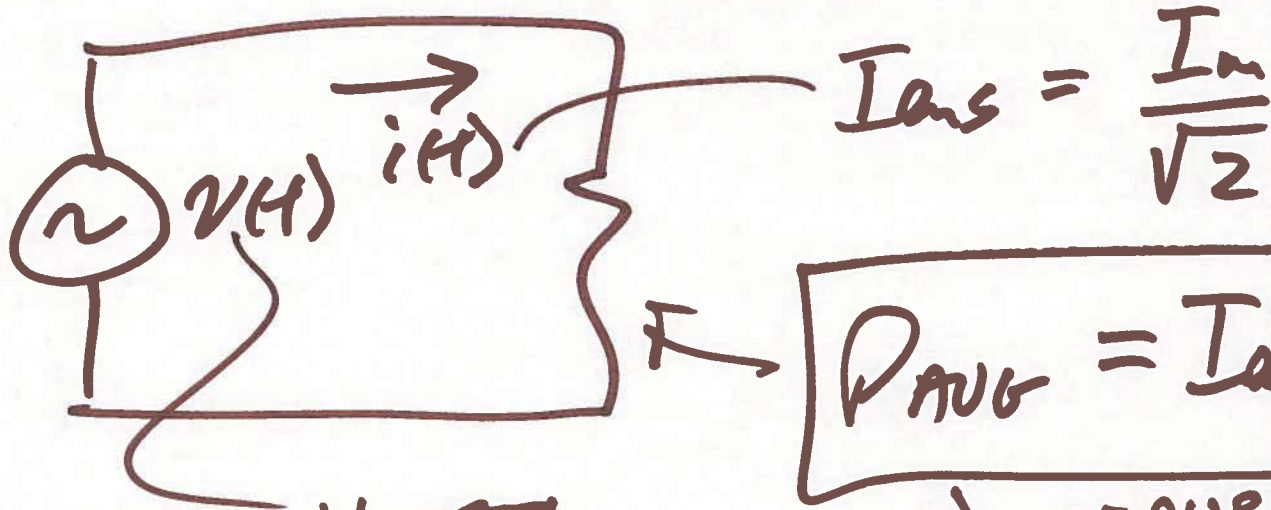

$$P_{avg} = I_{avg} \cdot V_{avg}$$

TRUE ONLY when
Resistive

$$V_m \cos(\omega t + \phi_v)$$


$$R_{avg} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

Magnitude
VP

$$V_{avg} = \frac{V_m}{\sqrt{2}}$$

$$v(t) = V_m \cos(\omega t + \phi_v)$$

$$i(t) = I_m \cos(\omega t + \phi_i)$$

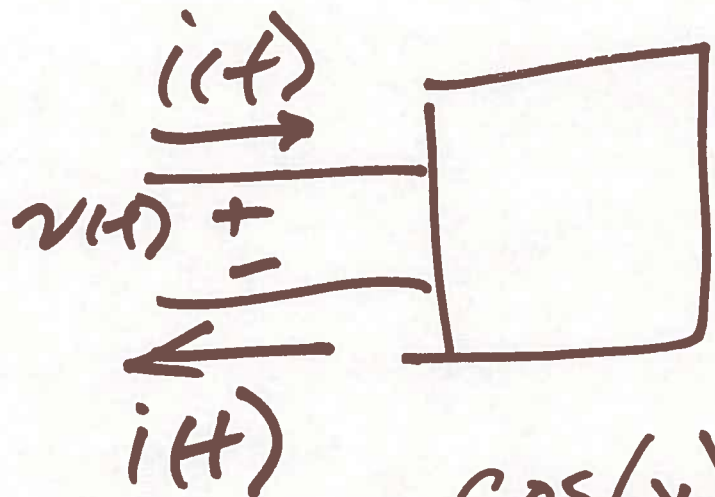

$$p(t) = v(t) \cdot i(t)$$

$$= V_m I_m \cos(\omega t + \phi_v) \cdot \cos(\omega t + \phi_i)$$

$$\cos(x) \cdot \cos(y) = \frac{1}{2} [\cos(x-y) + \frac{1}{2} \cos(x+y)]$$

instantaneous
power

$$p(t) = \frac{V_m I_m}{2} \left[\cos(\phi_v - \phi_i) + \cos(2\omega t + \phi_v + \phi_i) \right]$$

$$P_{AVG} = \frac{1}{T} \int_0^T p(t) \cdot dt, \quad \int_0^T dt = T - 0$$

$$a + jb \rightarrow a - jb$$

$$Ae^{j\theta} \rightarrow Ae^{-j\theta}$$

$$P_{AVG} = \frac{1}{T} \cdot (T - 0) \cdot \frac{V_m I_m}{2} \cos(\phi_V - \phi_I)$$



$$P_{AVG} = \frac{V_m I_m}{2} \cos(\phi_V - \phi_I)$$

resistive load!

$$= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} = I_{RMS} V_{RMS}$$

MOST NOT resistive

$$P_{AVG} = \frac{V_m I_m}{2} \cdot \underbrace{\cos(\phi_V - \phi_I)}_{\text{power factor}}$$