

EE 221 Circuits II

MARCH 4, 2019

Lecture 11

Introduction to freq. response



at one frequency

$$f = \text{const}$$

$$\frac{1}{1 + j\omega \cdot f \cdot c \cdot d} =$$

$$\frac{1}{1 + j \cdot \frac{f}{\frac{1}{acd}}} =$$


$$\frac{1}{1 + j \frac{f}{f_p}}$$

$$f_p = \frac{1}{acd}$$

CMOSedu.com

1)

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + j \frac{f}{f_p}} \Rightarrow \left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{(1)^2 + \left(\frac{f}{f_p}\right)^2}}$$

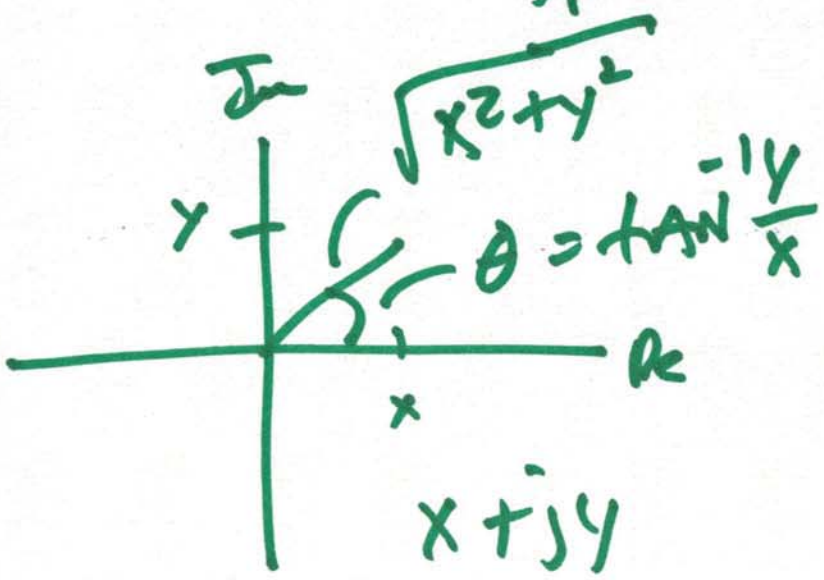

$$\angle \frac{V_{out}}{V_{in}} = -\tan^{-1} \frac{f}{f_p}$$

$$\frac{1}{a + jb} \cdot \underbrace{\frac{a - jb}{a - jb}}_{\text{complex conjugate}}$$

$$\sqrt{\left(\frac{a}{a^2 + b^2}\right)^2 + \left(\frac{-b}{a^2 + b^2}\right)^2}$$

$$\frac{a - jb}{a^2 + b^2} = \frac{a}{a^2 + b^2} + j \frac{-b}{a^2 + b^2}$$

$$\frac{\cancel{a^2 + b^2}}{(a^2 + b^2)^2} = \frac{1}{a^2 + b^2}, \quad \theta = \tan^{-1} \frac{-b}{a^2 + b^2} = -\tan^{-1} \frac{b}{a}$$

v)

$$\frac{20\pi f}{2\pi f} \left| \frac{1}{1 + j \frac{f}{f_p}} \right| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_p}\right)^2}} \rightarrow f = f_p \rightarrow | \cdot | = \frac{1}{\sqrt{2}} = 0.707 = -3dB$$

$$\angle \theta = -\tan^{-1} \frac{f}{f_p} \quad f \ll f_p \rightarrow | \cdot | \approx \frac{1}{1} = 1$$

$$f = \frac{f_p}{10} \rightarrow -\tan^{-1} \frac{1}{10} \approx 0 \quad dB = 20 \cdot \log \frac{1}{1} = 0dB$$

$$f = f_p \Rightarrow -\tan^{-1} 1 = -45^\circ \quad f \gg f_p \rightarrow | \cdot | \approx \frac{1}{\frac{f}{f_p}} = \frac{f_p}{f}$$

$$f = 10f_p \Rightarrow -\tan^{-1} 10 = -90^\circ \quad \text{EX: } f_p = 100 \text{ Hz}$$


- +40dB = x 100
- +20dB = x 20
- +14dB = x 5
- 0dB = x 1
- 3dB = x 0.707
- 6dB = x 1/2

$$f = 100 \cdot f_p = 10 \text{ kHz} \quad f = 10 \cdot f_p = 1 \text{ kHz}$$


$$+6dB = x 2 \quad | \cdot | = \frac{1}{100} \rightarrow -40dB \quad | \cdot | = \frac{1}{10} = -20dB$$

$$-20dB = x \frac{1}{10} \quad -20dB = 20 \log 10^{-1} = 20 \log \frac{1}{10}$$

3)

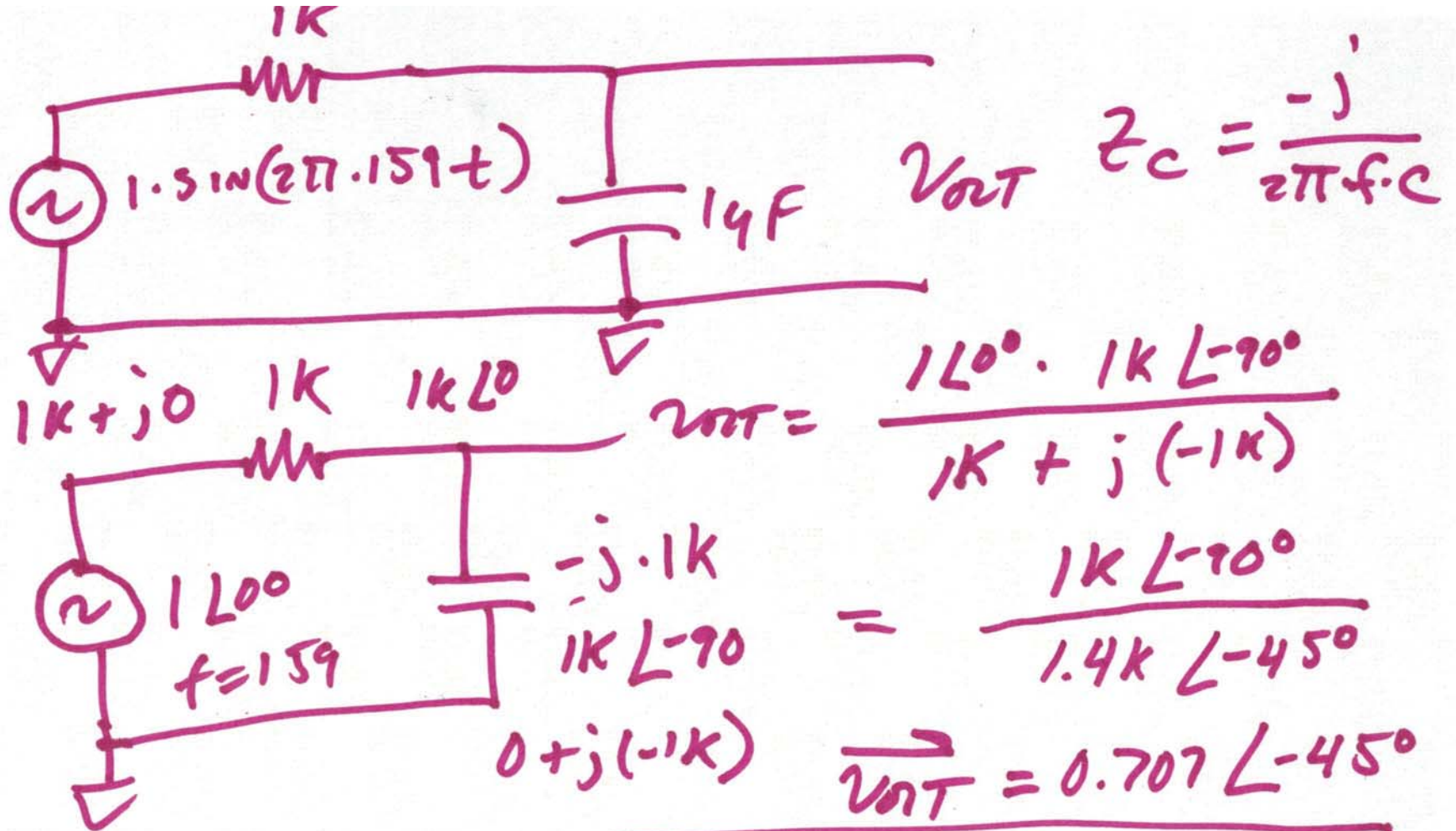
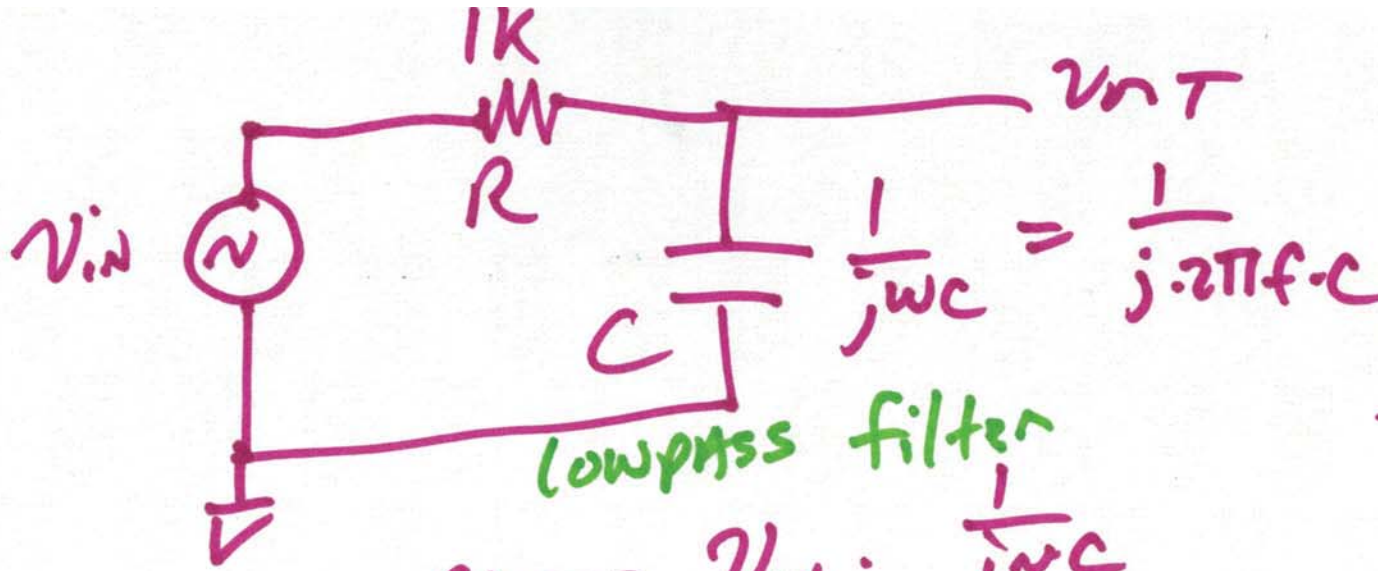
$$V_{out}(t) = 0.707 \sin(2\pi \cdot 159t - 45^\circ)$$




$$\frac{1}{j\omega C} = \frac{1}{j \cdot 2\pi f \cdot C}$$

$$V_{out} = V_{in} \cdot \frac{1}{j\omega C}$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{j\omega C}}{1 + R} = \frac{1}{1 + j2\pi f \cdot RC}$$
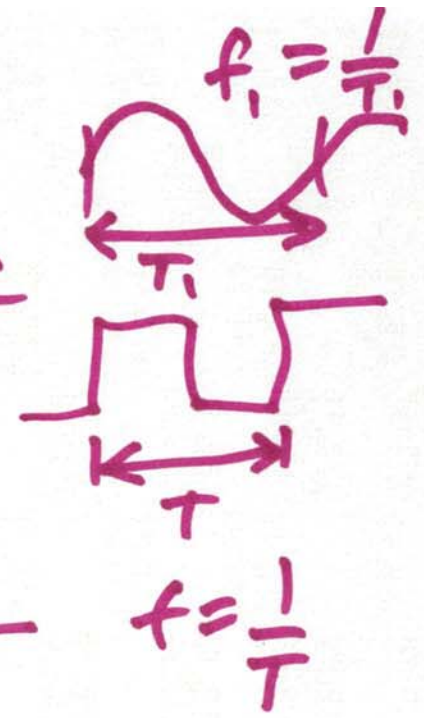
$$f_p = \frac{1}{2\pi \cdot 1K \cdot 10^{-6}} = 159 \text{ Hz}$$



$$f_p = \frac{1}{2\pi RC}$$


5)

log Allow showing

big and small things the plot!

$$\left| \frac{20V}{2V} \right| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_p}\right)^2}} = \frac{1}{\sqrt{1 + \left(\frac{f}{159}\right)^2}}$$
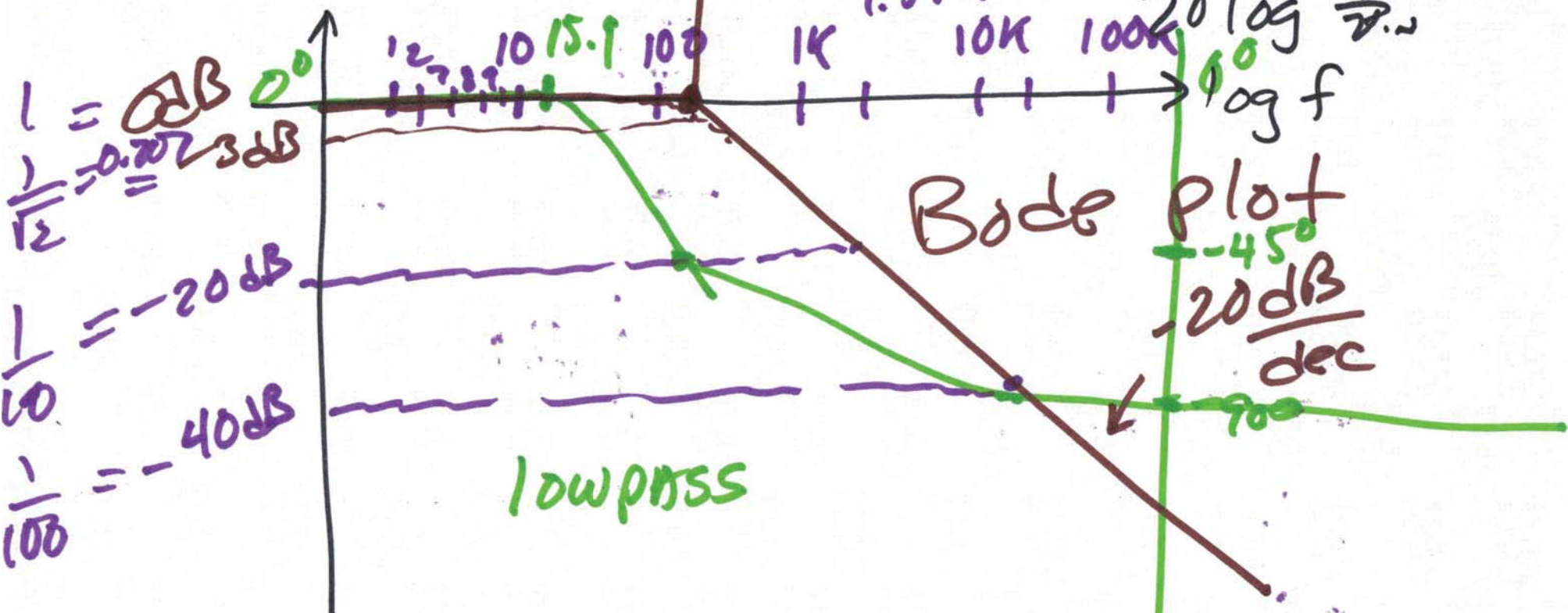
$$\angle \frac{20V}{2V} = -\tan^{-1} \frac{f}{159}$$



$1 = 0dB$
 $\frac{1}{\sqrt{2}} = -3dB$
 $\frac{1}{\sqrt{10}} = -20dB$
 $\frac{1}{\sqrt{100}} = -40dB$


6)

due MARCH 11, Lect 5





H.W. #11 EE 221 Spring 2019

Show your work for credit and put a box around each of your answers (follow the hw guidelines!)

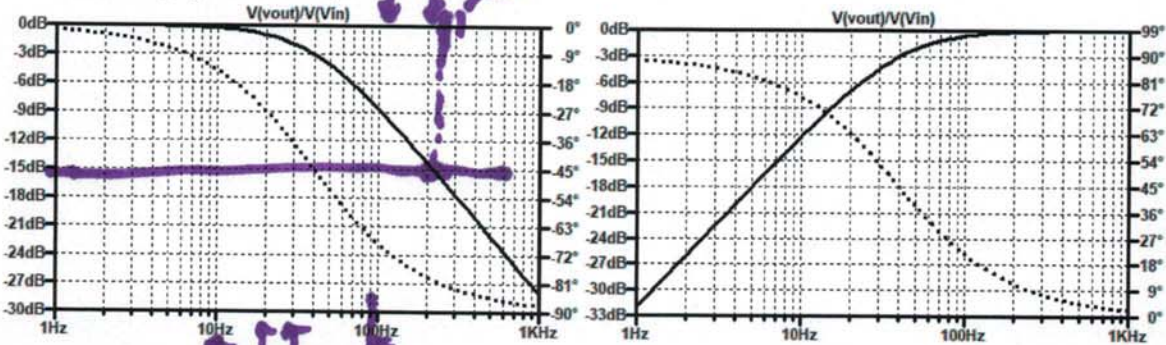- Examine the frequency response plots seen below. If the input to each of the corresponding circuits is a 2V peak signal with a frequency 60 Hz hand sketch the input and output of the circuits. (2 points each)



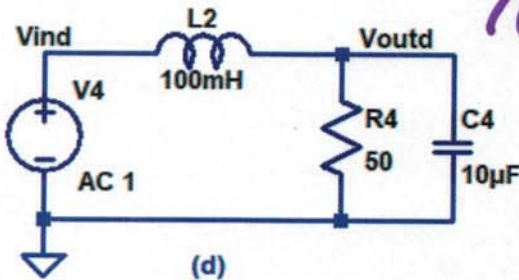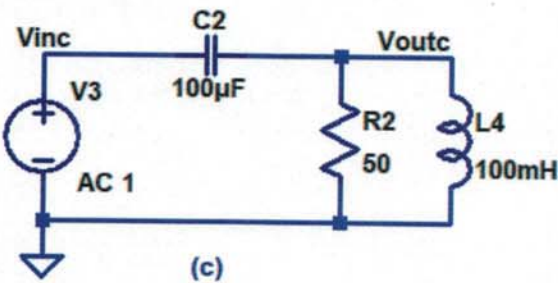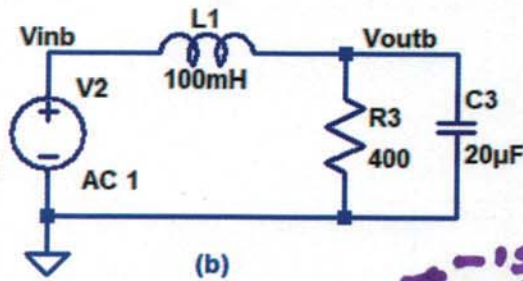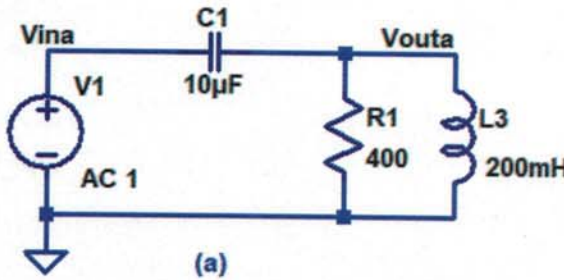- Sketch the Bode responses, both magnitude and phase, for the following circuits. Verify your answer using LTspice. (8 points)




Handwritten purple notes for circuit (b):
 109 dB
 $-15 \text{ dB} = 20 \frac{\text{dB}}{\text{decade}}$
 \downarrow
 $\frac{20 \text{ dB}}{20}$
 $= 1 \text{ dB/decade}$
 $10^{-15/20}$

Handwritten purple '7)'

Where does the zero & pole come from?

$$\frac{V_{out}}{V_{in}} = \frac{1 + j \frac{f}{f_z}}{1 + j \frac{f}{f_p}} \Rightarrow$$

$f = -f_z$
Add to zero

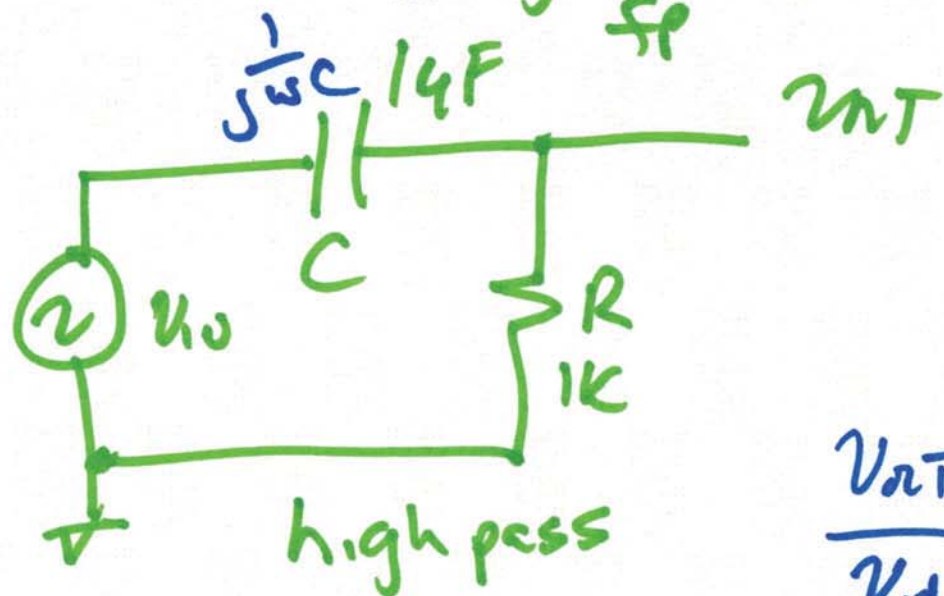

$f = -f_p$
pole

$$\frac{V_{out}}{V_{in}} = \frac{R}{R + \frac{1}{j\omega C}}$$


$$\frac{V_{out}}{V_{in}} = \frac{0 + j \frac{f}{\cancel{2\pi RC}}}{1 + j \frac{f}{\cancel{2\pi RC}}} = \frac{0 + j\omega RC}{1 + j\omega RC} = \frac{0 + j2\pi fRC}{1 + j2\pi fRC}$$

$$\frac{1}{2\pi RC} = 159$$

$$\frac{V_{out}}{V_{in}} = \frac{0 + j \frac{f}{159}}{1 + j \frac{f}{159}}, \quad \left| \frac{V_{out}}{V_{in}} \right| = \frac{\frac{f}{159}}{\sqrt{1 + \left(\frac{f}{159}\right)^2}}$$

$f = 15.9 \text{ Hz} \quad \left| \frac{V_{out}}{V_{in}} \right| \approx \frac{1}{10} = -20 \text{ dB}$
 $f = 1.59 \text{ Hz} \quad \left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{100} = -40 \text{ dB}$

20 dB per decade
40 dB per decade

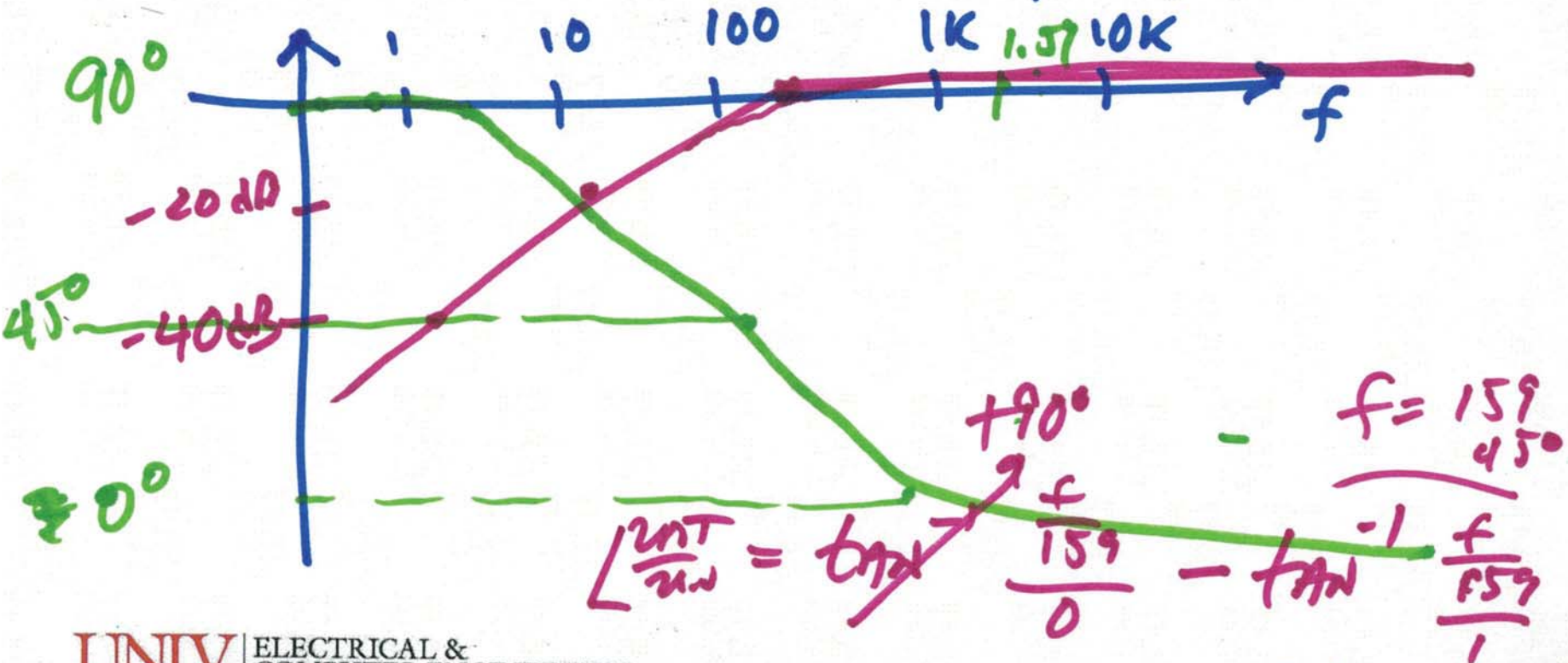

9)

$$f = 70 \text{ Hz} \quad \left| \frac{v_{out}}{v_{in}} \right| = -8 \text{ dB}$$

$$-8 \text{ dB} = 20 \log \left| \frac{v_{out}}{v_{in}} \right|$$

$$\text{if } v_{in} = 2 \sin 2\pi 70 \cdot t \quad \left| \frac{v_{out}}{v_{in}} \right| = 10^{-8/20}$$

$$v_{out} = 0.8 \sin(2\pi \cdot 70 \cdot t + 70^\circ) \quad = 0.4$$


$$\angle 70^\circ = \angle \frac{v_{out}}{v_{in}}$$

$$70 = 360 \cdot \frac{t_d}{T} = 360 \cdot t_d \cdot f$$

$$t_d = \frac{70^\circ}{360^\circ \cdot 70 \text{ Hz}} = 2.78 \text{ ms}$$


10)

AC RESP.

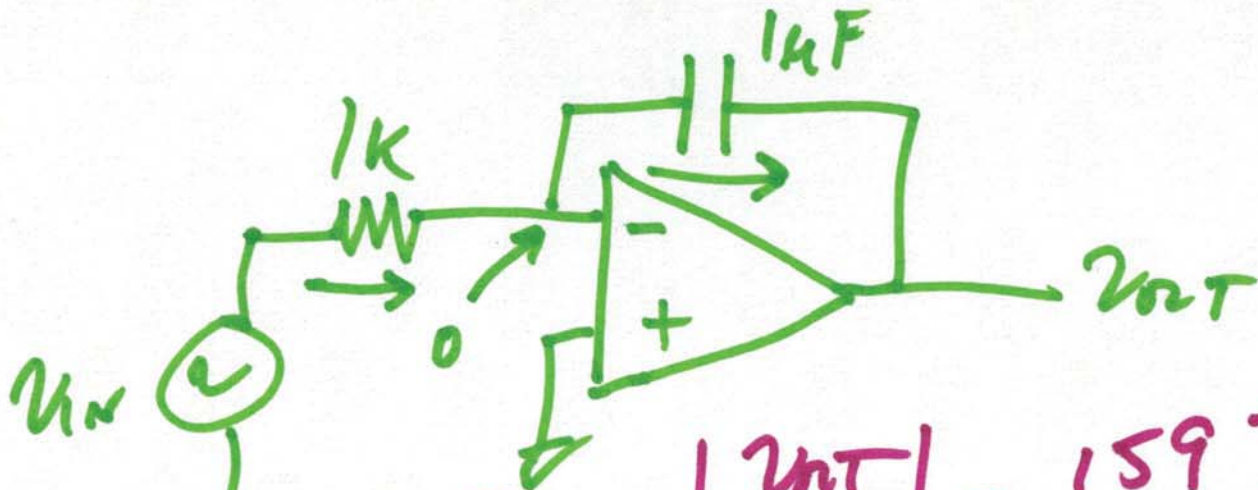

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{1}{\frac{f}{159}} = \frac{159}{f}$$

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{159}{f} \Rightarrow \frac{0 - 20 \text{ dB}}{1/j\omega C} = \frac{v_{out}}{v_{in}} = \frac{1}{R}$$

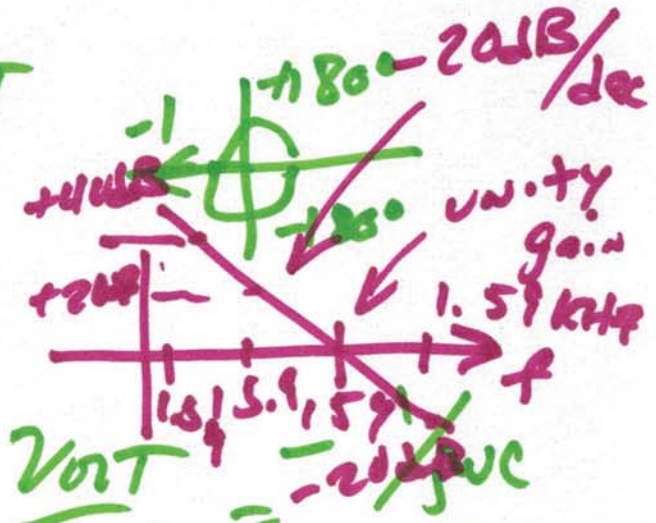

$$\frac{v_{out}}{v_{in}} = -\frac{1}{j\omega RC} = \frac{-1}{0 + j \cdot \frac{f}{2\pi RC}} = \frac{-1}{0 + j \frac{f}{159}}$$

$$\angle \frac{v_{out}}{v_{in}} = 180 - \tan^{-1} \frac{f}{159} = \underline{\underline{+90^\circ}}$$

ii)