


EE 221 circuits II

MARCH 6, 2019

Lecture 12

frequency response examples

high pass crossover

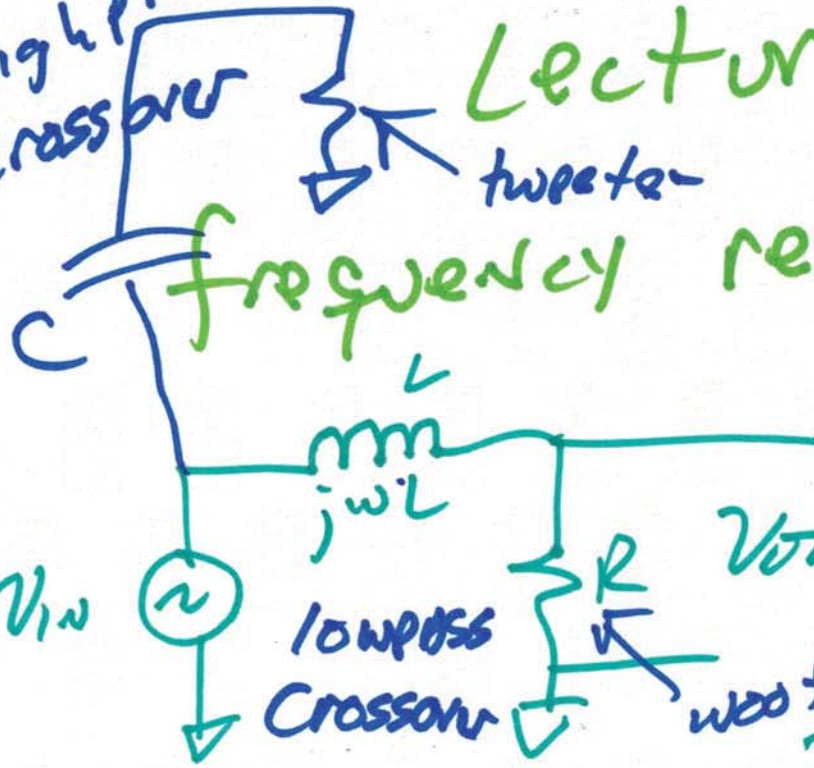

$$V_{OUT} = V_{in} \cdot \frac{R}{R + j\omega L}$$

$$\frac{V_{OUT}}{V_{in}} = \frac{1}{1 + j\omega \frac{L}{R}}$$

$$\left| \frac{V_{OUT}}{V_{in}} \right| = \frac{1}{\sqrt{1 + (2\pi f \cdot \frac{L}{R})^2}}$$

$$= \frac{1}{\sqrt{1 + \left(\frac{f}{f_p}\right)^2}} \quad f_p = \frac{1}{2\pi \frac{L}{R}}$$


$$\angle \frac{V_{OUT}}{V_{in}} = -\tan^{-1} \frac{f}{f_p}$$

1)


$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_p}\right)^2}}$$

$$f_p = \frac{1}{2\pi RC}$$

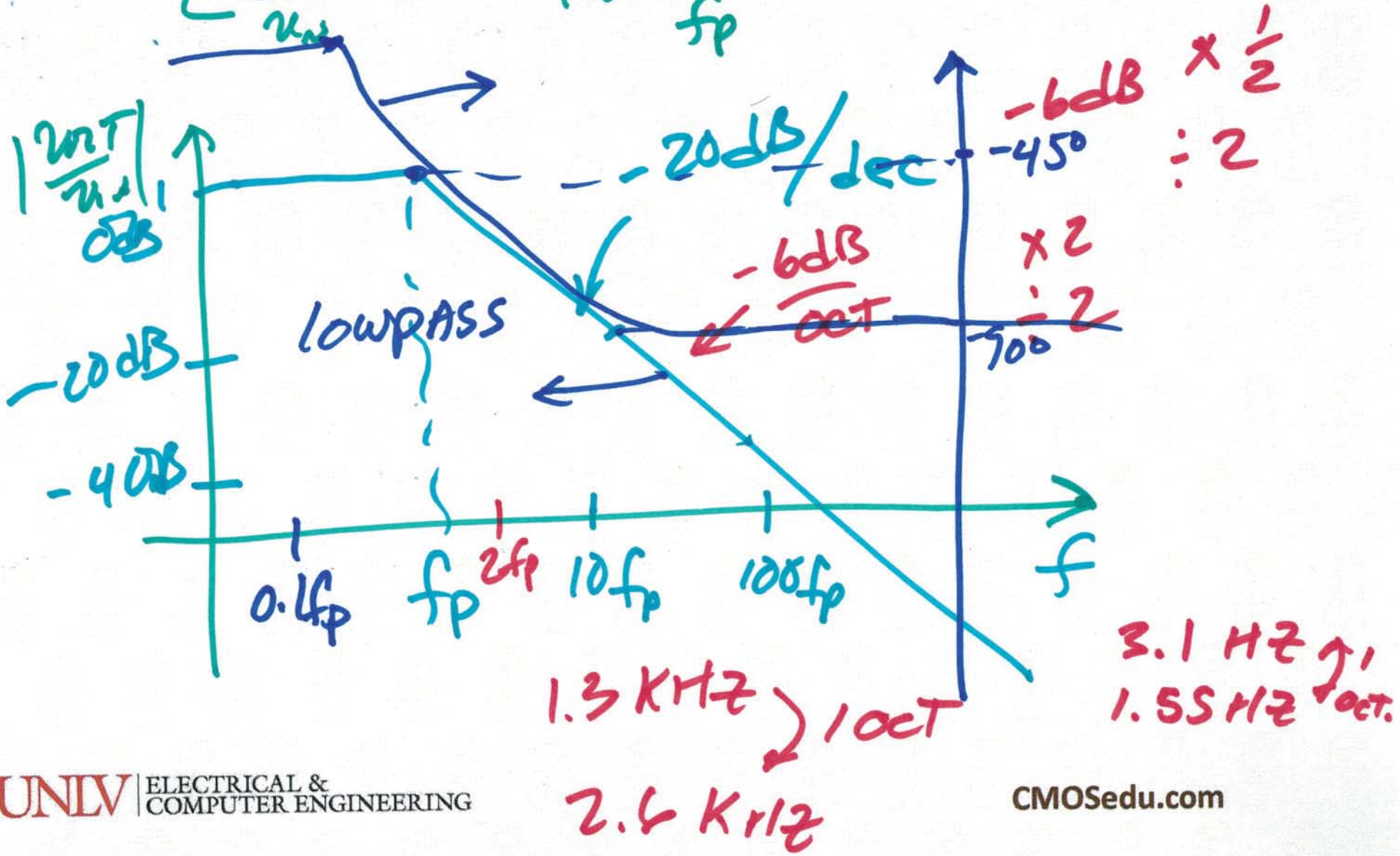
$$\angle \frac{v_{out}}{v_{in}} = -\tan^{-1} \frac{f}{f_p}$$



2)

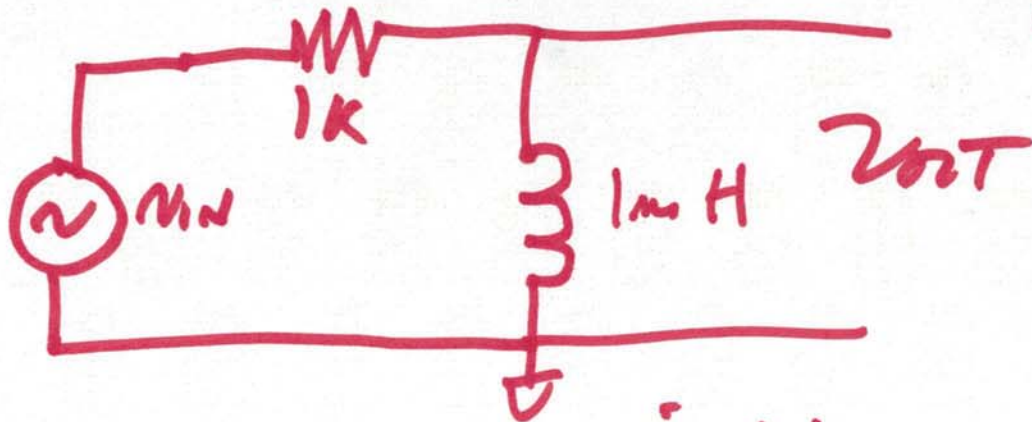

Plot Bode responses

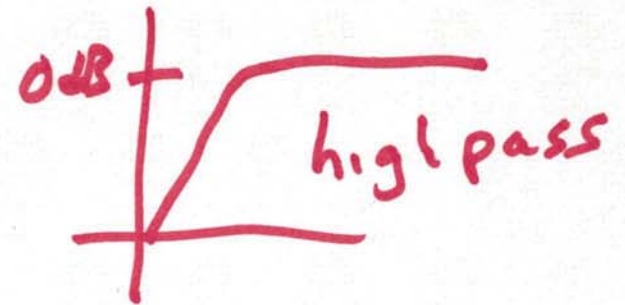


$$v_{out} = v_{in} \cdot \frac{j\omega L}{j\omega L + R}$$

$$\frac{v_{out}}{v_{in}} = \frac{j \cdot 2\pi \cdot f \cdot 10^{-3}}{j \cdot 2\pi \cdot f \cdot 10^{-3} + 10^3}$$

$$\angle \frac{v_{out}}{v_{in}} = \frac{0 + j \cdot f \cdot 2\pi \cdot 10^{-6}}{1 + j \cdot f \cdot 2\pi \cdot 10^{-6}}$$

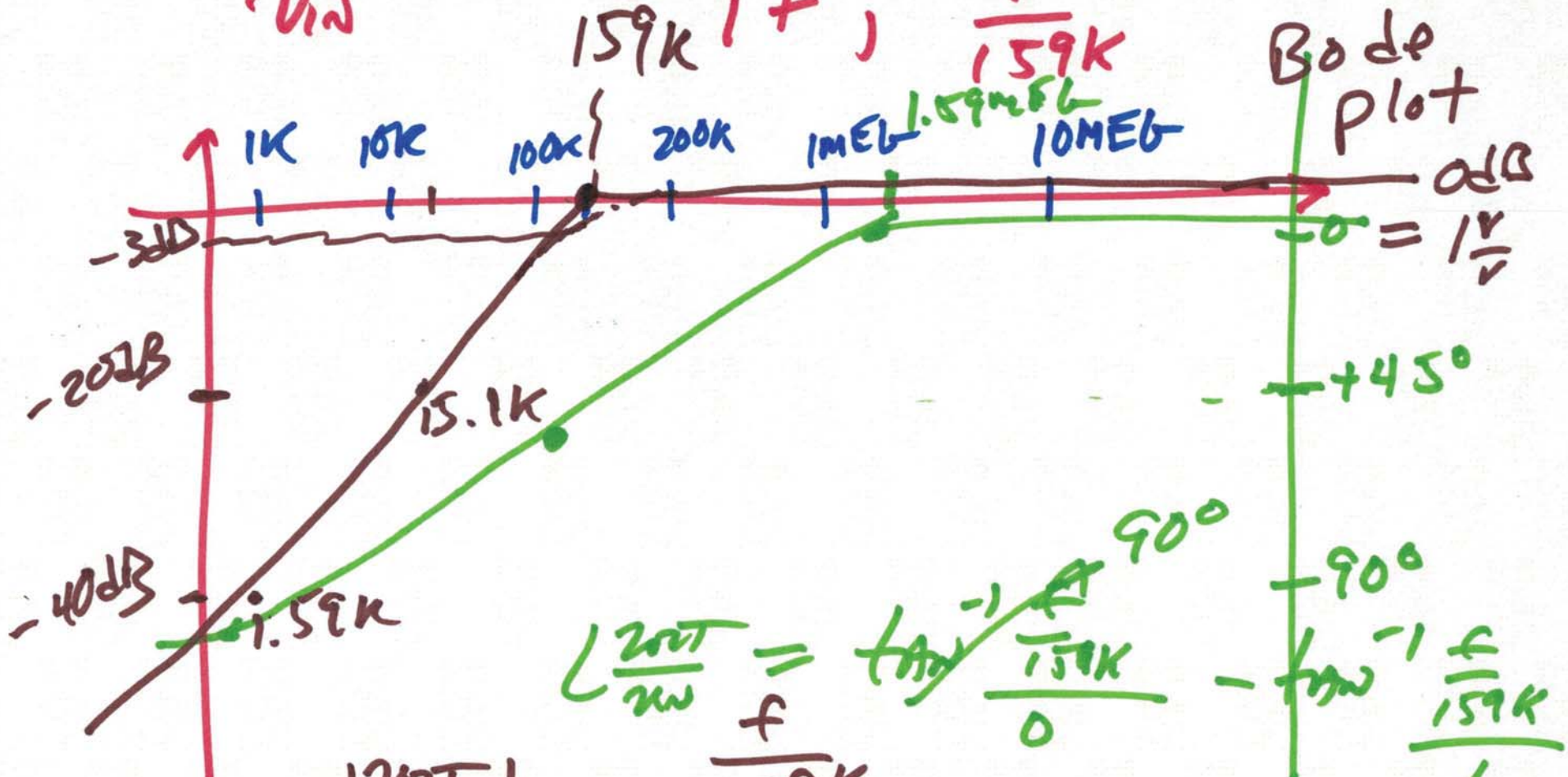3)

$$\frac{v_{out}}{v_{in}} = \frac{0 + j \frac{f}{159k}}{159k \left(1 + j \frac{f}{159k} \right)}$$



-30dB

-20dB

-40dB

$$\angle \frac{v_{out}}{v_{in}} = \tan^{-1} \frac{90^\circ}{\frac{f}{159k}} - \tan^{-1} \frac{f}{159k}$$

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{f}{159k} \sqrt{1 + \left(\frac{f}{159k} \right)^2}$$

4)

$$v_{in} = 3 \sin(2\pi \cdot 40k \cdot t)$$

$$f = 40 \text{ kHz}$$

$$\left| \frac{v_{out}}{v_{in}} \right| = -12 \text{ dB}$$

$$\angle \frac{v_{out}}{v_{in}} = +75^\circ$$

$$-12 \text{ dB} = 20 \log \left| \frac{v_{out}}{v_{in}} \right|$$

$$\frac{v_{out}}{v_{in}} = 10^{-12/20} = \frac{1}{4}$$

$$v_{out} = \frac{3}{4} \sin(2\pi \cdot 40k \cdot t + 75^\circ)$$

$$-20 \text{ dB} = \frac{1}{10}$$

$$-14 \text{ dB} = \frac{1}{5}$$


$$-12 = \frac{1}{4}$$


$$-6 = \frac{1}{2}$$

$$-3 = \frac{1}{\sqrt{2}} = 0.707$$

$$75 = \frac{t_d}{T} \cdot 360 = t_d \cdot 360 \cdot 40k$$
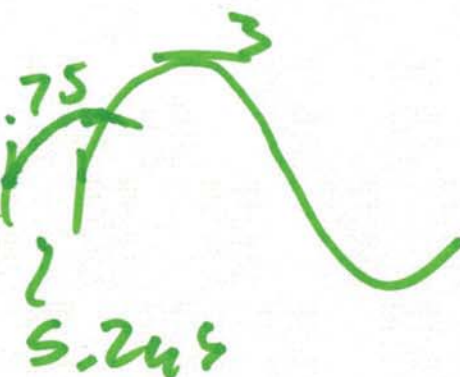
$$t_d = \frac{75}{360 \cdot 40k} = \underline{\underline{5.2 \mu s}}$$



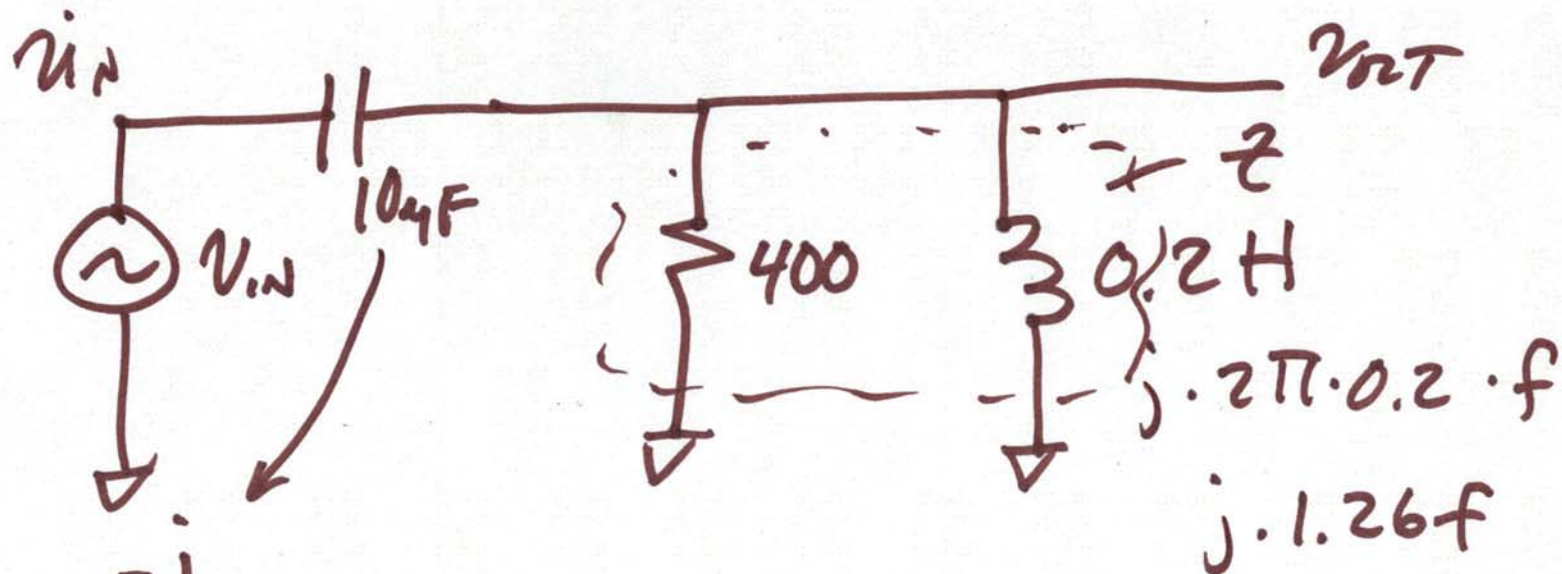

$$\frac{-j}{2\pi \cdot 10^5 \cdot f}$$

$$-j \frac{15.9k}{f}$$

$$Z = \frac{400 \cdot j \cdot 1.26 f}{400 + j \cdot 1.26 f}$$


$$= \frac{400 \angle 0^\circ \cdot 1.26 f \angle 90^\circ}{400 + j \cdot 1.26 f}$$

$$\frac{502.4 \cos 90^\circ + j 502.4 \sin 90^\circ}{400 + j \cdot 1.26 f}$$

$$= \frac{502.4 f \angle 90^\circ}{400 + j \cdot 1.26 f}$$

b)

$$(400 + j0)(0 + j1.26f)$$

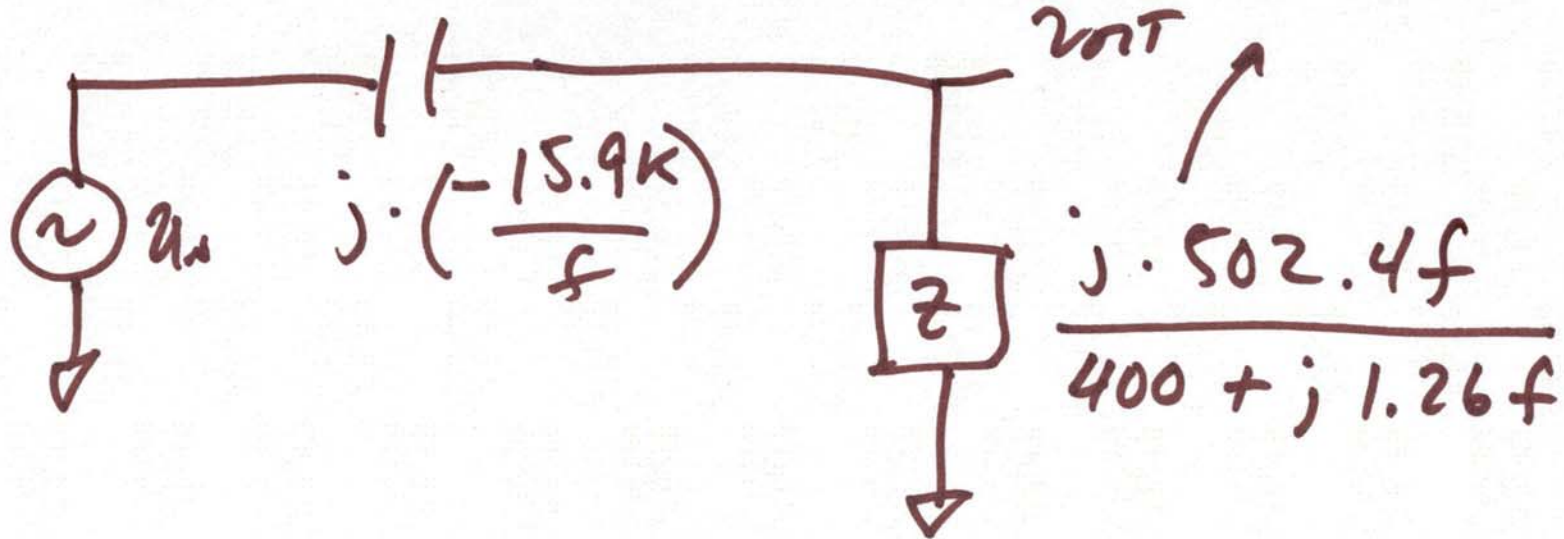

$$\frac{v_{Th}}{v_{in}} = \frac{j \cdot 502.4f}{400 + j1.26f} \div \left(\frac{j \cdot 502.4f}{400 + j1.26f} + j \left(\frac{15.9k}{f} \right) \cdot (400 + j1.26f) \right)$$

7)

$$\frac{v_{out}}{v_{in}} = \frac{j 502.4 f}{j 502.4 f + j \frac{6.36 \cdot 10^6}{f} - 20k}$$


$$j \frac{15.9k}{f} \cdot (400 + j 1.26 f) \cdot \frac{?}{\sqrt{(20k)^2 + \left(\frac{6.36 \cdot 10^6}{f}\right)^2}}$$

$$\frac{1.59k}{f} \angle 90^\circ \cdot \sqrt{(400)^2 + (1.26f)^2} \cdot \angle \tan^{-1} \frac{1.26f}{400}$$

$$\frac{1.59k}{f} \cdot \sqrt{(400)^2 + (1.26f)^2} \angle 90^\circ + \tan^{-1} \frac{1.26f}{400}$$

$\frac{160k \cdot (1.59k)^2}{f^2} + \frac{(1.26)^2}{(1.59k)^2}$

4×10^{11}
~~6.5k~~

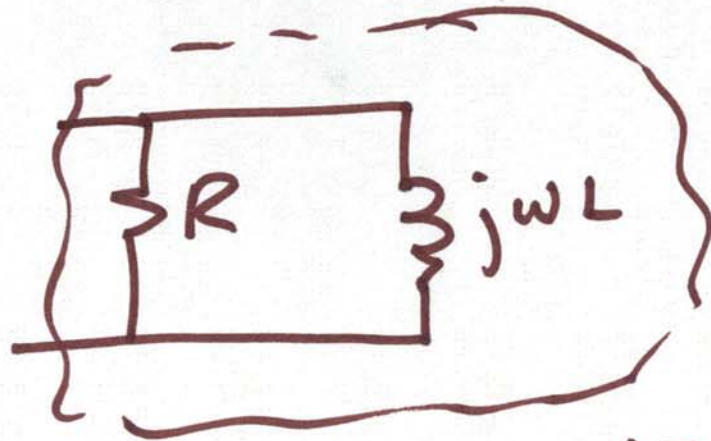


$$z = \frac{j\omega L \cdot R}{R + j\omega L R}$$

$$|z| = \frac{\omega L \cdot R}{\sqrt{R^2 + (\omega L R)^2}}$$

$$\frac{\omega L R \angle 90^\circ}{\sqrt{R^2 + (\omega L R)^2} \angle \tan^{-1} \frac{\omega L R}{R}}$$

$$\angle z = 90^\circ - \tan^{-1} \frac{\omega L R}{R}$$

yes!

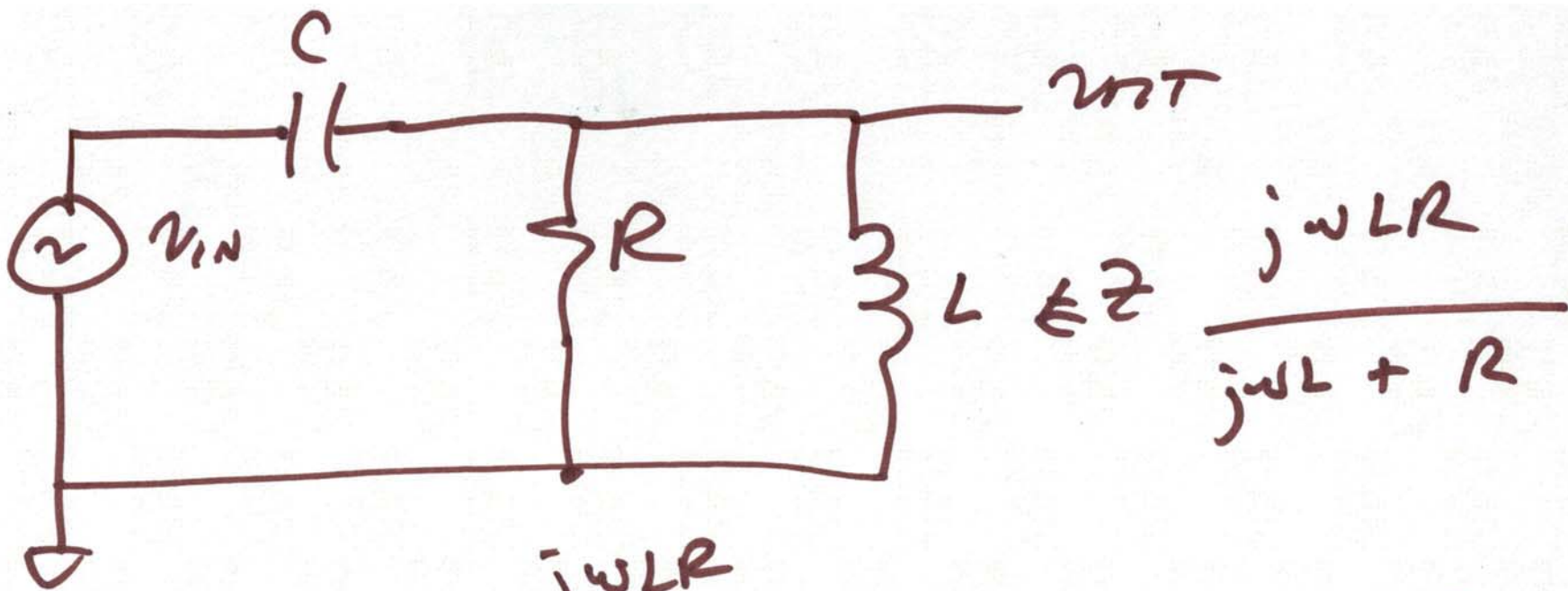

$$\frac{v_{out}}{v_{in}} = \frac{j\omega LR}{j\omega L + R}$$

$$= \frac{j\omega LR}{\frac{j\omega LR}{j\omega LR + R} + \frac{1}{j\omega C}} = \frac{j\omega LR}{j\omega LR + \frac{j\omega LR + R}{j\omega C}}$$

$$\frac{v_{out}}{v_{in}} = \frac{-\omega^2 LRC}{j\omega LR + R + j(-\omega^2 LRC)}$$

a)

$$\frac{v_{out}}{v_{in}} = \frac{-\omega^2 LRC + j0}{(R - \omega^2 LRC) + j\omega LR}$$

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{\sqrt{(\omega^2 LRC)^2 + 0^2}}{\sqrt{(R - \omega^2 LRC)^2 + (\omega LR)^2}}$$

$$\angle \frac{v_{out}}{v_{in}} = 180^\circ - \tan^{-1} \frac{\omega LR}{R - \omega^2 LRC}$$

$$L = 0.2$$

$$C = 10\mu$$

$$R = 400$$

$$\omega LR = f \cdot 2\pi \cdot 400 = 2512f$$

$$\omega^2 LRC = f^2 \cdot (2\pi)^2 \cdot 400 \cdot 10\mu = 0.158f^2$$

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{f \cdot 0.4}{\sqrt{(400 - 0.158f^2)^2 + (2512f)^2}}$$