

EE 221 CIRCUITS II

MARCH 11, 2019

Lecture 13



Review for the midterm

work quizzes & H.W.

NAME: Review ☺

Closed book and notes. No extra paper, do your work on this exam, use the back if needed.
Show your work for credit and be neat!

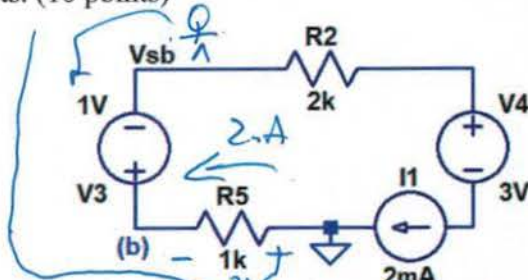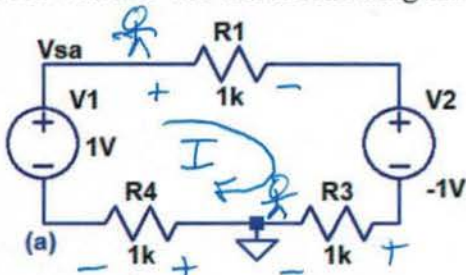1. Find V_{sa} and V_{sb} in the following circuits. (10 points)



$$0 = 1k \cdot I + (-1V) + 1k \cdot I - 1 + 1k \cdot I$$

$$0 = I \cdot 3k - 2$$

$$I = \frac{2}{3} \text{ mA}$$


$$V_{sa} = 1V + 1k \cdot I = 0, V_{sa} = 1 - \frac{2}{3} \text{ mA} \cdot 1k$$

$$V_{sa} = \frac{1}{3} \text{ V}$$

$$V_{sb} + 1V + 2V = 0$$

$$V_{sb} = -3V$$

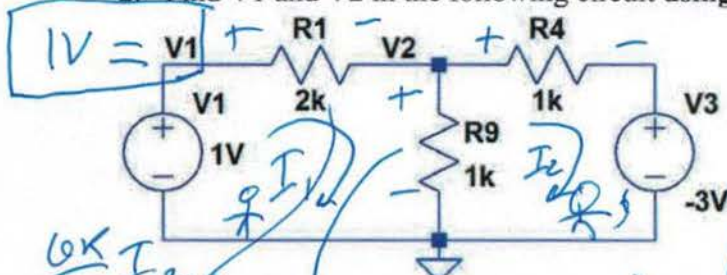2. Find V_1 and V_2 in the following circuit using mesh analysis. (10 points)



$$V_1 - I_1 \cdot 2k - 1k(I_1 - I_2) = 0$$

$$-3V + I_2 \cdot 1k - 1k(I_1 - I_2) = 0$$

$$V_1 + 1k \cdot I_2 = 3k I_1 \quad 333 \mu A$$

$$-3 + 2k I_2 - 1k I_1 = 0$$

$$I_1 = \frac{V_1}{3k} + \frac{1}{3} I_2 = \frac{200 \mu A}{3}$$

$$I_1 = 533 \mu A$$

$$-3 + 2k I_2 - 1k \left(\frac{V_1}{3k} + \frac{1}{3} I_2 \right) = 0$$


$$-3 + 2k I_2 - \frac{1}{3} V_1 - \frac{1}{3} k I_2 = 0$$

$$-3 + \frac{5}{3} k I_2 - \frac{1}{3} V_1 = 0$$

$$I_2 = \frac{-3 + \frac{1}{3} V_1}{\frac{5}{3} k} = 600 \mu A$$

$$V_2 = -1.066 + 1V = -0.066V$$

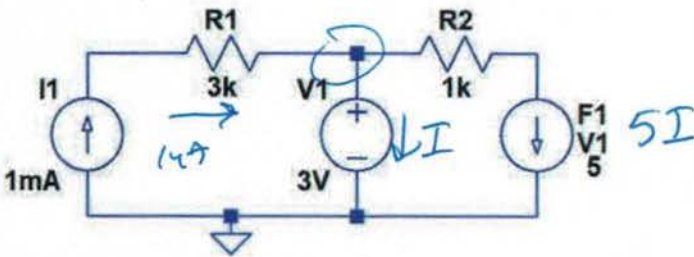3. Find the current through V1. (10 points)




$$1 \mu A = I + 5I$$

$$1 \mu A = 6I$$

$$I = \frac{1}{6} \mu A$$


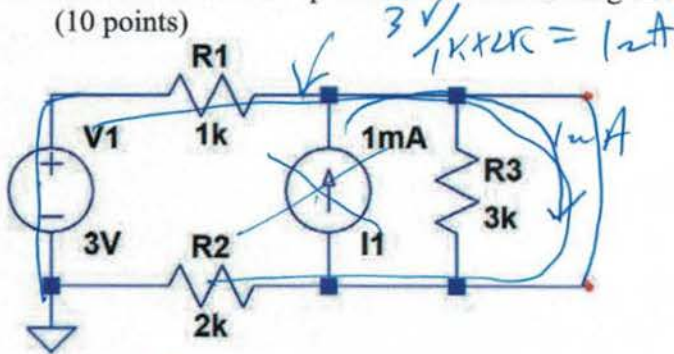
4. Find the Thevenin equivalent of the following circuit at the port indicated by the red dots. (10 points)



$$R_{TH} = 1.5k$$


$$I_{SC} = 2 \mu A$$

$$V_{OS} = I_{SC} \cdot R_{TH} = 3V$$

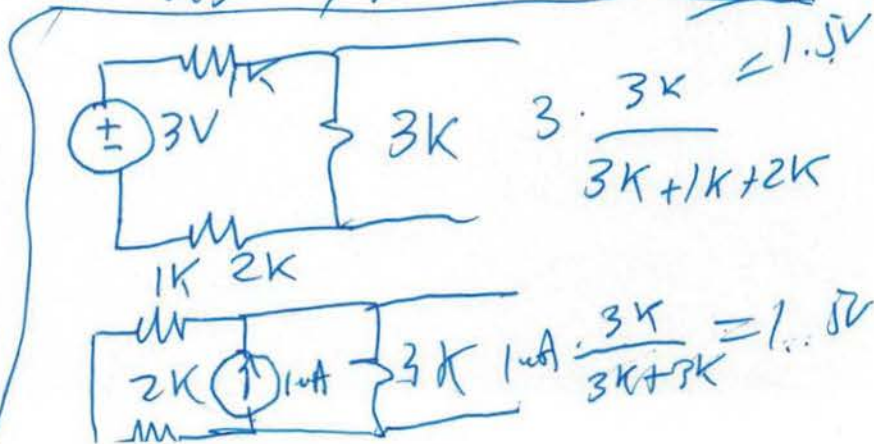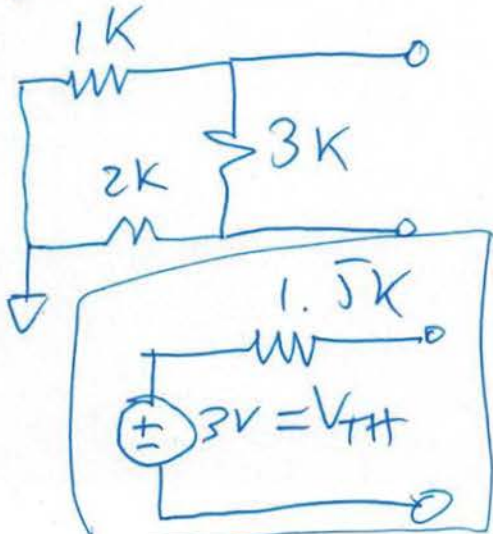


?)

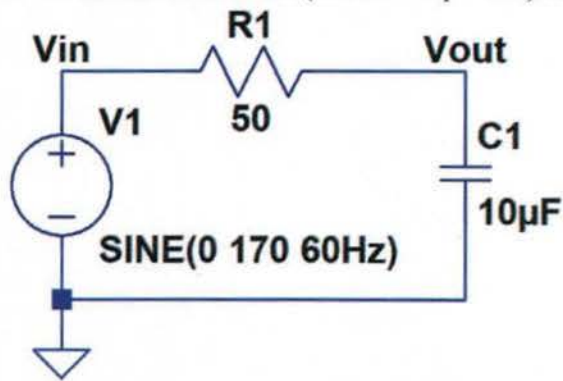5. Find the AC current (write an equation) flowing in the following circuit. (10 points)



$$\Rightarrow \frac{1}{j \cdot 2\pi \cdot 60 \cdot 10^{-5}} = j \cdot (-265.4)$$

\downarrow
 $265.4 \angle -90^\circ$

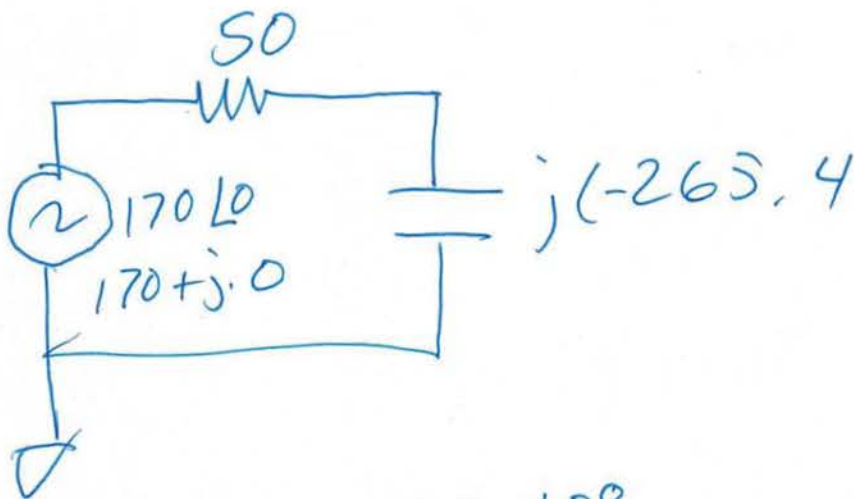


$$\vec{I} = \frac{170 \angle 0^\circ}{265.4 \angle -90^\circ} = 0.64 \angle 90^\circ$$


$$i(t) = 0.64 \sin(2\pi \cdot 60 \cdot t + 90) \text{ A}$$

f)

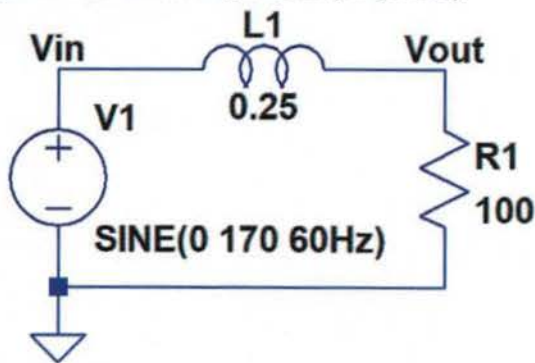6. Find V_{out} in the following circuit and sketch on the same plot with V_{in} , showing the phase shift and magnitude. (15 points)


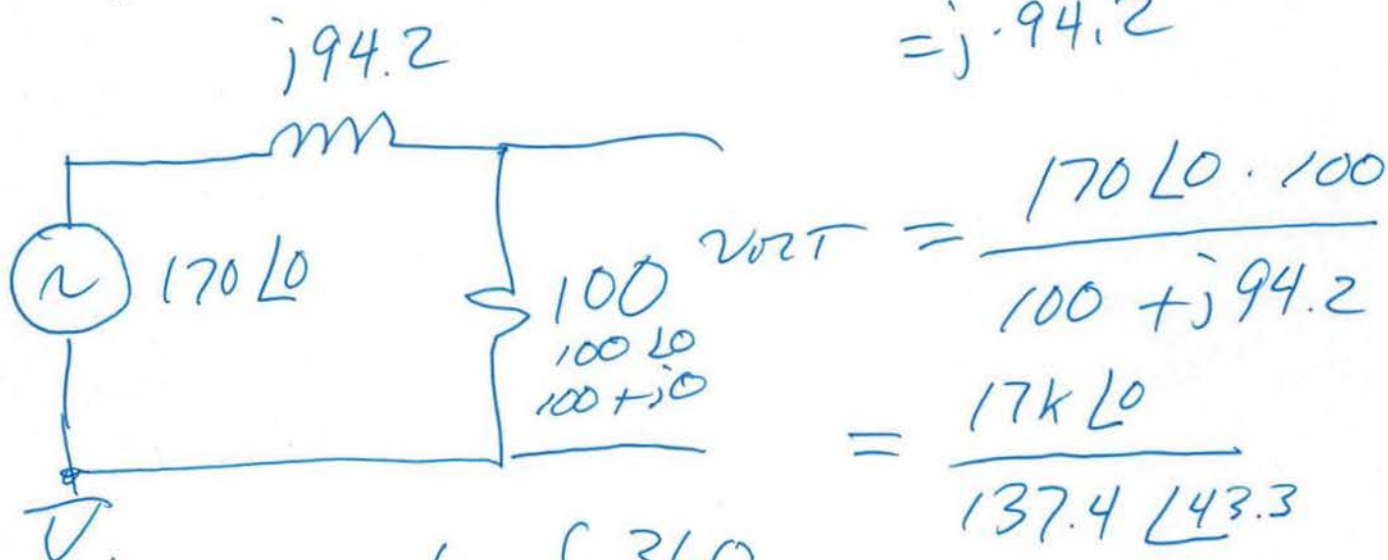
$$\begin{aligned}
 Z_L &= j\omega L \\
 &= j \cdot 2\pi f \cdot L \\
 &= j \cdot 2\pi \cdot 60 \cdot 0.25 \\
 &= j \cdot 94.2
 \end{aligned}$$




$$\theta = \frac{t_d}{T} \cdot 360 = t_d \cdot f \cdot 360$$

$$V_{out} = 123.7 \angle -43.3$$


$$43.3 = t_d \cdot 60 \cdot 360 \quad \boxed{V_{out}(t) = 123.7 \sin(2\pi 60t - 43.3^\circ)}$$

$$t_d = 2 \mu s$$

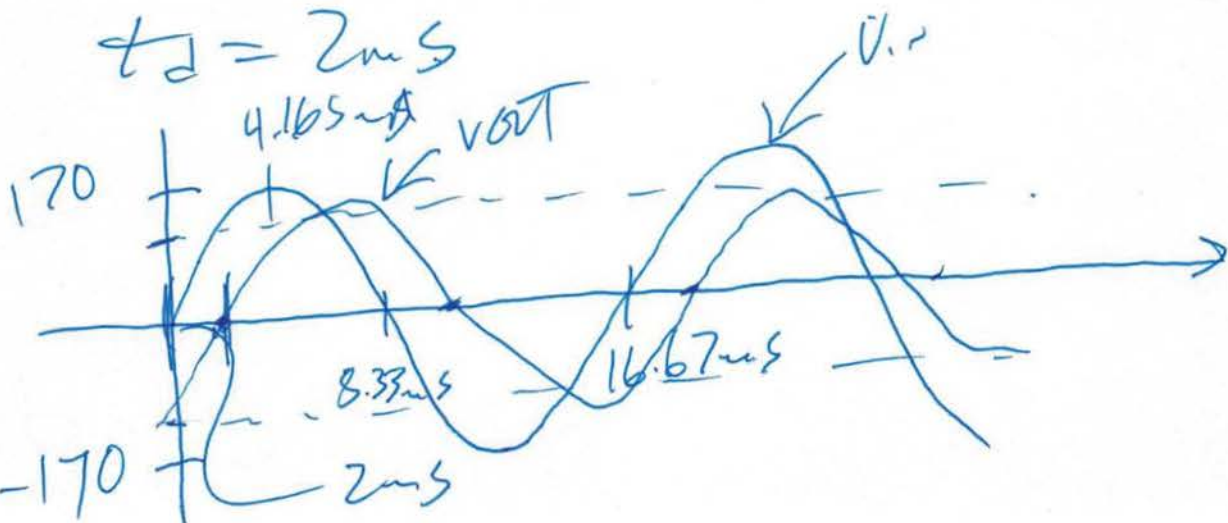


5) -170 2ms

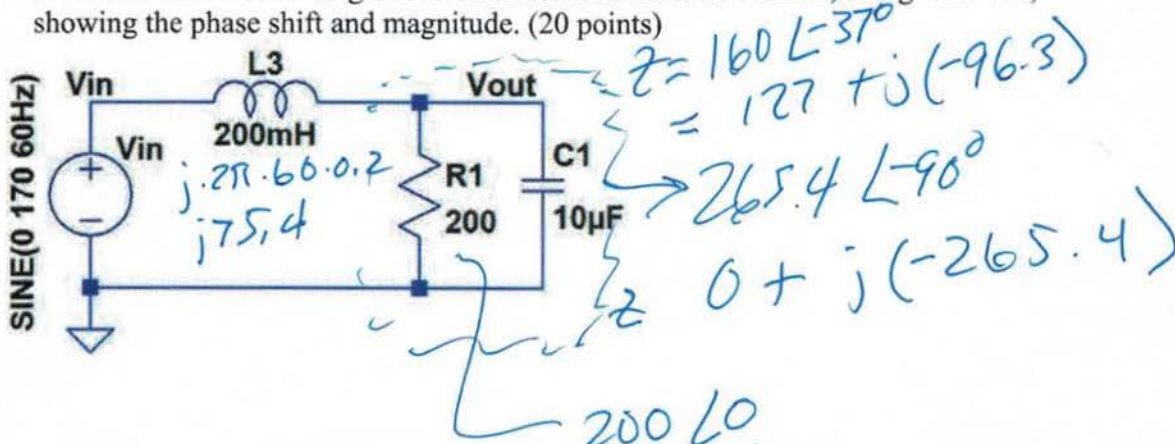
7. Find V_{out} in the following circuit and sketch in the time-domain, along with V_{in} , showing the phase shift and magnitude. (20 points)


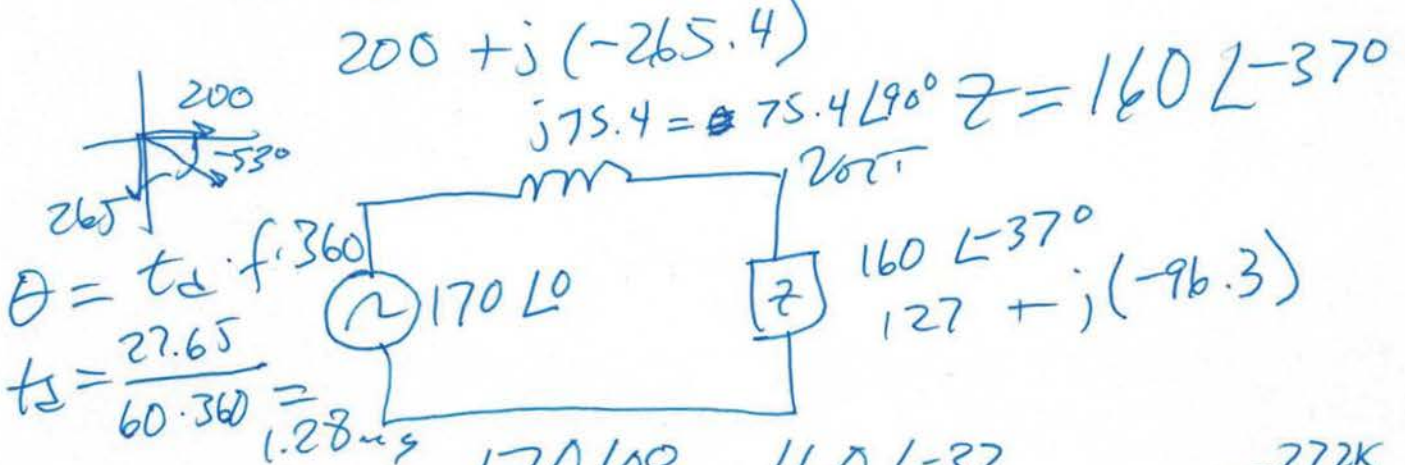
$$Z = \frac{200 \angle 0^\circ \cdot 265.4 \angle -90^\circ}{200 + j0 + 0 + j(-265.4)} = \frac{53080 \angle -90^\circ}{200 + j(-265.4)}$$



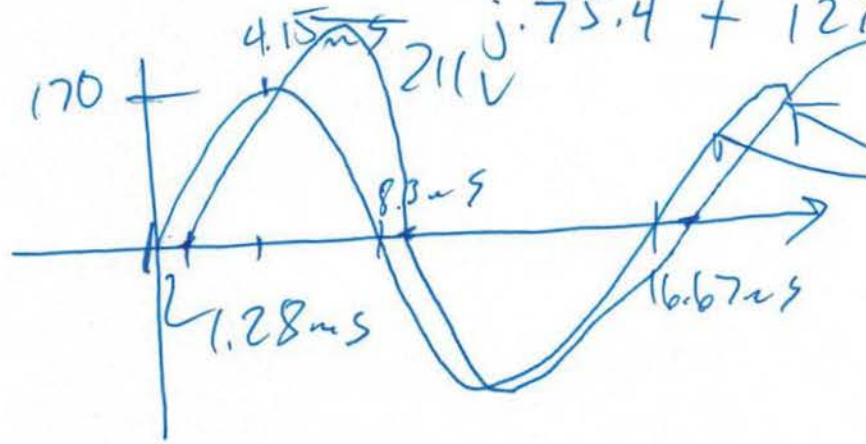
$$V_{out} = \frac{170 \angle 0 \cdot 160 \angle -37^\circ}{j \cdot 75.4 + 127 + j(-96.3)} = \frac{27.2K \angle -37^\circ}{127 + j(-20.9)}$$



$$V_{out} = \frac{27.2K \angle -37^\circ}{128.7 \angle -9.35^\circ} = 211.3 \angle -27.65^\circ$$

$$V_{out} = 211.3 \sin(2\pi \cdot 60 \cdot t - 27.65^\circ) \text{ V}$$

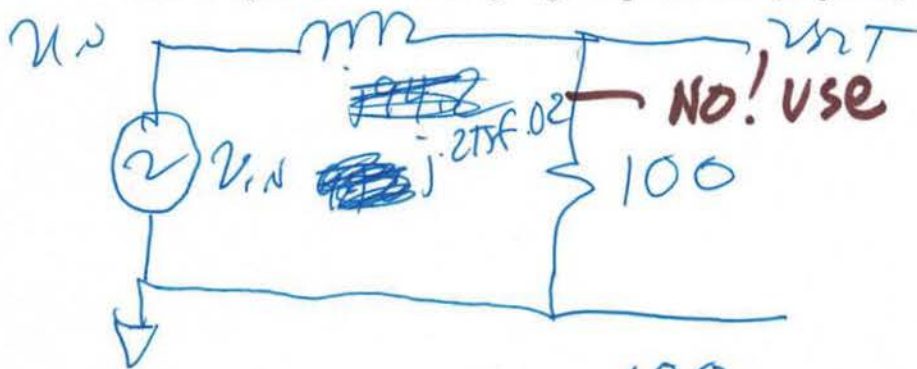8. Determine, and sketch, the frequency response (both magnitude and phase) of the circuit in problem 6. From your plots what are the magnitude and phase shifts at 60 Hz? How do these compare to the answers you got in problem 6? (15 points)



No! use 0.25!
NOT
0.2

$$\frac{v_{oT}}{v_{iN}} = \frac{100}{100 + j \frac{100}{j \cdot 2\pi f \cdot 0.2}} = \frac{1}{1 + j \frac{1}{j \cdot 2\pi f \cdot 0.2}}$$


$$\left| \frac{v_{oT}}{v_{iN}} \right| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_p} \right)^2}}$$

$$\angle \frac{v_{oT}}{v_{iN}} = -\tan^{-1} \frac{f}{f_p} = -\tan^{-1} \frac{f}{796}$$


$$\frac{1}{1 + j \frac{j \cdot 2\pi f \cdot 0.2}{100}}$$

$$\frac{1}{1 + j \frac{f}{100 \cdot 2\pi \cdot 0.2}}$$

$$= \frac{1}{1 + j \frac{f}{796}}$$

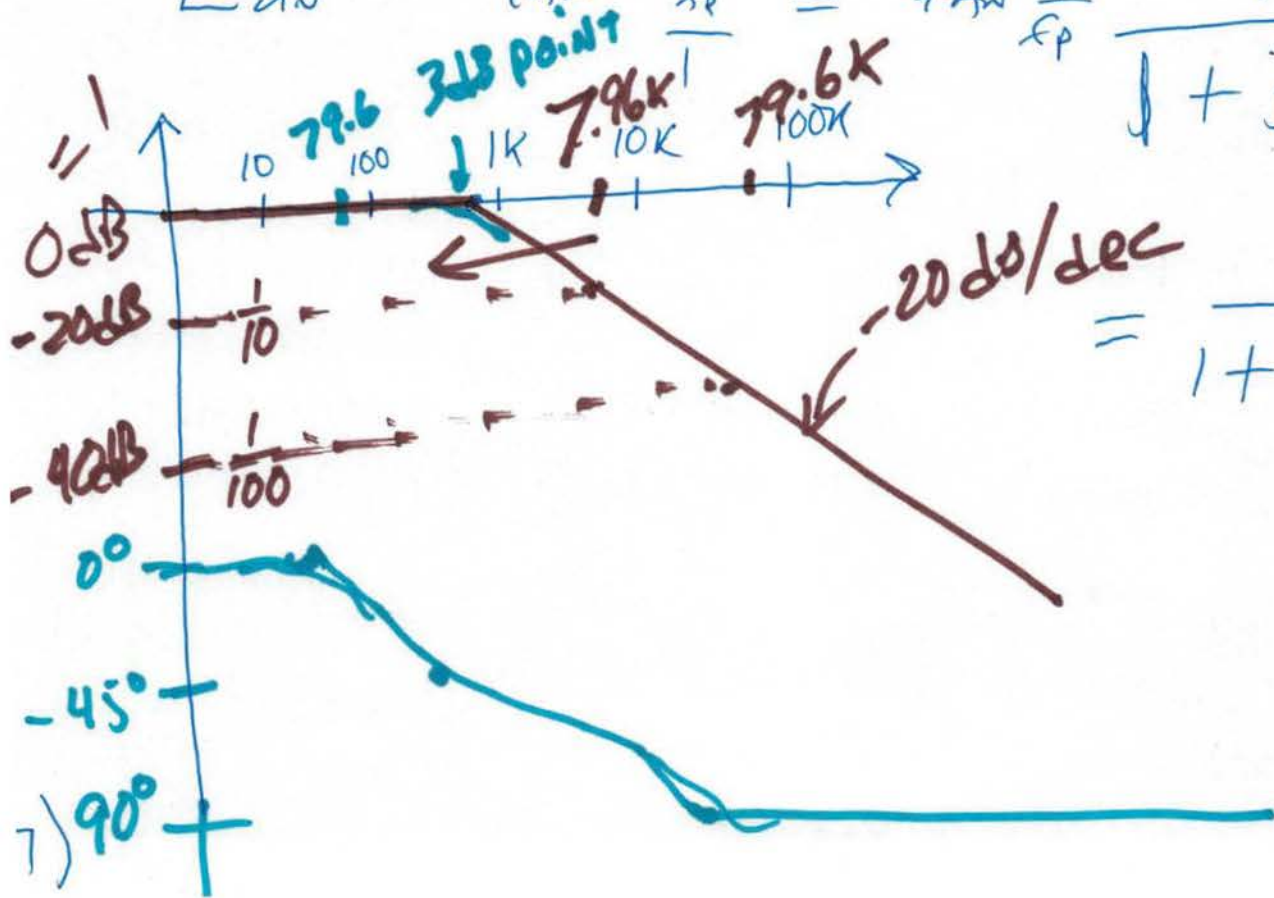


6)

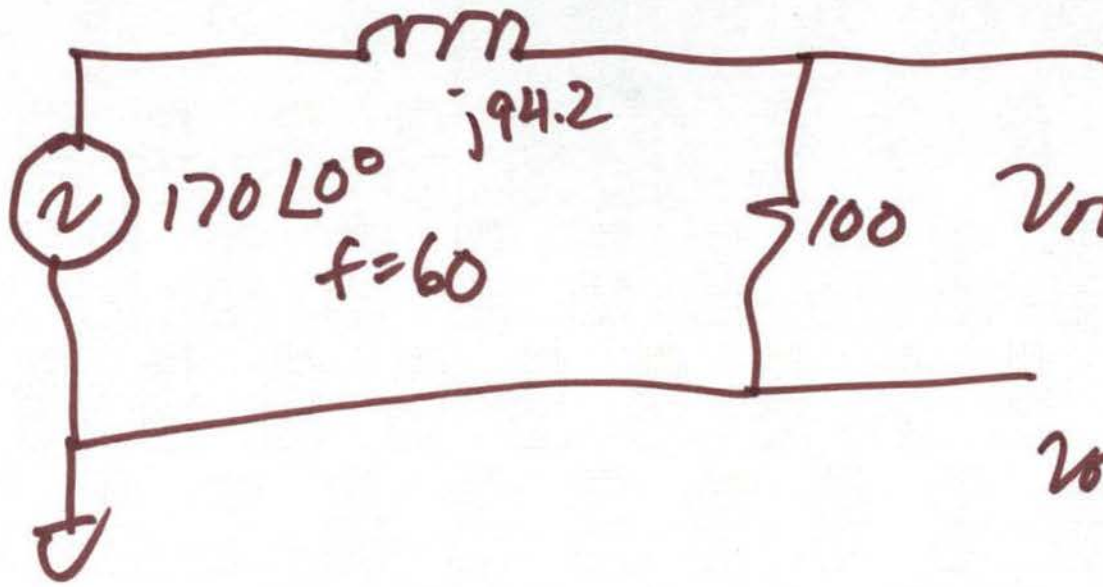

$$V_{NT} = \frac{170 \angle 0^\circ \cdot 100 \angle 0^\circ}{100 + j94.2}$$
$$V_{NT} = 137.3 \angle -43.3^\circ$$
$$V_{NT} = 123.7 \angle -43.3^\circ$$


Right!

8)

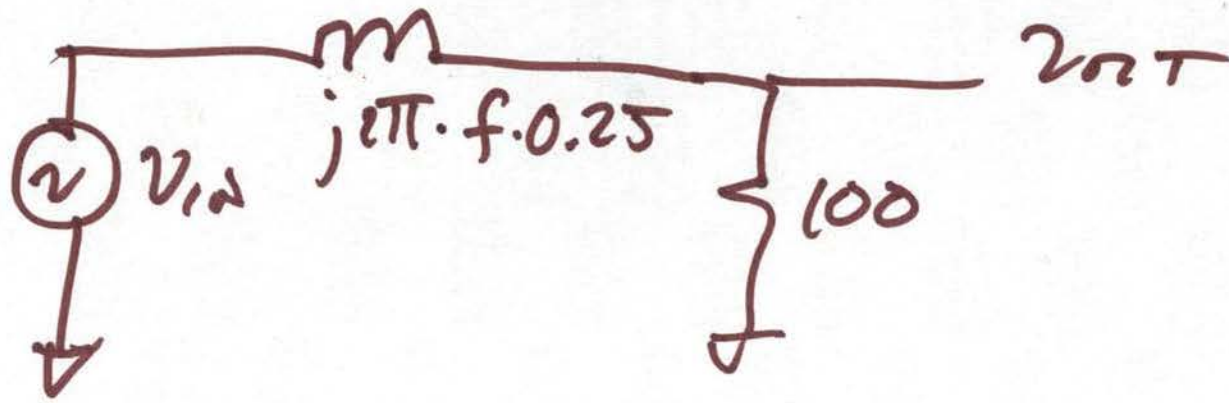

$$v_{out} = v_{in} \cdot \frac{100}{100 + j2\pi \cdot f \cdot 0.25} \Rightarrow \frac{v_{out}}{v_{in}} = \frac{1}{1 + j \frac{2\pi \cdot f \cdot 0.25}{100}}$$

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{1}{\sqrt{1 + \left(\frac{f}{63}\right)^2}}, \quad \angle \frac{v_{out}}{v_{in}} = -\tan^{-1} \frac{f}{63} = \frac{1}{1 + j \frac{f}{63}}$$

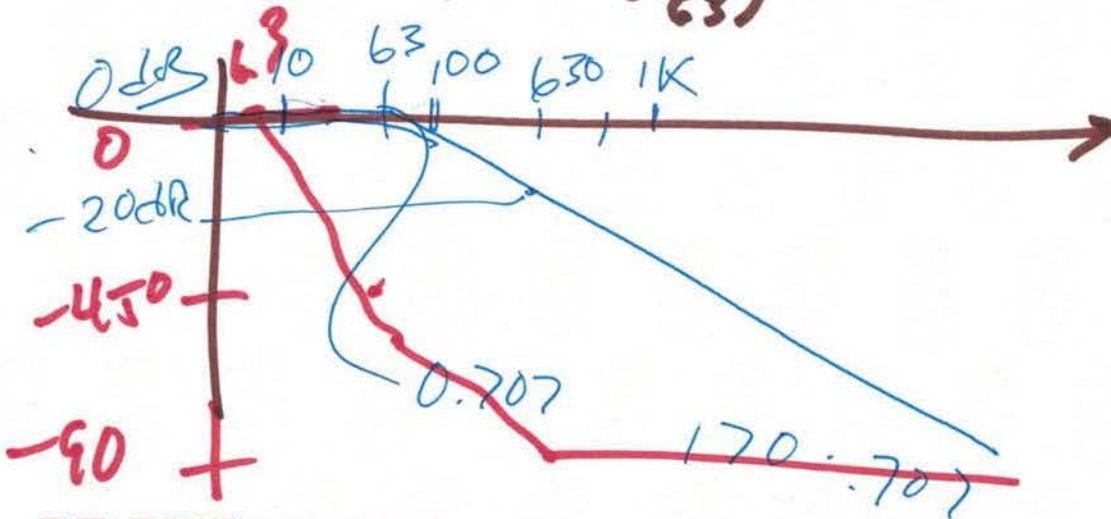

$$= \frac{1}{1 + j \frac{f}{63}}$$