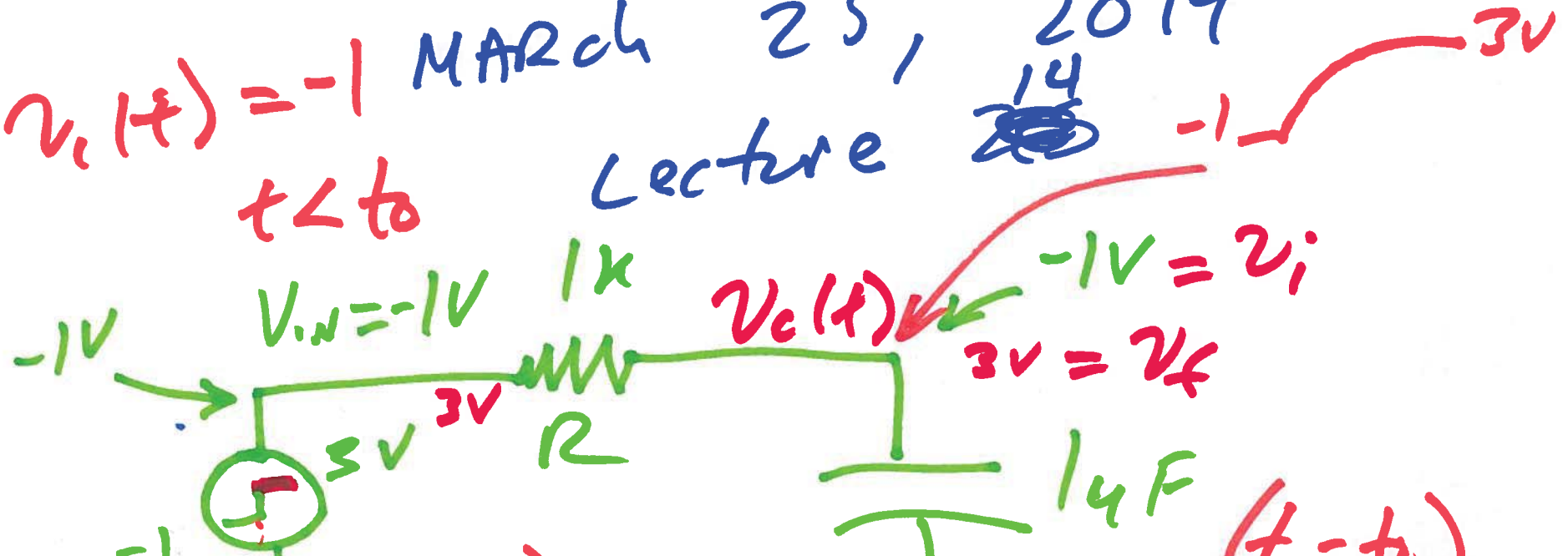


EE 221 Circuits II

$v_c(t) = -1$ MARCH 25, 2019
 Lecture ~~24~~ 14





$3 - 4e^{-\frac{(t-t_0)}{RC}}, t \geq t_0$

to $v_c(t) = v_f + (v_i - v_f)e^{-\frac{(t-t_0)}{RC}}$

$v_c(t) = 3 + (-1 - 3)e^{-\frac{(t-t_0)}{RC}}$

1)

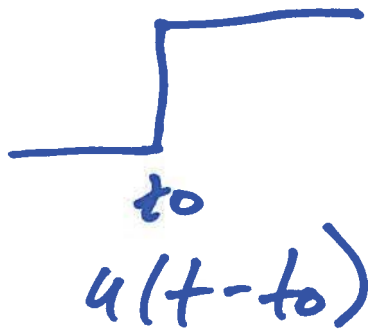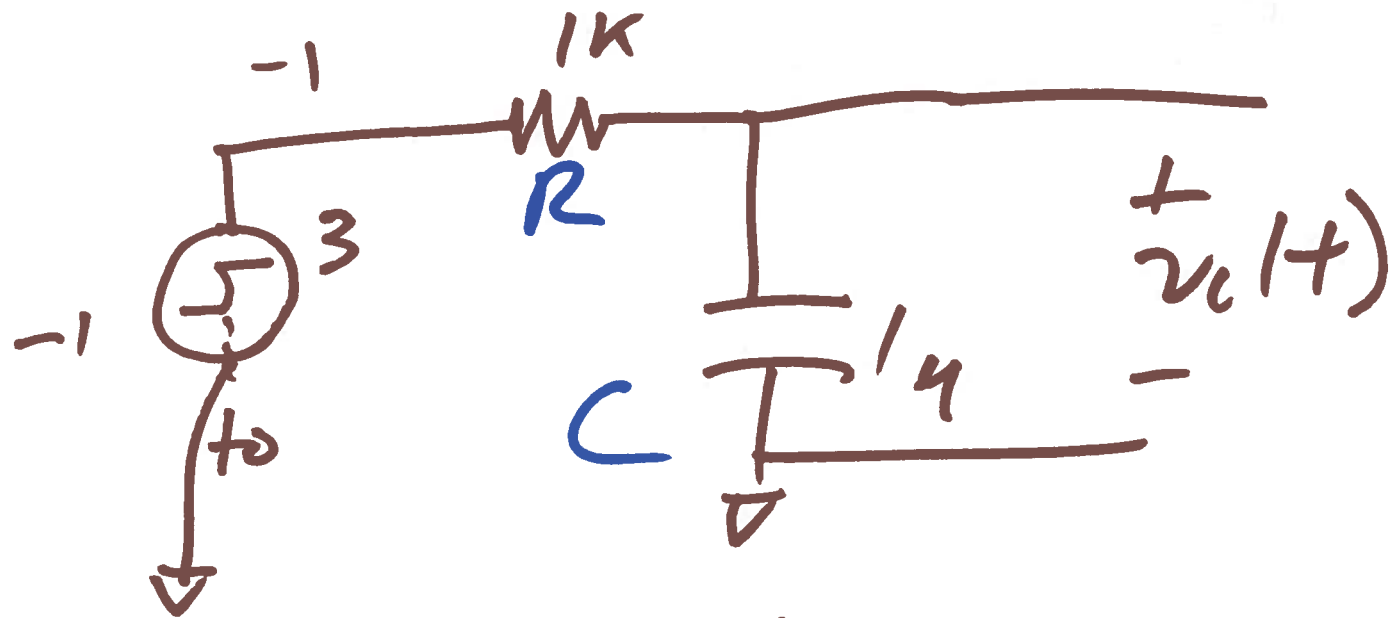


$$v_c(t) = -1V \quad t < t_0$$

$$v_c(\infty) = 3V \quad t \gg t_0$$

$$v_c(t) = 3 + (3 - 1 - 3)e^{-t/RC} \quad t > t_0$$

$$= 3 - 4e^{-t/RC}$$

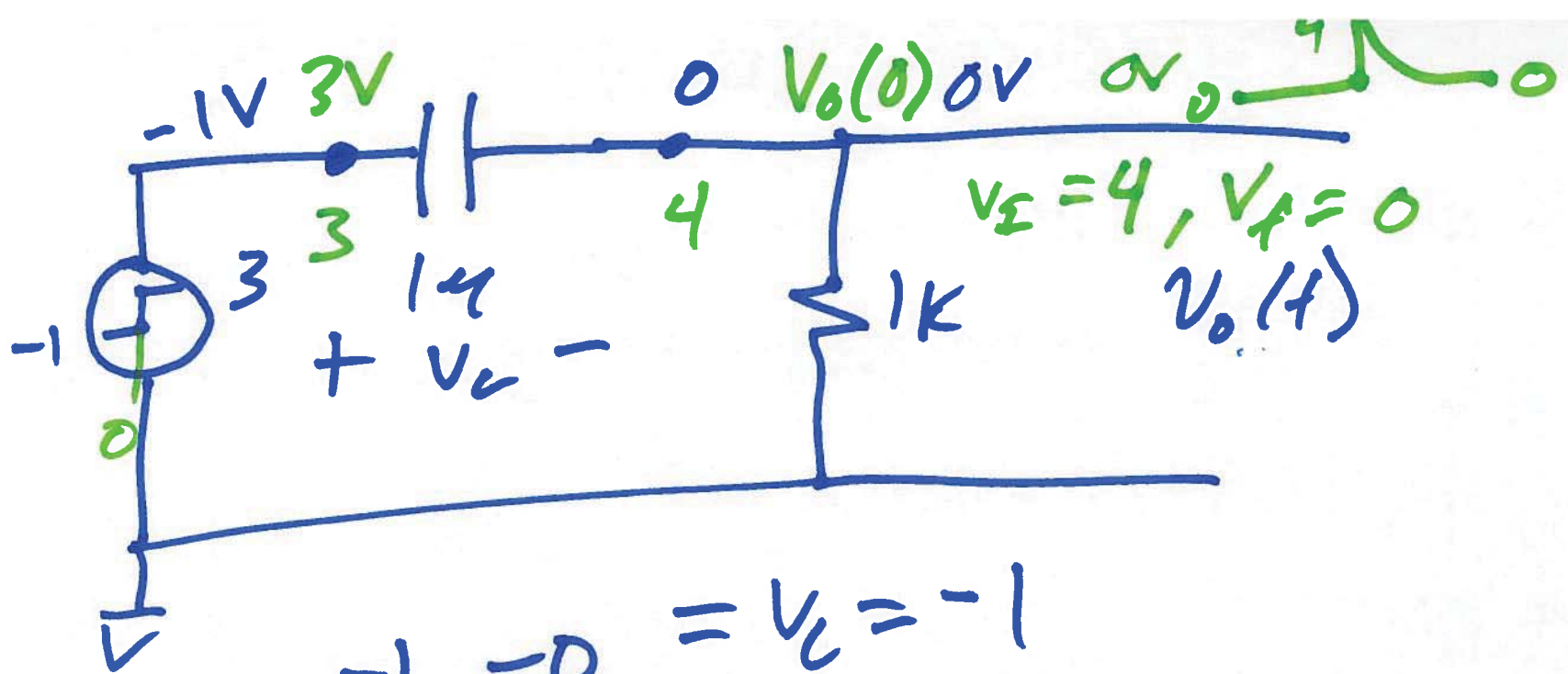


$$-1 - 0 = v_c = -1$$

$$v_c = -1 = 3 - V_o(0) \rightarrow V_o(0) = 4V$$

$$v_o(t) = v_f + (v_i - v_f) e^{-t/RC}$$

$$= 0 + (4 - 0) e^{-t/RC} = 4e^{-t/RC}$$

2)

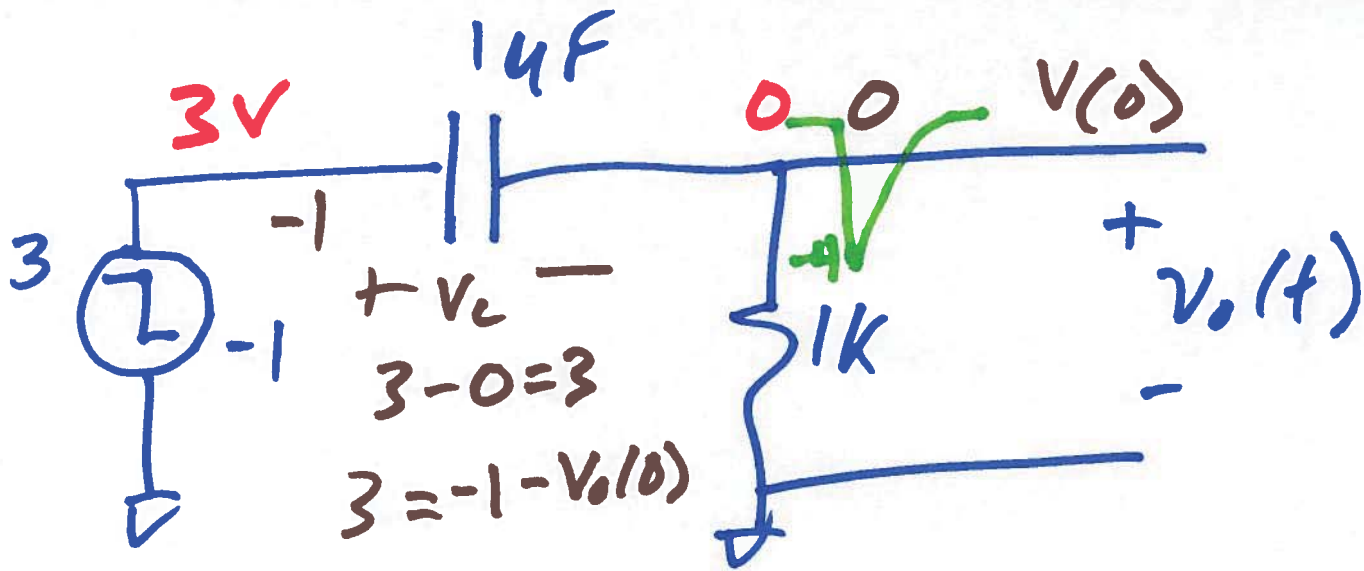


$+v_c -$
 $3 - 0 = 3$
 $3 = -1 - v_o(0)$


$v_o(0) = -4V$

$v_i = -4, v_f = 0$

4)

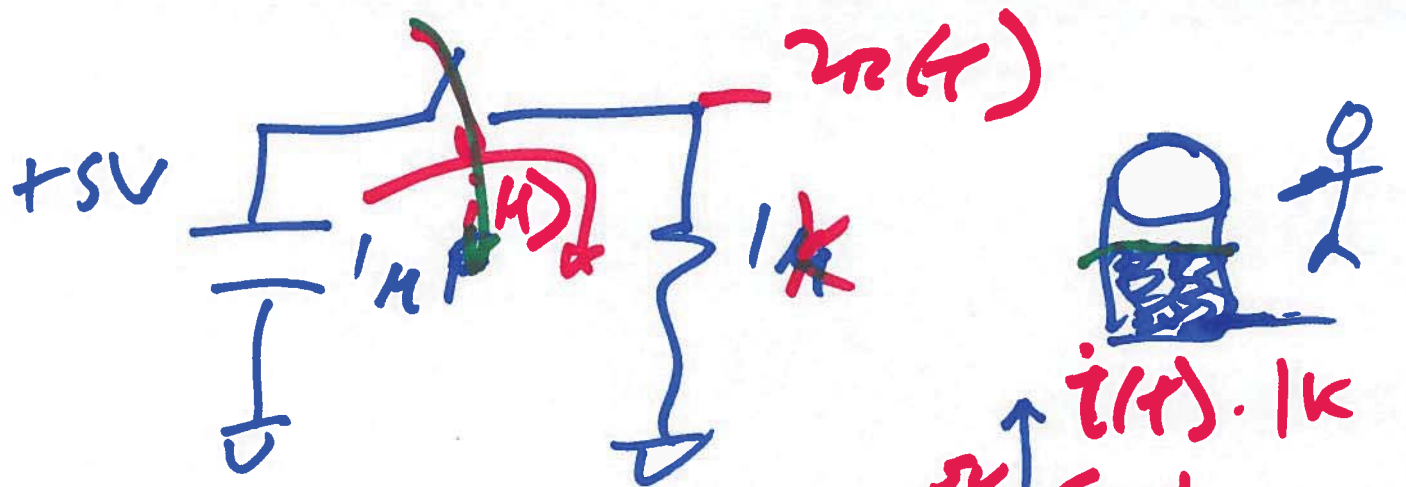

$v_i = 5V$
 $v_f = 0$

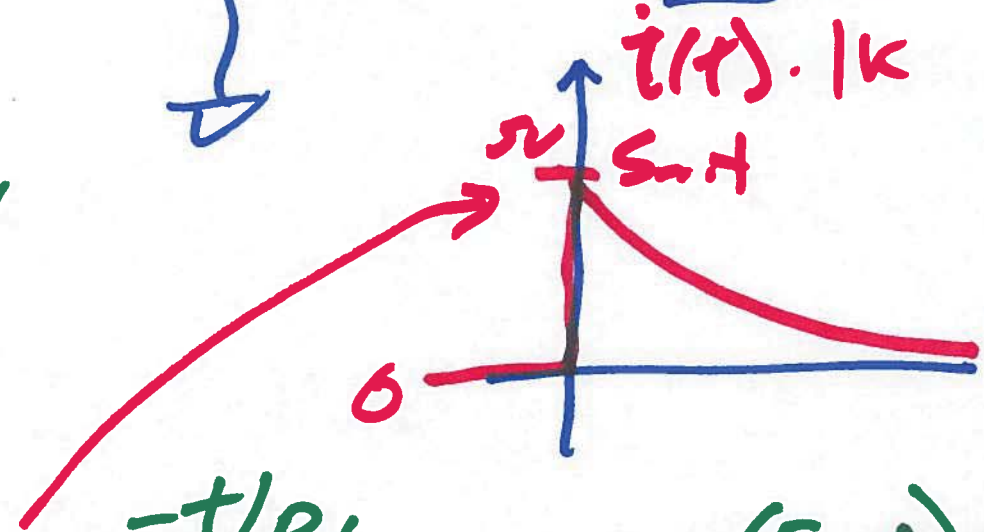


$$v_R(t) = 5e^{-t/RC} = 0 + (5-0)e^{-t/RC}$$

$$i(t) = \frac{v_R(t)}{1k} = 5mA e^{-t/RC} \quad t > 0$$

$$v_R(t) = v_f + (v_i - v_f)e^{-t/RC} \quad \text{switch closed}$$

5)

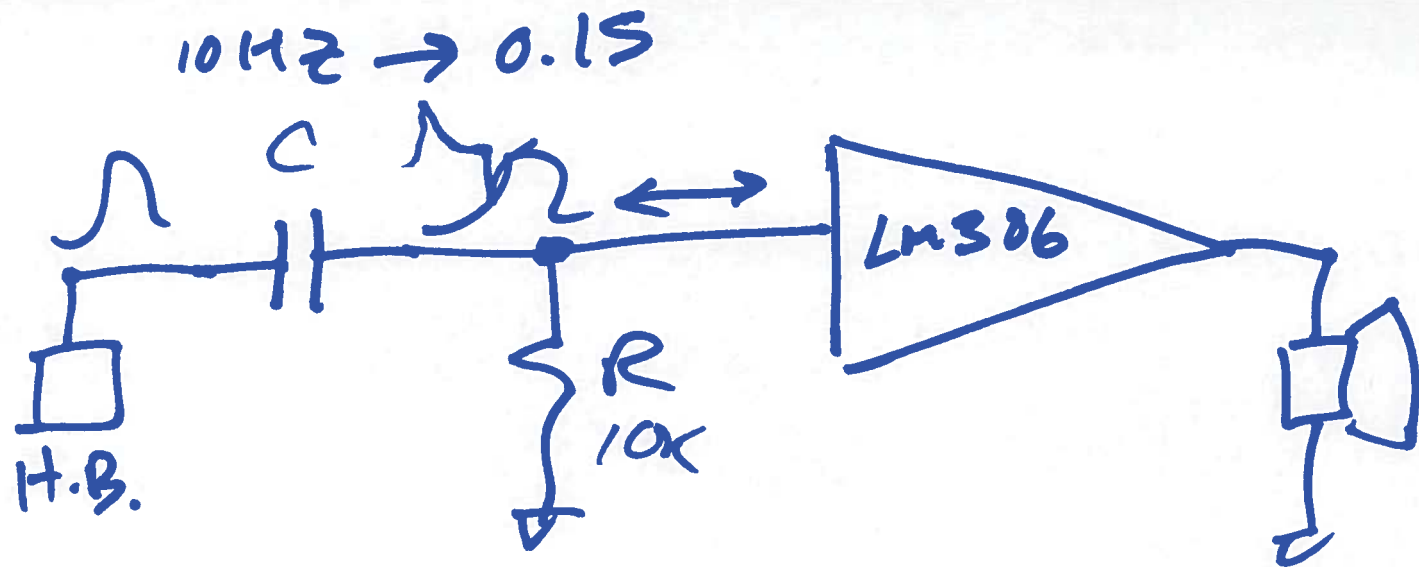


100 Hz - 1 kHz

$\tau \gg 0.15$



$$f = \frac{1}{T} = 10 = \frac{1}{0.1}$$

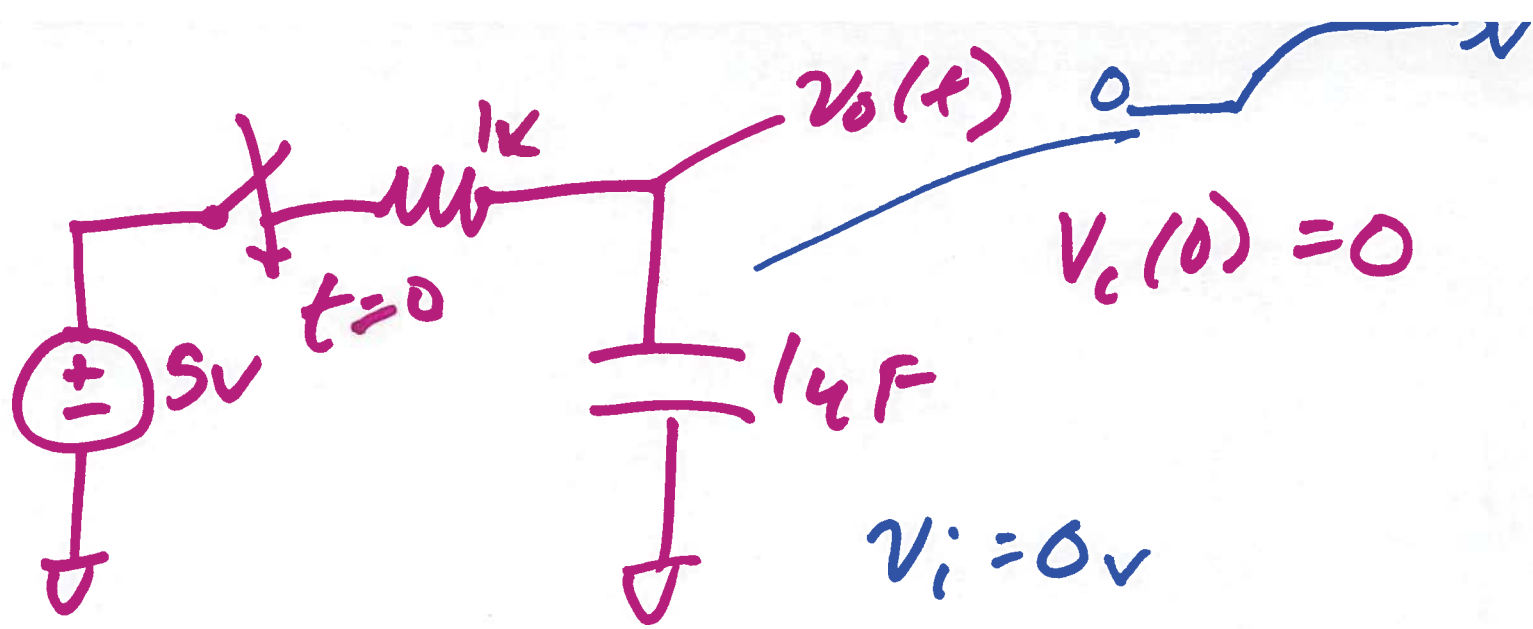

$$v_o(t) = 5 + (0 - 5)e^{-t/RC}$$

$$= 5(1 - e^{-t/RC})$$