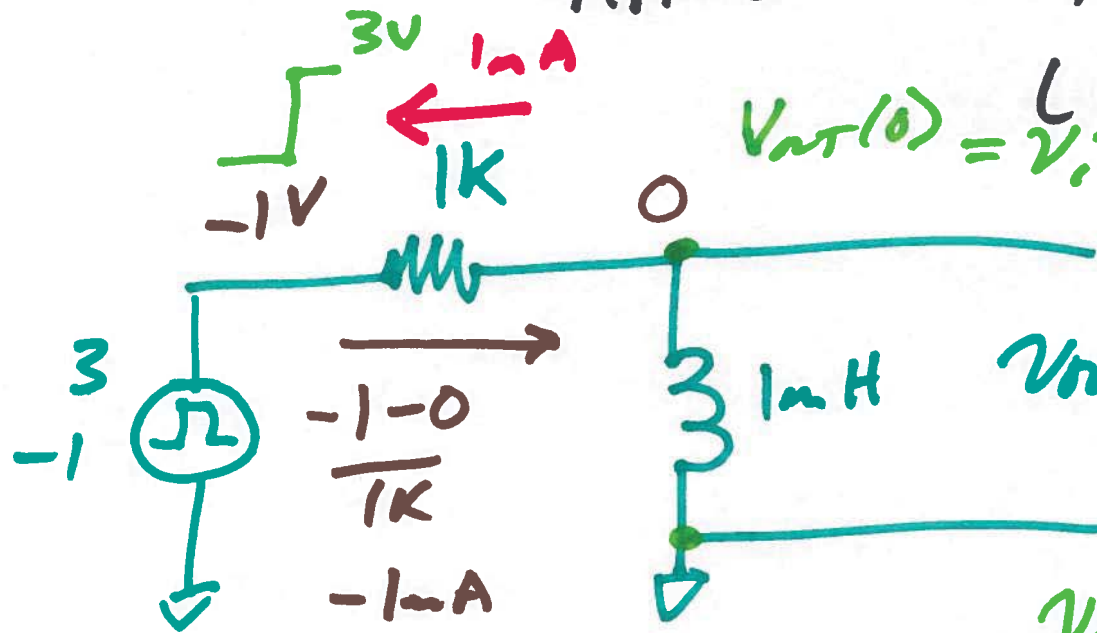


# EE 221 circuits II

MARCH 27,

Lecture 15



$$v_f = 0$$

$$v_i = 4V$$

$$v_{out}(t) = v_f + (v_i - v_f)e^{-t/\tau}$$

$$v_i - 3 = 1mA \cdot 1k$$

$$3 - v_i = (-1mA) \cdot 1k$$


$$= 0 + (4 - 0)e^{-t/4R}$$

$$= 4e^{-t/4R}$$

$$v_{out}(t) = 0 \quad t < t_0$$

$$v_{out}(t) = 4e^{-t/4R} \quad t > t_0$$

1)

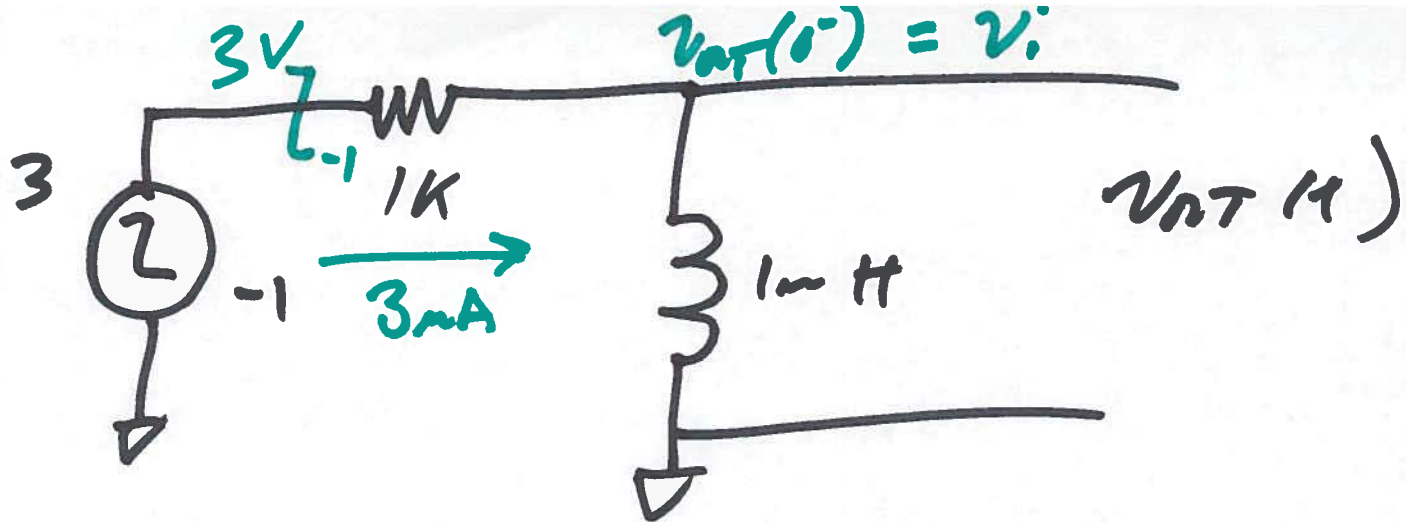

$$-1 - v_i = 3\text{mA} \cdot 1\text{k}$$



$$(v_i = -4\text{V})$$

$$v_{out}(t) = -4 e^{-\frac{(t-10\mu)}{1\text{M}}}$$

$$t \geq 10\mu$$

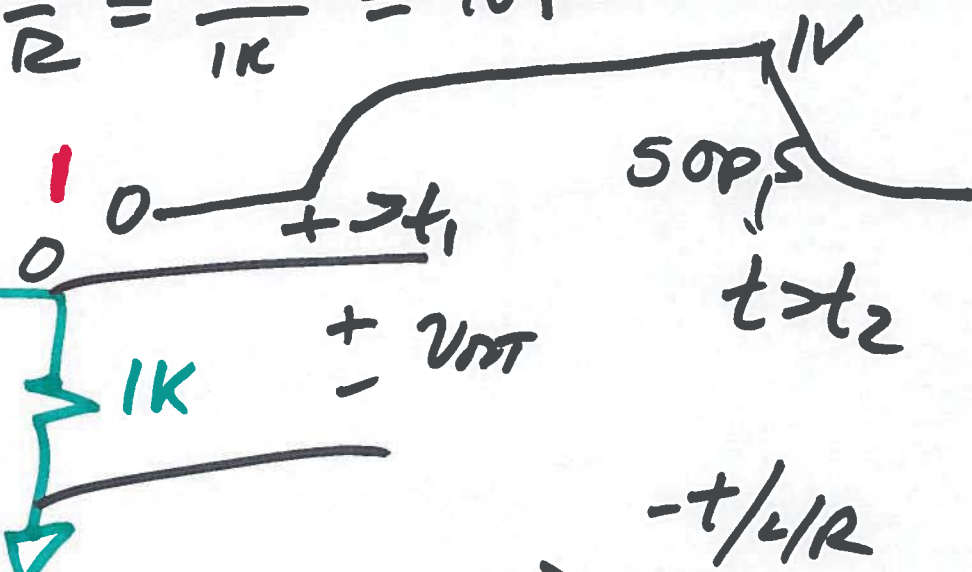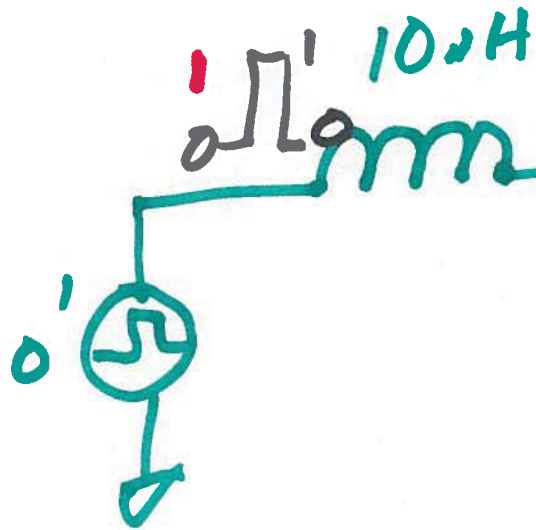2)

$$\tau = \frac{L}{R} = \frac{10\text{ nH}}{1\text{ k}} = 10\text{ ps}$$




$$v_{out}(t) = 1 + (0 - 1)e^{-t/\tau}$$


$$= 1(1 - e^{-t/\tau})$$

$$v_{out}(t) = 1e^{-t/\tau} \quad t > t_2$$

3)

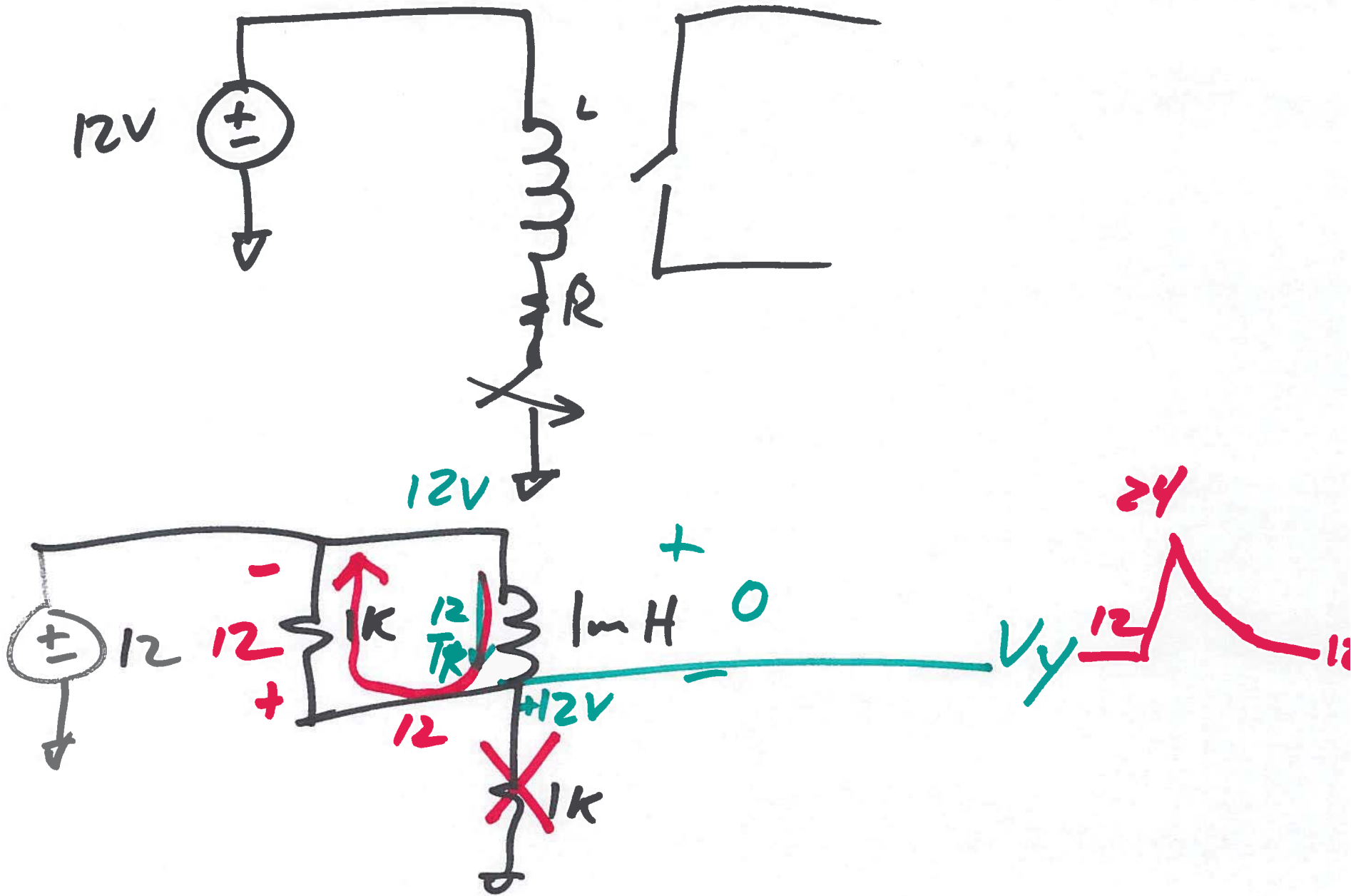



4)

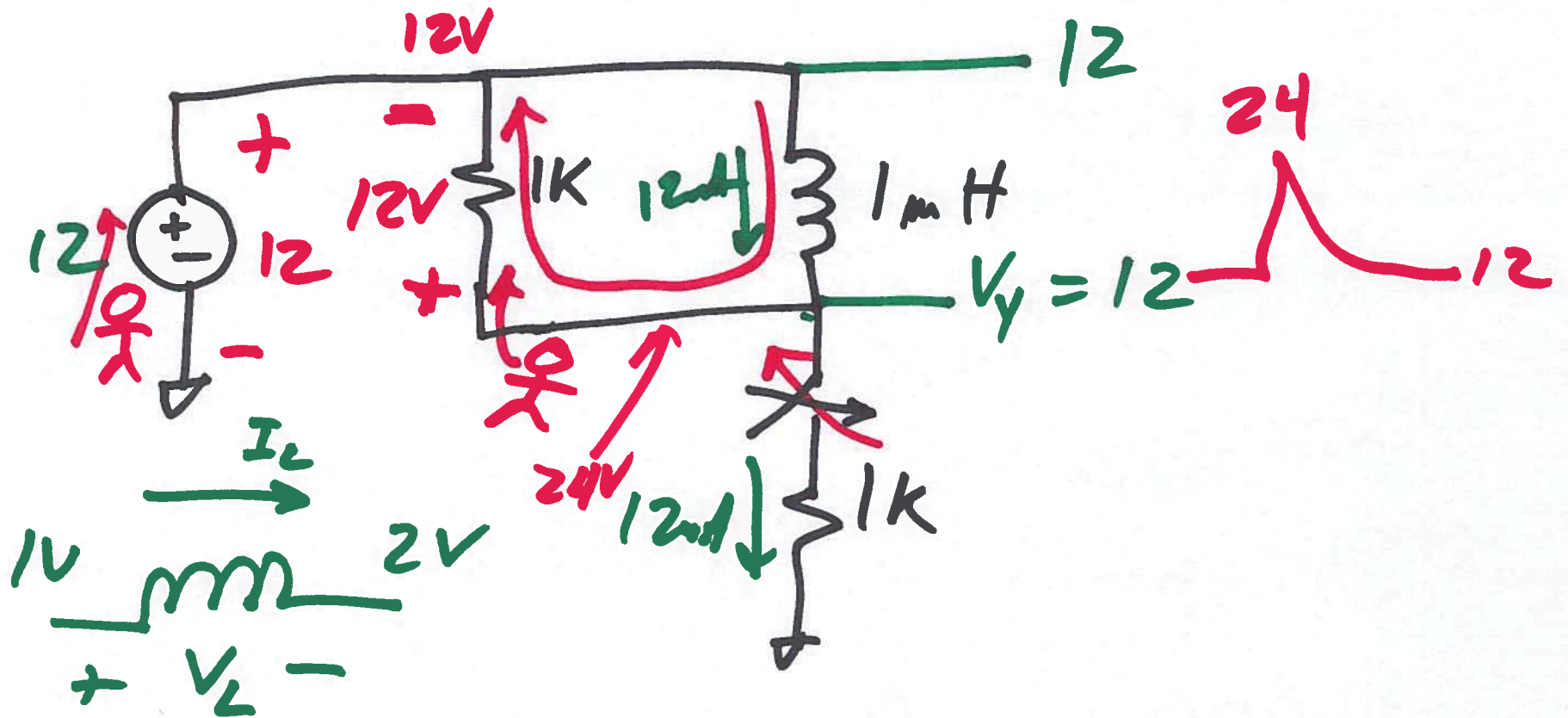

$$V_L = L \cdot \frac{dI_L}{dt}$$

$$1 - 2 = -1 = V_L = L \cdot \frac{dI_L}{dt}$$

5)

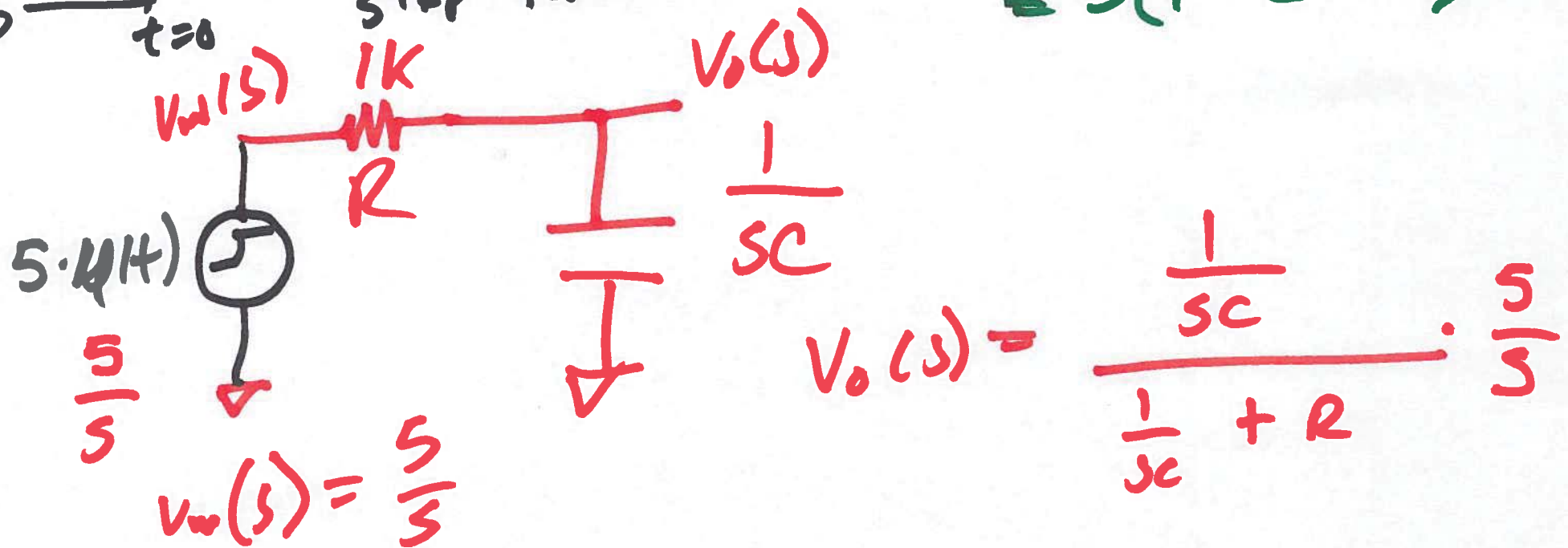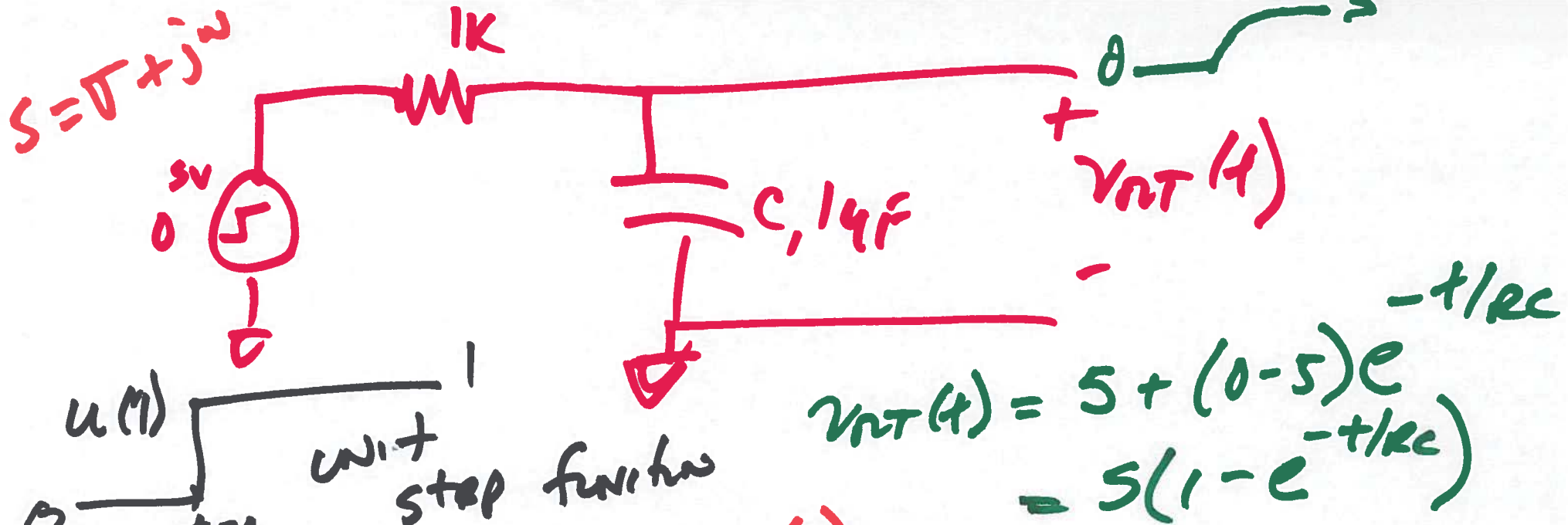

6)

$$V_0(s) = \frac{1}{1+sRC} \cdot \frac{5}{s}$$

$$= \frac{A}{1+sRC} + \frac{B}{s}$$

Partial Fraction expansion

$$s \cdot V_0(s) = \frac{A \cdot s}{1+sRC} + B$$