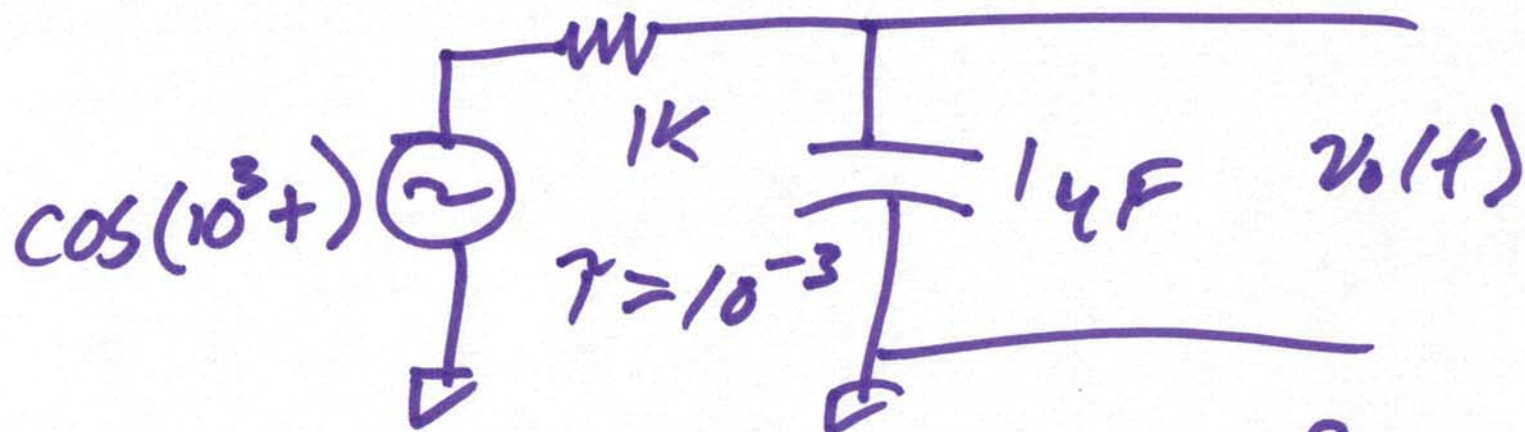


EE 221

# Circuits II

Lecture 19

April 15, 2019  $s^2$



$$V_o(s) = \frac{-\frac{1}{2}}{s + 10^3} + \frac{B}{s + j10^3} + \frac{C}{s - j10^3}$$

$$-\frac{1}{2} e^{-10^3 t} = -\frac{1}{2} e^{\frac{-t}{10^{-3}}}$$

$$V_o(s) = \left( \frac{-\frac{1}{2}}{s + j10^3} + \frac{B}{s + j10^3} + \frac{C}{s - j10^3} \right)$$

$$= \frac{s \cdot 10^3}{(s + 10^3) \cdot (s + j10^3) (s - j10^3)}$$

$s = -j10^3$   
 $s = -j10^3$

$$B = \frac{1}{(10^3 - j10^3)(-j \cdot 2 \cdot 10^3)}$$

$$= \frac{1}{2(1-j)}$$

$$V_0(s) = \frac{5 \cdot 10^3}{(s+10^3)(s+j10^3)(s-j10^3)} \quad \left| \begin{array}{l} \\ s=j10^3 \end{array} \right.$$

$$= \frac{C}{j10^3 + j10^3}$$

$$C = \frac{1}{(j10^3 + 10^3)(j \cdot 2 \cdot 10^3)}$$

$$C = \frac{1}{2(1+j)}$$

3)

$$V_o(s) = \frac{-\frac{1}{2}}{s+10^3} + \frac{\frac{1}{2(1-j)}}{s+j10^3} + \frac{\frac{1}{2(1+j)}}{s-j10^3}$$

$$v_o(t) = -\frac{1}{2}e^{-t/10^{-3}} + \frac{e^{-jt \cdot 10^3}}{(1+j)2(1-j)} + \frac{e^{jt \cdot 10^3}}{2(1+j)}$$

$$= \frac{1}{2} \left[ e^{-t/10^{-3}} + \frac{(1+j)e^{-jt \cdot 10^3}}{2} + \frac{(1-j)e^{jt \cdot 10^3}}{2} \right]$$

$$= \frac{1}{2} \left[ e^{-t/10^{-3}} + \frac{e^{-jt \cdot 10^3} + e^{jt \cdot 10^3}}{2} + j \cdot j \left( \frac{e^{-jt \cdot 10^3} - e^{jt \cdot 10^3}}{2j} \right) \right]$$


4)  $\frac{1}{2} \left[ e^{-t/10^{-3}} + \cos 10^3 t + \sin 10^3 t \right]$

$$\cos x = \frac{e^{jx} + e^{-jx}}{2}$$

$$\sin x = \frac{e^{jx} - e^{-jx}}{2j}$$


$$v_0(t) = \frac{1}{2} \left[ -e^{-t/10^{-3}} + \cos 10^3 t + \sin 10^3 t \right] u(t)$$

5)

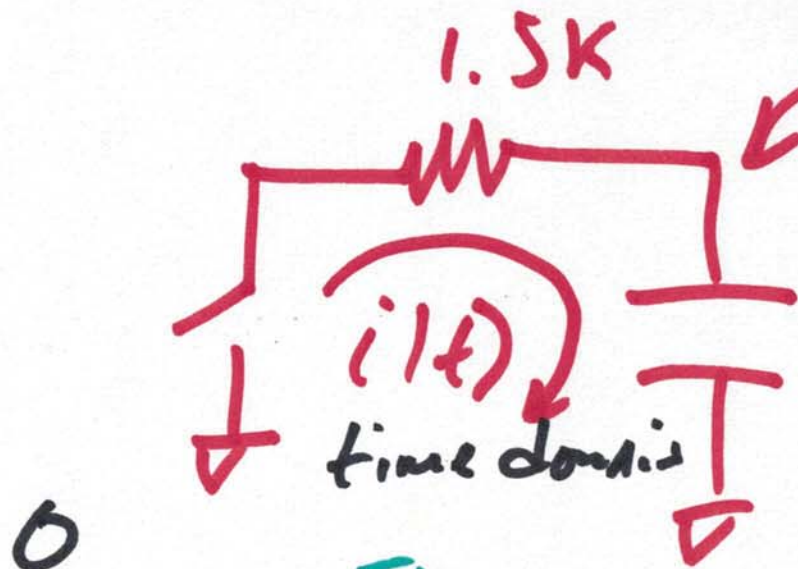

$t=0$   
 $v(0) = 1.5V$

$\tau = 1.5K \cdot 10^{-10}$

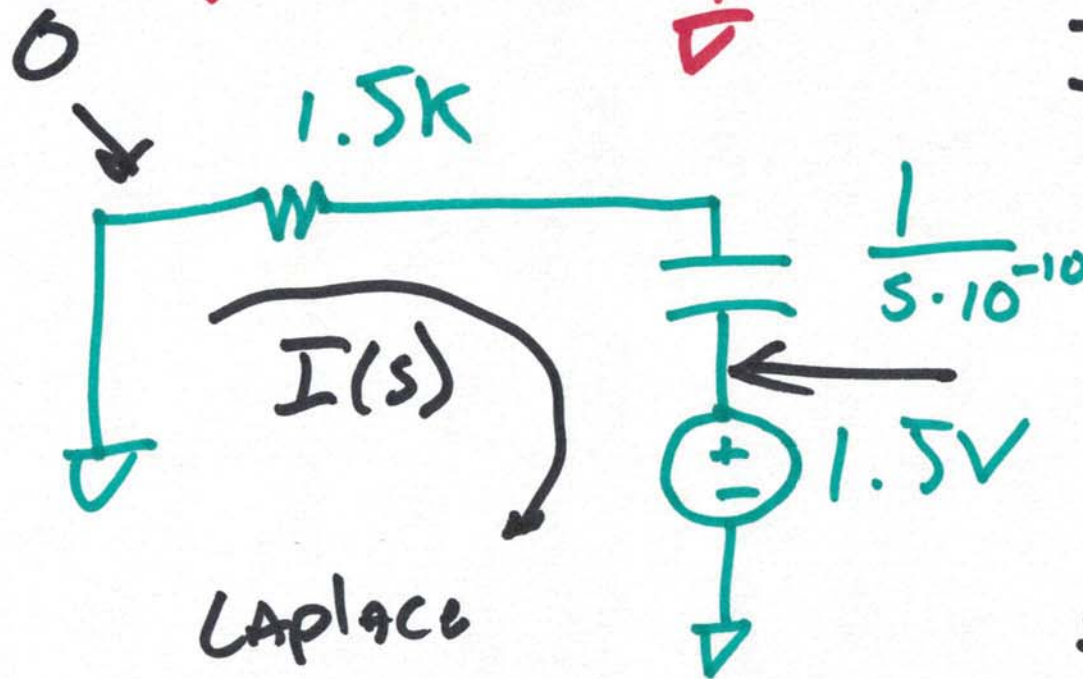

$$I(s) = \frac{0 - 1.5 \cdot \frac{1}{s}}{1.5K + \frac{1}{s \cdot 10^{-10}}}$$


$$= \frac{-1.5 \cdot s \cdot 10^{-10}}{1.5K \cdot s \cdot 10^{-10} + 1}$$


$$= \frac{-1.5 \cdot 10^{-10} \cdot s}{1.5K \cdot 10^{-10}}$$

$$\frac{s + \frac{1}{1.5K \cdot 10^{-10}}}{s + \frac{1}{1.5K \cdot 10^{-10}}}$$


$$I(s) = \frac{-10^{-3} \cdot s}{s + \frac{1}{1.5K \cdot 10^{-10}}}$$
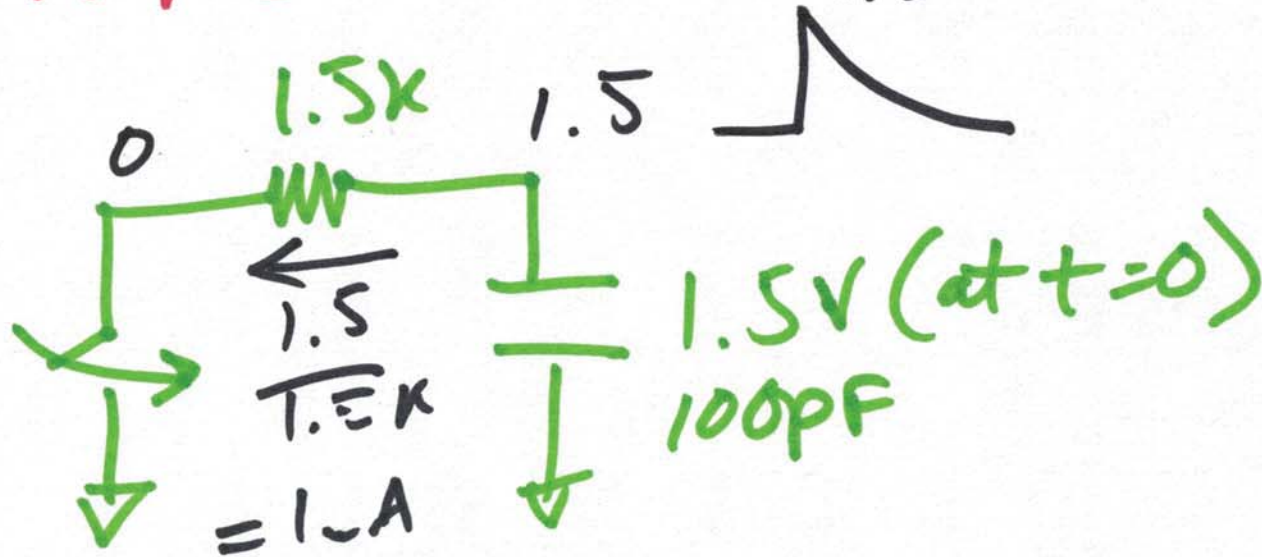
$$i(t) = -1mA \cdot e^{-\frac{t}{1.5K \cdot 10^{-10}}} \cdot u(t)$$



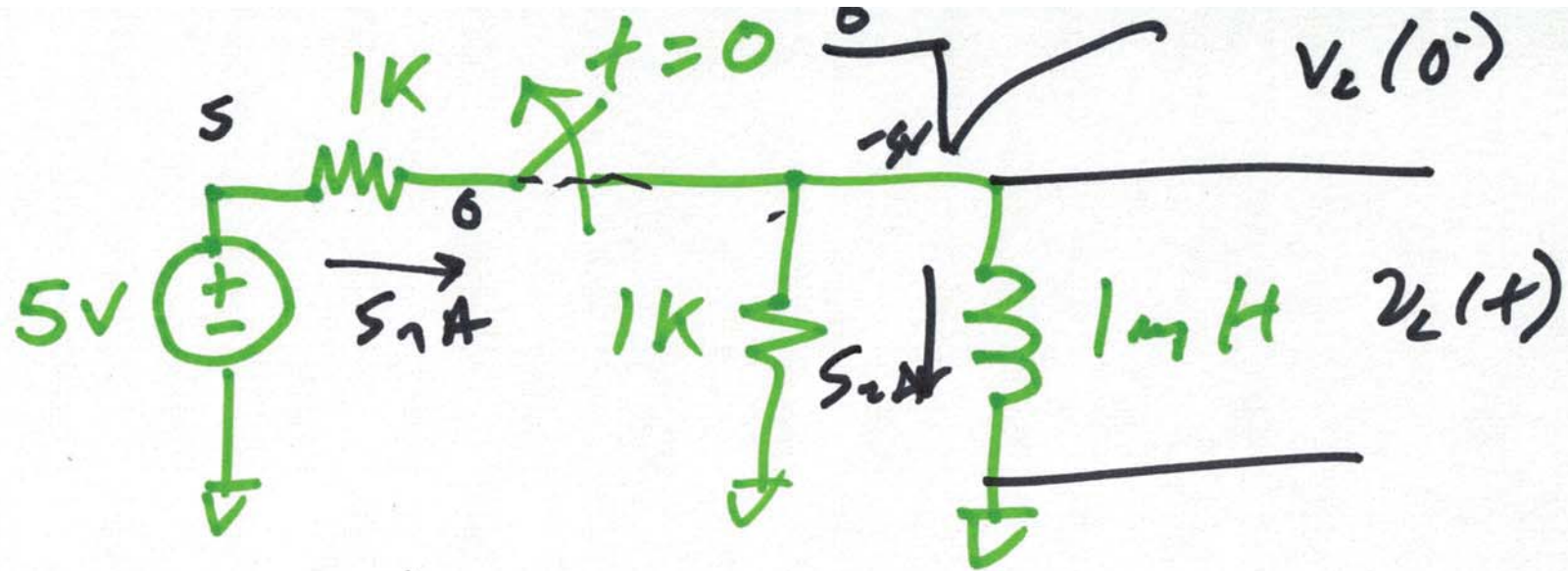

LAPLACE

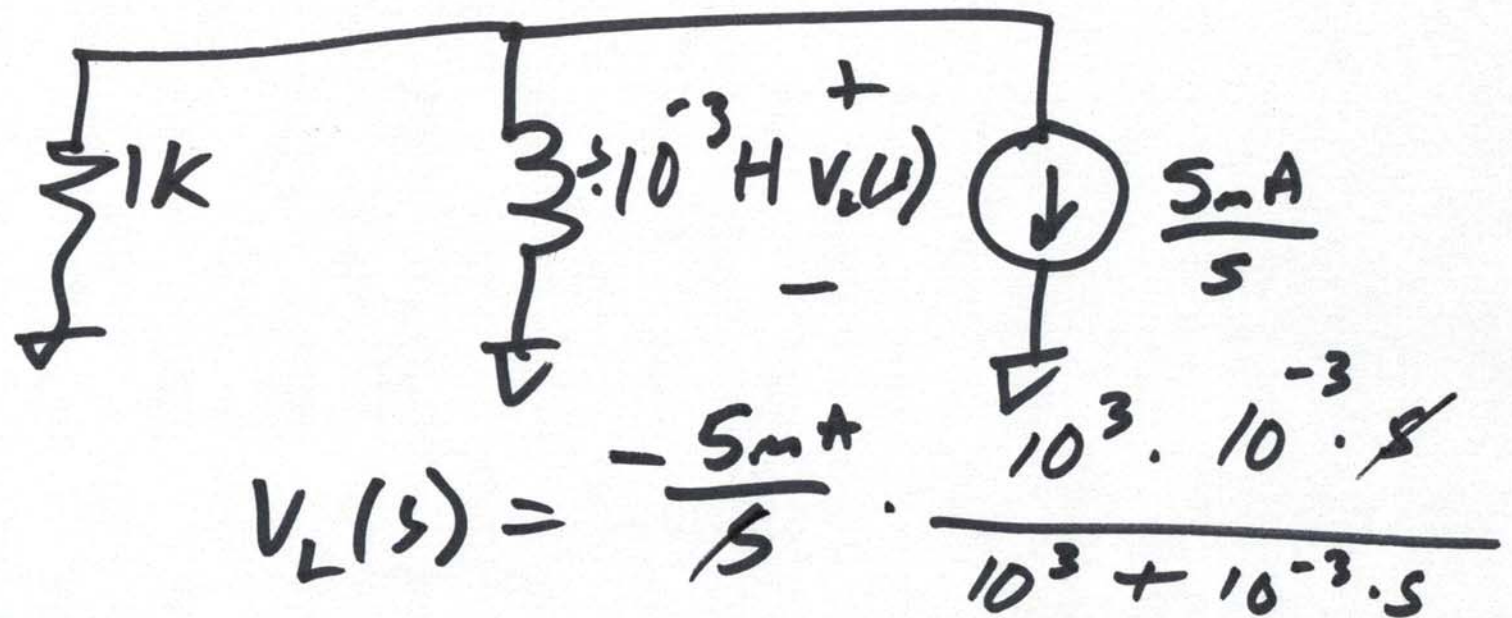


$$V_L(s) = \frac{-\frac{5mA}{s}}{10^3 + 10^{-3} \cdot s}$$

81






$$V_L(s) = -5 \text{ mA} \cdot \frac{10^3}{5 + 10^6}$$
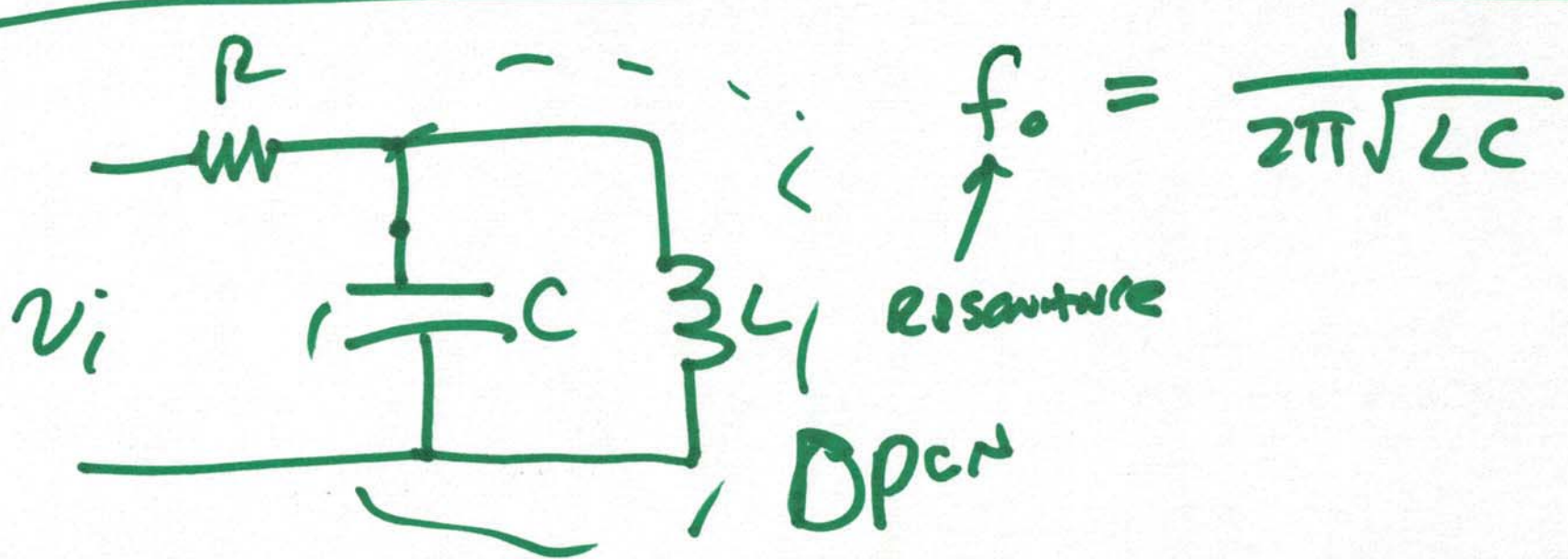
$$v_L(t) = -5 \text{ mA} \cdot 1 \text{ k} \cdot e^{-t/10^{-6}} \cdot u(t)$$



9)

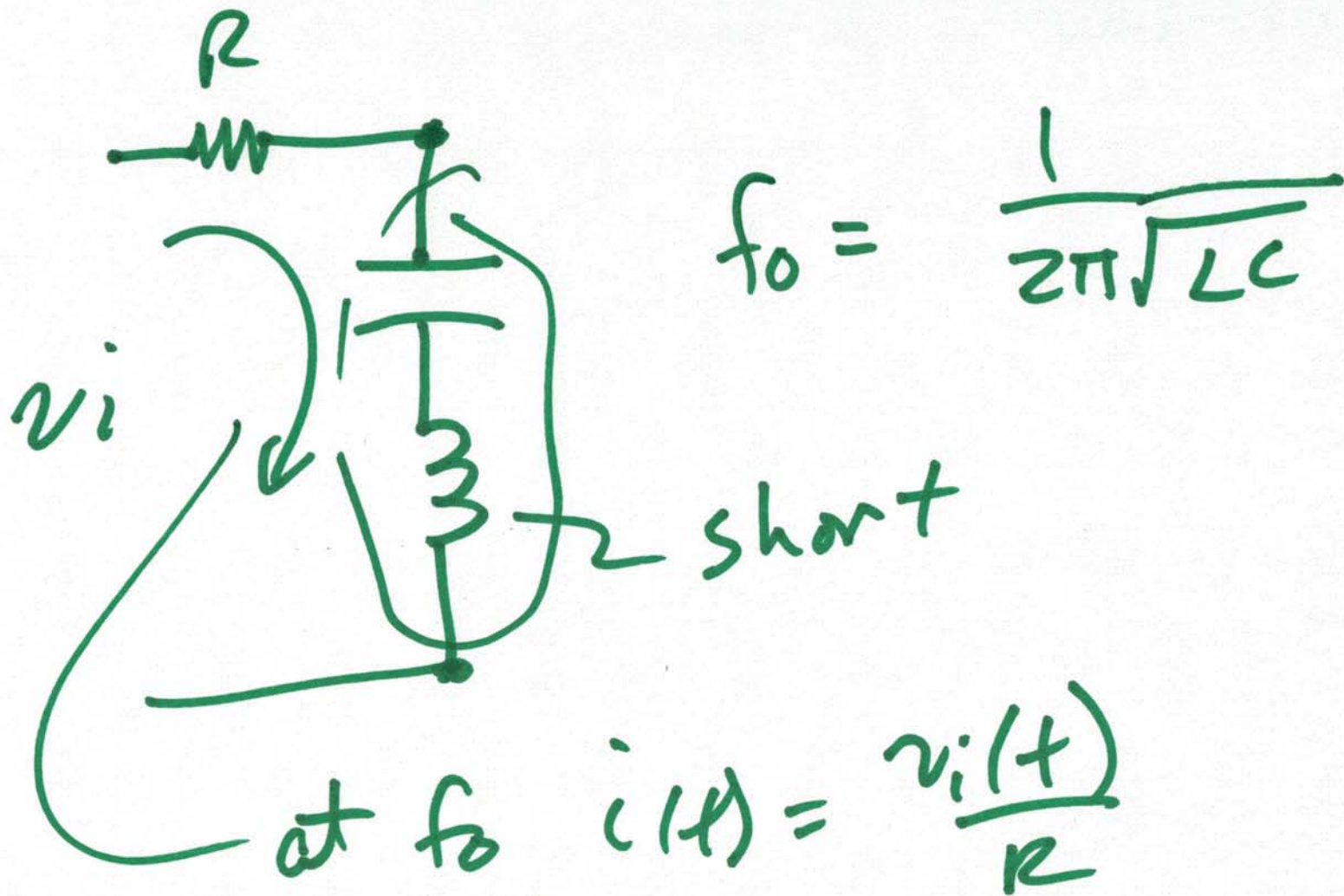

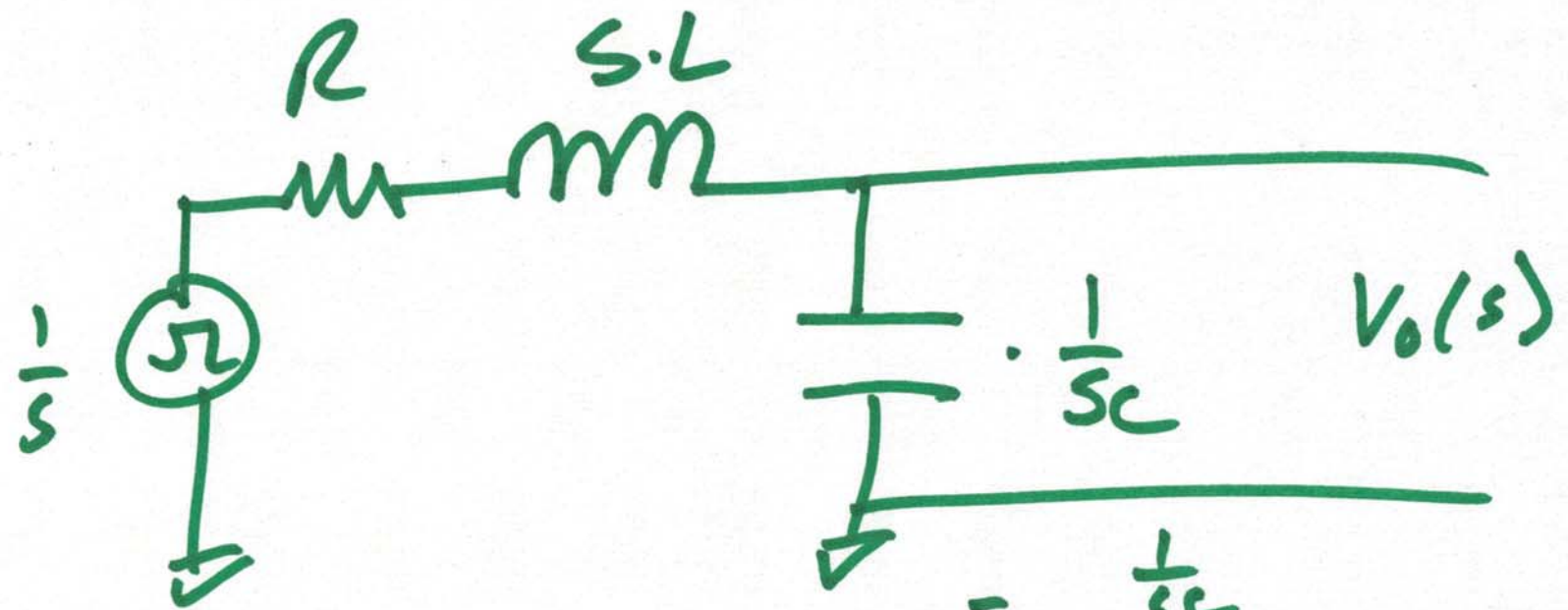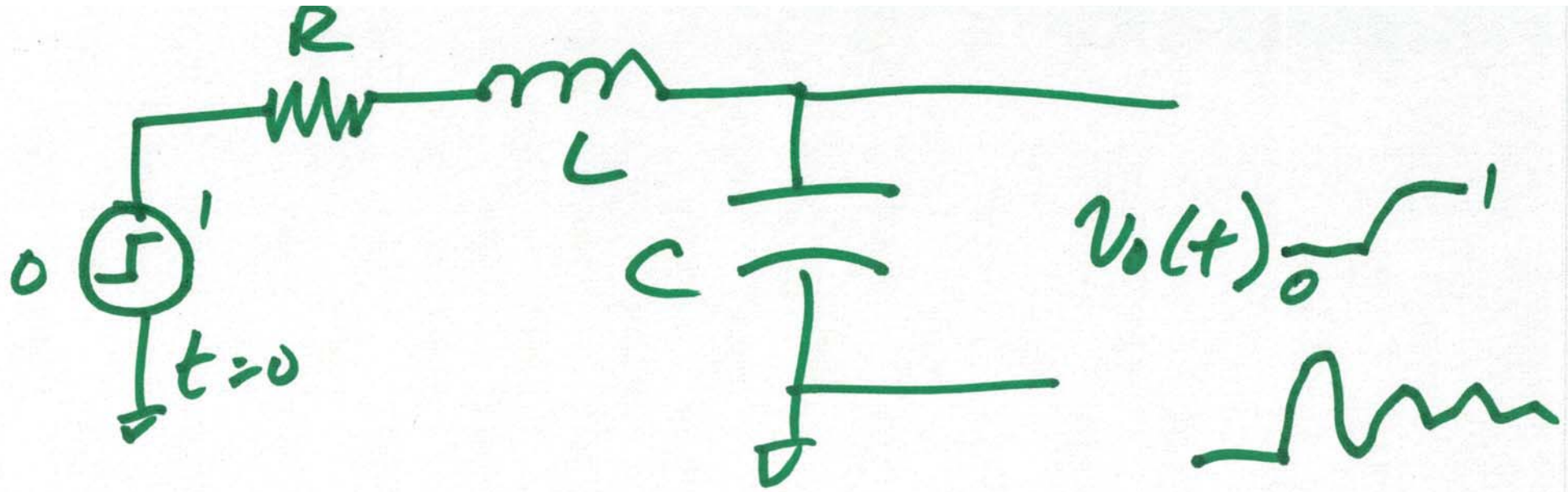

$$= \frac{\frac{1}{sC}}{\frac{1}{sC} + sL + R}$$

ii)

$$V_o(s) = \frac{1}{s} \cdot \frac{\frac{1}{sC}}{\frac{1}{sC} + sL + R}$$

$$= \frac{1}{s} \cdot \frac{1}{s^2 LC + sRC + 1}$$

$$= \frac{1}{s} \cdot \frac{\frac{1}{LC}}{s^2 + s \frac{R}{L} + \frac{1}{LC}}$$

$$s_{1,2} = \frac{-\frac{R}{L} \pm \sqrt{\frac{R^2}{L^2} - 4/LC}}{2}$$

$$V_o(s) = \frac{\frac{1}{Lc}}{s} \cdot \frac{1}{(s + s_1)(s + s_2)}$$

$$s_{1,2} = \frac{-\frac{R}{L} \pm \sqrt{\frac{R^2}{L^2} - \frac{4}{Lc}}}{2}$$

$$\frac{4}{Lc} > \frac{R^2}{L^2} \quad (\text{imaginary})$$

$$< \quad (\text{real})$$