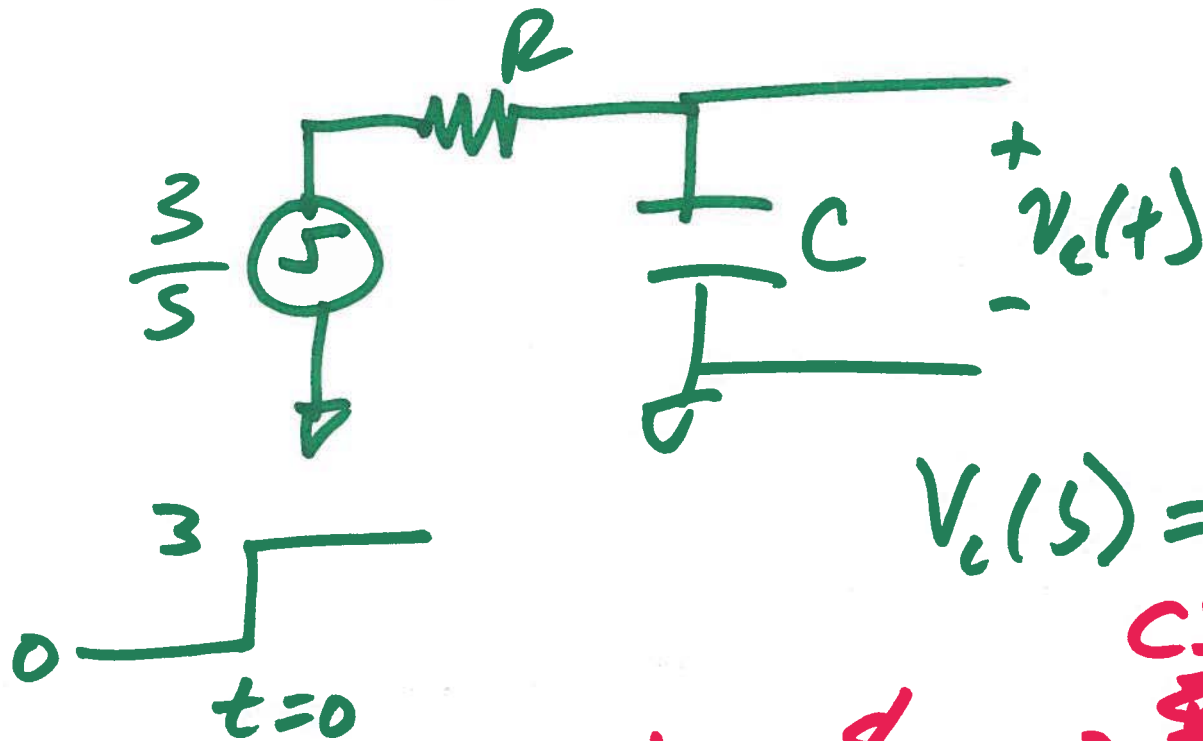


EE 221 Circuits II

April 17, 2019

Lecture 20




$$\frac{1}{1+sRC} \cdot \frac{3}{s}$$

$$\frac{\frac{1}{RC}}{\frac{1}{RC} + s} \cdot \frac{3}{s} \sin$$

$$V_c(s) = \frac{CS \cdot \frac{1}{s_0}}{CS \left(\frac{1}{sC} + R \right)}$$

$$V_c(s) = \frac{3}{s + \frac{1}{RC}} \rightarrow 3 \cdot \frac{1}{s + \frac{1}{RC}}$$

1)

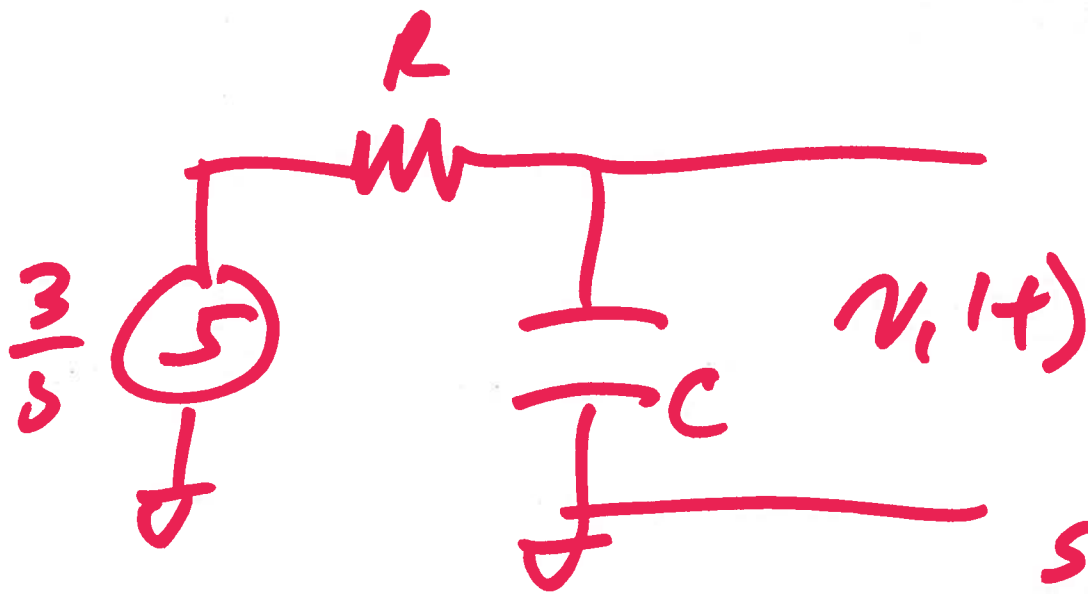

$$V_c(s) = \frac{\frac{3}{s}}{R \left(\frac{1}{sC} + R \right)} \cdot \frac{3}{s}$$

$$= \frac{\frac{1}{RC}}{\frac{1}{RC} + s} \cdot \frac{3}{s}$$

$$= \frac{A}{s} + \frac{B}{s + \frac{1}{RC}}$$

2)

$$\cancel{s} \left(\frac{\frac{1}{RC}}{\frac{1}{RC} + s} \cdot \cancel{\frac{3}{s}} \right) = \frac{A \cancel{s}}{\cancel{s}} + \frac{B}{s + \frac{1}{RC}}$$

$$A = \frac{\frac{1}{RC} \cdot 3}{\frac{1}{RC} + 0} = \boxed{3 = A}$$

$$\frac{1}{RC} + s \left(\frac{\frac{1}{RC}}{\frac{1}{RC} + s} \cdot \frac{3}{s} \right) = \left(\frac{A \cdot \frac{1}{RC} + \cancel{0}}{\cancel{s}} + \frac{B}{s + \frac{1}{RC}} \right)$$

$$B = \frac{\frac{1}{RC} \cdot 3}{-\frac{1}{RC}} \Rightarrow \boxed{B = -3}$$


$$V_c(s) = \frac{3}{s} + \frac{-3}{s + \frac{1}{RC}}$$

$$\frac{1}{s} \rightarrow u(t), \quad \frac{1}{s + \frac{1}{RC}} \rightarrow e^{-t/RC} u(t)$$

$$\rightarrow v_c(t) = 3u(t) - 3e^{-t/RC} u(t)$$


$$v_c(t) = 3(1 - e^{-t/RC})u(t)$$

for $t \geq 0$

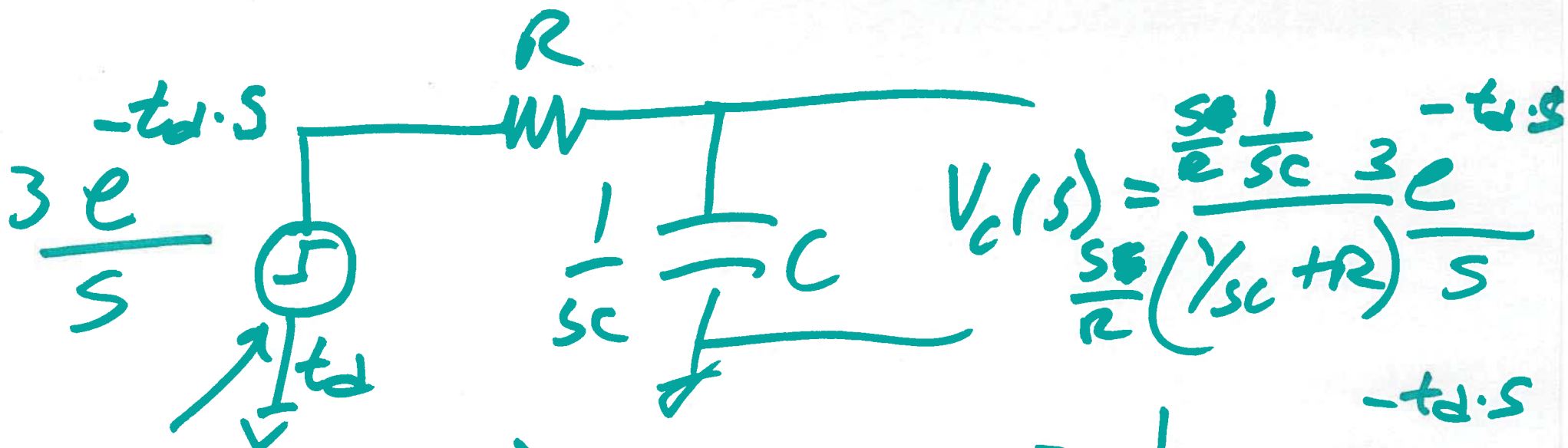

$$3u(t - t_d)$$
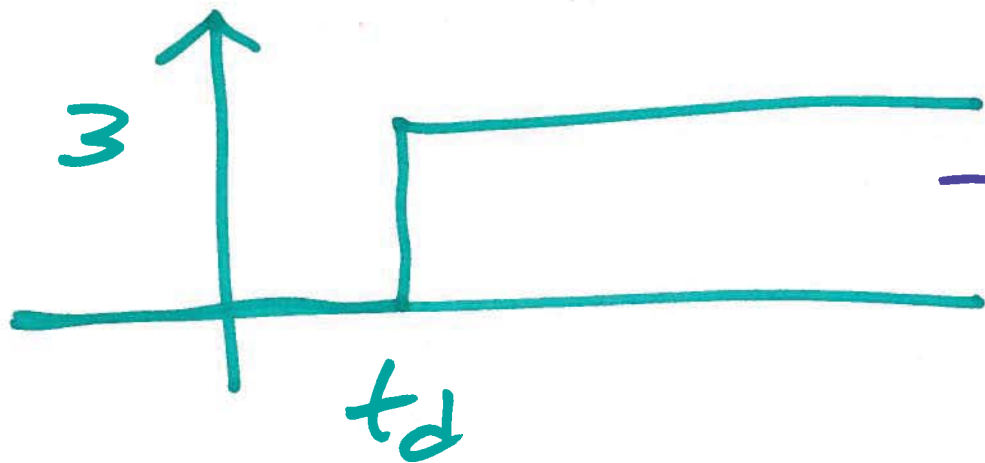
$$V_c(s) = \frac{3 \frac{1}{RC} \cdot e^{-t_d \cdot s}}{(s + \frac{1}{RC})s}$$



$$\rightarrow v_f + (v_i - v_f) e^{-\frac{t-t_d}{RC}}$$

$$3 \quad t > t_d$$

5)

$$V_1(s) = \left(\frac{\frac{3}{RC} e^{-t_d \cdot s}}{(s + \frac{1}{RC})s} \right)^{s + \frac{1}{RC}} = \left(\frac{A}{s} + \frac{B}{s + \frac{1}{RC}} \right)^{s + \frac{1}{RC}}$$

$s = -\frac{1}{RC}$

$$A = 3$$

$$B = \frac{\frac{3}{RC} \cdot e^{-t_d(-\frac{1}{RC})}}{-\frac{1}{RC}}$$

$$B = -3 e^{t_d/RC}$$


6)

$$V_1(s) = \frac{3}{s} + \frac{-3e^{-t_d/RC}}{s + \frac{1}{RC}}$$

$$\frac{3}{s} \rightarrow 3u(t), \quad \frac{-3e^{-t_d/RC}}{s + \frac{1}{RC}} \rightarrow -3e^{-\frac{t-t_d}{RC}} u(t-t_d)$$


$$-3e^{-\frac{t-t_d}{RC}} \cdot u(t-t_d)$$
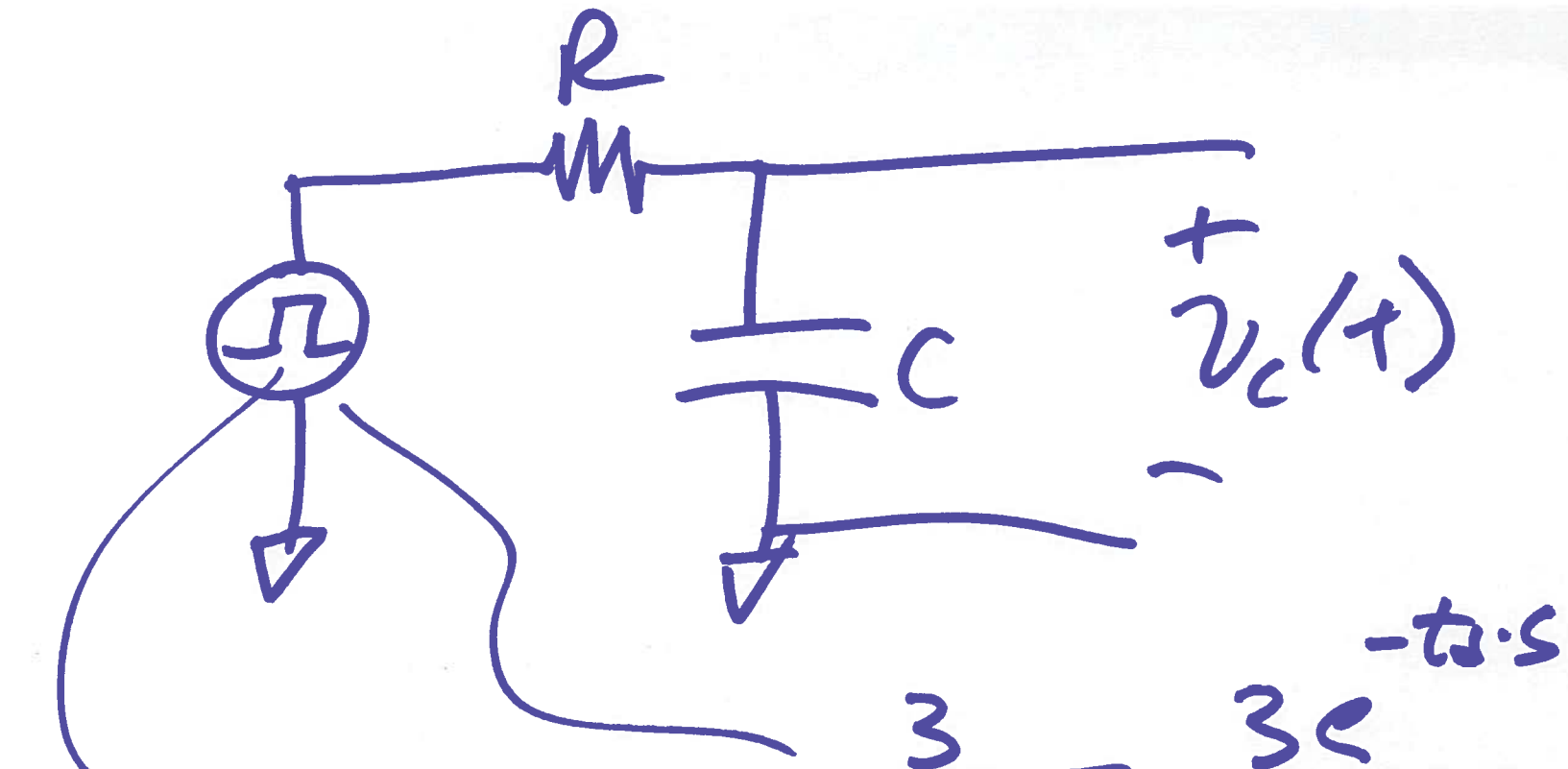
$$v_1(t) = 3u(t) - 3e^{-\frac{t-t_d}{RC}} u(t-t_d)$$



$$\frac{3}{s} - \frac{3e^{-t_d \cdot s}}{s}$$
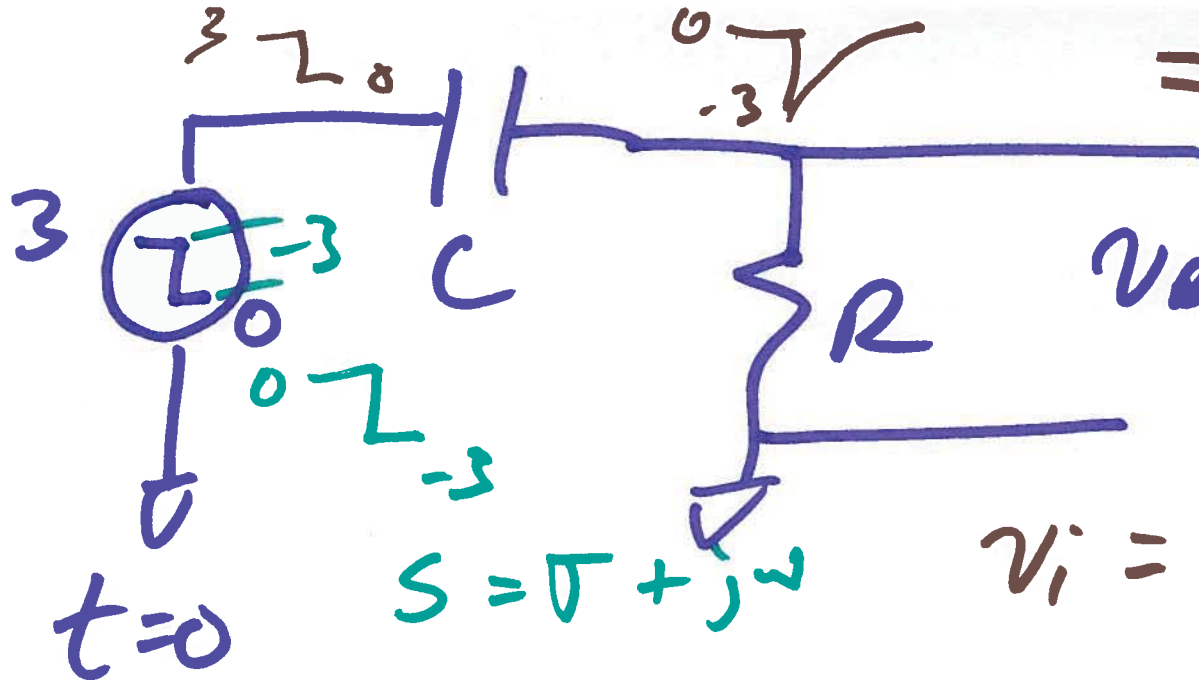
$$\rightarrow [u(t) - u(t - t_d)] \cdot 3$$



$$= v_f + (v_i - v_f)e^{-t/RC}$$

$$v_R(t) = -3e^{-t/RC}$$

$$t > 0$$

$$s = \sigma + j\omega$$

$$v_i = -3, v_f = 0$$

$$V_R(s) = \frac{R}{R + \frac{1}{sC}} \cdot \frac{-3}{s} = \frac{-3}{s + \frac{1}{RC}}$$

$$V_R(s) = \frac{-3}{s + \frac{1}{RC}}$$


$$= -3e^{-t/RC} \cdot u(t)$$

$$\frac{1}{a/b} = a$$

$$\frac{1}{a/b} = \frac{b}{a} \cdot \frac{a}{b} = \frac{cd}{fg}$$

$$b = \frac{afg}{cd}$$

a)

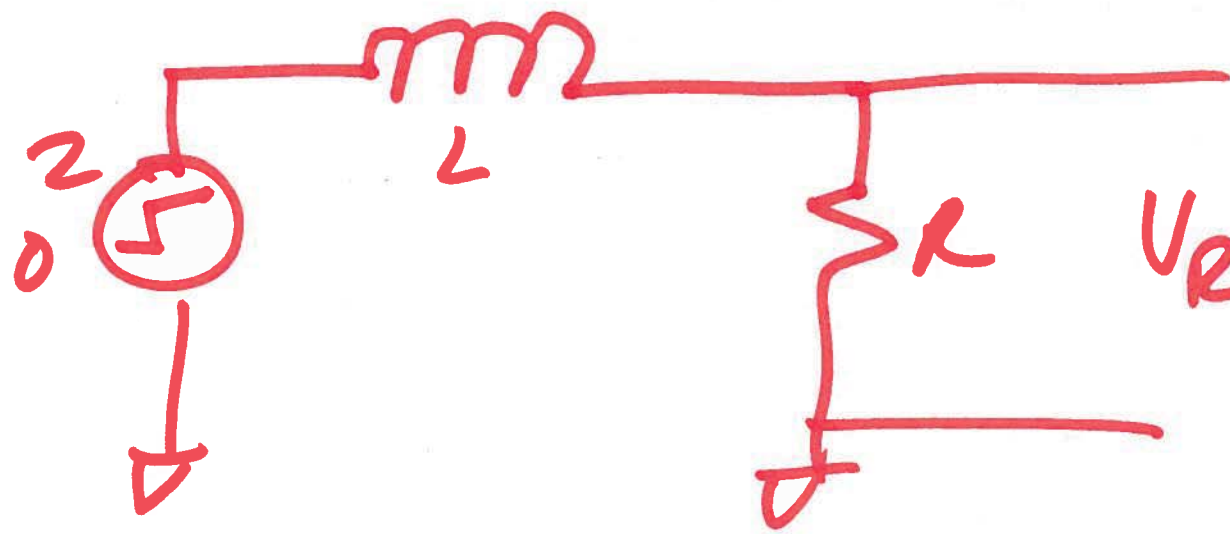

$$2(1 - e^{-t/4R})$$


$$V_R(t) = 2 - 2e^{-t/4R}$$

$$V_R(s) = \frac{R}{R + sL} \cdot \frac{2}{s} = \frac{2}{s} \cdot \frac{R/L}{s + R/L}$$

$$\frac{2}{s} \cdot \frac{R/L}{s + R/L} = \frac{A}{s} + \frac{B}{s + R/L}$$

$$A = 2, \quad B = \frac{2 \cdot R/L}{-R/L} = -2$$
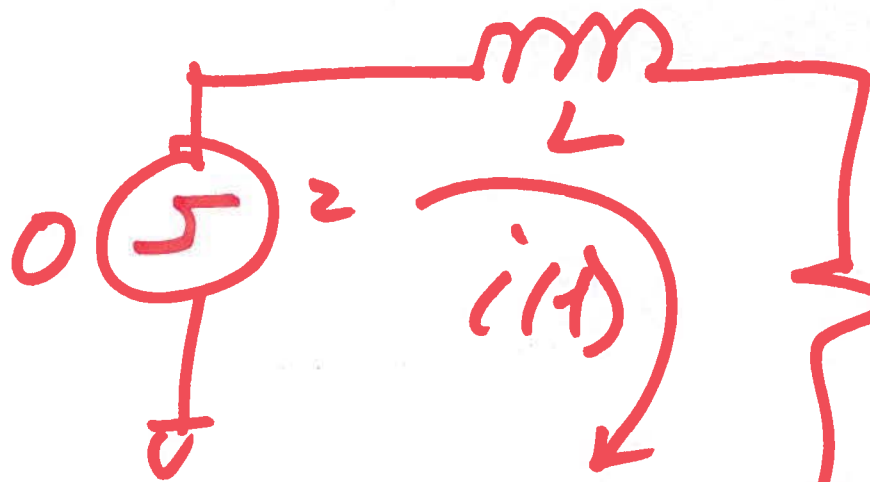
$$10) \quad V_R(t) = \frac{2}{s} + \frac{-2}{s + R/L} \rightarrow 2u(t) - 2e^{-t/4R} \cdot u(t)$$



$$\frac{2}{s} + \frac{-\frac{2}{R}}{s + R/L}$$



$$i(t) = \frac{2}{R} u(t) - \frac{2}{R} e^{-t/4/R}$$


$$I(s) = \frac{\frac{2}{s}}{sL + R} = \frac{2}{R} (1 - e^{-t/4/R})$$

$$= \frac{2}{s(sL + R)} = \frac{2/L}{s(s + R/L)} = \frac{A}{s} + \frac{B}{s + R/L}$$

$$A = \frac{2}{R}, \quad B = \frac{2/L}{-\frac{R}{L}} = -\frac{2}{R}$$

11)

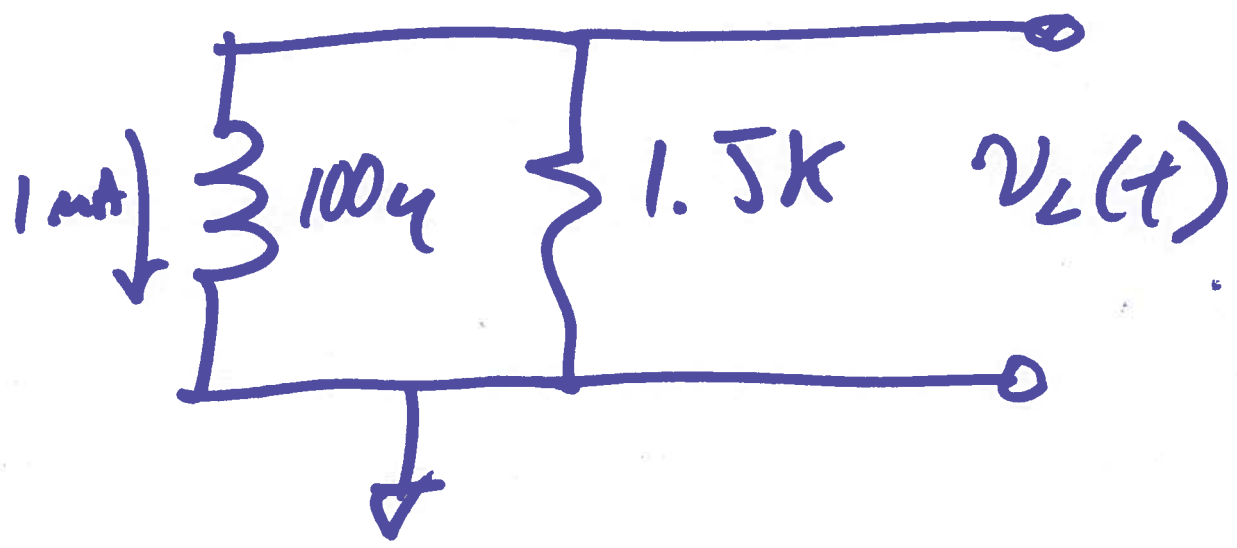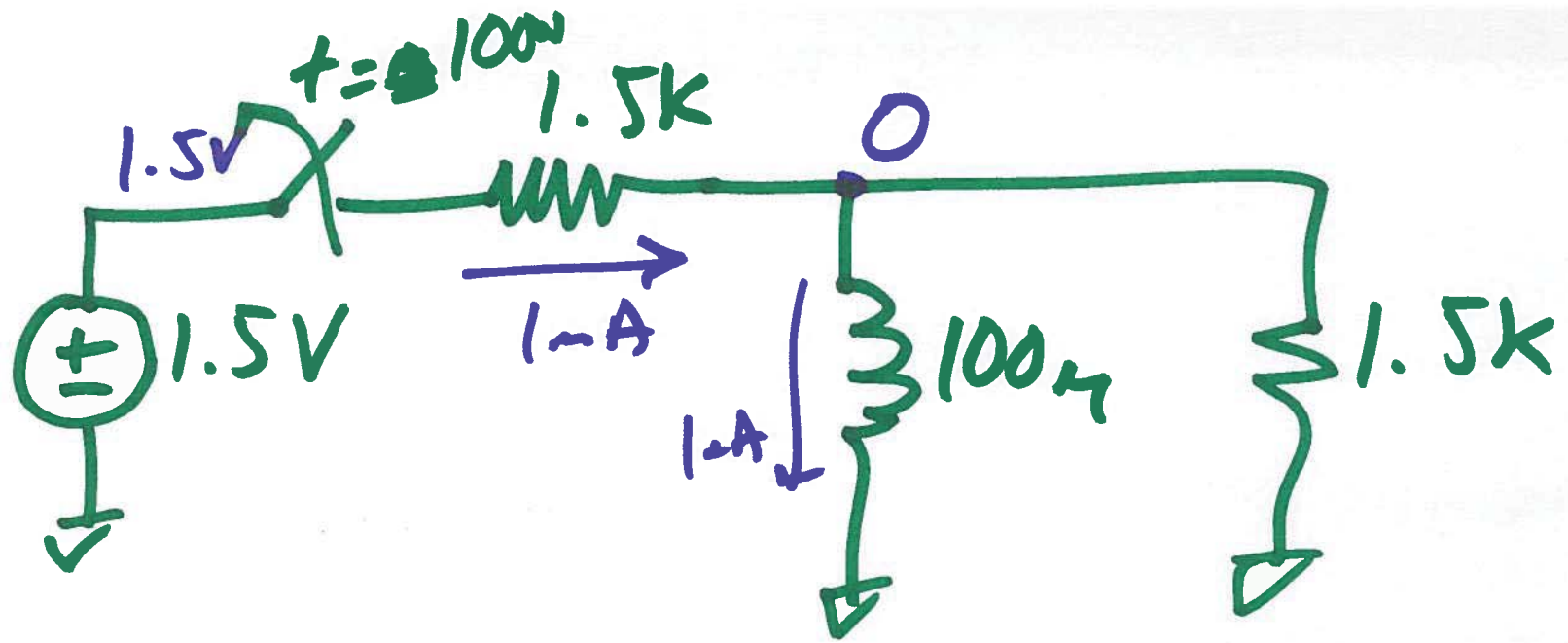

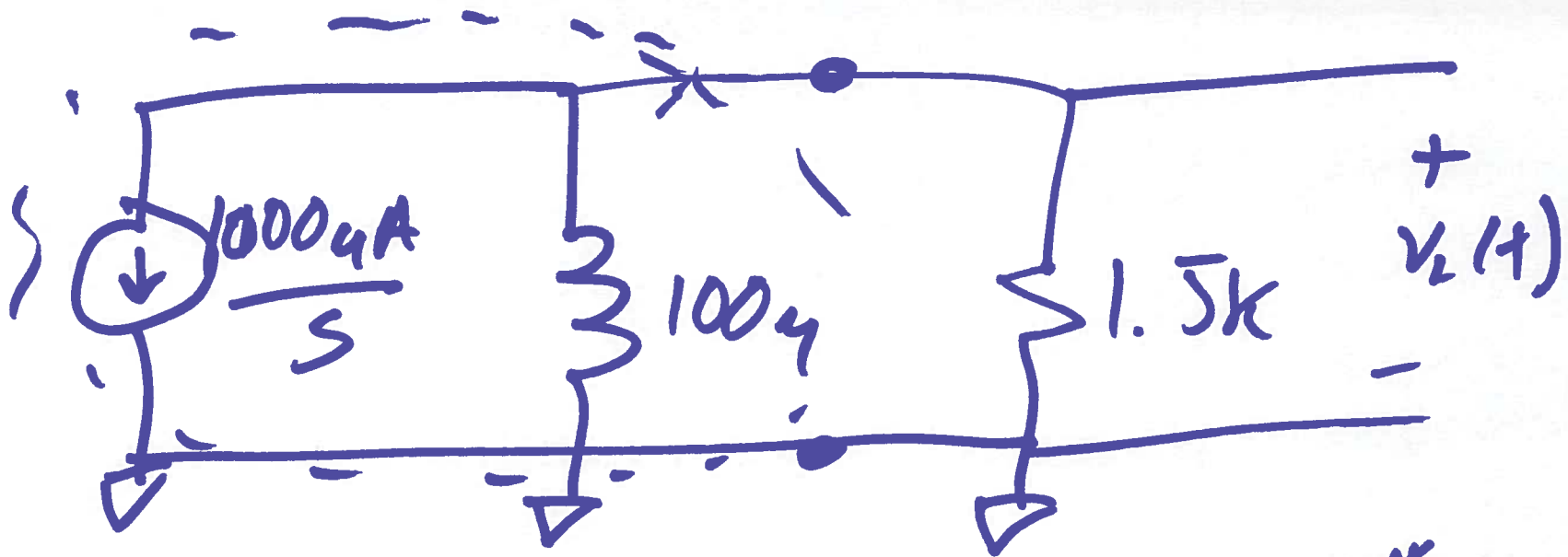

$$V_L(s) = \frac{-10 \mu A}{s} \cdot \frac{1.5k \cdot 8 \cdot 10^{-4}}{1.5k + 5 \cdot 10^{-4}}$$


$$\frac{L}{R} = \frac{100 \mu C}{1.5k} = 66 \text{ nS}$$

$$15 \cdot 10^6 = \frac{1}{R} \cdot 0 \rightarrow -1.5 \text{ V}$$


$$\rightarrow \underline{\underline{-1.5 \text{ V} e^{-\frac{t}{15 \cdot 10^{-6}}}}}$$

$$V_L(s) = \frac{-1 \mu A \cdot 1.5k}{s + 15 \cdot 10^6}$$

13)

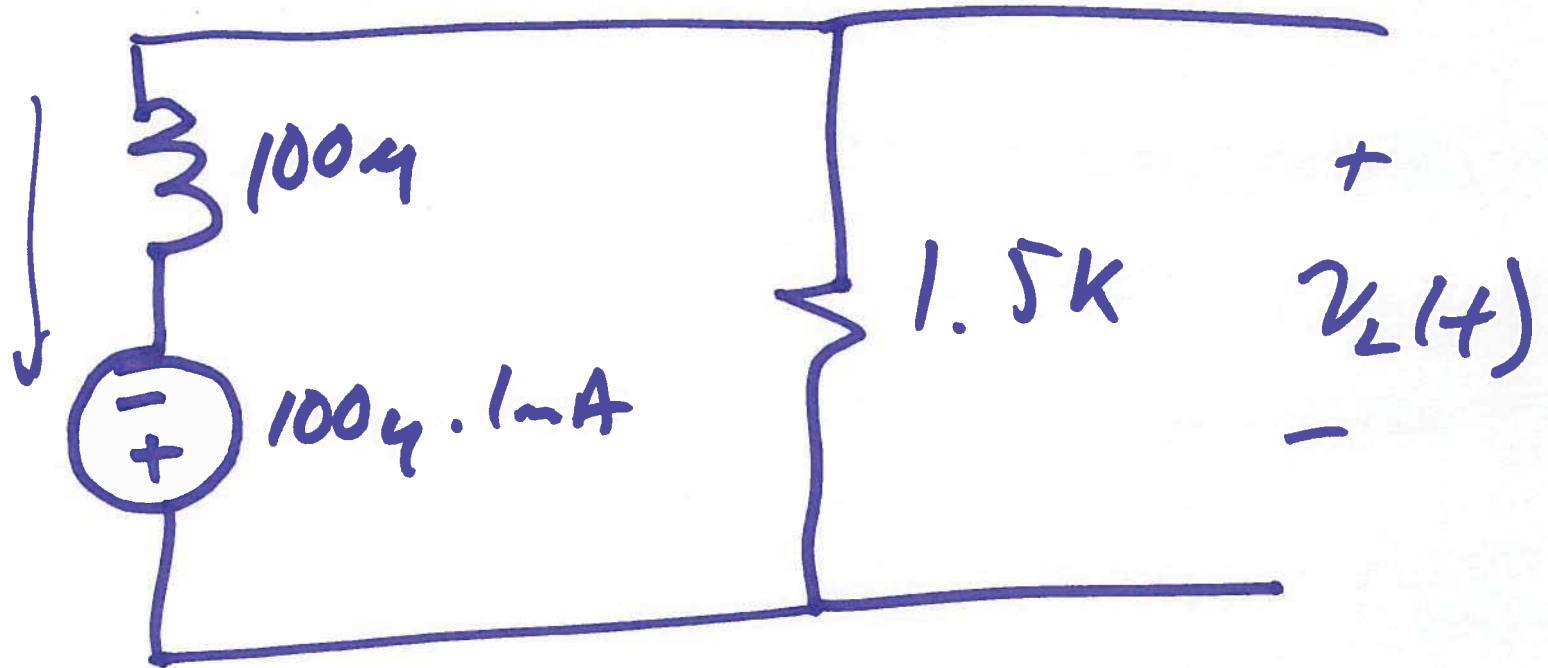
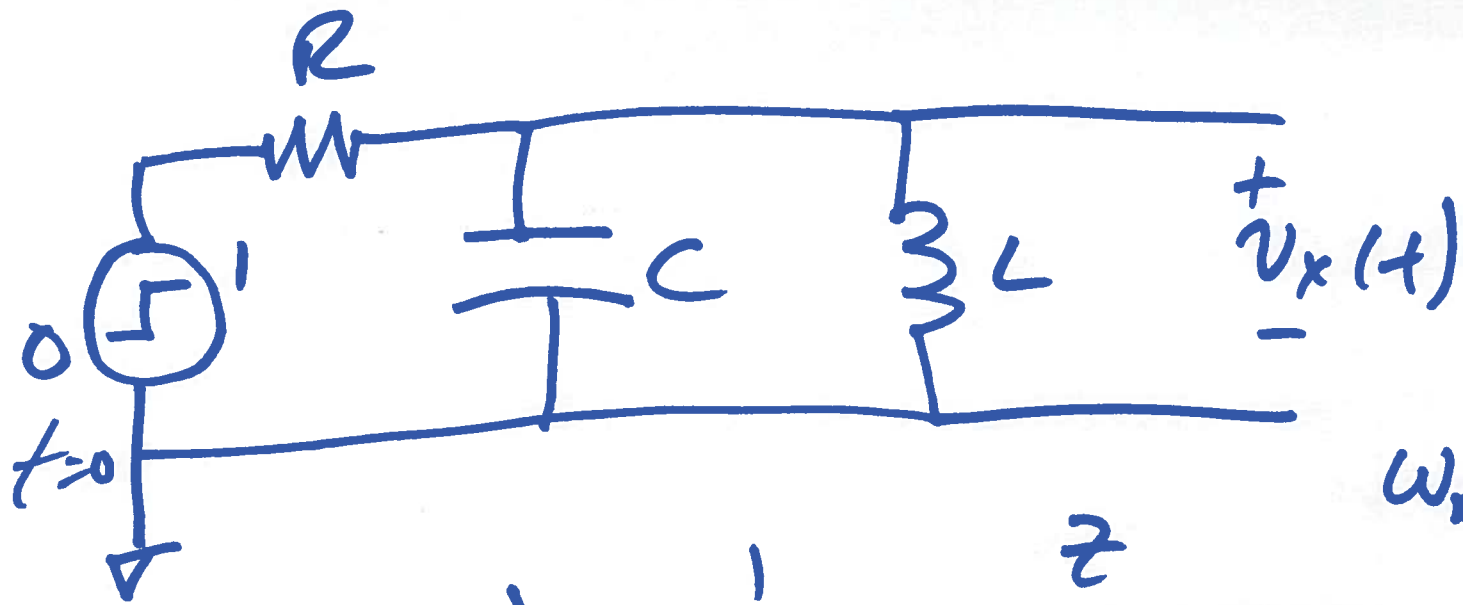
$$\begin{aligned}
 V_L(s) &= -100\ \mu\text{A} \cdot \frac{1.5\ \text{k}\Omega}{1.5\ \text{k}\Omega + s \cdot 100\ \Omega} \\
 &= \frac{-1.5\ \text{V}}{s + \frac{1.5\ \text{k}\Omega}{100\ \mu\text{s}}} \rightarrow -1.5 e^{-t/4\ \mu\text{s}}
 \end{aligned}$$



$$V_x(s) = \frac{1}{s} \cdot \frac{z}{z + R}$$

$$\omega_{res} = \frac{1}{\sqrt{LC}}$$

$$f_{res} = \frac{1}{2\pi\sqrt{LC}}$$

$$z = \frac{sL \cdot \frac{1}{sC}}{sL + \frac{1}{sC}} = \frac{sL}{s^2LC + 1}$$

$$V_x(s) = \frac{1}{s} \frac{\frac{s/c}{s^2 + 1/LC}}{s/c / (s^2 + 1/LC) + R}$$

$$V_x(s) = \frac{1}{s} \cdot \frac{\frac{s}{E}}{\frac{s}{C} + s^2 R + \frac{R}{LC}}$$

$$= \frac{1}{s + s^2 RC + \frac{R}{L}}$$

$$s_1, s_2 = \frac{-\frac{1}{RC} \pm \sqrt{\left(\frac{1}{RC}\right)^2 - \frac{4}{LC}}}{2} \cdot \frac{1}{RC}$$

$$= \frac{s^2 + s \cdot \frac{1}{RC} + \frac{1}{LC}}$$

$$= \frac{\frac{1}{RC}}{(s + s_1)(s + s_2)}$$