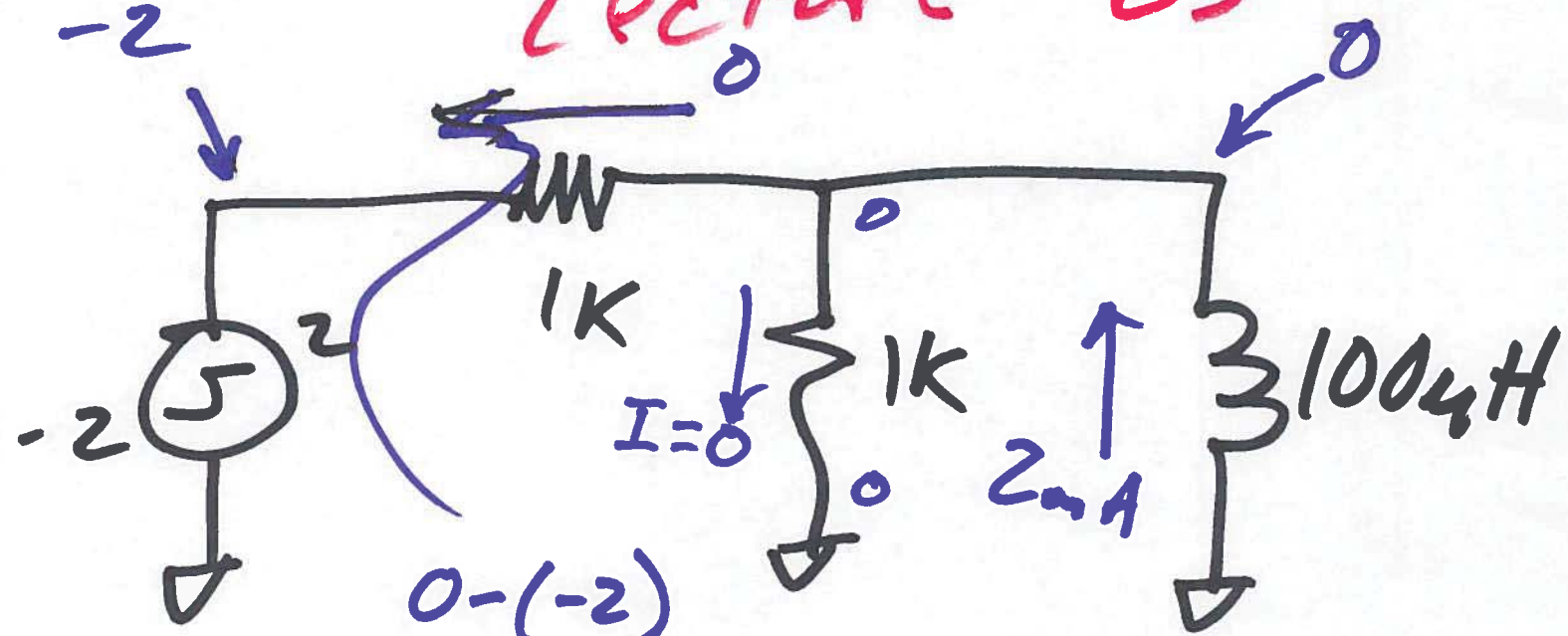


Circuits II

EE 221

April 29, 2019



Lecture 23




$$\frac{0 - (-2)}{1k} = 2mA$$

Before switch is


1)

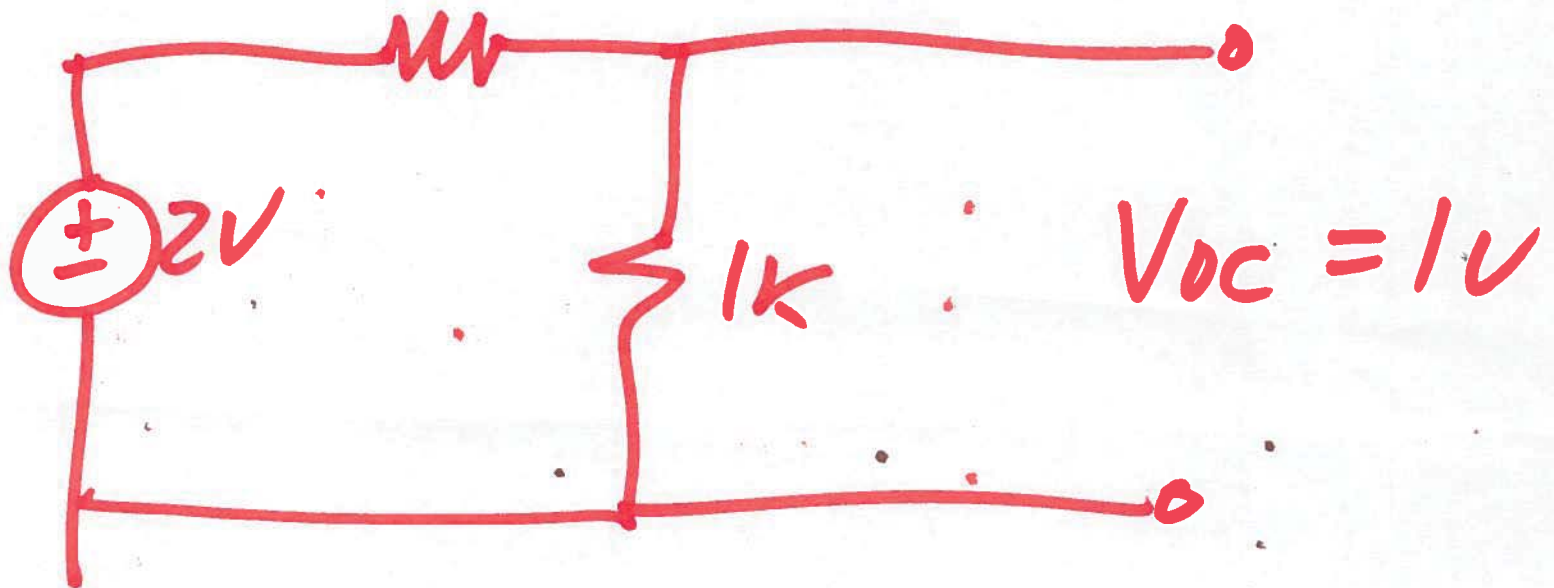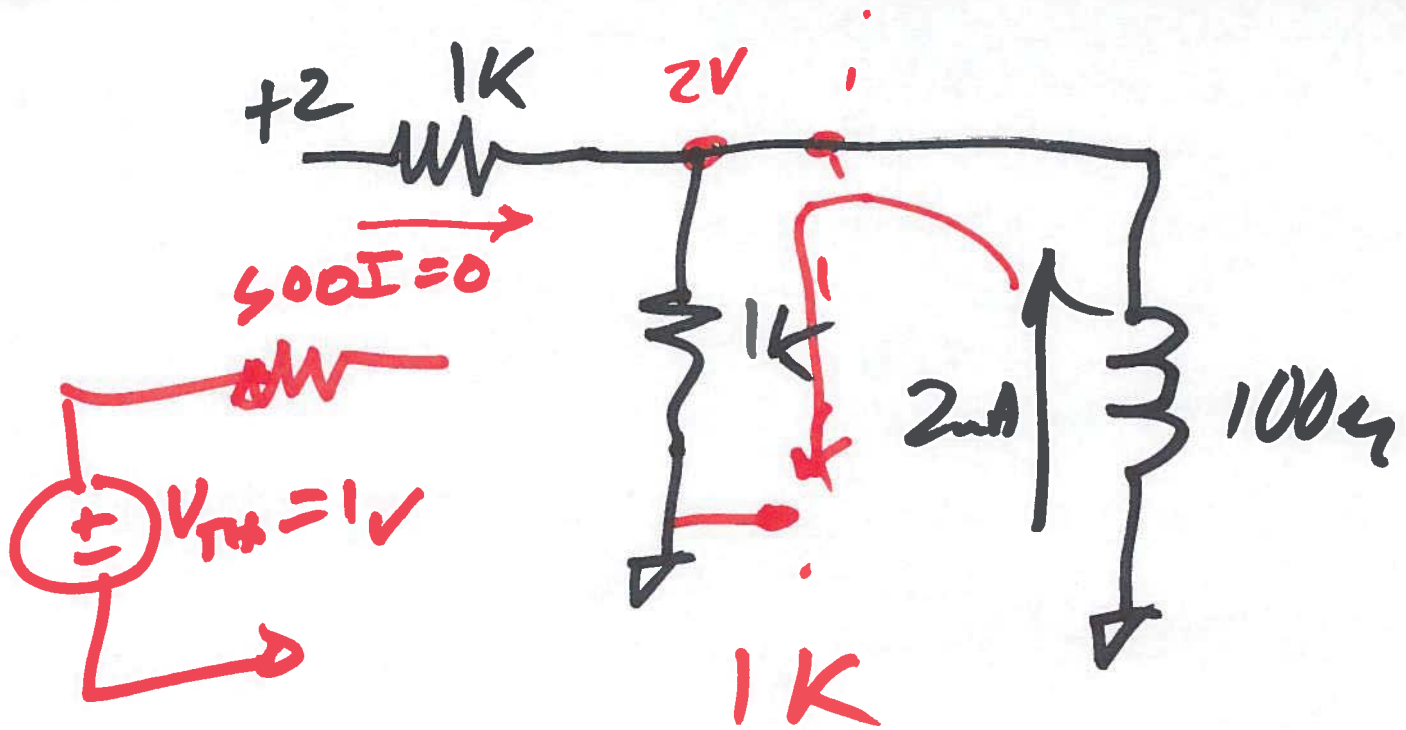

2)

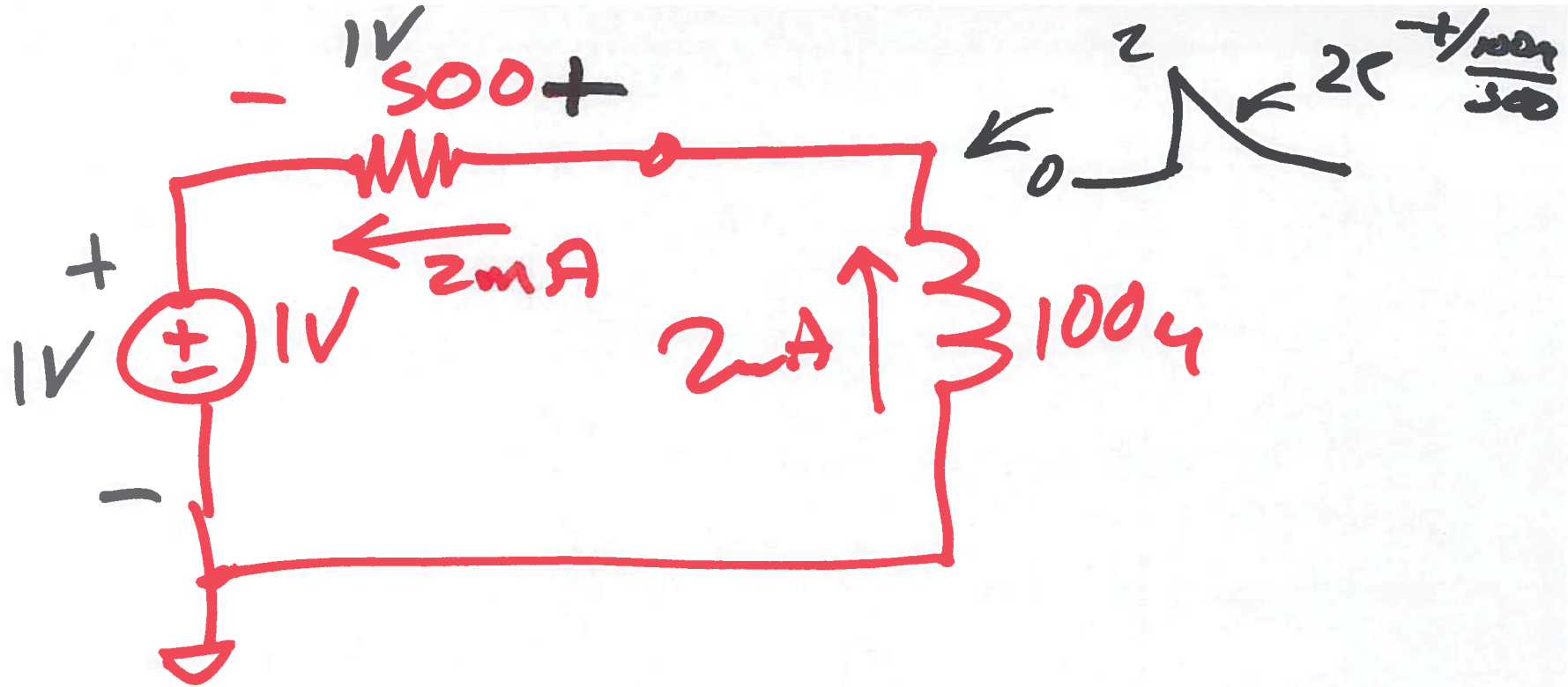

3)

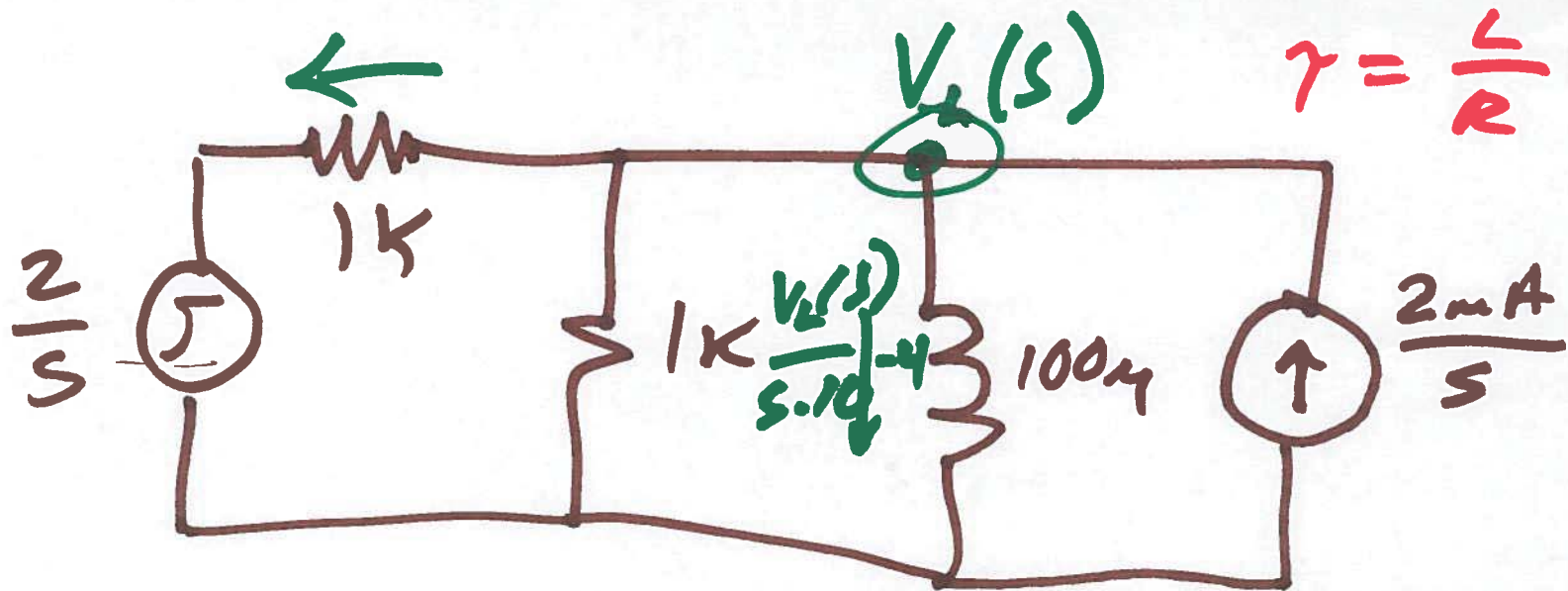

$$\tau = \frac{L}{R} = \frac{10^{-4}}{\frac{10^3}{2}}$$



$$\frac{2mA}{s} = \frac{V_L(s)}{5 \cdot 10^{-4}} + \frac{V_L(s)}{1k}$$

~~$$\frac{V_L(s) - \frac{2}{s}}{1k}$$~~

$$\frac{V_L(s)}{1k} = \frac{2mA}{s}$$

4)

$$\frac{10^3}{\frac{10^3}{s \cdot 10^{-4}} \cdot \frac{10^{-3}}{10^{-3}}} \left(\frac{2 \mu A}{s} + \frac{2 \mu A}{s} \right) = V_L(s) \left(\frac{1}{s \cdot 10^4} + \frac{1}{1k} + \frac{1}{1k} \right) \cdot 10^3$$



$$= \frac{1}{s \cdot 10^{-7}} \left(\frac{4}{s} = V_L(s) \cdot \left(\frac{1}{s \cdot 10^{-7}} + 1 + 1 \right) \right)$$

$$\frac{4}{s} = V_L(s) \cdot \left(\frac{1 + s \cdot 10^{-7} \cdot 2}{s \cdot 10^{-7}} \right)$$

$$\frac{4 \cdot 10^{-7}}{1 + s \cdot 2 \cdot 10^{-7}} = V_L(s) = \frac{2}{s + \frac{10^7}{2}}$$

$$v_L(t) = 2e^{-t/10^{-7} \cdot 2} u(t)$$

5)

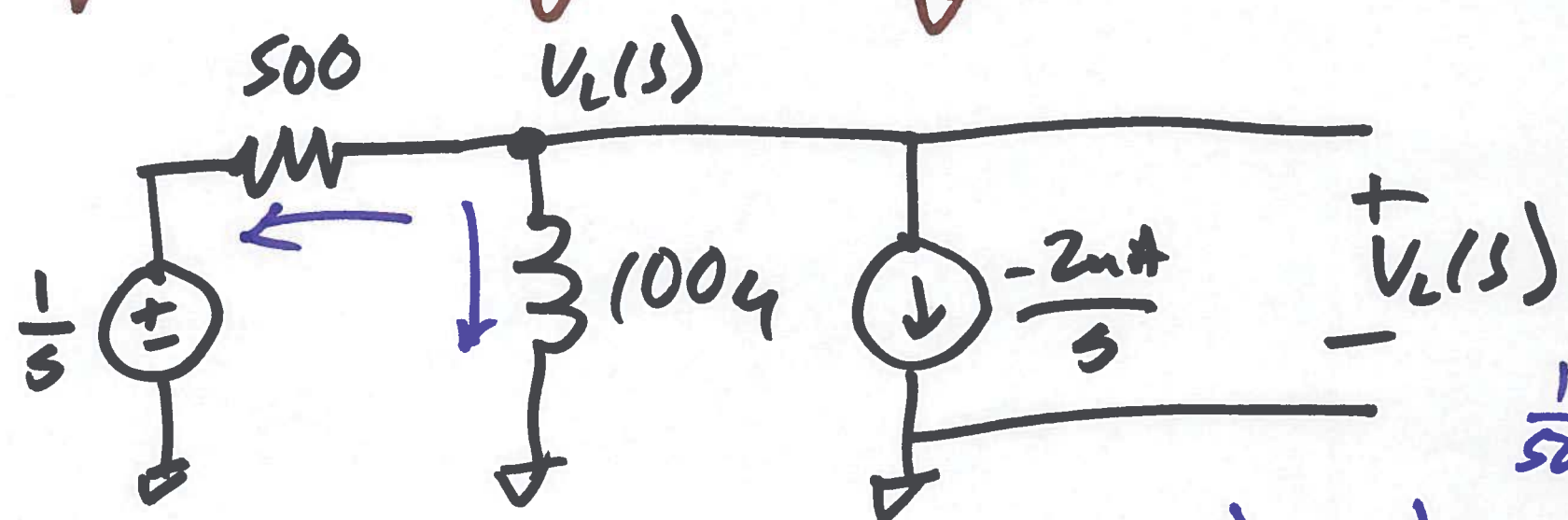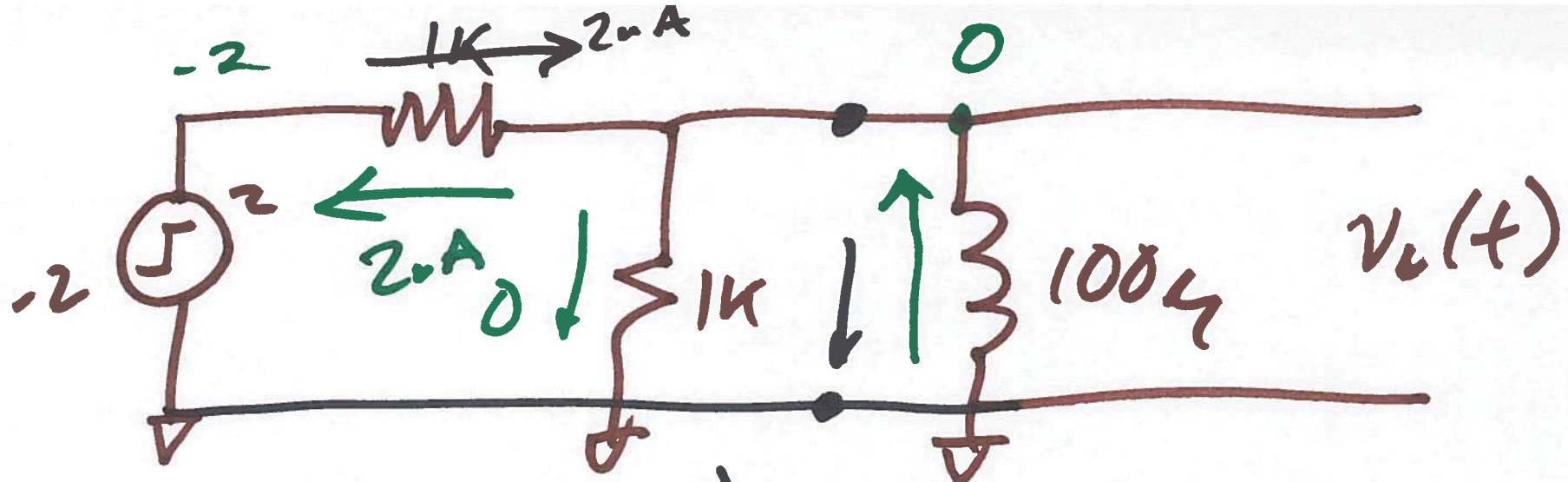

$$-\frac{2\mu A}{s} + \frac{v_L(s)}{s \cdot 10^{-4}} - \frac{v_L(s) - \frac{1}{s}}{500} = 0$$

$\frac{1}{500} = 0.002\mu A$

6)

$$V_L(s) \left(\frac{1}{s \cdot 10^{-4}} + \frac{1}{500} \right) = \frac{2 \mu A}{s} + \frac{2 \mu A}{s}$$

$$V_L(s) \left(\frac{1 + \cancel{2} s \cdot 10^{-4} \cdot 2 \cdot A}{\beta \cdot 10^{-4}} \right) = \frac{4 \mu A}{s}$$

$$10^{-4} \cdot 4 \cdot 10^{-3}$$


$$V_L(s) = \frac{1 + 5 \cdot 10^{-4} \cdot 2 \cdot 10^{-3}}{2}$$

$$V_L(t) = 2e^{-\frac{(t-100\mu)}{2 \cdot 10^{-7}}}$$

$$= \frac{1}{s + \frac{1}{2 \cdot 10^{-7}}}$$

$$V_L(t) = 2e^{-\frac{t}{2 \cdot 10^{-7}}} u(t)$$

7)

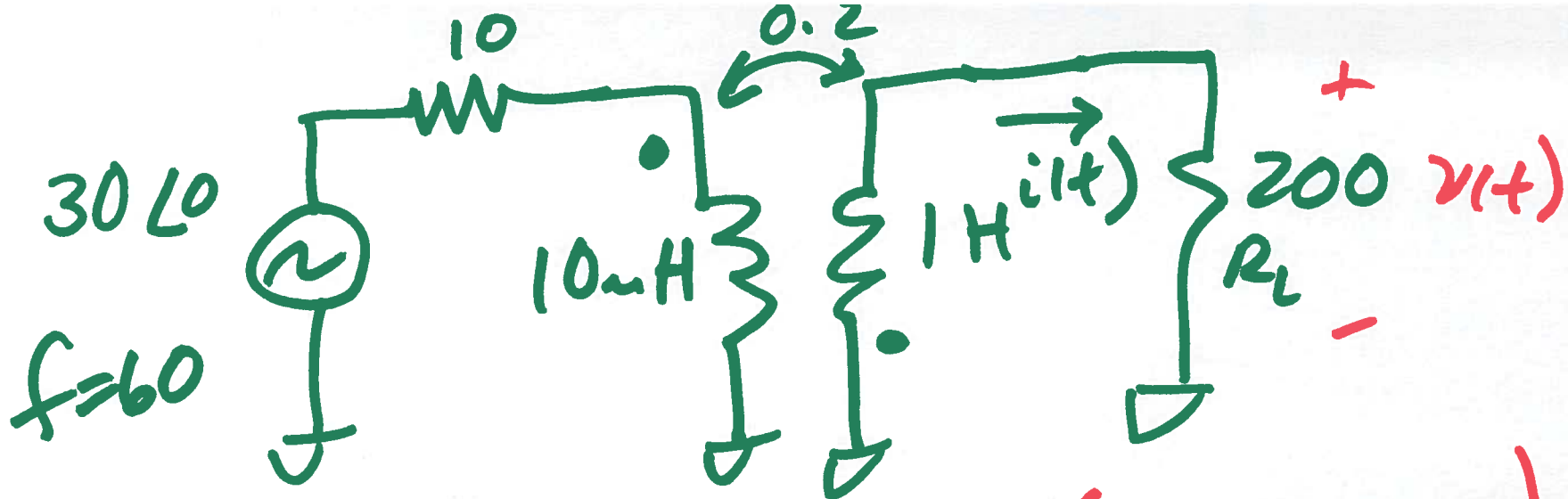

$$P_{RL} = I_{rms} \cdot V_{rms}$$

$$= I_{rms}^2 \cdot R$$

$$= \frac{V_{rms}^2}{R}$$


$$i(t) = I_p \cdot \cos(2\pi \cdot 60t + \theta)$$

$$I_{rms} = \frac{I_p}{\sqrt{2}}$$



$$v(t) = 200 \cdot I_p \cdot \cos(2\pi \cdot 60t + \theta)$$

$$= 200 \cdot i(t)$$
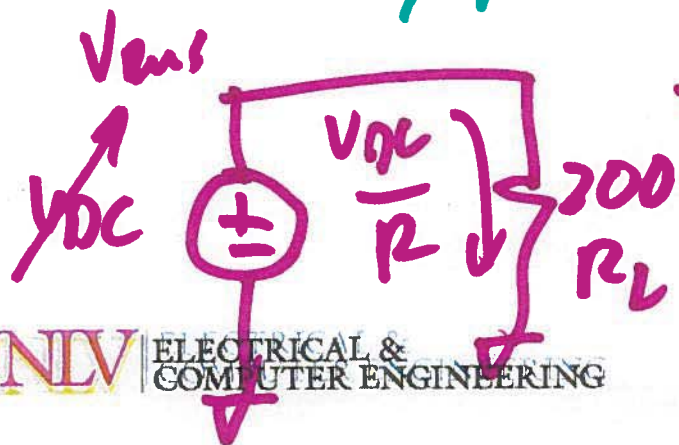
$$\frac{V_{oc}^2}{R} = I_{oc} \cdot V_{oc} = I_{oc}^2 \cdot R$$




8)

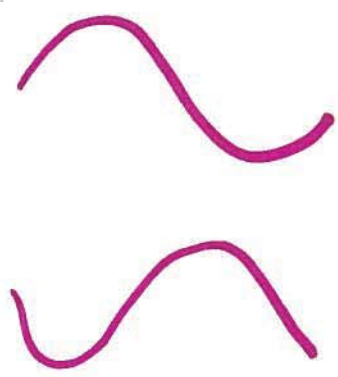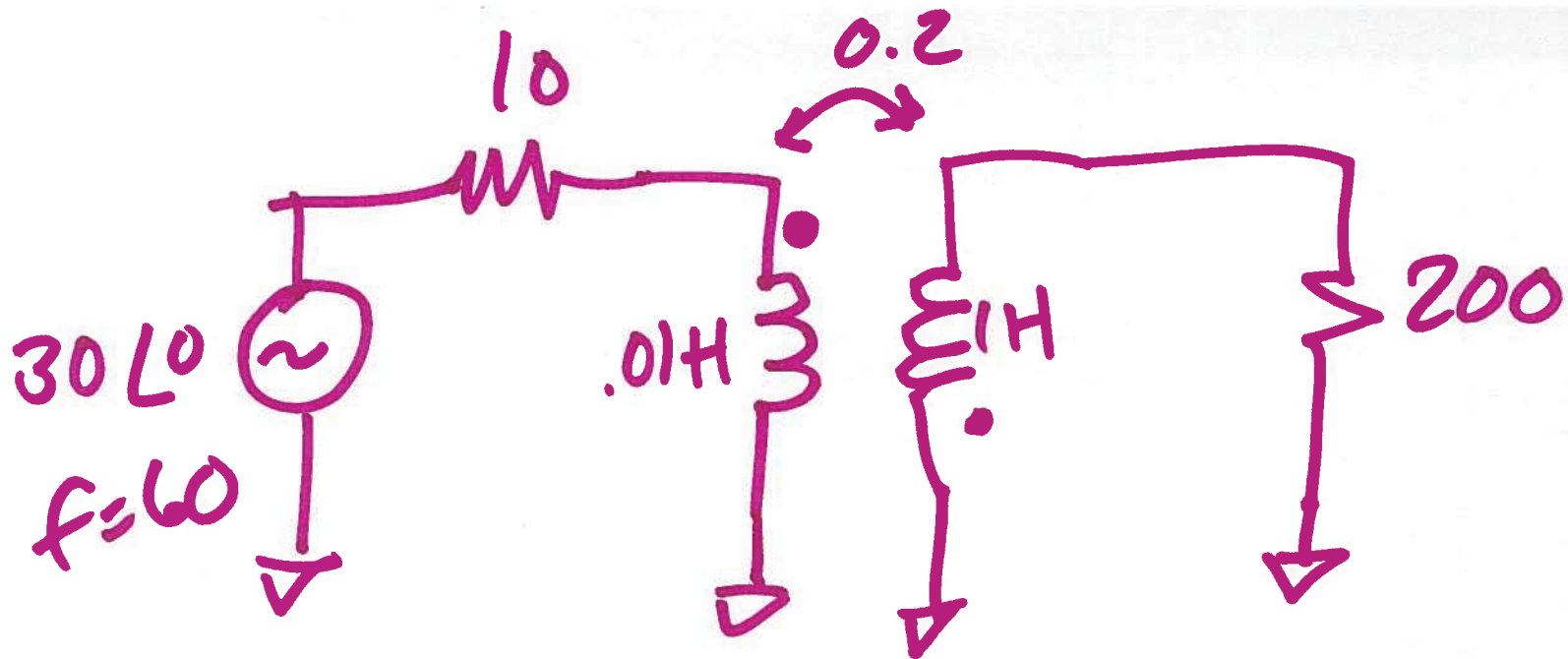

$$M = 0.2 = k \cdot \sqrt{0.01 \cdot 1}$$

$$k = 2$$

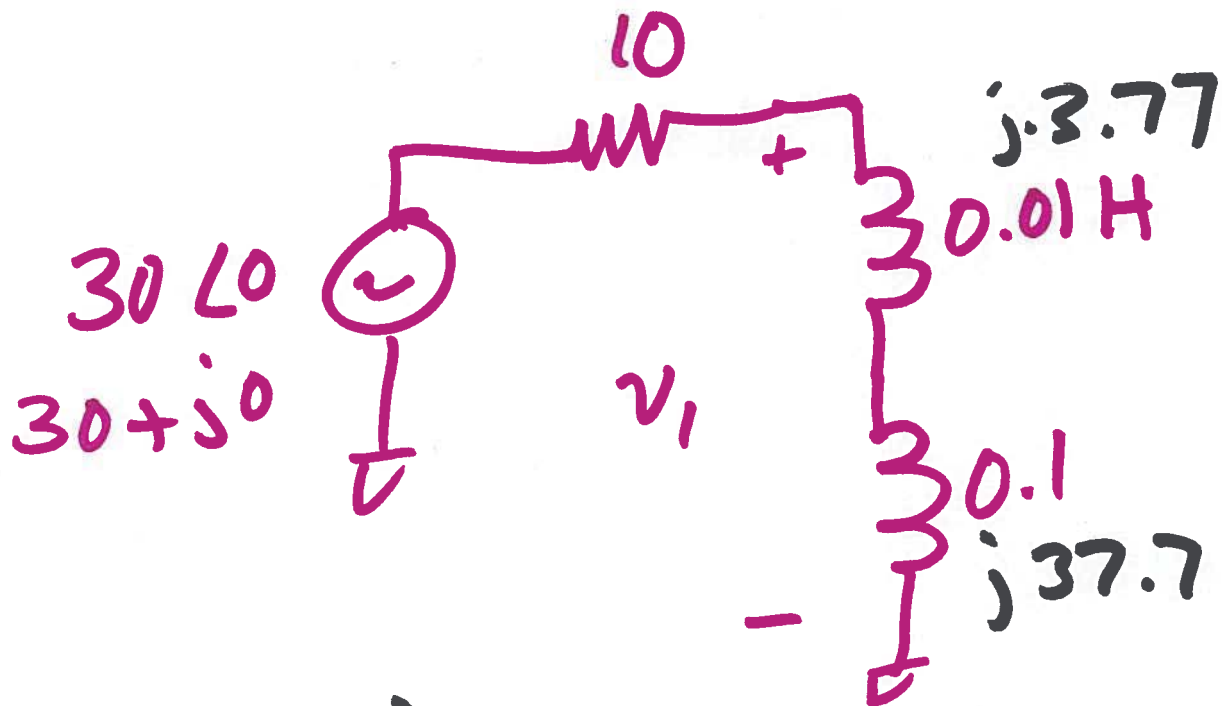This isn't possible so
 I assume $k = 0.1$ for
 $k = 1$



$$j\omega L = j \cdot 2\pi \cdot 60 \cdot 0.01$$

$$= 3.77j$$


$$30\angle 0 = I_1 \cdot 10$$

$$+ j \cdot 3.77 \cdot I_1$$

$$- I_2 \cdot j 37.7$$

$$30\angle 0 = I_1 \cdot 10 + I_1 \cdot j 3.77$$

$$- I_2 \cdot j 37.7$$

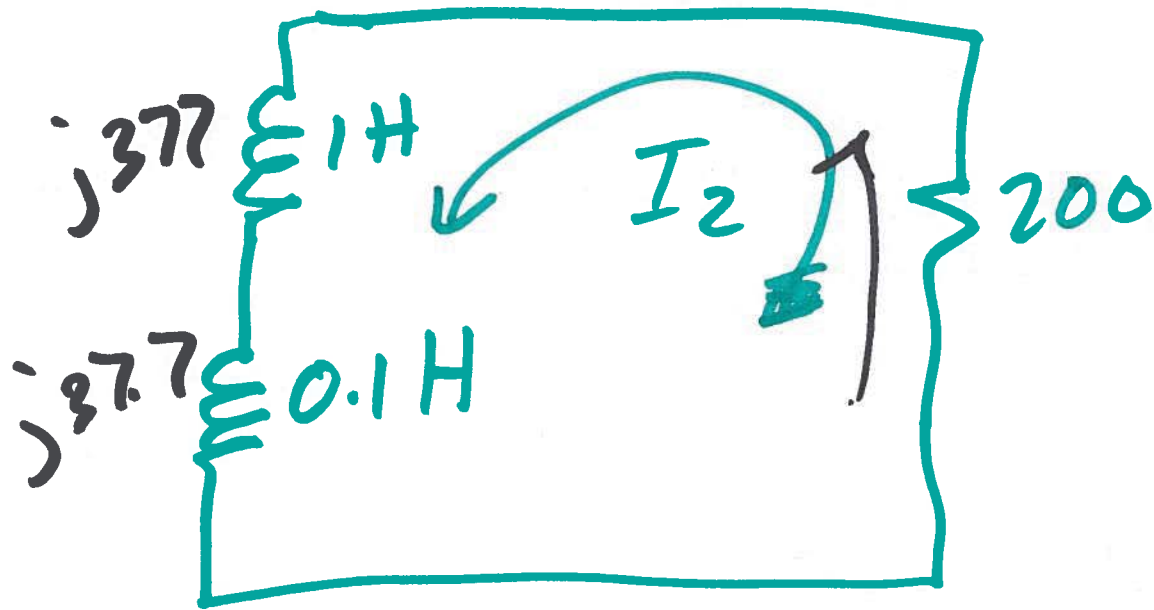

$$1. \quad I_2 \cdot j377 - I_2 \cdot 37.7 - 200 I_2 = 0$$

