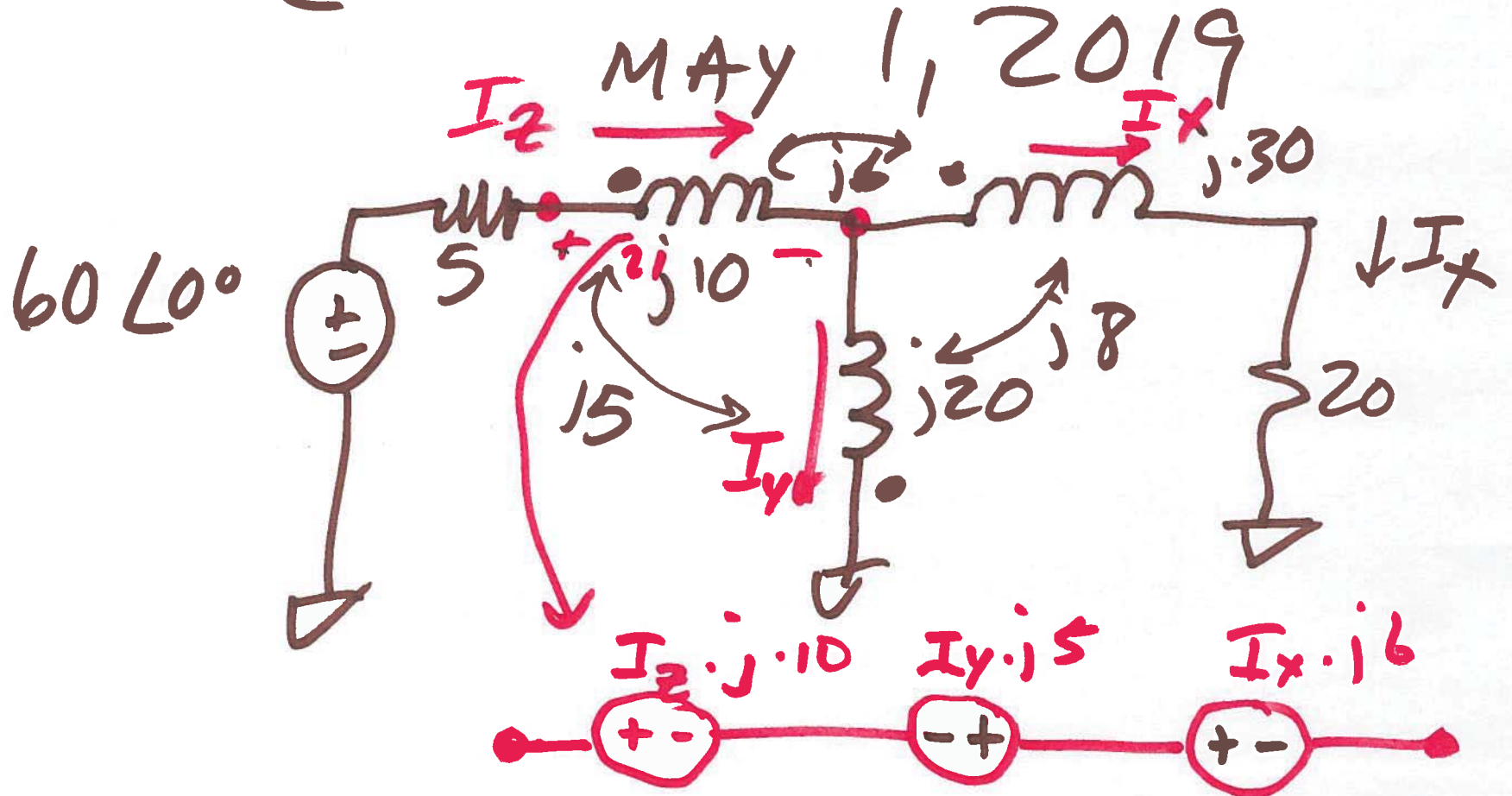


Circuits II


EE 221

Lecture 24

MAY 1, 2019



1)

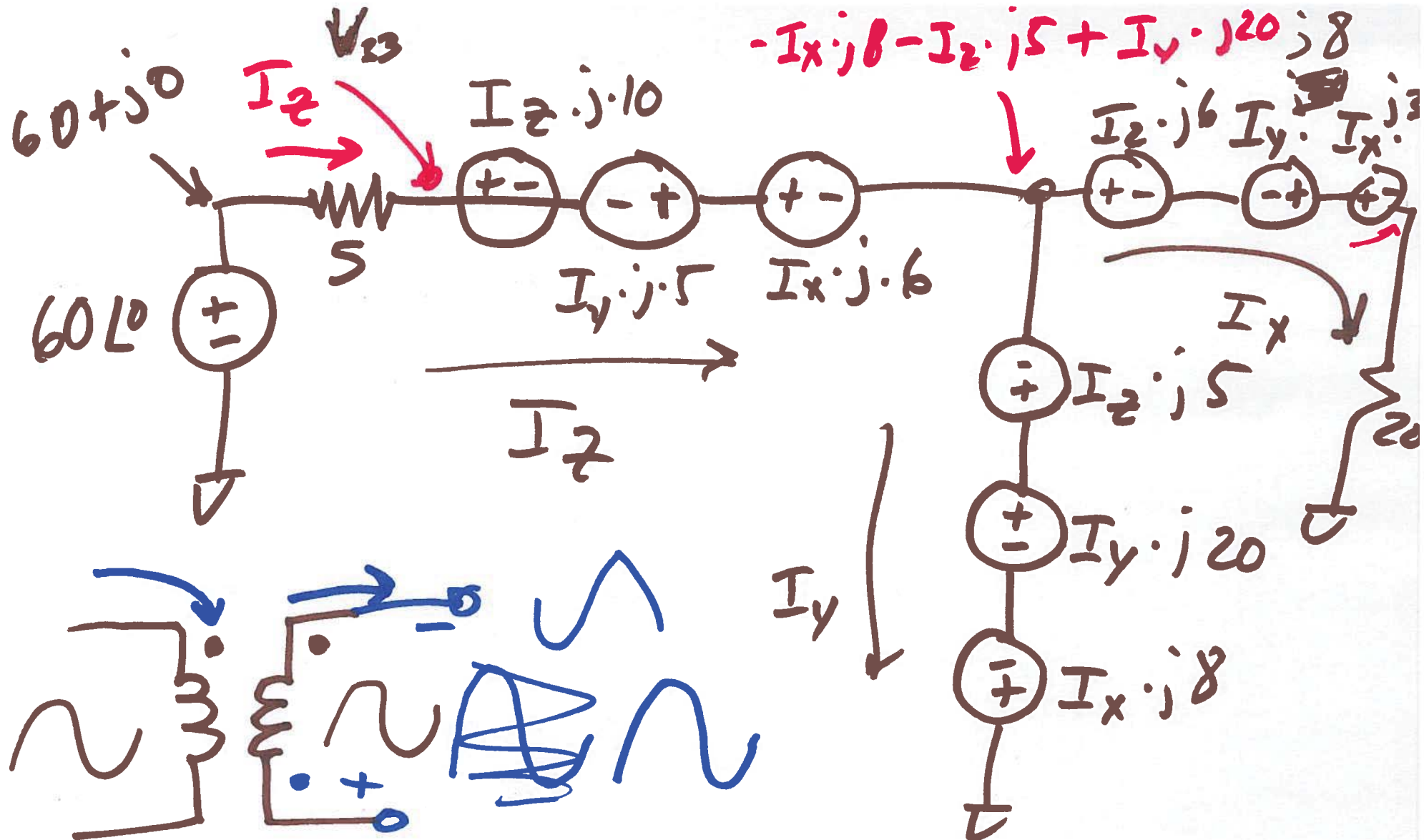

2)

$$V_{33} = I_2 \cdot j10 - I_y \cdot j5 + I_x \cdot j6 - I_x \cdot j8 - I_2 \cdot j5 + I_y \cdot j20$$

$$V_{33} = I_2 (j10 - j5) + I_y (j20 - j5)$$

$$+ I_x (j6 - j8)$$

$$V_{33} = -I_x j2 + I_y \cdot j15 + I_2 \cdot j5$$

$$I_2 = \frac{60 + j0 + I_x j2 - I_y \cdot j15 - I_2 \cdot j5}{5}$$

$$I_2 (5 + j5) = 60 + I_x \cdot j2 - I_y \cdot j15$$

$$I_2 = \frac{60 + I_x \cdot j2 - I_y \cdot j15}{5 + j5}$$


$$5 + j5 = \frac{1}{\sqrt{2}} \sqrt{5^2 + 5^2} \angle (\tan^{-1} 1)$$

$$= 5 \cdot \frac{1}{\sqrt{2}} \angle 45^\circ$$

$$\bar{I}_z = \frac{60 \angle 0}{5\sqrt{2} \angle 45^\circ} + I_x \cdot \frac{2 \angle 90}{5\sqrt{2} \angle 45^\circ} + \frac{I_y \angle -90}{5\sqrt{2} \angle 45^\circ}$$

$$\bar{I}_z = \frac{12}{\sqrt{2}} \angle -45 + I_x \frac{2}{5\sqrt{2}} \angle 45 + I_y \frac{3}{\sqrt{2}} \angle -135$$

$$\boxed{I_y = \bar{I}_z - I_x}$$

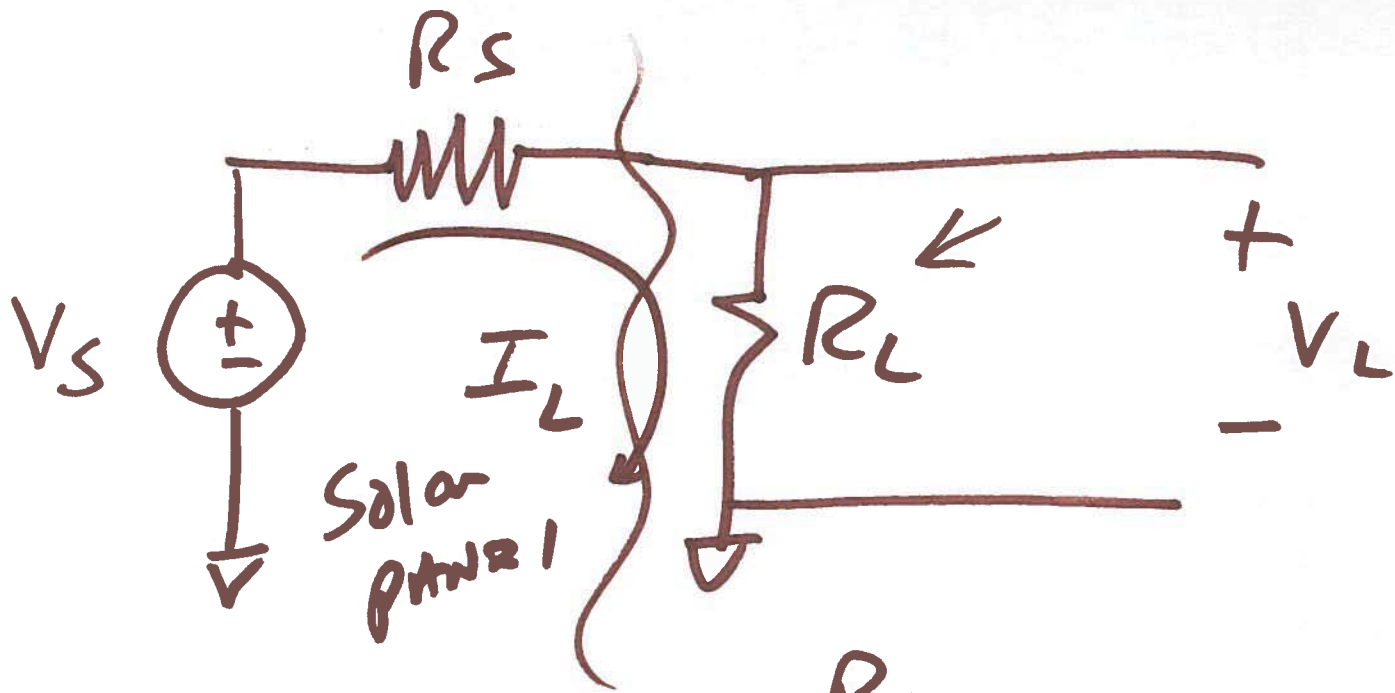

$$V_L = V_s \cdot \frac{R_L}{R_L + R_s}$$

$$I_L = \frac{V_s}{R_s + R_L}$$

$$V_L \Big|_{\text{power}} = V_L \cdot I_L = V_s^2 \cdot \frac{R_L}{(R_s + R_L)^2}$$

$$P = V_S^2 \cdot \frac{R_L}{(R_S + R_L)^2}$$


$$\frac{\delta P}{\delta R_L} = 0 = \frac{V_S^2}{\delta R_L} R_L \cdot (R_S + R_L)^{-2}$$

$$0 = (R_S + R_L)^{-2} + R_L(-2)(R_S + R_L)^{-3}$$

$$\frac{2 R_L}{(R_S + R_L)^3} = \frac{1}{(R_S + R_L)^2}$$

$$2 R_L \stackrel{?}{=} R_S + R_L$$

$$\boxed{R_L = R_S}$$

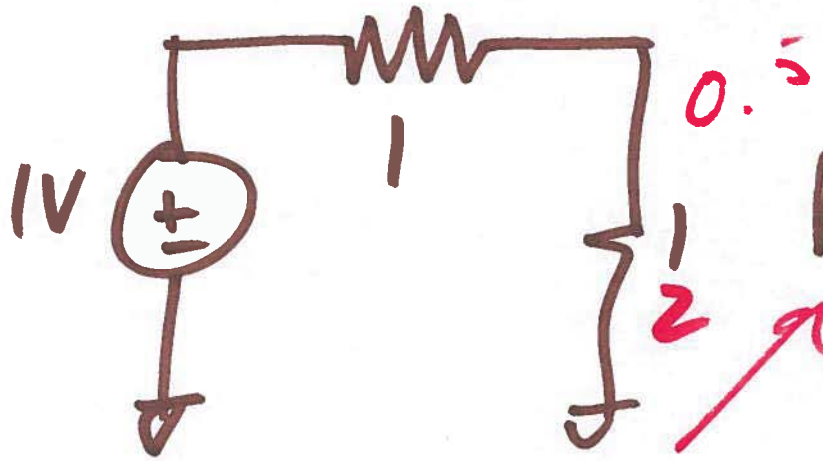


$$\begin{aligned}
 P_L &= \frac{1}{2} V \cdot \frac{1}{2} A = \frac{1}{4} W \\
 &= \frac{2}{3} V \cdot \frac{1}{3} A = \frac{2}{9} W \\
 &= \frac{1}{3} V \cdot \frac{2}{3} A = \frac{2}{9} W
 \end{aligned}$$

7)





Power Electronic

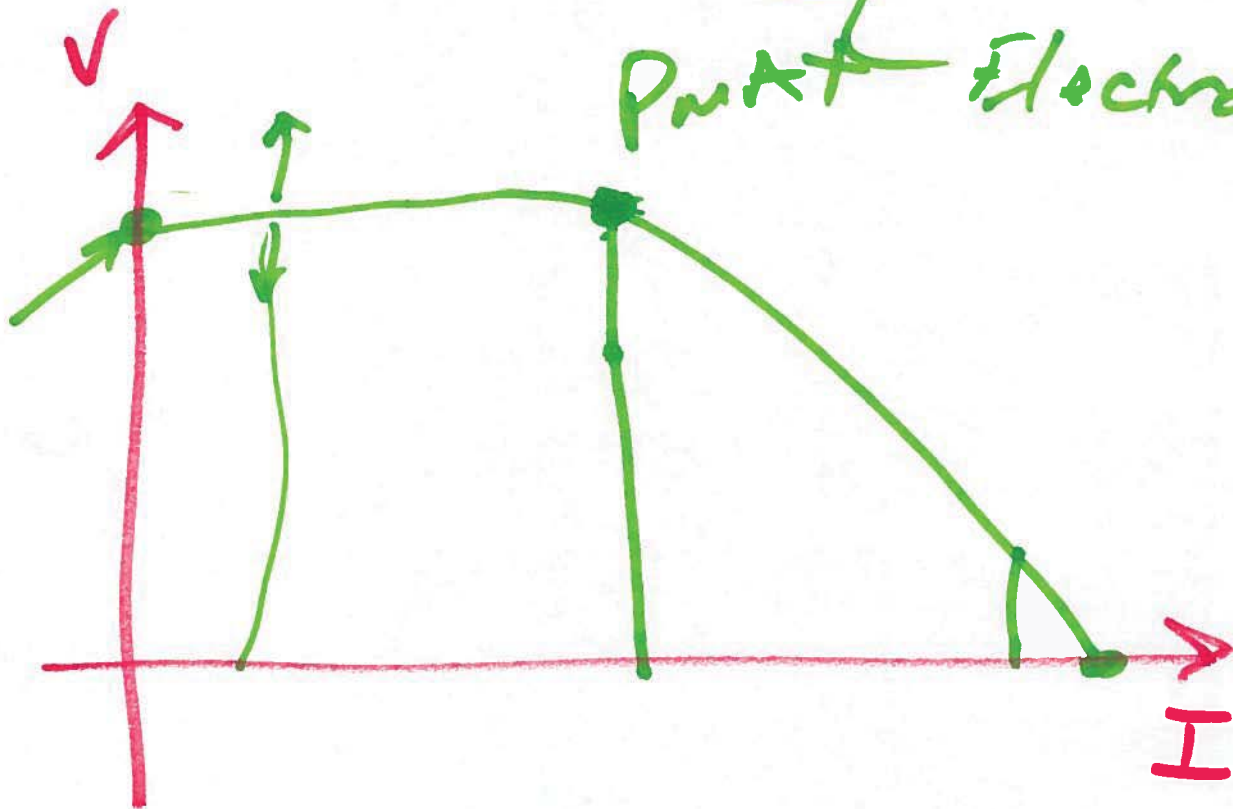

MAXIMUM power transfer

$$Z_s = R \pm jX$$

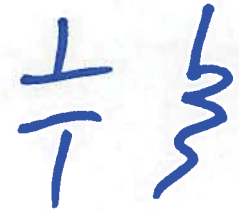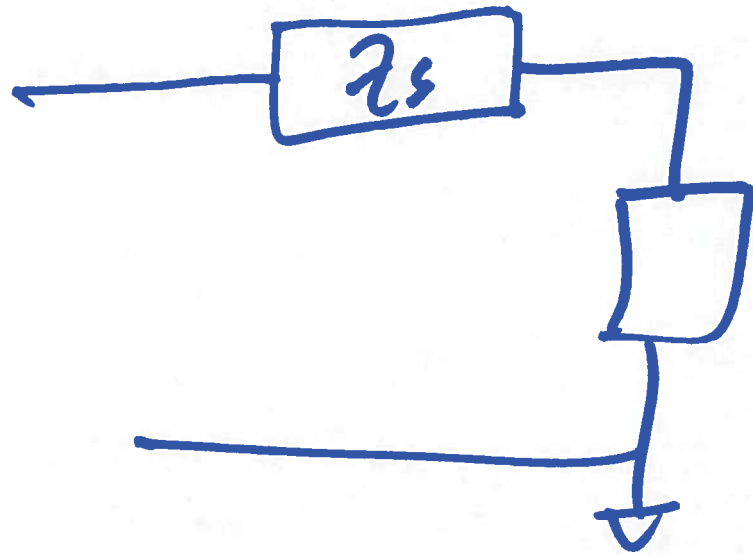


$$Z_L = R \mp jX$$

MAX power transfer

Z_L to complex conjugate
of Z_s

9)

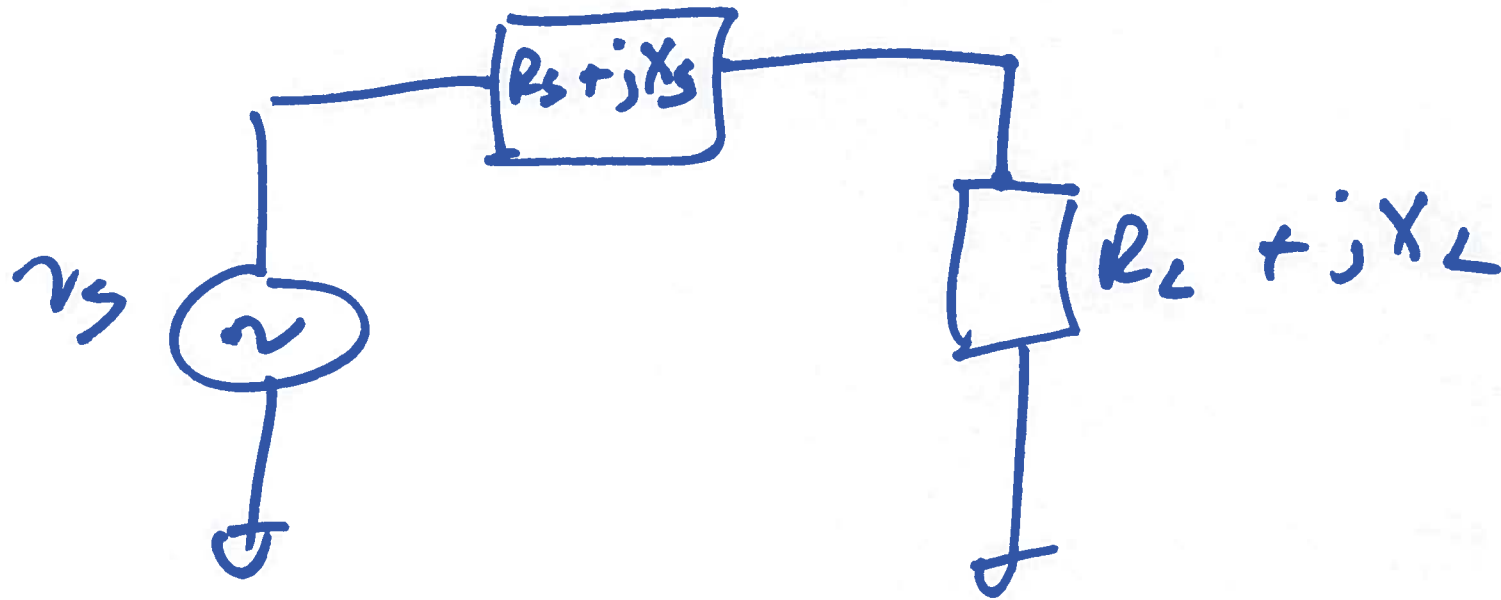

MAX power transfer

$$R_s = R_L$$

$$jX_s = -jX_L$$

10)