

EE 221 circuits II

May 6, 2019


Lecture 25 $\frac{1}{s+a} \rightarrow e^{-at}$

$$u(t) \leftrightarrow \frac{1}{s}$$

$$u(t-t_0) \rightarrow \frac{e^{-t_0 s}}{s}$$

$$A \cdot e^{-t/\tau} \rightarrow \frac{A}{s + \frac{1}{\tau}}$$
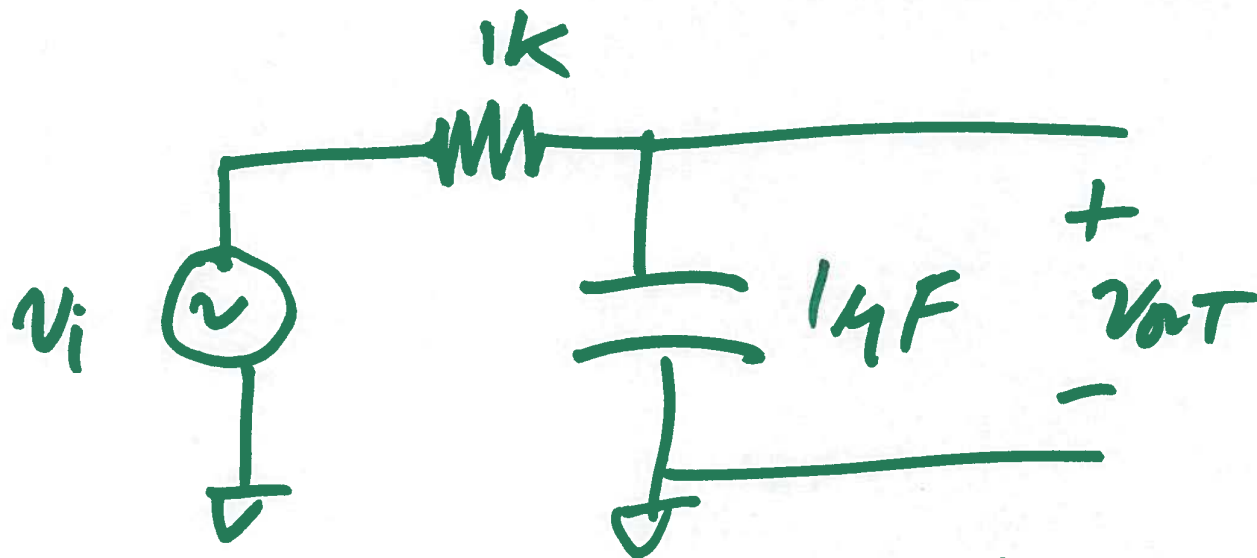
$$A \cdot e^{-\frac{(t-t_0)}{\tau}} \rightarrow \frac{A e^{-t_0 s}}{s + \frac{1}{\tau}}$$



transfer function,

$$\frac{v_{oT}}{v_i} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} = \frac{1}{1 + j\omega RC}$$


$$\left| \frac{v_{oT}}{v_i} \right| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{1}{\sqrt{1 + (2\pi fRC)^2}} \rightarrow f_{3dB} = \frac{1}{2\pi RC}$$

$$\frac{1}{2\pi \cdot 10^3 \cdot 10^{-6}} = \frac{1}{2\pi \cdot 10^{-3}}$$

$$= \frac{1}{0.00628} = \underline{\underline{159 \text{ Hz}}}$$
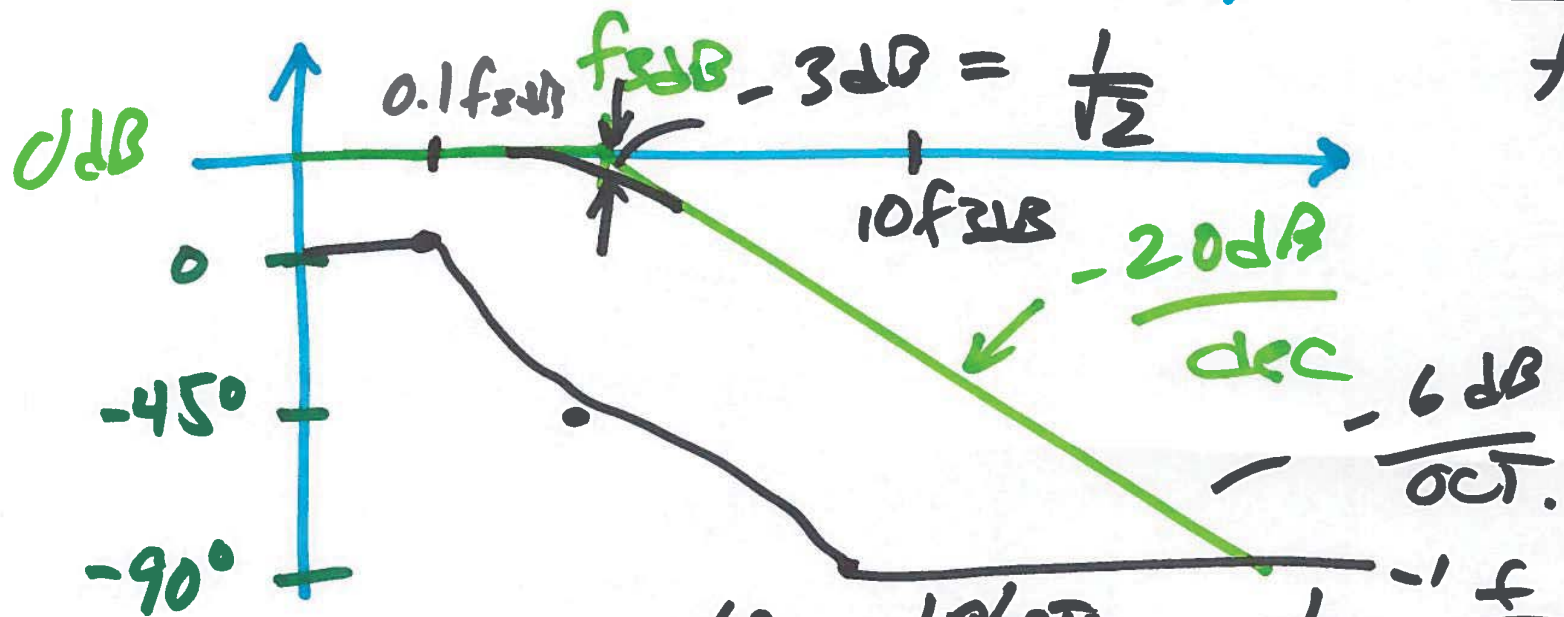
$$\frac{1}{\sqrt{1 + \left(\frac{f}{f_{3dB}}\right)^2}}, \quad f \gg f_{3dB} \approx \frac{f_{3dB}}{f}$$



$$\angle \theta = \angle \frac{v_{out}}{v_{in}} = -\tan^{-1} \frac{f}{f_{3dB}}$$

3)

Phase Shift

$$\theta = \frac{t_d}{T} \cdot 360 = \underline{t_d} \cdot f \cdot 360^\circ$$

$$f = \frac{1}{T}$$

$$\frac{V_{out}}{V_{in}} = \frac{1 + j0}{1 + j2\pi fRC}$$


$$\angle \frac{V_{out}}{V_{in}} = \cancel{\tan^{-1} \frac{0}{1}} - \tan^{-1} 2\pi fRC$$


$$= -\tan^{-1} \frac{f}{f_{3dB}}$$

$$-\tan^{-1} \infty = -90$$

$$-\tan^{-1} 0 = 0$$

$$-\tan^{-1} 1 = -45^\circ$$

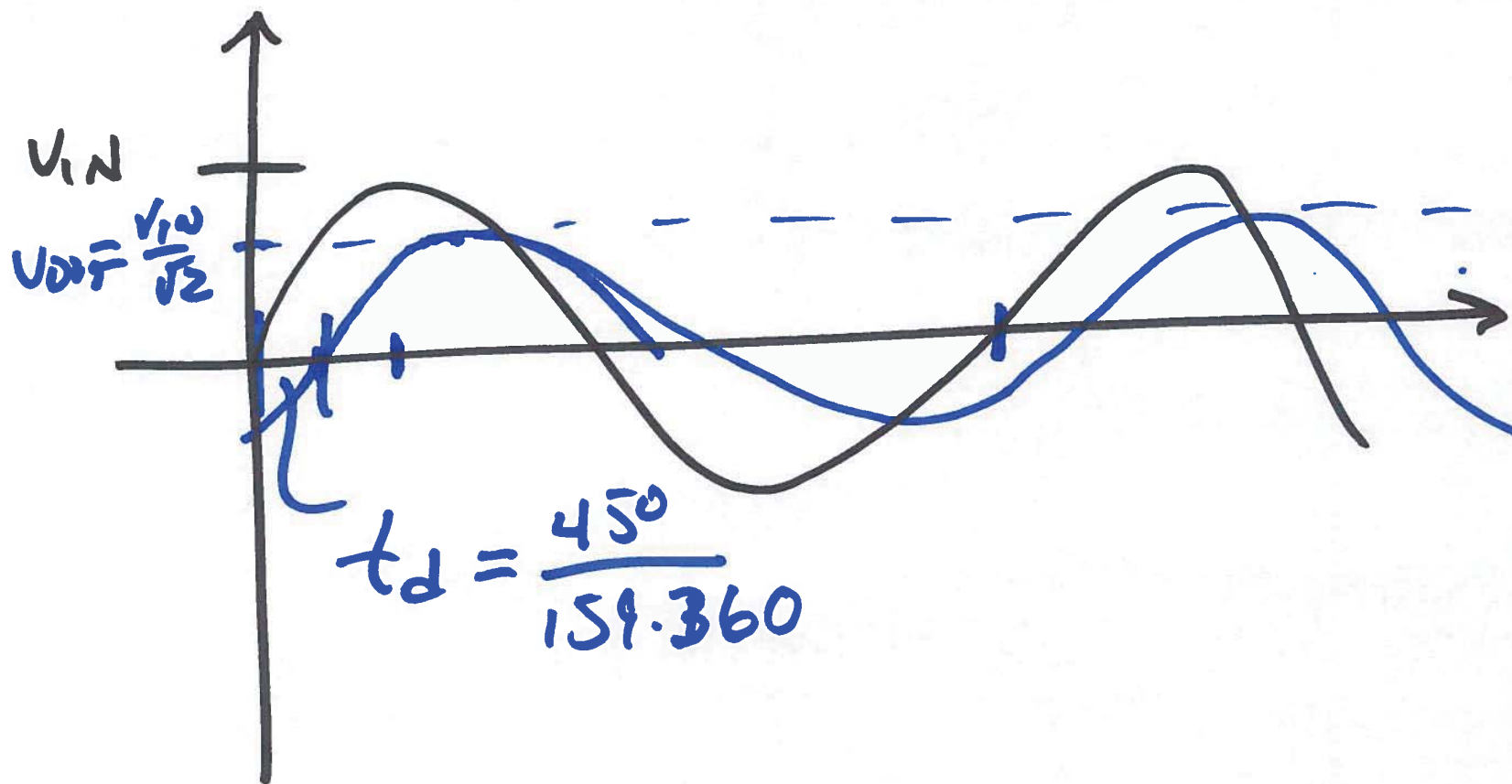

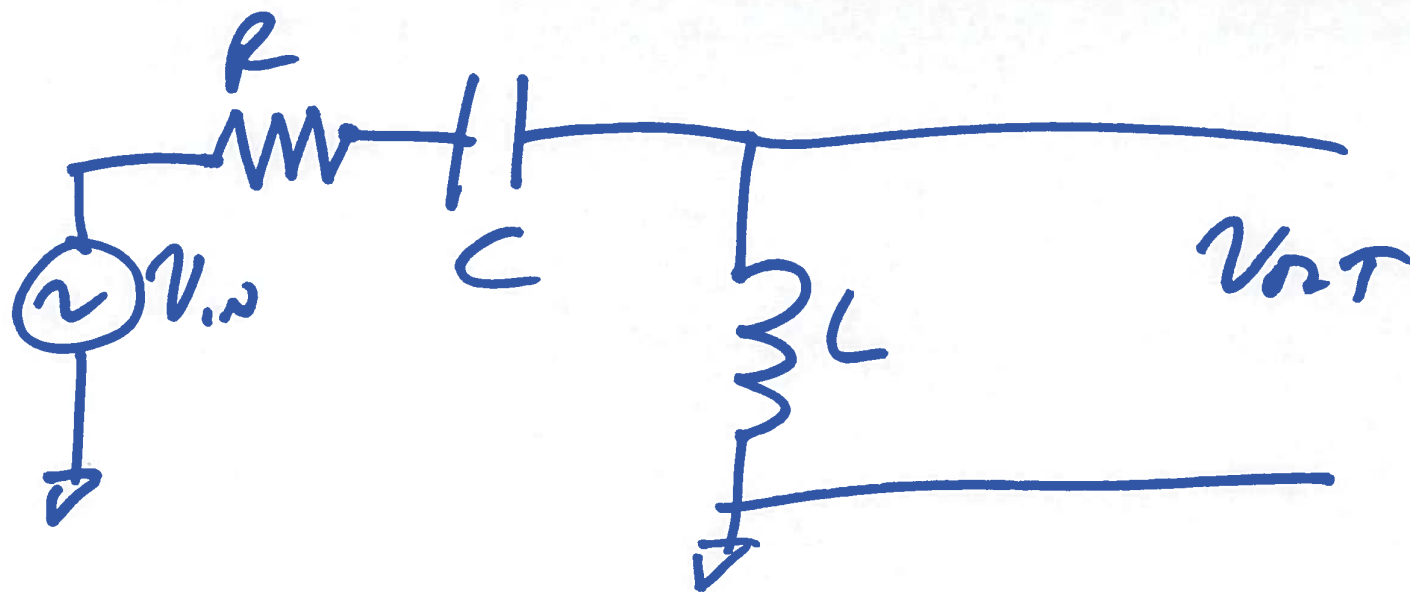


$$\frac{v_{out}}{v_{in}} = \frac{sL}{sL + \frac{1}{sC} + R} = \frac{s^2 LC}{s^2 LC + 1 + sR}$$

$$\frac{v_{out}}{v_{in}} = \frac{s^2 L C}{s^2 + s \cdot \frac{R}{L} + \frac{1}{LC}}$$

$$s^2 \rightarrow (0 + j\omega)(0 + j\omega)$$

$$|s^2| = \sqrt{0^2 + (\omega^2)} \cdot \sqrt{0^2 + \omega^2}$$

$$y, im \quad \sqrt{x^2 + y^2}$$

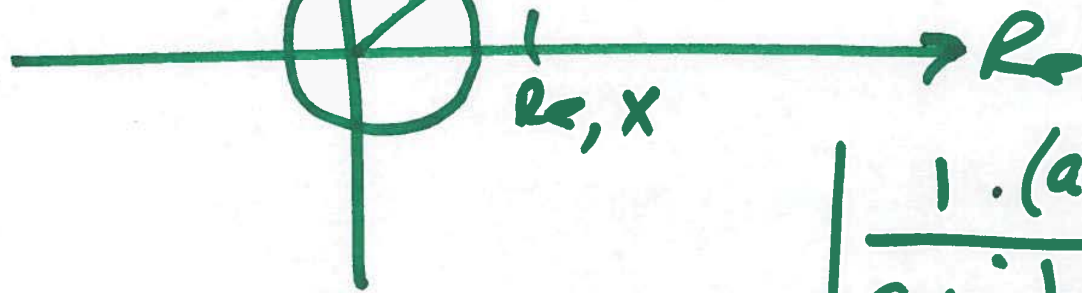

$$|s^2| = \omega^2$$

$$\left| \frac{1 \cdot (a - jb)}{(a + jb)(a - jb)} \right|$$

$$\left| \frac{1}{\sqrt{a^2 + b^2}} \right|$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \left| \frac{s^2}{s^2 + s \cdot \frac{R}{L} + \frac{1}{LC}} \right|$$

$$s_{1,2} = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}}{2}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \left| \frac{s^2}{(s - s_1)(s - s_2)} \right|$$

$$= \frac{\omega^2}{\sqrt{(10^3)^2 + (\omega)^2} \cdot \sqrt{(10^4)^2 + (\omega)^2}}$$

e)


$$\left| \frac{v_{out}}{v_{in}} \right| = \left| \frac{s^2}{(-s)(s_2) \left(1 + \frac{s}{s_1}\right) \left(1 + \frac{s}{s_2}\right)} \right|$$

$$= \frac{\omega^2}{\sqrt{\left(\left(\frac{\omega}{s_1}\right)^2 + 1\right)} \cdot \sqrt{1^2 + \left(\frac{\omega}{s_2}\right)^2}}$$

$$\omega = 2\pi f$$

$$s_1 = 2\pi \cdot 10^3, \quad s_2 = 2\pi \cdot 10^4$$
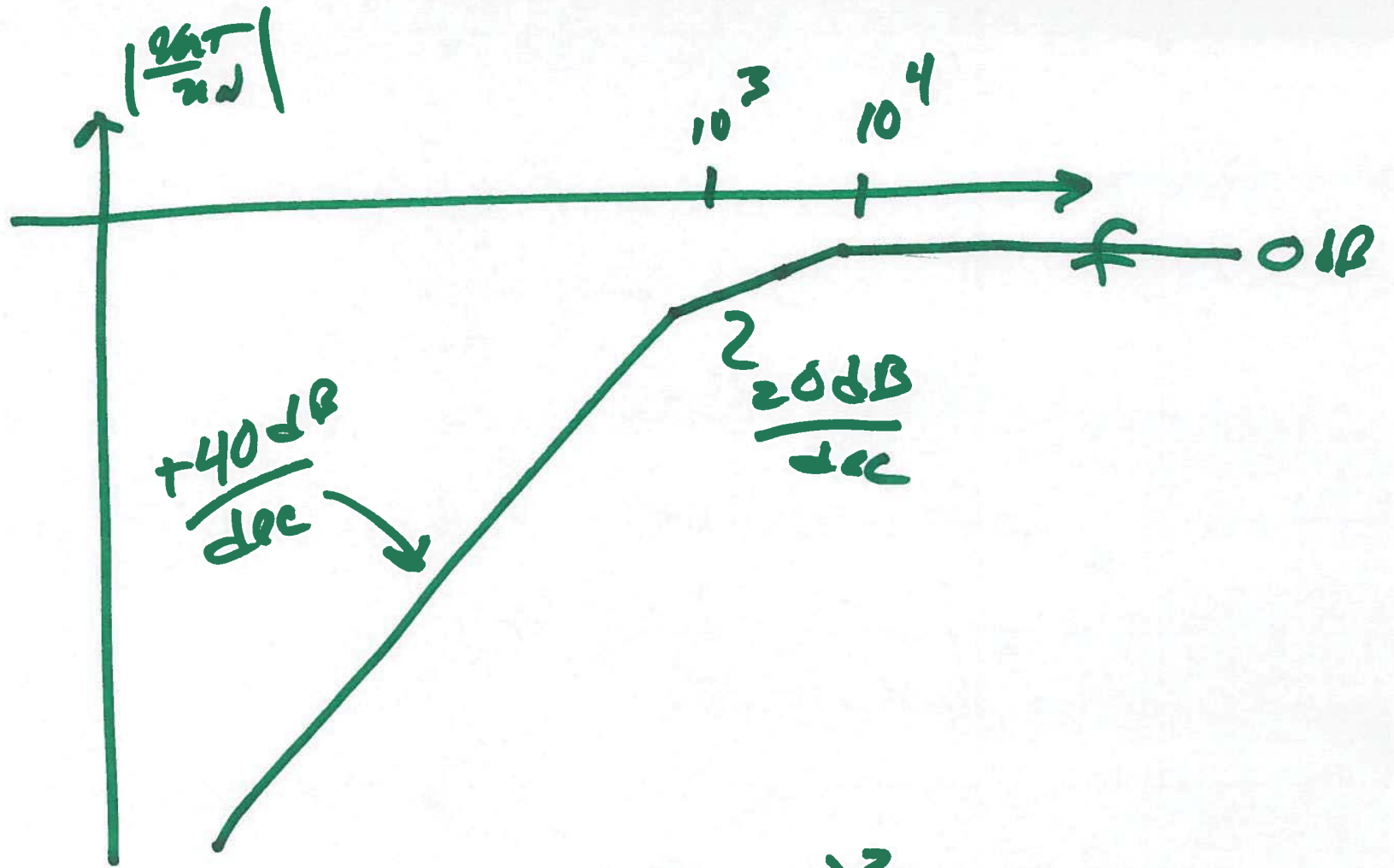
$$= \frac{\omega^2}{\sqrt{1 + \left(\frac{f}{10^3}\right)^2} \cdot \sqrt{1 + \left(\frac{f}{10^4}\right)^2}}$$



$$20 \log(2\pi f)^2$$

$$10 \cdot 40 \log 6.28$$


$$40 \log 2\pi \cdot f$$

$$40 \log 6.28$$

$$f=1 \rightarrow$$

CMOSedu.com
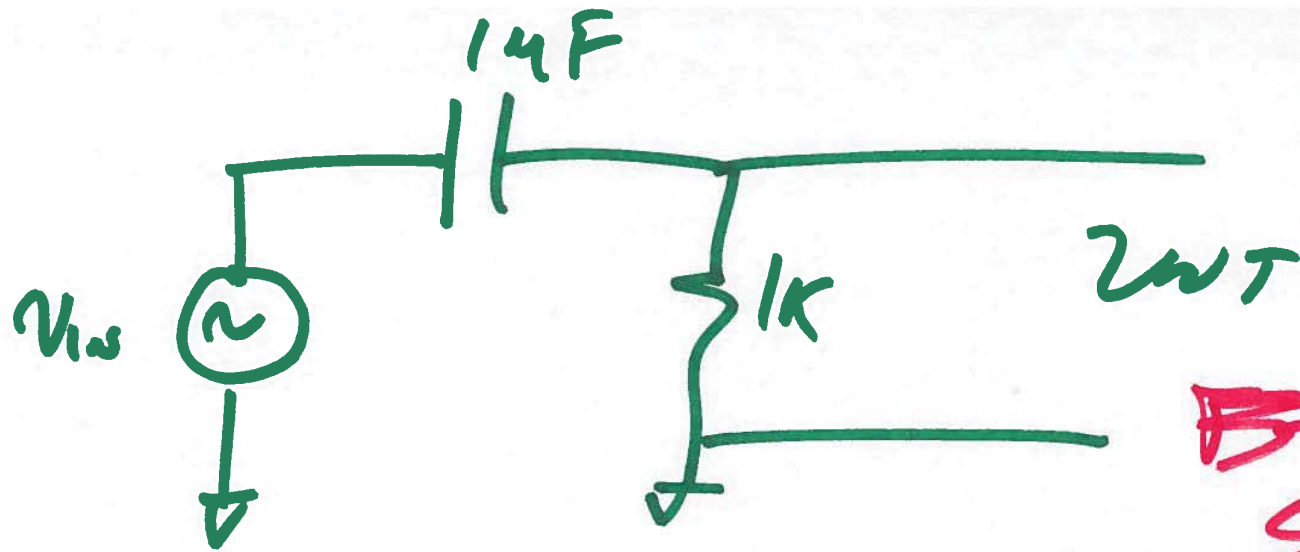
$$f=10 \rightarrow 40 \log 6.28 \cdot 10$$



$$s = \sigma + j\omega$$

$$\frac{5 \cdot 10^{-3}}{1 + s \cdot 10^{-3}}$$

$$\frac{V_{out}}{V_{in}} = \frac{10^3}{10^3 + \frac{1}{j \cdot \omega \cdot 10^{-6}}}$$


$$\frac{V_{out}}{V_{in}} = \frac{j\omega \cdot 10^{-3}}{1 + j\omega 10^{-3}}$$

11)

$$\frac{v_{out}}{v_{in}} = \frac{0 + j \frac{f}{159}}{1 + j \frac{f}{159}} \quad f \gg 159$$

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{\sqrt{0^2 + \left(\frac{f}{159}\right)^2}}{\sqrt{1 + \left(\frac{f}{159}\right)^2}} = \frac{\frac{f}{159}}{\sqrt{1 + \left(\frac{f}{159}\right)^2}}$$
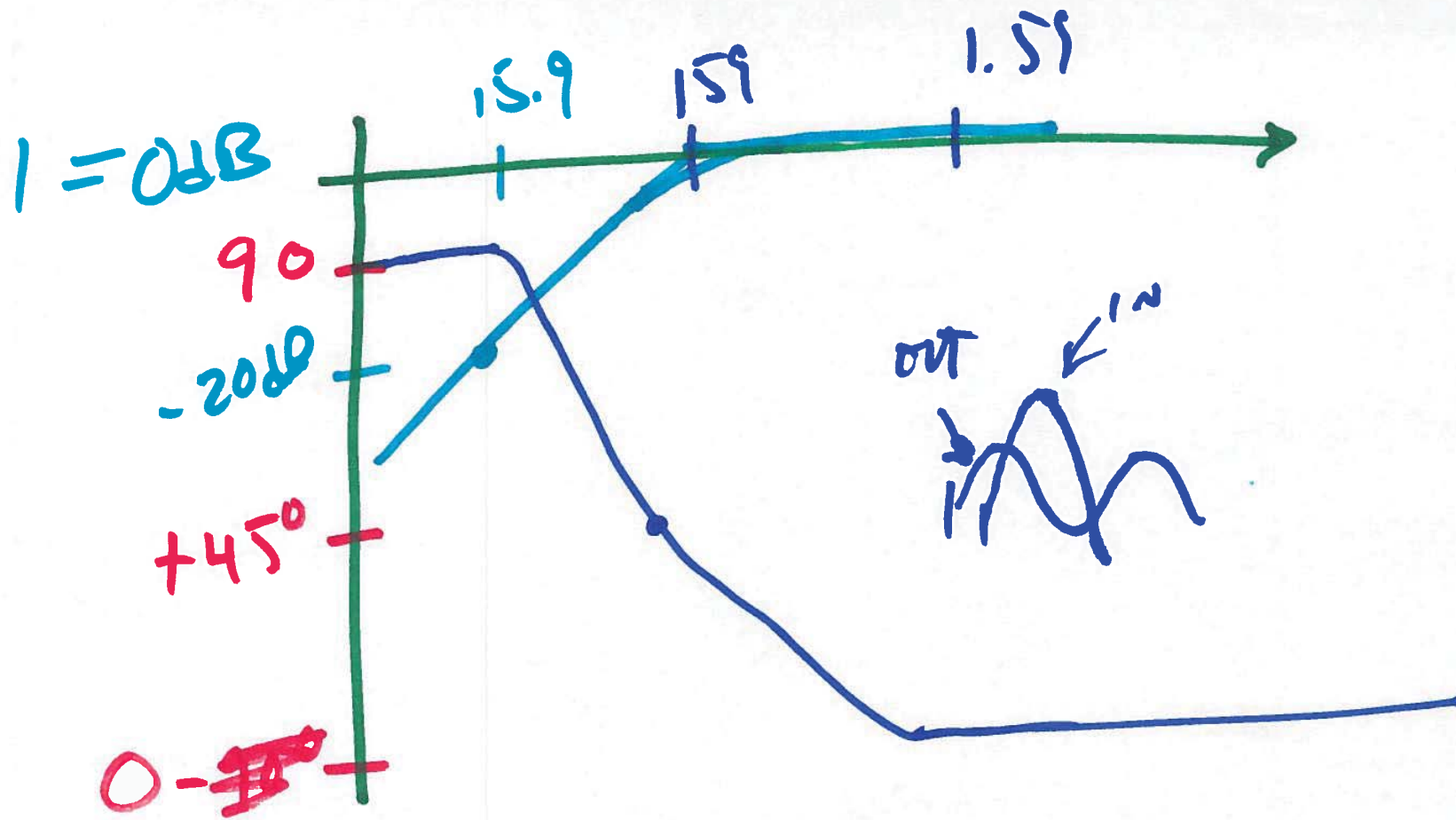
$$\angle \frac{v_{out}}{v_{in}} = \cancel{\tan^{-1} \frac{f}{0}}^{90} - \tan^{-1} \frac{f}{159}$$



$$\angle \frac{V_{out}}{V_{in}} = 90 - \tan^{-1} \frac{f}{159}$$