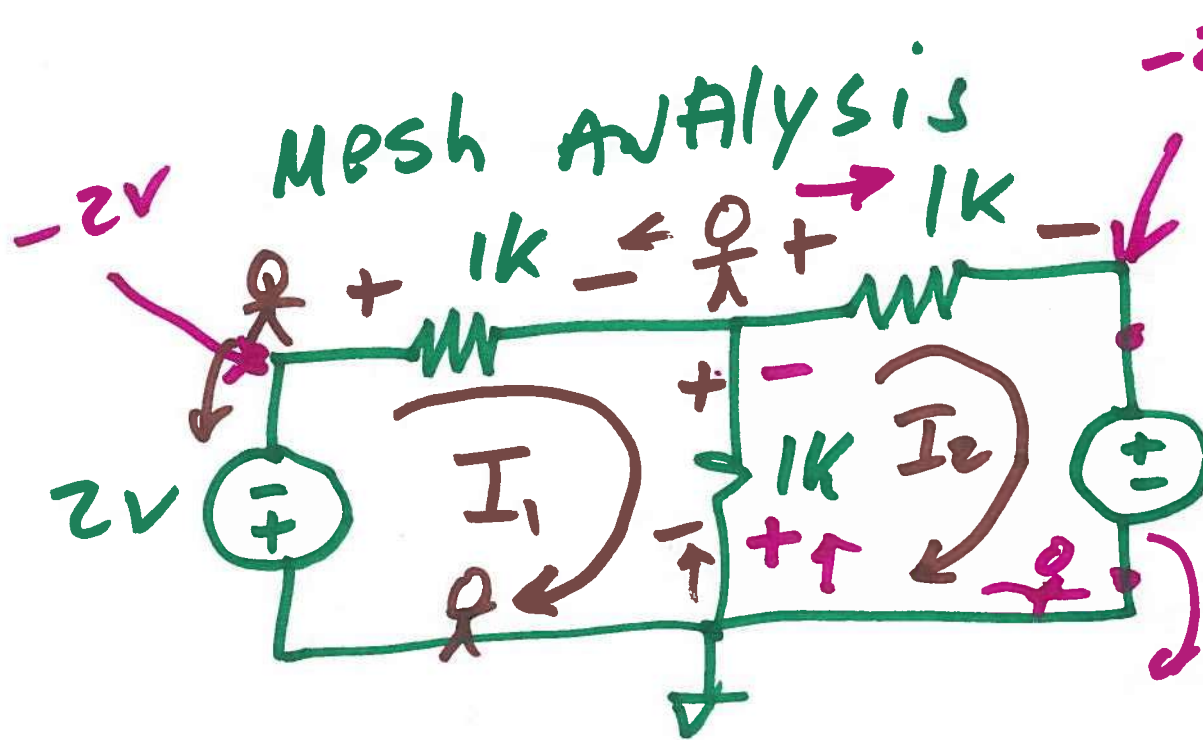



# EE 221 Circuits 11
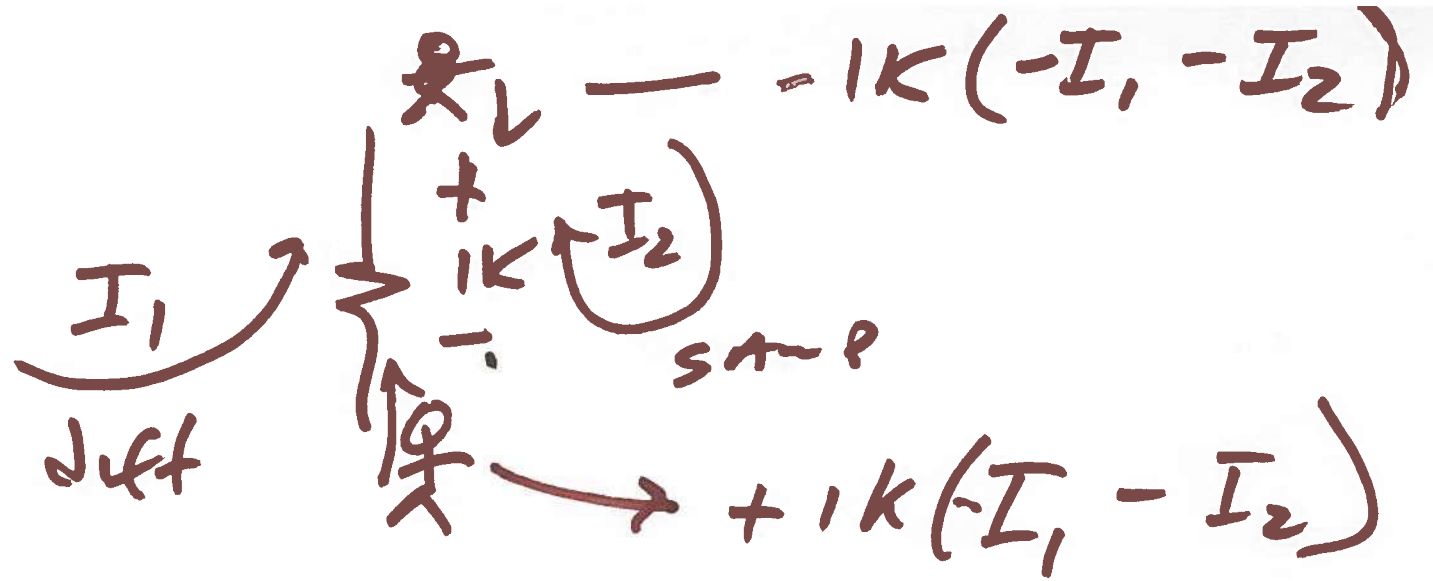
## Lecture 2

Jan. 28, 2019




$$\begin{aligned}
 & 1k \cdot I_1 + 2 + 1k(I_1 - I_2) - 2V - k(I_2 - I_1) \\
 & = 0 \\
 & -1k \cdot I_2 - (-2V) + 1k(I_1 - I_2) \\
 & -1k(I_2 - I_1) = 0
 \end{aligned}$$



$$I \downarrow \left\{ \begin{array}{l} + \\ - \end{array} \right. V = IR$$

$$\left( \begin{array}{l} + \\ - \end{array} \right) \uparrow I$$

$$V = R \cdot (-I)$$

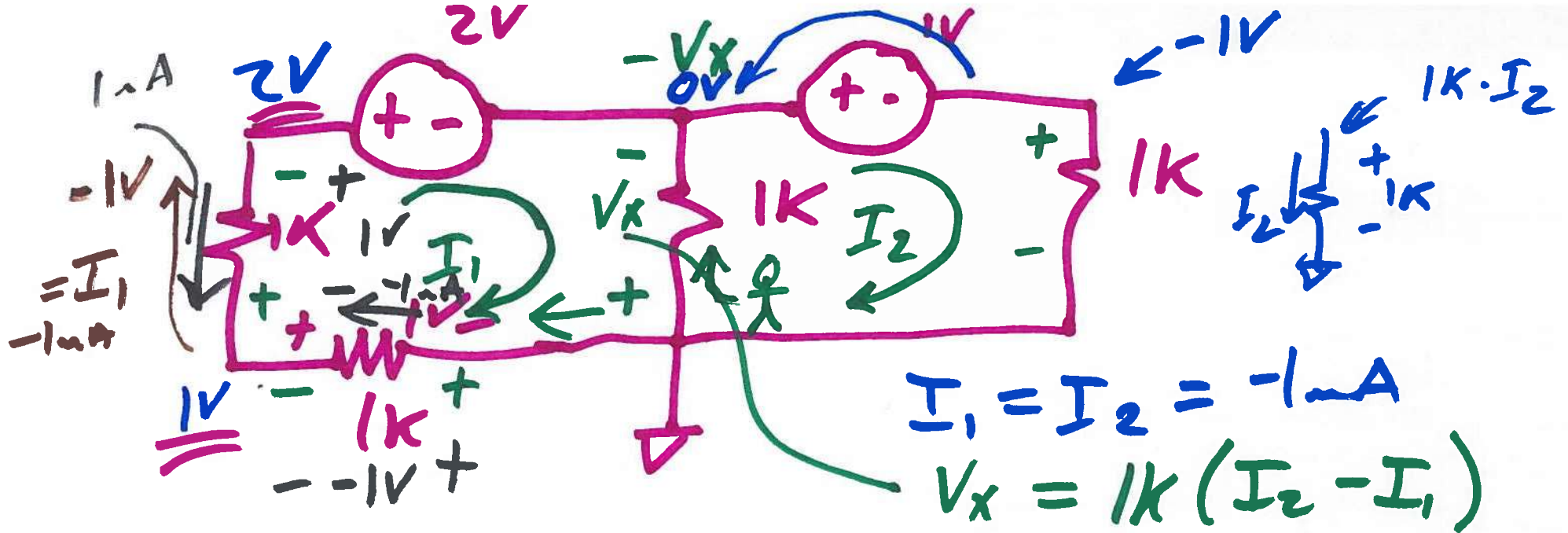

$$-1\text{k} \cdot I_1 - 1\text{k} I_1 - 2\text{V} + V_x = 0$$

$$-V_x - 1\text{V} - 1\text{k} I_2 = 0$$

$$\rightarrow -2\text{k} I_1 - 2 + 1\text{k} (I_2 - I_1) = 0$$

$$-3\text{k} I_1 - 2 + 1\text{k} I_2 = 0$$

$$I_2 = 2\text{mA} + 3I_1$$

3)

$$1k(I_1 - I_2) - 1 - 1kI_2 = 0$$

$$1kI_1 - 2kI_2 - 1 = 0$$


$$1kI_1 - 2(2 + 3k) - 1 = 0$$

$$1kI_1 - 4 - 6kI_1 - 1 = 0$$

$$-5kI_1 = 5$$

$$I_1 = -1 \mu A$$

$$I_2 = -1 \mu A$$

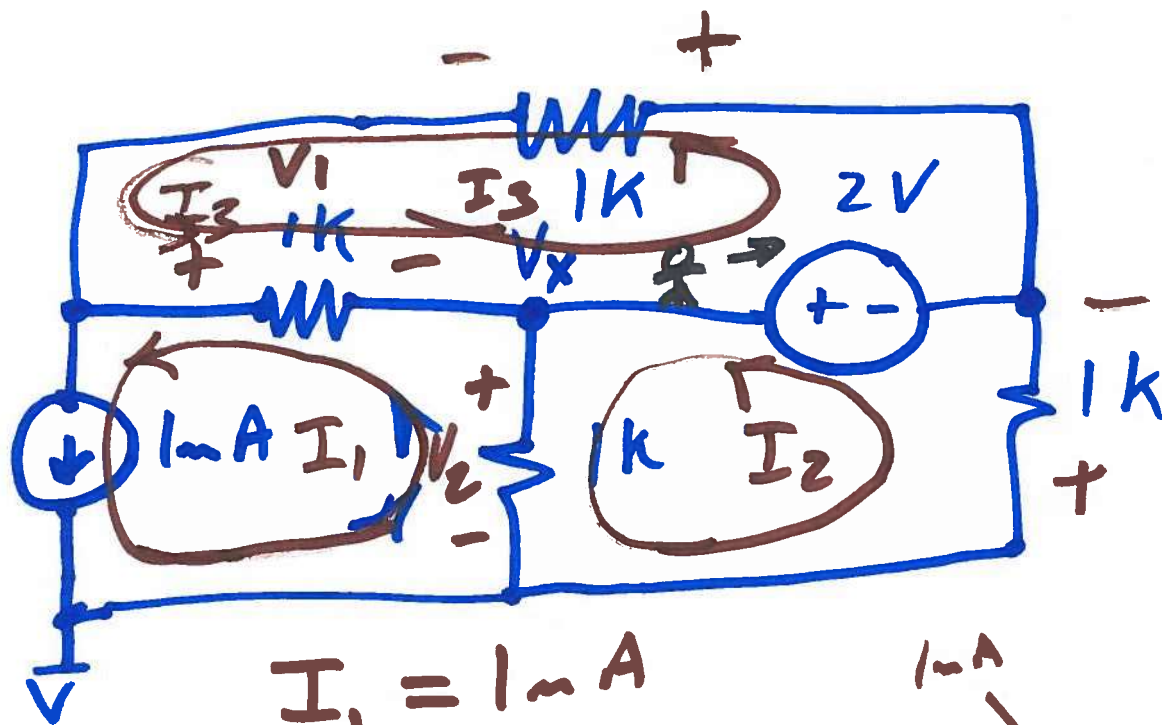

$$I \downarrow \begin{matrix} + \\ R \\ - \end{matrix} v = IR$$

$$I \uparrow \begin{matrix} + \\ R \\ - \end{matrix} v = -I \cdot R$$

$$I_1 = 1 \text{ mA}$$

$$V_1 = 1\text{K}(I_3 - I_1)$$

$$V_2 = 1\text{K}(I_2 - I_1)$$


$$-2 - 1\text{K}I_3 - 1\text{K} \cdot (I_3 - I_1) = 0$$

$$2 + 1\text{K}I_3 + 1\text{K}(I_3 - I_1) = 0$$

$$I_3: -2 - 1\text{K}I_3 - 1\text{K}(I_3 - I_1) = 0$$

$$I_2: -2 + 1\text{K}I_2 + 1\text{K}(I_2 - I_1) = 0$$

5)

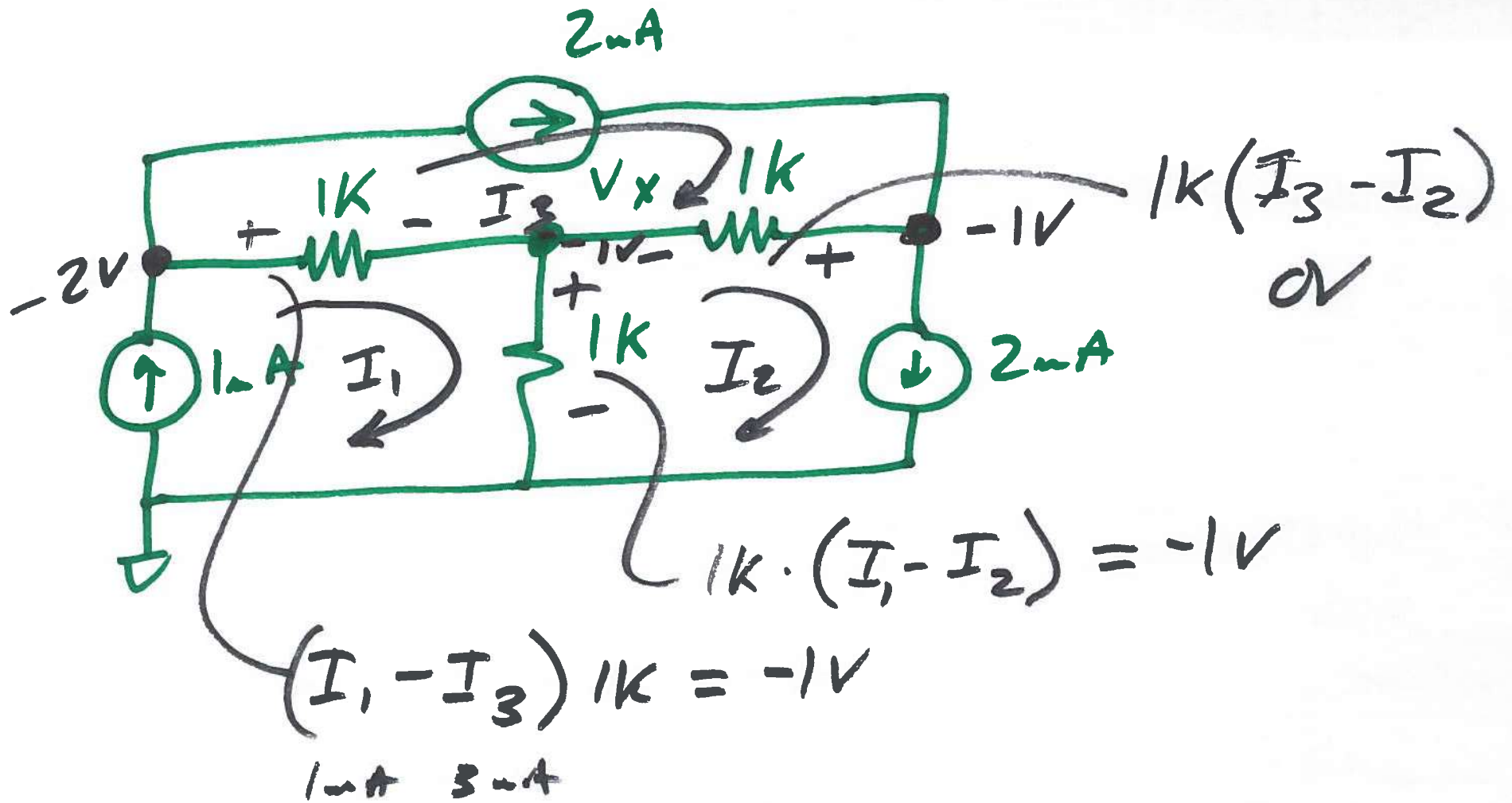

6)