

EE 221


Circuits 1

Lecture 5


Feb. 6, 2019

$$R_{TH} = \frac{V_{TH}}{I_N} = \frac{V_{OC}}{I_{SC}} = \frac{-1}{-\frac{1}{2} \text{ A}} = 2 \text{ k}$$

$$R_{TH} = 2 \text{ k}$$

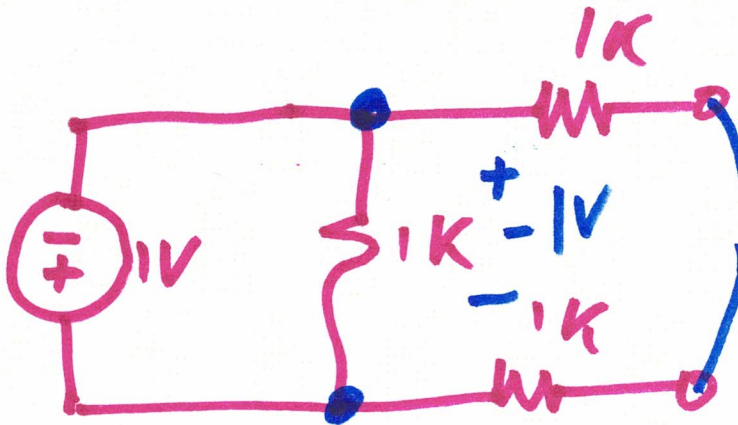

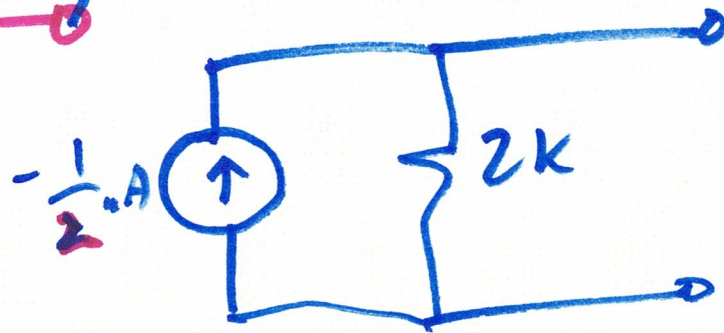
$$I_{SC} = I_N = \frac{-1 \text{ V}}{2 \text{ k}} = -\frac{1}{2} \text{ A}$$




Quiz #4 EE 221 Spring 2019 Name: _____

Closed book and notes.


Show your work for credit.

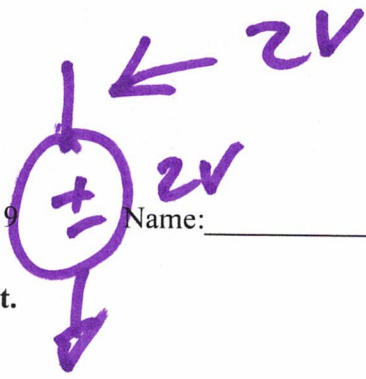

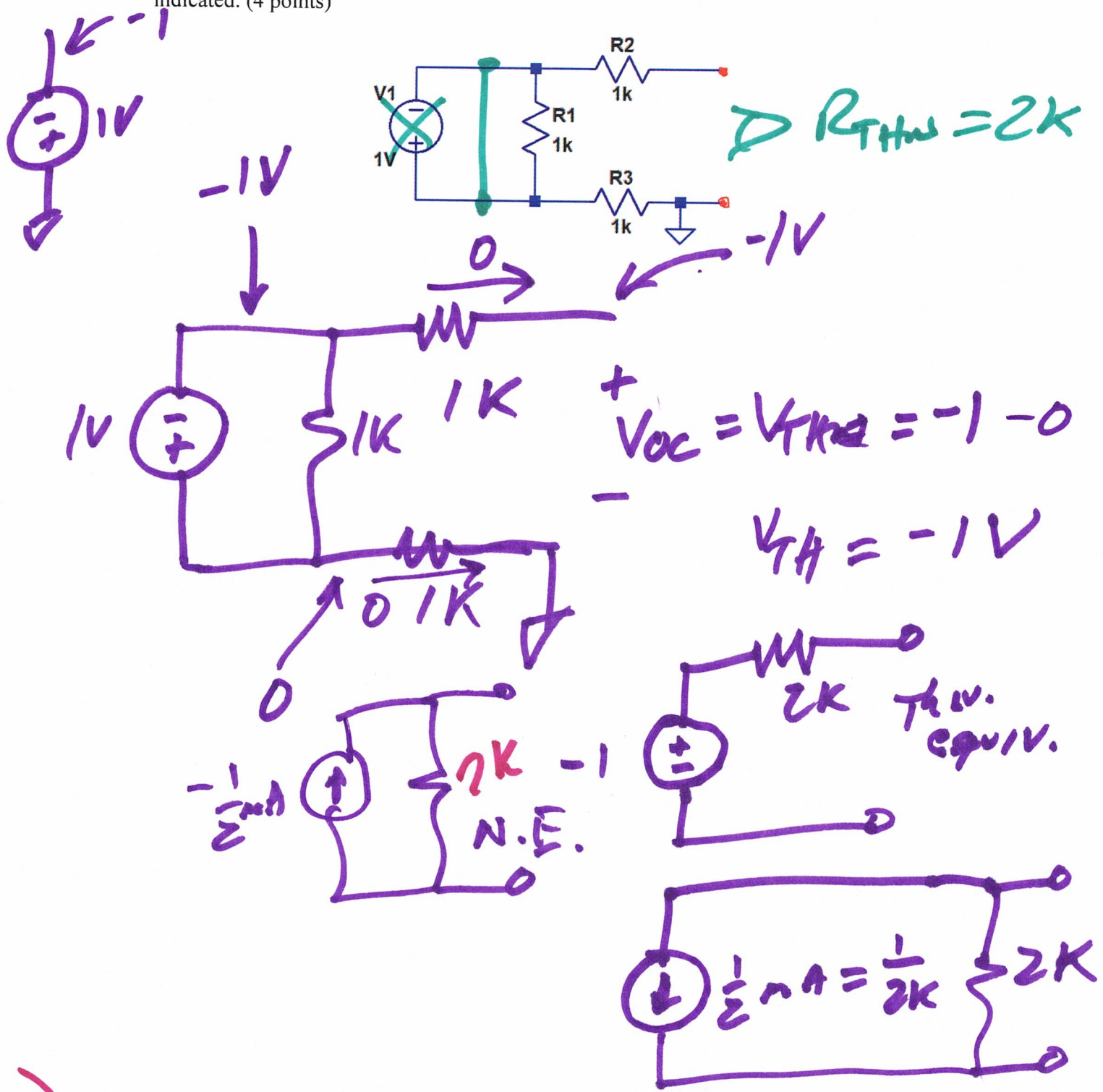1. Find the Thevenin and Norton equivalents of the following circuit at the red terminals indicated. (4 points)



2)

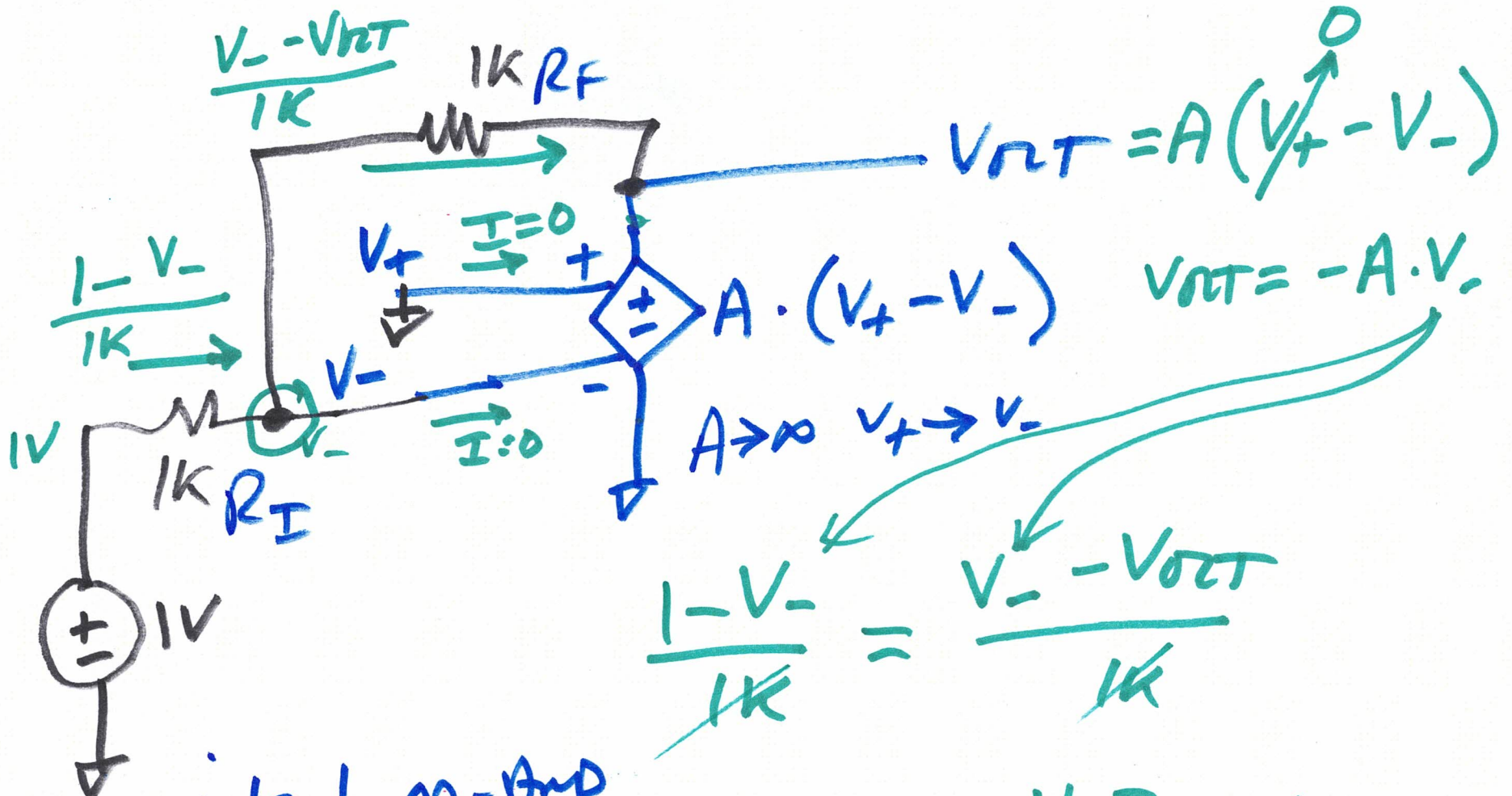

$$\frac{1 - V_-}{1k} = \frac{V_- - V_{OUT}}{1k}$$

ideal op-amp
 $A \rightarrow \infty$

$$1 + \frac{V_{OUT}}{A} = -\frac{V_{OUT}}{A} - V_{OUT}$$

$$-1 = V_{OUT} \left(\frac{1}{A} + \frac{1}{A} + 1 \right)$$

$$= -1 = -\frac{R_F}{R_I}$$

$$V_{OUT} = \frac{-1}{\frac{1}{A} + \frac{1}{A} + 1}$$


3)

Inverting op-amp

1) find V_+

2) set $V_+ = V_-$

3) KCL at inverting term

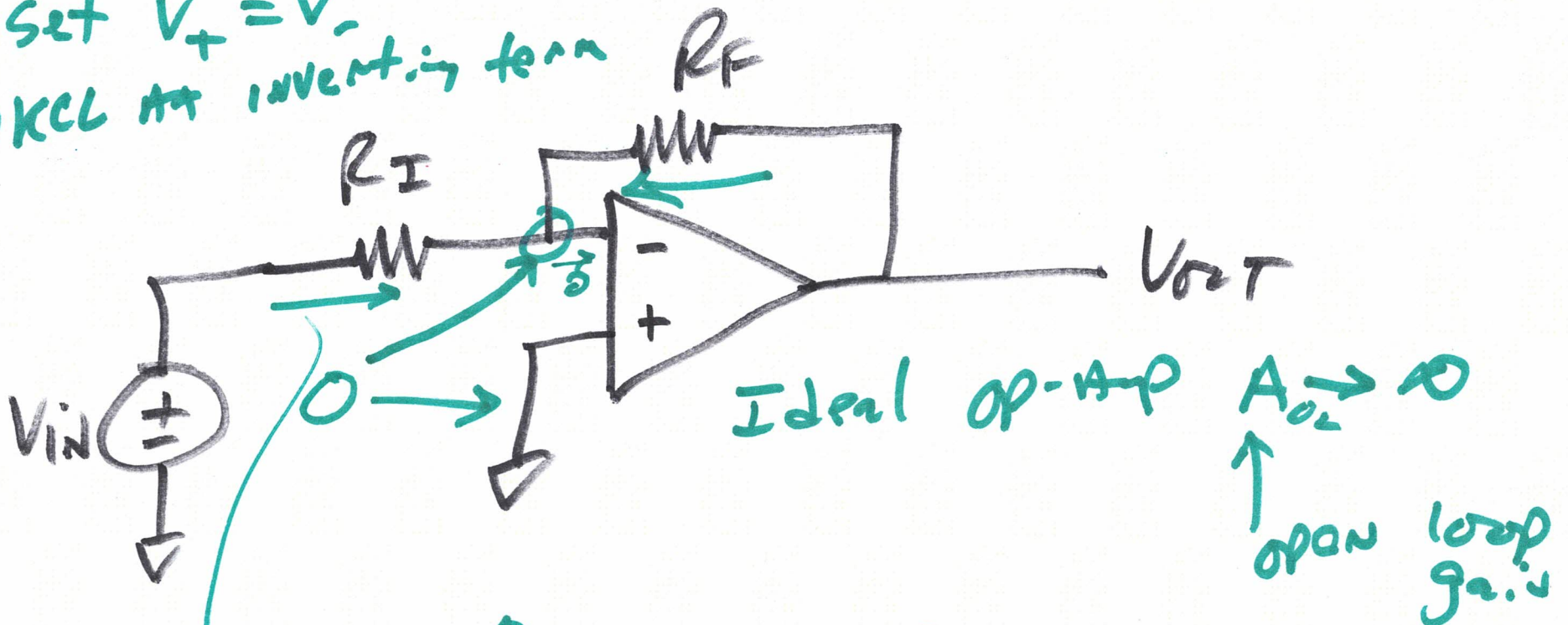


$$\frac{V_{IN} - 0}{R_I} + \frac{V_{OUT} - 0}{R_F} = 0$$

$$\frac{V_{OUT}}{V_{IN}} = -\frac{R_F}{R_I}$$

4)

NON-INVERTING Amplifier

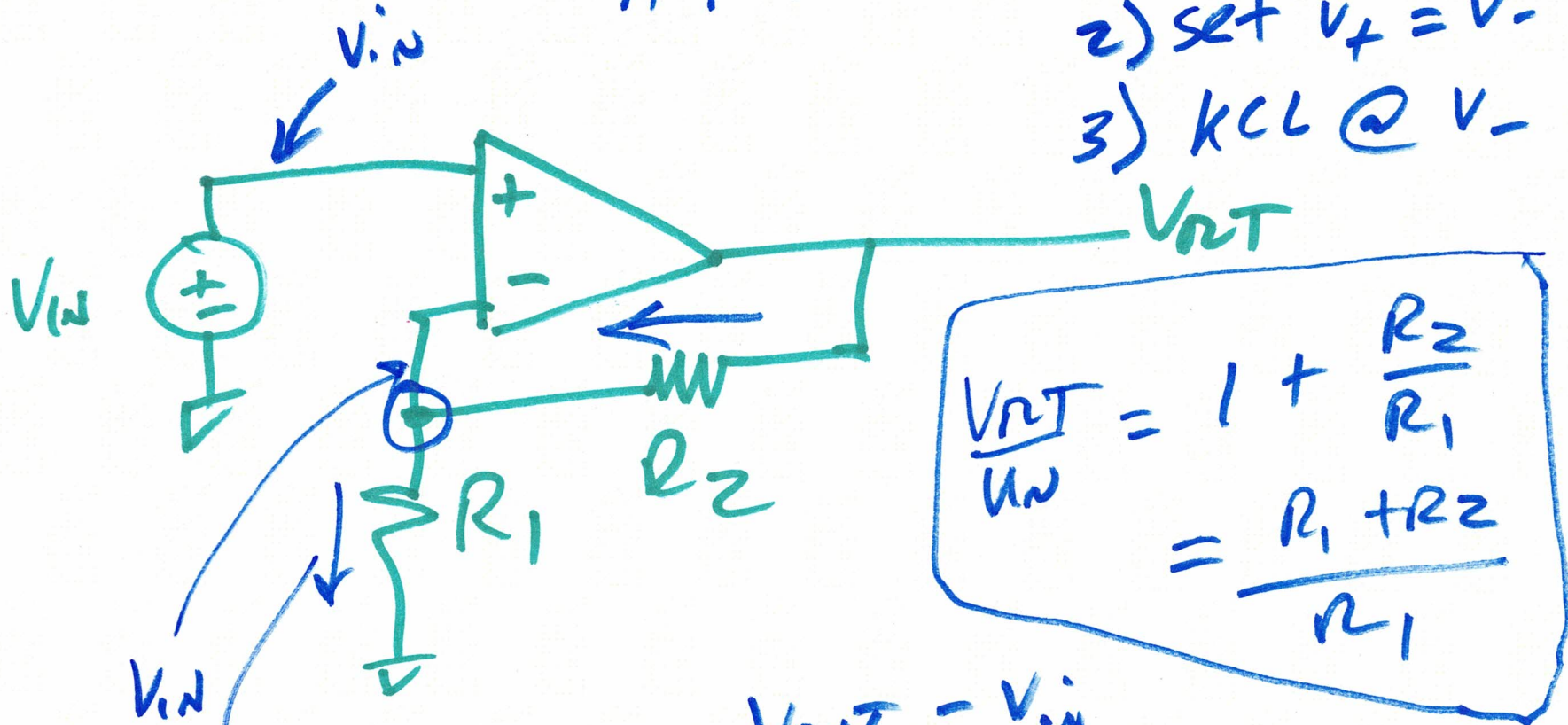- 1) find V_+
- 2) set $V_+ = V_-$
- 3) KCL @ V_-




$$\frac{V_{OUT}}{I} = 1 + \frac{R_2}{R_1} = \frac{R_1 + R_2}{R_1}$$

$$\frac{V_{in}}{R_1} = \frac{V_{OUT} - V_{in}}{R_2}$$

$$V_{in} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_{OUT}}{R_2}$$

5)

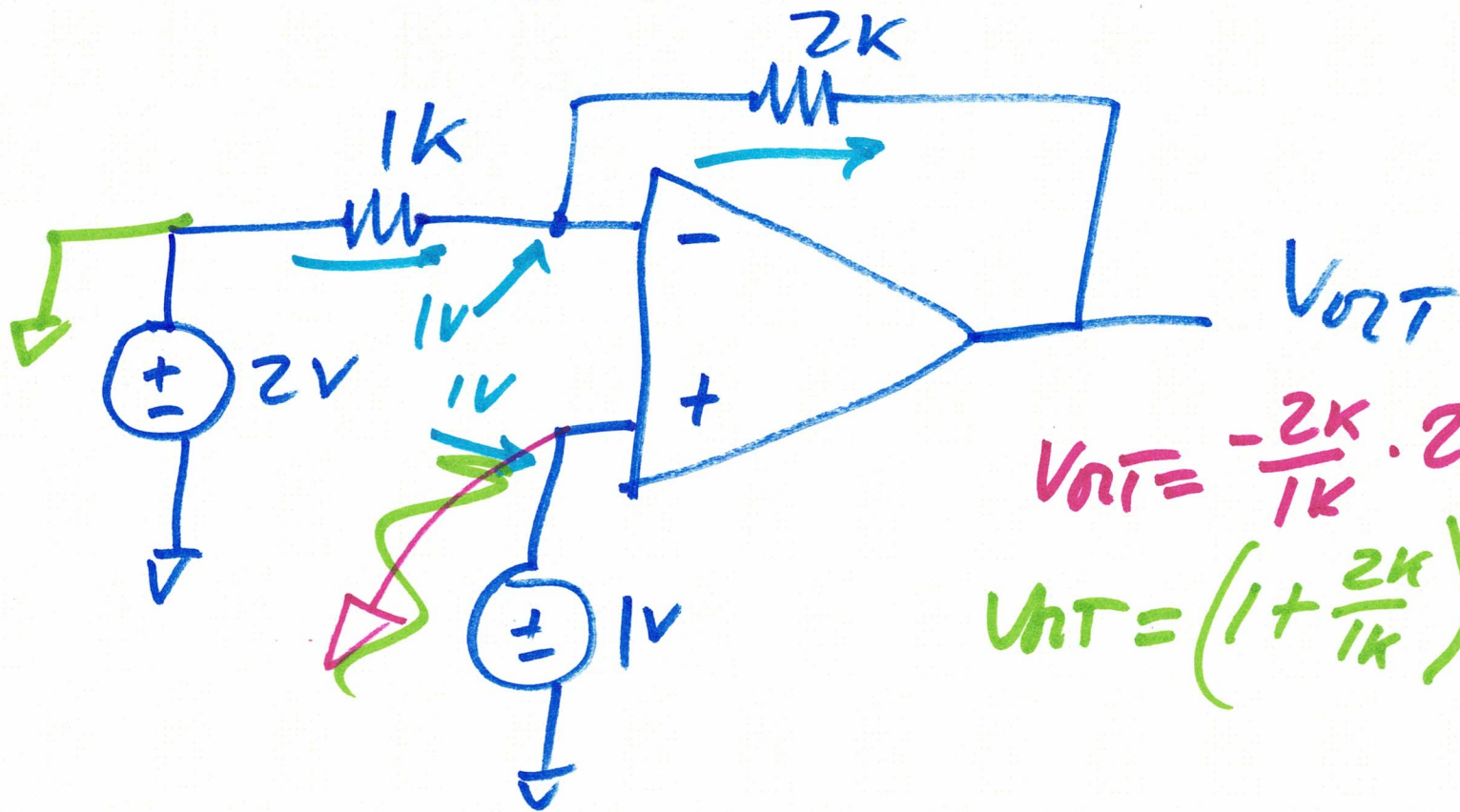

$$V_{out} = -\frac{2k}{1k} \cdot 2V = -4V$$

$$V_{out} = \left(1 + \frac{2k}{1k}\right) 1V = 3V$$

-1V
YAY!

$$\frac{2-1}{1k} = \frac{1 - V_{out}}{2k} = 1 = \frac{1}{2} - \frac{1}{2} V_{out}$$

$$V_{out} = -1V$$