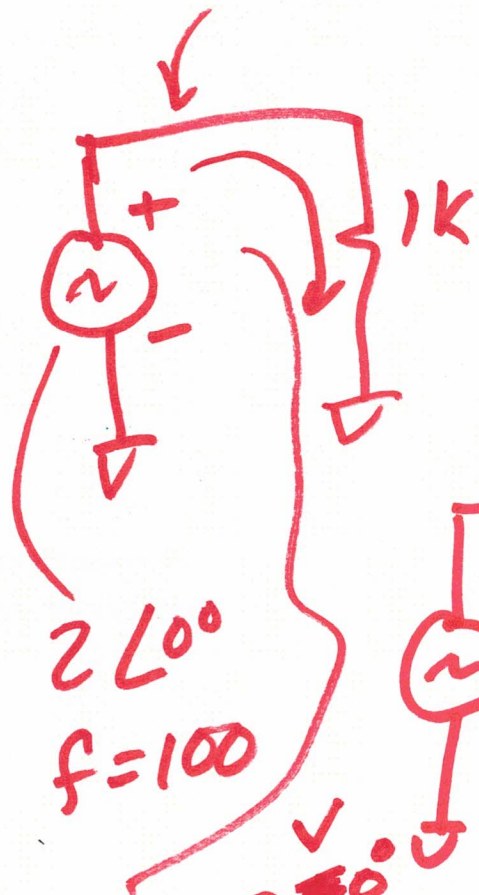


EE 221 Circuits II

Feb. 13, 2019

Lecture 7


$2V \sin @ 100Hz$



2V $\angle 0^\circ$
f=100

$$I = \frac{2V \angle 0^\circ}{1k \angle 0^\circ} = 2mA \angle 0^\circ$$

$I = 2mA \angle 0^\circ$

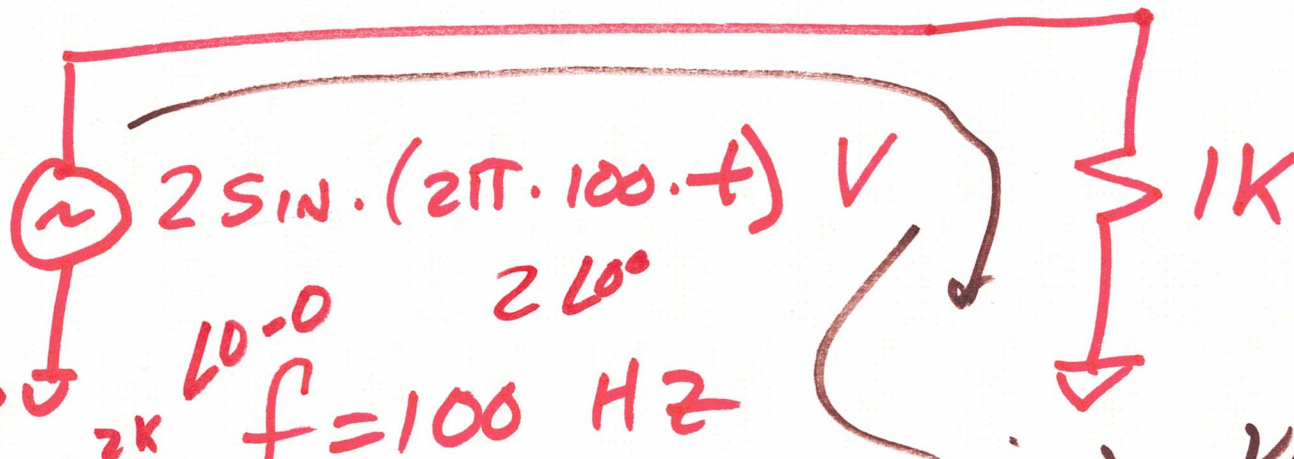


2V $\angle 0^\circ$
f=100 Hz

$$T = \frac{1}{f} = 10ms$$


$$i(t) = \frac{V(t)}{R} = \frac{2 \sin(2\pi \cdot 100 \cdot t)}{1k}$$

$$i(t) = 2mA \sin(2\pi \cdot 100 \cdot t)$$

$s = \sigma + j\omega$


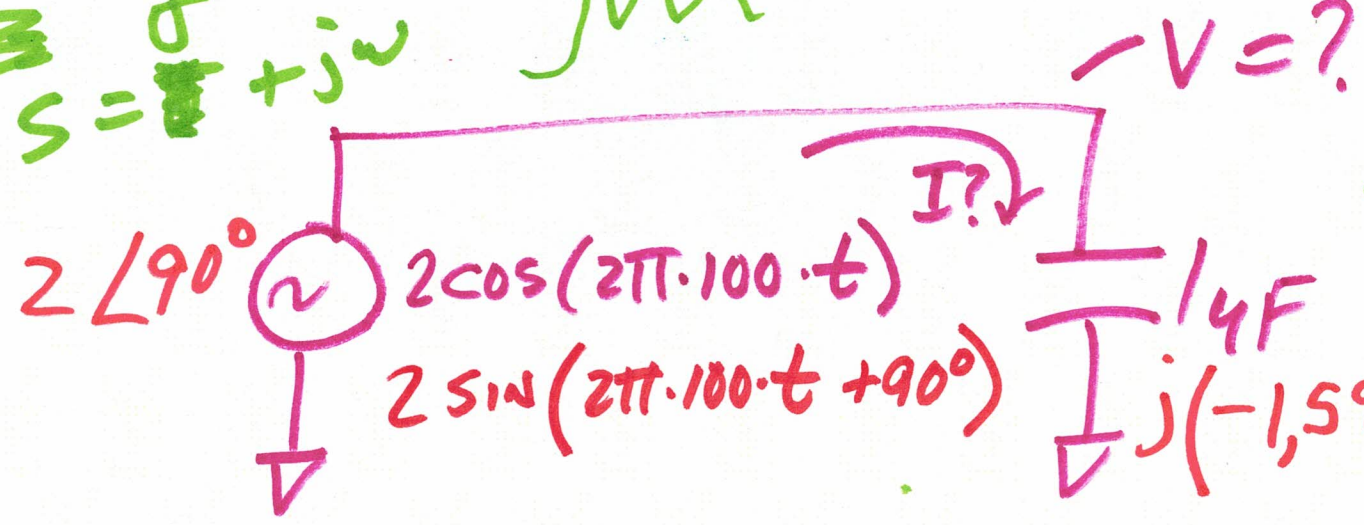


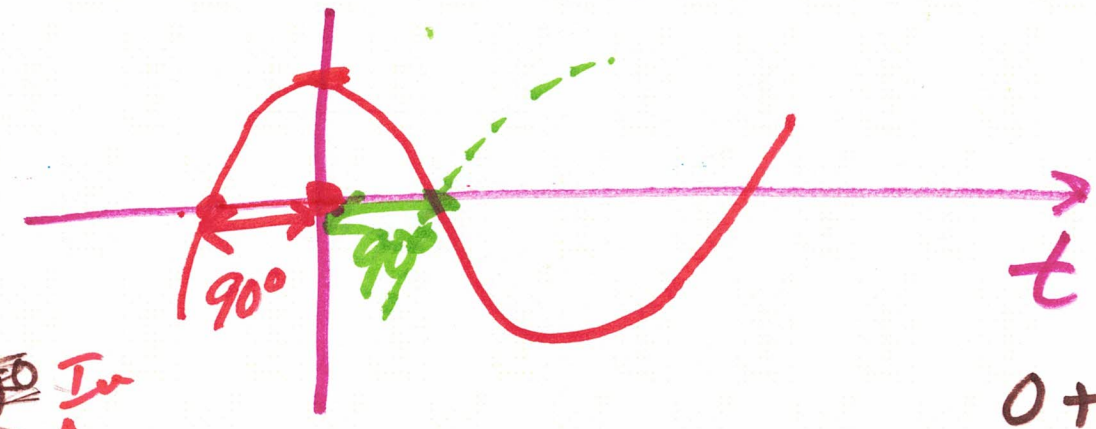$Z_C = \frac{1}{j \cdot 2\pi \cdot f \cdot C}$
 $\frac{1}{j \cdot 2\pi \cdot 100 \cdot 10^{-6}}$
 $= \frac{1}{j\omega C}$
 $= \frac{1}{sC}$



$Z_C = \frac{1}{j\omega C}$

$0 + j(-1.592k)$

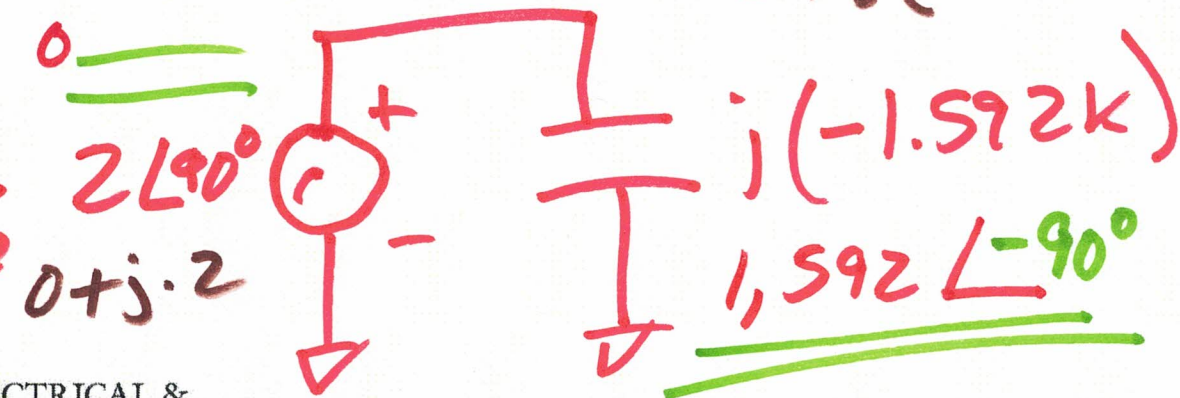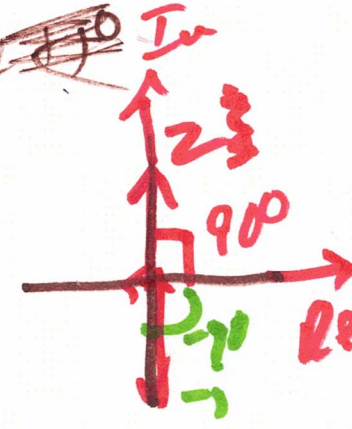

2)


$$\frac{A \angle \theta_1}{B \angle \theta_2} = \frac{A}{B} \angle \theta_1 - \theta_2$$

$$x = r \cos \theta$$

$$r = \sqrt{y^2 + x^2}$$

$$A \angle \theta_1 \cdot B \angle \theta_2 = AB \angle \theta_1 + \theta_2$$
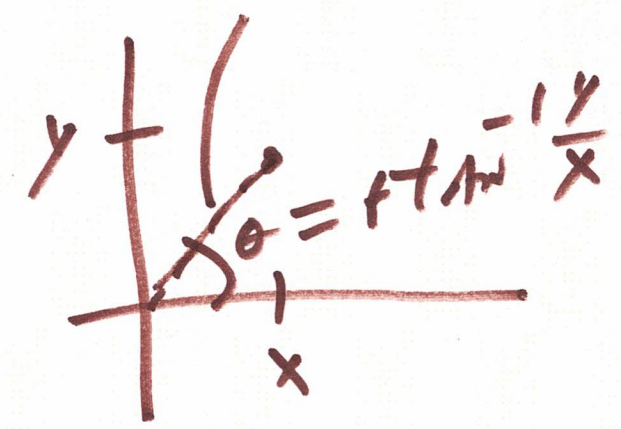
$$\vec{I} = 1.26 \mu A \angle 180^\circ = x + jy$$



$$= 1.26 \mu A \sin(2\pi \cdot 100t + 180^\circ)$$

$$= -1.26 \mu A \sin(2\pi \cdot 100t)$$

$$r = \sqrt{x^2 + y^2}$$

$$\vec{I} = 1.592 \angle -90^\circ \theta = \tan^{-1} \frac{y}{x}$$


$$2 \angle 90^\circ = \vec{V}$$

$$2 \sin(2\pi \cdot 100t + 90^\circ)$$

$$2 \cos(2\pi \cdot 100t)$$

in phasor


$= R + j \text{ reactance}$

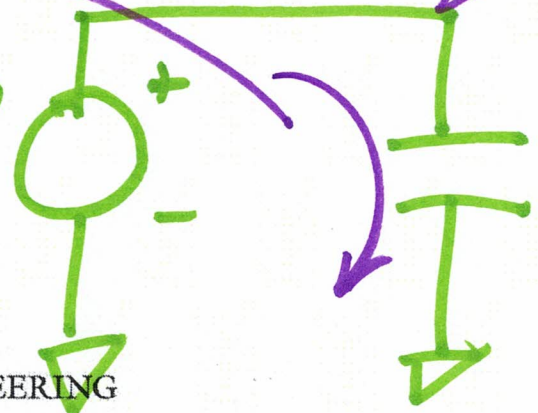


$2 \angle 90^\circ$

$1.592 \angle -90^\circ$

3)

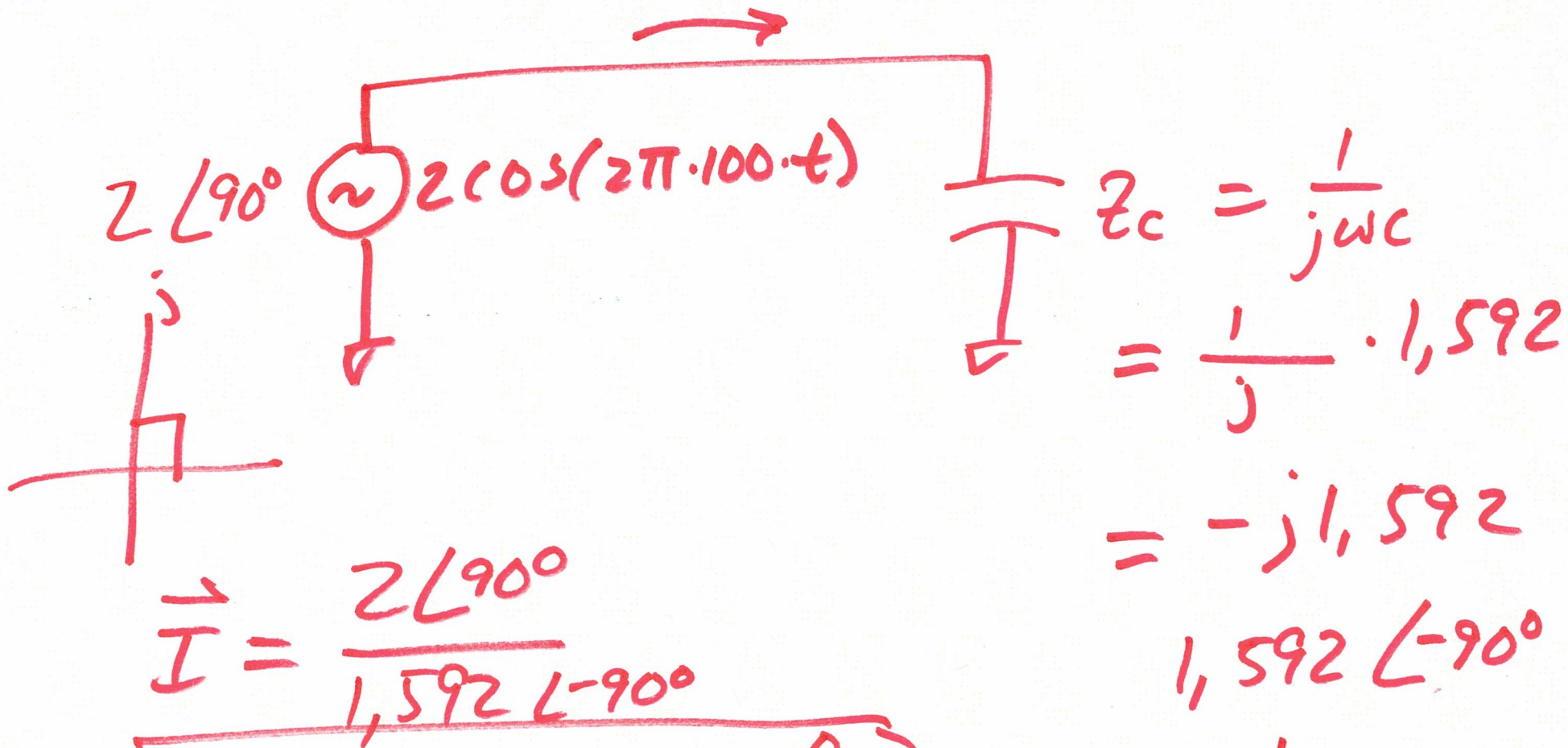


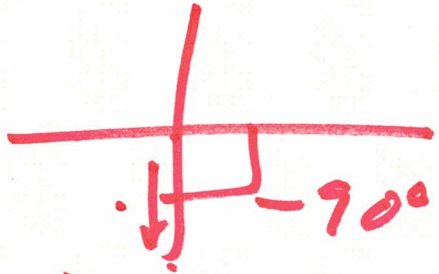
$$\vec{I} = \frac{2}{1,592} \angle 180^\circ \text{ A}$$



$$i(t) = \frac{2}{1,592} \sin(2\pi \cdot 100 \cdot t + 180)$$

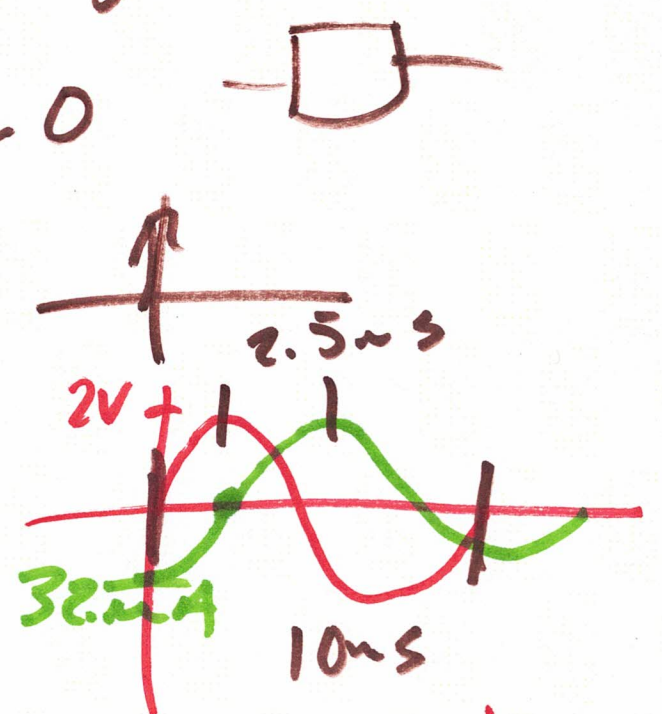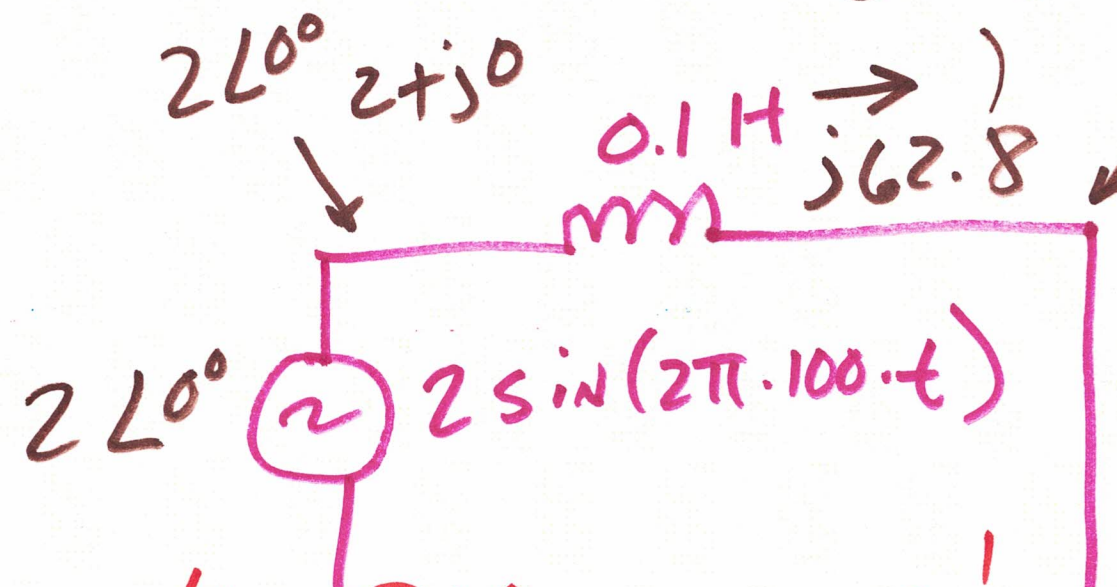4)

mm
 $Z_L = j\omega \cdot L$
 $62.8 \angle 90^\circ$ $j \cdot 2\pi \cdot 100 \cdot 0.1$
 $j62.8 \Omega$




$90^\circ = \frac{t_d}{10 \mu s} \cdot 360$
 $f = 100$
 $\theta = \frac{t_d}{T} \cdot 360$

$T = 10 \mu s = \frac{1}{f}$
 $I = \frac{2 \angle 0^\circ}{62.8 \angle 90^\circ} = 32 \text{ mA} \angle -90^\circ$


$t_d = \frac{T}{4} = 2.5 \mu s$

$i(t) = 32 \text{ mA} \sin(2\pi \cdot 100 \cdot t - 90^\circ)$

5)

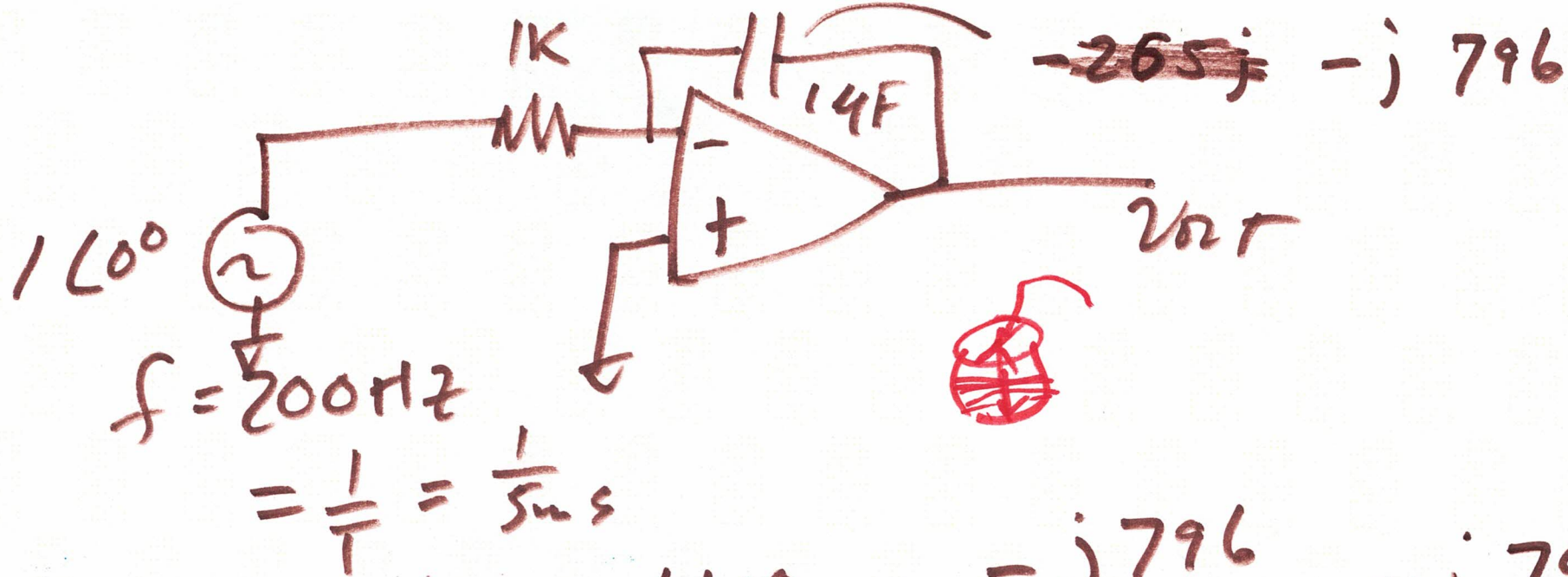

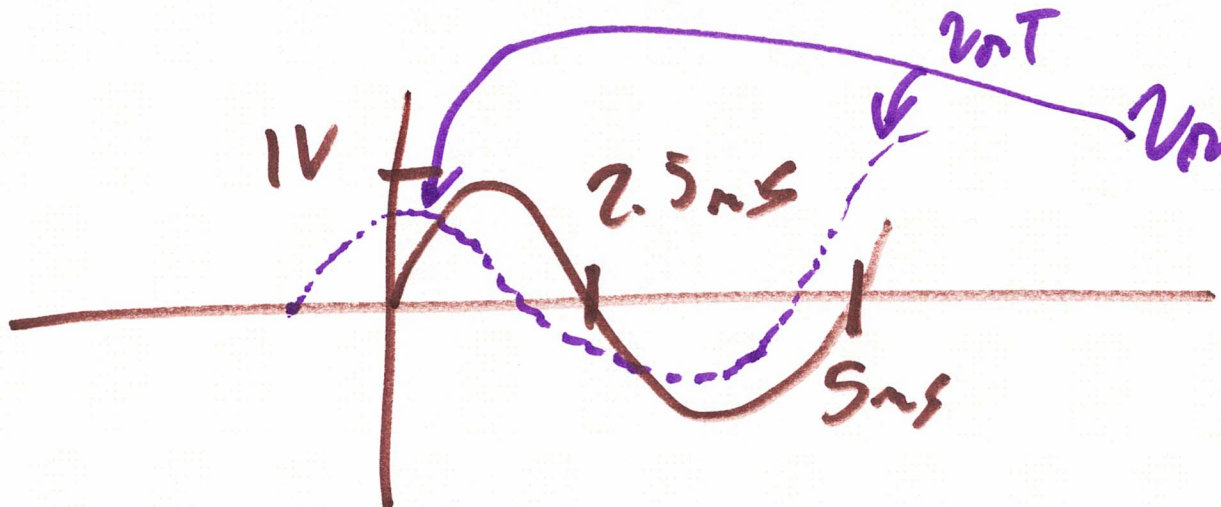
$$V_{out} = 100 = - \frac{-j796}{1k} = j.796$$



$$V_{out} = 0.796V \cdot \sin(2\pi \cdot 200 \cdot t + 90)$$


6)

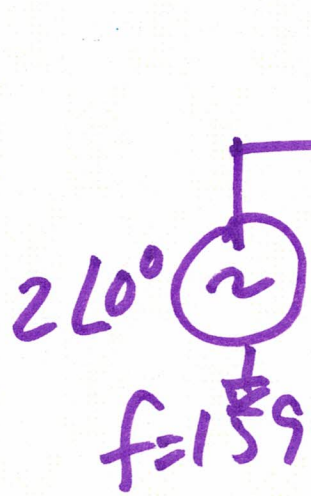

$$0 + j(-1) \quad \downarrow$$

$$1 \angle -90^\circ$$
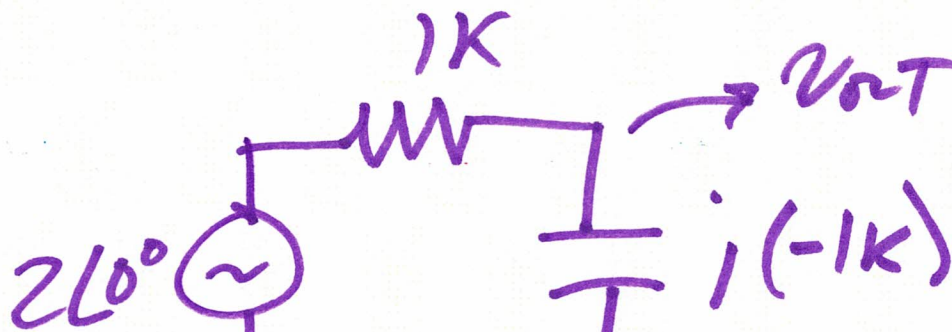
$$Z_C = \frac{-j}{2\pi \cdot 159 \cdot 10^{-6}} \approx 1k \cdot (-j)$$




$$V_{out} = 2\angle 0^\circ \cdot \frac{0 + j(-1k)}{1k + j(-1k)}$$

$$\tan^{-1} \frac{-1}{1} = -\tan^{-1} 1 = -45^\circ$$

$$1 + j(-1) = \sqrt{(1)^2 + (-1)^2} = \sqrt{2}$$
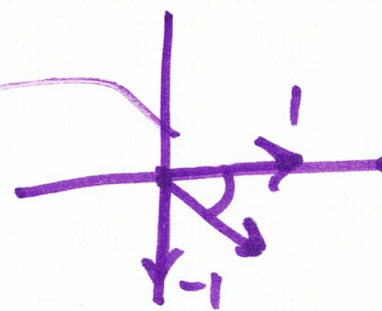
$$= \frac{2\angle 0^\circ \cdot 1 \angle -90^\circ}{\sqrt{2} \angle -45^\circ}$$



$$= \frac{2}{\sqrt{2}} \angle -45^\circ$$

7)