


# EE 221 Circuits II

Lecture 9

Feb. 25, 2019

$$2\pi f = 2.5 \times 10^4$$

$$f = \frac{2.5 \times 10^4}{6.28}$$

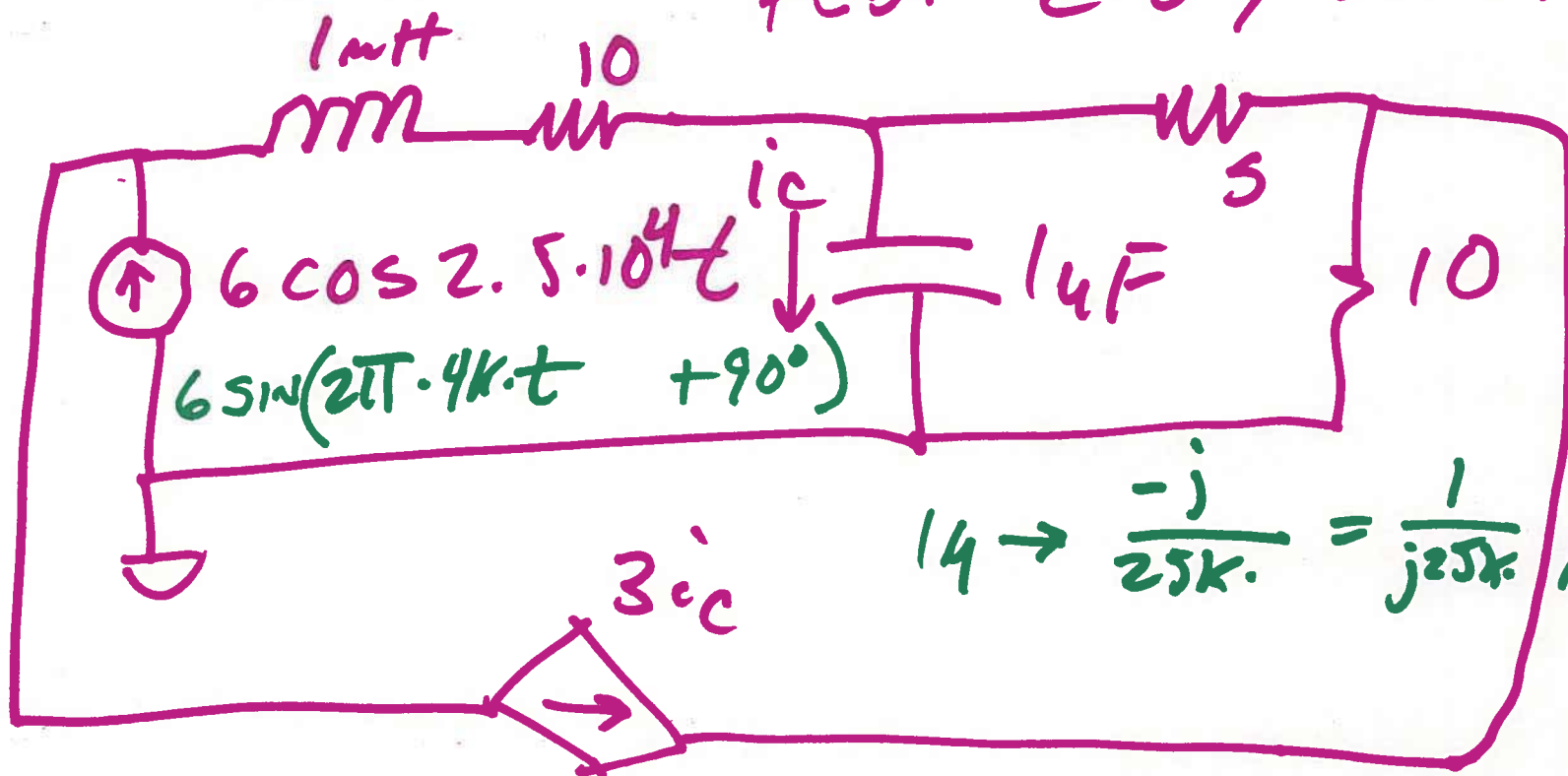


$$1\mu \rightarrow \frac{-j}{25k} = \frac{1}{j25k} \cdot 10^{-6} = -j40$$

$$1m\Omega \rightarrow j \cdot 2\pi \cdot 4k \cdot 0.001 = j \cdot 25k \cdot 0.001 = \boxed{25j = z_L}$$

$$25000 \times 0.001$$

1)

$26.92 \angle 68.2^\circ$

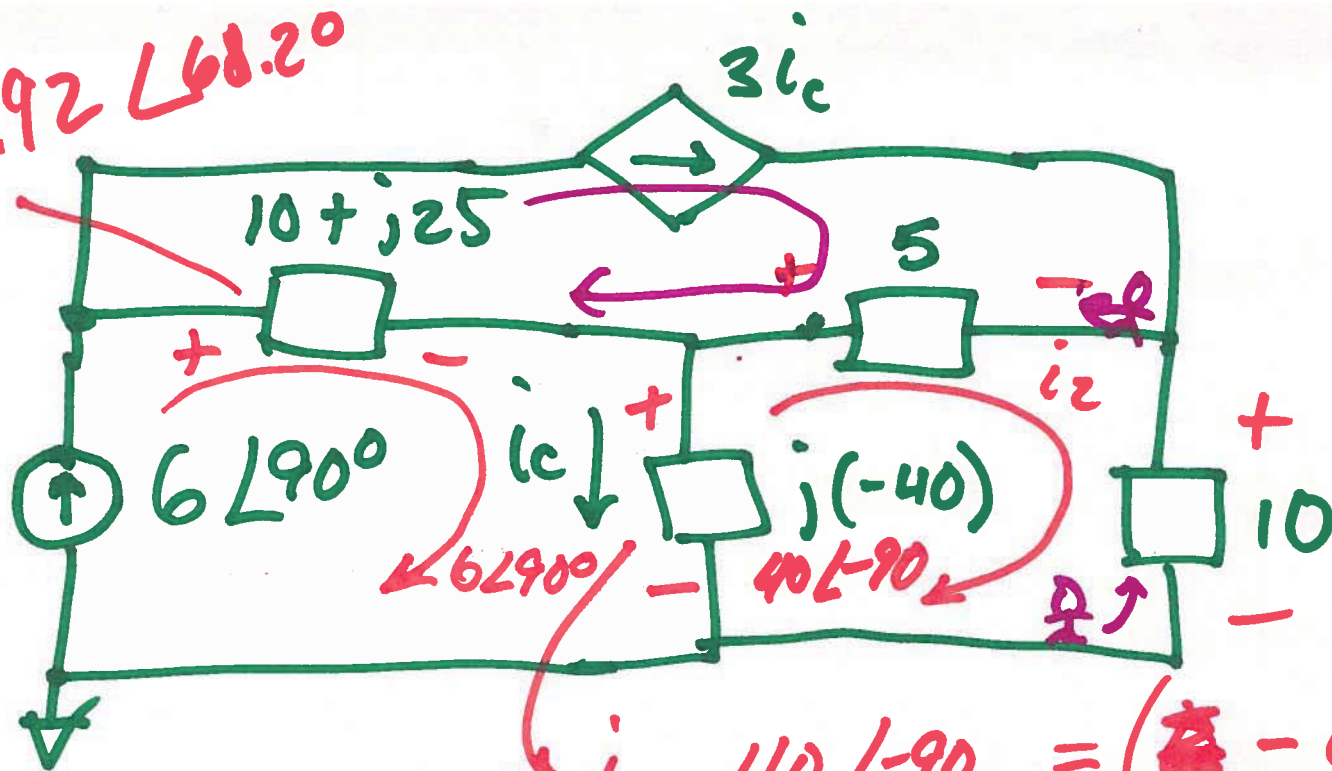

$$i_c \cdot 40 \angle -90 = \left( \frac{6 \angle 90}{6 \angle 90} - i_2 \right) \cdot 40 \angle -90$$

$$10 \cdot i_2 + 5(i_2 - 3i_c) - i_c \cdot j(-40) = 0$$

$$i_c = 6 \angle 90 - i_2 \rightarrow i_2 = 6 \angle 90 - i_c$$

$$15i_2 - i_c(15 - 40j) = 0$$

$$15(6 \angle 90 - i_c) - i_c \cdot 15 + i_c \cdot 40j = 0$$

$$90 \angle 90 + i_c (-30 + 40j) = 0$$

$$-90 \angle 90$$

$$50 \angle 126.7^\circ$$



↑ NO!



$$i_c \cdot 50 \angle 126.7^\circ = 90 \angle 270^\circ \quad 1.8A$$


$$i_c = \frac{90 \angle 270^\circ}{50 \angle 126.7^\circ} = \frac{9}{5} \angle 143.3^\circ$$


$$90 \sin(25kt + 90) \quad i_c(t) = 1.8 \sin(25kt + 143.3^\circ)$$

$$-90 \sin(25kt + 90)$$

$$= 90 \sin(25kt + 270)$$

A

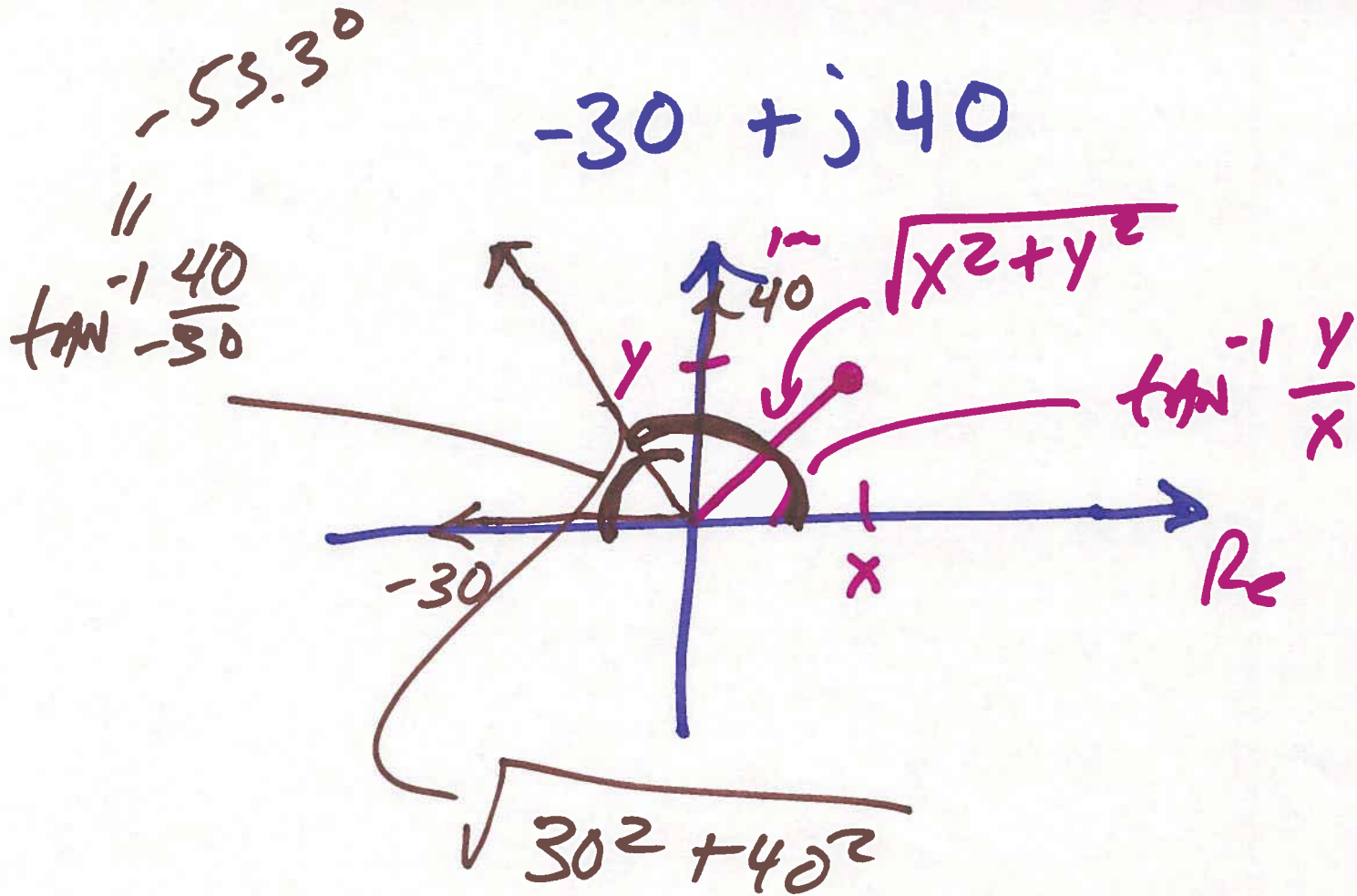


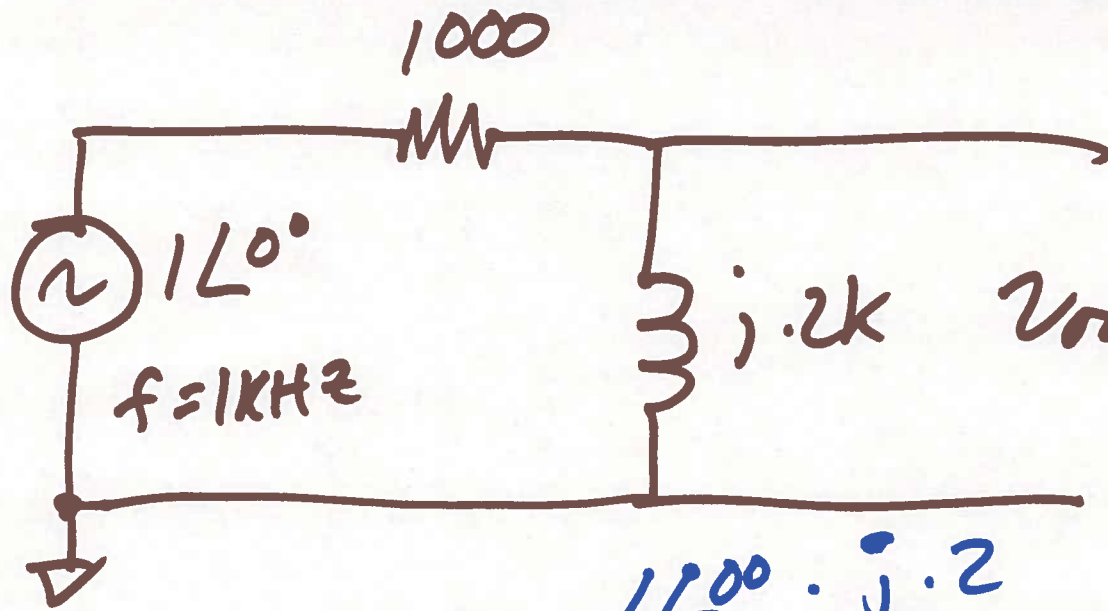

$$v_{out} = \frac{120 \cdot j2k}{1k + j2k}$$

$$v_{out} = \frac{1200 \cdot j \cdot 2}{1 + j \cdot 2} = \frac{120 \cdot 2 \angle 90^\circ}{\sqrt{5} \angle 63.4^\circ}$$

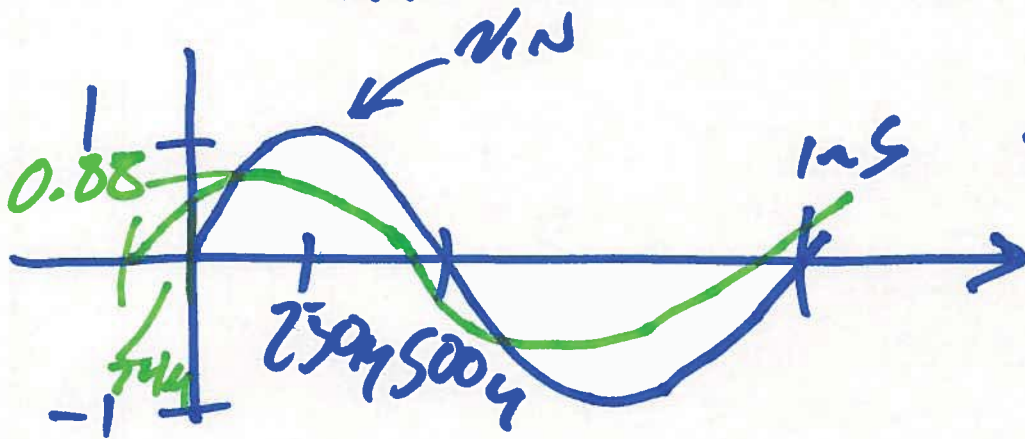
$$v_{out} = 0.88 \sin(2\pi \cdot 1k \cdot t + 26.6) = \frac{0.88 \angle 26.6}{0.88}$$




$$t_d \cdot f \cdot 360 = \frac{t_d}{T} \cdot 360 = 26.6$$

$$t_d = \frac{26.6}{360 \cdot 1k} = 74.5$$

5)

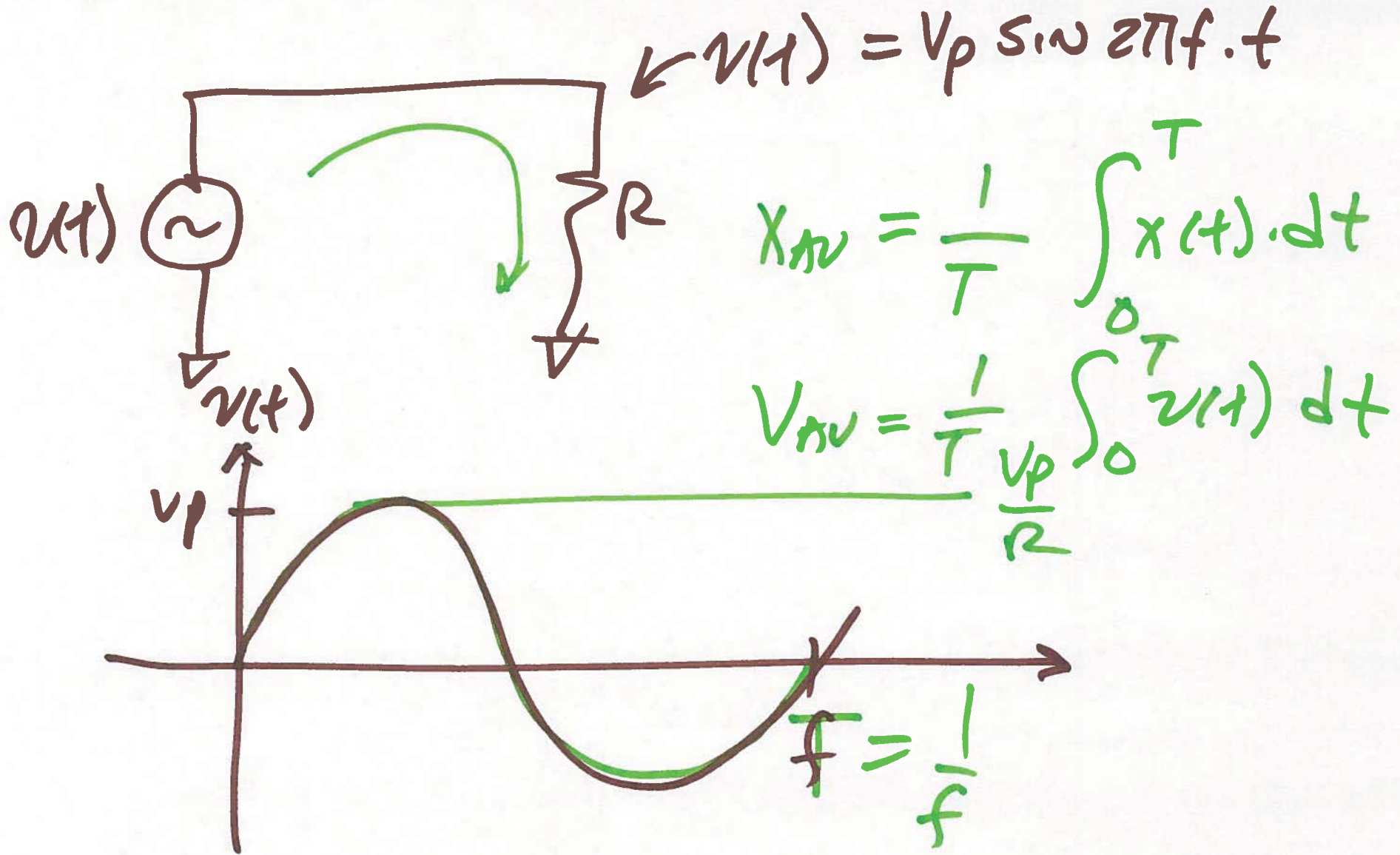

b)

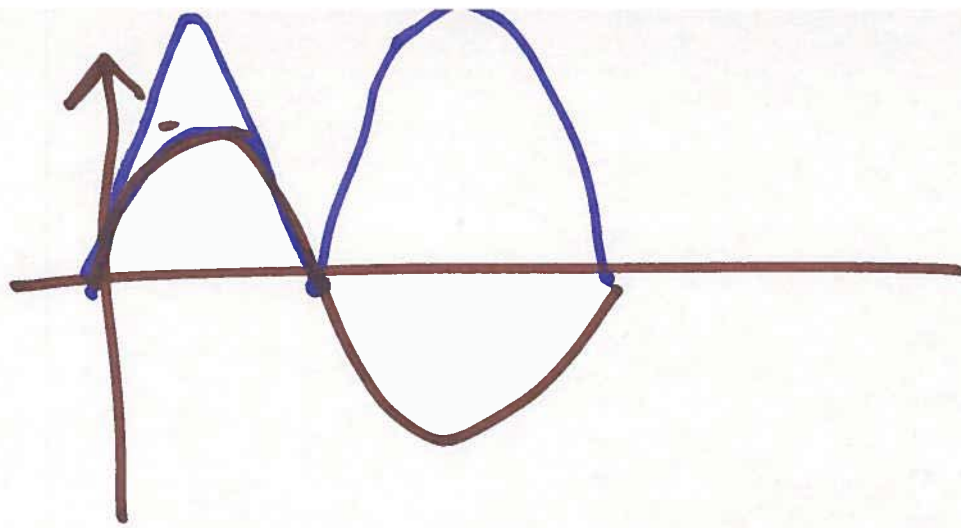

$$P = \frac{V^2}{R}$$

## Root MEAN SQUARE

$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T V_p^2 \sin^2(2\pi f t) \cdot dt}$$

$$= \sqrt{\frac{V_p^2}{2T} \int_0^T (1 - \cos(4\pi f \cdot t)) dt}$$

$$V_{RMS} = \sqrt{\frac{V_p^2}{2}}$$

$$V_{RMS} = \frac{V_P}{\sqrt{2}}$$

OUTPUT of wall socket

$$120V \text{ RMS } \pm 5\%$$

$$114 \rightarrow 124$$

$$V_P = \sqrt{2} \cdot 120 = 170$$

$$v(t) = 170 \sin(2\pi \cdot 60 \cdot t)$$



POWER in resistive load AC

$$P_{AC} = \frac{V_{Rms}^2}{R}$$

power in resistive load DC

$$P_{DC} = \frac{V_{dc}^2}{R}$$

9)