

EE 221 Circuits II

Feb. 26, 2020


$$170 \sin(2\pi 60 \cdot t + 240)$$

$$V_{p3} =$$

Lecture 10

$$V_{X3}$$

$$V_{X1} = V_{p1} \cdot \frac{5}{5+10}$$

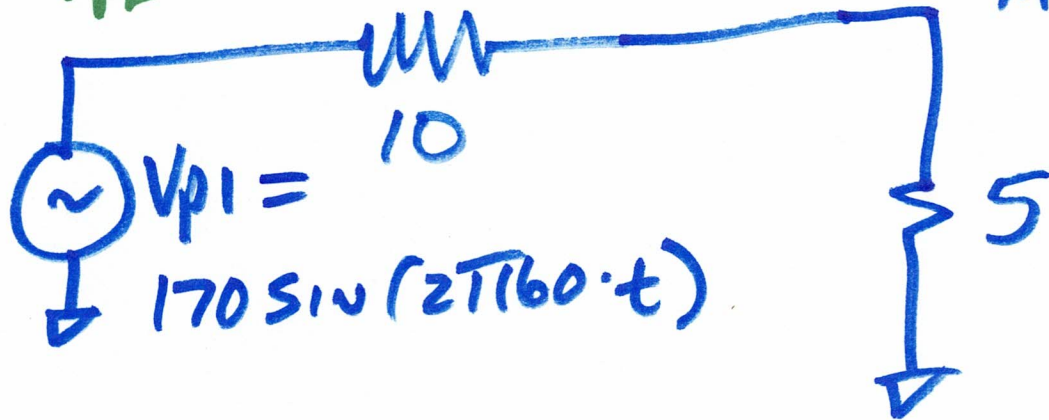


$$V_{X1,2,3} = \frac{V_{p1,2,3}}{3}$$



$$V_x = V_{x1} + V_{x2} + V_{x3} =$$

$$= \frac{1}{3} V_p \left(\sin(2\pi 60t) + \sin(2\pi 60t + 120^\circ) + \sin(2\pi 60t + 240^\circ) \right)$$

$$V_x = 0$$

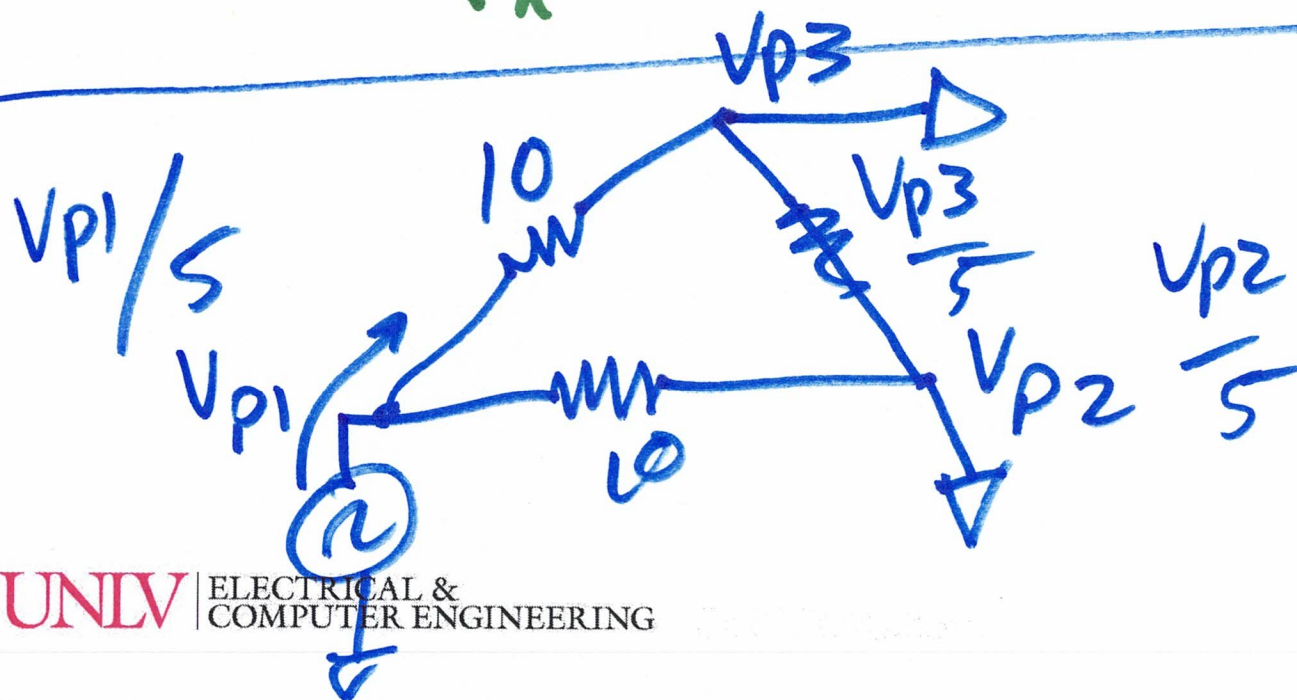

2)

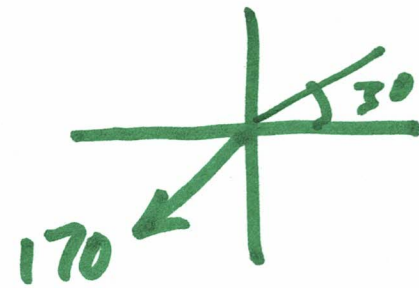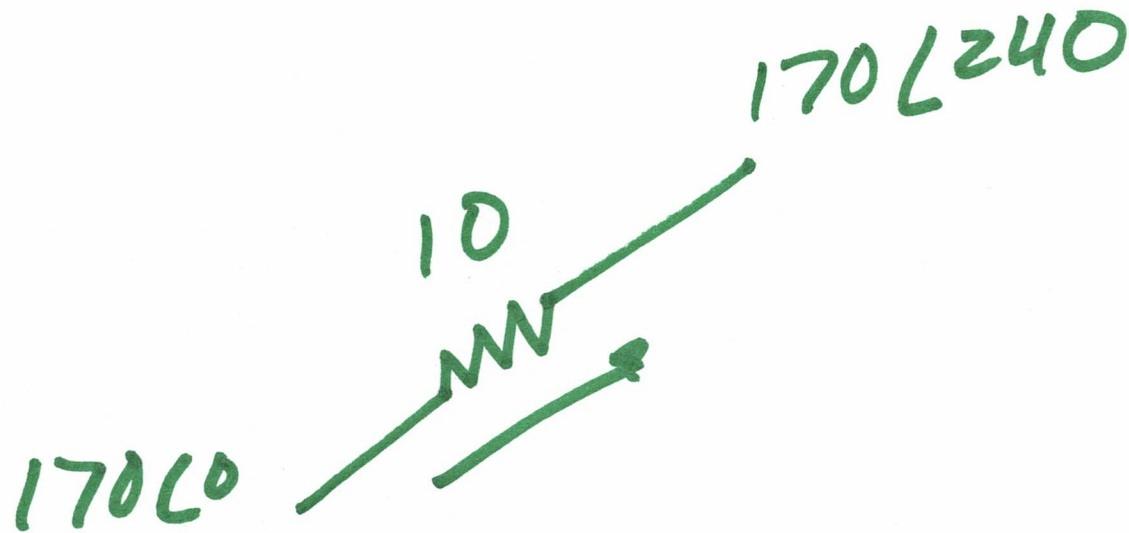


$$-(-85 + -j147)$$

\Rightarrow

$$\frac{170 + j0 + 85 + 147j}{10}$$

$$= \frac{\cancel{170} + 255 + 147j}{10}$$


$$= \frac{294.3}{10} \angle 210$$

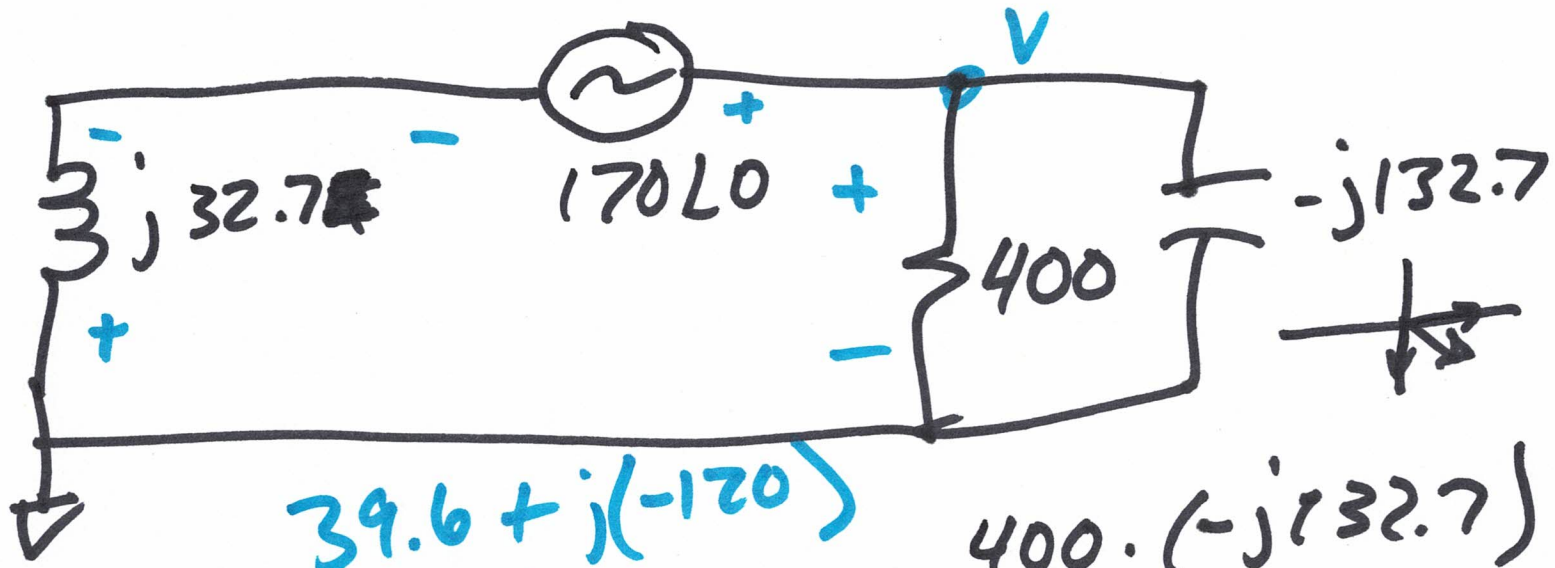

$$39.6 + j(-120)$$

$$400 \cdot (-j132.7)$$
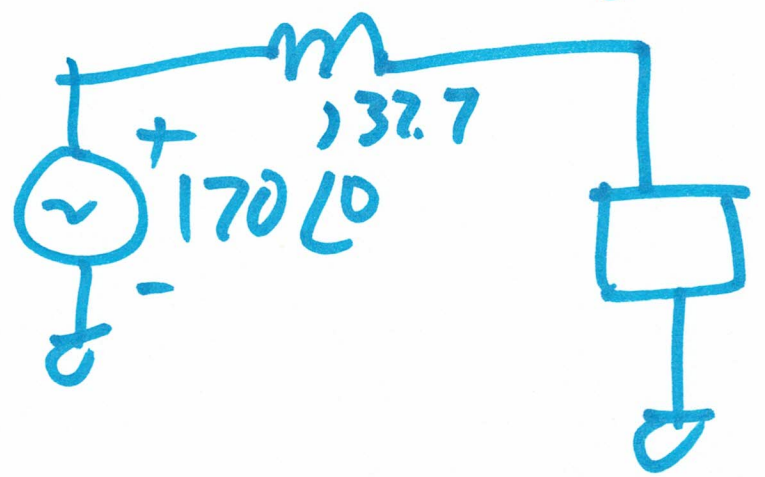
$$Z = \frac{400 \cdot (-j132.7)}{400 + j(-132.7)}$$



$$126 \angle -71.7$$

$$\frac{j(-53k)}{400 + j(-132.7)} = \frac{53k \angle -90}{421 \angle -18.3}$$

$$V = 170 \cdot \frac{126 \angle -71.7}{j \cancel{32.7} + 39.6 + 32.7 j(-120)}$$

$$Z = 126 \angle -71.7$$

4)

$$|V| = \frac{170 \cdot 126}{|39.6 + j(-87.3)|}$$

$$V_{rms} I_{rms} = \frac{1576^2}{400} |V| = \frac{170 \cdot 126 \cdot 96}{96}$$
$$V_{peak} = 223.1$$
$$V_{rms} = \frac{223.1}{\sqrt{2}} = 157.6$$


62.16W

$$ABCDEF = \frac{F}{1} = \frac{F}{F_{3dB}}$$

TRANSFER FUNCTION

$$F_{3dB} = \frac{1}{ABCDEF}$$

$$\frac{V_{out}}{V_{in}}$$

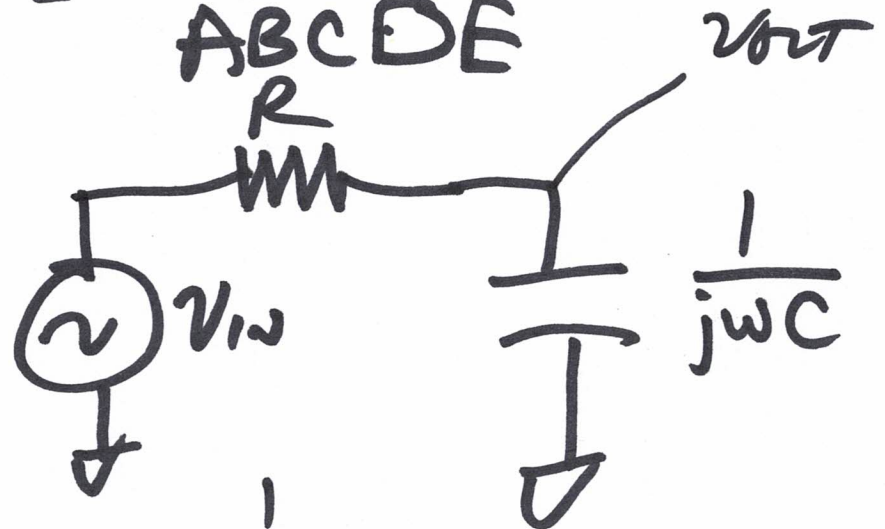

$$V_{out} = V_{in} \cdot \frac{1}{jwC}$$

$$\frac{1}{R + \frac{1}{jwC}}$$

b)

$$\left| \frac{1}{a + jb} \right| \frac{V_{out}}{V_{in}} = \frac{1}{1 + j\omega RC}$$


$$= \frac{1}{\sqrt{a^2 + b^2}} = \frac{1}{1 + j 2\pi f RC}$$

$$\angle \frac{1}{a + jb} = -\tan^{-1} \frac{b}{a} \quad f_{3dB} = \frac{1}{2\pi RC}$$

$$\frac{1}{|a + jb|} = \frac{1}{\sqrt{a^2 + b^2}} = \frac{1}{1 + j \frac{f}{f_{3dB}}}$$

$$\angle \frac{1}{a + jb} = -\tan^{-1} \frac{b}{a}$$

$$\left| \frac{u_{out}}{u_{in}} \right| = \frac{1}{\sqrt{1^2 + \left(\frac{f}{f_{3dB}}\right)^2}} \approx \frac{f_{3dB}}{f} \quad f \gg f_{3dB}$$

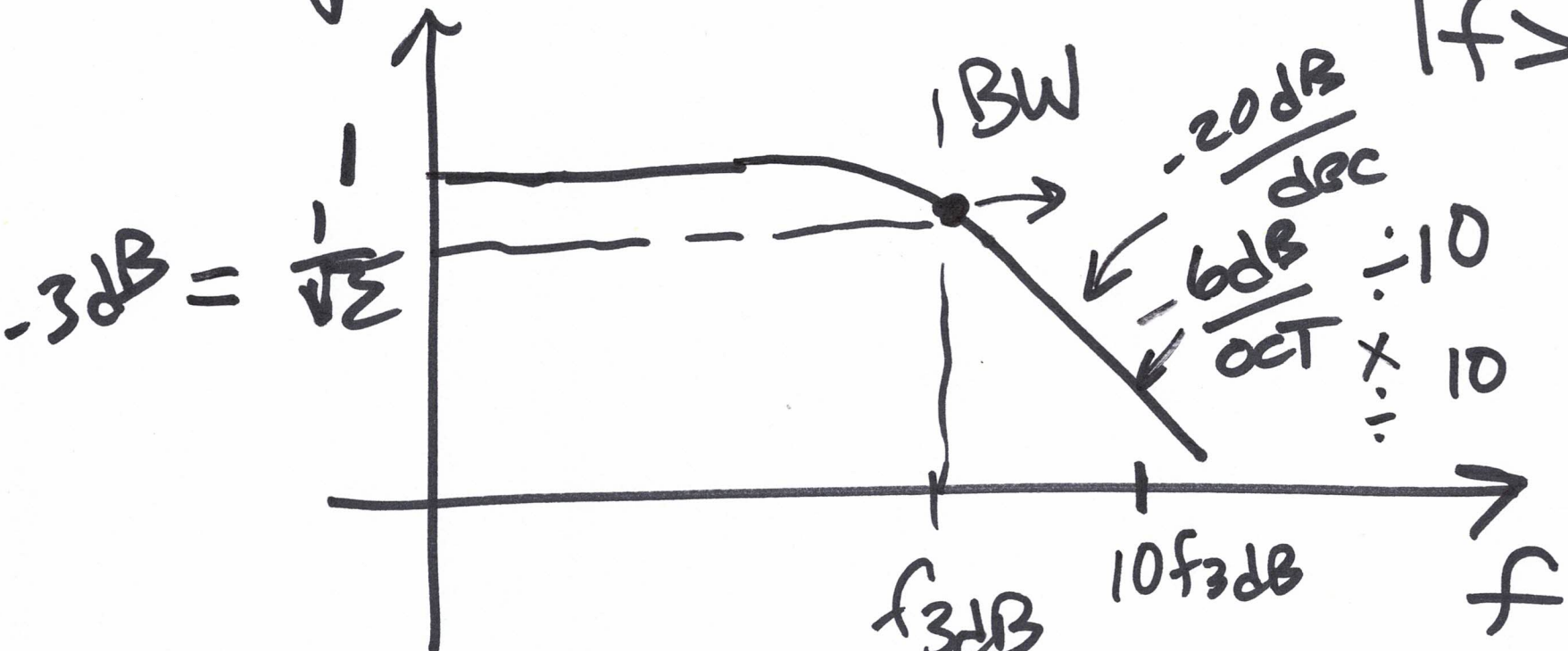

$-3dB = \frac{1}{\sqrt{2}}$

dec $\rightarrow \times 10$

oct $\rightarrow \times 2$

8)

decibels

Voltage or current

$$20 \log \frac{v_{out}}{v_{in}}$$

$$\frac{V_o/R}{V_i/R}$$

$$\frac{v_{out}}{v_{in}} = \frac{1}{10} \rightarrow -20 \text{ dB}$$

$$\frac{v_{out}}{v_{in}} = \frac{1}{2} \rightarrow -6 \text{ dB}$$

$$\frac{v_{out}}{v_{in}} = \frac{1}{\sqrt{2}} = -3 \text{ dB}$$

Power

$$10 \log$$

$$\frac{P_{out}}{P_{in}}$$

$$\frac{1}{10} \rightarrow -10 \text{ dB}$$