

EE 221 Circuits II


i
 v

V_{out}
 i_{in}

Lecture 11

1K, R

MARCH 2, 2020

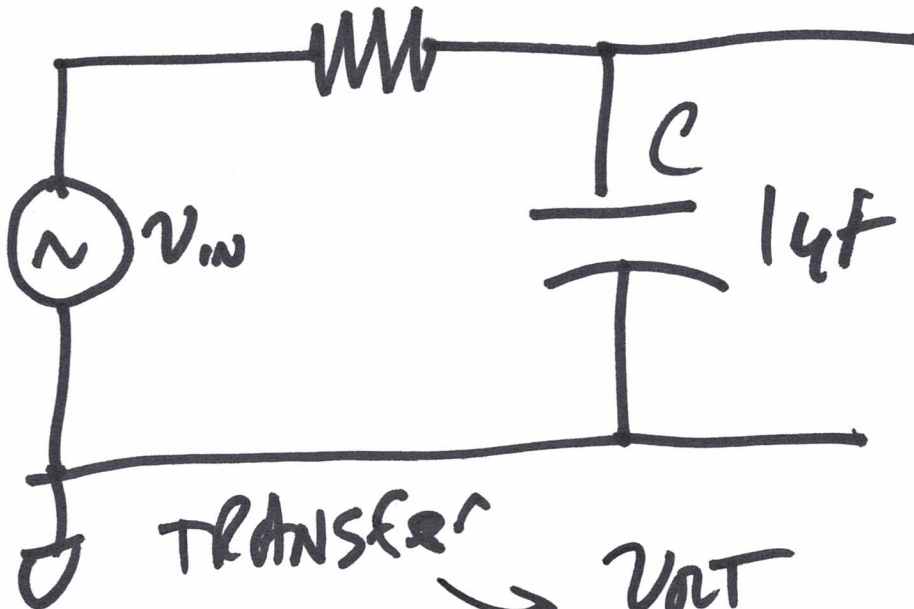

$$V_{out} = V_{in} \cdot \frac{1}{j\omega C + R}$$

TRANSFER

$$\frac{V_{out}}{V_{in}} =$$

$$\frac{1}{1 + j\omega RC}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + j2\pi fRC} = \frac{1}{1 + j \frac{f}{\frac{1}{2\pi RC}}}$$

$$= \frac{1}{1 + j \frac{f}{f_{3dB}}}, \quad f_{3dB} = \frac{1}{2\pi RC}$$

$$= \frac{1}{2\pi \cdot 10^3 \cdot 10^{-6}}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + j \frac{f}{159}}$$

$$= 159 \text{ Hz}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + \left(\frac{f}{159}\right)^2}}, \quad \angle \frac{V_{out}}{V_{in}} = -\tan^{-1} \frac{f}{159}$$


$$= -\tan^{-1} \frac{f}{159}$$

2)

$$dB = 20 \log \frac{v_{out}}{v_{in}}$$

$$s = j\omega = 2\pi f$$

$$1 \rightarrow 0 \text{ dB}$$

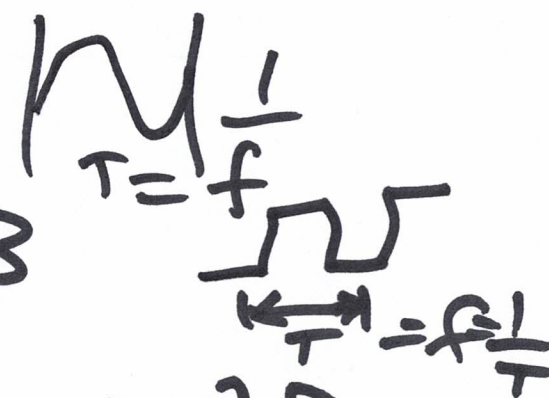

@ 300 Hz

$$\left| \frac{v_{out}}{v_{in}} \right| = -6.5 \text{ dB}$$

$$\angle \frac{v_{out}}{v_{in}} = -61^\circ$$

$$-6.5 = 20 \log \frac{v_{out}}{v_{in}}$$


$$61^\circ = 360 \cdot \frac{t_d}{T}$$
$$= 360 \cdot t_d \cdot f$$

$$\frac{v_{out}}{v_{in}} = 10^{-6.5/20}$$
$$= 0.47$$

$$t_d = \frac{60}{360} \cdot \frac{1}{300}$$
$$f = \frac{1}{T}$$

$$t_d = 0.55 \text{ ms}$$

3)

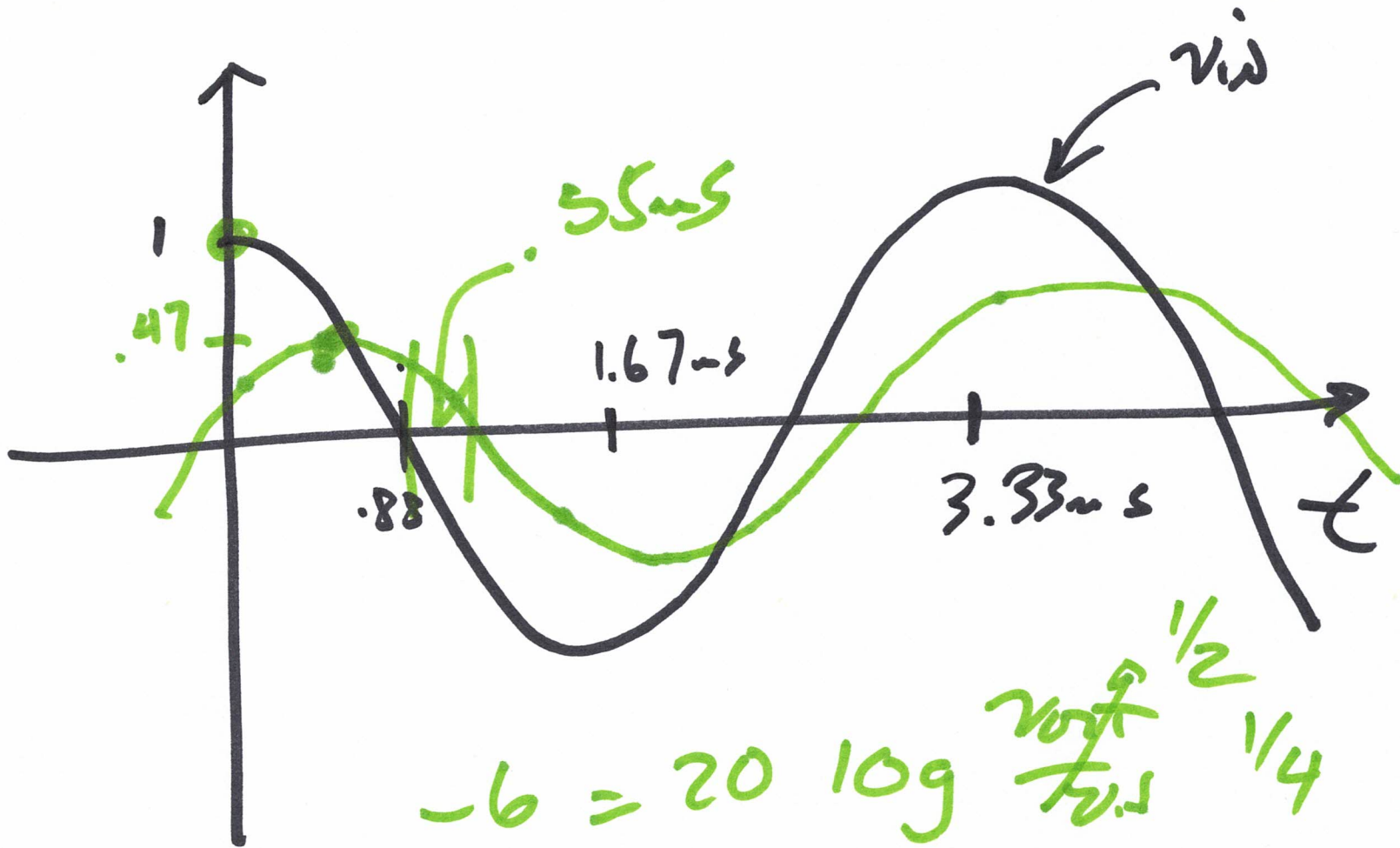

$$-6 = 20 \log \frac{v_{out}^{1/2}}{v_{in}^{1/4}}$$

$$\frac{v_{out}}{v_{in}} = 10^{-6/20} = \frac{1}{2}$$

$$\frac{v_{out}}{v_{in}} =$$

$$\frac{1}{1 + j \frac{f}{f_{3dB}}}$$


FRENZEL
Euler

Bode Plot

$$f = f_{3dB}$$


$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{1}{\sqrt{2}}$$
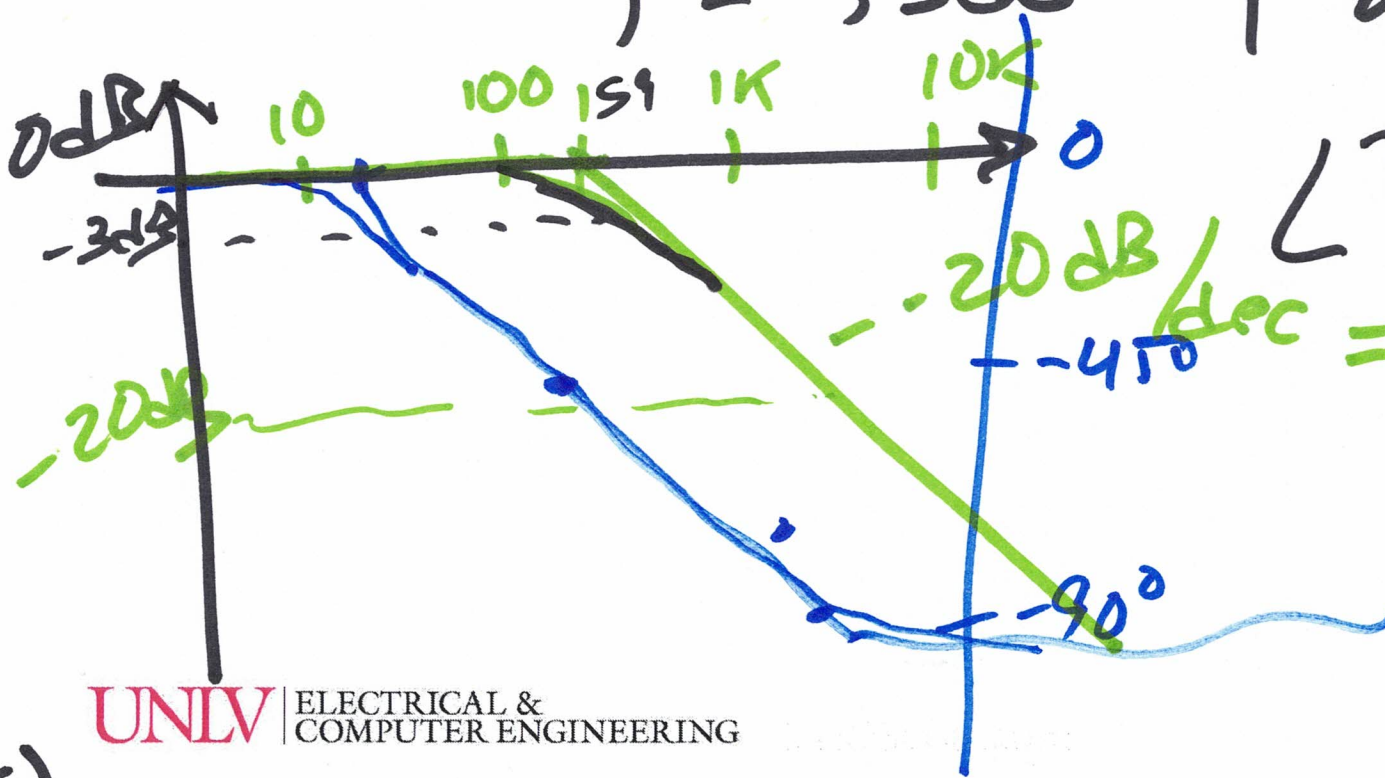
$$\angle \frac{v_{out}}{v_{in}} = -\tan^{-1} \frac{f}{f_{3dB}} = -45^\circ$$



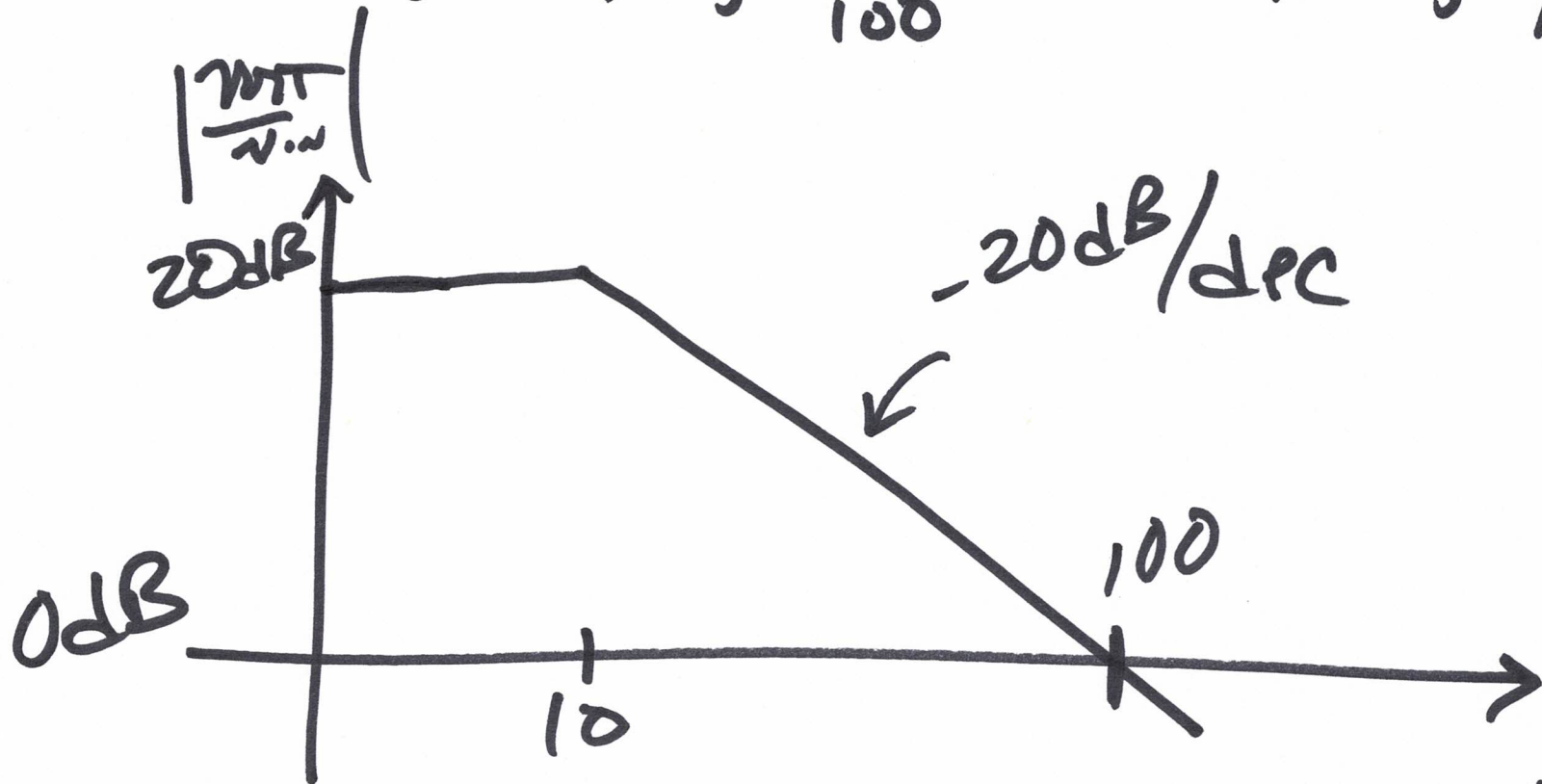
5)

$$\frac{20V}{2V} = \frac{1}{0.1 + j \frac{f}{100}} = \frac{10}{1 + j \frac{f}{10}}$$



$$20 \log 10 = 20 \text{ dB}$$

6)

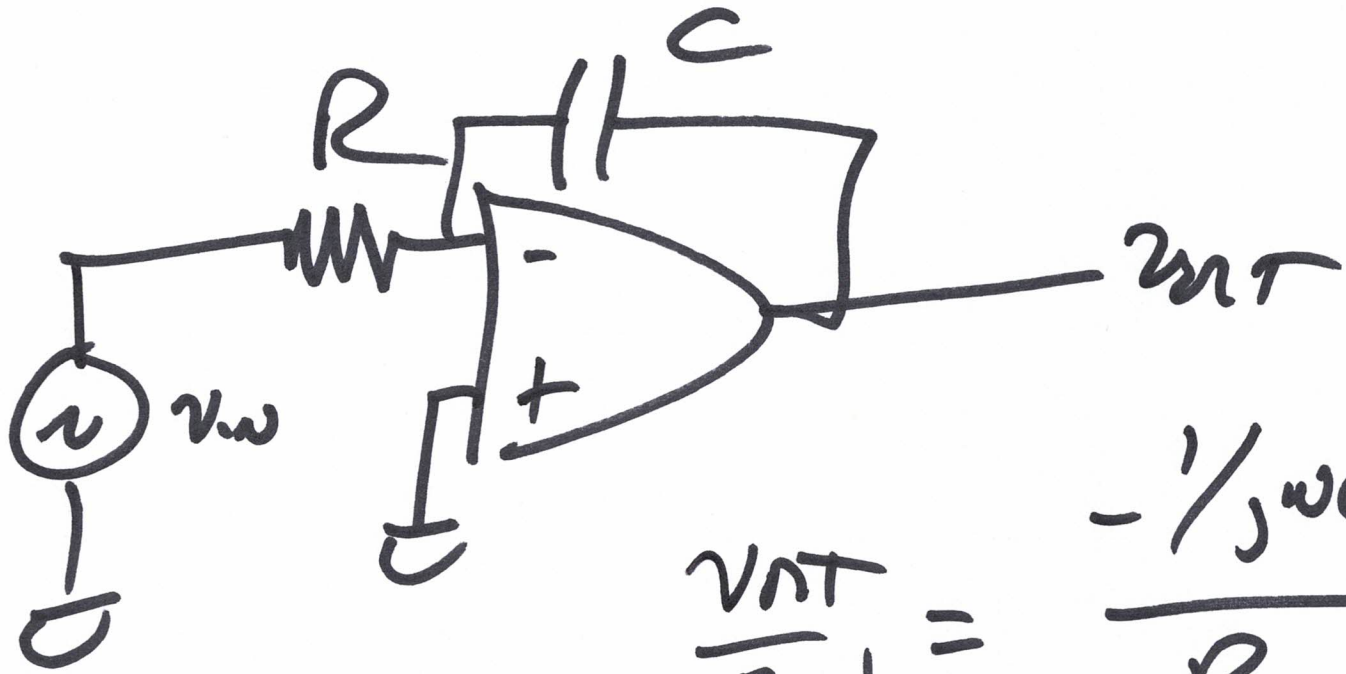

$$\frac{v_{OUT}}{v_{IN}} = \frac{-1/j\omega C}{R}$$

$$\left| \frac{v_{OUT}}{v_{IN}} \right| = \frac{1}{\sqrt{0^2 + (\omega RC)^2}} = \frac{-1}{0 + j\omega RC}$$

$$= \frac{1}{\omega RC}$$



$$10 = \frac{1}{\omega RC \cdot 0.1}$$

7)

$$| | = \frac{1}{0.37 \cdot f}$$

$$f = \frac{1}{0.37} \rightarrow | | = 1$$

$$f = \frac{10}{0.37}$$


up in freq
one dec

$$\frac{1}{f}$$

$$| | = \frac{1}{10}$$

$$\frac{-20dB}{dec} = \frac{\nearrow 10}{\nwarrow 10} - 20dB$$

5)

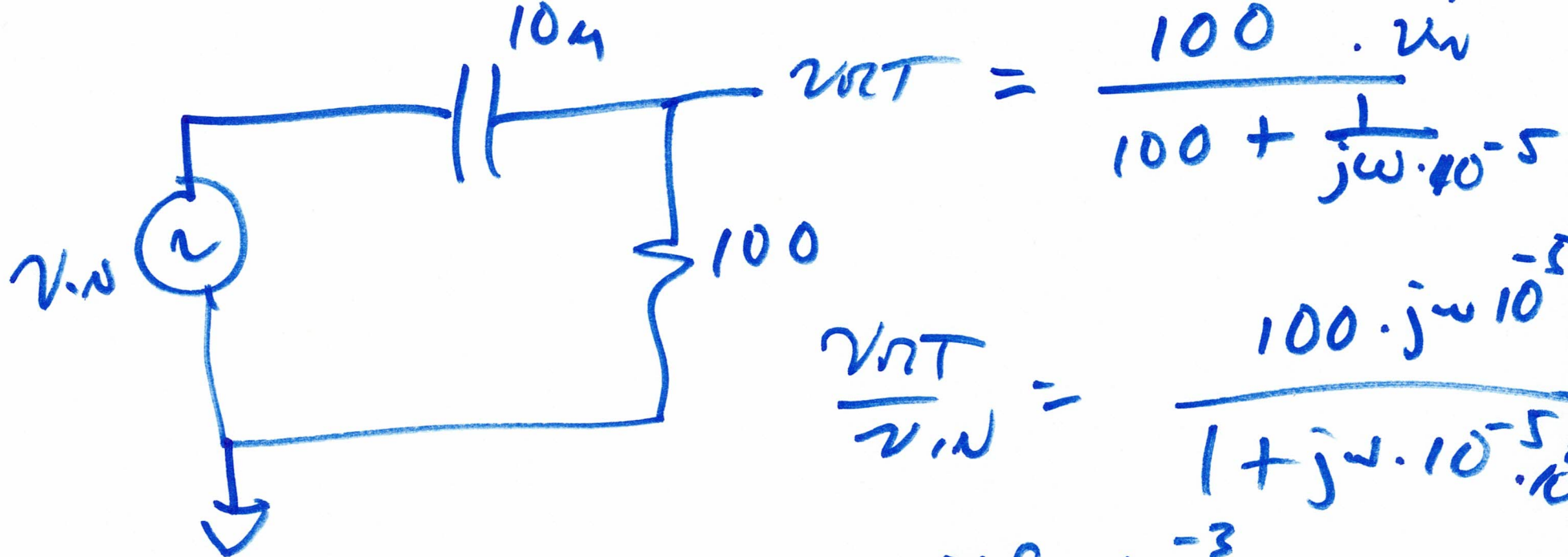

$$v_{OUT} = \frac{100 \cdot v_{in}}{100 + \frac{1}{j\omega \cdot 10^{-5}}}$$

$$\frac{v_{OUT}}{v_{in}} = \frac{100 \cdot j\omega \cdot 10^{-5}}{1 + j\omega \cdot 10^{-5} \cdot 100}$$

$$\frac{v_{OUT}}{v_{in}} = \frac{0 + j \cdot 2\pi f \cdot 10^{-3}}{1 + j \cdot 2\pi f \cdot 10^{-3}}$$

$$\left| \frac{v_{OUT}}{v_{in}} \right| = \frac{2\pi f \cdot 10^{-3}}{\sqrt{1 + (2\pi f \cdot 10^{-3})^2}}$$

$$\angle \frac{v_{out}}{v_{in}} = \tan^{-1} \frac{\infty}{0} - \tan^{-1} \frac{2\pi f \cdot 10^{-3}}{1}$$

$$f_{3dB} = \frac{1}{2\pi \cdot 10^{-3}} = 154$$