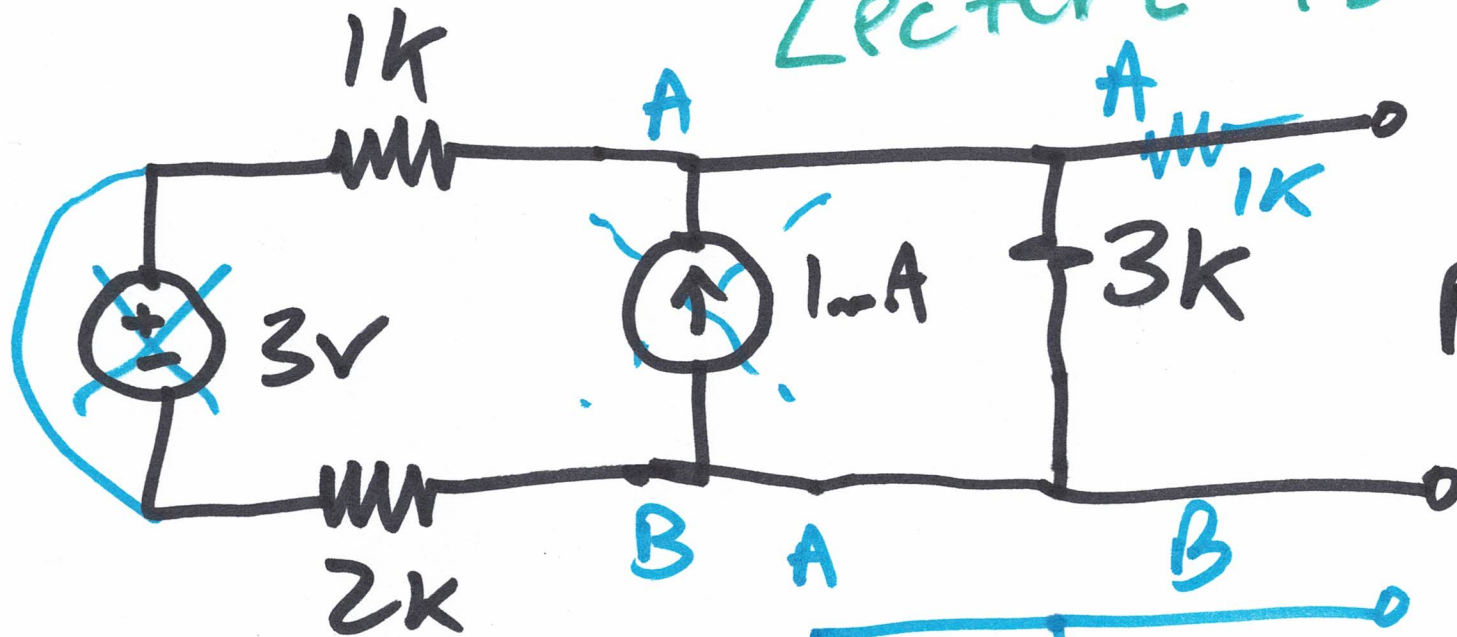


EE 221 circuits II


March 9, 2020


Lecture 13




$$R_{TH} = 1.5k$$

$$R_{TH} = \frac{V_{oc}}{I_{sc}}$$

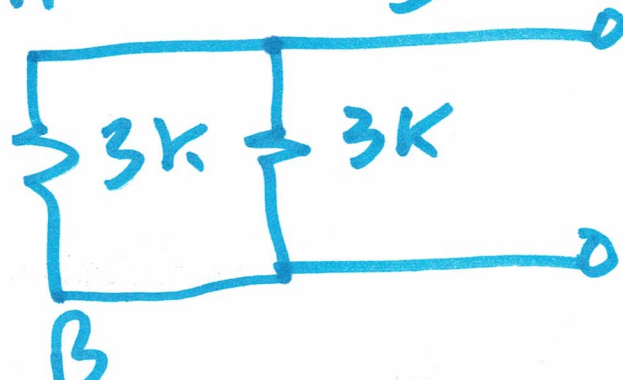

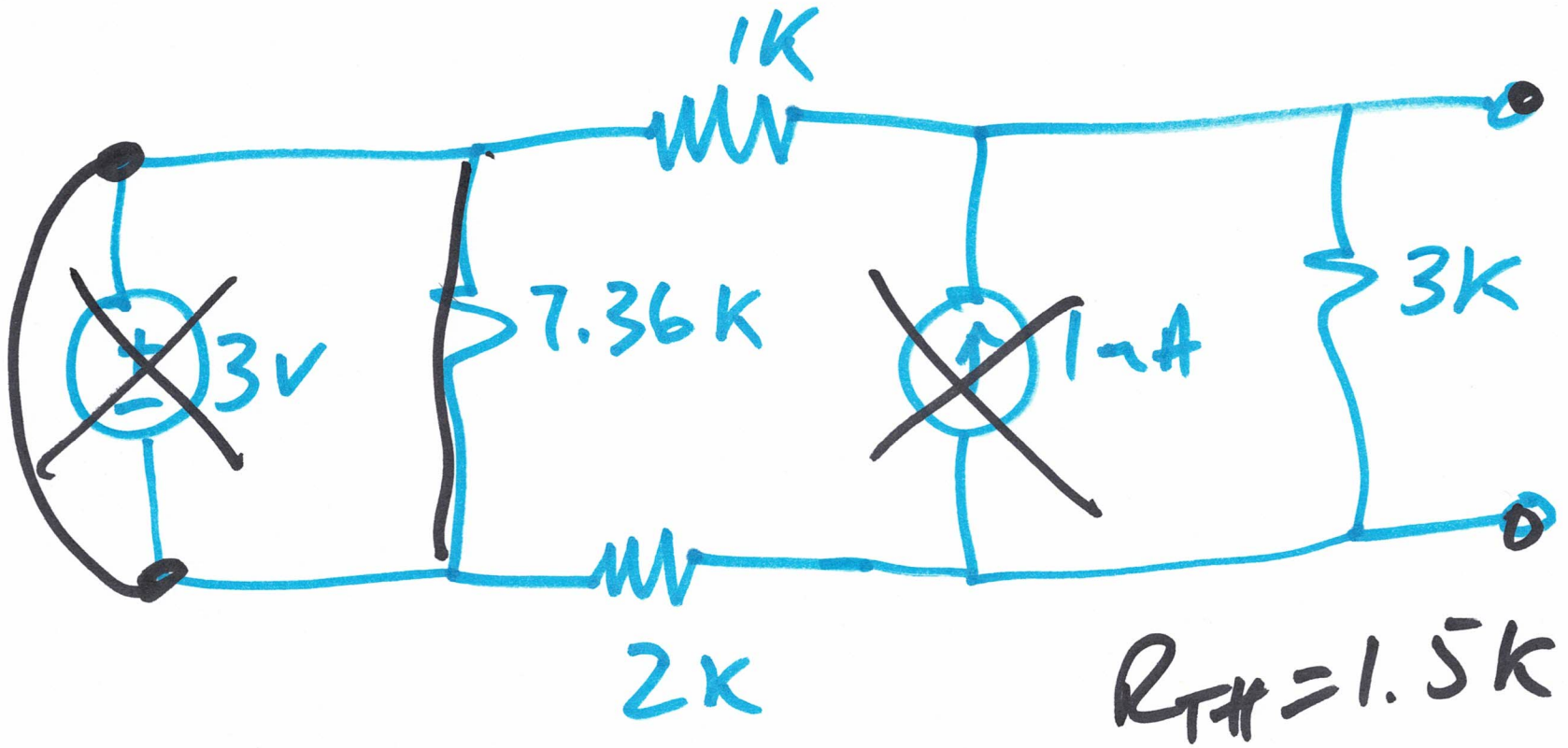

2)

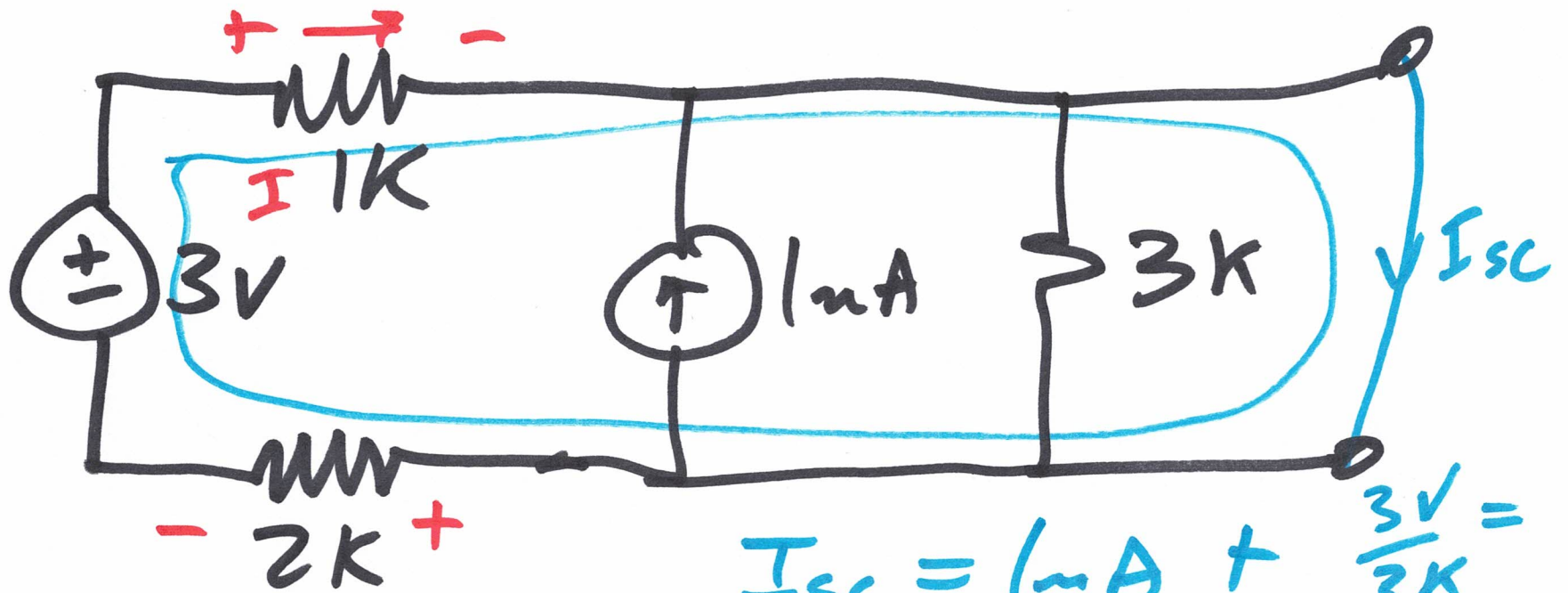



$$I_{sc} = 1\mu A + \frac{3V}{3k} =$$


$$3V - I \cdot 1k - I \cdot 2k = 0 \quad \rightarrow \quad I = 1\mu A = \frac{3V}{3k}$$

$$I_{sc} = 2\mu A$$


$$R_{TH} \cdot I_{sc} = V_{TH} = 3V$$

$$1.5k \cdot 2\mu A$$

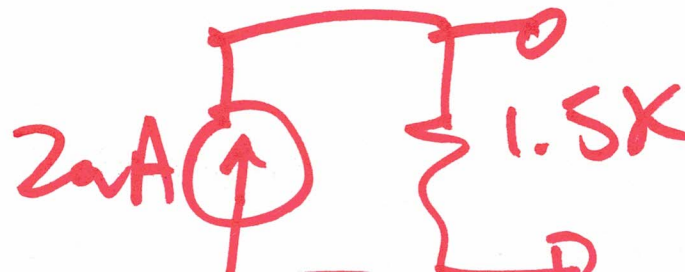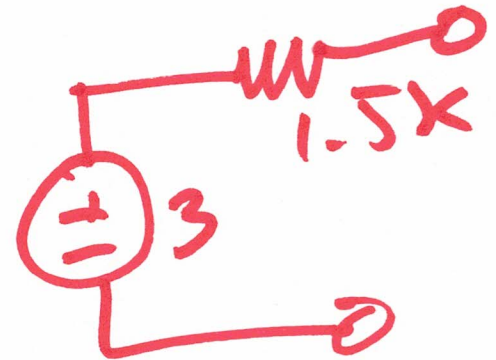

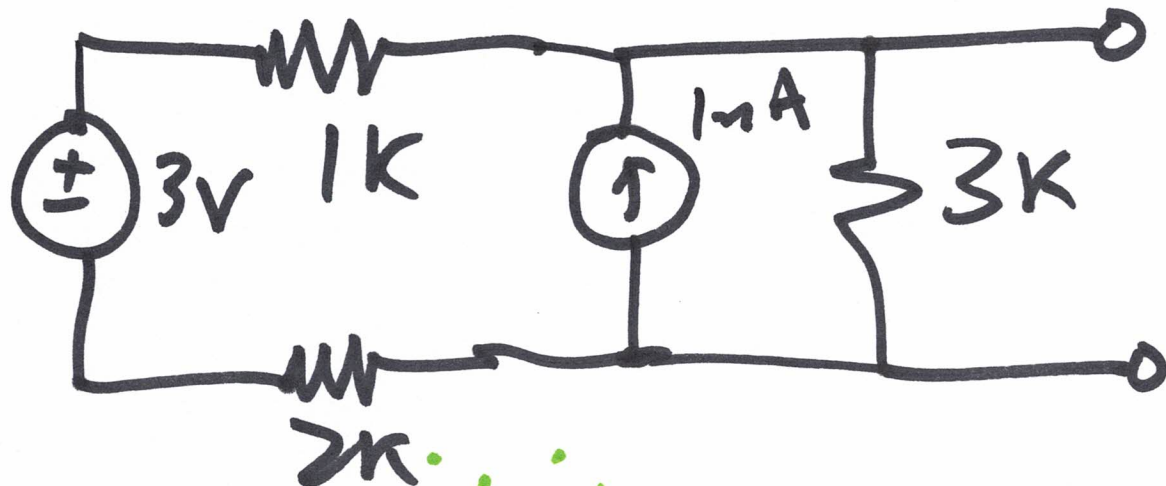


Superposition

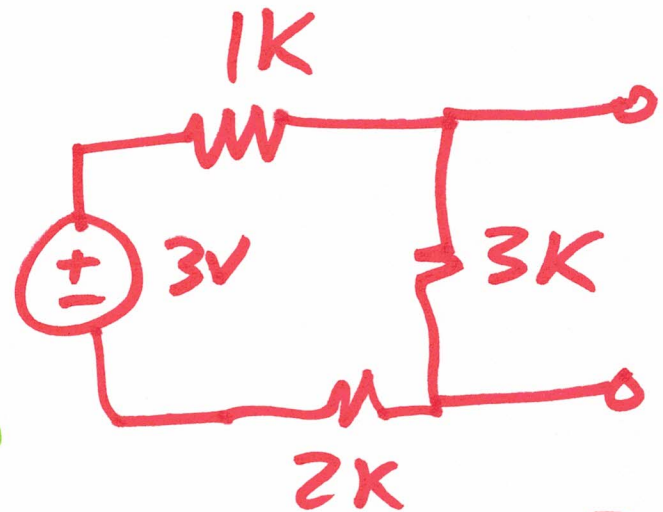

$$V_{oc2} = \frac{3 \cdot 3}{1+2+3}$$

$$= \frac{9}{6}$$

$$= 1.5V$$

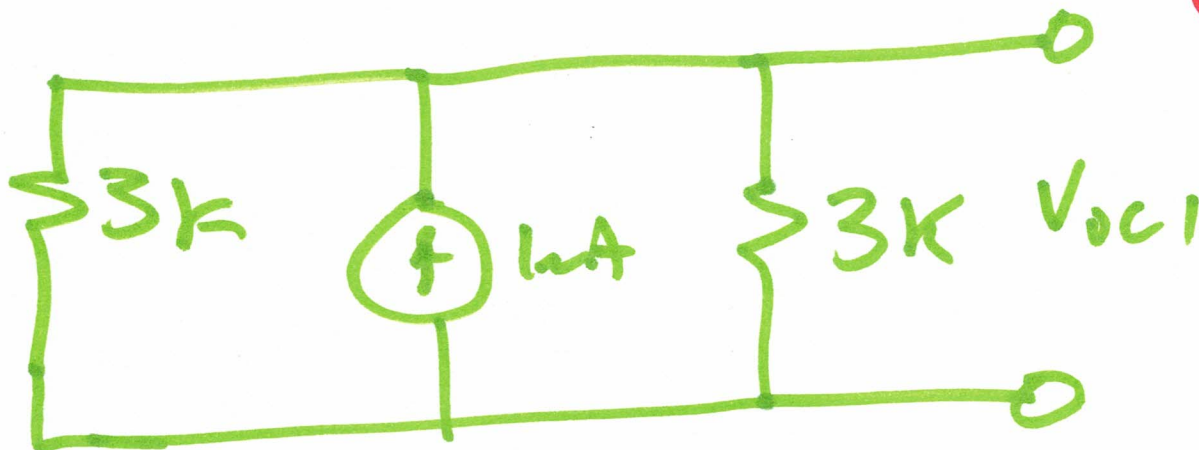



$$V_{th} = 1.5 + 1.5$$

$$= 3V$$



4)

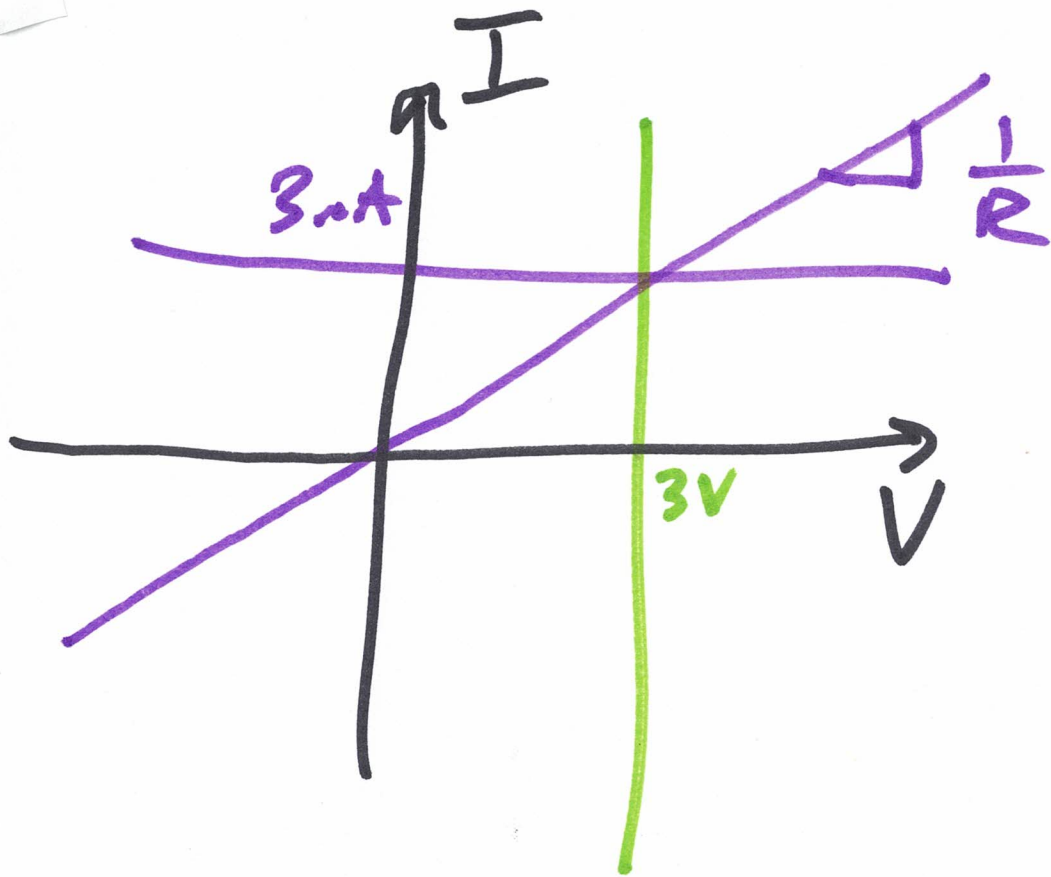

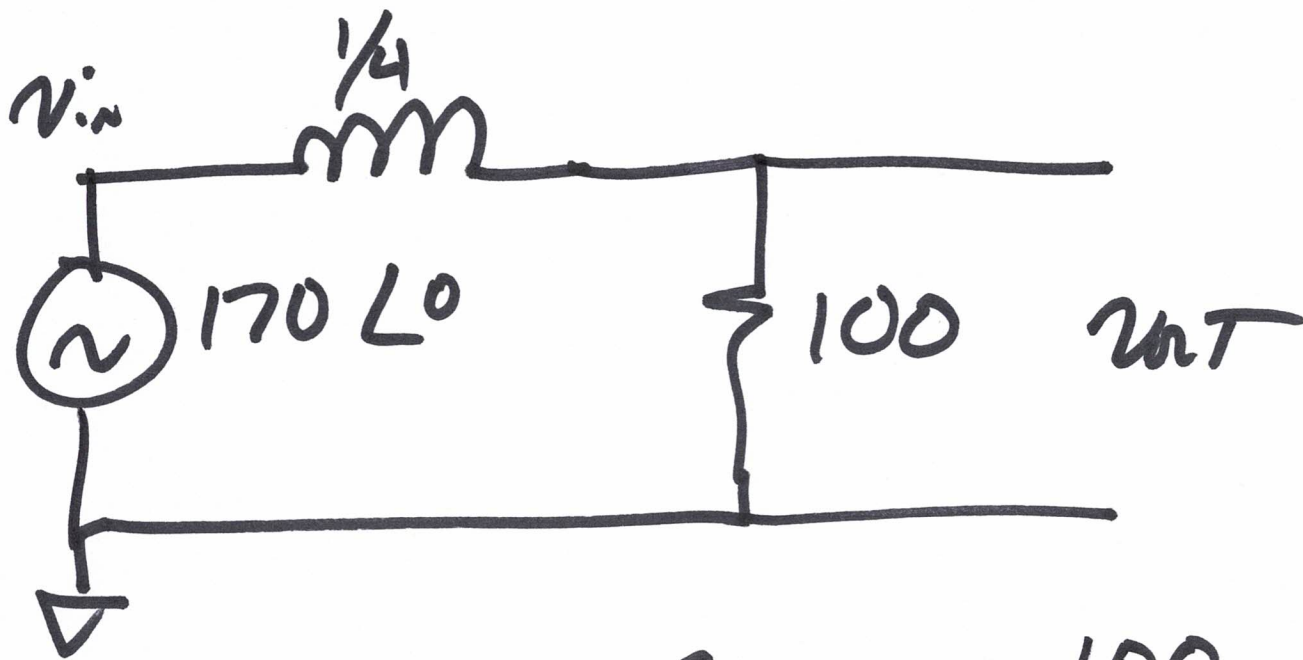

$$v_{OUT} = v_{in} \cdot \frac{100}{100 + j \cdot 2\pi f \cdot \frac{1}{4}}$$

$$\frac{v_{OUT}}{v_{in}} = \frac{1}{1 + j \frac{\pi}{200} \cdot f}$$

#6

$$|V_{out}| = 170 \angle 0^\circ$$

$$\frac{1}{60} = 16.67 \text{ ms}$$

$$\sqrt{1 + \left(\frac{\pi}{200} \cdot 60\right)^2}$$

$$|V_{out}| = 123.7 \text{ V}$$

$$t_d = 2 \text{ ms}$$

$$\angle V_{out} = 0^\circ - \tan^{-1} \frac{\pi}{200} \cdot 60$$

$$43 = t_d \cdot 60 \cdot 360$$


$$\approx \frac{t_d}{\frac{1}{60}} \cdot 360$$

INPUT (TOP)

$$\angle V_{out} = -43^\circ$$

$$v_{in} = 170 \sin(2\pi \cdot 60 \cdot t)$$
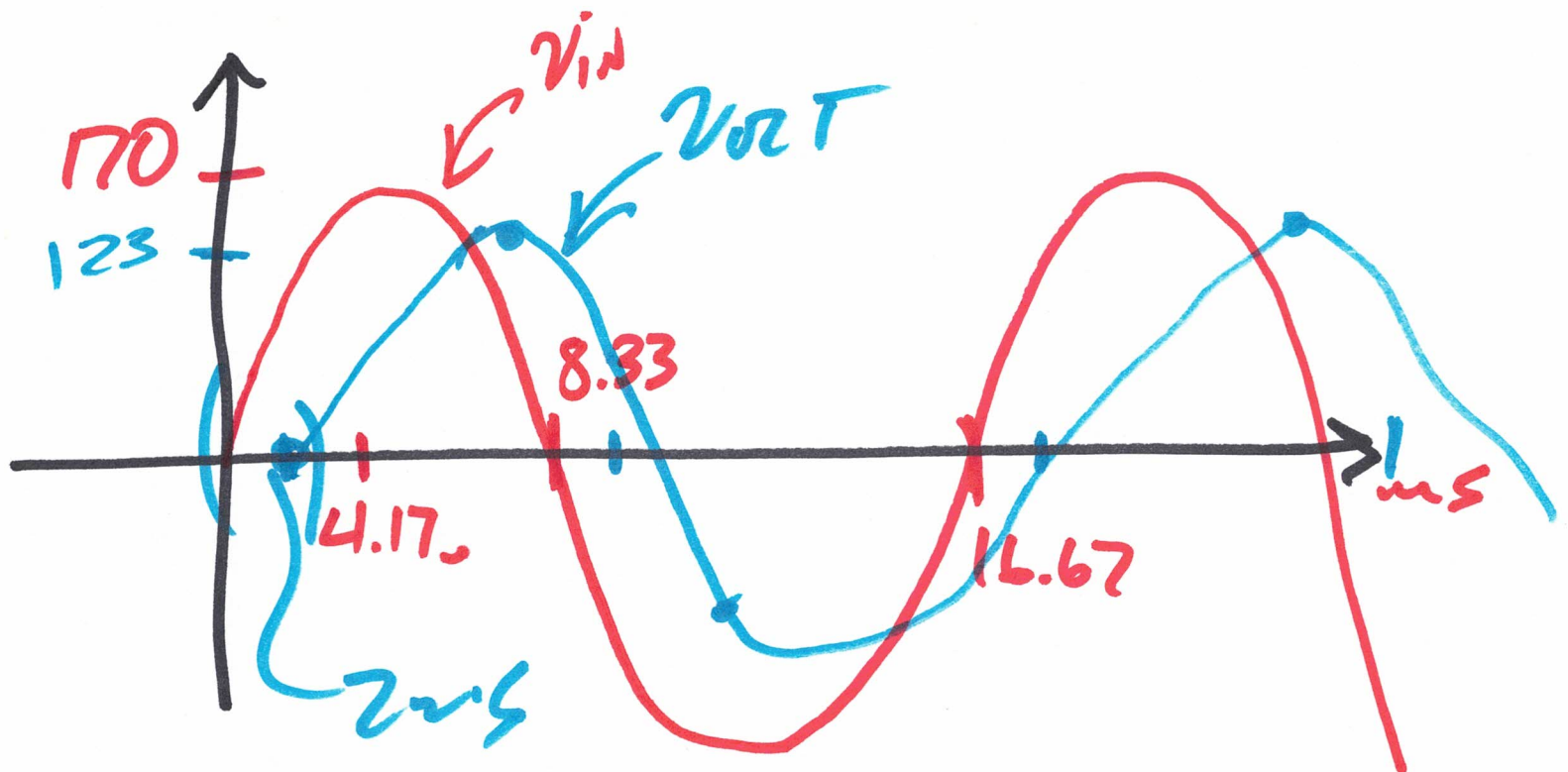
$$v_{out} = 123.7 \sin(2\pi \cdot 60 \cdot t - 43^\circ)$$




$$\frac{v_{out}}{v_{in}} = \frac{1}{1 + j \frac{\pi}{200} \cdot f} = \frac{1}{1 + j \frac{f}{63.7}}$$


$$f_{3dB} = \frac{1}{\frac{\pi}{200}} = \frac{200}{\pi}$$

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{1}{\sqrt{1 + \left(\frac{f}{63.7} \right)^2}}$$

$$\angle \frac{v_{out}}{v_{in}} = -\tan^{-1} \frac{f}{63.7}$$

@ 60 Hz
 $\left| \frac{v_{out}}{v_{in}} \right| \approx -3dB$
 $\angle \approx -45^\circ$

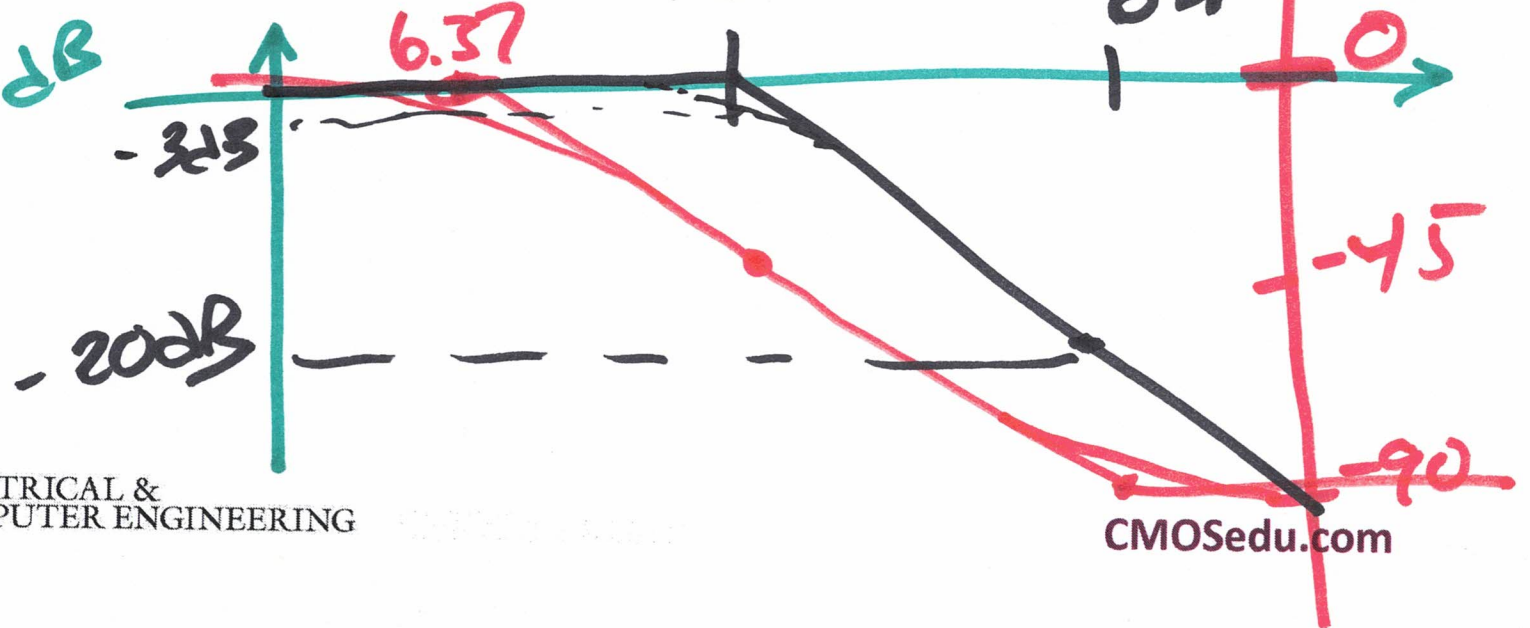

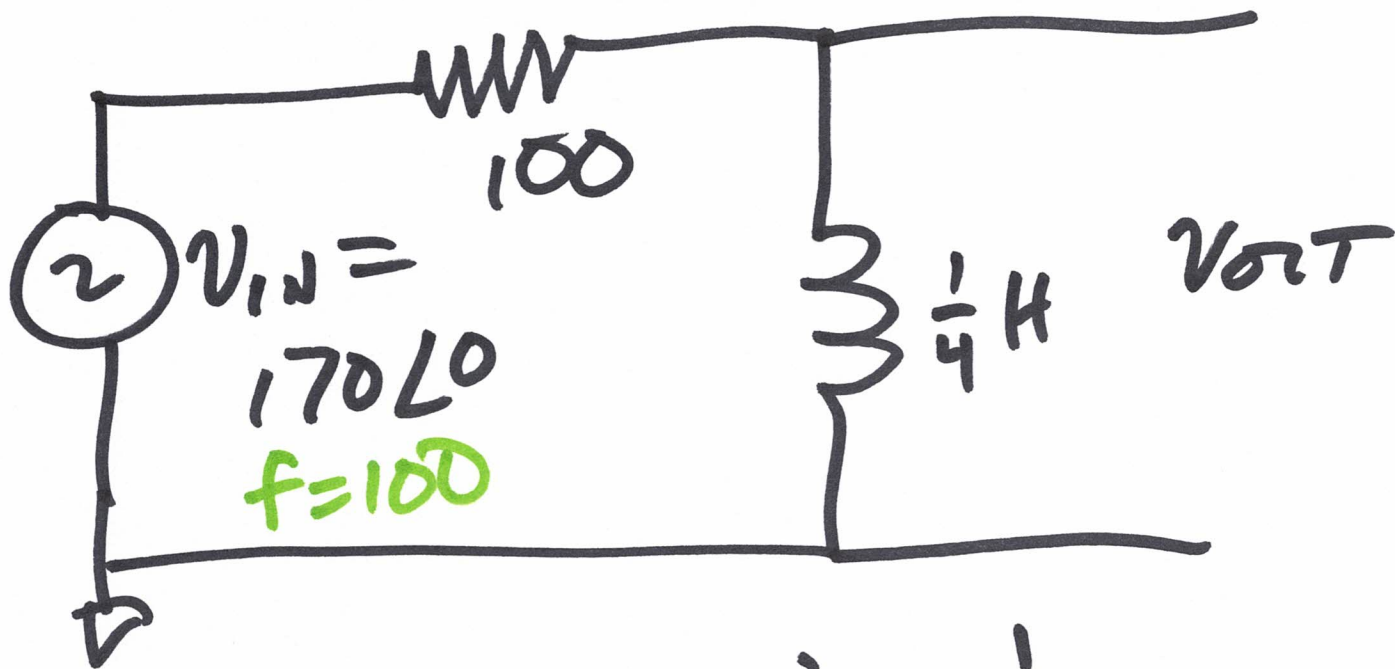

$$\frac{v_{out}}{v_{in}} = \frac{j\omega \frac{1}{4}}{100 + j\omega \frac{1}{4}}$$

$$= \frac{j \cdot \frac{2\pi}{400} \cdot f}{1 + j \frac{2\pi}{400} \cdot f}$$

10
9

$$\frac{v_{out}}{v_{in}} = \frac{0 + j \frac{f}{63.7}}{1 + j \frac{f}{63.7}}$$

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{\sqrt{0^2 + \left(\frac{f}{63.7}\right)^2}}{\sqrt{1^2 + \left(\frac{f}{63.7}\right)^2}} = \frac{f}{63.7} \frac{1}{\sqrt{1 + \left(\frac{f}{63.7}\right)^2}}$$

$$\angle \frac{v_{out}}{v_{in}} = 90 - \tan^{-1} \frac{f}{63.7}$$

$$-3dB \leftarrow \frac{1}{\sqrt{2}}$$

$$20 \log \frac{1}{\sqrt{2}} = -3dB$$

