




EE 221

CIRCUITS II

JANUARY 27, 2020

Lecture 2

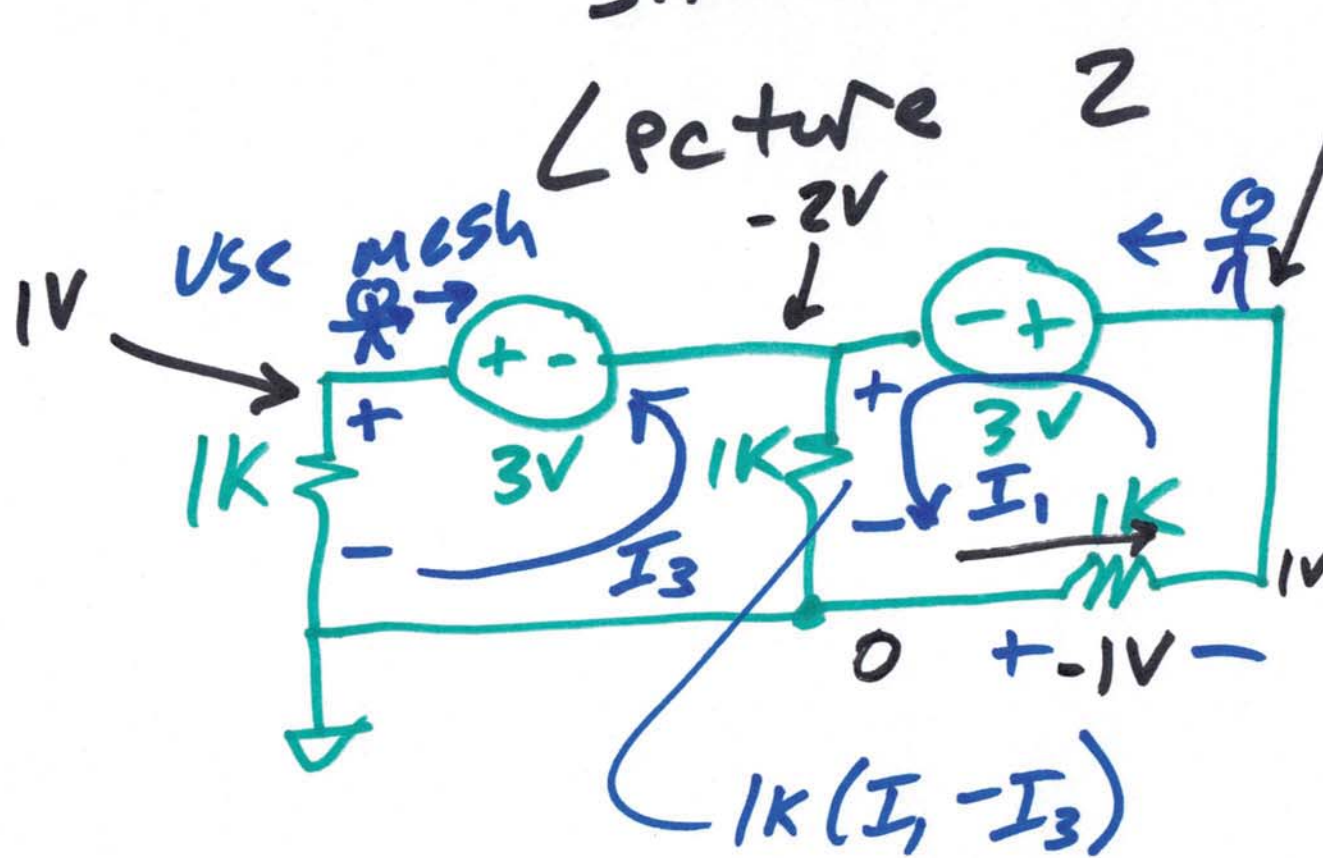

$$\begin{aligned}
 & -3 - 1k(I_1 - I_3) \\
 & -1k \cdot I_1 = 0 \\
 & -3 - 1k(I_1 - I_3) \\
 & + 1k I_3 \\
 & I_1 = -1 \text{ A} \\
 & I_3 = 1 \text{ A}
 \end{aligned}$$

$$-3 - 1K(I_1 - I_3) - 1K \cdot I_1 = 0$$

$$-(-3 - 1K(I_1 - I_3) + 1K I_3) = 0$$

$$0 + 0 + \cancel{-1KI_1} - \cancel{1KI_3} = 0$$

$$I_1 = -I_3$$


$$-3 - 1K 2I_1 - 1K I_1 = 0 \quad I_3 = -I_1$$

$$-3 - 3KI_1 = 0$$

$$I_1 = -1 \mu A$$

$$I_3 = 1 \mu A$$

2)

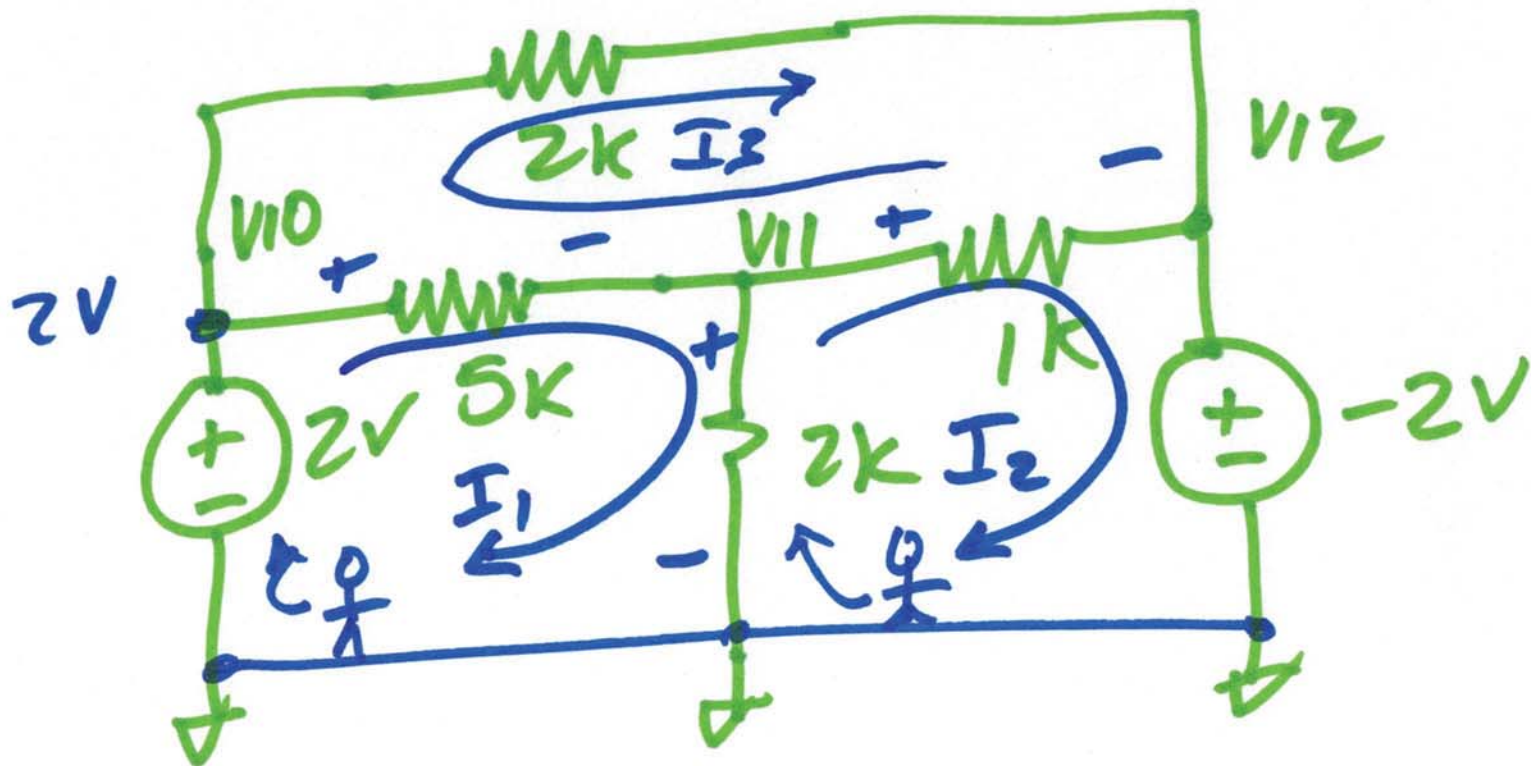

$$2V - I_3 \cdot 2K - (-2V) = 0$$

$$I_3 = \frac{4V}{2K} = 2\mu A$$

$$2V - 5K(I_1 - 2\mu A) - 2K(I_1 - I_2) = 0$$

$$2V - 1K(I_2 - 2\mu A) + 2K(I_1 - I_2) = 0$$

3)



$$1 \mu\text{A} - 2.5 I_1 + 5 \mu\text{A} - I_1 + I_2 = 0$$

$$6 \mu\text{A} - 3.5 I_1 + I_2 = 0$$

$$2 \mu\text{A} - I_2 + 2 \mu\text{A} + 2 I_1 - 2 I_2 = \epsilon$$

$$4 \mu\text{A} + 2 I_1 - 3 I_2 = 0$$

$$18 \mu\text{A} - 10.5 I_1 + 3 I_2 = 0$$

$\times 3$

$$22 \mu\text{A} - 8.5 I_1 = 0$$

$$6 \mu\text{A} - \frac{7}{2} \cdot \frac{44}{17} + I_2 = 0$$


$$I_1 = \frac{22}{\frac{17}{2}} \mu\text{A}$$

$$6 \mu\text{A} - \frac{154 \mu\text{A}}{17} + I_2 = 0$$

$$I_1 = \frac{44}{17} \mu\text{A}$$

$$\frac{102}{17} \mu\text{A} - \frac{154}{17} \mu\text{A} + I_2 = 0$$
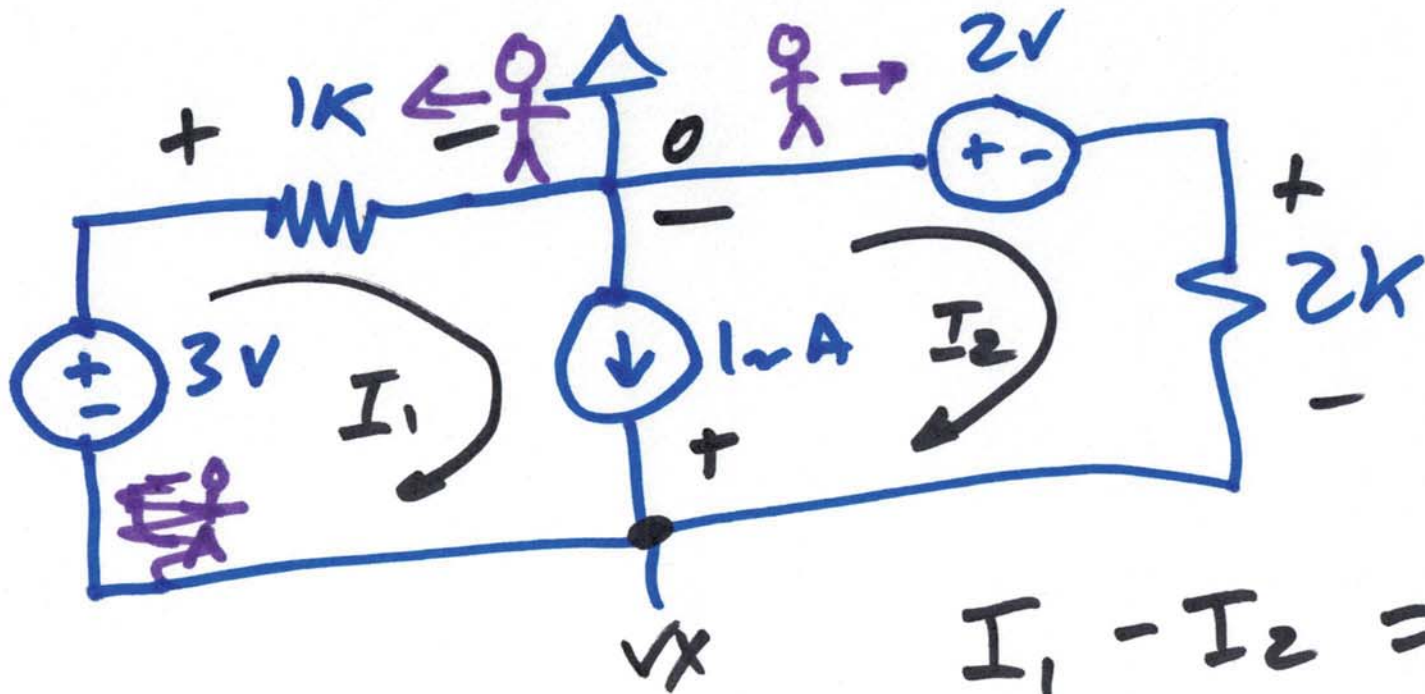
$$I_2 = \frac{52}{17} \mu\text{A} = 3 \frac{1}{17} \mu\text{A}$$




$$I_1 - I_2 = 1\text{mA}$$

$$-2\text{V} - 2\text{k}\Omega I_2 + 3 - 1\text{k}\Omega I_1 = 0 \leftarrow$$

$$-2 - 2\text{k}\Omega I_2 - V_x = 0$$

$$1\text{k}\Omega I_1 - 3 - V_x = 0$$

$$V_x = 1\text{k}\Omega I_1 - 3$$

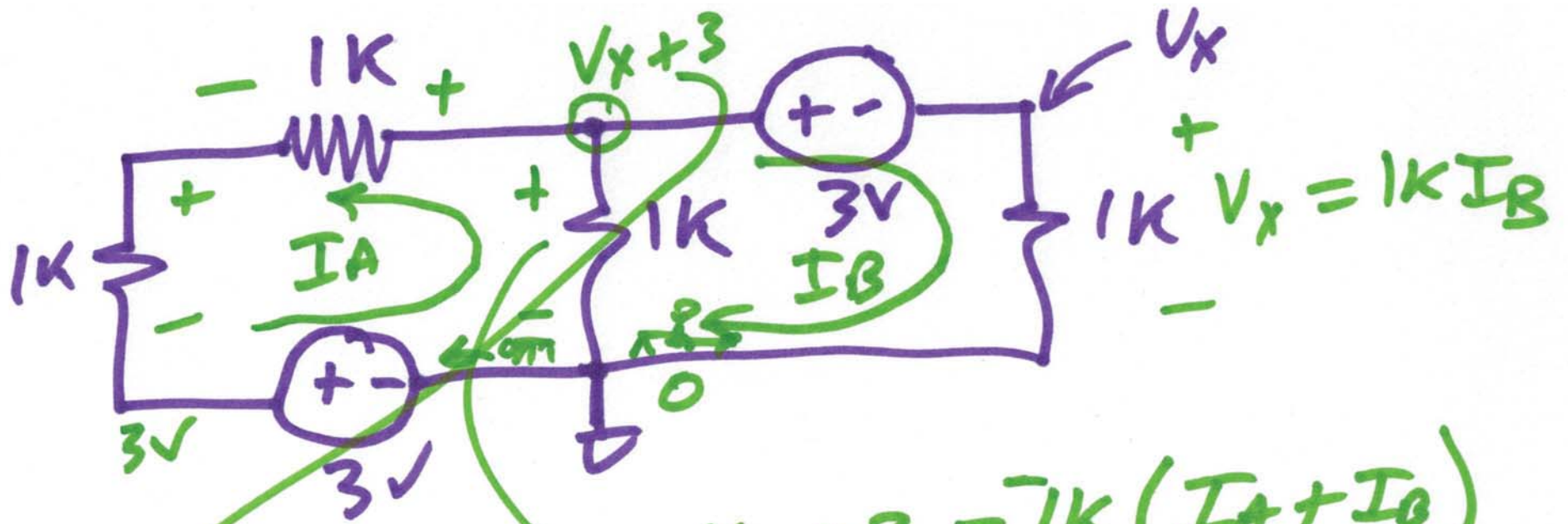

$$1k V_x = 1k I_B$$

$$V_x + 3 = 1k (I_A + I_B)$$


$$3v + I_A \cdot 1k + I_A \cdot 1k + 1k (I_A + I_B) = 0$$

$$1k I_B + 3 + 1k (I_A + I_B) = 0$$

Super Node!

6)



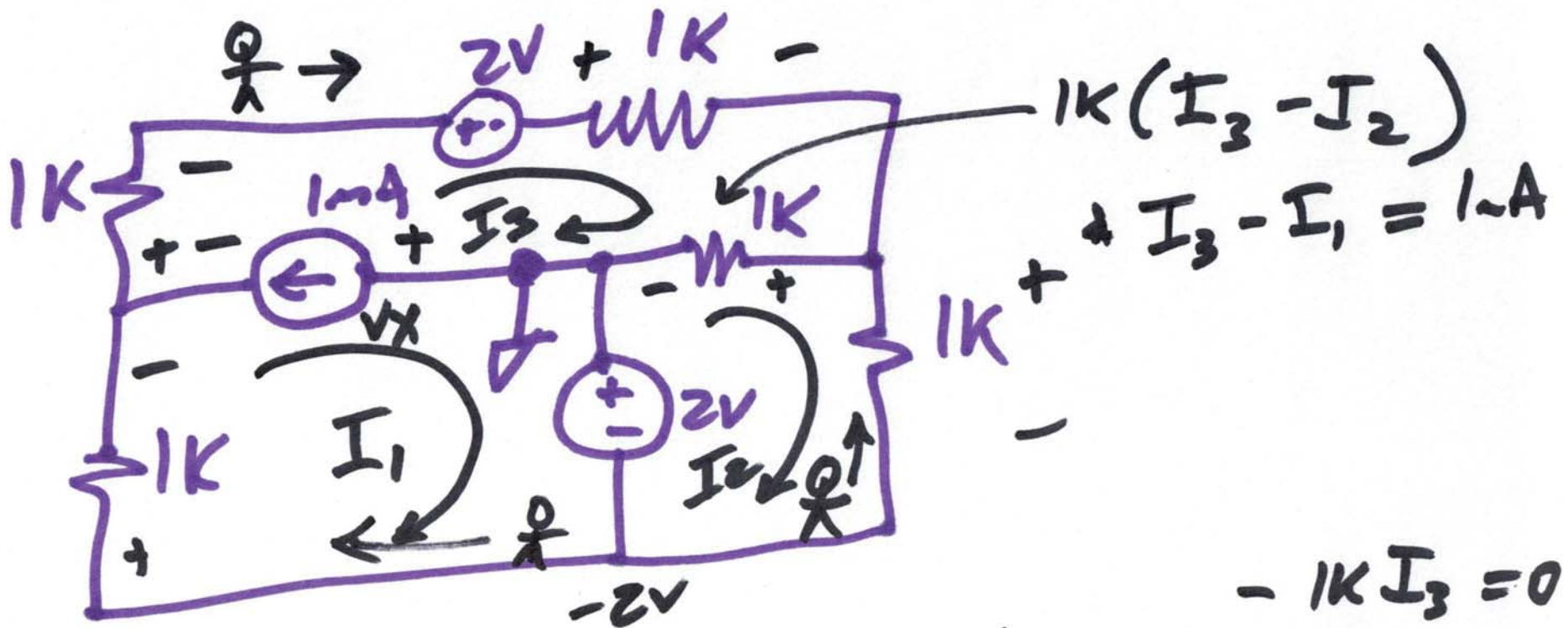

$$1K(I_3 - I_2)$$

$$I_3 - I_1 = 1mA$$

$$-1K I_3 = 0$$

$$-2 - I_2 \cdot 1K - 1K(I_3 - I_2) - V_x = 0$$

$$-I_1 \cdot 1K + V_x - 2 = 0$$

$$+1K I_2 - 1K(I_3 - I_2) - 2 = 0$$

