
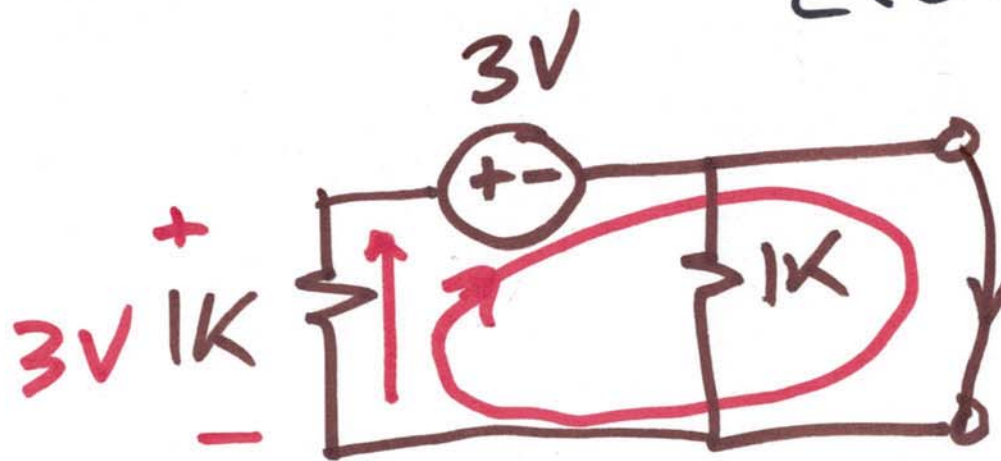


# EE 221 Circuits II


Feb. 3, 2020

Lecture 4

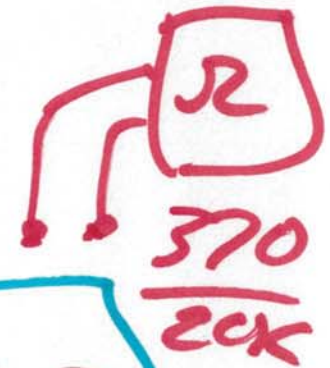

$R_{TH} = 500\Omega$

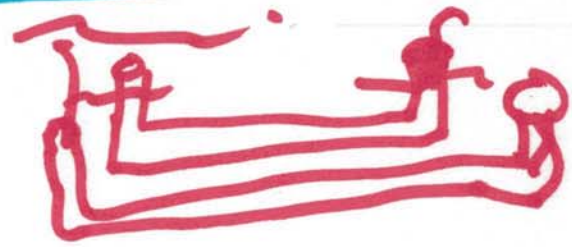
jump  
+ +  
 $I_{sc}$   
- -  
 $V_{oc}$



$$I_{sc} = -3\text{mA}$$

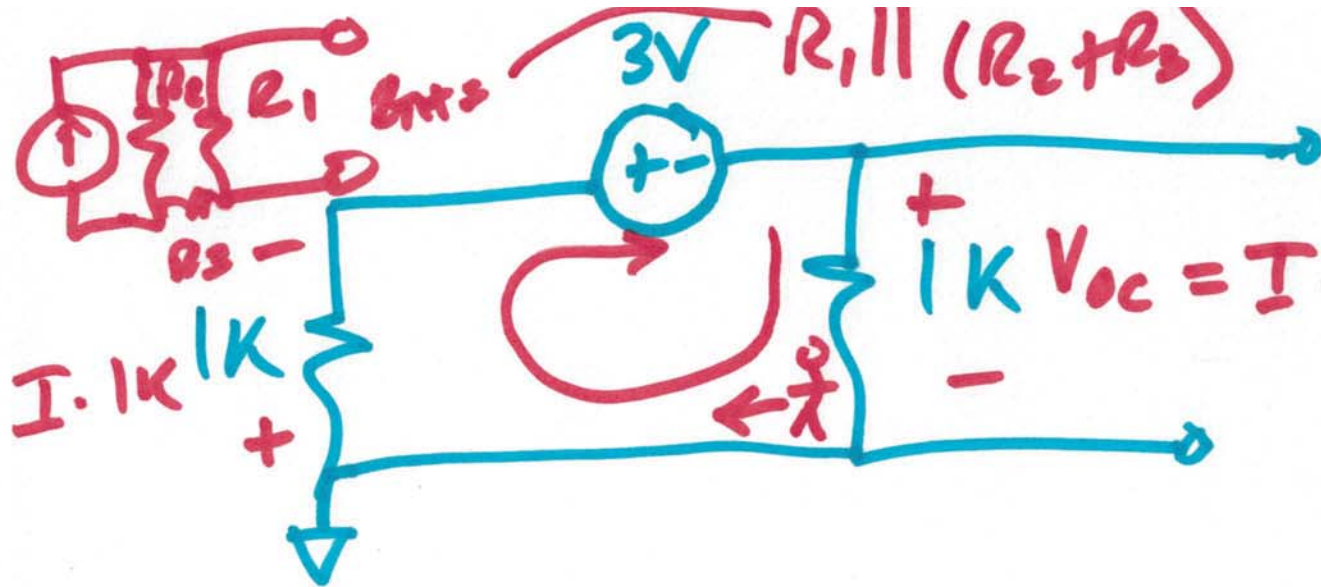
$$V_{oc} = 500 \cdot -3\text{mA} = -1.5\text{V} = V_{TH}$$






$$500 - I \cdot 1k - 3 - I \cdot 1k = 0$$

$$I = -1.5 \mu A$$

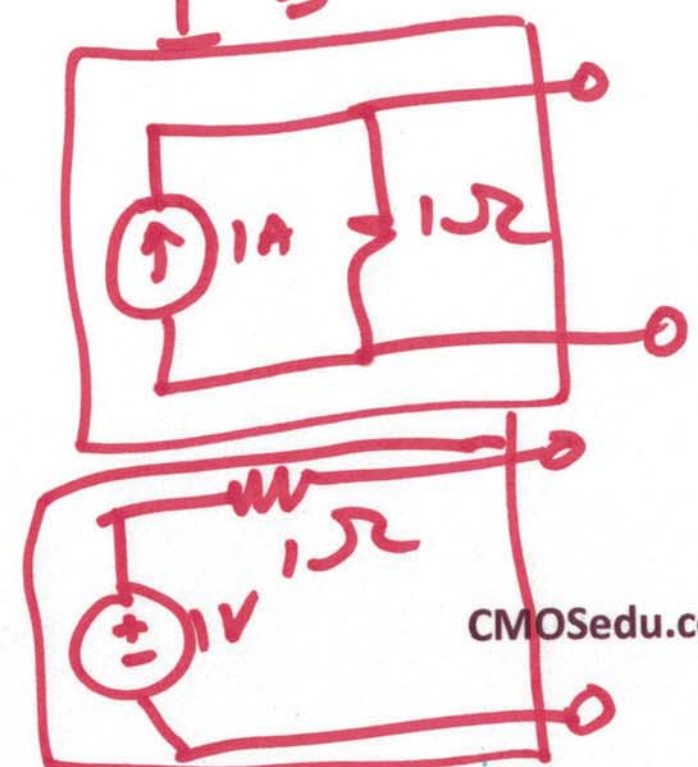


2)



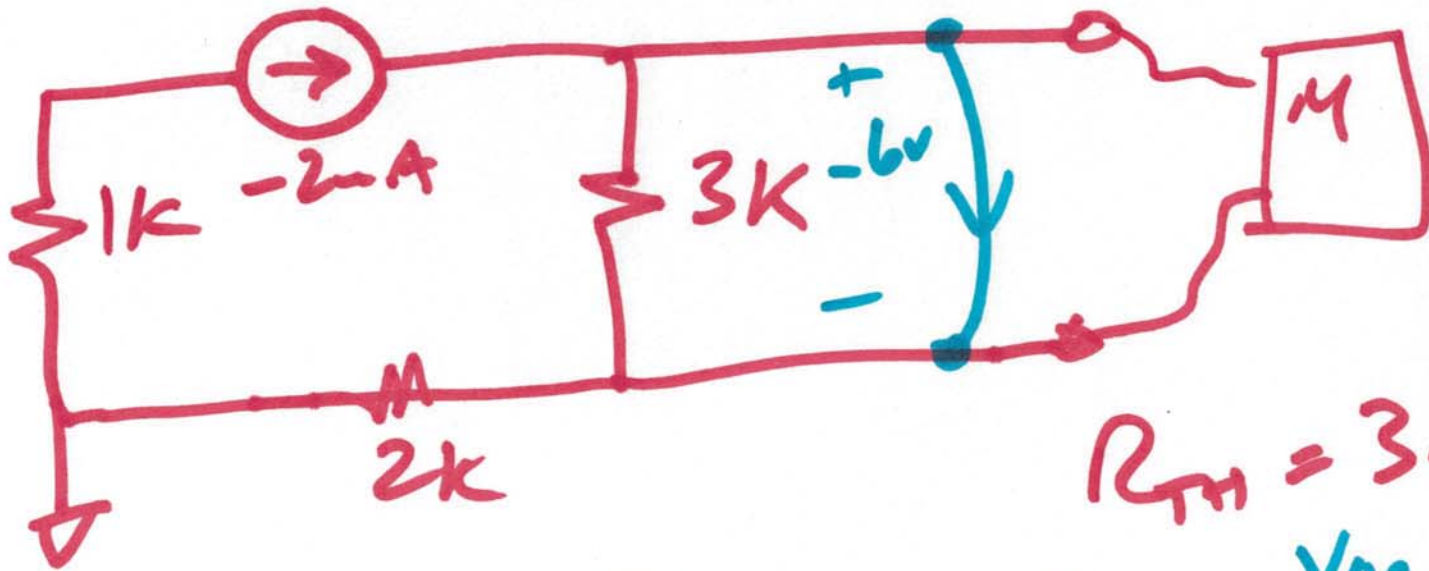

$$R_{TH} = 3k$$

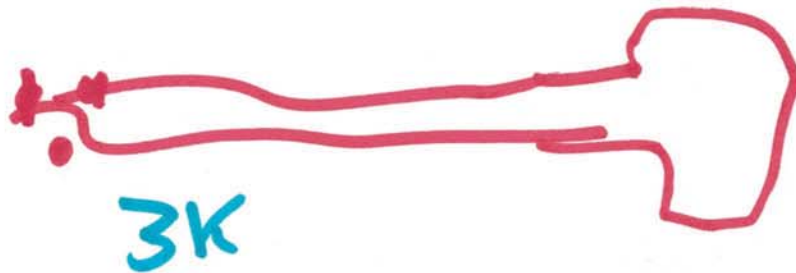
$$R_{TH} = \frac{V_{OC}}{I_{SC}} = \frac{V_{TH}}{I_{TH}}$$




$$I_{SC} = -2mA$$

$$V_{OC} = -6V$$

$$R_{TH} = \frac{-6}{-2mA} = 3k$$

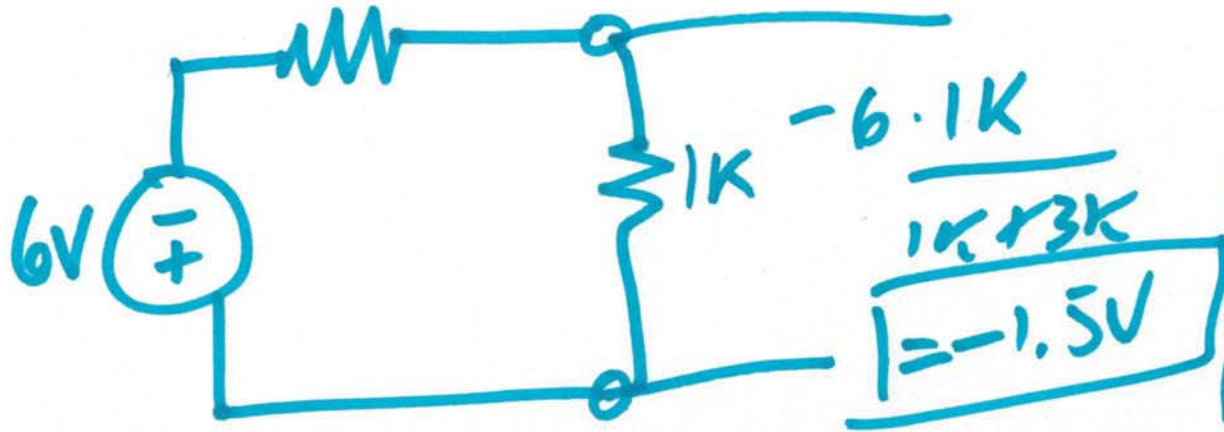


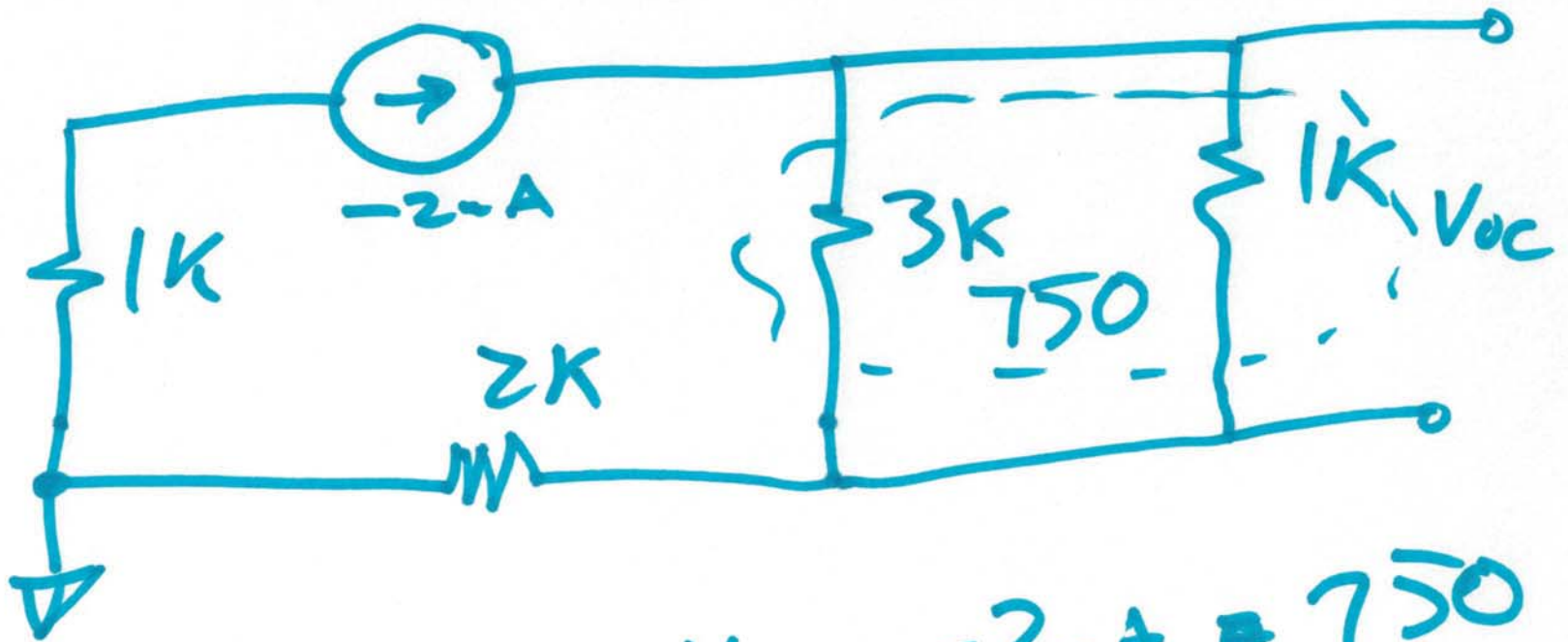

$$V_{oc} = -2\text{A} \cdot 750 = -1.5\text{V}$$




$$s = j\omega$$

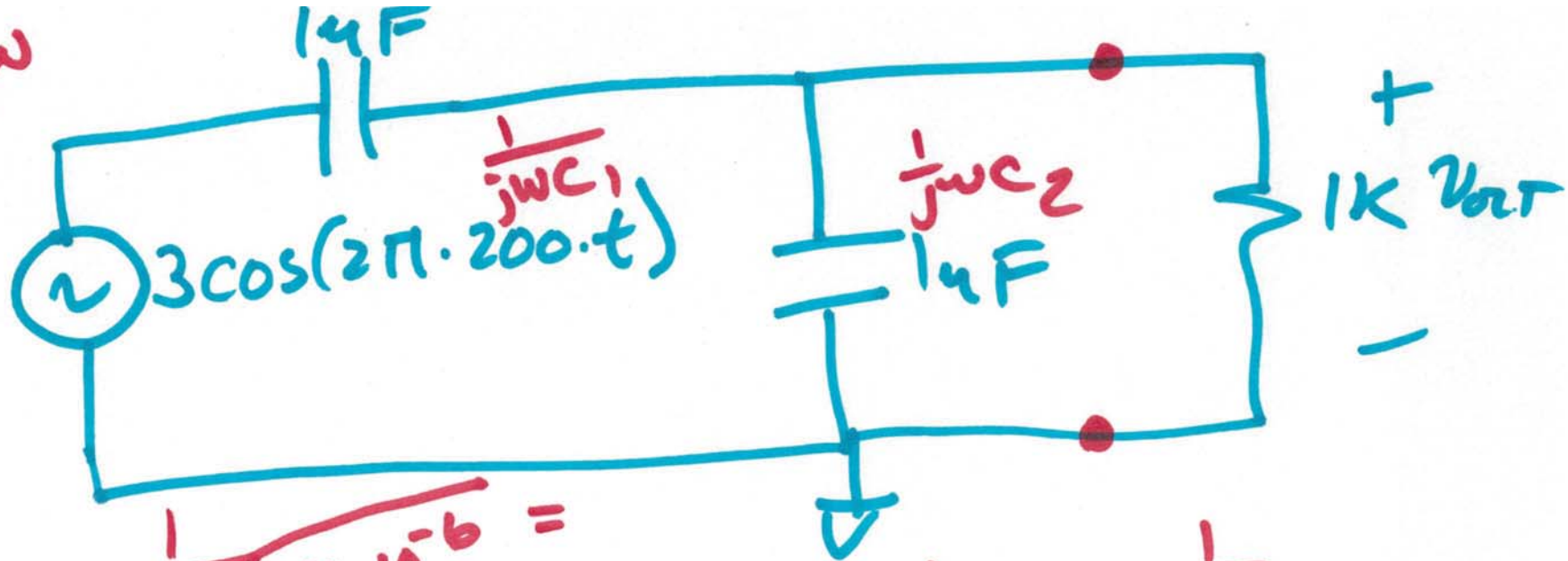


$$\frac{1}{j \cdot 2\pi \cdot 200 \cdot 10^{-6}} =$$
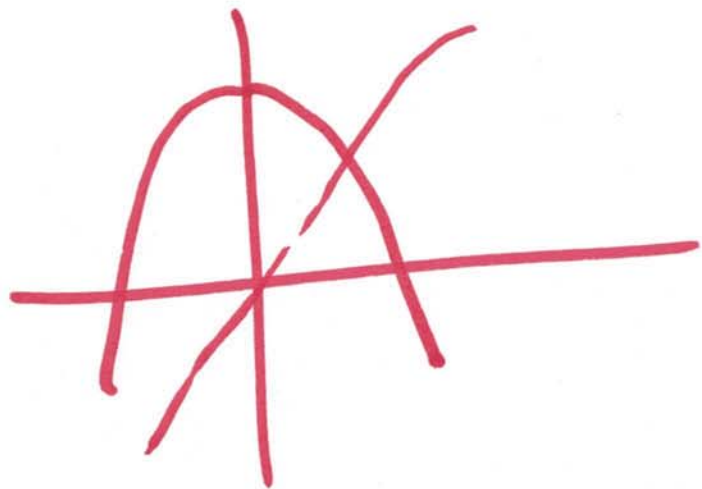
$$\begin{aligned} Z_{TH} &= \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} \\ &= -j(796 + 796) \\ Z_{TH} &= -j1,592 \end{aligned}$$





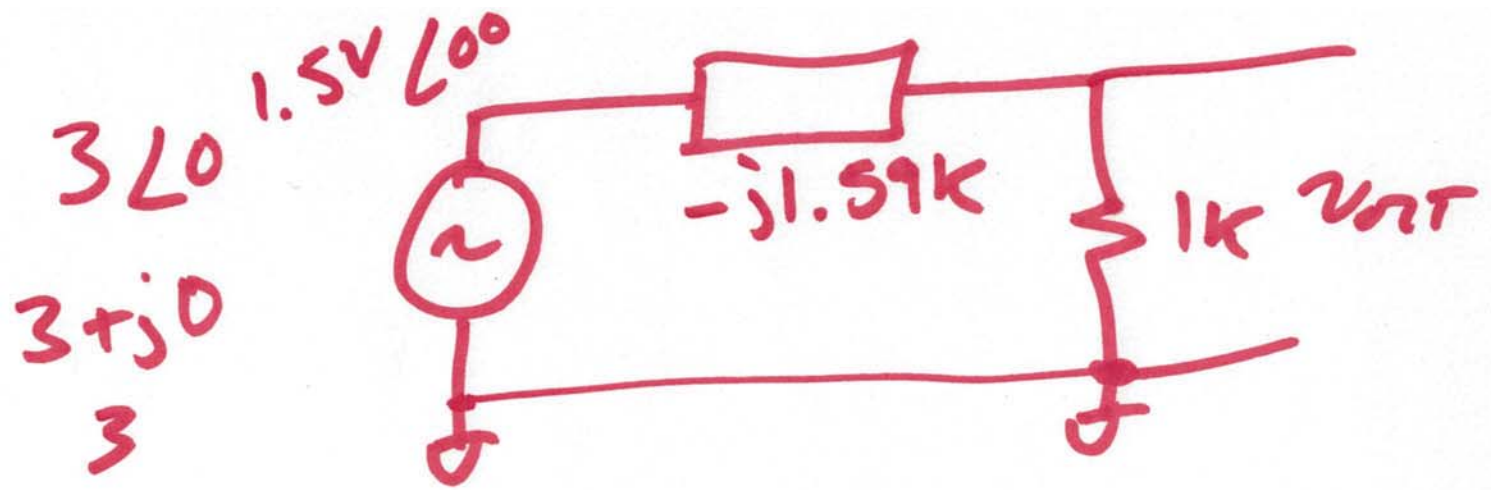

$$\frac{3 \angle 0}{3 + j0}$$

$$T = 5 \mu s$$

$$f = 200 \text{ kHz}$$

$$V_{out} =$$

$$\frac{3 \angle 0 \cdot 1k}{1k + j(-1.59k)}$$

$$\frac{3,000 \angle 0^\circ}{1.88k \angle -58^\circ}$$

$$1.6 \angle -1.14 \text{ rad}$$

$$\frac{t_d}{T} \cdot 360 = 58$$

$$t_d = \frac{58 \cdot 5 \mu s}{360}$$

$$= 6.8 \mu s$$

$$V_{out} = 1.6 \angle 58^\circ$$

$$V_{out} = 1.6 \cos(2\pi \cdot 200 \cdot t + 58)$$

6)