
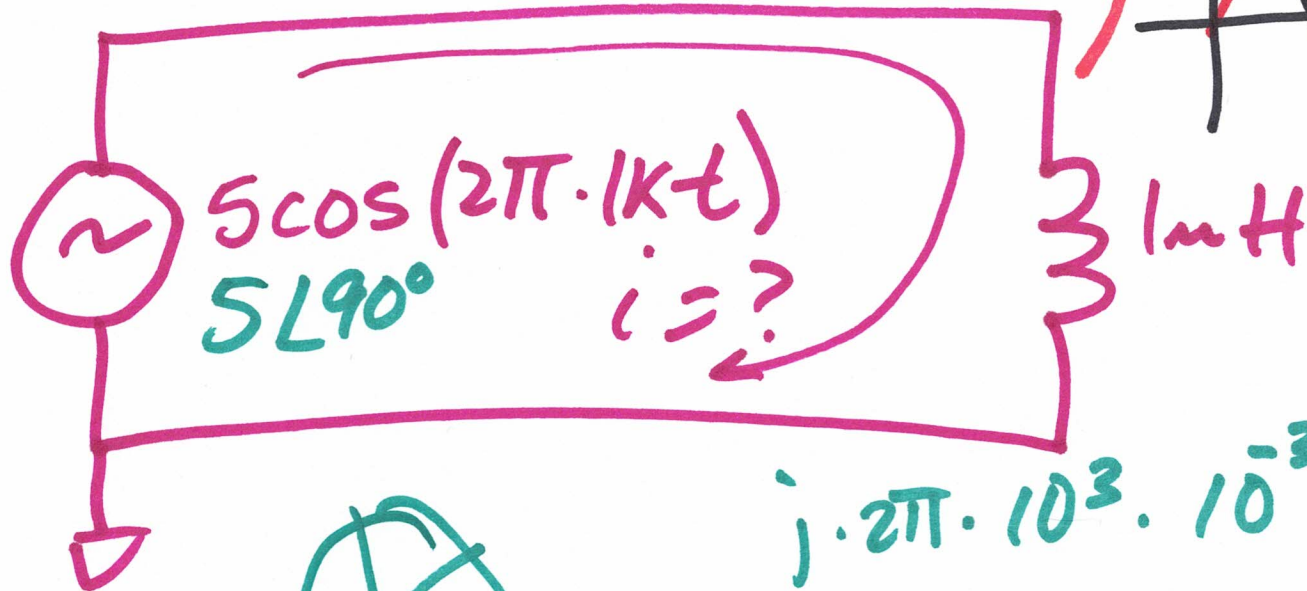
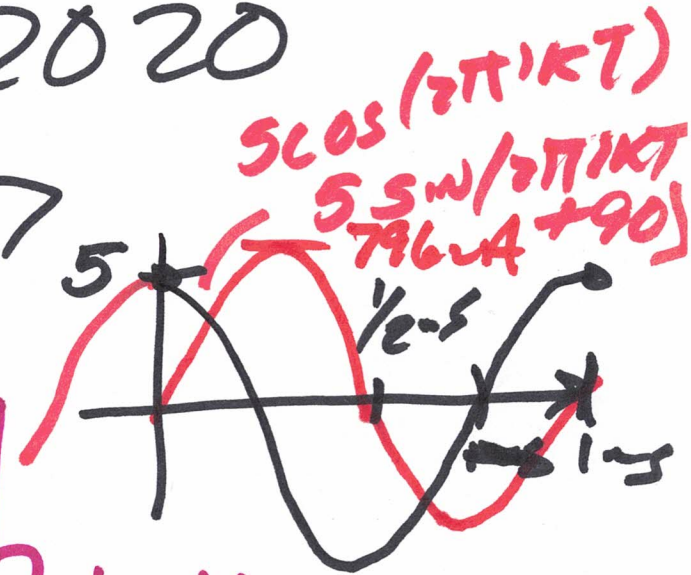


# EE 221 Circuits II


Feb. 12, 2020

## Lecture 7

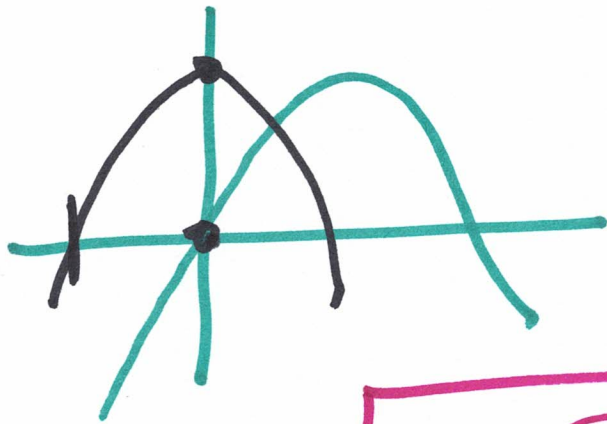

$$j \cdot 2\pi \cdot 10^3 \cdot 10^{-3} = j6.28$$


$$f = 1 \text{ kHz}, T = 1 \text{ ms}$$

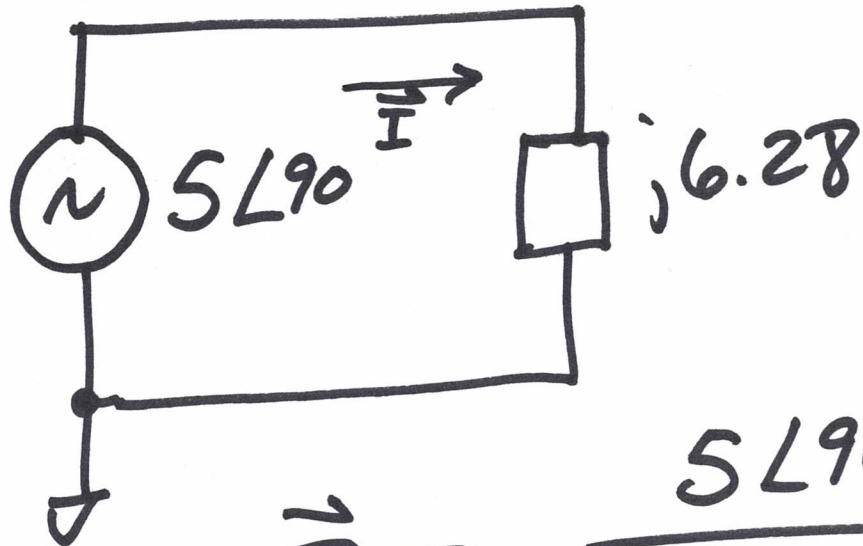

796 A

$$\vec{I} = \frac{5 L90}{6.28 L90} = 796 \text{ mA } \angle 0^\circ$$
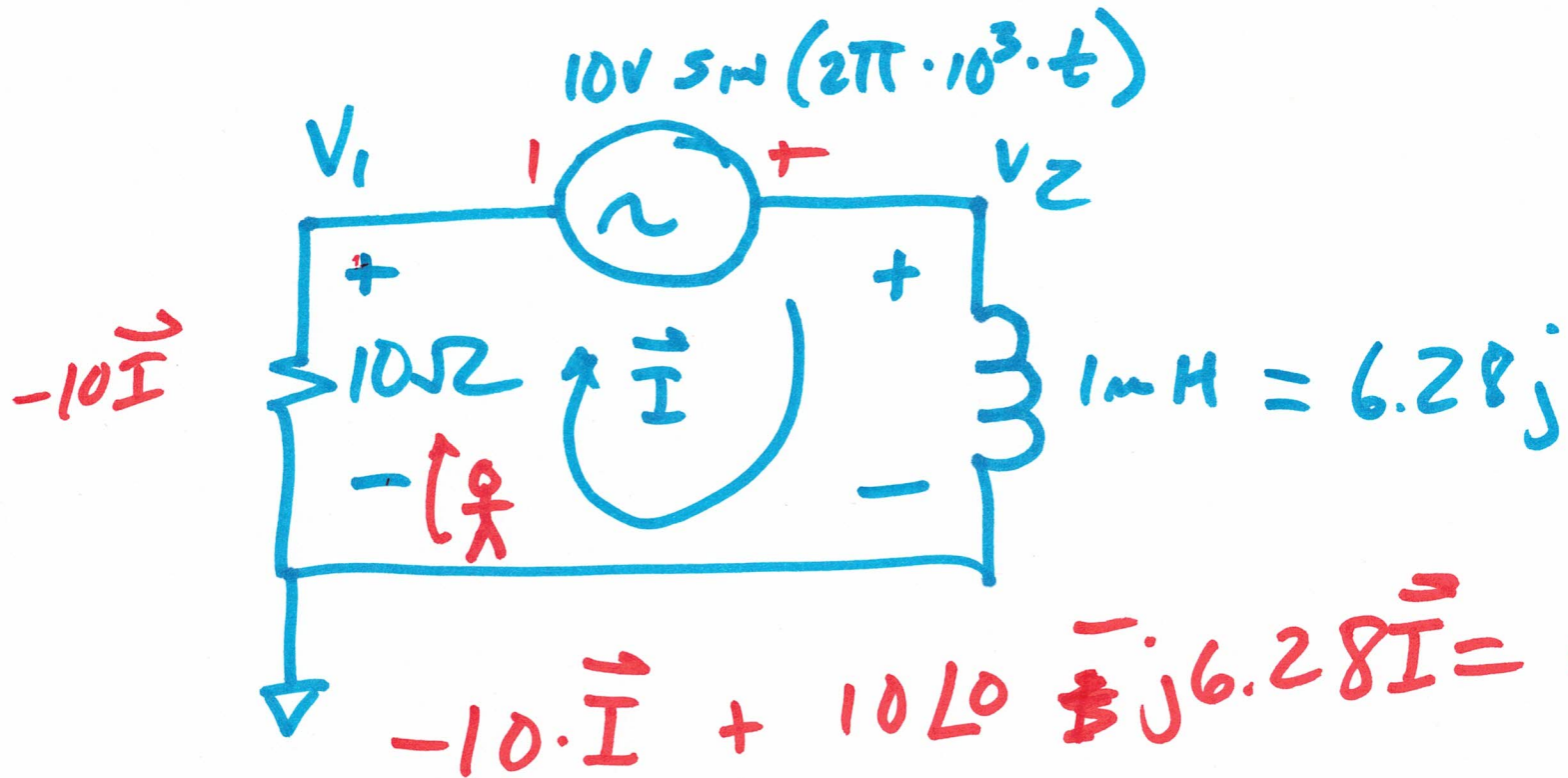
$$i(t) = 796 \text{ mA } \sin(2\pi \cdot 1 \text{ kHz} \cdot t)$$



$$\vec{I}(-10 - j6.28) + 10 \angle 0 = 0$$

$$10 \angle 0 = \vec{I} (10 + j6.28)$$

$$10 \angle 0 = \vec{I} \cdot 11.8 \angle 32.1^\circ$$

$$\vec{I} = \frac{10}{11.8} \angle -32.1^\circ$$


$$\vec{I} = .85 \angle -32.1^\circ$$

$$i(t) = 850 \text{mA} \sin(2\pi \cdot 10^3 \cdot t - 32^\circ)$$

884s

$$\frac{32}{360} \cdot 1 - s$$

3)

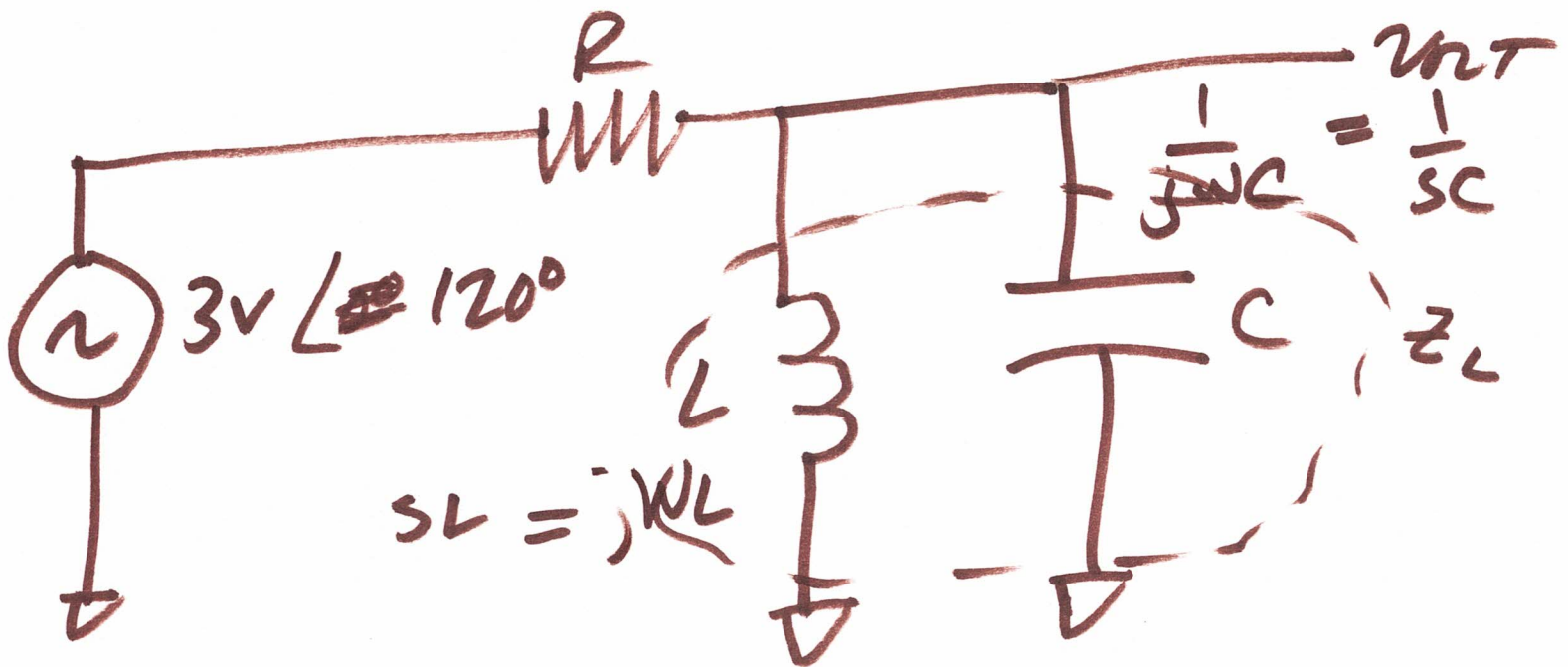

$$V_{out} = 3 \angle 120 \cdot \frac{z_L}{z_L + R}$$

$$z_L = \frac{sL \cdot \frac{1}{sC}}{sL + \frac{1}{sC}} = \frac{sL}{1 + s^2 LC}$$



$$V_{out} = 3L\omega \cdot \frac{sL}{1+s^2LC}$$


$$\frac{sL}{1+s^2LC} + R \quad j\omega L$$

$$= \frac{3L\omega \cdot sL}{sL + R + s^2LCR}$$


$$s_{1,2} = \frac{-L \pm \sqrt{L^2 - 4 \cdot LCR \cdot R}}{2 \cdot LCR}$$

$$= \frac{3L\omega \cdot \omega L \angle 90^\circ}{(s + s_1)(s - s_2)}$$

5)

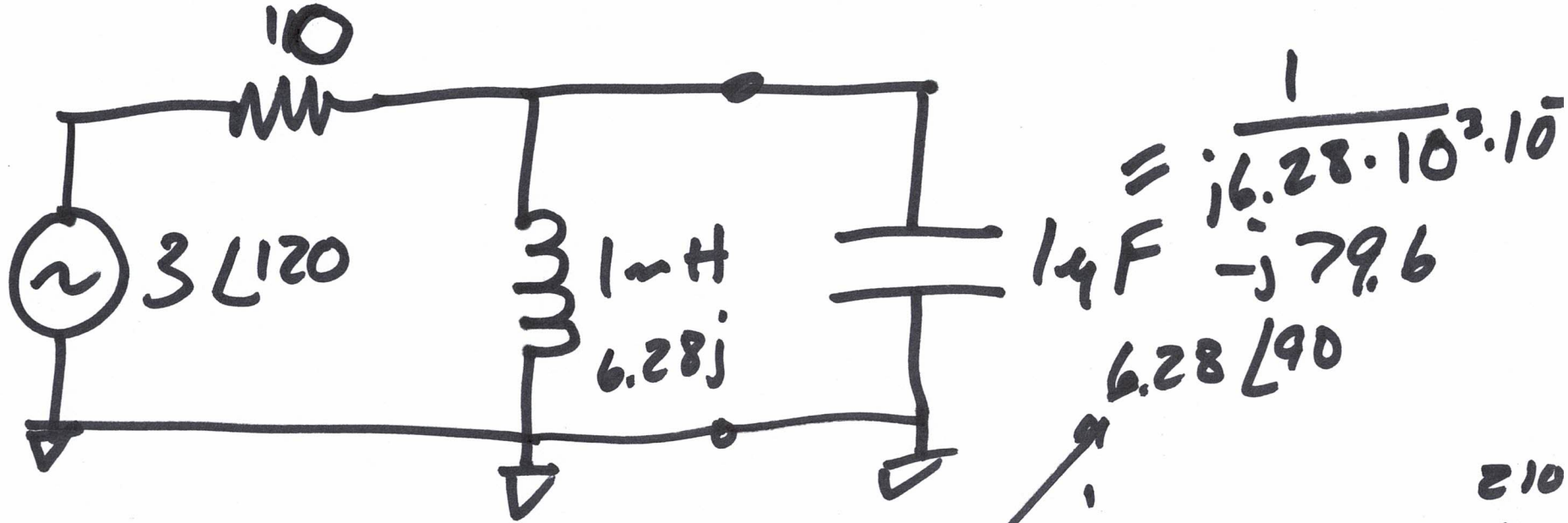
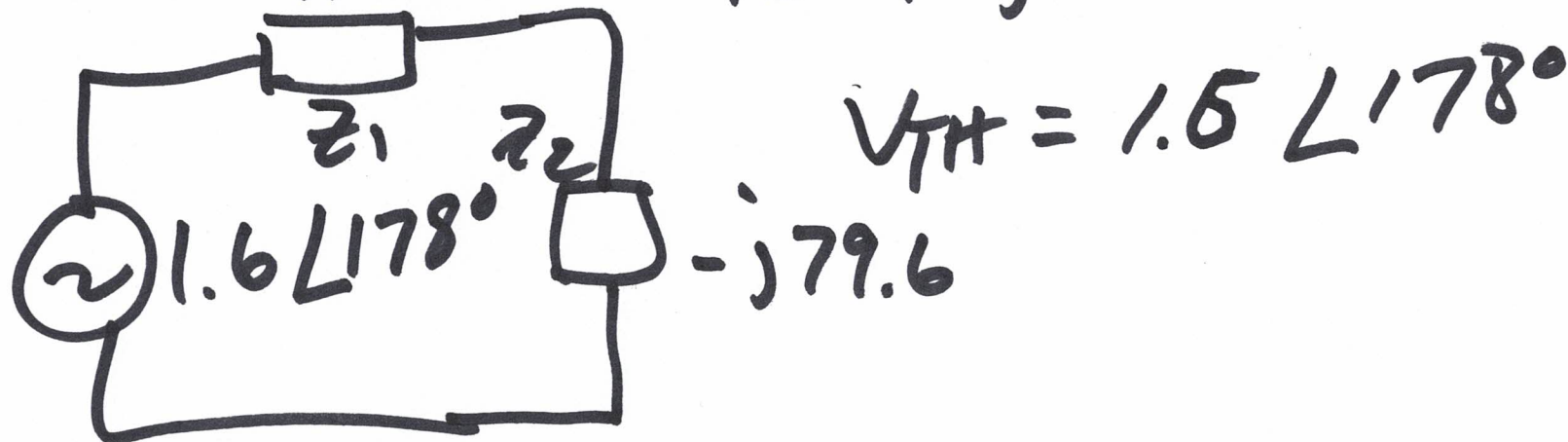
$$V_{oc} = V_{TH} = \frac{3 \angle 120 \cdot 6.28j}{10 + j6.28} = \frac{18.84 \angle 101.3}{11.8 \angle 32.0}$$



6)

$$V_{NT} = 1.6 \angle 178 \cdot \frac{z_2}{z_1 + z_2}$$

$$z_2 = 10 \parallel j6.28$$

$$= \frac{10 \cdot j6.28}{10 + j6.28} = \frac{j62.8}{10}$$

62.8  $\angle 90$   
↓  
j62.8  
10