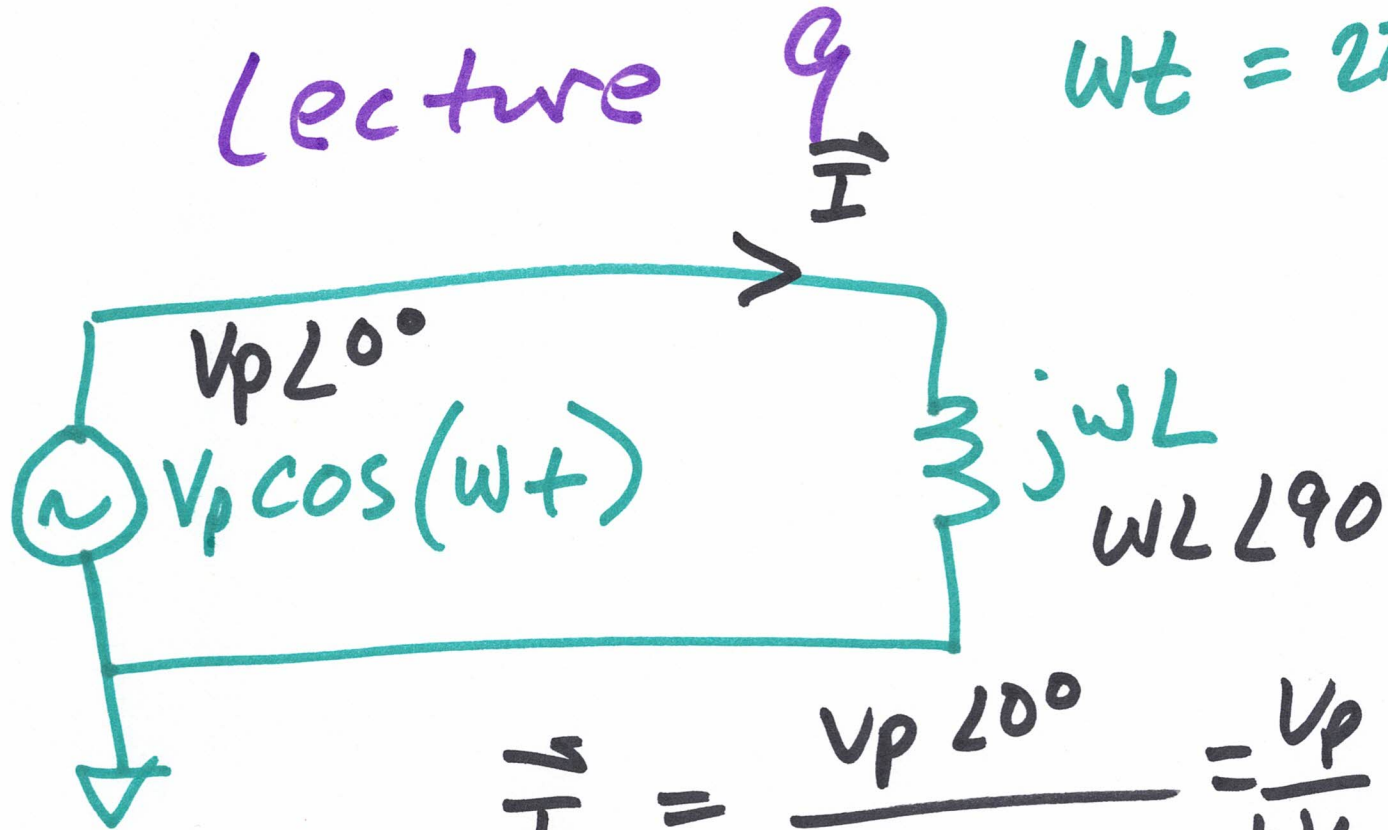


# EE 221 circuits II

Feb. 24, 2020

Lecture 9  $\omega t = 2\pi f \cdot t$




$$I = \frac{V_p \angle 0^\circ}{\omega L \angle 90} = \frac{V_p}{\omega L} \angle -90$$

1)

$$\theta_V + \theta_I = -90^\circ$$

$$I_p \cos(\omega t + \theta_I)$$

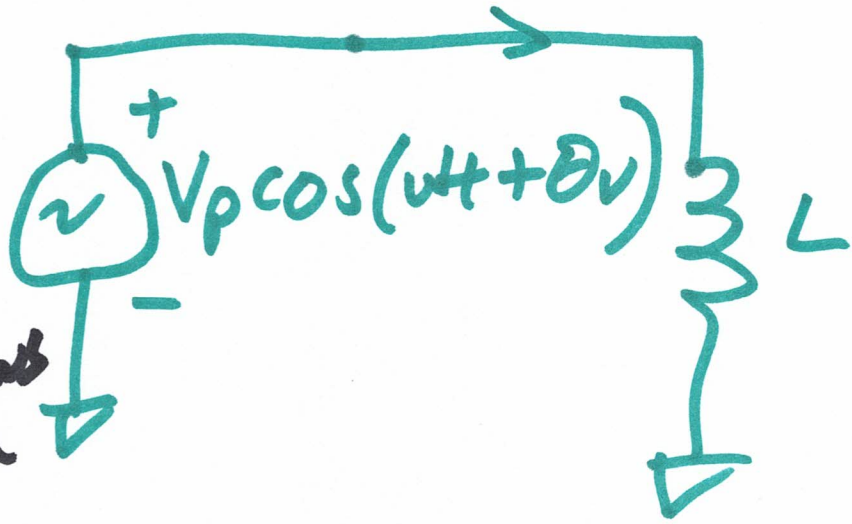

instantaneous power


$$P(t) = v(t) \cdot i(t) = V_p I_p \cos(\omega t + \theta_V) \cdot \cos(\omega t + \theta_I)$$

$$\cos a \cdot \cos b = \frac{1}{2} (\cos(a+b) + \cos(a-b))$$

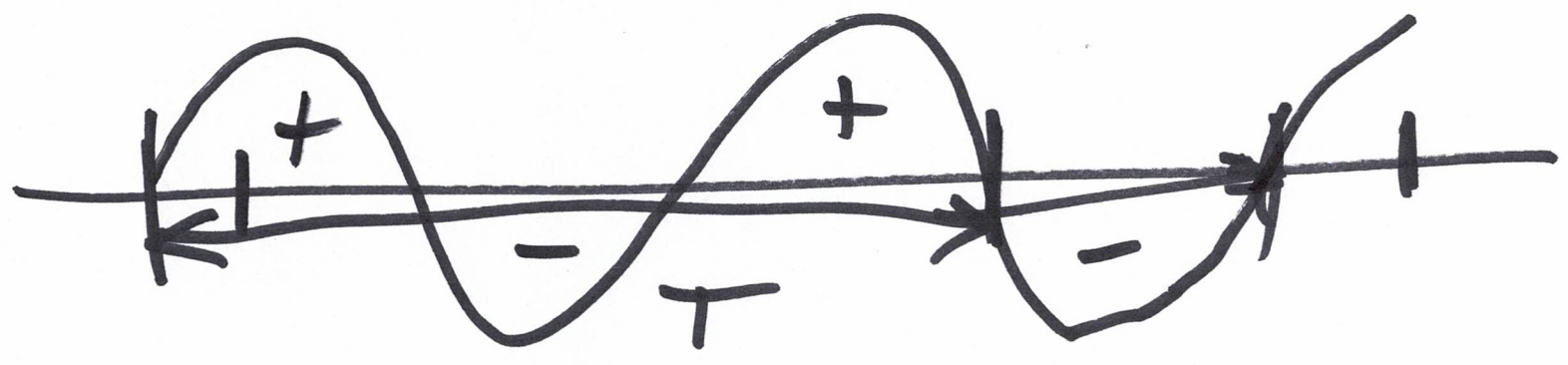2)


$$p(t) = \frac{V_p I_p}{2} \left( \overset{\omega}{\cos(2\omega t + \theta_V + \theta_I)} + \cos(\omega t - \omega t + \theta_V - \theta_I) \right)$$

$$P_{AVG} = \frac{1}{T} \int_{t_0}^{t_0+T} p(t) \cdot dt = \frac{1}{T} \int_{t_0}^{t_0+T} P(t) \cdot dt$$



3)

$$V_{pp} = 2V_p = 2\sqrt{2} V_{Rms}$$

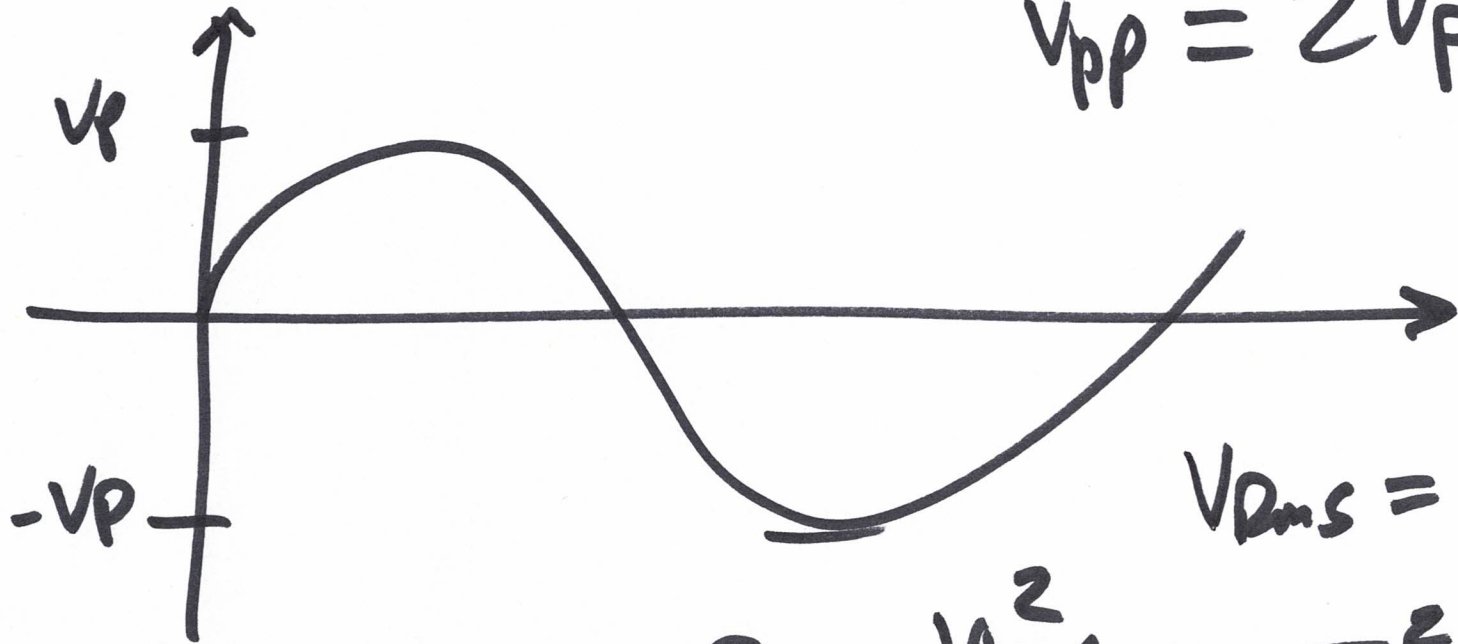

$$V_{Rms} = \frac{V_p}{\sqrt{2}}$$


$$P_R = \frac{V_{Rms}^2}{R} = I_{Rms}^2 \cdot R$$

$$= V_{Rms} \cdot I_{Rms}$$

ONLY for resistors!



$V_{Rms} = V_{AC}$

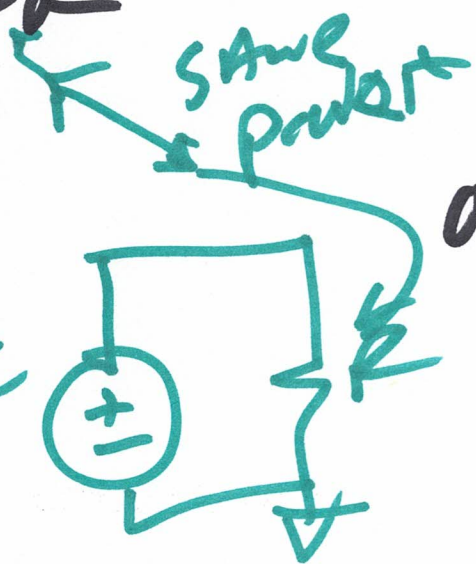



4)

$$P_{AVG} = \frac{1}{T} \frac{V_p I_p}{2} \int_0^T \cos(\theta_V - \theta_I) dt$$

$$= \frac{V_p I_p}{2} \cos(\theta_V - \theta_I) \cdot \frac{1}{T} \int_0^T dt$$

$$P_{AVG} = \frac{V_p I_p}{2} \underbrace{\cos(\theta_V - \theta_I)}_{\text{p.f.}}$$

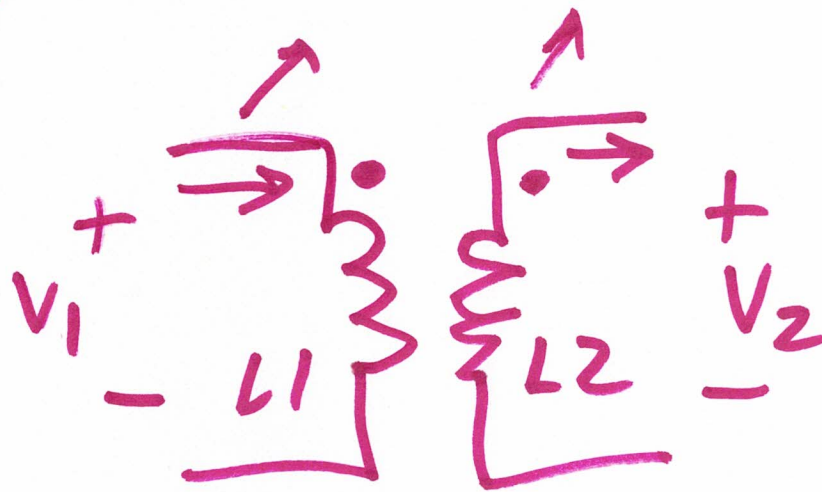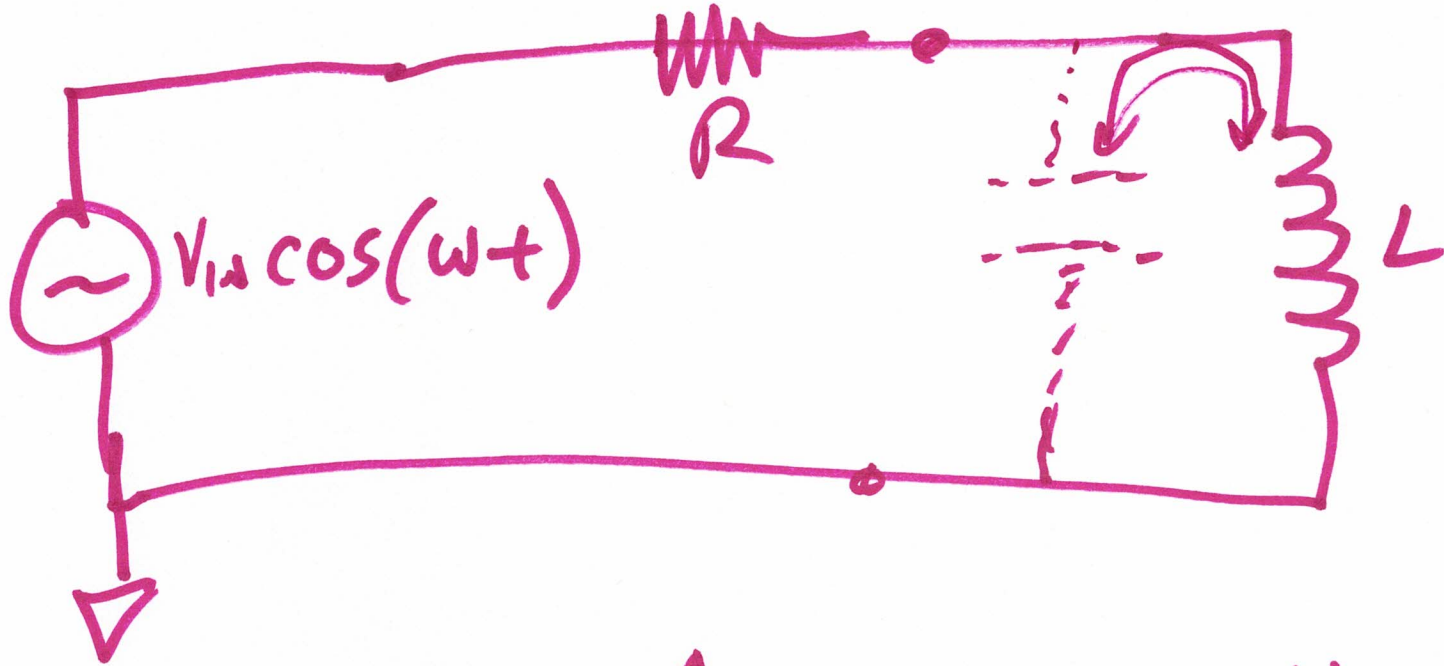
for ~~resistive~~ resistive loads  
 p.f. = 1



$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \sqrt{\frac{L_1}{L_2}}$$


$$\frac{V_1}{I_1} = \frac{V_2}{I_2} \cdot \frac{N_1^2}{N_2^2}$$
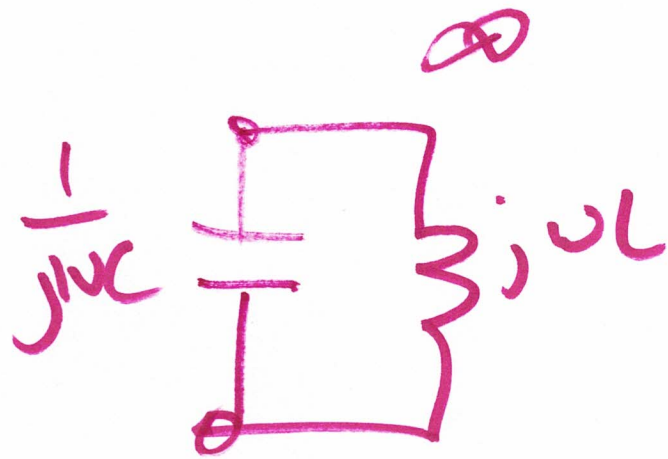
$$= \frac{L_1}{L_2} \cdot \frac{V_2}{I_2}$$



$$|S| = \frac{1}{\sqrt{LC}}$$

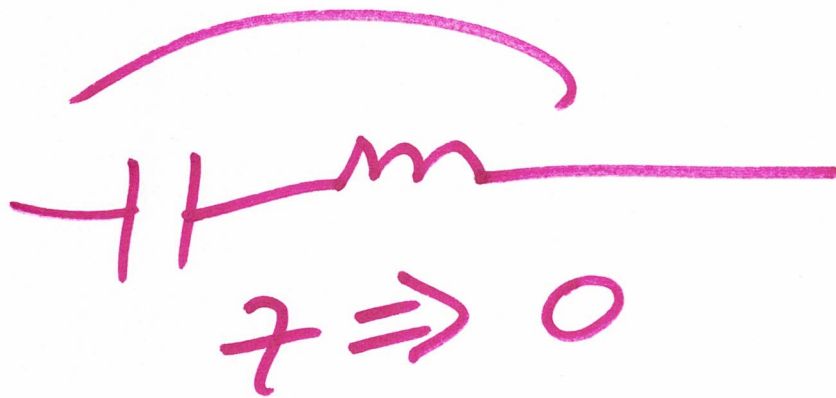~~$$\frac{j\omega L}{sL + \frac{1}{sC}}$$~~



$$z \Rightarrow 0$$